
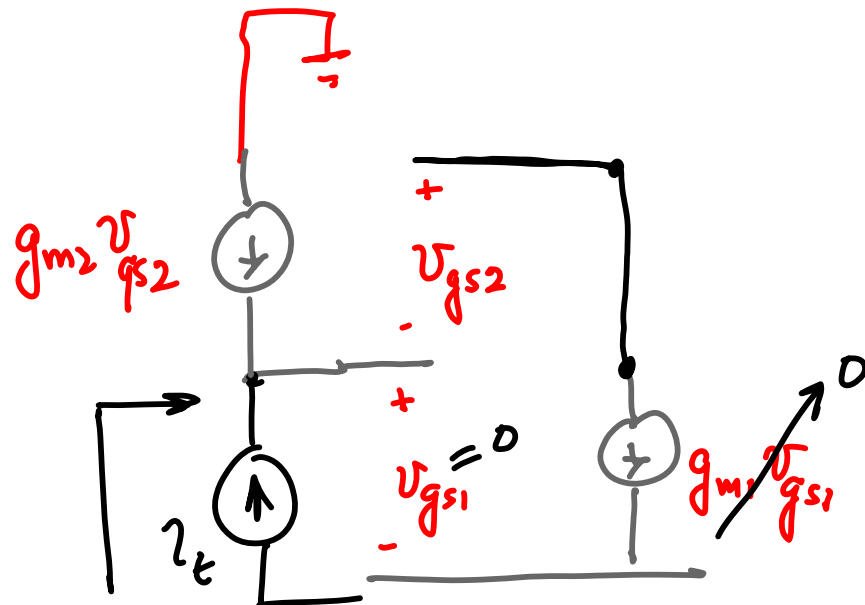




HW #3: Q4(c)

522 (F07) 2b

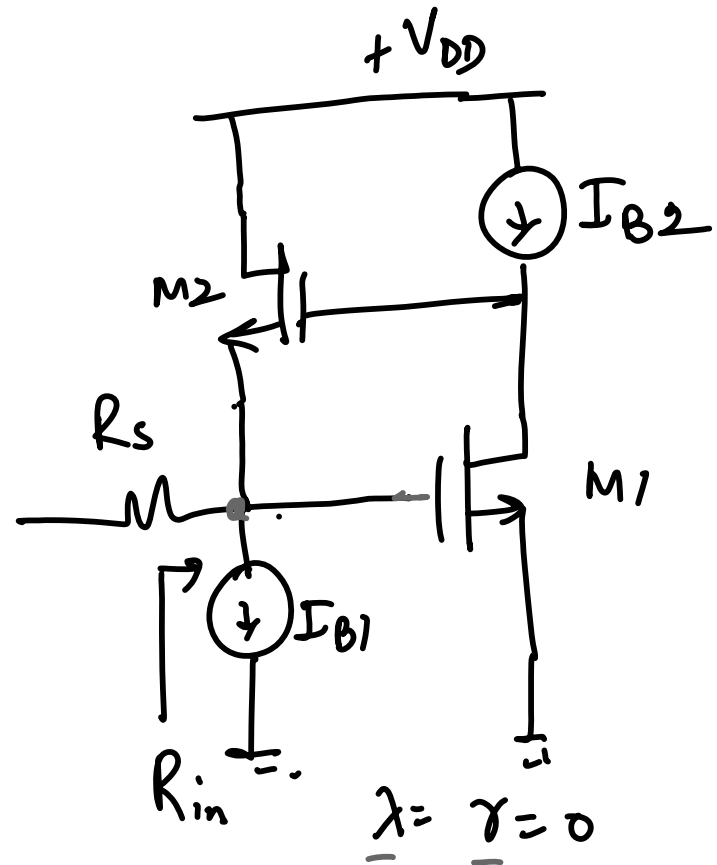

$R_{in} = 0$



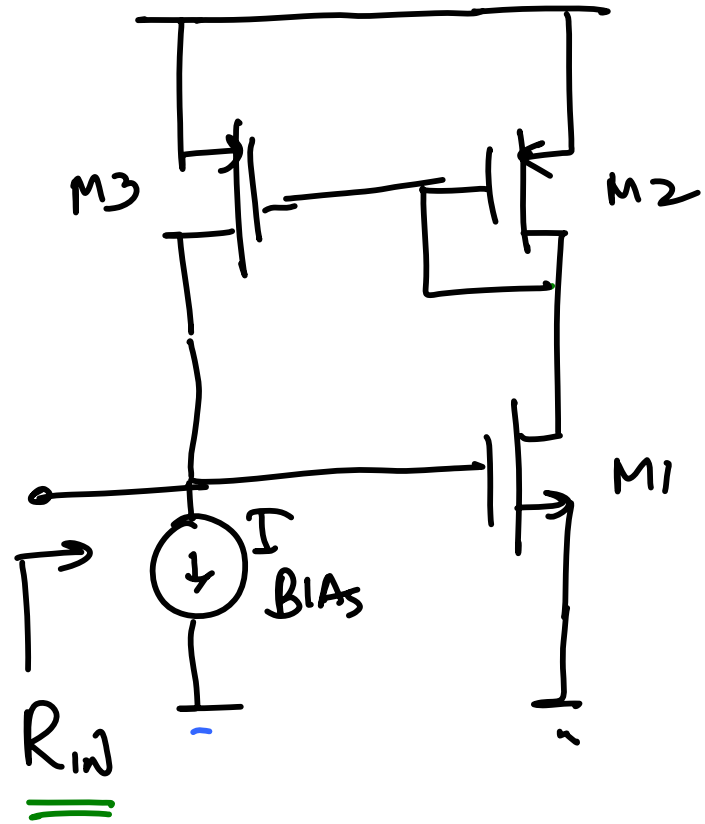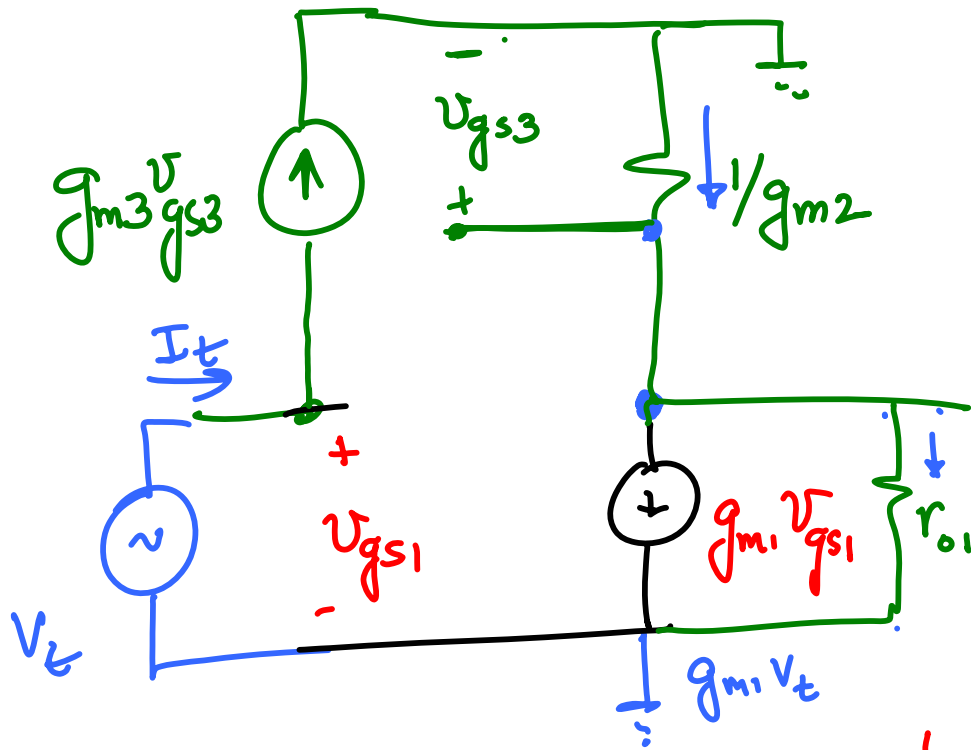

$$I_t = g_{m3} v_{gs3}$$

$$= -g_m v_t$$

$$R_{in} = v_t / I_t = -\frac{1}{g_m} g_{m1} v_t + \frac{v_{gs3}}{r_{o1}} + v_{gs3} \cdot g_{m2} = 0$$



$$g_{m1} v_t + g_{m2} v_{gs3} = 0$$

$$v_{gs3} = -v_t + \left(\frac{1}{r_{o1}} + g_{m2} \right) v_{gs3}$$

$A_v \rightarrow A_{dm}, A_{cm}$



Half circuit analysis

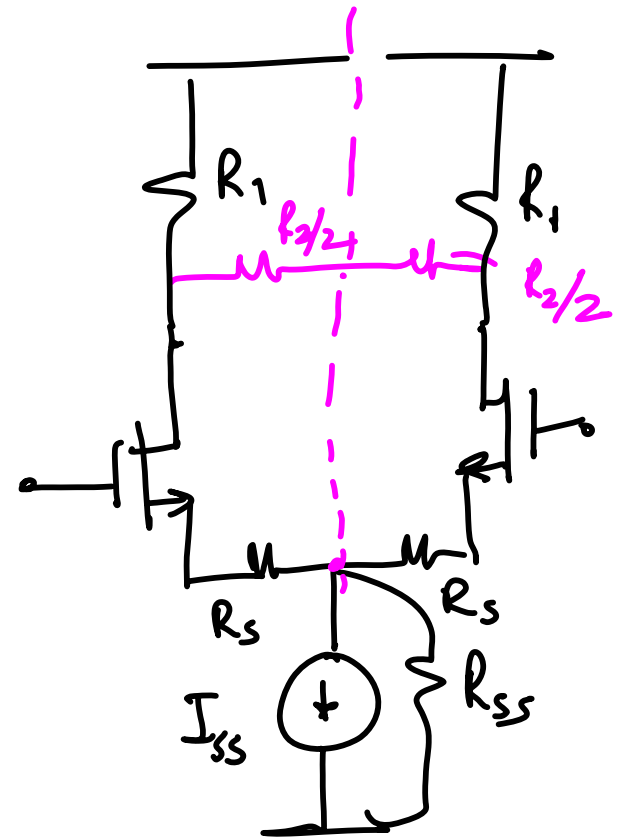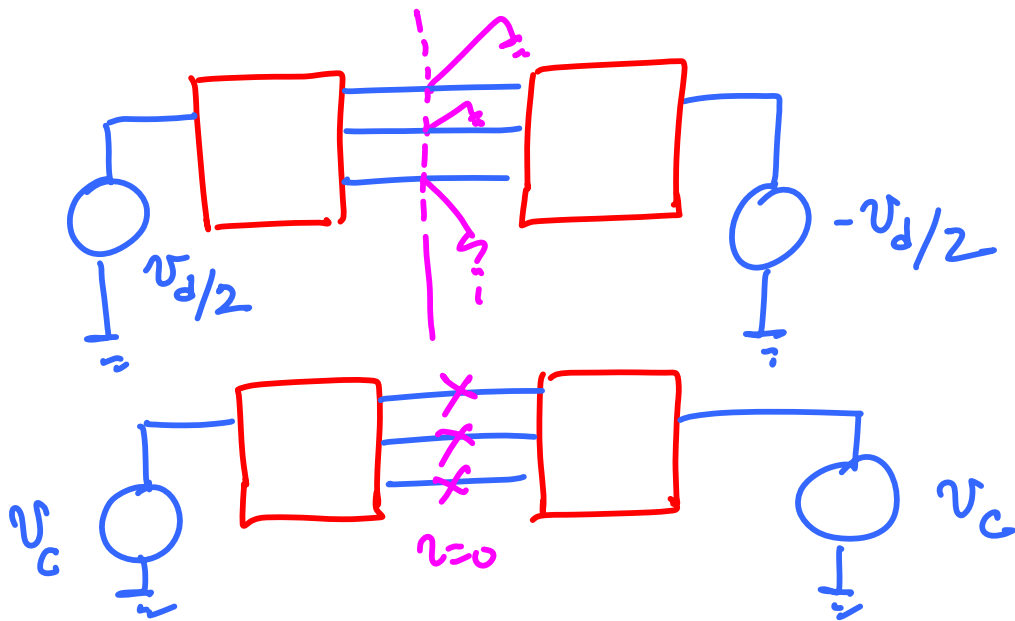1. Circuit must be symmetrical
2. Depending on the signal type



$$R_o \parallel R_o$$

$$= \frac{V_t}{I_t}$$

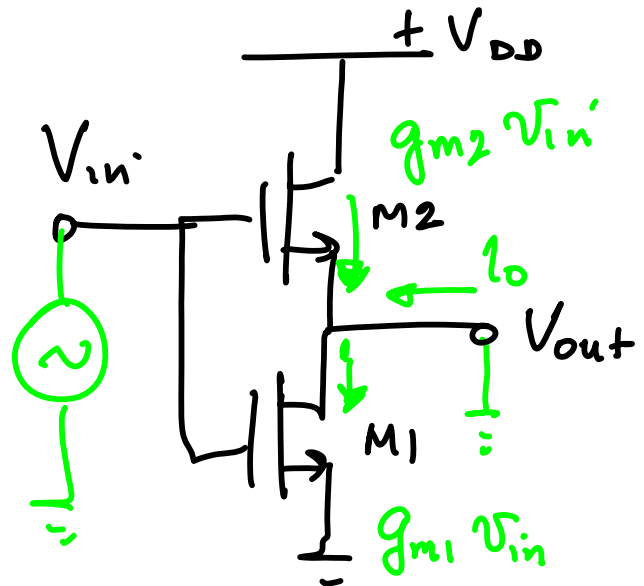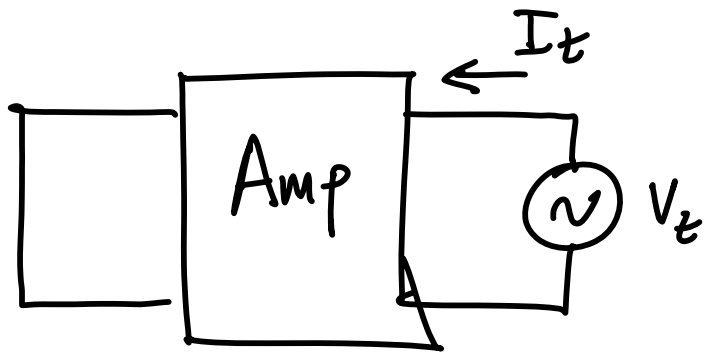


$$r = 0 \quad \lambda \neq 0$$

$$G_m = \frac{I_o}{V_{in}}$$

$$= \frac{g_{m1} V_{in} - g_{m2} V_{in}}{V_{in}}$$



$$= g_{m1} - g_{m2}$$

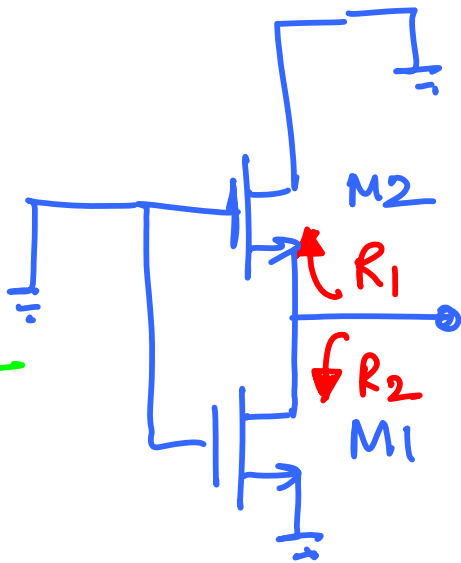

$$R_o = R_1 \parallel R_2$$

$$\frac{1}{g_{m2}} \parallel \parallel r_{o1} \approx \frac{1}{g_{m2}}$$


$$v_{gs1} = v_t$$

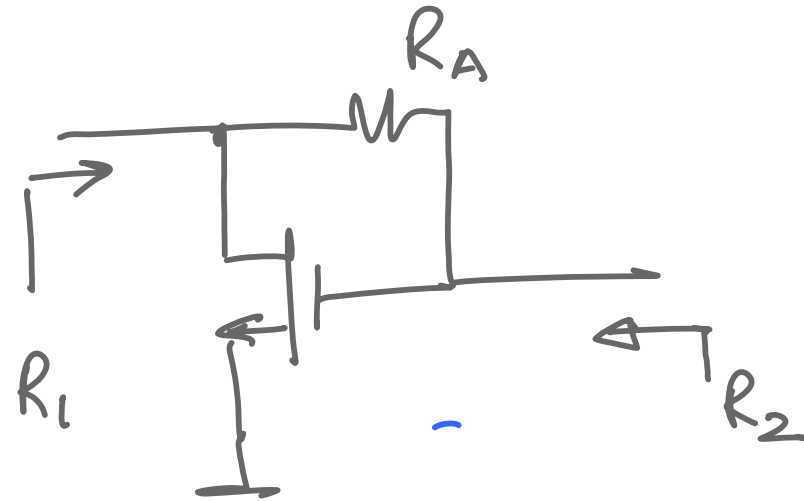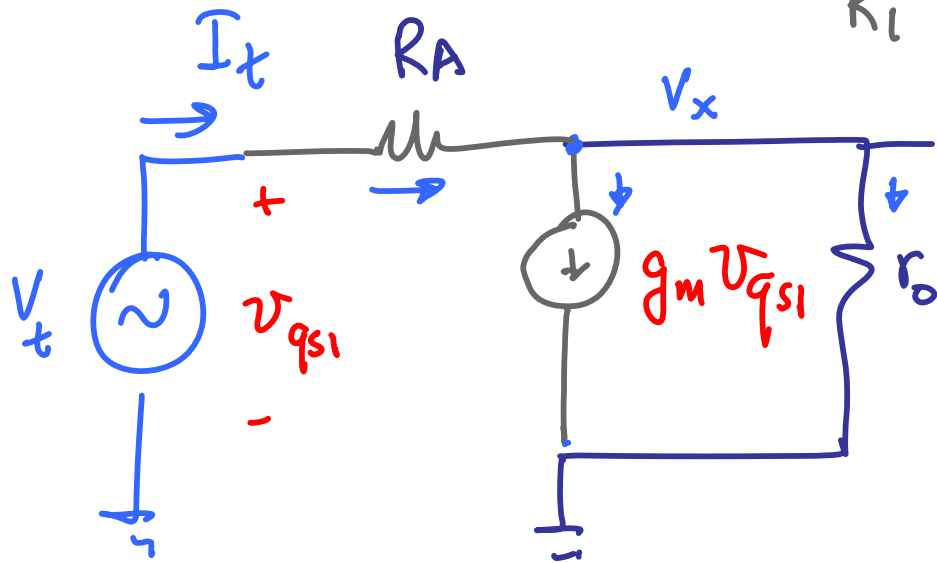

$$I_t = \frac{v_t - v_x}{R_A}$$


$$\frac{v_t - v_x}{R_A} - g_m v_t - \frac{v_x}{r_o} = 0$$

$$R_o = r_o + R_L \quad \text{X}$$

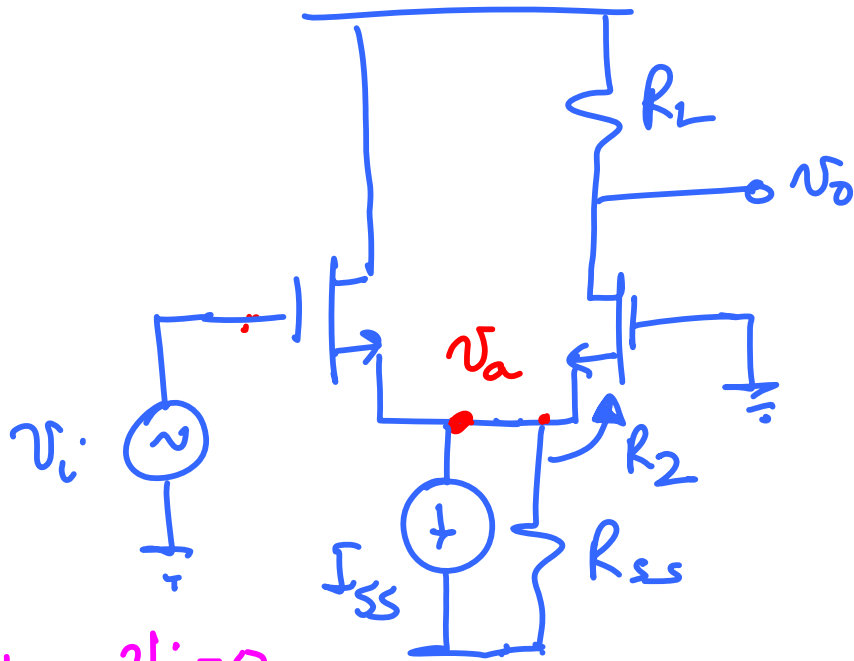



$$v_{id} = v_i - 0$$

$$v_{ic} = v_i / 2$$

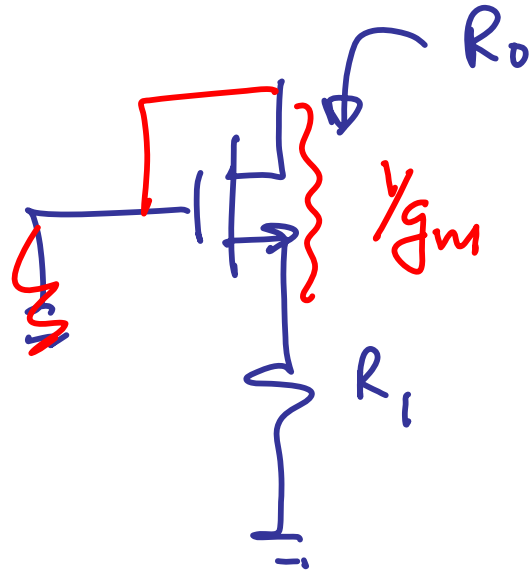

$$A_v = \frac{v_o}{v_i} = \frac{v_o}{v_a} \cdot \frac{v_a}{v_i}$$

$$\frac{v_o}{v_a} = g_m R_L$$

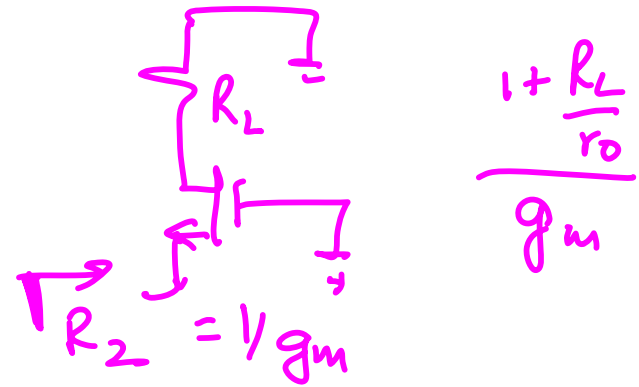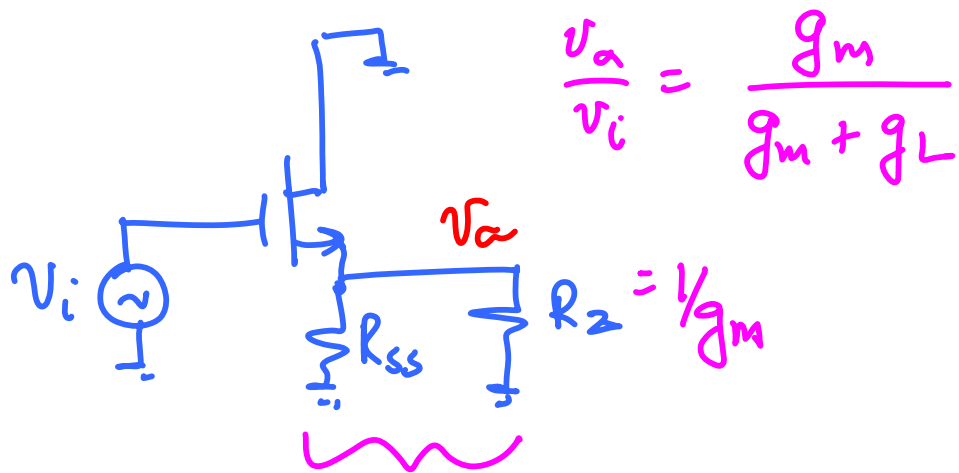

$$R_L = R_{ss} \parallel 1/g_m \rightarrow 1/g_m$$

$$g_L = \frac{1}{R_L} = g_m$$

$$\frac{v_o}{v_i} = \frac{g_m}{g_m + g_m} = \frac{1}{2}$$

$$A_v = \frac{g_m R_L}{2}$$

A_{dm} , A_{cm} are known


$$\frac{v_{od}}{v_{id}} = A_{dm}$$

$$\frac{v_{oc}}{v_{ic}} = A_{cm}$$

$$v_{id} = v_i - 0 = v_i$$

$$v_{ic} = \frac{v_i + 0}{2} = \frac{v_i}{2}$$

$$v_o = -\frac{v_{od}}{2} + v_{oc}$$

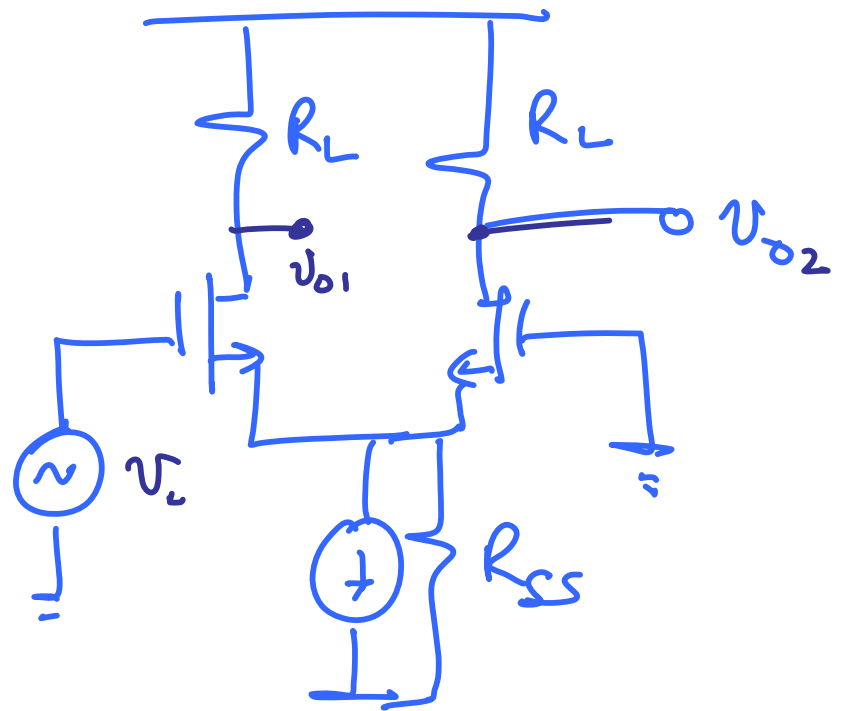

$$v_{o1} = \frac{v_{od}}{2} + v_{oc}$$

$$v_{o2} = -\frac{v_{od}}{2} + v_{oc}$$

$$= -\frac{A_{dm} v_i}{2} + \frac{A_{cm}}{2} \cdot v_i$$

$$= \left(-\frac{A_{dm} + A_{cm}}{2} \right) v_i$$