

$V_{ic\ mini}$ ,  $V_{ic\ max}$

$$V_{ic\ max} = V_{DD} - |V_{GS3}| + V_T$$



$$V_{ic\ min} = V_{GS1} + V_{dsat5} - V_{SS}$$

# of poles in a circuit  
 $\leq$  # of caps in the circuit

ONE POLE




For analysis only

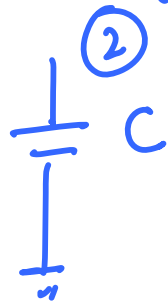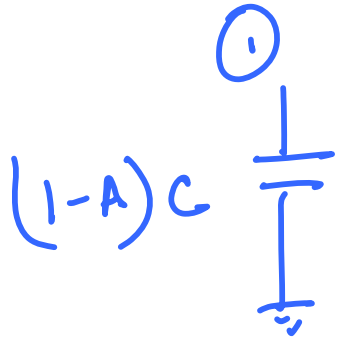

$$\tau = \left( \frac{1}{g_m} \parallel R_s \right) C_1 (1 - g_m R_L) + C_1 R_L$$

$$\omega_p = \frac{1}{\tau}$$

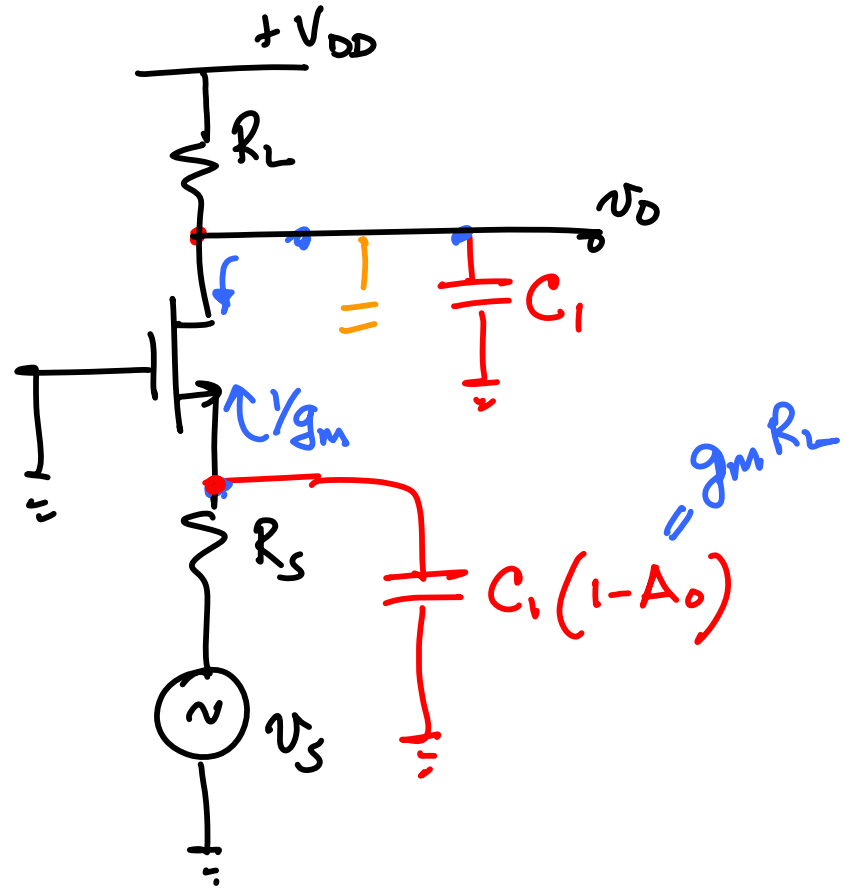


# of poles 2

$$\tau = \left[ C_{gs} + C_{sb} + C_A(1 - g_m R_L) \right] \frac{1}{g_m} \parallel R_s + (C_{gd} + C_{db} + C_A) R_L$$


$$\omega_p = \frac{1}{\tau_1}$$

$$\tau_1 \tau_2 = \frac{R_1 R_2}{\omega} \left[ C_1 C_2 + C_A C_1 + C_A C_2 \right]$$

$$\tau_2 = \frac{\tau_1}{\omega}$$

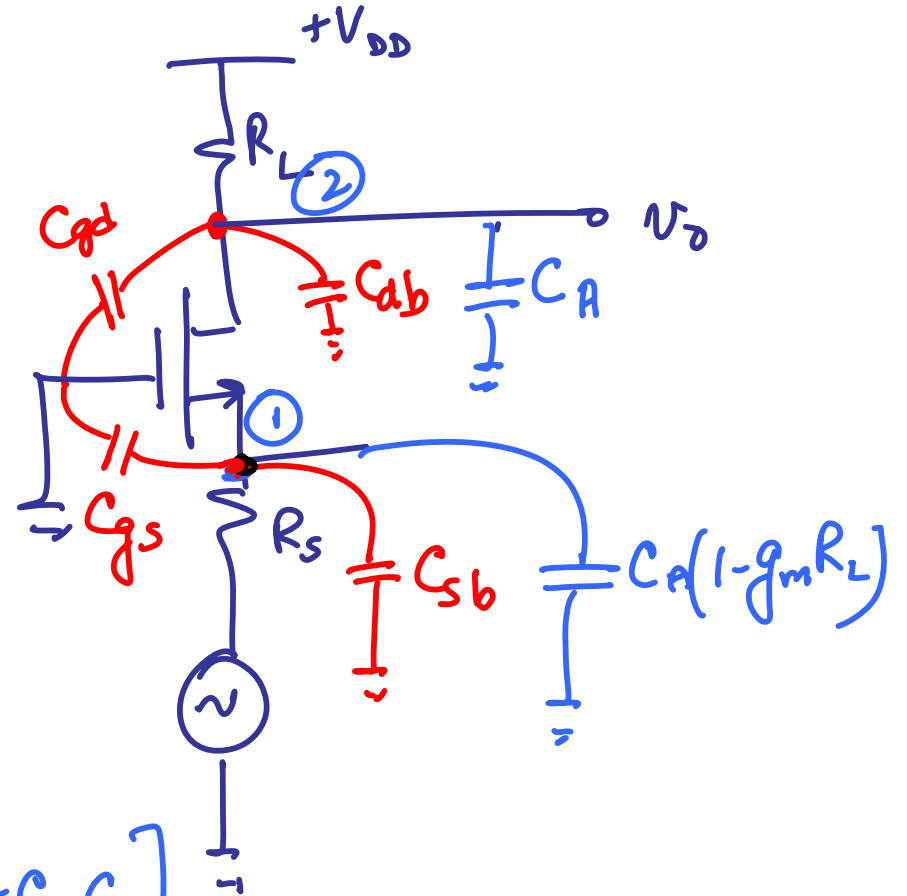


ONE

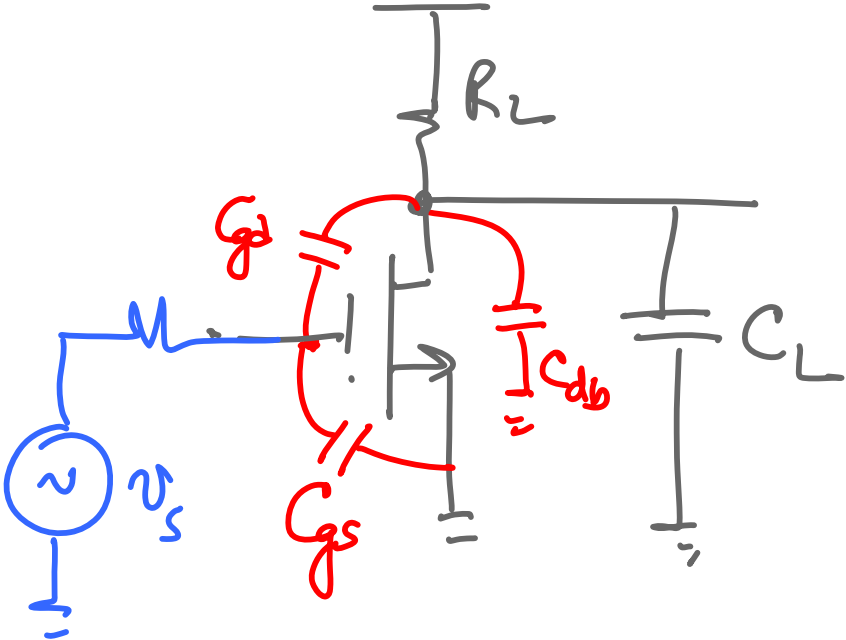

Find  $I_o$ ,  $V_{omin}$   
 $R_{out}$ .

$k' = 100 \mu A/V^2$

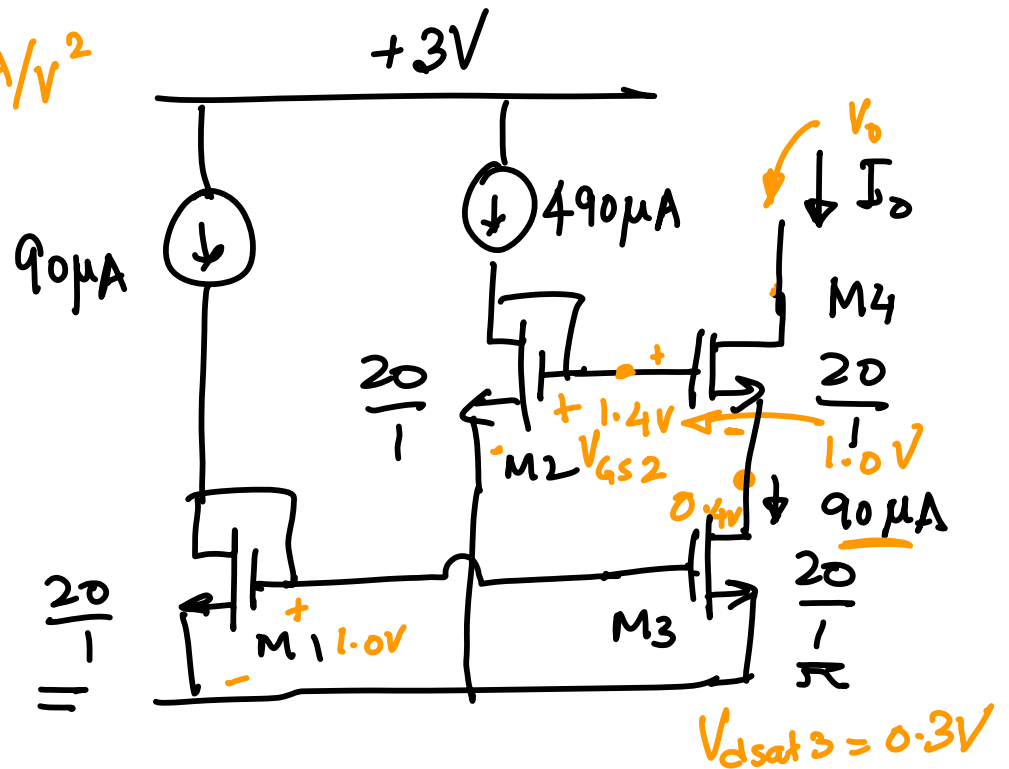$I_o = 90 \mu A$ ,  ~~$490 \mu A$~~   
 ~~$\frac{490 \times 90}{2} \mu A$~~



$R_{out} \approx g_{m4} r_{o4} r_{o3}$

$V_{omin} = 1.4 - 0.7 = 0.7 V$

$V_{GS1} = 0.7 + \sqrt{\frac{2 \times 90}{100 \left(\frac{20}{1}\right)^{10}}}$

$= 0.7 + 0.3 = 1.0 V$

$V_{GS2} = 0.7 + \sqrt{\frac{2 \times 490}{100 \left(\frac{20}{1}\right)^{10}}}$   $1.4 V$


$$\frac{W}{L} = \frac{80}{1} \quad V_{T0} = 0.7V$$

$R = ?$   $M1$  is biased  
with  $V_{ds} = V_{dsat}$

$$V_{GS3} = 0.7 + \sqrt{\frac{2 \times 250}{100 \left(\frac{80}{1}\right)}}$$

$$= 0.7 + \frac{5}{20} = 0.95V$$
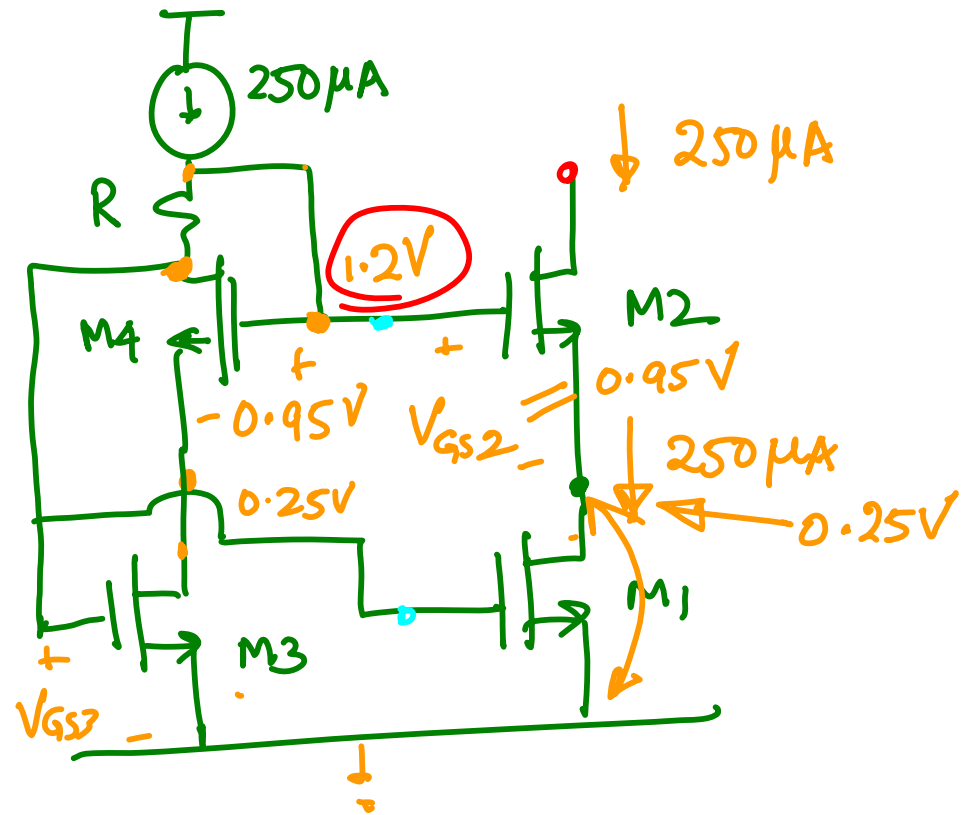
$$R = \frac{1.2 - 0.95}{250 \mu A} = 1k\Omega$$



$$R_{out} = g_{m2} r_{o2} r_{o1}$$

