

HW # 1 Graded handed back

Grading Part 1 pulse grading
 ✓ ✓ - ✓ - -

Part 2 Scored out of 75

Stamping errors: - sign errors
 - completely incorrect stamps

Gyrator - full MNA formulation

$$\begin{cases} i_1 = -g v_2 \\ i_2 = g v_1 \end{cases} \left. \begin{array}{l} \text{voltage controlled} \\ \text{formulation} \\ \Rightarrow \text{plain nodal stamp} \end{array} \right\}$$

Transformer only 1 Branch current
 2 branch currents not needed

branchNum = mappedBranchName() ..

branchNum1 = branchNum + 1

NumBranches ++

branchNum1 = NumBranches

r1 node1 vsrc 1


vsrc node1 0 1

Stamping of '0' entries not required

Test circuits - 1 line circuit

Two ports:

n_1 A B C D n_2

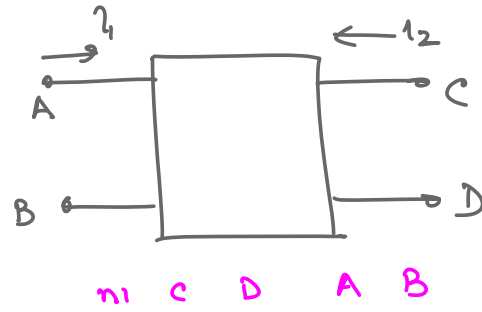

Testing:

Continuation methods


- Source stepping - natural parameter continuation
- GMIN stepping (SPICE3, HSPICE)

Artificial parameter continuation methods

$$\tilde{f}(x(\lambda), \lambda) = 0 \quad \text{sweep } \lambda \text{ from } 0 \text{ to } 1$$


$$\tilde{f}(x(\lambda), \lambda) = \lambda f(x) + (1-\lambda)x$$
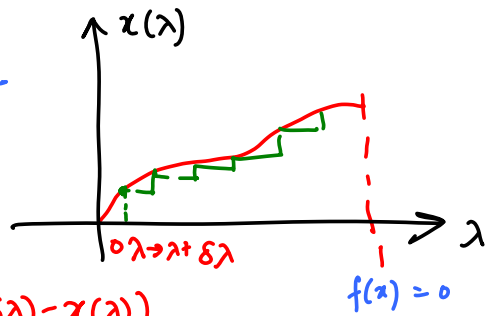
$$\tilde{f}(x(\lambda+\delta\lambda), \lambda+\delta\lambda) = \tilde{f}(x(\lambda), \lambda) + \frac{\partial \tilde{f}}{\partial x} (x(\lambda+\delta\lambda) - x(\lambda)) + \frac{\partial \tilde{f}}{\partial \lambda} \delta\lambda$$



$$\frac{\partial \tilde{f}}{\partial x} (x(\lambda+\delta\lambda) - x(\lambda)) = - \frac{\partial \tilde{f}}{\partial \lambda} \delta\lambda$$
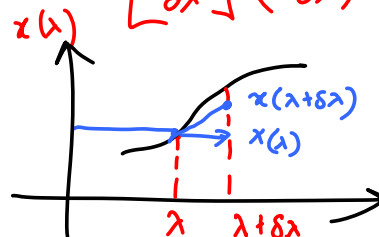
$$x(\lambda+\delta\lambda) = x(\lambda) + \left[\frac{\partial \tilde{f}}{\partial x} \right]^{-1} \left(- \frac{\partial \tilde{f}}{\partial \lambda} \right) \delta\lambda$$



Parameterized in terms of the arc length (σ)

$$\sigma = 0 \text{ to } \sigma_L$$

$$x(\sigma), \lambda(\sigma)$$


$$\delta\sigma = \sqrt{(\delta\lambda)^2 + \delta x^2}$$

$$\|\delta x\|^2 + |\delta\lambda|^2 = \delta\sigma^2$$

$$\left\| \frac{dx}{ds} \right\|^2 + \left| \frac{d\lambda}{ds} \right|^2 = 1 \quad \text{actual arc length (s)}$$

$$\|\dot{x}(s)\|^2 + |\dot{\lambda}(s)|^2 = 1$$

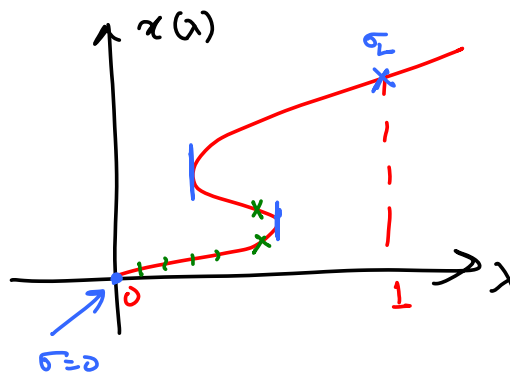HOMPACK is a public domain solver (homotopy methods)



- Choice of embedding function


$$\tilde{f}(x(\lambda), \lambda) = \lambda f(x) + (1-\lambda)x$$

Choice of \tilde{f} affects convergence

- $\tilde{f}(x(0), 0)$ must have a unique solution
avoid the situation shown

- The solution $x(\lambda)$ must be bounded

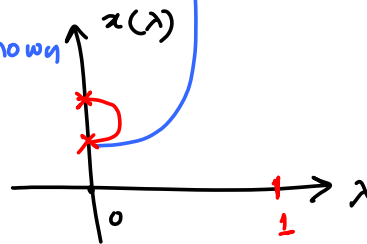This ensures that the track doesn't go to infinity



DC operating point analysis
DC transfer curve "

Small-signal AC analysis


- Frequency domain analysis of linear circuits
 - provides information on magnitude/phase of response or transfer functions
- ⇒ phase margin, stability

MNA equations

$$G(V_1 - V_2) + I_E = 0$$

$$G(V_2 - V_1) + \frac{C dV_2}{dt} = 0$$

$$V_1 = E_S$$

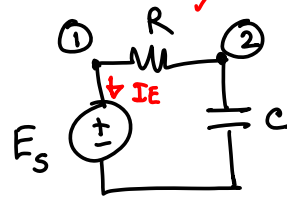

$$x = x_0 + x_{ac} e^{j\omega t}$$

$$G(V_1 - V_2) + I_E = 0$$

$$G(V_2 - V_1) + j\omega C V_2 = 0$$

$$V_1 = E_S$$

AC stamp of a linear capacitor

$$\begin{matrix} & v_A & v_B \\ A & \begin{bmatrix} +j\omega C & -j\omega C \\ -j\omega C & +j\omega C \end{bmatrix} \\ B & \end{matrix}$$



We will now have a system of complex linear equations

Sparse 1.4 can solve such systems

Procedure

for $\omega = \omega_{\text{initial}}$ to ω_{final} }
assemble circuit equations for each ω

$$\text{Solve } A(j\omega) x = b$$

LU Factorization of $A(j\omega)$

Forward/Back solves


x is a function of frequency

Nonlinear capacitor

$$i_c = \frac{dq}{dt} = \frac{dq(v)}{dt}$$

$$= \frac{\partial q(v)}{\partial v} \frac{dv}{dt}$$

incremental capacitance at a DC operating point $C(v_{op}) = \left. \frac{\partial q(v)}{\partial v} \right|_{op. pt.}$

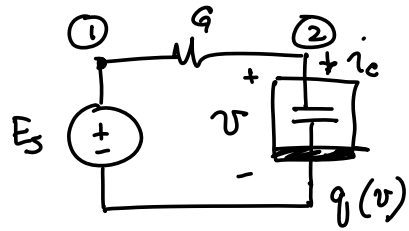


Linear Inductor

$$v = L \frac{di}{dt}$$

$$= j\omega L I$$

$$V_{N+} - V_{N-} - j\omega L I = 0 \Rightarrow I = \frac{V_{N+} - V_{N-}}{j\omega L}$$

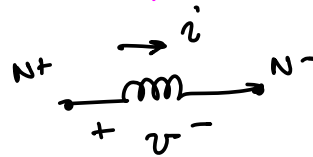Current controlled element \Rightarrow MNA stamp



$$\begin{matrix} N+ & N- & I \\ N+ & & +1 \\ N- & & -1 \\ I & \begin{bmatrix} 1 & -1 & -j\omega L \end{bmatrix} \end{matrix}$$

For DC

$$\begin{bmatrix} +1 \\ -1 \\ 0 \end{bmatrix}$$

Nodal stamp

$$\begin{bmatrix} +\frac{1}{j\omega L} & -\frac{1}{j\omega L} \\ -\frac{1}{j\omega L} & +\frac{1}{j\omega L} \end{bmatrix}$$

$$\omega = 1, \quad L = 1 \text{ nH}, \quad C = 1 \text{ pF}$$

$$\omega C = 10^{-12}; \quad \frac{1}{\omega L} = 10^9 \quad [10^{-12}, 10^9]$$

$$\omega L = 10^{-9} \quad \text{dynamic range } [10^{-12}, 1]$$

Summary

- For small-signal ac analysis (linearize around a DC operating point)
 - nonlinear capacitors replaced by incremental capacitors at dc op. pt.
 - nonlinear conductances ($i = i(v)$) replaced by linear conductances ($\frac{\partial i}{\partial v}$) calculated at the dc. op. pt.
- Inductors — use MNA formulation
- Assemble a linear complex system of equations
- Solve equations at each frequency.

$$A(j\omega) x = b$$

Frequency independent $\left[\begin{matrix} G \\ +j\omega C \end{matrix} \right] x = b$

Transient analysis


- large-signal time-domain analysis of nonlinear circuits
- input source(s) time varying (sine, pulse, PWL, ...)
determine currents/voltage waveforms as a function of time
- Used as the basis for a Fourier analysis
(• FOUR vs SPICE)

Consider a linear circuit

$$G(V_1 - V_2) + IE = 0$$

$$G(V_2 - V_1) + C \frac{dV_2}{dt} = 0$$

$$V_1 = E_s(t)$$

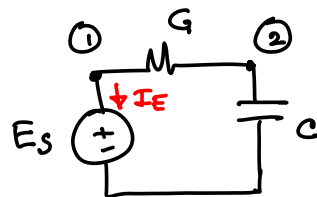


Given $E_s(t)$ find $V_1(t)$, $V_2(t)$, $I_E(t)$

Suppose we can express $\frac{dV_2}{dt} = \alpha V_2 + \beta$


The derivative is the slope

B.E. (Backward Euler) $\left. \frac{dv}{dt} \right|_{t_{n+1}} = \frac{v(t_{n+1}) - v(t_n)}{h}$

F.E. (Forward Euler) $\left. \frac{dv}{dt} \right|_{t_n} = \frac{v(t_{n+1}) - v(t_n)}{h}$

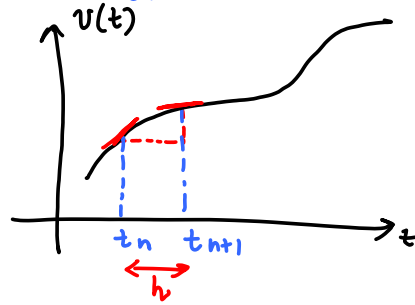

Observe that we are discretizing time

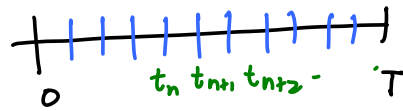


Questions?

What should 'h' be. Error control
Which integration method should be used (FE, BE, or others?)

⇒ properties of integration methods


Should 'h' be uniform or nonuniform

⇒ variable timesteps

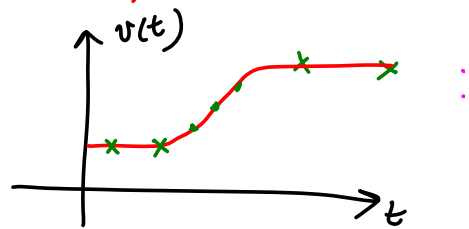



$$G(V_2 - V_1) + C \frac{dV_2}{dt} = 0$$

$$C \left. \frac{dv}{dt} \right|_{t+h} = C \frac{v(t+h) - v(t)}{h}$$

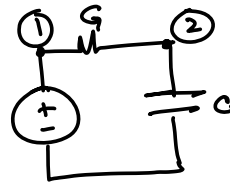


$$I_c(t+h) = \frac{C}{h} v(t+h) - \frac{C}{h} v(t)$$

$$\frac{dV_2}{dt} = \alpha V_2 + \beta$$

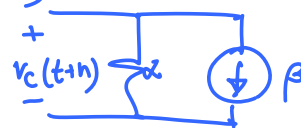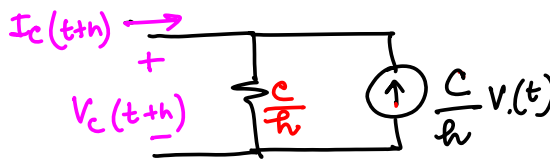


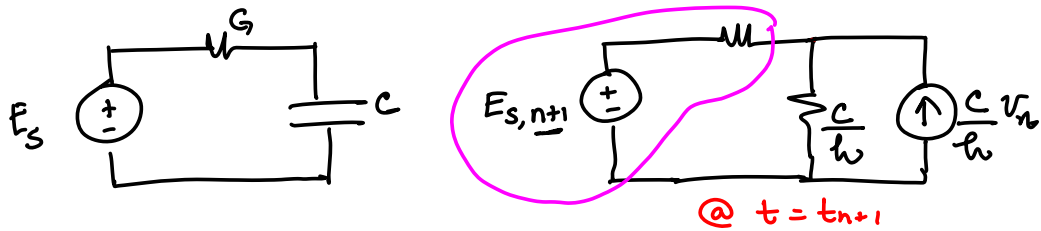
Companion model of a capacitor for transient analysis



Given an initial condition across the capacitor v_0
 we can solve $v_1, v_2, v_3, \dots, v_M$

Example $R = 1\Omega, C = 1F, E_s(t) = 1V \text{ step}$

$h = 0.1 \text{ sec} \quad v_c(0) = 0$

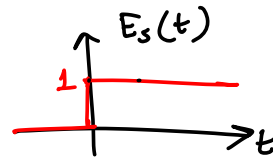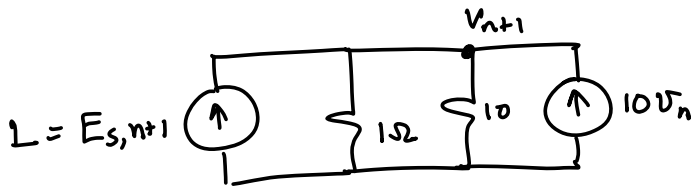

$$v(t) = 1 - e^{-t}$$

$$1. v_{n+1} + 10 v_{n+1} = 10 v_n + 1$$

$$v_{n+1} = \frac{1}{11} (1 + 10 v_n)$$


	Numerical	Exact
$v(0.1)$	0.0909	0.095
$v(0.2)$	0.174	0.181
$v(0.3)$	0.249	0.259
$v(0.4)$	0.317	0.33

Change h from 0.1 to 0.05

Global error is the error accumulated over the whole time interval

What about the local error (one-step error)

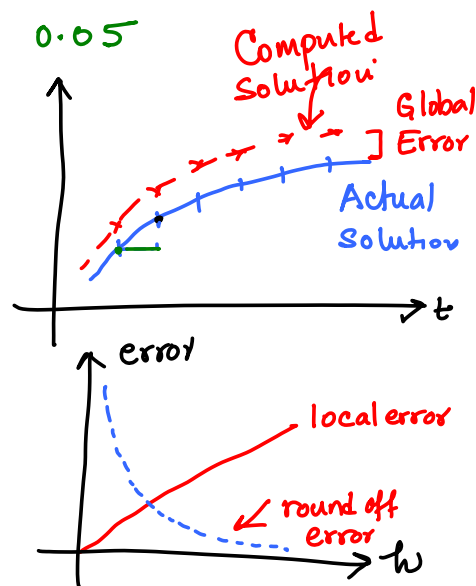Naturally, as $h \rightarrow 0$ this error should go to zero



$$\frac{dv}{dt} = \frac{v(t+h) - v(t)}{h}$$

Convergent method

Consistency

Stability

Consistency + Stability \iff Convergence