

Noise in Integrated Circuits

- Sensitivity of communication systems limited by noise
- We are interested in noise phenomena caused by small current and voltage fluctuations generated within the devices
 - These fluctuations give rise to uncertainty in current/voltage at nodes of a circuit
- Noise is present due to the fact that charge is not continuous but is carried in discrete amounts $q=1.6 \times 10^{-19}$ C (quantization of charge)

Nyquist, Johnson, Schottky were pioneers who explained the origins of noise

Why is Noise a Problem?

- Noise represents a lower limit to the amplitude of the signal that can be amplified (or the circuit can process) without seriously affecting the signal quality
- Noise places an upper limit on the useful gain of an amplifier
 - If gain is increased without limit, output stages of the circuit eventually begin to limit – on the amplified noise from the input stages



Shot Noise

- Described and explained by Schottky in 1918
- Associated with flow of carriers across a barrier (pn junction)


Consider a diode:

Some carriers get enough energy to cross over the barrier

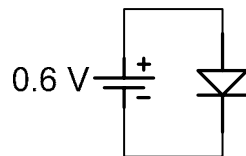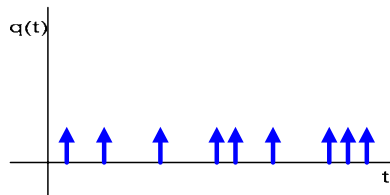Since they cross the barrier randomly arrival of charge is random




Shot Noise (Frequency Spectrum)

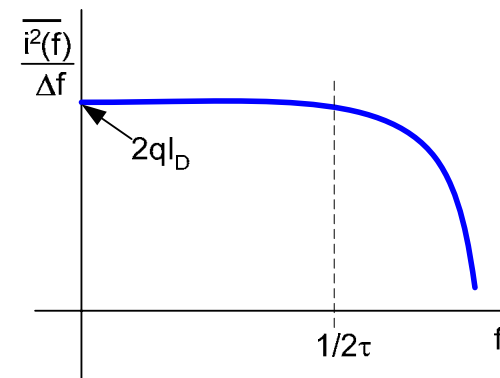

$$\frac{\overline{i^2}}{\Delta f} = 2qI_D \quad \text{is constant over the frequency range of interest} \Rightarrow \text{white noise}$$

Physical Interpretation

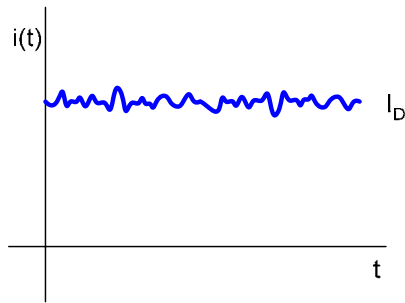

$i(t)$ is the sum of a DC term I_D and a time varying term that is random


$$I = I_D + i \text{ (random, zero mean)}$$

$$\overline{i^2} = \text{mean square variation} = \overline{(I - I_D)^2}$$

$$= \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T (I - I_D)^2 dt$$

$$= 2qI_D \Delta f$$

Measurement of Noise

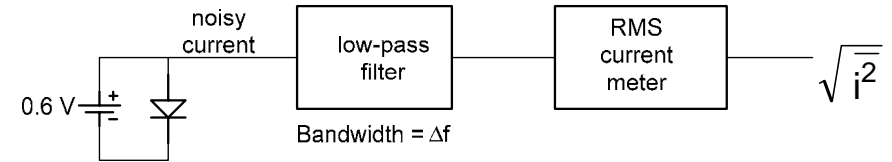


$\overline{i^2}$ = mean squared value (A^2)
power delivered by the noise current over a bandwidth of Δf to a 1Ω resistor

$\sqrt{\overline{i^2}}$ = root mean squared value (A) (RMS)

$\frac{\overline{i^2}}{\Delta f}$ = power per unit Hz (spectral density)

Why is This a Random Phenomena
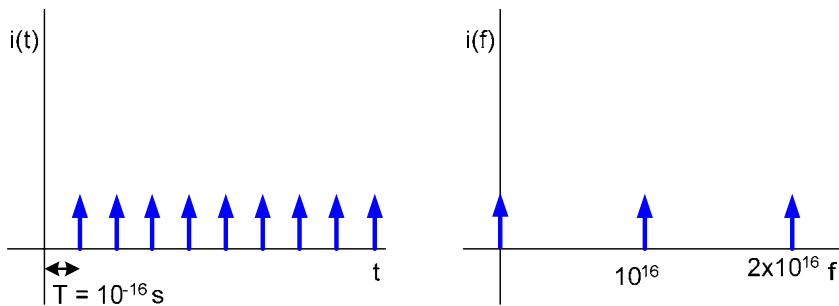
$$I_D = 1.6\text{mA} \Rightarrow \text{current pulses every } (1/1.6 \times 10^{-3}) 1.6 \times 10^{-19} \text{ s} = 10^{-16} \text{ s}$$



The spectrum is periodic with a fundamental of 10^{16} Hz, i.e., no noise would be produced in the normal frequency range

\Rightarrow Shot noise would not even be a problem!

Properties of Shot Noise

- Related to a dc current
- Independent of temperature
- Spectral density independent of frequency

$$\frac{\overline{i^2}}{\Delta f} = 2qI_D \Rightarrow \text{white noise}$$


- Noise power $\propto \Delta f, I_D$

Diode: Example + Small-Signal Model

$$I_D = 1\text{mA}, \quad \Delta f = 1\text{MHz}$$

$$\begin{aligned} \overline{i_D^2} &= 2q(1\text{mA})\Delta f = 2 \times 1.6 \times 10^{-19} \times 10^{-3} \times 10^6 \\ &= 3.2 \times 10^{-16} \text{A}^2 \end{aligned}$$
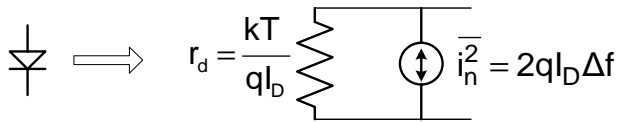
$$\therefore \text{rms value} = \sqrt{\overline{i_D^2}} = 1.7 \times 10^{-8} \text{A} = 17\text{nA}$$




Since the noise signal has random phase, and is defined solely in terms of its mean square value, it has no polarity

Thermal Noise

- Also called Johnson or Nyquist noise
- Associated with random thermal motion of electrons within the physical body of a resistor
- Thermally agitated charge carriers in a conductor result in a randomly varying current, hence, a random voltage
- Thermal origin \Rightarrow **directly related to temperature**. As temperature approaches 0 absolute, thermal noise also approaches 0

Resistor Thermal Noise

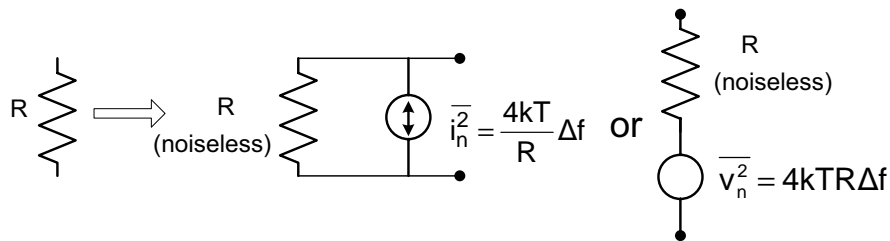

Properties of Thermal Noise

- White noise, uniformly distributed in frequency domain
- Proportional to absolute temperature
- Noise source not associated with a dc current or barrier
- Present in any physical resistor (not for resistors used in small signal equivalent circuits such as r_o , r_π)

Thermal Noise Example

For a 1k resistor at 300°K

$$\frac{\overline{v_n^2}}{\Delta f} = 16 \times 10^{-18} \text{ V}^2/\text{Hz}$$

$$\therefore \sqrt{\overline{v_n^2}} = (4nV/\sqrt{\text{Hz}})\sqrt{\Delta f}$$

Thermal noise current of a 1kΩ resistor at 300°K is the same as 50 μ A of direct current exhibiting shot noise

The only way to reduce thermal noise of a given resistance is to keep the temperature as low as possible and the limit the bandwidth to the minimum useful value

Flicker Noise or 1/f Noise (Pink Noise)

- Origins of flicker noise are varied
- Present in diodes, BJTs, and MOSFETs
- Tends to be associated with surface states
 - Surface states capture and release carriers in a random manner
- The noise signal has energy concentrated at low frequencies

$$\overline{i^2} = k_1 \frac{I^a}{f^b} \Delta f$$


I = direct current

a = a constant $0.5 < a < 2$

b = a constant $\sim 1 \Rightarrow$ “1/f noise”


k_1 varies with device

Flicker Noise Spectrum

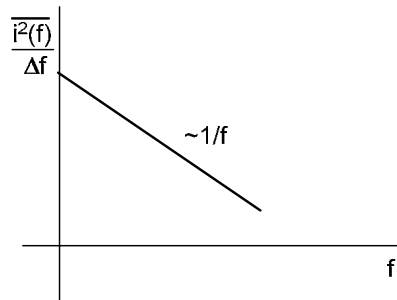


- 1/f noise important for low frequency operation
- K_1 can vary orders of magnitude from one device type to another
- K_1 can also vary widely for different transistors on the same wafer due to dependence on defects

Small-Signal Diode Noise Model

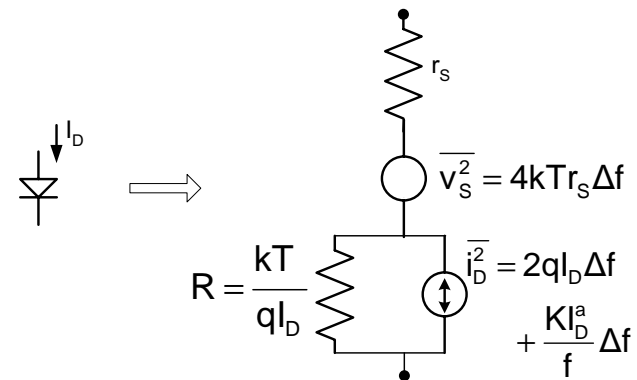

r_s = series ohmic resistance (a physical resistor)

Small-Signal BJT Noise Model

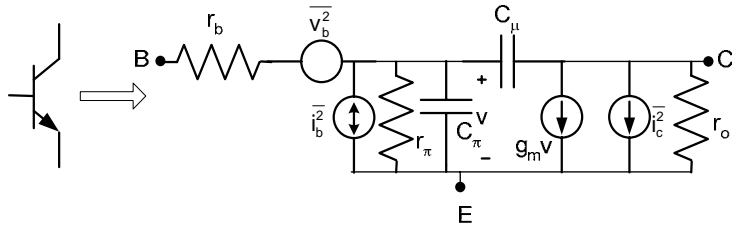


$$\overline{v_b^2} = 4kTr_b\Delta f$$

$$\overline{i_b^2} = 2qI_B\Delta f + K_1 \frac{I_B^a}{f} \Delta f$$

$$\overline{i_c^2} = 2qI_C\Delta f$$

r_b = series base resistance (a physical resistor)

Small-Signal MOSFET Noise Model

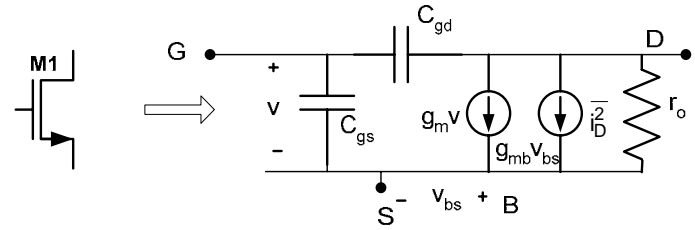

$$\overline{i_D^2} = 4kT\gamma g_{d0}\Delta f + \frac{K}{f} \frac{g_m^2}{WLC_{ox}^2} \Delta f$$

where $g_{d0} = g_{ds}|_{V_{ds}=0}$
 $\gamma = 1$ at zero V_{DS} and $2/3$ in saturation
 for long channel devices

In short - channel devices γ is typically 2-3 and could be larger (??)

$$g_{ds}|_{V_{ds}=0} = g_{m,sat}$$

$$4kT\gamma g_{d0}\Delta f = 4kT\left(\frac{2}{3}\right)g_m$$


MOSFET Induced Gate Noise

- Current flow through resistive channel \Rightarrow thermal noise (drain current noise)
- Because of capacitive coupling between channel and gate \Rightarrow thermal noise current at gate
- Important at high frequencies

$$\overline{i_g^2} = 4kT\delta g_g\Delta f$$


$$\text{where } g_g = \frac{\omega^2 C_{gs}}{5g_{do}}$$

$\delta = 4/3$ for long channel devices

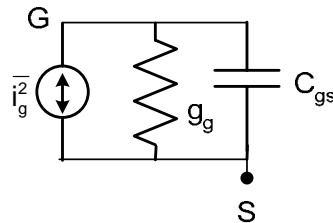

More on Induced Gate Noise

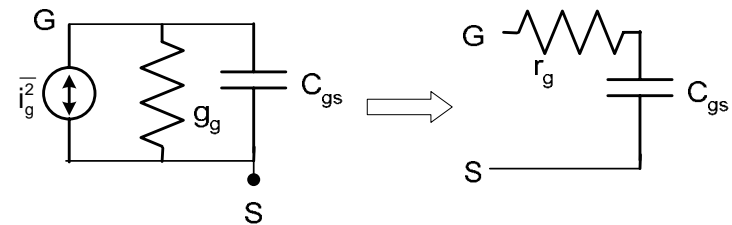
- The spectral density of gate current increases with frequency \Rightarrow important at high frequencies
- Noise source can be recast into equivalent form



$$\overline{v_g^2} = 4kT\delta r_g\Delta f$$

$$\text{where } r_g = \frac{1}{5g_{do}}$$

Circuit Noise Calculations

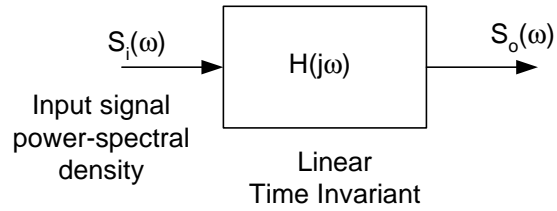

$$S_o(\omega) = S_i(\omega) [H(j\omega)H^*(j\omega)]$$

$$= S_i(\omega) |H(j\omega)|^2$$

$$\therefore \sqrt{S_o(\omega)} = \sqrt{S_i(\omega)} |H(j\omega)|$$

Analysis Procedure

Assume noise sources are uncorrelated
(**separate, independent physical mechanisms**)

For each source $\overline{i_n^2}$ ($\overline{v_n^2}$):

1) Replace with a sinusoidal, deterministic source of value i_n (v_n)


$$\sqrt{\overline{i_n^2}} \quad \left(\sqrt{\overline{v_n^2}} \right)$$

2) Calculate $v_{on}(\omega) = i_n(\omega) |H(j\omega)|$

$$\frac{\overline{v_{on}^2}}{\Delta f} = \text{output voltage spectral density due to } i_n^2$$

$$\overline{v_{o_{total}}^2} = \overline{v_{on1}^2} + \overline{v_{on2}^2} + \dots$$

Resistor Example

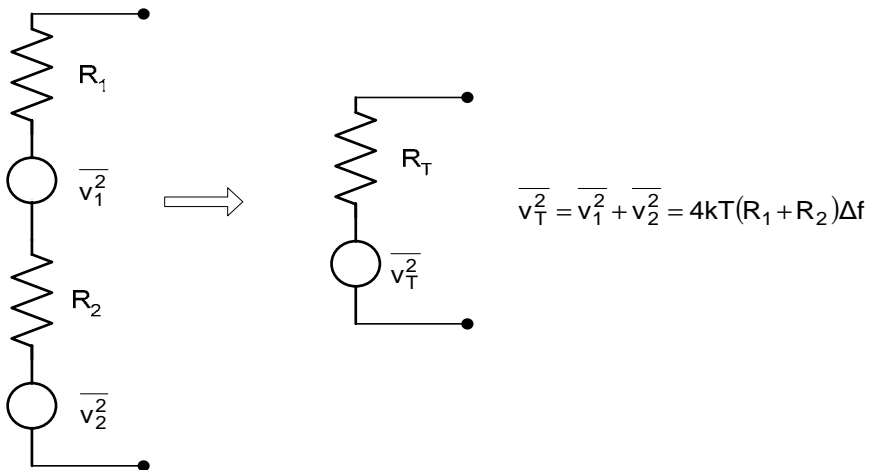

BJT Example



$$\overline{v_s^2} = 4kTR_s\Delta f$$

$$\overline{v_b^2} = 4kTr_b\Delta f$$


$$\overline{i_b^2} = 2qI_B\Delta f \text{ (ignore } 1/f \text{ noise)}$$

$$\overline{i_c^2} = 2qI_C\Delta f$$
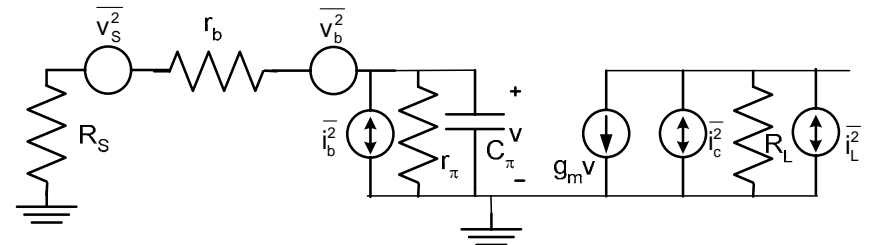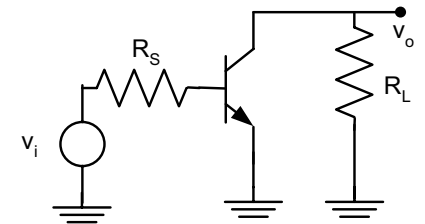
$$\overline{i_L^2} = 4kT \frac{1}{R_L} \Delta f$$



Output Noise Due to $\overline{v_s^2}$

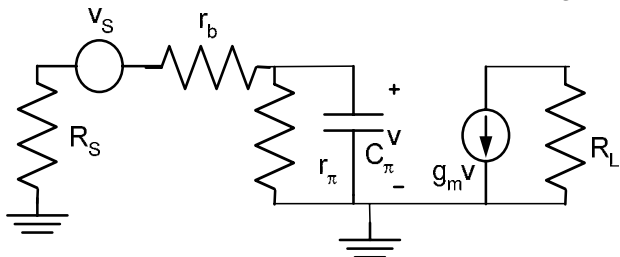

$$v = \frac{r_\pi \| 1/j\omega C_\pi}{R_s + r_b + r_\pi \| 1/j\omega C_\pi} v_s = \frac{r_\pi / (1 + j\omega C_\pi r_\pi)}{R_s + r_b + r_\pi / (1 + j\omega C_\pi r_\pi)} v_s$$

$$v_o = -g_m R_L v$$

$$= -g_m R_L r_\pi \frac{1}{r_\pi + (R_s + r_b)(1 + j\omega C_\pi r_\pi)} v_s$$

$$v_o = -\frac{\beta R_L}{r_\pi + R_s + r_b} \left(\frac{1}{1 + j\omega\tau} \right) v_s$$


$$\text{where } \tau = C_\pi (r_\pi \| (R_s + r_b))$$

Output Noise Due to $\overline{v_s^2}$

$$\overline{v_{o1}^2} = \left(\frac{\beta R_L}{r_\pi + R_s + r_b} \right)^2 \left(\frac{1}{1 + (\omega\tau)^2} \right) \overline{v_s^2}$$

$$= \left(\frac{\beta R_L}{r_\pi + R_s + r_b} \right)^2 \frac{1}{1 + \left(\frac{f}{f_1} \right)^2} \overline{v_s^2} \quad \text{where } f_1 = \frac{1}{2\pi\tau}$$


Output Noise Due to $\overline{v_b^2}$

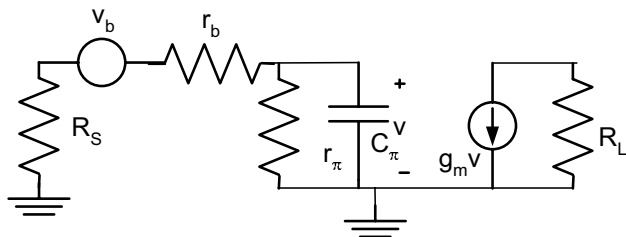


$$\overline{v_{o2}^2} = \left(\frac{\beta R_L}{r_\pi + R_s + r_b} \right)^2 \left(\frac{1}{1 + (\omega\tau)^2} \right) \overline{v_b^2}$$

$$= \left(\frac{\beta R_L}{r_\pi + R_s + r_b} \right)^2 \frac{1}{1 + \left(\frac{f}{f_1} \right)^2} \overline{v_b^2} \quad \text{where } f_1 = \frac{1}{2\pi\tau}$$


Output Noise Due to $\overline{i_b^2}$

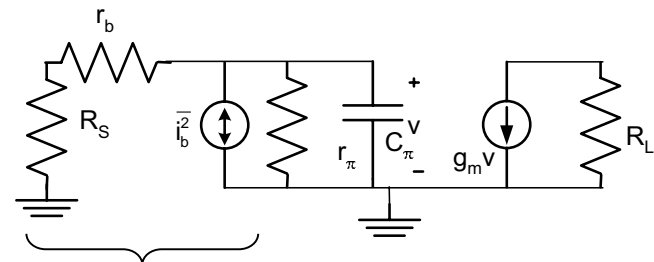

Thevenin's equivalent

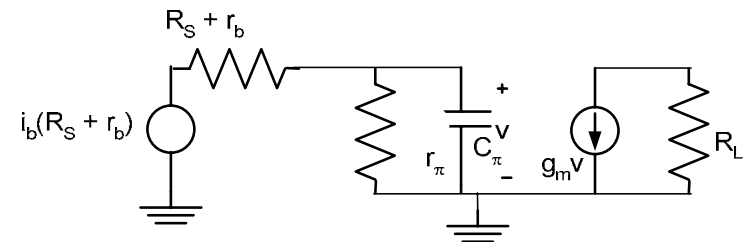


Output Noise Due to $\overline{i_b^2}$

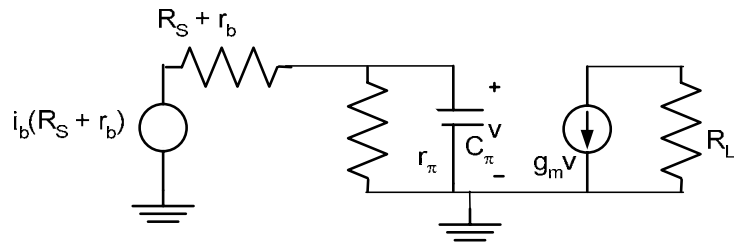

$$\overline{v_{o3}^2} = \left(\frac{\beta R_L}{r_\pi + R_S + r_b} \right)^2 \frac{1}{1 + \left(\frac{f}{f_1} \right)^2} (R_S + r_b)^2 \overline{i_b^2} \quad \text{where } f_1 = \frac{1}{2\pi\tau}$$

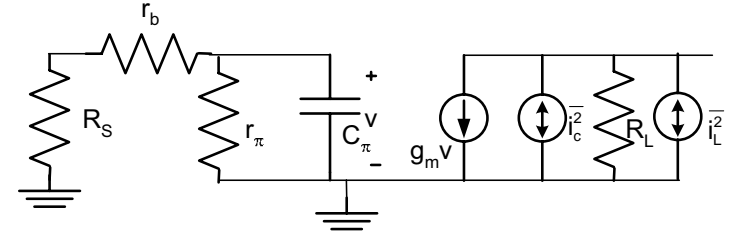Output Noise Due to $\overline{i_c^2}$ and $\overline{i_L^2}$



$$\overline{v_{o4}^2} = R_L^2 \overline{i_c^2}$$

$$\overline{v_{o5}^2} = R_L^2 \overline{i_L^2}$$

Total Output Noise

$$\overline{v_{oT}^2} = \sum_{i=1}^5 \overline{v_{oi}^2}$$

$$\overline{v_{oT}^2} = |A_V|^2 (\overline{v_s^2} + \overline{v_b^2} + (r_b + R_S)^2 \overline{i_b^2}) + R_L^2 \overline{i_c^2} + R_L^2 \overline{i_L^2}$$

$$\text{where } A_V = \frac{\beta R_L}{r_\pi + R_S + r_b} \frac{1}{1 + j \frac{f}{f_1}}$$

$$\overline{v_{oT}^2} = |A_V|^2 (4KT(r_b + R_S) + 2qI_B(r_b + R_S)^2) \Delta f + 2qI_C R_L^2 \Delta f + 4KTR_L \Delta f$$