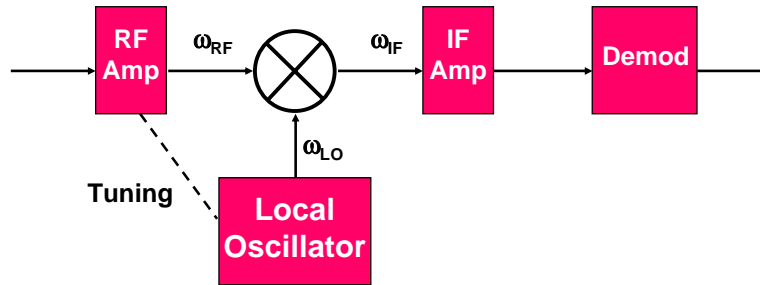


## Down Conversion Mixer

- Super-heterodyne receiver




- Mixer translates high frequency RF signal to a lower frequency IF

$$\omega_{IF} = \omega_{LO} - \omega_{RF}$$

## Up Conversion Mixer

- Super-heterodyne transmitter

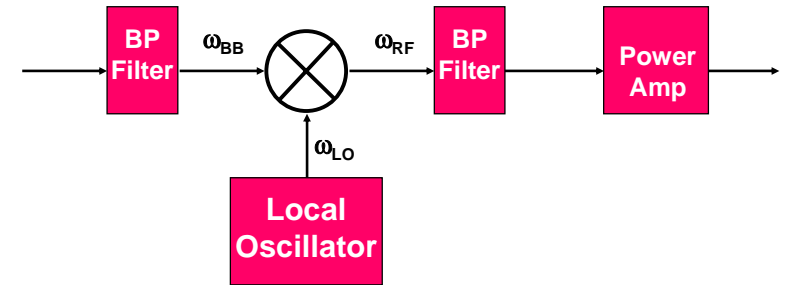

- Mixer translates a low frequency baseband signal to a higher frequency RF


$$\omega_{RF} = \omega_{LO} + \omega_{BB}$$

## Down Conversion Mixer

$$\omega_{IF} = \omega_{LO} - \omega_{RF}$$

- Linear time invariant networks do not produce spectral components **not** in the input

⇒ Use time varying or nonlinear networks

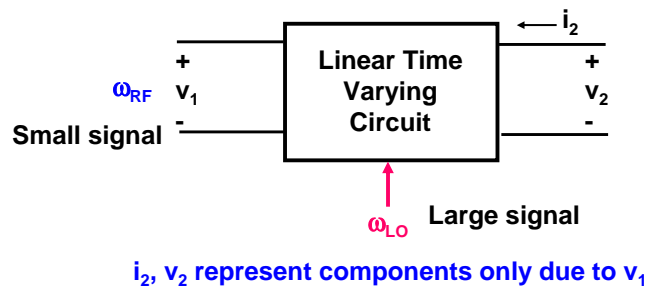

## Analysis of LTV Network

$$i_2 = g(t)v_1$$

$g(t)$  is the time varying transconductance due to the LO at  $\omega_{LO}$

$$g(t) = g_0 + g_1 \cos \omega_{LO} t + g_2 \cos 2\omega_{LO} t + \dots$$


For  $v_1(t) = V_1 \cos \omega_{RF} t$

$$\begin{aligned} i_2(t) &= (g_0 + g_1 \cos \omega_{LO} t + g_2 \cos 2\omega_{LO} t + \dots) V_1 \cos \omega_{RF} t \\ &= g_0 V_1 \cos \omega_{RF} t + \frac{g_1 V_1}{2} \cos(\omega_{LO} \pm \omega_{RF}) t + \frac{g_2 V_1}{2} \cos(2\omega_{LO} \pm \omega_{RF}) t + \dots \end{aligned}$$

The component of  $i_2(t)$  at the IF is  $\frac{g_1 V_1}{2} \cos(\omega_{LO} - \omega_{RF}) t$

$$G_{mconv} = \frac{|\text{IF current output}|}{|\text{RF voltage input}|} = \frac{g_1 V_1 / 2}{V_1} = \frac{g_1}{2}$$

## Nonlinear Network

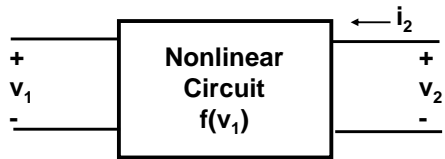

$$i_2 = f(v_1) = \sum_i a_i v_1^i$$

Consider a quadratic nonlinearity

$$i_2 = a_1 v_1 + a_2 v_1^2$$

$$v_1(t) = V_{RF} \cos \omega_{RF} t + V_{LO} \cos \omega_{LO} t$$

$$i_2(t) = a_1 (V_{RF} \cos \omega_{RF} t + V_{LO} \cos \omega_{LO} t) + a_2 (V_{RF} \cos \omega_{RF} t + V_{LO} \cos \omega_{LO} t)^2$$

$$a_2 V_{RF} V_{LO} [\underbrace{\cos(\omega_{LO} - \omega_{RF}) t}_{\omega_{IF}} + \cos(\omega_{LO} + \omega_{RF}) t]$$

$$G_{mconv} = \frac{|\text{IF current output}|}{|\text{RF voltage input}|} = \frac{a_2 V_{RF} V_{LO}}{V_{RF}} = a_2 V_{LO}$$

## Transistor $G_{mconv}$

For a BJT under small signal conditions

$$a_2 = \frac{1}{2} \frac{I_C}{V_{th}^2} \Rightarrow G_{mconv} = \frac{1}{2} \frac{I_C}{V_{th}^2} V_{LO}$$

depends on bias, LO amplitude and temperature

For a MOSFET

$$a_2 = \frac{1}{2} k' \frac{W}{L} \Rightarrow G_{mconv} = \frac{1}{2} k' \frac{W}{L} V_{LO} = \frac{1}{2} \mu C_{ox} \frac{W}{L} V_{LO}$$

Independent of bias


Depends on LO amplitude and temperature

## Mixer Design Considerations

- **Linearity**
  - Third-order intermodulation (IP3) is an important consideration
- **Isolation**
  - Interaction between RF, IF, and LO ports has to be minimized
- **Conversion gain**
- **Noise performance**
- **Power**
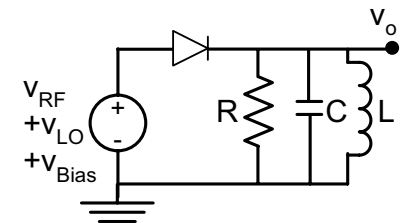
## Single-Diode Mixer

- Simplest and oldest mixer
- Diode nonlinearity generates current at harmonic and intermod frequencies
- Tank filters except IF
- No isolation
- No conversion gain
- Suitable for high frequencies
- Used in early UHF TV tuners



## Single-Device BJT Mixer

- High gain
- Collector tuned to IF

$$I_C = I_S \exp\left(\frac{V_{BS} + v_s + v_{io}}{V_t}\right)$$

$$= I_{CA} \exp\left(\frac{v_s}{V_t}\right) \exp\left(\frac{v_{io}}{V_t}\right)$$


$$I_{CA} = I_S \exp\left(\frac{V_{BS}}{V_t}\right)$$

$$\exp\left(\frac{V_{sA} \cos \omega_s t}{V_t}\right) = I_0(d) + 2I_1(d) \cos \omega_s t + \dots$$

$$d = \frac{V_{sA}}{V_t}$$

$$\exp\left(\frac{V_{ioA} \cos \omega_{io} t}{V_t}\right) = I_0(y) + 2I_1(y) \cos \omega_{io} t + \dots$$

$$y = \frac{V_{ioA}}{V_t}$$

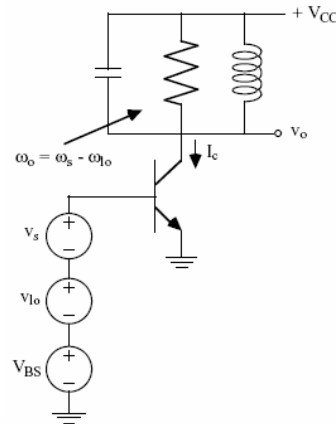

## Single-Device BJT Mixer Analysis

$$I_C = I_{CA} I_0(d) I_0(y) + \dots + 2I_{CA} I_1(d) I_1(y) \cos(\omega_s - \omega_{io})t + \dots$$

$$= I_{DC} \left[ 1 + \dots + 2 \frac{I_1(d)}{I_0(d)} \frac{I_1(y)}{I_0(y)} \cos(\omega_s - \omega_{io})t + \dots \right]$$

$$I_{DC} = I_{CA} I_0(d) I_0(y)$$

Since the RF is a small signal  $V_{sA} \ll V_t \Rightarrow d \ll 1$

$$\Rightarrow \frac{I_1(d)}{I_0(d)} = \frac{1}{2}$$

$$I_C(\omega_{IF}) = I_{dc} d \frac{I_1(y)}{I_0(y)} \cos \omega_{IF} t = I_{dc} \frac{V_{sA}}{V_t} \frac{I_1(y)}{I_0(y)} \cos \omega_{IF} t$$

$$G_{mconv} = \frac{I_{dc}}{V_t} \frac{I_1(y)}{I_0(y)} \cong 0.95 \frac{I_{dc}}{V_t} \text{ for large } b$$

## LO Feed Through

The collector current at the fundamental of the LO

$$I_C(\omega_{LO}) = I_{dc} 2 \frac{I_1(y)}{I_0(y)} \cos \omega_{LO} t = 1.9 I_{dc} \cos \omega_{LO} t \text{ for large } b$$

The collector current at IF

$$I_C(\omega_{IF}) = I_{dc} \frac{V_{sA}}{V_t} \frac{I_1(y)}{I_0(y)} \cos \omega_{IF} t = 0.95 I_{dc} \frac{V_{sA}}{V_t} \cos \omega_{IF} t \text{ for large } b$$

$$\text{Therefore, } \frac{I_C(\omega_{IF})}{I_C(\omega_{LO})} = 2 \frac{V_{sA}}{V_t}$$

Example:  $V_{sA} = 1\text{mV}$   $\frac{I_C(\omega_{IF})}{I_C(\omega_{LO})} = 2 \frac{V_{sA}}{V_t} = 2 \times 25.85 = 51.7$

$\Rightarrow$  output tuned circuit must provide adequate rejection at LO frequency

## Avoiding LO Feed Through

Consider an ideal multiplier

$$V_{RF} \cos \omega_{RF} t \times V_{LO} \cos \omega_{LO} t$$

$$= \frac{V_{RF} V_{LO}}{2} [\cos(\omega_{LO} - \omega_{RF})t + \cos(\omega_{LO} + \omega_{RF})t]$$

- There is perfect isolation from RF and LO to IF  
 $\Rightarrow$  Double-balanced mixer
- No third-order IM term!


## Simplified Bipolar Multiplier (Mixer)

Assume  $v_{RF}$  is small

$$i_{out} = g_m v_{RF} = \frac{I_{EE} + I_{LO} \cos \omega_{LO} t}{2V_{th}} v_{RF}$$

$$= \left( \frac{I_{EE} + I_{LO} \cos \omega_{LO} t}{2V_{th}} \right) v_{RF} \cos \omega_{RF} t$$


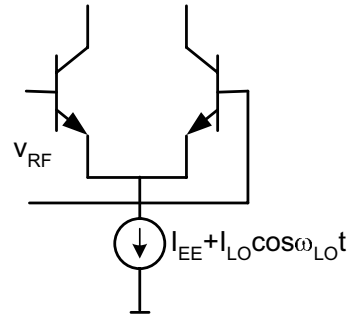
$$= \frac{I_{EE}}{2V_{th}} v_{RF} \cos \omega_{RF} t + \frac{I_{LO}}{4V_{th}} v_{RF} [\cos(\omega_{LO} - \omega_{RF})t + \cos(\omega_{LO} + \omega_{RF})t]$$



Output contains


- RF term and IF term (multiplicative term)
- No LO  $\Rightarrow$  single-balanced mixer

## Switching Emitter-Coupled Pair

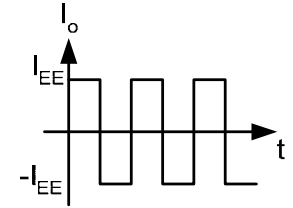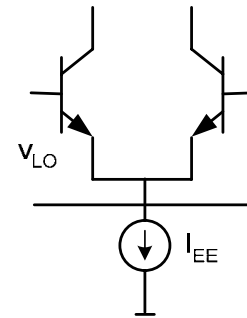

$$I_o = I_{c1} - I_{c2} = I_{EE} \left( \frac{4}{\pi} \cos \omega_{LO} t - \frac{4}{3\pi} \cos 3\omega_{LO} t + \dots \right)$$

## Single-Balanced Mixer

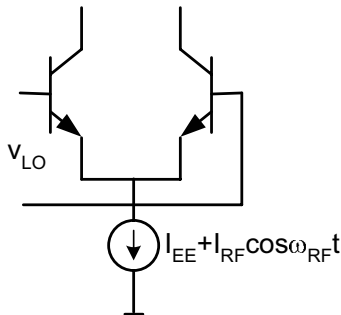

$$I_o = (I_{EE} + I_{RF} \cos \omega_{RF} t) \left( \frac{4}{\pi} \cos \omega_{LO} t - \frac{4}{3\pi} \cos 3\omega_{LO} t + \dots \right)$$

$$= \underbrace{\frac{4}{\pi} I_{EE} \cos \omega_{LO} t}_{\text{LO feed through}} + \underbrace{\frac{2}{\pi} I_{RF} \cos(\omega_{LO} - \omega_{RF})t + \frac{2}{\pi} I_{RF} \cos(\omega_{LO} + \omega_{RF})t}_{\text{IF component}} + \dots$$

LO feed through

IF component

## V-I Conversion


Assuming  $I_{RF} = g_m v_{RF}$ , where  $g_m$  is the transconductance of the V-I converter, we have

$$I_{IF} = \frac{2}{\pi} g_m v_{RF}$$


$\Rightarrow$  the conversion transconductance is

$$G_{mconv} = \frac{2}{\pi} g_m$$

## Examples of Transconductors

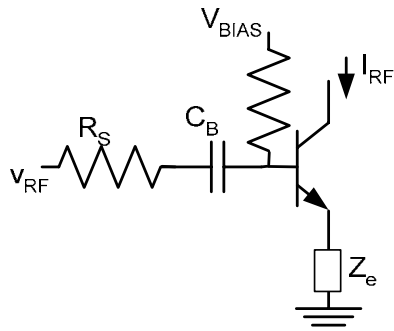

CE (CS) with degeneration

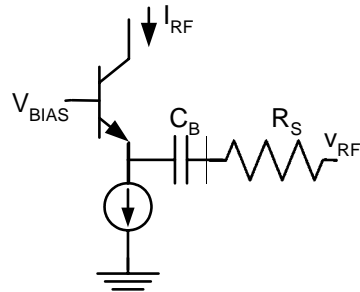


CB (CG) with linearization due to  $R_S$

- Inductive degeneration preferred

- No thermal noise
- No dc voltage drop
- Attenuation of high frequency harmonics, intermod

## Eliminating LO Feedthrough

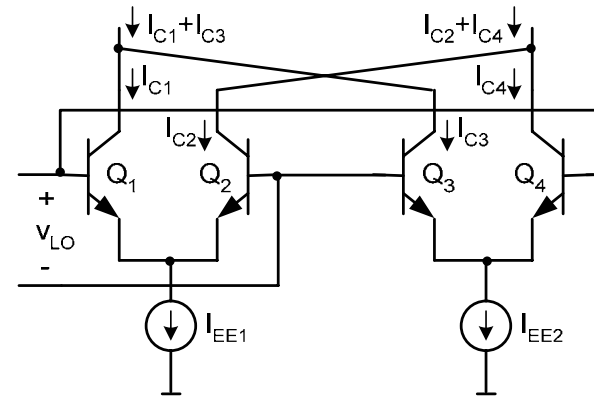

$$I_o = (I_{C1} + I_{C3}) - (I_{C2} + I_{C4}) = (I_{C1} - I_{C2}) - (I_{C4} - I_{C3})$$

$$= (I_{EE1} - I_{EE2}) \left( \frac{4}{\pi} \cos \omega_{LO} t - \frac{4}{3\pi} \cos 3\omega_{LO} t + \dots \right)$$

## RF Currents

Now if we have

$$I_{EE1} = I_{EE} + I_{RF} \cos \omega_{RF} t$$

$$I_{EE2} = I_{EE} - I_{RF} \cos \omega_{RF} t$$


Then,

$$I_o = 2I_{RF} \cos \omega_{RF} t \left( \frac{4}{\pi} \cos \omega_{LO} t - \frac{4}{3\pi} \cos 3\omega_{LO} t + \dots \right)$$

$$= \frac{4}{\pi} I_{RF} \cos(\omega_{LO} - \omega_{RF}) t + \frac{4}{\pi} I_{RF} \cos(\omega_{LO} + \omega_{RF}) t + \dots$$

i.e., no LO or RF feedthrough!

## Generation of RF Currents

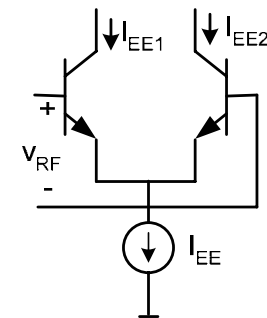


$$I_{EE1} - I_{EE2} = g_m v_{RF} = \frac{I_{EE}}{2V_{th}} v_{RF}$$

$$I_o = g_m v_{RF} \cos \omega_{RF} t \left( \frac{4}{\pi} \cos \omega_{LO} t - \frac{4}{3\pi} \cos 3\omega_{LO} t + \dots \right)$$


$$= \frac{2}{\pi} g_m v_{RF} \cos(\omega_{LO} - \omega_{RF}) t + \frac{2}{\pi} g_m v_{RF} \cos(\omega_{LO} + \omega_{RF}) t + \dots$$

whereby,  $G_{mconv} = \frac{2}{\pi} g_m$


## Double-Balanced (Gilbert) Mixer

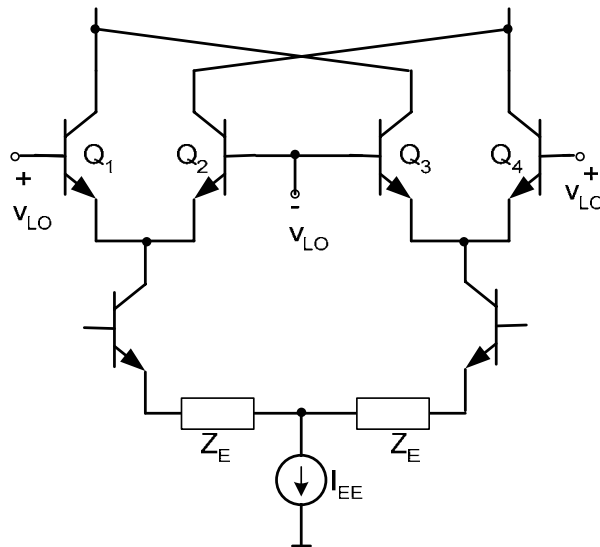

## Gilbert Cell Multiplier

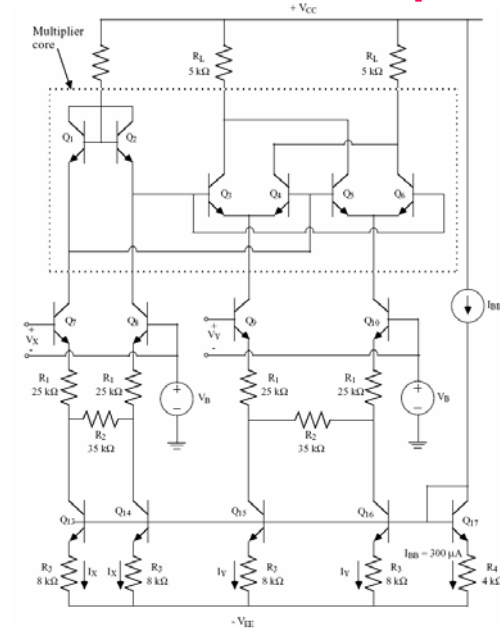


## Down Conversion Mixer

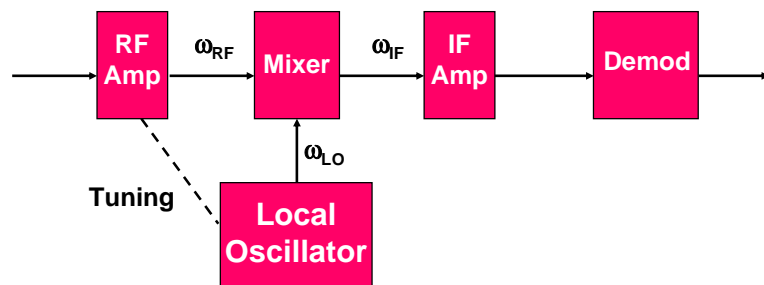

- Mixer also translates noise to IF
- Noise figure is an important specification
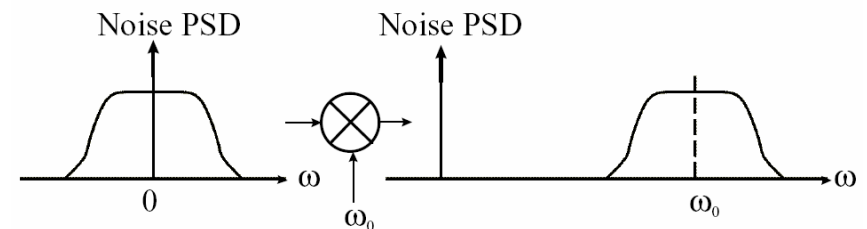
## Mixing Noise


- Up/down conversion of noise due to mixing



- SPICE noise analysis does not work
- Cyclostationarity/frequency correlation important
- Monte Carlo or stochastic methods

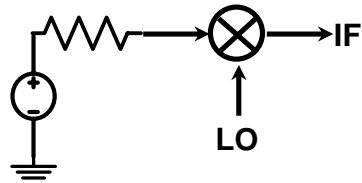
## Noise in a Mixer

- Consider white noise at the input and a noiseless mixer



Assume that the mixer has a conversion gain of 1 for all frequencies

⇒ Output SNR is half of input SNR

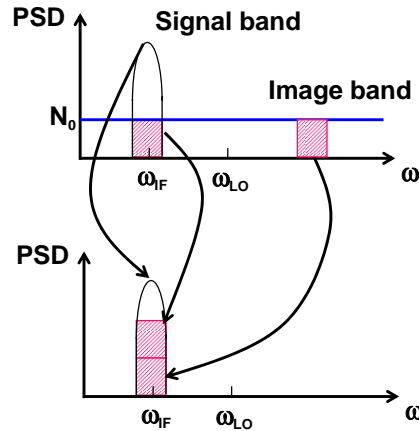

## Down Conversion of Noise

- Since noise in the image band is also downconverted to IF  
⇒ NF for noiseless mixer is 3dB
- This NF is called the single-sideband (SSB) NF, i.e., desired signal spectrum is on one side of the LO frequency as in heterodyne receivers


## Homodyne Receiver

- For a noiseless mixer the input and output SNR are equal

⇒ NF = 0dB

- This is the double-sideband (DSB) NF

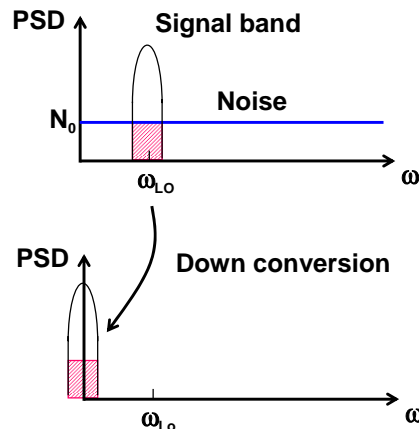
⇒ Signal spectrum exists on both sides of the LO



## Noise Down Conversion in a Real Mixer

- For a stationary noise source

$$S_{out}(\omega) = \sum_{n=-\infty}^{+\infty} |H(\omega) \cdot G_n|^2 \cdot S_{in}(\omega + n\omega_0)$$

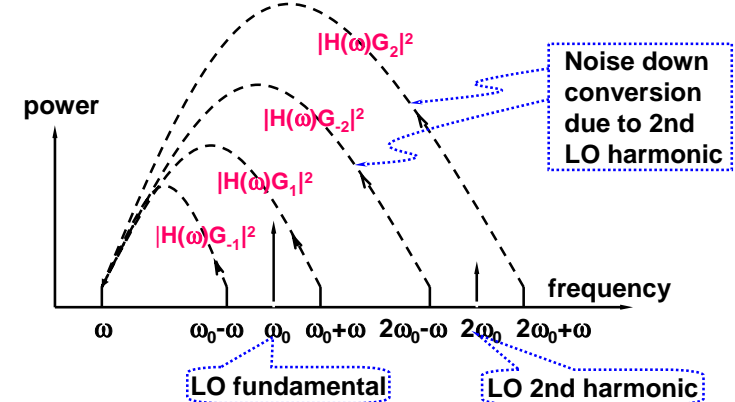


## Mixer Noise Analysis

- **Simulation approach**
  - Available in SpectreRF, Agilent/EEsof ADS
  - Linear time-varying analysis used
    - **Circuit linearized around the LO**
    - **Noise applied as a small-signal**
  - Can be used for any circuit in periodic steady state
- **Indirect approach**
  - Applicable to mixers (Hull & Meyer, 1993)
  - SPICE simulations and 2D FFT used for calculating noise

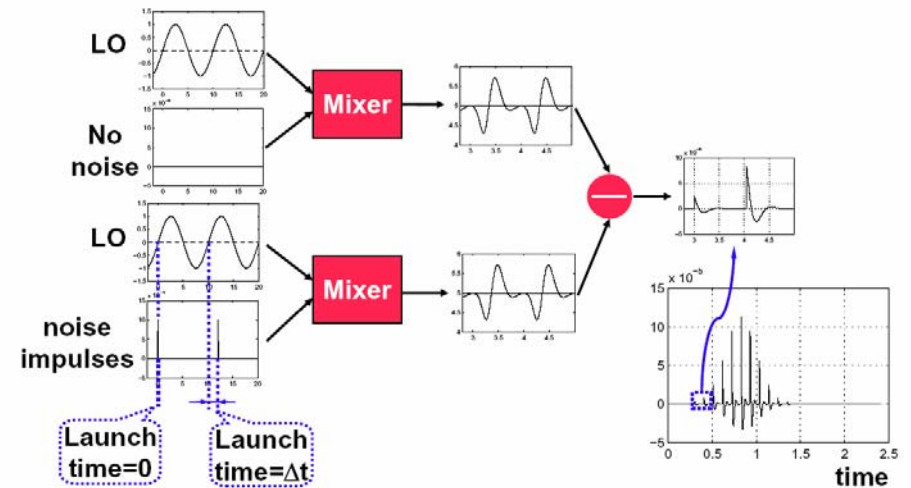
## Hull & Meyer's Approach

- Impulse response from noise source to output (SPICE transient analyses)



## Hull & Meyer's Approach

- Frequency response (2D FFT)

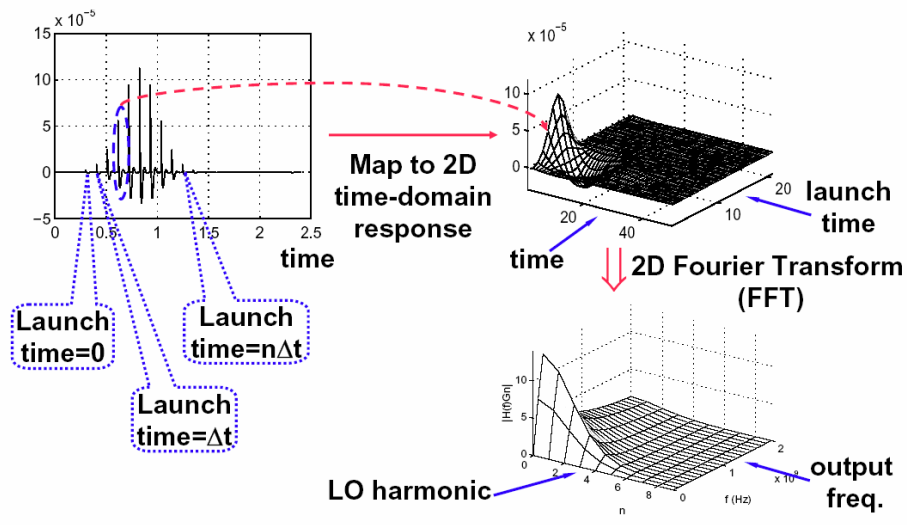

## Noise in a Switching Mixer

