


$$\therefore \frac{R_p}{R_I} = 1 + Q_2^2 \Rightarrow Q_2 = \sqrt{\frac{R_p}{R_I} - 1}$$

$$\text{Also } Q_2 = \omega_0 \frac{L_2}{R_I} \Rightarrow \frac{\omega_0 L_2}{R_I} = \sqrt{\frac{R_p}{R_I} - 1}$$

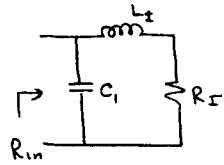2) Upward transformer

$$R_{in} = (1 + Q_1^2) R_I$$

$$\therefore Q_1 = \sqrt{\frac{R_{in}}{R_I} - 1} = \omega_0 \frac{L_1}{R_I}$$



The overall Q of the network is

$$Q = \frac{\omega_0 (L_1 + L_2)}{R_I} = \sqrt{\frac{R_{in}}{R_I} - 1} + \sqrt{\frac{R_p}{R_I} - 1} \quad \text{--- ①}$$

Given  $Q \ll R_{in}, R_p$   $R_I$  can be computed

$$\Rightarrow L_1 + L_2 = \frac{Q R_I}{\omega_0} \text{ i.e. } L \text{ can be determined}$$

Then capacitors can be calculated as


$$C_1 = \frac{Q_1}{\omega_0 R_{in}}, \quad C_2 = \frac{Q_2}{\omega_0 R_p}$$

Remarks


- Solution of ① can be determined iteratively for  $R_I$
- If  $Q$  is large  $R_I \approx \frac{(\sqrt{R_{in}} + \sqrt{R_p})^2}{Q^2}$

- Parasitic capacitances can be absorbed in network design. This is important because capacitance parasitics can dominate in many cases

The T-match

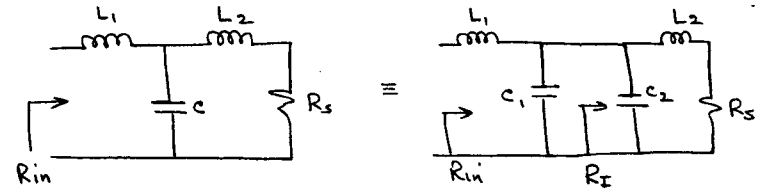

Tapped Capacitor Resonator

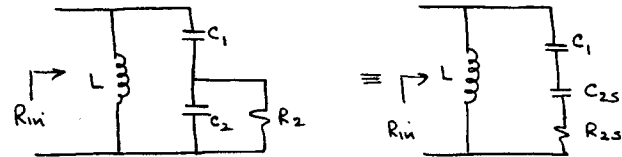

$$C_{2S} = C_2 \frac{(Q_2^2 + 1)}{Q_2^2}, \quad R_{2S} = \frac{R_2}{Q_2^2 + 1}$$

where  $Q_2$  is the Q of the parallel  $R_2 C_2$  section

$$R_S = \frac{R_{in}}{Q^2 + 1} = R_{2S}$$

$$\Rightarrow \frac{R_{in}}{Q^2 + 1} = \frac{R_2}{Q_2^2 + 1}$$

$$\text{whereby } Q_2 = \sqrt{\frac{R_2}{R_{in}} (Q^2 + 1) - 1} = \omega_0 R_2 C_2$$

$$\therefore C_2 = \frac{Q_2}{\omega_0 R_2} = \frac{1}{\omega_0 R_2} \sqrt{\frac{R_2}{R_{in}} (Q_2^2 + 1) - 1}$$

To obtain  $C_1$ , consider  $C_{eq} = \frac{C_1 C_{2s}}{C_1 + C_{2s}}$

The network  $Q$  is also  $Q = \frac{1}{\omega_0 R_{2s} C_{eq}}$

$$\begin{aligned} Q &= \frac{1}{\omega_0 R_{2s}} \frac{C_1 + C_{2s}}{C_1 C_{2s}} \\ &= \frac{1}{\omega_0 R_2} \cdot C_1 C_2 \frac{(\frac{Q_2^2 + 1}{Q_2^2})}{Q_2^2} \left[ C_1 + C_2 (\frac{Q_2^2 + 1}{Q_2^2}) \right] \\ &= \frac{1}{\omega_0 R_2 C_1 C_2} (Q_2^2 C_1 + C_2 (Q_2^2 + 1)) \\ &= \frac{Q_2^2 C_1 + Q_2^2 C_2 + C_2}{C_1 Q_2} \end{aligned}$$

$$\therefore Q Q_2 C_1 = Q_2^2 C_1 + C_2 (Q_2^2 + 1)$$

$$C_1 (Q Q_2 - Q_2^2) = C_2 (Q_2^2 + 1)$$

$$\Rightarrow C_1 = \frac{C_2 (Q_2^2 + 1)}{Q Q_2 - Q_2^2}$$

To calculate L

$$Q = \frac{R_{in}}{\omega_0 L} \Rightarrow L = \frac{R_{in}}{\omega_0 Q}$$

The network  $Q$  is determined from  $Q = \frac{\omega_0}{\omega_b}$ , where  $\omega_b$  is the BW over which the transformation ratio is approx. constant.

## Transformation Ratio

$$\text{We have } \frac{R_{in}}{Q^2 + 1} = \frac{R_2}{Q_2^2 + 1}$$


$$\Rightarrow \frac{R_{in}}{R_2} \approx \frac{Q^2}{Q_2^2}$$

$$\begin{aligned} \text{Also } Q &= \frac{Q_2^2 C_1 + C_2 (Q_2^2 + 1)}{C_1 Q_2} \approx \frac{Q_2^2 C_1 + C_2 Q_2^2}{C_1 Q_2} \\ &= \left( \frac{C_1 + C_2}{C_1} \right) Q_2 \end{aligned}$$

$$\therefore \frac{Q}{Q_2} = \frac{C_1 + C_2}{C_1}$$

$$\Rightarrow \frac{R_{in}}{R_2} \approx \left( \frac{C_1 + C_2}{C_1} \right)^2 \Rightarrow R_{in} > R_2$$

## Tapped Inductor Match

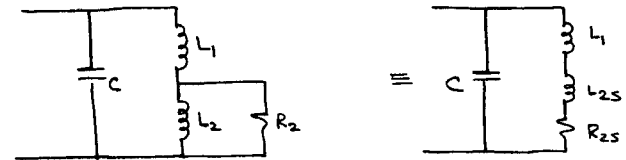

## Remark

- impractical values may be needed in the various transformation networks described so far. A double tapped resonator can be used to bring  $L \ll C$  to realizable values

Relationship between  $Q$ ,  $\omega_0$  & poles

Denominator of transfer function

$$D(s) = s^2 + \frac{G}{C}s + \frac{1}{LC} = s^2 + \omega_b s + \omega_0^2$$


$$\text{where } \omega_b = \frac{G}{C} \quad \& \quad \omega_0^2 = \frac{1}{LC}$$

The poles are roots of  $D(s)$ , i.e.,  $s^2 + \omega_b s + \omega_0^2 = 0$

$$\Rightarrow s_{1,2} = -\frac{\omega_b}{2} \pm j \sqrt{\omega_0^2 - \left(\frac{\omega_b}{2}\right)^2}$$

Distance of poles from origin
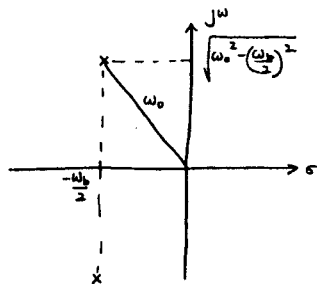
$$= \sqrt{\left(\frac{\omega_b}{2}\right)^2 + \omega_0^2 - \left(\frac{\omega_b}{2}\right)^2} = \omega_0$$



$$Q = \frac{\omega_0}{\omega_b} = \frac{\sqrt{Re^2 + Im^2}}{2 Re}$$

where  $Re = \text{real}(s_1, s_2)$   
 $Im = \text{imag}(s_1, s_2)$

Remark

- A  $Q$  can be defined for any complex conjugate pole pair.

$$\begin{aligned} |D(\omega)| &= \left| -\omega^2 + \omega_b j\omega + \omega_0^2 \right| = \sqrt{(\omega_0^2 - \omega^2)^2 + \omega_b^2 \omega^2} \\ &= \frac{\omega \omega_b}{Q} \sqrt{1 + Q^2 \left(\frac{\omega_0 - \omega}{\omega_0}\right)^2} = \omega \omega_b \sqrt{1 + Q^2 \left(\frac{\omega_0 - \omega}{\omega_0}\right)^2} \end{aligned}$$

<http://holist.stanford.edu/~CPYue>

yuechik@holist.stanford.edu

## A Typical Planar Spiral Inductor

