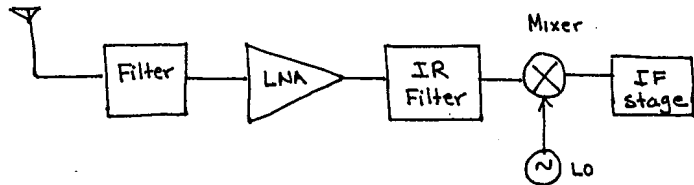


Low Noise Amplifier (LNA)

Consider the super heterodyne architecture



Note

- LNA needs to provide enough gain to overcome the noise of subsequent stages
- should add as little noise as possible
- present a specific impedance (50Ω) to the input source
- handle large signals without distortion

So the design objectives should be

- gain
- minimum noise figure
- input match
- linearity
- power consumption

Classical 2-port noise theory has several shortcomings


- source impedance for F_{min} differs from that which maximizes power
- power consumption is ignored

The assumption is that one is given a device with fixed characteristics. This is not true for the IC scenario!

MOSFET Two-port Noise Parameters


Ignoring $1/f$ noise since it is not important for high-frequency amplifiers we have
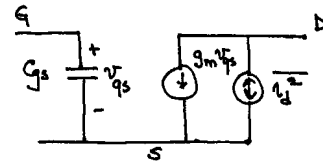
$$\overline{v_d^2} = 4KT r_{gdo} \Delta f$$



The equivalent input noise generators are given by
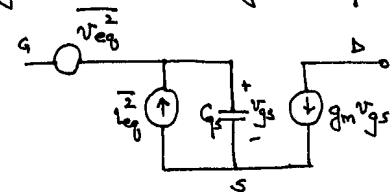
$$\begin{aligned} \overline{v_{eq}^2} &= \frac{\overline{v_d^2}}{g_m^2} \\ &= \frac{4KT r_{gdo} \Delta f}{g_m^2} \end{aligned}$$



$$\Rightarrow R_n = \frac{r_{gdo}}{g_m^2}$$

$$\text{and } \overline{v_{eq}^2} = \frac{\omega^2 C_{gs}^2}{g_m^2} \overline{v_d^2} = \omega^2 C_{gs}^2 \overline{v_{eq}^2}$$

whereby $\overline{v_{eq}^2}$ and $\overline{v_{eq}^2}$ are correlated.

Now let us introduce the induced gate noise

$$\overline{v_g^2} = 4KT \delta g_g \Delta f$$

$$\text{where } g_g = \frac{\omega^2 C_{gs}^2}{5g_{do}}$$

The gate noise is correlated with the drain noise with a correlation coefficient


$$c = \frac{v_g v_d^*}{\sqrt{\overline{v_g^2} \overline{v_d^2}}} = -0.395j \text{ for long-channel devices}$$

$$\begin{aligned} \overline{i_g^2} &= \overline{(i_{gc} + i_{gu})^2} = \overline{i_{gc}^2} + \overline{i_{gu}^2} \\ &= \underbrace{4kTs g_g |c|^2 \Delta f}_{\overline{i_{gc}^2}} + \underbrace{4kTs g_g (1-|c|^2) \Delta f}_{\overline{i_{gu}^2}} \end{aligned}$$

Now we consider the complete MOSFET noise

The correlation admittance Y_c can be calculated as
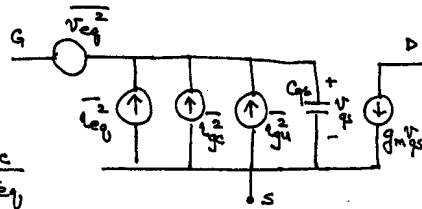
$$Y_c = \frac{i_{gc} + i_{gc}}{v_{eq}} = j\omega C_{gs} + \frac{i_{gc}}{v_{eq}}$$



$$\text{Since } v_{eq} = \frac{i_d}{g_m} \Rightarrow Y_c = j\omega C_{gs} + g_m \frac{i_{gc}}{i_d}$$

Let us examine the term $\frac{i_{gc}}{i_d}$

$$\begin{aligned} \frac{i_{gc}}{i_d} &= \frac{i_{gc} i_d^*}{i_d i_d^*} = \frac{i_{gc} i_d^*}{i_d^2} = \frac{i_{gc} i_d^*}{\sqrt{i_d^2} \sqrt{i_d^2}} \\ &= \frac{i_g i_d^*}{\sqrt{i_d^2} \sqrt{i_d^2}} \sqrt{\frac{i_g^2}{i_d^2}} = c \sqrt{\frac{i_g^2}{i_d^2}} = -j|c| \sqrt{\frac{i_g^2}{i_d^2}} \end{aligned}$$

assuming that c is a purely imaginary number

$$\sqrt{\frac{i_g^2}{i_d^2}} = \sqrt{\frac{8\omega^2 C_{gs}^2}{5r g_{do}^2}} = \frac{\omega C_{gs}}{g_{do}} \sqrt{\frac{8}{5r}}$$

$$\therefore Y_c = j\omega C_{gs} - j|c| \frac{\omega C_{gs}}{g_{do}} g_m \sqrt{\frac{8}{5r}}$$

$$\Rightarrow Y_c = j\omega C_{gs} \left(1 - \alpha |c| \sqrt{\frac{8}{5r}} \right)$$

where $\alpha = \frac{g_m}{g_{do}} = 1$ for long-channel devices
 < 1 " short-channel "

Observations

- Y_c is purely imaginary ; $G_c = 0$
- $Y_c \propto \omega C_{gs}$ (= Y_{in})
 i.e. noise figure cannot be minimized when maximizing power transfer

The uncorrelated portion of the gate noise current i_{gu}^2 gives G_u

$$G_u = \frac{\overline{i_{gu}^2}}{4kT\Delta f} = \frac{8\omega^2 C_{gs}^2}{5g_{do}} (1-|c|^2)$$

From the above analysis we have

Summary of two-port noise parameters

$$\begin{aligned} G_c &\sim 0 \\ B_c &= \omega C_{gs} \left(1 - \alpha |c| \sqrt{\frac{8}{5r}} \right) \end{aligned}$$

$$R_n = r \frac{g_{do}}{g_m^2} = \frac{r}{\alpha} \frac{1}{g_m}$$

$$G_u = \frac{8\omega^2 C_{gs}^2}{5g_{do}} (1-|c|^2)$$

From the two-port noise theory, to minimize the noise figure

$$B_{opt} = -B_c = -\omega C_{gs} \left(1 - \alpha |c| \sqrt{\frac{8}{5r}} \right)$$

$$G_{opt} = \sqrt{G_c^2 + \frac{G_u}{R_n}} = \sqrt{\frac{\delta \omega^2 C_{gs}^2}{5g_{do}} (1-|c|^2) \frac{\alpha g_m}{\gamma}}$$

$$= \alpha \omega C_{gs} \sqrt{\frac{\delta}{5\gamma} (1-|c|^2)}$$

and $F_{min} = 1 + 2R_n (G_{opt} + G_c)$

$$= 1 + \frac{2\gamma}{\alpha} \frac{1}{g_m} \cdot \alpha \omega C_{gs} \sqrt{\frac{\delta}{5\gamma} (1-|c|^2)}$$

$$= 1 + \frac{2}{\sqrt{5}} \frac{\omega}{\omega_T} \sqrt{\delta\gamma (1-|c|^2)}$$

where $\omega_T = \frac{g_m}{C_{gs}}$

Remarks

- If there was no gate current noise, i.e. $\delta = 0$ then $F_{min} = 1$. An unrealistic value \Rightarrow gate noise must exist
- increasing the correlation c would improve noise figure
- $F_{min} \propto \frac{\omega}{\omega_T}$ i.e. a technology with a higher ω_T will improve F for a given ω

Example

$\gamma = 2, \delta = 4, |c| = 0.395$

ω_T/ω	$F_{min} (dB)$
20	0.5
10	0.9
5	1.6

Summary


- For a MOSFET, the source impedance for F_{min} is inductive in nature
- The input impedance of the MOSFET is inherently capacitive
- Z_s for F_{min} unrelated to maximum power transfer

How do we provide a good match to a 50Ω source?

A straight forward approach
Common-source amplifier with shunt input resistor

Note

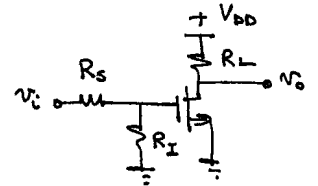R_I adds its own thermal noise and attenuates input signal by a factor of 2




For low frequencies and ignoring gate noise

$$\overline{v_o^2} = \overline{v_i^2} + \frac{g_m^2}{4} \overline{v_n^2}$$

$$+ g_m^2 R^2 \frac{\overline{v_n^2}}{4}$$
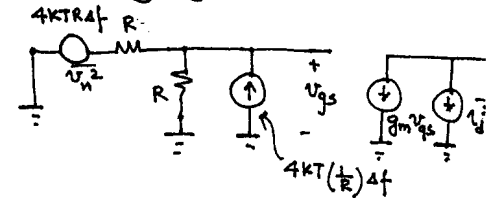
$$\overline{v_{o,R}} = \frac{g_m^2}{4} \overline{v_n^2}$$



$$\therefore F = \frac{\overline{v_o^2}}{\frac{g_m^2}{4} \overline{v_n^2}} + 2 = 2 + \frac{4kT\gamma g_{do} \Delta f}{\frac{g_m^2}{4} \cdot 4kTR \Delta f}$$

$$= 2 + \frac{4\gamma}{\alpha} \frac{1}{g_m R}$$


Another choice

Common-gate configuration

For input match require

$$R_s = \frac{1}{g_m} = 50 \Omega$$

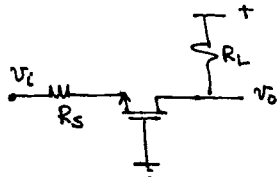By a proper choice of device size and bias current can provide the input match.




What about F?

Assuming low frequencies and ignoring gate noise

$$R_s = 1/g_m$$

$$\overline{v_o^2} = g_m^2 \frac{\overline{v_n^2}}{4} + \frac{\overline{v_s^2}}{4}$$
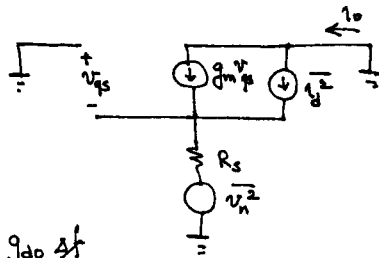
$$\text{since } G_m = \frac{g_m}{1 + g_m R_s} = \frac{g_m}{2}$$



$$\therefore F = 1 + \frac{\overline{v_s^2}}{g_m^2 \overline{v_n^2}} = 1 + \frac{4kT \gamma g_{do} \Delta f}{g_m^2 4kT R \Delta f}$$

$$= 1 + \gamma \frac{g_{do}}{g_m} = 1 + \frac{\gamma}{\alpha} \quad \text{since } \alpha = \frac{g_m}{g_{do}}$$

Example

Long-channel device $\gamma = 2/3, \alpha = 1$


$$\therefore F = 1 + \frac{2}{3} \Rightarrow 2.2 \text{ dB}$$

How can we provide a resistive input impedance without using resistors (or the MOSFET channel resistance)?

Consider a MOSFET with inductive source degeneration

$$Z_{in} = sL + \frac{1}{sC_{gs}} + \frac{g_m}{C_{gs}} L$$

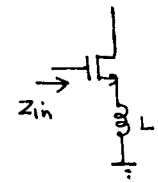At the frequency $\omega_0 = \frac{1}{\sqrt{LC_{gs}}}$



$$Z_{in} = \frac{g_m}{C_{gs}} L \quad \text{which is real}$$

i.e. at resonance the input impedance is purely resistive.

Note


This circuit provides only a narrow band input match, which is desirable in several cases.

$$\text{At resonance } Z_{in} = \frac{g_m}{C_{gs}} L = \omega_T L$$

which indicates that L is used to provide the desired input resistance. To have a desired resonance frequency an inductor is added in series with the gate.

For a general case:
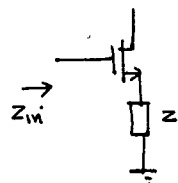
$$Z_{in}(j\omega) = \frac{1}{j\omega C_{gs}} + Z + \frac{\omega_T}{j\omega} Z$$



Therefore, capacitive degeneration contributes a negative resistance at the input

$\Rightarrow C_{sb}$ offsets the positive resistance from inductive degeneration

Example (cs amplifier)


RF LNA

Find F assuming matched conditions

$$Z_{in}(s) = sL_1 + \frac{1}{sC_{gs}} + \left(\frac{g_m}{sC_{gs}} + 1\right) sL_2$$

$$= sL_1 + \frac{1}{sC_{gs}} + sL_2 + \frac{g_m L_2}{C_{gs}}$$
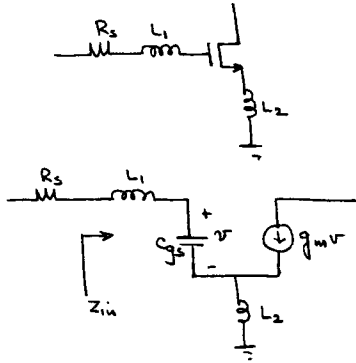
$$= s(L_1 + L_2) + \frac{1}{sC_{gs}} + \frac{g_m L_2}{C_{gs}}$$



At the resonance frequency ω_0 $Z_{in}(j\omega_0)$ is real because of matching considerations

$$\text{i.e. } j\omega_0(L_1 + L_2) + \frac{1}{j\omega_0 C_{gs}} = 0$$

$$\omega_0(L_1 + L_2) - \frac{1}{\omega_0 C_{gs}} = 0$$

$$\Rightarrow \omega_0 = \sqrt{\frac{1}{(L_1 + L_2) C_{gs}}}$$

$$\text{Also } R_s = \frac{g_m L_2}{C_{gs}} = \omega_T L_2 \quad (\omega_T = \text{unity gain frequency})$$


To determine noise factor we consider noise due to the amplifier only and then noise due to R_s

$$F = 1 + \frac{N_{oa}}{N_{ors}}$$

and we consider the output short circuit current

At high frequencies $1/f$ noise is negligible

b

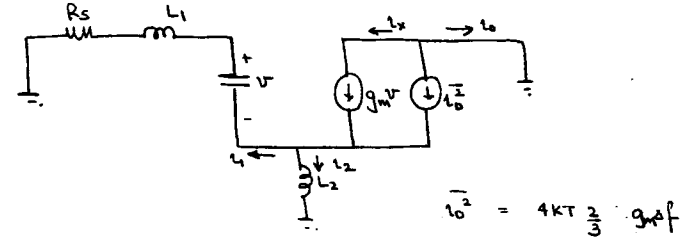

$$\overline{i_o^2} = 4KT \frac{2}{3} g_m \Delta f$$

$$g_m v + i_o = i_1 + i_2$$

$$i_1 = -j\omega_0 C_{gs} v$$

$$i_2 = \left[\frac{(R_s + j\omega_0 L_1)(-j\omega_0 C_{gs} v) - v}{j\omega_0 L_2} \right]$$

$$\therefore i_1 + i_2 = \left[-j\omega_0 C_{gs} - \frac{(R_s + j\omega_0 L_1)(j\omega_0 C_{gs} + 1)}{j\omega_0 L_2} \right] v$$

$$= - \left[\frac{-\omega_0^2 L_2 C_{gs} + R_s j\omega_0 C_{gs} - \omega_0^2 L_1 C_{gs} + 1}{j\omega_0 L_2} \right] v$$

$$= - \frac{R_s C_{gs}}{L_2} v = -g_m v \quad \text{from matching}$$


$$\therefore g_m v + i_o = -g_m v$$

$$\Rightarrow v = -\frac{i_o}{2g_m} \quad \& \quad i_x = g_m v = -\frac{i_o}{2}$$

$$\therefore i_o = i_o + i_x = i_o - \frac{i_o}{2} = \frac{1}{2} i_o$$

$$\Rightarrow \overline{i_o^2} = \frac{1}{4} \overline{i_o^2} = \frac{1}{4} \cdot \frac{28}{3} KT g_m \Delta f = \frac{2}{3} KT g_m \Delta f$$

output noise due to R_s

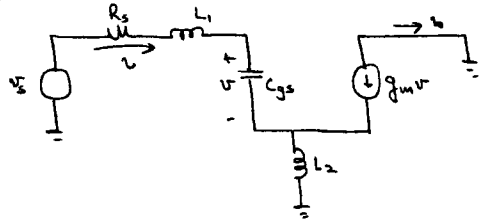

$$i = \frac{v_s}{2R_s} \quad \text{due to the match condition}$$

$$\therefore v = \frac{1}{j\omega_0 C_{gs}} \cdot \frac{1}{2R_s} v_s$$

$$\text{and } i_o = -\frac{1}{j\omega_0 C_{gs}} \frac{g_m}{2R_s} v_s$$


$$\Rightarrow \overline{i_o^2} = \frac{1}{\omega_0^2 C_{gs}^2} \frac{g_m^2}{4R_s^2} \overline{v_s^2} = \frac{1}{\omega_0^2 C_{gs}^2} \frac{g_m^2}{R_s^2} \cdot K T R_s \Delta f$$

$$\begin{aligned} \therefore F &= 1 + \frac{\frac{2}{3} K T \frac{g_m}{\Delta f}}{\frac{1}{\omega_0^2 C_{gs}^2} \frac{g_m^2}{R_s} \cdot K T \Delta f} \\ &= 1 + \frac{2}{3} \frac{\omega_0^2 C_{gs}^2 R_s}{g_m} = 1 + \frac{2}{3} \frac{1}{\left(\frac{g_m}{C_{gs} R_s}\right) \frac{L_2}{L_1 + L_2}} \\ &= 1 + \frac{2}{3} \frac{L_2}{L_1 + L_2} = 1 + \frac{2}{3} \frac{1}{1 + L_1/L_2} \end{aligned}$$

Remark

- F decreases as L_1 increases

Overall stage transconductance

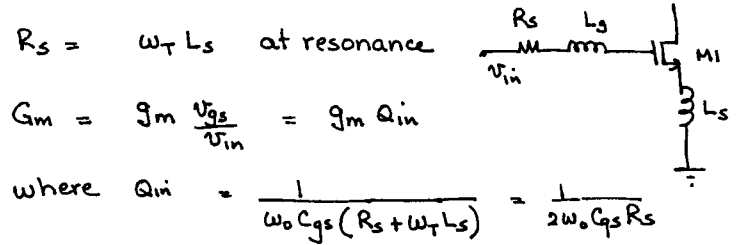

$$R_s = \omega_T L_s \quad \text{at resonance}$$

$$G_m = g_m \frac{v_{gs}}{v_{in}} = g_m Q_{in}$$

$$\text{where } Q_{in} = \frac{1}{\omega_0 C_{gs} (R_s + \omega_T L_s)} = \frac{1}{2\omega_0 C_{gs} R_s}$$


$$\therefore G_m = \frac{g_m}{2\omega_0 C_{gs} R_s} = \frac{g_m}{C_{gs}} \frac{1}{2\omega_0 R_s} = \frac{\omega_T}{2\omega_0 R_s}$$

i.e. the overall transconductance is independent of the device g_m

Analysis of Common-source LNA (including gate noise)

Contribution due to i_g^2

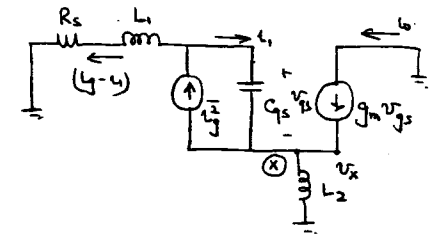First let us determine the output current i_o due to a gate current i_g



$$v_{gs} = \frac{L_1}{j\omega_0 C_{gs}}$$

$$v_x = (R_s + j\omega_0 L_1)(i_g - i) - \frac{L_1}{j\omega_0 C_{gs}}$$

Using KCL at \otimes we have

$$i_g - i - \frac{g_m L_1}{j\omega_0 C_{gs}} + \left[(R_s + j\omega_0 L_1)(i_g - i) - \frac{L_1}{j\omega_0 C_{gs}} \right] \frac{1}{j\omega_0 L_2} = 0$$

$$\therefore i_g \left[1 + \frac{R_s + j\omega_0 L_1}{j\omega_0 L_2} \right] = i \left[1 + \frac{g_m}{j\omega_0 C_{gs}} + \frac{R_s + j\omega_0 L_1}{j\omega_0 L_2} - \frac{1}{\omega_0^2 L_2 C_{gs}} \right]$$

Note that $\frac{1}{\omega_0^2 L_2 C_{gs}} = \frac{1}{(L_1+L_2)C_{gs}} = 1 + \frac{L_1}{L_2}$

and $\frac{R_s C_{gs}}{L_2} = g_m \Rightarrow \frac{R_s}{L_2} = \frac{g_m}{C_{gs}}$

$$\therefore \lg \left[1 + \underbrace{\frac{R_s}{j\omega_0 L_2}}_{\frac{g_m}{j\omega_0 C_{gs}}} + \frac{L_1}{L_2} \right] = \lg \left[1 + \frac{g_m}{j\omega_0 C_{gs}} + \frac{R_s}{j\omega_0 L_2} + \frac{L_1}{L_2} - \cancel{\left(\frac{1+L_1}{L_2} \right)} \right]$$

$$\lg \left[\frac{1}{\omega_0^2 L_2 C_{gs}} - j \frac{g_m}{\omega_0 C_{gs}} \right] = \frac{2g_m}{j\omega_0 C_{gs}} l_1$$

$$l_0 = g_m v = \frac{g_m l_1}{j\omega_0 C_{gs}} = \frac{l_1}{2} \cdot \frac{g_m}{\omega_0 C_{gs}} \left[\frac{1}{\omega_0 g_m L_2} - j \right]$$

But $\frac{1}{\omega_0 g_m L_2} = \frac{1}{\omega_0 R_s C_{gs}} = Q_L$

$$\therefore l_0 = \frac{l_1}{2} \cdot \frac{g_m}{\omega_0 C_{gs}} [Q_L - j]$$

Now consider the correlation i.e. l_d & l_0 are correlated

Recall $l_0 = \frac{1}{2} l_d$

Correlation $\Rightarrow \overline{l_0^2} = \left| \frac{l_d}{2} + \frac{l_{gc}}{2} \frac{g_m}{\omega_0 C_{gs}} (Q_L - j) \right|^2$
 $= \left| 1 + \frac{g_m}{\omega_0 C_{gs}} (Q_L - j) \frac{l_{gc}}{l_d} \right|^2 \frac{l_d^2}{4}$

Also recall that $\frac{l_{gc}}{l_d} = -j|c| \sqrt{\frac{l_d^2}{l_d^2}}$

when c is purely imaginary

and $\sqrt{\frac{l_d^2}{l_d^2}} = \frac{\omega C_{gs}}{g_m} \sqrt{\frac{\delta \alpha^2}{5r}}$

$$\begin{aligned} \therefore \overline{l_0^2} &= \left| 1 - \frac{jg_m}{\omega_0 C_{gs}} (Q_L - j) j|c| \frac{\omega_0 C_{gs}}{g_m} \sqrt{\frac{\delta \alpha^2}{5r}} \right|^2 \frac{l_d^2}{4} \\ &= \underbrace{\left[\left(1 - |c| \sqrt{\frac{\delta \alpha^2}{5r}} \right)^2 + |c|^2 Q_L^2 \frac{\delta \alpha^2}{5r} \right]}_{\mathcal{K}} \frac{l_d^2}{4} \end{aligned}$$

So we have the contribution due to the drain and correlat part of the gate noise at the output

$$\overline{l_0^2} = \mathcal{K} \frac{l_d^2}{4} = \mathcal{K} \frac{4KT r g_{do}}{4}$$

Now determine the contribution due to the uncorrelated part

$$\begin{aligned} \overline{l_0^2} &= \frac{l_{gu}^2}{4} \frac{g_m^2}{\omega_0^2 C_{gs}^2} (Q_L^2 + 1) \\ &= \frac{1}{4} 4KTS \frac{\omega_0^2 C_{gs}^2}{5g_{do}} (1 - |c|^2) \frac{g_m^2}{\omega_0^2 C_{gs}^2} (Q_L^2 + 1) \\ &= \frac{1}{4} 4KT \frac{\delta}{5r g_{do}^2} \frac{g_m^2}{\omega_0^2 C_{gs}^2} (1 - |c|^2) (Q_L^2 + 1) r g_{do} \\ &= \underbrace{\frac{\delta \alpha^2}{5r} (1 - |c|^2) (Q_L^2 + 1)}_{\mathcal{F}} \frac{l_d^2}{4} \end{aligned}$$

The output noise due to r_d & l_g is

$$\overline{i_{o,d,g}^2} = 4kTY \chi \frac{g_{do}}{4}$$

$$\text{where } \chi = \gamma + \xi = 1 - 2|c| \sqrt{\frac{\delta \alpha^2}{5Y} + \frac{\delta \alpha^2}{5Y} (1 + \theta_L^2)}$$

$$\begin{aligned} \therefore F &= 1 + \frac{4kTY \chi g_{do}/4}{\frac{1}{\omega_0^2 C_s^2} \frac{g_m^2}{4R_s^2} \cdot 4kTR_s} \\ &= 1 + \omega_0^2 \frac{C_s^2}{g_m^2} R_s \gamma \chi g_{do} \\ &= 1 + \left(\frac{\omega_0}{\omega_T}\right)^2 R_s \gamma \chi g_{do} \end{aligned}$$

$$\text{Note that } g_{do} Q_L = \frac{g_m}{\alpha} \frac{1}{\omega_0 R_s C_s} = \frac{\omega_T}{\alpha \omega_0 R_s}$$

whereby

$$F = 1 + \frac{\gamma}{\alpha} \frac{\chi}{Q_L} \left(\frac{\omega_0}{\omega_T}\right)$$

Remarks

- χ contains a constant term and a term $\propto Q_L^2$

$\Rightarrow F$ contains a term in Q_L , $\frac{1}{Q_L}$

\Rightarrow minimum of F exists for a particular Q_L

We will now consider the power consumption in the amplifier. To do this revisit the short-channel MOSFET I-V characteristics.

$$\text{In saturation: } I_d = W C_{ox} v_{sat} \frac{(V_{gs} - V_T)^2}{V_{gs} - V_T + L E_{sat}}$$

$$\begin{aligned} \therefore I_d &= \frac{W}{L} C_{ox} \frac{v_{sat}}{E_{sat}} \frac{(V_{gs} - V_T)^2}{1 + \frac{V_{gs} - V_T}{L E_{sat}}} \\ &= \frac{\mu_{eff}}{2} \frac{W}{L} C_{ox} \frac{(V_{gs} - V_T)^2}{1 + p} \end{aligned}$$

$$\text{where } v_{sat} = \frac{\mu_{eff}}{2} E_{sat} \text{ and } p = \frac{V_{gs} - V_T}{L E_{sat}}$$

$$\text{Calculate } g_m = \frac{\partial I_d}{\partial V_{gs}} = \frac{\mu_{eff}}{2} \frac{W}{L} C_{ox} \left[\frac{2(V_{gs} - V_T)}{1 + p} - \frac{(V_{gs} - V_T)^2}{(1 + p)^2} \frac{1}{L E_{sat}} \right]$$

$$\Rightarrow g_m = \frac{\mu_{eff}}{2} \frac{W}{L} C_{ox} (V_{gs} - V_T) \left[\frac{2}{1 + p} - \frac{p}{(1 + p)^2} \right]$$

$$= \mu_{eff} \frac{W}{L} C_{ox} (V_{gs} - V_T) \frac{1 + p/2}{(1 + p)^2}$$

Calculate power consumption

$$P_d = V_{DD} I_d = V_{DD} W C_{ox} v_{sat} \frac{(V_{gs} - V_T)^2}{(V_{gs} - V_T) + L E_{sat}}$$

$$\begin{aligned} \text{Since } C_s &\approx \frac{2}{3} W L C_{ox} \Rightarrow Q_L = \frac{1}{\omega_0 R_s C_s} = \frac{1}{\omega_0 R_s \cdot \frac{2}{3} W L C_{ox}} \\ &= \frac{3}{2} \frac{1}{\omega_0 R_s W L C_{ox}} \end{aligned}$$

$$\text{Since } P_d = V_{DD} W L C_{ox} E_{sat} v_{sat} \frac{p^2}{1 + p}$$

$$\Rightarrow \frac{1}{W L C_{ox}} = \frac{V_{DD} E_{sat} v_{sat}}{P_d} \frac{p^2}{1 + p}$$

$$\begin{aligned} \text{which gives } Q_L &= \frac{3}{2} \frac{1}{P_d} \frac{V_{DD} E_{sat} v_{sat}}{\omega_0 R_s} \frac{p^2}{1 + p} \\ &= \frac{P_0}{P_d} \frac{p^2}{1 + p} \end{aligned}$$

$$\text{Where } P_0 = \frac{3}{2} \frac{V_{dd} E_{sat} v_{sat}}{\omega_0 R_S}$$

Observations

- v_{sat} & E_{sat} are physical (technological) parameters
- V_{dd} , ω_0 , R_S are design specifications

⇒ P_0 is a constant i.e. independent of bias

Now express ω_T in terms of device parameters

$$\begin{aligned} \omega_T &= \frac{g_m}{C_{gs}} = \frac{g_m}{\frac{2}{3} W L C_{ox}} = \frac{3}{2} \mu_{eff} \frac{V_{gs} - V_T}{L^2} \frac{1+p/2}{(1+p)^2} \\ &= \frac{3}{2} \mu_{eff} \frac{V_{gs} - V_T}{L^2} \alpha \end{aligned}$$

$$\text{Since } \alpha = \frac{g_m}{g_{do}} = \frac{1+p/2}{(1+p)^2}$$

$$\therefore \omega_T = \frac{3}{2} \underbrace{\frac{\mu_{eff} v_{sat}}{E_{sat}}}_p \frac{V_{gs} - V_T}{L} \alpha = \frac{3 \alpha p v_{sat}}{L}$$

Now we can rewrite the expression for F

$$\begin{aligned} F &= 1 + \frac{\gamma}{\alpha} \frac{\chi}{Q_L} \left(\frac{\omega_0}{\omega_T} \right) \\ &= 1 + \frac{\gamma}{\alpha} \frac{\chi}{\frac{P_0}{P_d} \frac{p^2}{1+p}} \cdot \frac{\omega_0}{\frac{3 \alpha p v_{sat}}{L}} \\ &= 1 + \frac{\gamma \omega_0 L}{3 v_{sat}} \frac{\chi}{\frac{P_0}{P_d} \frac{p^2}{1+p} \alpha p} \\ &= 1 + \frac{\gamma \omega_0 L}{3 v_{sat}} P(p, P_d) \end{aligned}$$

$$\text{where } P(p, P_d) = \frac{\chi}{\frac{P_0}{P_d} \frac{p^2}{1+p} \alpha^2 p}$$

$$= \frac{1 - 2|c| \alpha \sqrt{\frac{\delta}{5\gamma}} + \frac{\delta \alpha^2}{5\gamma} \left[1 + \left(\frac{P_0}{P_d} \frac{p^2}{1+p} \right)^2 \right]}{\frac{P_0}{P_d} \frac{p^2}{1+p} p \frac{(1+p/2)^2}{(1+p)^4} \alpha^2}$$

$$\therefore P(p, P_d) = \frac{P_d}{P_0} \left[1 - 2|c| \frac{(1+p/2)}{(1+p)^2} \sqrt{\frac{\delta}{5\gamma}} + \frac{\delta}{5\gamma} \frac{(1+p/2)^2}{(1+p)^4} \right] + \frac{\delta}{5\gamma} \frac{P_0}{P_d} \frac{p^4}{(1+p)^2} \cdot \frac{(1+p/2)^2}{(1+p)^4}$$

$$\frac{p^3 (1+p/2)^2 (1+p)}{(1+p)^6}$$

$$= \frac{P_d}{P_0} \left[(1+p)^6 - 2|c| \sqrt{\frac{\delta}{5\gamma}} (1+p)^4 (1+p/2) + \frac{\delta}{5\gamma} (1+p/2)^2 (1+p)^2 \right] + \frac{P_0}{P_d} \frac{\delta}{5\gamma} p^4 (1+p/2)^2$$


$$\frac{p^3 (1+p/2)^2 (1+p)}{(1+p)^6}$$

Note F is a function of two variables p & P_d .

Therefore, we can fix P_d and find p for the minimum F.

OR

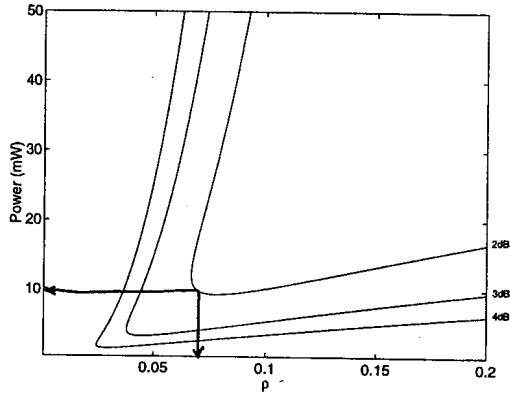Given F we can find the minimum P_d and the corresponding p



Constant NF contours can be plotted for different values of P_d and p as shown above.

Example For NF = 2dB $P_d(\min) \approx 10 \text{ mW}$, $p = 0.07$
 For NF = 4dB $P_d(\min) \approx 1.5 \text{ mW}$, $p = 0.025$

For a special case $p \ll 1$, we can derive closed-form expressions that allow us to minimize F for a given P_d .

Assume $p \ll 1$ then

$$P(p, P_d) \approx \frac{P_d}{p^3} \left[1 - 2|c| \sqrt{\frac{\delta}{5\gamma} + \frac{\delta}{5\gamma}} + \frac{P_o}{P_d} \frac{\delta}{5\gamma} p^4 \right]$$

Recall $F = 1 + \frac{\gamma \omega_o L}{3 \sqrt{3} \text{sat}} P(p, P_d)$

So minimize $P(p, P_d)$ for a given $P_d \Rightarrow \frac{\partial P(p, P_d)}{\partial p} = 0$

$$\Rightarrow \frac{P_d}{P_o} \left[1 - 2|c| \sqrt{\frac{\delta}{5\gamma} + \frac{\delta}{5\gamma}} \right] \left(-\frac{3}{p^4} \right) + \frac{P_o}{P_d} \frac{\delta}{5\gamma} = 0$$

$$\therefore \frac{P_o}{P_o} \frac{\delta}{5\gamma} p^4 = \frac{P_o}{P_o} 3 \left[1 - 2|c| \sqrt{\frac{\delta}{5\gamma} + \frac{\delta}{5\gamma}} \right]$$

$$\Rightarrow P_{opt}^2 = \frac{P_d}{P_o} \sqrt{\frac{15\gamma}{\delta}} \sqrt{1 - 2|c| \sqrt{\frac{\delta}{5\gamma} + \frac{\delta}{5\gamma}}}$$

$$\text{and } Q_{L, opt} = \frac{P_o}{P_d} \frac{P_{opt}^2}{1 + P_{opt}^2} \approx \frac{P_o}{P_d} P_{opt}^2$$

$$= \sqrt{\frac{15\gamma}{\delta}} \sqrt{\left(1 + \frac{\delta}{5\gamma}\right) - 2|c| \sqrt{\frac{\delta}{5\gamma}}}$$

Substitute $\gamma = 2$, $\delta = 4$ & $|c| = 0.395$ then
 $Q_{L, opt} \approx 2.6$

From $Q_{L, opt}$ we have $\chi_{opt} = 1 - 2|c| \sqrt{\frac{\delta \alpha^2}{5\gamma} + \frac{\delta \alpha^2}{5\gamma} (1 + Q_{L, opt}^2)}$

where $\alpha = \frac{1 + p/2}{(1+p)^2} \approx 1$ i.e. a long-channel device

$$\therefore \frac{\chi_{opt}}{Q_{L, opt}} \approx 1.4 \Rightarrow F_{min} = 1 + 1.4 \frac{\gamma}{\alpha} \left(\frac{\omega_o}{\omega_T} \right)$$

For a long-channel device $\gamma = 2/3$, $\delta = 4/3$, $|c| = 0.395$

$$Q_{L, opt} \approx 3.8 \quad \text{since } \frac{\delta}{\gamma} = 2.$$

$$\therefore F_{min} = 1 + 1.4 \left(\frac{2}{3} \right) \left(\frac{\omega_o}{\omega_T} \right) = 1 + 0.93 \left(\frac{\omega_o}{\omega_T} \right)$$

For short-channel devices we have

$$F_{min} > 1 + 0.93 \left(\frac{\omega_o}{\omega_T} \right)$$

Once $Q_{L,opt}$ is known then ω for the optimum device can be calculated

$$Q_L = \frac{1}{\omega_0 R_s C_{gs}} = \frac{1}{\omega_0 R_s \frac{2}{3} \omega L C_{ox}}$$

$$\therefore \omega_{L,opt} = \frac{3}{2} \frac{1}{L C_{ox} R_s Q_{L,opt}} \approx \frac{1}{3 \omega_0 L C_{ox} R_s}$$

assuming $Q_{L,opt} \approx 4.5$

Remarks

- absolute minimum F is the transistor F_{min} :

$$F_{min} = 1 + \frac{2}{\sqrt{5}} \frac{\omega}{\omega_T} \sqrt{\gamma \delta (1 - |c|^2)} = 1 + 2.3 \left(\frac{\omega}{\omega_T} \right)$$

- For the common-source LNA

$$F_{min} = 1 + 1.4 \frac{\gamma}{\alpha} \left(\frac{\omega}{\omega_T} \right)$$

Example $\omega/\omega_T = \frac{1}{10}$, $\gamma = 2$, $\alpha \approx 1$

$$F_{min} (\text{device}) = 1 + 2.3 \left(\frac{1}{10} \right) = 1.23 \quad (0.9 \text{ dB})$$


$$F_{min} (\text{CS amp}) = 1 + 1.4 \frac{2}{1} \left(\frac{1}{10} \right) = 1.28 \quad (1.1 \text{ dB})$$

i.e. excellent noise figures are possible.

Remark

For narrowband applications it is advantageous to tune out the output capacitance for improved gain.

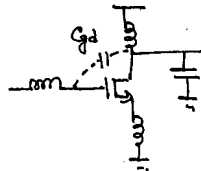C_{gd} can cause problems due to its effect on the input impedance




C_{gd} causes several problems by coupling the input and output tuned circuits

- loading of the output tank
- detuning of the tank
- potential for instability

To avoid this problem decouple the input and output by a cascode device

Hence, the overall LNA design is

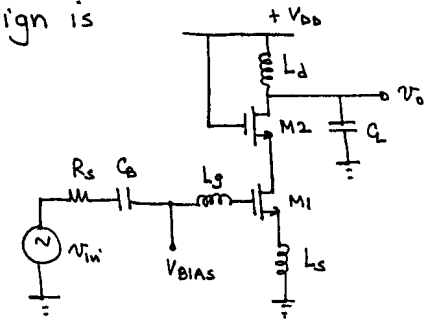M_2 reduces the effect of M_1 's C_{gd} and the interaction of the input and output tuned circuits



L_d resonates with

capacitance at drain of M_2

\Rightarrow increased gain & bandpass filtering

C_b is a blocking capacitor that allows M_1 to be biased properly. It should have a negligible effect at the signal frequency.

Note C_b is in series with C_{gs} , so the effective series capacitance is

$$\frac{1}{C_{eff}} = \frac{1}{C_b} + \frac{1}{C_{gs}} \approx \frac{1}{C_{gs}} \quad \text{for } C_b \gg C_{gs}$$

If M_2 and M_1 are sized the same then the Miller capacitance at the input is $2C_{gd}$ in parallel with C_{gs}