

Inductor

Defining relationship : $V_L = L \frac{di}{dt}$, Also $\frac{di}{dt} = \frac{1}{L} V_L$

This tells us that...

- 1) with a constant applied voltage, the rate of change in current w.r.t. time is constant; i.e., A straight line.

V_{in} ind-in gnd PULSE(0 1v 0ns 1ps 1ps 25ms 50ms)

L_1 ind-in tie 1mh


R_1 tie gnd 0.001 ; sense resistor to determine current control

tran 1us 10ms

plot $v(tie)/.001$; plot current through inductor

• endc

• end

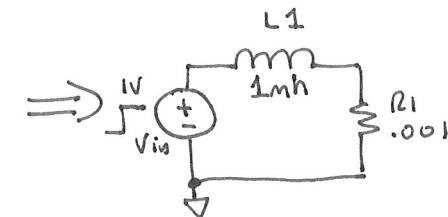

$$\text{if } L = 1 \times 10^{-3} \text{ H}$$

$$V_{in} = 1 \text{ V}$$

$$\frac{di}{dt} = \frac{1}{L} V_L \quad (V_{in} \approx V_L)$$

- 2) If the current through the inductor is not changing, the voltage across the inductor is zero. ∴ The inductor must be a short circuit to DC,

$$\frac{di}{dt} \left(\frac{A}{s}\right) = \frac{1}{1 \times 10^{-3}} \frac{V_s}{A} \cdot 1 \text{ V}$$

$$\frac{di}{dt} \left(\frac{A}{s}\right) = 1000 \frac{A}{s} \text{ or } \frac{10A}{10ms}$$

