## Using Spice for KCL Analysis

Figure **??** is a circuit analyzed by hand earlier. We shall now create a Spice netlist for this circuit and simulate it.

Figure 1: KVL Spice problem.

The Spice netlist for the circuit above is placed in a nornal text file with whatever editor you like. It looks like this:

```
.title class example problem (kcl)
***** netlist follows *****
       z gnd
                      10
v1
rl
       У
             Z
                      5
       gnd y
v x
r2
                      10
r3
                      10
r4
       gnd
              х
                      10
i1
              У
                       2
       х
***** netlist done *****
.control
       set numdgt=2
       op
       echo Node voltages:
       print line v(x) v(y) v(z)
       echo
       show vl
       quit
.endc
.end
```

The body of the netlist is shown below. A review of its fonnat is given below. Note that nodes Vx, Vy, and Vz have been abbreviated x, y and z respectively.

```
type of element and its reference designation
r = resistor
v = voltage source
i = current source
node to which the positive terminal of element is connected
node to which the negative terminal of element is connected
       value of the element
z
              gnd
v1
                     10
rl
                     5
       У
              z
                     10
r2
       gnd
              У
                     10
r3
       у
              х
r4
       gnd
              х
                     10
i1
                     2
       х
              у
```

Spice is involked on the file kcl1.sp at the Unix prompt by typing:

ngspice kcl1.sp > output

The results from the simulation are in the file *output*.

```
Circuit: class example problem (kcl)
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
No. of Data Rows : 1
node voltages:
v(x) = -5.7e+00
v(y) = 8.57e+00
v(z) = 1.00e+01
Vsource: Independent voltage source
     device
                                    v 1
  dc
acmag
pulse -
sine -
sin -
exp -
pwl -
sffm -
am -
trnoise -
trrandom -
i
p
          dc
                                    10
                                      0
                          -0.285714
                             2.85714
ngspice-21plus done
```