

In Class Problems

- KVL Analysis

In the circuit in figure ??, determine the current I_x , the voltage V_{r1} and the power dissipated in the -6 volt source.

Figure 1: KVL problem.

- Power calculation

Determine if the potatoes are generating or dissipating power.

Figure 2: Power problem.