

ECE112 - An Introduction to Electrical Engineering

Roger Traylor

In class Problem

Find the equivalent resistance of the network

Box

Figure 1: Go figure.