

## Spice HW Example

Print this page out. On that page, write just the SPICE netlist for the schematic shown in figure ?? in the shaded area. Using the template file given on the website, enter your netlist into a file named "probXX.sp", where XX is the problem number.

Run the simulator and redirect the output into another file:

```
ngspice prob<XX>.sp > prob<XX>.sp.results
```

Print out the results file by typing:

```
a2ps -P <printer_name> prob<XX>.sp.results
```

and paste the contents of the results file onto this page also. You must include the header timestemp.

Figure 1: Spice problem 1.

Result file printed from a2ps:

```
Circuit: example problem

Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

No. of Data Rows : 1
node voltages:
node voltages:
v(a) = 1.50e+01
v(b) = -5.0e+00
v(c) = 5.00e+00
v(d) = 7.00e+00
v(e) = 1.20e+01
```

Your netlist:

```
.title netlist
v1      gnd    e      -12
r1      gnd    a      30
r2      b      c      20
r3      e      d      10
v2      b      a      -20
v3      c      d      -2
```