

## Voltage dividers

Often, two resistors are put in series to develop a voltage that is some fraction of the voltage applied across them. Such an arrangement is called a *voltage divider*.

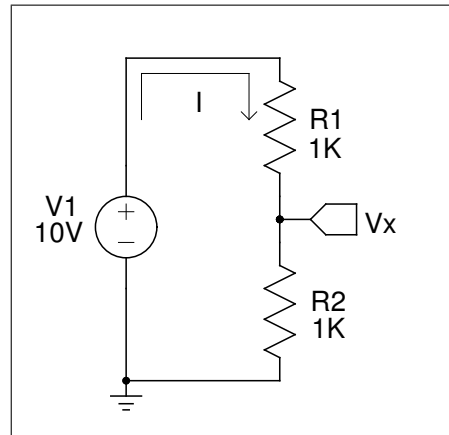


Figure 1: Voltage divider.

To solve for  $V_x$  in the general case of a voltage divider:

We know:  $V_x = I \times R_2$ , so first solve for I

$$-V + I_{R_1} + I_{R_2} = 0 \quad (\text{the KVL loop equation for the circuit})$$

$$I(R_1 + R_2) = V$$

$$I = (V / (R_1 + R_2))$$

Now, knowing I, multiply by  $R_2$  to get  $V_x$ .

$$V_x = (V / (R_1 + R_2)) \times R_2, \text{ or}$$

$$V_x = \frac{R_2}{R_1 + R_2} \times V_1$$

This is the general form for determining the voltage created by a voltage divider.