

Name: _____

Student ID# _____


KEY

Check one box:

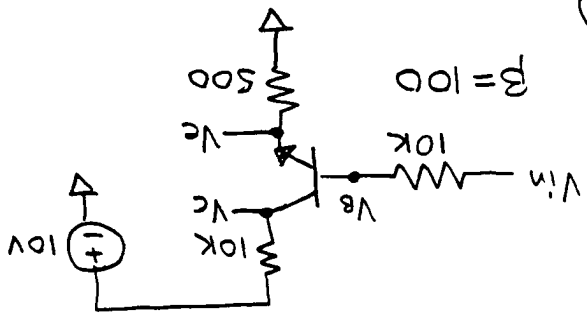- Problems 7 and 8 are to be graded and are to replace my midterm exam.
- Only grade problems 1 - 6.

If neither box is checked, only problems 1 thru 6 will be graded and will count only as a final exam.

[12] 1. For the schematic below, a set of conditions are described. For the condition given, circle the correct region of operation.



(2 pts each)

- a) $V_C = 10V$
- b) $V_{CE} = 1.4V, I_C = \beta I_B$
- c) $V_{BE} = -0.7V, V_{CE} = 10V$
- d) $I_E \neq I_B(\beta + 1), V_{BE} = 0.7V$
- e) $I_B > \phi, V_E = 0.7V, V_C = 0.9V$
- f) $I_B = 2\mu A, I_C = 100\mu A$

CIRCLE ONE


- OFF SATURATED ACTIVE FWD.
- OFF SATURATED ACTIVE FWD.
- OFF SATURATED ACTIVE FWD.
- OFF SATURATED ACTIVE FWD.
- OFF SATURATED ACTIVE FWD.

[30] 2. For the circuit below find:

- [10] a) I_B
- [2] b) I_C
- [5] c) I_E
- [3] d) V_C

- [3] e) V_{out}
- [5] f) V_{CE}

[2] g) Approximate gain of amplifier

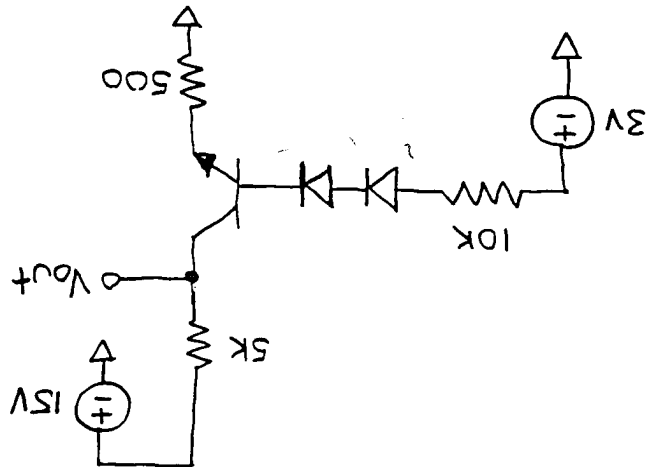

- Transistor beta (β) = 150
- Diode drops (V_D) = 0.7V
- Transistor is in active forward region of operation

$$-3 + 10000I_B + 1.4 + 0.7 + (151)5000I_B = 0$$

g) $I_C = 10.53 \mu A$

b) $I_C = 1.58 \mu A$

c) $I_E = 1.59 \mu A$

d) $V_C = I_E(5200) = 0.795V$

e) $V_{out} = 1.5 - I_C(5200) = 7.1V$




f) $V_C - V_E = V_{CE} = 6.3V$

g) $gain \approx \frac{I_C}{I_B} = \frac{10.53}{1.58} = 6.67$

(minus sign)
opt: m)



- [5] 3. Using the truth table below, do the following:
 [5] a) draw the unminimized schematic diagram that implements the function given by the truth table.
 [5] b) minimize the function with a K-map.
 [5] c) draw the minimized schematic diagram.

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

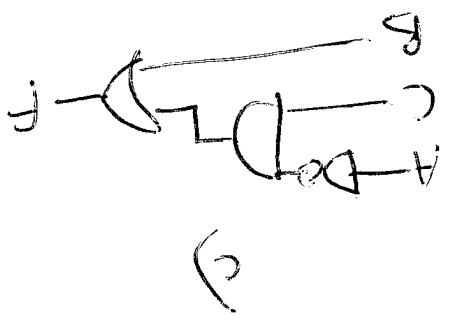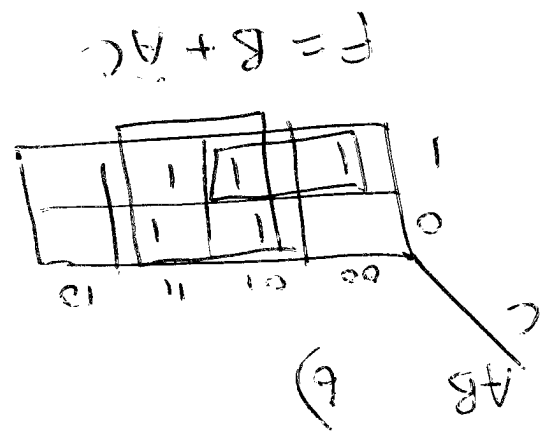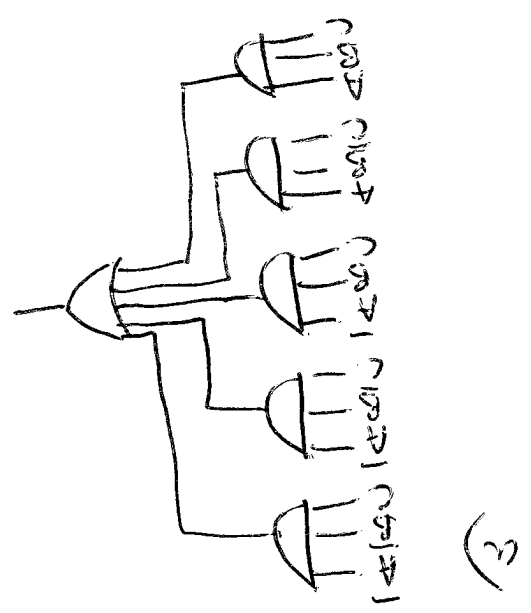


[25]6. A digital system has three inputs labeled A, B and C. They are binary representations of the decimal numbers 0 through 7. Design the digital logic necessary to illuminate a light that indicates if the input represents a number that is either even (zero is even) or is divisible by three. Show your K-map. Show your logic schematic.

INPUT ₀	INPUT ₁	INPUT ₂	OUTPUT
A	B	C	
0	0	0	
1	0	0	
2	0	1	
3	0	1	
4	1	0	
5	1	0	
6	1	1	
7	1	1	

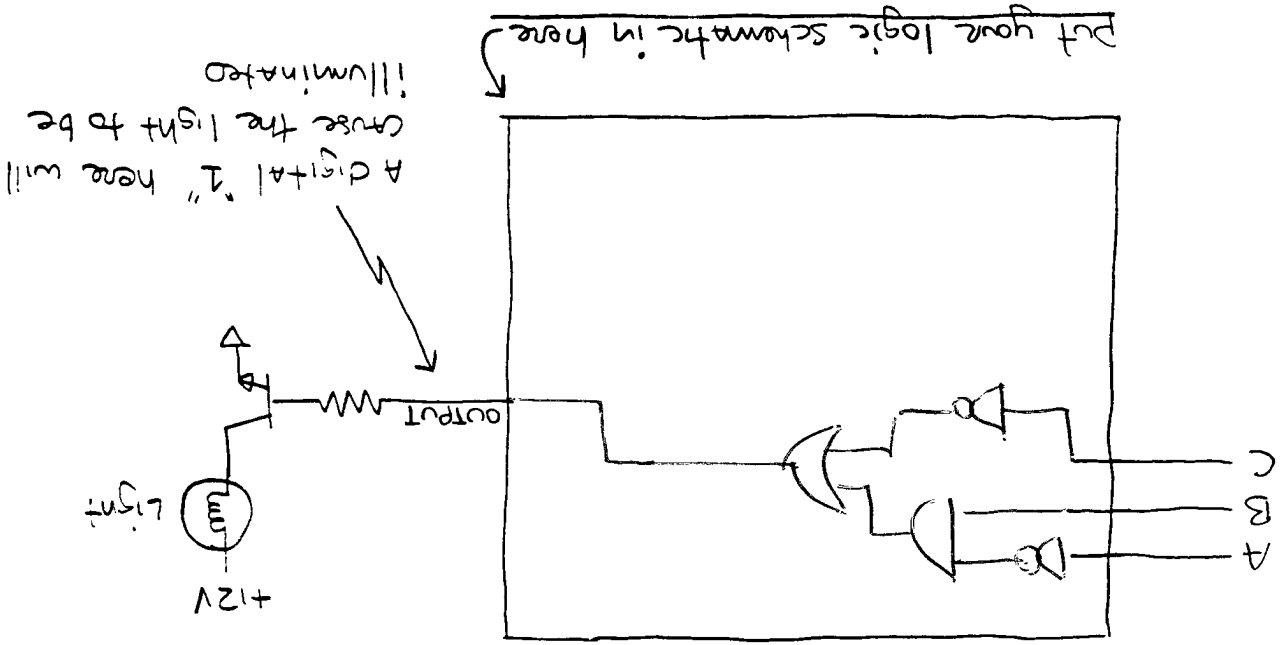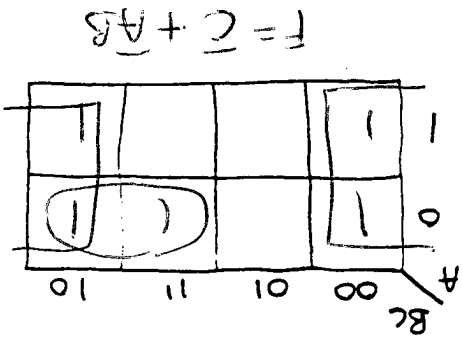

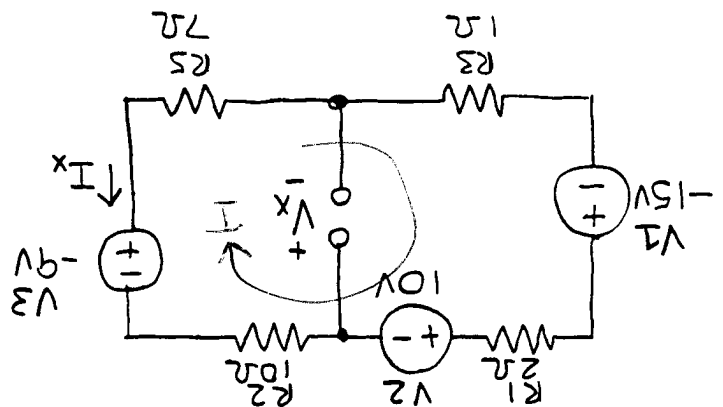[40] 7. (OPTIONAL - MIDTERM REPLACEMENT PROBLEM)



For the circuit above, find

- a) I_x
- b) V_x
- c) Power supplied by R_5
- d) Power generated by V_3

$$15 + 2I + 10 + 10I + 9 + 8I = 0$$

$$20I = -34$$

$$I = -1.7A$$

$$I_x = 1.7A$$

$$-V_x - 10 + 1.7(2) - 15 + 1.7 = 0$$

$$-V_x = +19.90$$

$$V_x = -19.9V$$

$$P_{R5} = 1.7^2 \cdot 7 = -20.23W$$

$$P_{V3} = 1.7(-9) = -15.3W \text{ dissipated}$$


$$P_{V3} = 15.3W \text{ generated}$$

[60] 8, (OPTIONAL - MIDDLEM REPLACEMENT PROBLEM)

For the circuit below, find:

- a) V_a
- b) V_b

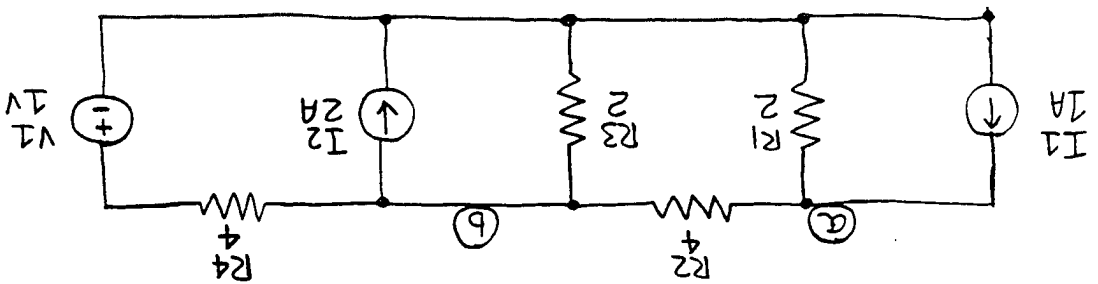- c) Power dissipated by 1A current source
- d) Power dissipated by 1V voltage source



KVL @ x: $1 - I_1 - I_2 = 0 + 15$

$1 - \frac{V_x}{2} - \frac{V_x - V_y}{4} = 0 + 10$

$4 - 2V_x - V_x + V_y = 0$

$-3V_x + V_y = -4$ ①

Sub into ①: $-3(7+4V_y) + V_y = -4$

$-21 - 12V_y + V_y = -4$

$-11V_y = 17$

$V_y = -\frac{17}{11}$

② $V_y = -1.545V$

$\frac{V_x - V_y}{4} - \frac{V_y}{2} - 2 = -\frac{V_x - 1}{4} = 0 + 10$

$V_x - V_y - 2V_y - 8 - V_y + 1 = 0$

$-4V_y + V_x = 7$ ②

$V_x = 7 + 4V_y$

$V_x = 7 + 4(-1.545)$

$7 + -6.182$

③ $= 0.818V$

④ I_a for $P = IV$

$I_a = \frac{4}{V_x - 1} = \frac{4}{-1.545 - 1} = \frac{4}{-2.545} = -1.571$

$P = IV$

-1.6363×1

$= -1.6363W$ dissipated

+ 5

$P = IV = 1 \times 0.8182 = 0.82W$ dissipated

