
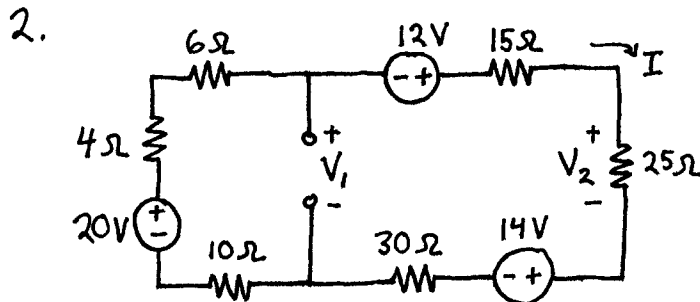



Find the values of R_1, R_2 .

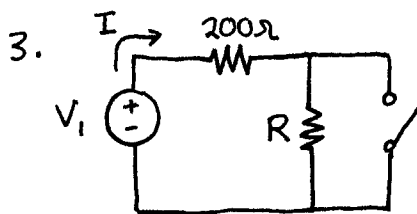


Find I, V_1, V_2 , power supplied by 12V source.



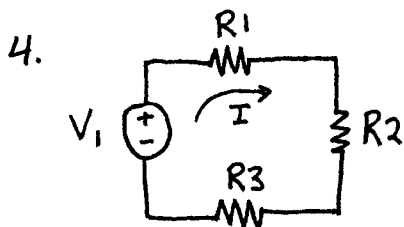
When the switch is open, $I = 1 \text{ mA}$.
When closed, $I = 10 \text{ mA}$.
Find V_1 and R .



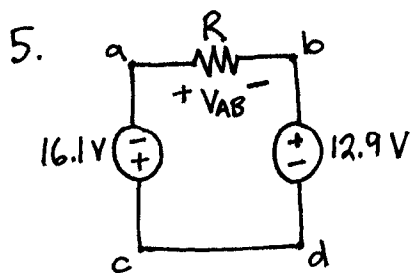When $V_1 = 10 \text{ V}$, $I = 1 \text{ A}$, and the voltage drops across R_1 and R_2 are 2 V and 3 V , respectively. Find R_3 and the power dissipated in R_3 .




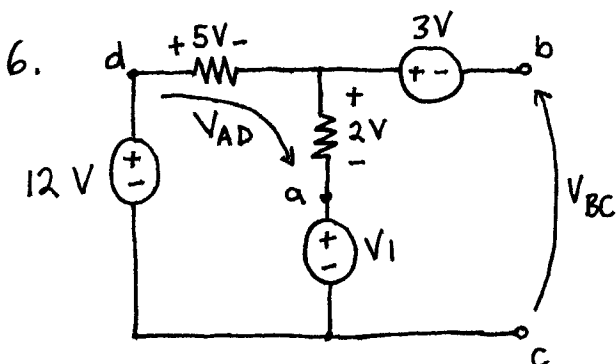
Determine V_{AB} using KVL. If a voltage source were inserted between C and D to make $V_{AB} = 12.3 \text{ V}$, draw the circuit showing the voltage source polarity and magnitude.




Find V_1, V_{AD}, V_{BC} .

Note: the convention V_{AD} means the voltage between points "A" and "D" with "A" understood as the more positive point, i.e., node "D" is the reference (-) node.

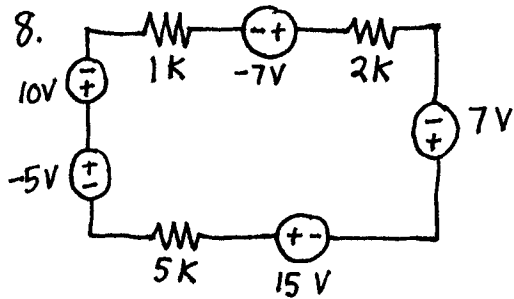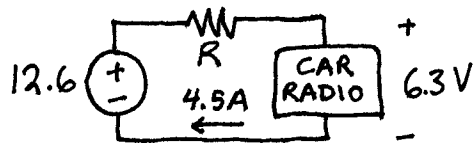7. A car radio designed to operate from 6.3 volts draws 4.5 A of current. What value of R should be placed in series with the radio if it is to be used in a 12.6 Volt car? What should the power rating of the resistor be?




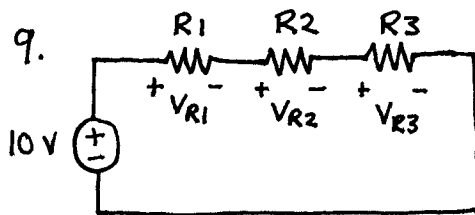Draw an equivalent circuit that contains only one resistor and one voltage source.




R_1 is twice R_2 .
 R_1 is one-half R_3 .
 Determine V_{R1} , V_{R2} , V_{R3} .

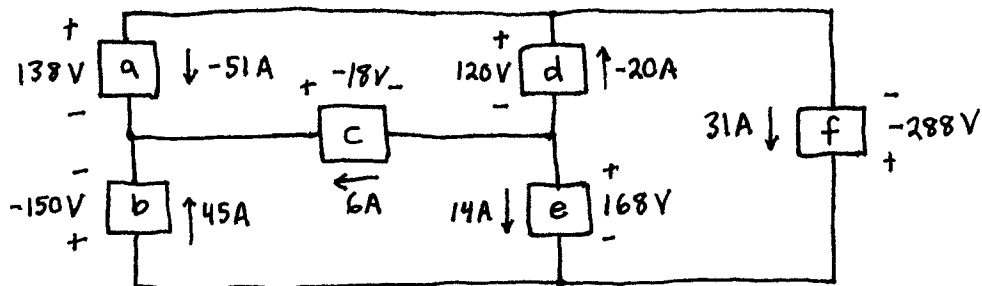10. The following circuit was left on your floor. Spot, your faithful homework checking dog, begins to bark, as if he senses an error in your calculations. Is something wrong with your calculations or is Spot simply asking to use your homework as a restroom?




11.

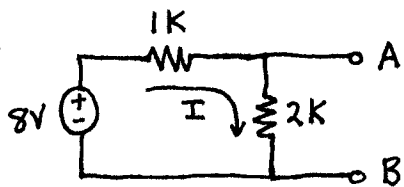

If a voltmeter is connected to points "A" and "B," what is I , and what is the voltage measured?


If an ammeter is connected to points "A" and "B," what is I , and is this a dangerous thing to do?

12.

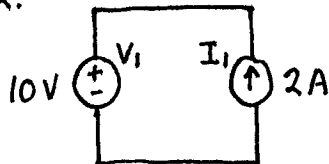

How much power is supplied by $V_1 + I_1$?

13.

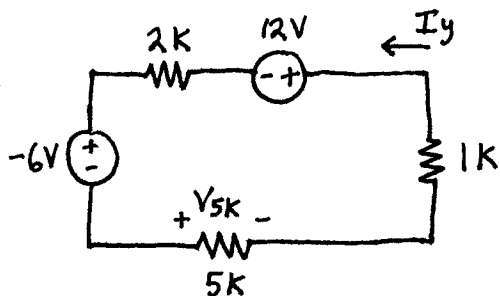

Determine I_y , V_{5K} , power generated by $-6V$ source.