

HW #5 ECE112

For the schematics given below, write the SPICE netlist for the circuit and simulate the circuit with HSPICE. Turn in your spice output and on it compare the SPICE output with your hand calculations and comment on how the answers compare. Note that these problems are ones from prior homework sets.

Please use a2ps with small fonts to do printing for your spice input. The default a2ps settings are probably adequate.

