

(3pts) Problem 6

A typical house wiring circuit can safely pass 15 amps before the circuit breaker trips. How many 100 W bulbs can be illuminated on such a circuit?

$$V = 120 \text{ V}$$

$$I = 15 \text{ A}$$

$$P = (120 \text{ V})(15 \text{ A}) = 1800 \text{ W}$$

Each bulb is 100W $\Rightarrow \frac{1800 \text{ W}}{100 \text{ W}} = \boxed{18 \text{ Bulbs}}$