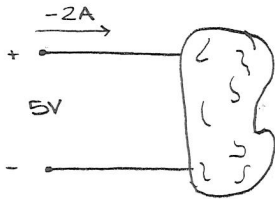



(2pts) Problem 8

Circle the correct answer below to indicate if the potato is generating or dissipating power.



Generating

Dissipating

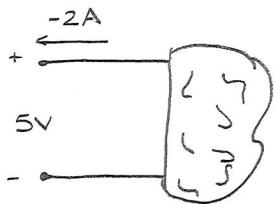

Generating

Dissipating