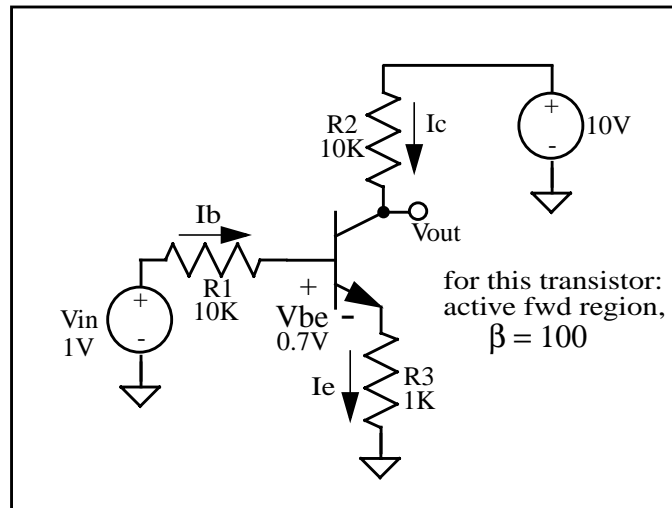


BJT amplifier DC Operating Point

Consider the circuit below with the assumption that the transistor is in the active forward region and $\beta = 100$. Let's solve for the voltage V_{out} .



To analyze this circuit, first write the KVL loop equation around the base-emitter circuit.

$$\begin{aligned}
 -1 + 10000I_b + 0.7 + 1000I_e &= 0 \\
 \text{however, we know that } I_c &= \beta I_b, \text{ thus } I_e = (I_b + \beta I_b) \\
 &= \underline{(\beta + 1)I_b}
 \end{aligned}$$

now, rewriting the KVL loop equation, we get:

$$\begin{aligned}
 -1 + 10000I_b + 0.7 + 1000(\beta + 1)I_b &= 0 \\
 -1 + 10000I_b + 0.7 + 101000I_b &= 0 \\
 111000I_b &= 0.3 \\
 \underline{I_b = 2.7\mu A}
 \end{aligned}$$

Now, knowing I_b , we can calculate I_c and thus the voltage drop across the collector resistor.

$$\begin{aligned}
 I_c &= 100(2.7\mu A) = 270\mu A; \\
 \text{thus the voltage drop across the collector resistor is:} \\
 10000(270\mu A) &= 2.7V \\
 \text{and therefore, } V_{out} &\text{ is } 10 - 2.7 = \underline{7.3V}.
 \end{aligned}$$

As a check to our assumption that the transistor is not in saturation, we can see that:

$$\begin{aligned}
 V_{ce} &= 10 - 10000I_c - 1000I_e \\
 \text{where; } I_e &= 101 * 2.7\mu A = .273mA, \text{ and} \\
 I_c &= 100 * 2.7\mu A = .27mA, \text{ therefore} \\
 V_{ce} &= 10 - 10000(.00027) - 1000(.000273) \\
 &= 10 - 2.7 - .273 \\
 &= \underline{7.027V} \text{ (not in saturation)}
 \end{aligned}$$