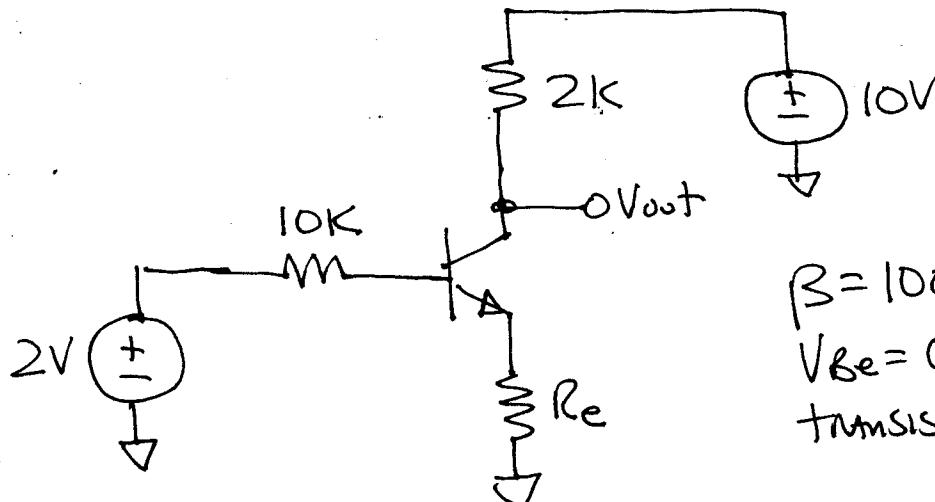


BJT Analysis - In Class Problem

Determine: R_E such that $V_{out} = 5V$

Power Dissipation of the transistor neglecting I_B



$$\beta = 100$$

$$V_{BE} = 0.7$$

transistor in active linear region

When is $V_{out} = 5V$? When I_C across 2k resistor drops 5V. Write KVL loop in output.

$$(KVL) \quad -10 + 2000I_C + V_{out} = 0$$

$$-10 + 2000I_C + 5 = 0$$

$$2000I_C = 5 \quad \therefore I_C = \underline{2.5 \text{ mA}}$$

Since we are in active linear region $I_B = I_C/\beta$ thus,

$$I_B = \underline{25 \mu A}$$

Now determine R_E by KVL loop in base emitter loop.


$$(KVL) \quad -2 + 10000I_B + 0.7 + (\beta + 1)I_B R_E = 0 \quad || \begin{matrix} \text{Remember } I_E = (\beta + 1)I_B \\ \text{in active linear region.} \end{matrix}$$

$$-2 + 10000(25 \times 10^{-6}) + 0.7 + 2.5 \times 10^{-3} R_E = 0$$

$$R_E = \frac{1.05}{0.0025 \times 10^{-3}} = \underline{415.8}$$

nearest standard value
is 430Ω

Using 430Ω as R_e ...

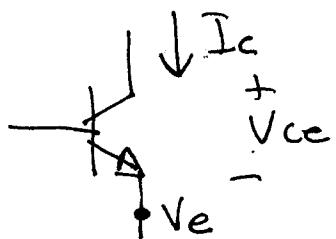

Power dissipation of transistor would be $(I_c * V_{ce})$. We need to find V_e to find V_{ce}

Neglecting I_B , $I_e = I_c$

$$\text{thus } V_e = I_c * 430 = 1.075V$$

and

$$V_{ce} = V_c - V_e = 5 - 1.075 = 3.925$$

thus

$$P_D(\text{transistor}) = 3.925 * 2.5 \times 10^{-3} = \underline{\underline{9.8mW}}$$

cool as a cucumber!