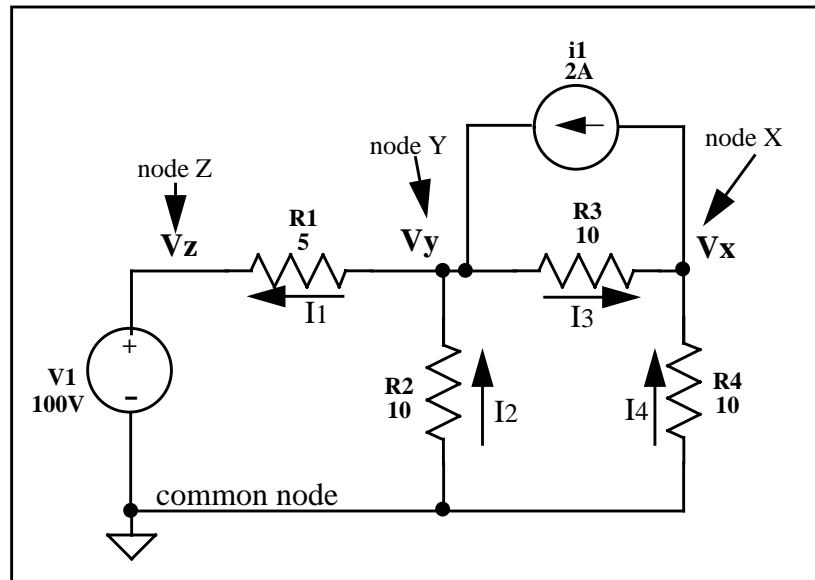


Using Spice for KCL Analysis

Below is a circuit analyzed by hand earlier. We shall now create a Spice netlist for this circuit and simulate it.



The Spice netlist for the circuit above is placed in a normal text file with whatever editor you like. It looks like this:

```
.title spice example for circuit kcl1.sp
.options
+ badchr=1 $detect bad chars
+ ingold=1 $combined exp and fixed output format
+ numdgt=4 $number of significant digits for output variables
$ netlist follows
v1      z      gnd    10v
r1      y      z      5
r2      gnd    y      10
r3      y      x      10
r4      gnd    x      10
i1      x      y      2
$ netlist done
.op $find dc operating point
.options post $save data for post processing
.end
```

The .options line sets up some convenient settings for your simulation. The “+” is the continuation character for continuing the .options selections.

The body of the netlist is shown below. A review of its format is given below. Note that nodes

Vx, Vy, and Vz have been abbreviated x, y and z respectively.

type of element and its reference designation			
r = resistor			
v = voltage source			
i = current source			
	node to which the positive terminal of element is connected		node to which the negative terminal of element is connected
			value of the element
v1	z	gnd	10v
r1	y	z	5
r2	gnd	y	10
r3	y	x	10
r4	gnd	x	10
i1	x	y	2

Hspice is invoked on the file *kc11.sp* at the unix prompt by typing:

```
hspice kc11.sp > output
```

The results from the simulation are in the file *output*:

```
***** operating point information tnom = 25.000 temp = 25.000
node   = voltage   node   = voltage   node   = voltage
+0:x   = -5.7143    0:y    = 8.5714    0:z    = 10.0000

**** voltage sources
subckt
element 0:v1
volts    10.0000
current  -0.2857
power    2.8571

total voltage source power dissipation = 2.8571 watts

**** current sources
subckt
element 0:i1
volts    -14.2857
current   2.0000
power    28.5714

total current source power dissipation = 28.5714 watts

**** resistors
```

Node voltages

Current is flowing out of "+" terminal of voltage source

subckt				
element	0:r1	0:r2	0:r3	0:r4
r value	5.0000	10.0000	10.0000	10.0000
v drop	-1.4286	-8.5714	14.2857	5.7143
current	-0.2857	-0.8571	1.4286	0.5714
power	0.4082	7.3469	20.4082	3.2653

We see that the node voltages are identical to the hand calculated values. The dc operating point analysis also gives the voltage across, current through, and power.