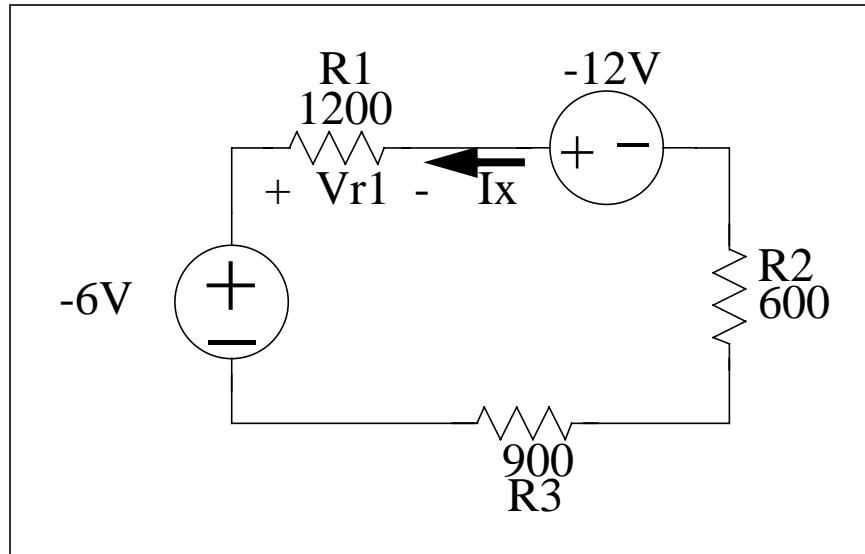


## In Class Problems

### KVL Analysis

In the circuit below, determine the current  $I_x$ , the voltage  $V_{r1}$  and the power dissipated in the -6 volt source.



### Power Calculation

Determine if the potatoes are generating or dissipating power.

