

In class Problem

Find the equivalent resistance of the network

