

Biasing Guidelines

- ▶ Basic guidelines for biasing a common-emitter BJT amplifier that is stable over temperature, voltage and part variations.
 1. Choose an appropriate transistor for your circuit. Make sure that $\beta \geq 100$ at the anticipated current level.
Allows the assumption that $I_c \approx I_e$ and $I_b \approx 0$.
 2. Choose I_e to set the transistor transconductance.
Lessens the dependence of I_c on Beta and temperature.
 3. Choose a collector resistor to set $V_c \approx 0.5V_{cc}$.
Gives the greatest output voltage swing.
 4. With chosen I_e , pick R_e such that $V_e \geq 10V_t$. Voltages from 0.5V - 1V are typical.
Minimizes variations in I_c due to V_{be} temperature dependence.
 5. Create the base bias resistor network so that $V_b = V_e + 0.6$ with the constraint that the current through the bias resistors is $0.1I_e$. With $\beta \geq 100$, this corresponds to a bias resistor current that is $\geq 10I_b$.
Keeps variations in β (thus, I_b) from effecting V_b .