
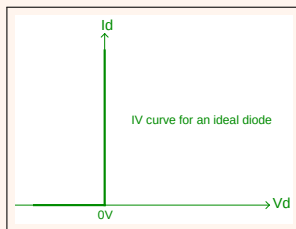

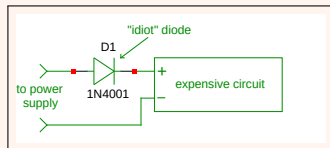
## Diode Models

- ▶ Depending upon the diode application, different models can be used. The simplest model is the *ideal diode* which looks like this.




- ▶ In this model, if  $V_d > 0$ , the diode acts as a zero resistance wire.
- ▶ This model does find purpose as an *idiot* diode. An idiot diode is put in series with the power connections to protect circuitry from reverse polarity.



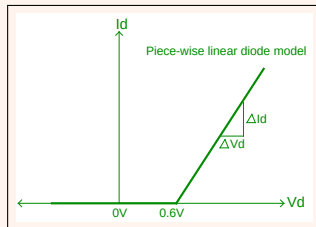
# Diode Models

- ▶ A slightly more accurate diode model is the piece-wise linear model.
- ▶ This model accounts for the forward voltage drop across the diode plus an equivalent resistance  $R_d$  equal to  $\frac{\Delta V_d}{\Delta I_d}$ , also known as the static diode resistance.



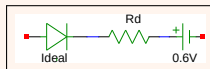- ▶ The schematic for this model would look like this:



## Diode Models

- ▶ A much more accurate model is a mathematical expression that has its origin from the physics point of view. This model is given by:

$$I_d = I_s \left( e^{\frac{qV_d}{nkT}} - 1 \right); \text{ where:}$$

$n = 1.65$  ideality factor varies with the diode

$I_s = 5 * 10^{-9}$  reverse saturation current

$q = 1.602 * 10^{-19}$  charge on an electron


$K = 1.38 * 10^{-23}$  Boltzmann's constant

$T = 300$  absolute temperature

- ▶  $k, T$  and  $q$  are constants, so  $\left(\frac{kT}{q}\right)$  is equal to  $\sim 26\text{mV}$  at  $300\text{K}$ , so the equation can be written as:  $I_d = I_s \left( e^{\frac{V_d}{nV_T}} - 1 \right)$ ; where  $V_T$  is called the *thermal voltage*.
- ▶  $I_s$  is on the order of  $10^{-9}$ , so it can be ignored relative to the exponential term, yielding:  $I_d = I_s \left( e^{\frac{V_d}{nV_T}} \right)$

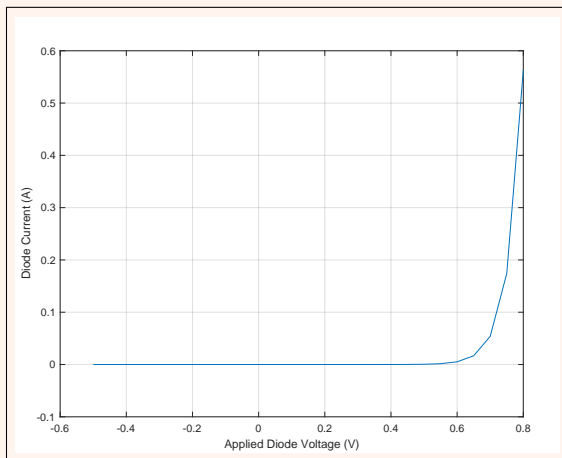
# Diode Models

- ▶ Using the mathematical model and data for a 1N4148 silicon diode, a Matlab plot of its IV characteristics looks like this:


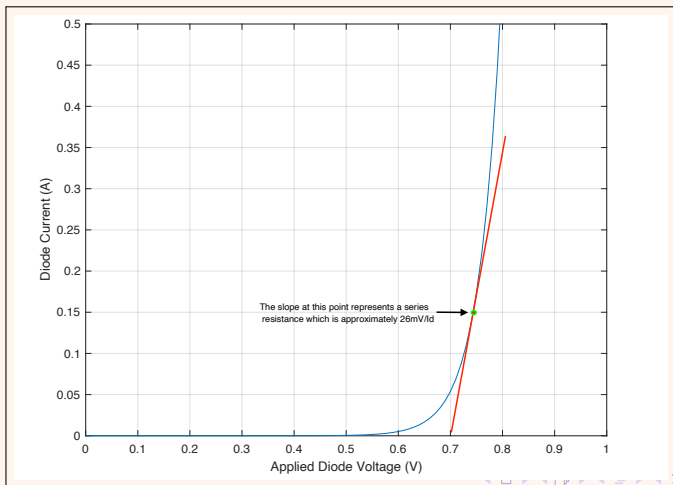
## Diode Models

- ▶ Looking at the previous plot, we see a point with a given slope on the curve.
- ▶ The slope of the tangent line represents the *dynamic resistance*  $r_d$  of the diode.



## Diode Models

- ▶ The slope of the tangent line  $r_d$  is obtained by differentiation of the diode equation.

$$I_d = I_s(e^{\frac{V_d}{nV_T}}) \quad \text{now, differentiate diode equation WRT } V_D$$

$$\frac{dI_d}{dV_d} = I_s \frac{d}{dV_d} (e^{\frac{V_d}{nV_T}}) \quad \text{remembering: } \frac{d}{dx} a e^{ax} = a e^{ax}$$

$$\frac{dI_d}{dV_d} = \frac{I_s}{nV_T} (e^{\frac{V_d}{nV_T}}) \quad \text{now, substitute } I_s(e^{\frac{V_d}{nV_T}}) \text{ for } I_d \text{ from first equation}$$

$$\frac{dI_d}{dV_d} = \frac{I_d}{nV_T} \quad \text{now, invert both sides to obtain a resistance } \frac{V}{I}$$


$$\frac{dV_d}{dI_d} = \frac{nV_T}{I_d} \quad \text{if } n=1, nV_t = 26mV, \text{ so since}$$

$$\frac{dV_d}{dI_d} = r_d \quad \text{then...}$$

$$r_d = \frac{26mV}{I_d}$$
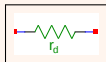
# Diode Models

- ▶  $r_d$  is the model of the diode in the small signal condition. Its just a resistance with no voltage source.



- ▶ The small signal diode resistance only applies for the condition where we are well beyond the barrier voltage  $0.6V$  of the diode. Why?
  - ▶ When  $V_d < 0V$ , the equation does not hold since we removed the  $I_s$  term.
  - ▶ Before we are a little past the threshold voltage, the exponential term will not dominate  $I_s$ .
- ▶ A small signal condition is one where our signal amplitude is a small value in comparison with the other circuit voltages or currents.
- ▶ For example, a  $100mV_{pp}$  AC signal is a small signal with an amplifier that operates from  $10V$ .