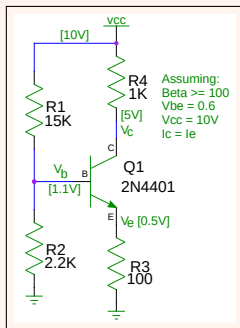



## Fixing the Amplifier Gain

- ▶ Let's see how we can change the gain to match our requirements.
- ▶ Remember from before that the gain of our amplifier can be approximated as  $\frac{R4}{R3}$ .
- ▶ We would like to increase the gain from  $\frac{1000}{100} = 10$  to 20.
- ▶ Our circuit, set up for the correct DC operating point looks like this:



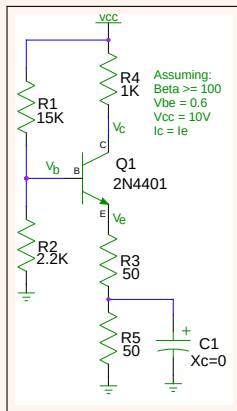
## Fixing the Amplifier Gain

- ▶ If we could *bypass* half of the 100 ohm emitter resistor with a capacitor, we would have an small-signal AC gain of  $\frac{1000}{50} = 20$ .
- ▶ Here is how that could be done:



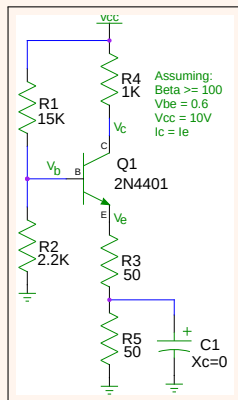
## Fixing the Amplifier Gain

- ▶ Now we have the same DC circuit, but a very different AC circuit.
- ▶ The reactance of a capacitor is:  $X_c = \frac{1}{2\pi FC}$
- ▶ The bypass capacitor should have a low reactance at the frequencies of interest relative to 50 ohms.
- ▶ At 1Khz, a 100uF capacitor:  $X_c = \frac{1}{2\pi 1000 * 10^{-4}} = 1.6 \text{ ohms}$ , or 2% of 50 ohms.


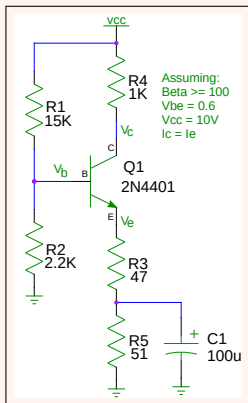
## Fixing the Amplifier Gain

- ▶ To make the gain 20, subtract the  $X_c = 1.6\Omega$  from 50 ohms, but keep the DC resistance equal.
- ▶ The new R3 value would be about 47 ohms, and R5 would be 51 ohms. These are standard values.
- ▶ The revised circuit looks like this:



## Fixing the Amplifier Gain

- ▶ Almost ready to simulate. The AC input signal source must be capacitively *coupled* in case there is a DC offset to the AC signal.
- ▶ The capacitor size is important. It should not attenuate the signal when the input source drives the input impedance of the amplifier.
- ▶ The small signal model calculation of  $r_\pi$  is:
- ▶  $r_\pi = \frac{26mV}{.005} \approx 5 \text{ ohms};$


$$\begin{aligned} r_{in} &= \left( \frac{V_{in}}{I_{in}} \right) \parallel R_{th} ; \text{ where } R_{th} = R1 \parallel R2 \\ &= \left( \frac{(j\omega r_\pi) + (\beta + 1)j\omega Z_e}{j\omega} \right) \parallel 1919 ; Z_e = \text{impedance emitter to gnd} \\ &= (r_\pi + (\beta + 1)Z_e) \parallel 1919 \\ &= (5 + (101)48.6) \parallel 1919 \\ &= 4752 \parallel 1919 \\ &= 1350\Omega \text{ (note: bias resistors dominating input impedance)} \end{aligned}$$

## Fixing the Amplifier Gain

- ▶ With  $r_{in} = 1350$  ohms, a reasonable input coupling capacitor would be  $10\mu\text{F}$ . In that case,  $X_c \approx 16$  ohms or 1% of the input resistance.
- ▶ Note that the output is assumed to come directly from the collector ( $R_{load} = \infty$ ) which is not the typical case but makes this example easier to digest.
- ▶ Also note that the input impedance is lowered by the inclusion of the bypass capacitor since it bypassed part of the emitter resistor.
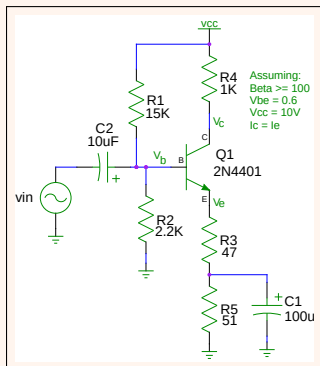
# Fixing the Amplifier Gain

- ▶ Now our circuit to simulate looks like:



```
.title dcopt3.sp


*simulation to determine AC small signal gain

.include 2n4401.mod
Vin in          gnd          ac=0.1 ;AC swept source
C2 in          base         10u    ;input coupling cap
Vcc vcc        gnd          10v
R1 vcc        base         15K
R2 base       gnd           2.2K
R3 emitter   emitter_tie   47
R5 emitter_tie gnd         51
C1 emitter_tie gnd         100u ; bypass cap
R4 vcc        collector     1K
Q1 collector  base         emitter 2N4401

.control
  ac dec 10 1 1meg ; AC small sig analysis
*
*                   ; decade variation, 10 points per decade,
*                   ; 1 hz to 1mhz
*
  set hcopydevtype=postsript
  set xbrushwidth=3
  set hcopypscolor=0
  set color0=rgb:f/f/f
  set color1=rgb:0/0/0
  set color2=blue
  set color3=red
  plot vm(in) vm(collector) ; plot AC magnitude
  hardcopy dcopt3.eps vm(in) vm(collector) ; hardcopy plot
.endc
.end
```
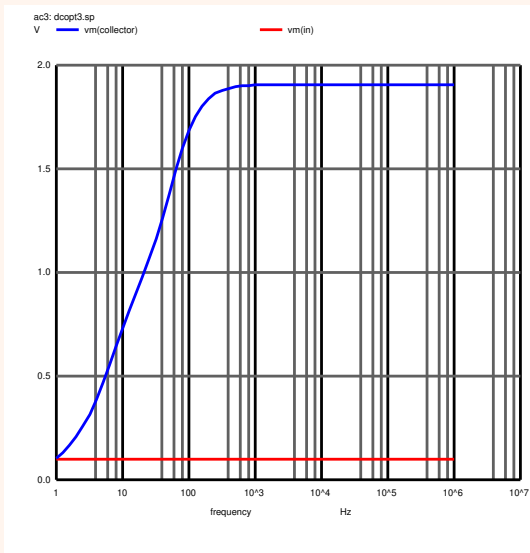
# Fixing the Amplifier Gain

- ▶ Missed it by a hair! Gain is 19.2.
- ▶ This is a plot of voltage magnitudes. Plot command uses `vm(node)`.





## Fixing the Amplifier Gain

- ▶ Lowering  $R_3$  by 4 ohms we get a gain of 20.1. This is splitting hairs and would probably not be worth the trouble in practice. If your system was that sensitive to gain, something is not well thought out.