

ECE474/574


Quiz 2

5.8.2017


Name: _____

Draw the logic created by the following code. Use only D-type FFs/latches, muxes, and combinatorial logic. Label all pins and wires. Assume the input and output signals have been previously defined.

 
```
always_ff @(posedge clk, negedge reset_n)
  if(!reset_n)
    out <= '1;
  else
    out <= in;
```



 
```
always_ff @(posedge clk, negedge reset_n)
  if(!reset_n)
    out <= '0;
  else
    out <= ~out;
```



 
```
reset applied to reset pin
always_ff @(posedge clk)
  if(!reset_n)
    out <= '0;
  else
    out <= in;
```


 
```
syn reset
always_latch
  if (clk) out2 <= in;
```


 
```
always_ff @(posedge clk, negedge reset_n)
  if(!reset_n)
    out <= '0;
  else
    if (en == 1'b1)
      out <= in;
```



```
always_ff @(posedge clk, negedge reset_n)
  if(!reset_n) begin out <= '0; out1 <= '0; end
  else begin out <= in; out1 <= out; end
```

