

# for Statement

- ▶ Provides an indexed looping expression
- ▶ Must be used inside `always` or `initial` statement
- ▶ The `for` loop is structured just as in C.
- ▶ For loops must be used carefully when constructing combo logic.
- ▶ Non-synthesizable loops are easy to create.
- ▶ For loops are seldom used in synthesizable code.


## for Statement

- ▶ The priority encoder looks at input bus a and outputs the encoding of the highest bit that is set on bus y.
- ▶ Input value 0x00 is illegal. The valid bit detects this case.
- ▶ Could the valid bit be used for a timing (hardware) indication that the output is ready?

```
module priority_encoder (  
    input      [7:0]  a,  
    output reg      valid, //indicates output valid  
    output reg  [2:0]  y);  
  
    integer i;  
    always_comb begin  
        valid = 0; //default output  
        y = 3'bx;  //default output  
        for (i=0; i<8; i++) begin  
            if (a[i]) begin  
                valid = 1; y = i;  
            end //if  
        end //for  
    end //always_comb  
endmodule
```
 
## for Statement

Output from synthesis for priority\_encoder.sv



# for Statement


- Here's a neat bit of code using a for loop. What's it do?

```
module whatisit(  
    input      [15:0]  a,    //data in a  
    input      [15:0]  b,    //data in b  
    output reg [31:0]  z      //data output  
);  
  
integer i;  
always_comb begin  
    z=0;  
    for(i=0;i<=15;i++) begin  
        if (a[i]) begin  
            z = z + (b<<i);  
        end  
    end  
end  
endmodule
```
 
## for Statement

Synthesis output from whatisit.sv

1700 gates, 6.5nS worst case delay b[1] to z[31]



## for Statement

- ▶ Note that in both cases, the sequential behavioral description using for DOES NOT produce a sequential implementation.
- ▶ The operation of the gates is produced via concurrent evaluation.