

if/else, unique, priority

- ▶ To create hierarchy and create combinatorial logic gates, we use the `always_comb` block.
- ▶ Inside the `always_comb` block, we describe the behavior of combinational logic in a sequential, algorithmic way with `if`, `else`, `while` and `case` statements.
- ▶ These statements, inherited from procedural languages, provide a powerful means of expression. We therefore refer to the `always_comb` block as a procedural block.
- ▶ Keep in mind that you are not writing a program, but instead you are describing how the *logic* behaves.
- ▶ Digital logic does not "execute" statement by statement but instead it evaluates in a parallel "all-at-once", and "all-the-time" fashion.

if/else, unique, priority

- ▶ If there are multiple statements within `always_comb`, they must be bracketed with `begin`, `end` statements.

```
always_comb begin
    prod_reg_ld_high  = 1'b0;    //statement 1
    prod_reg_shift_rt = 1'b0;    //statement 2
end //always_comb
```


- ▶ Single statements within `always_comb` do not need `begin`, `end`.

```
always_comb
    if (sel) d_out = din_1;
    else     d_out = din_0;
```

if/else, unique, priority

- ▶ The `if` statement creates combinatorial logic that outputs a value depending upon the value of a conditional expression.
- ▶ If the conditional expression evaluates true (non-zero), the following signal assignment is made. Otherwise, that assignment is skipped and the next statement is evaluated.
- ▶ A conditional expression evaluates to false when its `X`, `Z`, or zero.
- ▶ Note the use of blocking assignments.
 
```
module mux2_1 (  
  input      sel,  
  input      din_0,  
  input      din_1,  
  output logic d_out);  
  always_comb  
    if (sel) d_out = din_1;  
    else    d_out = din_0;  
endmodule
```




Synthesis Output

if/else, unique, priority

- ▶ If there are multiple assignment statements they must be grouped within a begin, end set.
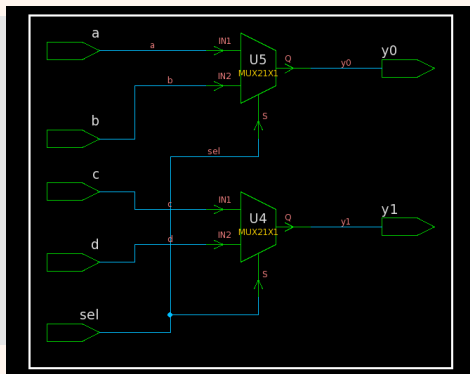
```
module dual_mux2_1 (  
  input      sel,  
  input      a,b,c,d,  
  output logic y0,  
  output logic y1);  
  always_comb  
    if (sel) begin y0 = b;  
                 y1 = d;  
    end  
    else begin y0 = a;  
              y1 = c;  
    end  
endmodule
```




Synthesis Output

if/else, unique, priority


- ▶ The `if` statement tests a conditional expression to determine which output assignment to make.
- ▶ Relational operators in the conditional expression can add substantial additional logic.
- ▶ Commonly used relational operators used are:
 - ▶ equals (`==`)
 - ▶ not-equals (`!=`)
 - ▶ greater-than (`>`)
 - ▶ less-than (`<`)
 - ▶ greater-than-or-equal-to (`>=`)
 - ▶ less-than-or-equal-to (`<=`)
- ▶ How would you realize these operators in logic gates? Which would be cheapest?

if/else, unique, priority

 - ▶ Four-bit, 2:1 Mux with 4-bit comparison operators.



 
```
if (a==b) z = c; //equals uses XOR primarily
else     z = d;
```



```
if (a<=b) z = c; //lteq, gteq, takes far more gates
else     z = d;
```

if/else, unique, priority

 - ▶ Wide comparisons can be produce lots of deep and thus slow logic.
- ▶ Here, the comparison logic is far bigger that the desired 2x1 mux at bottom right.




```
if (a<=b) z = c;  
else     z = d;
```

if/else, unique, priority

- ▶ Deeply nested if statements can produce slow logic.
- ▶ Some paths are far slower than others.
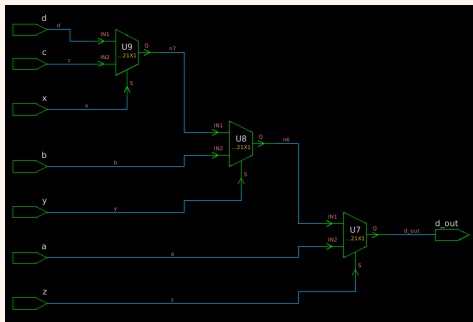
```
module serial_mux (  
  input  a,b,c,d  
  input  x,y,z  
  output logic d_out  
);  
  
always_comb  
  if      (z) d_out = a;  
  else if (y) d_out = b;  
  else if (x) d_out = c;  
  else      d_out = d;  
endmodule
```



if/else, unique, priority


- ▶ The schematics seen here are produced by Synopsys Design Compiler aka "dc_shell" or "design_vision-xg" using a standard cell logic library.
- ▶ FPGA combinational logic uses SRAM looktables.
- ▶ As such, an *apples-to-apples* comparison is not possible.
- ▶ However, standard cell synthesis helps us to see the complexity of inferred gate structures.
- ▶ FPGA SRAM memories can be used to create wide logic structures that have uniform delay paths. Why?

if/else, unique, priority

- ▶ If an if statement has no else, the synthesizer has to make an assumption as to what the newest value of the output is to be.
- ▶ The assumption, wrong or right, is to **hold the last value**. Note the synthesis warning. Hence the saying...*"if without else gives a latch"*

```
Warning: no_else_mux.sv:6:  
Netlist for always_comb block contains a latch.
```
 
```
module no_else_mux (  
    input      sel,  
    input      a,b,  
    output logic y0 );  
    always_comb  
        if (sel) y0 = a;  
    // else      y0 = b; //commented  
endmodule
```




Synthesis Output

if/else, unique, priority

- ▶ The decision modifiers `unique` and `priority` reduce ambiguities and can trap potential design errors early.
- ▶ What is the intention here? Priority or not? Note inferred latch.

 
```
module nunique(  
input [2:0] sel, //selection input  
input a,b,c,  
output logic mux_out);  
always_comb  
if (sel == 3'b001) mux_out = a;  
else if (sel == 3'b010) mux_out = b;  
else if (sel == 3'b100) mux_out = c;  
endmodule
```



if/else, unique, priority

- ▶ The simulator evaluates `if...else...if` decisions in order and synthesis creates logic enforcing priority so that RTL and gate simulation behave identically.
- ▶ What if you didn't care about order or priority? The `unique` modifier lets you say so. The result is no priority logic, and no latch.
 
```
module unique1(  
input [2:0]    sel,  //selection input  
input         a,b,c,  
output logic  mux_out);  
always_comb  
    unique if (sel == 3'b001) mux_out = a;  
    else if  (sel == 3'b010) mux_out = b;  
    else if  (sel == 3'b100) mux_out = c;  
endmodule
```



if/else, unique, priority

- ▶ Another action of the `unique` modifier is to direct the simulator to issue a run-time warning if none of the `if` branches are executed.
- ▶ In our present example, a run-time warning would be issued if `sel` was any other value than 1, 2, or 4.

```
VSIM73> force a 0
VSIM74> force b 0
VSIM75> force c 0
VSIM76> force sel 16#5
VSIM77> run 50
# ** Warning: (vsim-8315) unique1.v(6): No condition is true in the unique/priority if/case statement.
#   Time: 0 ns   Iteration: 0   Instance: /unique1
```


Signal	Value
/unique1/sel	3'h5
/unique1/a	1'h0
/unique1/b	1'h0
/unique1/c	1'h0
/unique1/mux_out	1'hx

- ▶ Note that the simulator output is "x" for `sel=3'b101`. What would the gate output be? Can real gates ever have an output of "x"?

if/else, unique, priority

- ▶ Since unique gives us a way to check in simulation that at least one branch is taken, a "concluding else" is not needed to prevent latches.
 
```
module unique1(  
input [2:0]    sel, //selection input  
input         a,b,c,  
output logic  mux_out);  
always_comb  
    unique if (sel == 3'b001) mux_out = a;  
    else if  (sel == 3'b010) mux_out = b;  
    else if  (sel == 3'b100) mux_out = c;  
endmodule
```



if/else, unique, priority

- ▶ Here, potential for overlapping conditions exist as any number of conditions could be true at once.

```
module unique2(  
input [2:0]    sel,  //selection input  
input        a,b,c,  
output logic  mux_out);  
always_comb  
    unique if (sel[0]) mux_out = a;  
    else if  (sel[1]) mux_out = b;  
    else if  (sel[2]) mux_out = c;  
endmodule
```

- ▶ If `unique` removes priority encoding, the conditions must be mutually exclusive. Therefore in this situation, `unique` acts as an assertion, telling the simulator to issue a run-time warning if more than one condition ever true.

if/else, unique, priority

- ▶ Forcing sel[2:0] to 3'b011 makes the conditions non-mutually exclusive and the simulator issues a warning.


```
force sel 16#3
```

```
run 100
```


```
# Warning: (vsim-8360) unique2.sv(6):
```

```
# The if/case statement is not unique.
```
 
```
# Time: 200 ns Iteration: 0 Instance: /unique2
```



 - ▶ This is totally appropriate as if priority was enforced, the "a" input should have been chosen. The synthesis results show why.



if/else, unique, priority

- ▶ unique if final points...
- ▶ At any point in time, unique causes the simulator to issue a run-time warning if:
 - ▶ *more than one condition is true*
 - ▶ *no condition is true and there is no else branch*
- ▶ unique, informs the synthesis tool that:
 - ▶ *every legal condition has been listed*
 - ▶ *the conditions are mutually exclusive*
 - ▶ *no priority logic is required*
- ▶ unique is placed just before the if.
- ▶ In a series of if...else decisions, unique is only specified for the first if. All subsequent if statements within the sequence are affected.
- ▶ Presently, Quartus does not support modifiers for if, only case.


if/else, unique, priority

- ▶ The decision modifier `priority` points to the designer's intention that the order of decisions is important.
- ▶ Each conditional statement is evaluated in the order listed.
- ▶ An example would be a priority encoder.

```
module encoder(  
input          in0, in1, in2, in3,  
output logic [3:0] encoded_output;  
always_comb  
    priority if (in0) encoded_output = 4'b0001;  
    else if    (in1) encoded_output = 4'b0010;  
    else if    (in2) encoded_output = 4'b0100;  
    else if    (in3) encoded_output = 4'b1000;  
endmodule
```

if/else, unique, priority


- ▶ The priority encoder in operation:

 

- ▶ Note run-time warning in the first 100ns.

```
VSIM 6> run 100
# ** Warning: (vsim-8315) encoder.sv(5): No condition is true in the unique/priority if/case statement.
# Time: 0 ns Iteration: 0 Instance: /encoder
```

 
- ▶ Synthesis results are rather unexpected



if/else, unique, priority

- ▶ Redraw schematic from the synthesis netlist. Is this right?

```
////////////////////////////////////  
// Created by: Synopsys DC Expert(TM) in wire load mode  
// Version : L-2016.03-SP2  
////////////////////////////////////  
module encoder ( in0, in1, in2, in3, encoded_output );  
  output [3:0] encoded_output;  
  input in0, in1, in2, in3;  
  wire n3, n4;  
  assign encoded_output[0] = in0;  
  NOR3X0 U8 (.IN1(encoded_output[0]), .IN2(in2), .IN3(in1), .QN(encoded_output[3]) );  
  NOR3X0 U9 (.IN1(n3), .IN2(in1), .IN3(encoded_output[0]), .QN(encoded_output[2]) );  
  INVX0 U10 (.IN(in2), .QN(n3) );  
  NOR2X0 U11 (.IN1(encoded_output[0]), .IN2(n4), .QN(encoded_output[1]) );  
  INVX0 U12 (.IN(in1), .QN(n4) );  
endmodule
```

 

if/else, unique, priority

- ▶ `priority if` final points...
- ▶ At any point in time, `priority` causes the simulator to issue a run-time warning if:
 - ▶ *no condition is true and there is no else branch*
- ▶ `priority`, informs the synthesis tool that:
 - ▶ *every legal condition has been listed*
 - ▶ *priority logic is required*
- ▶ `priority` is placed just before the `if`.
- ▶ In a series of `if...else` decisions, `priority` is only specified for the first `if`. All subsequent `if` statements within the sequence are affected.
- ▶ Presently, Quartus does not support modifiers for `if`, only `case`.