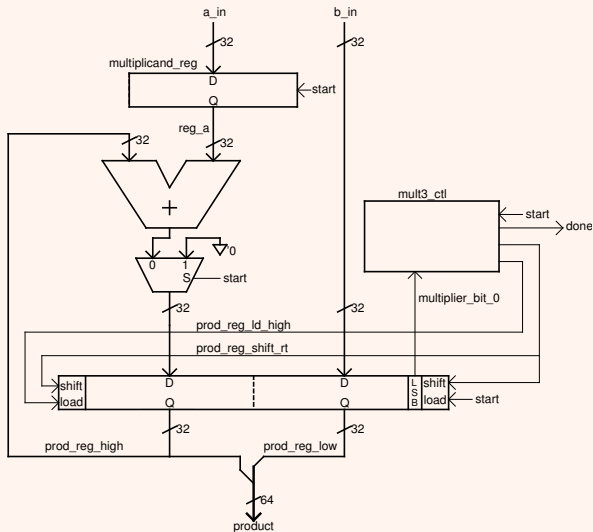



## Modules, ports, instantiation

- ▶ Development of timing and state diagrams refined the block diagram
- ▶ Cleaned up and added better names, added detail



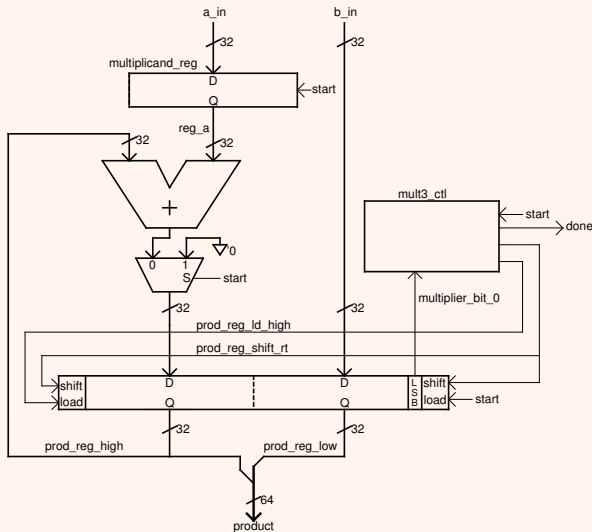
## Modules, ports, instantiation

- ▶ As its reasonable, we want to maintain our partitioning in SV
- ▶ We have two mechanisms to do this: **modules** and **always blocks**


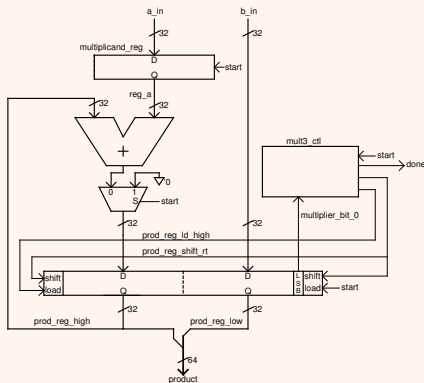
## Modules, ports, instantiation

- ▶ Simple functionality belongs in an always block.
- ▶ If considerable complexity or natural boundary (data vs. control) exists, a module is appropriate.
- ▶ Our datapath logic is simple and will be in always blocks
- ▶ "mult3\_ctl" is a natural partitioning boundary and will be in its own module.



# Modules, ports, instantiation

The module is the basic unit of hierarchy in Verilog


- ▶ Modules describe:
  - ▶ boundaries [module, endmodule]
  - ▶ inputs and outputs [ports]
  - ▶ how it works [behavioral or RTL code]
- ▶ Can be a single element or collection of lower level modules
- ▶ Module can describe a hierarchical design (a module of modules)
- ▶ A module should be contained within one file
- ▶ Module name should match the file name
- ▶ Module mult3\_ctl resides in file named mult3\_ctl.sv
- ▶ Multiple modules can reside within one file (not recommended)

# Modules, ports, instantiation

- ▶ Modules are declared with their name and ports

```
module mult3_ctl(  
    input  reset,  
    input  clk,  
    input  start,                               //begin multiplication  
    input  multiplier_bit0,  
    output logic prod_reg_ld_high,             //load high half of register  
    output logic prod_reg_shift_rt,          //shift product register right  
    output logic done);                       //signal completion of mult op
```

 - ▶ The Verilog declaration of the module corresponds directly to the block diagram. The module `mult3_ctl` will reside inside `mult3_ctl.sv`



# Modules, ports, instantiation

## ▶ Comments

- ▶ Comments are done just like C
- ▶ One line comments begin with //
- ▶ Multi-line comments start with /\*, end with: \*/

## ▶ Identifiers

- ▶ Identifiers are names given to objects so that they may be referenced
- ▶ They start with alphabetic chars or underscore
- ▶ They cannot start with a number or dollar sign
- ▶ All identifiers are case sensitive unlike VHDL

# Modules, ports, instantiation

- ▶ ANSI C Style Ports in System Verilog are declared as:
  - ▶ port mode, port type, port width, port name... where:
    - ▶ Port mode is *input*, *output* or *inout*
    - ▶ Port type defaults to *wire*, outputs are usually type *logic*
    - ▶ Port width is [MSB:LSB]
    - ▶ Port name is simply the name of the port


```
input      [31:0] register_in,    //register input
output logic [31:0] register_out, //register output
```

- ▶ Input ports are understood as nets (wires) within the module, and can only be read from.
- ▶ Output ports are understood as nets (wires) within the module and can be read from or written to if they are type *logic*.
- ▶ Inout ports are understood as nets (wires) within the module and can be read from or written to if they are type *logic*.
- ▶ Use *inout* ports for tri-state logic only.

# Modules, ports, instantiation
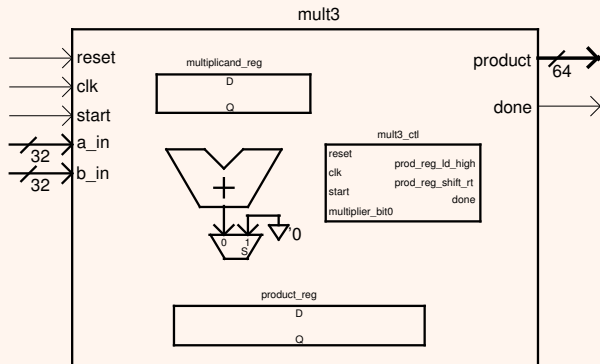
## Hierarchical Design

- ▶ Hierarchical designs have a top level module and lower level modules.
- ▶ Lower level modules (like `mult3_ctl`) are *instantiated* within the higher level module (`mult3`)





# Modules, ports, instantiation

- ▶ Module mult3 is just a higher-level module, so we define it as before.
- ▶ Module mult3 will reside in another file called mult3.sv.
- ▶ The beginning of mult3.sv looks like this:

```
module mult3(  
    input  reset ,  
    input  clk ,  
    input  [31:0] a_in ,  
    input  [31:0] b_in ,  
    input  start ,  
    output logic [63:0] product ,  
    output logic done);
```


# Modules, ports, instantiation

- ▶ Module `mult3_ctl` is instantiated within `mult3` as shown and is concluded with the keyword `endmodule`

```
module mult3(  
    input  reset,  
    input  clk,  
    input  [31:0] a_in,  
    input  [31:0] b_in,  
    input  start,  
    output logic [63:0] product,  
    output logic done);  
//  
//  Other code goes in here  
//  
//instantiate the control module  
mult3_ctl mult3_ctl_0(  
    .reset          (reset          ),  
    .clk            (clk            ),  
    .start         (start           ),  
    .multiplier_bit0 (prod_reg_low[0] ),  
    .prod_reg_ld_high (prod_reg_ld_high ),  
    .prod_reg_shift_rt (prod_reg_shift_rt ),  
    .done          (done           ));  
endmodule
```
 
## Modules, ports, instantiation

- ▶ The instantiation associates a wire in an upper-level module with a pin (or port) on a lower level module. Pins on left, wires on right.



```
//instantiate the control module
mult3_ctl mult3_ctl_0(
    .reset          (reset          ),
    .clk            (clk            ),
    .start          (start          ),
    .multiplier_bit0 (prod_reg_low [0] ), //LSB of product reg
    .prod_reg_ld_high (prod_reg_ld_high ),
    .prod_reg_shift_rt (prod_reg_shift_rt ),
    .done          (done          ));
```

# Modules, ports, instantiation

## Instantiation subtleties

- ▶ Ports of the upper-level module are understood to be wires within that module.
- ▶ Wires connected to pins can have differing names.
- ▶ Wires and pins *should not* have differing widths!
- ▶ Following the module name is an instance name that makes each instantiation of the same module unique.

```
mult3_ctl mult3_ctl_0(
```

- ▶ Comment each line if designer intention is not crystal clear.
- ▶ This method of instantiation is called *named association*. Its the preferred way of doing instantiation when pins/names differ.

# Modules, ports, instantiation

- ▶ Its possible to instantiate using pin/wire position only.
- ▶ This is called *positional association*. Its a bad idea.
- ▶ For example:

```
//instantiate the control module  
mult3_ctl mult3_ctl_0(reset,clk,start,prod_reg_low[0],  
                      prod_reg_ld_high, prod_reg_shift_rt,done);
```

- ▶ How do you know pins and wires are connected correctly?
- ▶ Could you check it quickly if the module had 50 pins on it?
- ▶ What if you wanted to add wire in the middle of the list?
- ▶ *Do not use Positional Association!*
- ▶ It saves time once, and costs you dearly afterwards

## Modules, ports, instantiation

*Implicit Naming* is useful when most pins/wires have the same name.

```
//instantiate the control module
mult3_ctl mult3_ctl_0(
    .reset          (reset          ),
    .clk            (clk            ),
    .start         (start         ),
    .multiplier_bit0 (prod_reg_low[0] ), //product reg LSB
    .prod_reg_ld_high (prod_reg_ld_high ),
    .prod_reg_shift_rt (prod_reg_shift_rt ),
    .done          (done          ));
```

```
//instantiate the control module
mult3_ctl mult3_ctl_0(
    .reset          ,
    .clk            ,
    .start         ,
    .multiplier_bit0 (prod_reg_low[0]), //named association
    .prod_reg_ld_high ,
    .prod_reg_shift_rt ,
    .done          );
```

Implicit and named association forms can be mixed

# Modules, ports, instantiation

If all pins and associated wires have the same name we can do this:

```
//instantiate the control module  
mult3_ct1 mult3_ct1_0(.*); //now that's a short cut!
```

- ▶ This is the most powerful form of implicit association.
- ▶ This method is best reserved for top level testbench/top module instantiation, else, it could hide intent.

# Modules, ports, instantiation

Unconnected port pins may be left unconnected like this...

```
//instantiate the control module, don't need connection to done pin
mult3_ctl mult3_ctl_0(
    .reset          (reset          ),
    .clk            (clk            ),
    .start          (start          ),
    .multiplier_bit0 (prod_reg_low[0] ), //product reg LSB
    .prod_reg_ld_high (prod_reg_ld_high ),
    .prod_reg_shift_rt (prod_reg_shift_rt ),
    .done           (                ));
```

- ▶ Unused ports *may* simply be left out of the port list...*bad idea!*
- ▶ Keep your intent clear!
- ▶ Careful formatting of names, parenthesis and commas makes it easy to catch errors.



## Modules, ports, instantiation

- ▶ How are lower level modules connected if a port definition has not created the wire?
- ▶ In the upper-level module, wires are declared; usually near the beginning of the module.

```
module mult3(  
    input  reset,  
    input  clk,  
    input  [31:0] a_in,  
    input  [31:0] b_in,  
    input  start,  
    output logic [63:0] product,  
    output logic done);  
  
//declare internal wires  
    logic [31:0] reg_a;           //output, multiplicand reg  
    logic [31:0] prod_reg_high; //output, upper half of product reg  
    logic [31:0] prod_reg_low;  //output, lower half of product reg  
    logic prod_reg_ld_high;     //load, upper half of product reg  
    logic prod_reg_shift_rt;    //shift product regright  
  
//lots more code goes here  
  
endmodule
```

# Modules, ports, instantiation

- ▶ Format of wire declaration is: `type width[MSB:LSB] wire_name;`
- ▶ Width is optional

```
logic [31:0] prod_reg_low; //lower half of product register
```

- ▶ If no width is given, the wire is assumed to be a single conductor.
- ▶ If width is given, a bus is created of that width. Busses are groups of logically related wires.

# Modules, ports, instantiation

- ▶ Parametrization of modules allows for code reuse
- ▶ In the module declaration, the keyword "parameter" is optional

```
//a generic width register declaration
module multi_reg #(parameter width=8) (
    input      reset
    input      clk
    input      enable
    input      data_in  [width-1:0]
    output logic data_out [width-1:0]
)
\\
\\description of register goes here
\\
endmodule
```

# Modules, ports, instantiation

- ▶ The parametrized register could be instantiated like this:

```
module top_module;

logic [31:0] data_out;
wire reset, clk, enable, data_in;

//instantiate register and override width to 32 bits
multi_reg #(.width(32)) multi_reg_0(
    .reset      (reset      ),
    .clk        (clk        ),
    .enable     (enable     ),
    .data_in    (data_in    ),
    .data_out   (data_out   ));
endmodule
```

# Modules, ports, instantiation

- ▶ Verilog modules...
  - ▶ provide a coarse-grain structuring mechanism
  - ▶ contain RTL logic or other modules
  - ▶ provide an abstraction mechanism via complexity hiding
  - ▶ provide a way for design reuse
- ▶ Question: How is a Verilog module different from a C function?