

# Verilog - Modules

The module is the basic unit of hierarchy in Verilog

- ▶ Modules describe:
  - ▶ boundaries [module, endmodule]
  - ▶ inputs and outputs [ports]
  - ▶ how it works [behavioral or RTL code]
- ▶ Can be a single element or collection of lower level modules
- ▶ Module can describe a hierarchical design (a module of modules)
- ▶ A module should be contained within one file
- ▶ Module name should match the file name
- ▶ Module fadder resides in file named fadder.sv
- ▶ Multiple modules can reside within one file (not recommended)
- ▶ Correct partitioning a design into modules is critical

# Verilog - Modules (cont.)



## A sample module

```
//-----  
//one-bit full adder module  
//-----  
module fadder(  
    input a,          //data in a  
    input b,          //data in b  
    input cin,        //carry in  
    output sum_out,   //sum output  
    output c_out      //carry output  
);  
    wire c1, c2, c3; //wiring needed  
    assign sum_out = a ^ b ^ cin; //half adder (XOR gate)  
    assign c1      = a & cin;      //carry condition 1  
    assign c2      = b & cin;      //carry condition 1  
    assign c3      = a & b;        //carry condition 1  
    assign c_out   = (c1 + c2 + c3);  
endmodule
```

What kind of logic do you expect synthesis to produce? This is always a good question to ask.

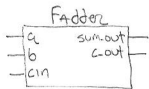 
# Verilog - Modules (cont.)

When fadder.sv is synthesized by dc\_shell, we get...



```
module fadder(  
    input a,           //data in a  
    input b,           //data in b  
    input cin,         //carry in  
    output sum_out,    //sum output  
    output c_out       //carry output  
);  
    wire c1, c2, c3; //wiring needed
```
 
```
    assign sum_out = a ^ b;    //half adder (XOR gate)  
    assign c1      = a * cin;  //carry condition 1  
    assign c2      = b * cin;  //carry condition 1  
    assign c3      = a * b;    //carry condition 1  
    assign c_out   = (c1 + c2 + c3);
```



# Verilog - Modules (cont.)

Two brief digressions...wire and assign

- ▶ "wire"
  - ▶ The declaration "wire" simply is what you think it is
  - ▶ A wire carries a value. It has no memory or sense of state.
  - ▶ More later about this....
- ▶ "assign"
  - ▶ The assign statements may execute in any order
  - ▶ We can consider that they are executed simultaneously
  - ▶ This is how the logic would operate

## Verilog - Modules (cont.)

Modules are declared with their name and ports

Listing 1: Spice file for KVL problem

```
%\scriptsize %sets right font size for the code
%\begin{verbatim}
module fadder(
    input  a,          //data in a
    input  b,          //data in b
    input  cin,        //carry in
    output sum\_out,    //sum output
    output c\_out       //carry output
);
%\end{verbatim}
```

# Verilog - Modules (cont.)

## Some Lexical Conventions - Comments

- ▶ Comments are signified the same as C
- ▶ One line comments begin with "//"
- ▶ Multi-line comments start: /\*, end: \*/

## Some Lexical Conventions - Identifiers

- ▶ Identifiers are names given to objects so that they may be referenced
- ▶ They start with alphabetic chars or underscore
- ▶ They cannot start with a number or dollar sign
- ▶ All identifiers are case sensitive

# Verilog - Modules (cont.)

ANSI C Style Ports are declared as

- ▶ input //simple input
- ▶ output //simple output
- ▶ inout //tri-state inout

Input port

- ▶ Always understood as a net within the module
- ▶ Can only be read from [check this against SVerilog]

Output port

- ▶ Understood as a net by default
- ▶ Can be type logic as well

Inout port

- ▶ Understood as a net by default
- ▶ Is always a net

# Verilog - Modules (cont.)

## Testbench Modules


- ▶ To test a chip at the top hierarchical level, we use a testbench
- ▶ Testbench encompasses the chip at the top level
- ▶ Testbench has *no ports*,...but probably some file i/o



# Verilog - Modules (cont.)
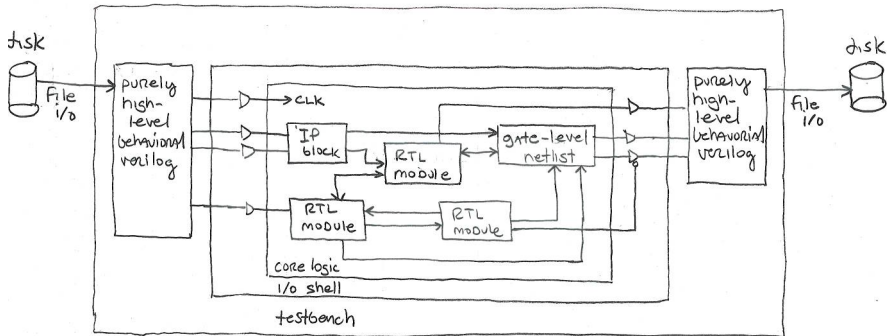
## Module to Module Connections

- ▶ A hierarchical design has a top level module and lower level ones
- ▶ Lower level modules are instantiated within the higher level module
- ▶ Lower level modules are connected together with wires



## Verilog - Modules (cont.)

Lower level modules can be instantiated within the upper one:

```
//-----  
//one bit full adder - using builtin verilog gates  
//-----  
module fadder_struct(  
    input a,          //data in a  
    input b,          //data in b  
    input cin,        //carry in  
    output sum_out,   //sum output  
    output c_out      //carry output  
);  
    wire c1, c2, c3, psum; //wiring needed  
  
    xor    xor_0    (a, b, psum);          //half-adder partial output  
    xor    xor_1    (psum, cin, sum_out);  //half-adder output  
    and    and_0    (a, cin, c1);          //carry condition 1  
    and    and_1    (b, cin, c2);          //carry condition 2  
    and    and_2    (a, b, c3);            //carry condition 3  
    or     or_0     (c1, c2, c3, c_out);    //form carry output  
endmodule
```

## Verilog - Modules (cont.)

Back to instantiation.... Typically, complex modules are connected under the top level

```
//module instantiations
shift_reg shift_reg_1(
    .clk          (clk_50),
    .reset_n      (reset_n),
    .data_ena     (data_ena),
    .serial_data  (serial_data),
    .parallel_data (shift_reg_out));
```

```
ctrl_50mhz ctrl_50mhz_0(
    .clk_50  (clk_50),
    .reset_n (reset_n),
    .data_ena (data_ena),
    .a5_or_c3 (a5_or_c3),
    .wr_fifo  (wr_fifo));
```

%[draw partial block diagram showing connections]

# Verilog - Modules (cont.)

## Dissection of shift\_reg instantiation

```
shift_reg shift_reg_1(    //module name and instance of the module
.clk                    (clk_50),    //the pin clk is connected to the wire clk_50
.reset_n                (reset_n),  //the "." denotes the pin
.data_ena               (data_ena), //the value in the parens is the wire
.serial_data            (serial_data),
.parallel_data          (shift_reg_out)); //wires and pins do not have to match
[show with arrows and such the various parts]
```

This method of declaring pins/wires is called "named association".  
This is the preferred way of doing instantiation when pins/names differ.  
Comment each wire connection if its function is not obvious.

## Verilog - Modules (cont.)

Its possible to connect wires to pins by position alone

Called "positional association" ... **just say no!**

```
shift_reg shift_reg_1(clk_50,reset_n,data_ena,serial_data,shift_reg_out);
```

How do you know its connected correctly?

What if the module had 50 pins on it?

What if you wanted to add wire in the middle of the list?

***Do not use Positional Association!***

It saves time once, and costs you dearly afterwards

# Verilog - Modules (cont.)

## System Verilog instantiation short cuts

These are useful when most all pins/wires have the same name

```
shift_reg shift_reg_1(  
    .clk          (clk          ),  
    .reset_n      (reset_n      ),  
    .data_ena     (data_ena     ),  
    .serial_data  (serial_data  ),  
    .parallel_data (shift_reg_out));
```

Implicit naming can shorten this to:

```
shift_reg shift_reg_1(  
    .clk,                                //implicit .name port connection  
    .reset_n,                            //implicit .name port connection  
    .data_ena,                           //implicit .name port connection  
    .serial_data,                        //implicit .name port connection  
    .parallel_data (shift_reg_out)); //named association, pin/wire differ
```

"implicit name" and "named association" form can be mixed as required

## Verilog - Modules (cont.)

Another instantiation short cut

```
ctrl_50mhz ctrl_50mhz_0(  
    .clk_50    (clk_50  ),  
    .reset_n   (reset_n ),  
    .data_ena  (data_ena),  
    .a5_or_c3  (a5_or_c3),  
    .wr_fifo   (wr_fifo));
```

All pins and wires have the same name, so...

```
ctrl_50mhz ctrl_50mhz_0(.*);    //wow, that's a short cut!
```

This is the most powerful form of implicit association.  
Its best reserved for use at the top level testbench/top module.  
Otherwise, it could hide intent.

## Verilog - Modules (cont.)

Unconnected port pins may be left unconnected like this...

```
ctrl_50mhz ctrl_50mhz_0(  
    .clk_50    (clk_50  ),  
    .reset_n   (reset_n ),  
    .data_ena  (data_ena),  
    .a5_or_c3  (        ), //parenthesis left empty  
    .wr_fifo   (wr_fifo));
```

Unused ports may be left out of the port list...*not recommended*

Make your intent clear!



# Verilog - Modules (cont.)

Parametrization of modules allows for module reuse (powerful!)

```
//-----  
//Shift register with width parameter  
//-----  
module shift_reg #(parameter width=8) (  
    input                reset_n,          //reset async active low  
    input                clk,              //input clock  
    input                data_ena,         //serial data enable  
    input                serial_data,      //serial data input  
    output logic [width-1:0] parallel_data //parallel data out  
);  
always @ (posedge clk, negedge reset_n)  
    if(!reset_n)    parallel_data <= '0; //could not do "width'd0"  
    else if (data_ena)  
        parallel_data <= {serial_data, parallel_data[width-1:1]};  
endmodule
```

In the module declaration, the keyword "parameter" is not required  
It does read more clearly however

## Verilog - Modules (cont.)

Paramaterized "shift\_reg" could now be instantiated like this:

```
module top_module;
  logic [31:0] parallel_data;
  wire reset_n, clk, data_ena, serial_data;

  //instantiate shift reg, overriding width to 32 bits
  shift_reg #(.width(32)) sr_inst0(
    .reset_n      (reset_n      ),
    .clk          (clk          ),
    .data_ena     (data_ena     ),
    .serial_data  (serial_data  ),
    .parallel_data (parallel_data));
endmodule
```

## Verilog - Modules (cont.)

- ▶ Verilog modules provide a coarse-grain structuring mechanism
- ▶ Modules contain RTL logic or other modules
- ▶ Modules provide an abstraction mechanism via complexity hiding
- ▶ Modules provide a way to reuse designs
- ▶ How is a Verilog module different from a C function?