

# Conditional Concurrent Signal Assignment

**The conditional concurrent signal assignment statement is modeled after the “if statement” in software programming languages.**

The general format for this statement is:

```
target_signal <= value1 WHEN condition1 ELSE
                    value2 WHEN condition2 ELSE
                    value3 WHEN condition3 ELSE
                    .....
                    valueN;
```

When one or more of the signals on the right-hand side change value, the statement executes, evaluating the condition clauses in textual order from top to bottom. If a condition is found to be true, the corresponding expression is executed and the values are assigned to the target signal.

The conditions must evaluate to a boolean value. i.e, True or False

Example:

```
z_out <=  a_input WHEN (select = "00") ELSE
          b_input WHEN (select = "01") ELSE
          c_input WHEN (select = "10") ELSE
          d_input WHEN (select = "11") ELSE
          "X"; -- what am I?
```

# Conditional Concurrent Signal Assignment


**What happens when we don't completely specify all the choices?**

**First, lets do it right.**

```
--5:1 mux, 1 bit wide
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY mux5_1_1wide IS
  PORT(
    a_input   : IN STD_LOGIC;  --input a
    b_input   : IN STD_LOGIC;  --input b
    c_input   : IN STD_LOGIC;  --input c
    d_input   : IN STD_LOGIC;  --input d
    e_input   : IN STD_LOGIC;  --input e
    sel       : IN STD_LOGIC_VECTOR(2 DOWNTO 0);  --sel input
    z_out     : OUT STD_LOGIC  --data out
  );
END mux5_1_1wide;
ARCHITECTURE beh OF mux5_1_1wide IS
  BEGIN
    z_out <= a_input WHEN (sel = "000") ELSE
           b_input WHEN (sel = "001") ELSE
           c_input WHEN (sel = "010") ELSE
           d_input WHEN (sel = "011") ELSE
           e_input WHEN (sel = "100") ELSE
           'X';
  END beh;
```

**When synthesized, we get:**

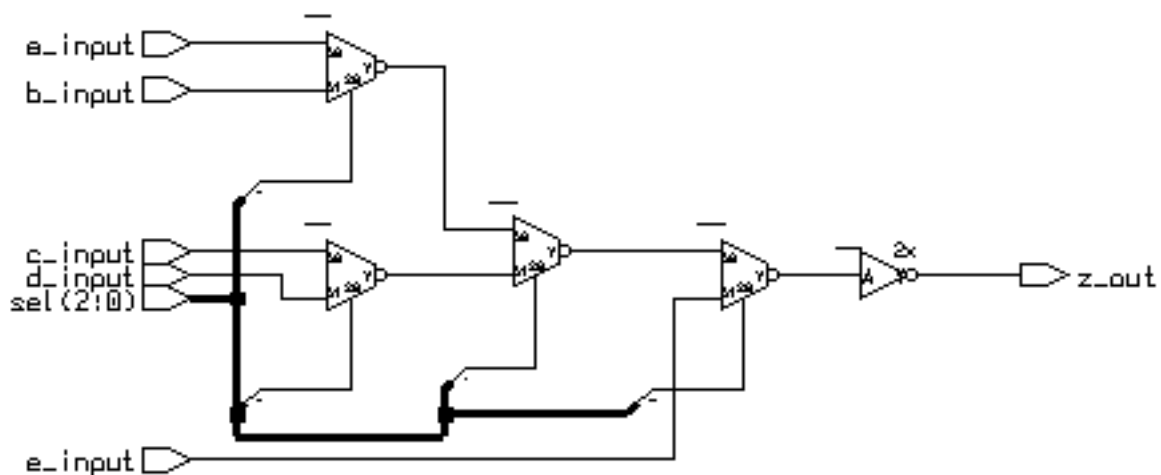


# Conditional Concurrent Signal Assignment

Now let's incompletely specify the choices.

```
ARCHITECTURE noelse OF mux5_1_1wide IS
  BEGIN
    z_out <= a_input WHEN (sel = "000") ELSE
             b_input WHEN (sel = "001") ELSE
             c_input WHEN (sel = "010") ELSE
             d_input WHEN (sel = "011") ELSE
             e_input WHEN (sel = "100"); -- no ending else
  END beh;
```

When synthesized:

 

What happened?

- How does a transparent latch operate?
- What is the truth table for the decoder to the latch "clk" pin?

<u>sel(2:0)</u>	<u>latch enable pin</u>	<u>behavior</u>
000	1	latch is transparent
001	1	ditto
010	1	ditto
011	1	ditto
100	1	ditto
101	0	latch is in "hold" state
110	0	hold state
111	0	hold state