

Concurrent Statements - GENERATE

VHDL provides the GENERATE statement to create well-patterned structures easily.

Any VHDL concurrent statement can be included in a GENERATE statement, including another GENERATE statement.

Two ways to apply

- **FOR scheme**
- **IF scheme**


FOR Scheme Format:

```
label : FOR identifier IN range GENERATE  
    concurrent_statements;  
END GENERATE [label];
```

Generate Statement - FOR scheme

```
ARCHITECTURE test OF test IS
  COMPONENT and02
    PORT( a0 : IN  std_logic;
          a1 : IN  std_logic;
          y  : OUT std_logic);
  END COMPONENT and02;

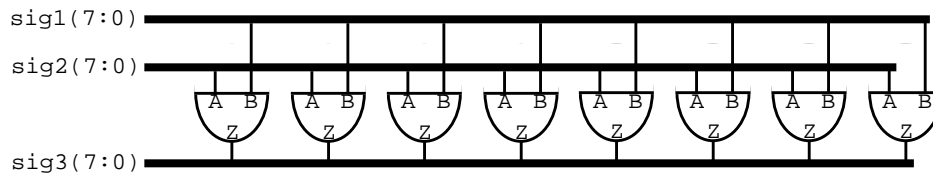BEGIN
  G1 : FOR n IN (length-1) DOWNT0 0 GENERATE
    and_gate:and02
      PORT MAP( a0 => sig1(n),
                a1 => sig2(n),
                y  => z(n));
  END GENERATE G1;
END test;
```



With the FOR scheme

- All objects created are similar.
- The **GENERATE** parameter must be discrete and is undefined outside the **GENERATE** statement.
- Loop cannot be terminated early

Note: This structure could have been created by:

```
sig3 <= sig1 AND sig2;
```

provided the AND operator was overloaded for vector operations.

Generate Statement - IF scheme

Allows for conditional creation of components.

Can't use ELSE or ELSIF clauses.


IF Scheme Format:

```
label : IF (boolean_expression) GENERATE  
    concurrent_statements;  
END GENERATE [label];
```

The next slide will show how we can use both FOR and IF schemes.

Use of GENERATE - An example

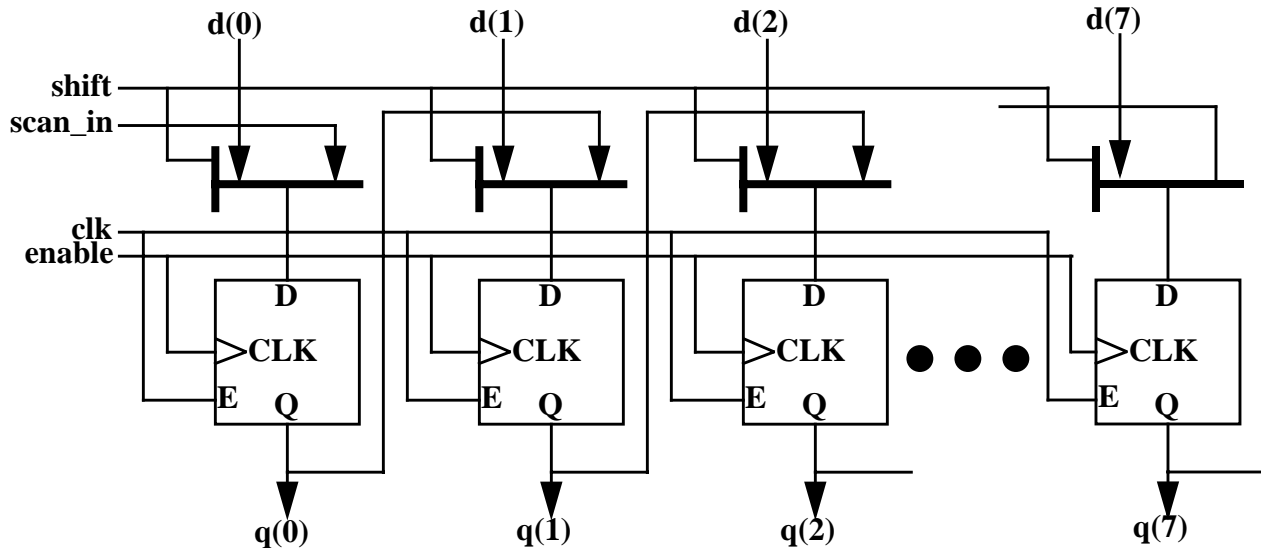Suppose we want to build an 8-bit shift register.



Suppose furthermore that we had previously defined the following components:

```
ENTITY dff IS
  PORT(d, clk, en      : IN    std_logic;
        q, qn          : OUT   std_logic);
END ENTITY dff;
```

```
ENTITY mux21 IS
  PORT(a, b, sel      : IN    std_logic;
        z              : OUT   std_logic);
END ENTITY mux21;
```

Using GENERATE

From the block diagram we know what the entity should look like.

```
ENTITY sr8 IS
  PORT(
    din      : IN std_logic_vector(7 DOWNTO 0);
    sel      : IN std_logic;
    shift    : IN std_logic;
    scan_in  : IN std_logic;
    clk      : IN std_logic;
    enable   : IN std_logic;
    dout     : OUT std_logic_vector(7 DOWNTO 0));
```

Within the architecture statement we have to declare the components within the declaration region before using them. This is done as follows:

```
ARCHITECTURE example OF sr8 IS
  --declare components in declaration area
  COMPONENT dff IS
    PORT(d, clk, en : IN  std_logic;
          q, qn     : OUT std_logic);
  END COMPONENT;
  COMPONENT mux21 IS
    PORT(a, b, sel : IN  std_logic;
          z        : OUT std_logic);
  END COMPONENT;
```

Component declarations look just like entity clauses, except COMPONENT replaces ENTITY. Use cut and paste to prevent mistakes!

Using Generate

After the component declarations, we declare the internal signal.

```
SIGNAL mux_out : std_logic_vector(7 DOWNT0 0);
```

With loop and generate statements, instantiate muxes and dff's.

```
BEGIN
  OUTERLOOP: FOR i IN 0 TO 7 GENERATE
    INNERLOOP1: IF (i = 0) GENERATE
      MUX: mux21 PORT MAP(a => d(i),
                          b => scan_in,
                          z => mux_out(i));
      FLOP: dff PORT MAP(d => mux_out(i),
                        clk => clk,
                        en => enable,
                        q  => dout(i)); --qn not listed
    END GENERATE INNERLOOP1;
    INNERLOOP2: IF (i > 0) GENERATE
      MUX: mux21 PORT MAP(a => d(i),
                          b => dout(i-1),
                          z => mux_out(i));
      FLOP: dff PORT MAP(d => mux_out(i),
                        clk => clk,
                        en => enable,
                        q  => dout(i),
                        qn => OPEN); --qn listed as OPEN
    END GENERATE INNERLOOP2;
  END GENERATE OUTERLOOP;
END example;
```

Concurrent Statements - ASSERT

The assertion statement checks a condition and reports a message with a severity level if the condition is not true.

Format:

```
ASSERT condition;
```

```
ASSERT condition REPORT "message"
```

```
ASSERT condition SEVERITY level;
```

```
ASSERT condition REPORT "message" SEVERITY  
level;
```

Example:

```
ASSERT signal_input = '1'  
    REPORT "Input signal_input is not 1"  
    SEVERITY WARNING;
```

Severity levels are:

- **Note** - general information
- **Warning** - undesirable condition
- **Error** - task completed, result wrong
- **Failure** - task not completed

Simulators stop when the severity level matches or exceeds the specified severity level.

Simulators generally default to a severity level of “failure”

Assert Statements

Assert statements may appear within:

- **concurrent statement areas**
- **sequential statement areas**
- **statement area of entity declaration**

Example:

```
ENTITY rs_flip_flop IS
    PORT(r, s      : IN  std_logic;
          q, qn    : OUT std_logic);
END rs_flip_flop;

ARCHITECTURE behav OF rs_flip_flop IS
BEGIN
    ASSERT NOT (r = '1' AND s = '1')
        REPORT "race condition!"
        SEVERITY FAILURE;
        *
        *
        *
END behav;
```

Remember, the ASSERT statement triggers when the specified condition is *false*.

Concurrent Statements - Process Statement

The PROCESS statement encloses a set of *sequentially executed* statements. Statements within the process are executed in the order they are written. However, when viewed from the “outside” from the “outside”, a process is a single concurrent statement.

Format:

```
label:
PROCESS (sensitivity_list) IS
  --declarative statements
  BEGIN
    --
    --sequential activity statements
    --only sequential statements go in here
    --
  END PROCESS [label];
```

Example:

```
ARCHITECTURE example OF nand_gate IS
  BEGIN
    nand_gate: PROCESS (a,b)
    BEGIN
      IF a = '1' AND b = '1' THEN
        z <= '0';
      ELSE
        z <= '1';
      END IF;
    END PROCESS nand_gate;
```

Why use a process? Some behavior is easier and more natural to describe in a sequential manner. The next state decoder in a state machine is an example.

Process Sensitivity List

The process *sensitivity list* lists the signals that will cause the process statement to be executed.

Any transition on *any* of the signals in the signal sensitivity list will cause the process to execute.

Example:

```
ARCHITECTURE example OF nand_gate IS
  BEGIN
    bozo: PROCESS (a,b)
      -- wake up process if a and/or b changes
      BEGIN
        IF a = '1' AND b = '1' THEN
          z <= '0' ;
        ELSE
          z <= '1' ;
        END IF;
      END PROCESS bozo;
END example;
```

Signals to put in the sensitivity list:

- Signals on the right hand side of assignment statements.
- Signals used in conditional expressions

What happens if a signal is left out of the sensitivity list?
What does the synthesis tool do with the sensitivity list?

Avoid problems with sensitivity list omissions by compiling with “synthesis check” on. Like this:

```
vcom -93 -check_synthesis test.vhd
```

What about Delay?

Note that so far we haven't mentioned delay. Why not?

Both propagation delay and wiring delay is a real-world problem that must be eventually dealt with. However, at the model creation stage, it is helpful to not have to consider delay. Instead, the emphasis is to create correct functional behavior.

However, this does not mean the designer can go about designing with no concern about delay. When writing HDL code, you must have a very good idea what the structure you are creating will look like in a schematic sense. Otherwise, the synthesized circuit may have excessive delays, preventing its operation at the desired speed.

VHDL does have statements for representing several different kinds of delay. However, when describing a circuit to be synthesized, we never use them because the synthesis tool ignores them on purpose.

The aspect of delay is added to a synthesized netlist after the functionality has been proven correct. When real delays are inserted into your design (this is done automatically) often a whole world of problems crop up.


The basic idea is to make a model work, and then make it work at the desired speed. Only experience will help you determine how fast your HDL code will eventually run.

Delay Types

VHDL signal assignment statements prescribe an amount of time that must transpire before a signal assumes its new value.

This prescribed delay can be in one of three forms:

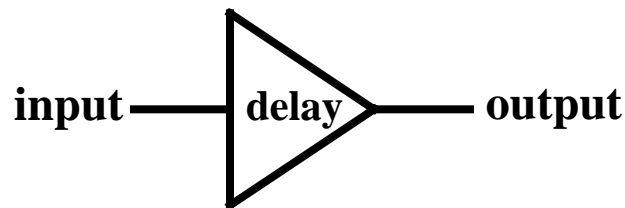- **Transport:**
propagation delay only
- **Inertial:**
minimum input pulse width and propagation delay
- **Delta:**
the default if no delay time is explicitly specified



Signal assignment is actually a *scheduling* for a future value to be placed on the signal.

Signals maintain their original value until the time for the scheduled update to occur.

Any signal assignment will incur a delay of one of the three types above.


Delay Types - Transport

Delay must be explicitly specified by the user by the keyword `TRANSPORT`.

The signal will assume the new value after specified delay.

 Example:

```
output <= TRANSPORT buffer(input) AFTER 10ns;
```



Transport delay is like a infinite bandwidth transmission line.

Delay Types - Inertial

Inertial delay is the default in VHDL statements which contain the “AFTER” clause.


Inertial delay provides for specification of input pulse width, i.e. ‘inertia’ of output, and propagation delay.

Format:

```
target <= [REJECT time_expr] INERTIAL waveform  
AFTER time
```

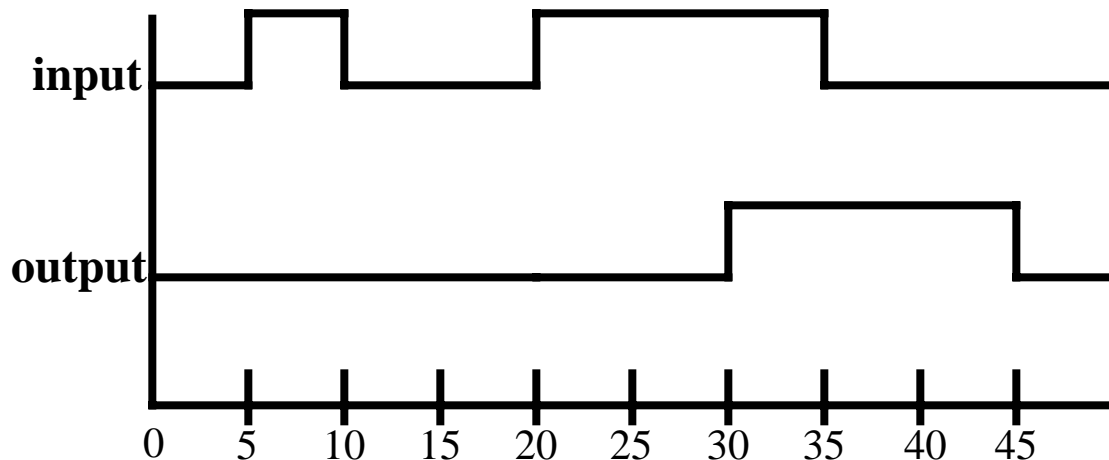Example (most common):

```
output <= buffer(input) AFTER 10ns;
```



When not used, the REJECT clause defaults to the value of the AFTER clause.


Inertial delay acts like a real gate. It “eats” pulses narrower in width than the propagation delay.

Delay Types - Inertial

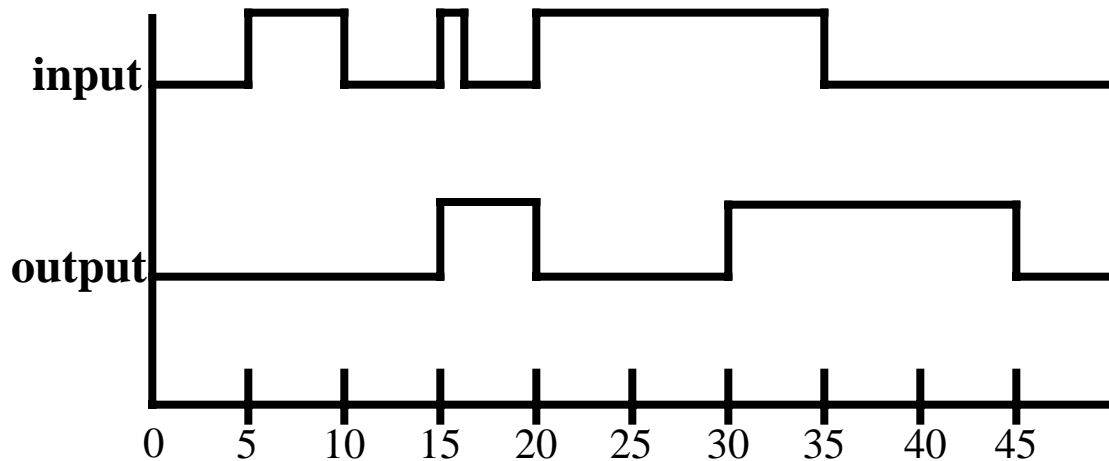Example of gate with “inertia” smaller than propagation delay:

This shows a buffer that has a prop delay of 10ns, but passes pulses greater than 5ns.

```
output <= REJECT 5ns INERTIAL buffer(input)
AFTER 10ns;
```



REJECT can be used only with the keyword **INERTIAL**.

Delay Types - Delta Delay

Delta delay is the signal assignment propagation delay if none is explicitly prescribed.

A delta time is an infinitesimal, but quantized unit of time.

An infinite number of delta times equals zero simulator time.

The delta delay mechanism provides a minimum delay so that the simulation cycle can operate correctly when no delays are stated explicitly. That is:

- all active processes to execute in the same simulation cycle
- each active process will suspend at some *wait* statement
- when all processes are suspended, simulation is advanced the minimum time step necessary so that some signals can take on their new values
- processes then determine if the new signal values satisfy the conditions to proceed again from the wait condition

Sequential Operations

Statements within processes are executed in the order in which they are written.

The sequential statements we will look at are:

- **Variable Assignment**
- **Signal Assignment***
- **If Statement**
- **Case Statement**
- **Loops**
- **Next Statement**
- **Exit Statement**
- **Return Statement**
- **Null Statement**
- **Procedure Call**
- **Assertion Statement***

***Have both a sequential and concurrent form.**

Variable Declaration and Assignment

Variables can be used only within sequential areas.

Format:

```
VARIABLE var_name : type [:= initial_value];
```

Example:

```
VARIABLE spam : std_logic := '0';
```

```
ARCHITECTURE example OF funny_gate IS
SIGNAL c : STD_LOGIC;
BEGIN
    funny: PROCESS (a,b,c)
    VARIABLE temp : std_logic;
    BEGIN
        temp := a AND b;
        z <= temp OR c;
    END PROCESS funny;
END ARCHITECTURE example;
```

Variables assume value instantly.

Variables simulate more quickly since they have no time dimension.

Remember, variables and signals have different assignment operators:

```
a <= new_value; --signal assignment
a := new_value; --variable assignment
```

Sequential Operations - IF Statement

Provides conditional control of sequential statements.

Condition in statement must evaluate to a Boolean value.

Statements execute if boolean evaluates to TRUE.

Formats:

```
IF condition THEN                                --simple IF (latch)
-- sequential statements
END IF;
```

```
IF condition THEN                                --IF-ELSE
-- sequential statements
ELSE
-- sequential statements
END IF;
```

```
IF condition THEN                                --IF-ELSIF-ELSE
-- sequential statements
ELSIF condition THEN
-- sequential statements
ELSE
-- sequential statements
END IF;
```

Sequential Operations - IF Statement

Examples:


```
--enabled latch
IF (a = '1' AND b = '0') THEN
    spud <= potato;
END IF;
```

```
--a very simple "gate"
IF (lucky = '1') THEN
    buy_lottery_tickets <= '1';
ELSE
    buy_lottery_tickets <= '0';
END IF;
```

```
--a edge triggered 4-bit counter with enable
--and asynchronous reset
IF (reset = '1') THEN
    cnt <= "0000";
ELSIF (clk'EVENT AND clk = '1') THEN
    IF enable = '1' THEN
        cnt <= cnt + 1;
    END IF ;
END IF;
```

**A Hint: Only IF.....
needs END IF**


Synthesized example from previous page

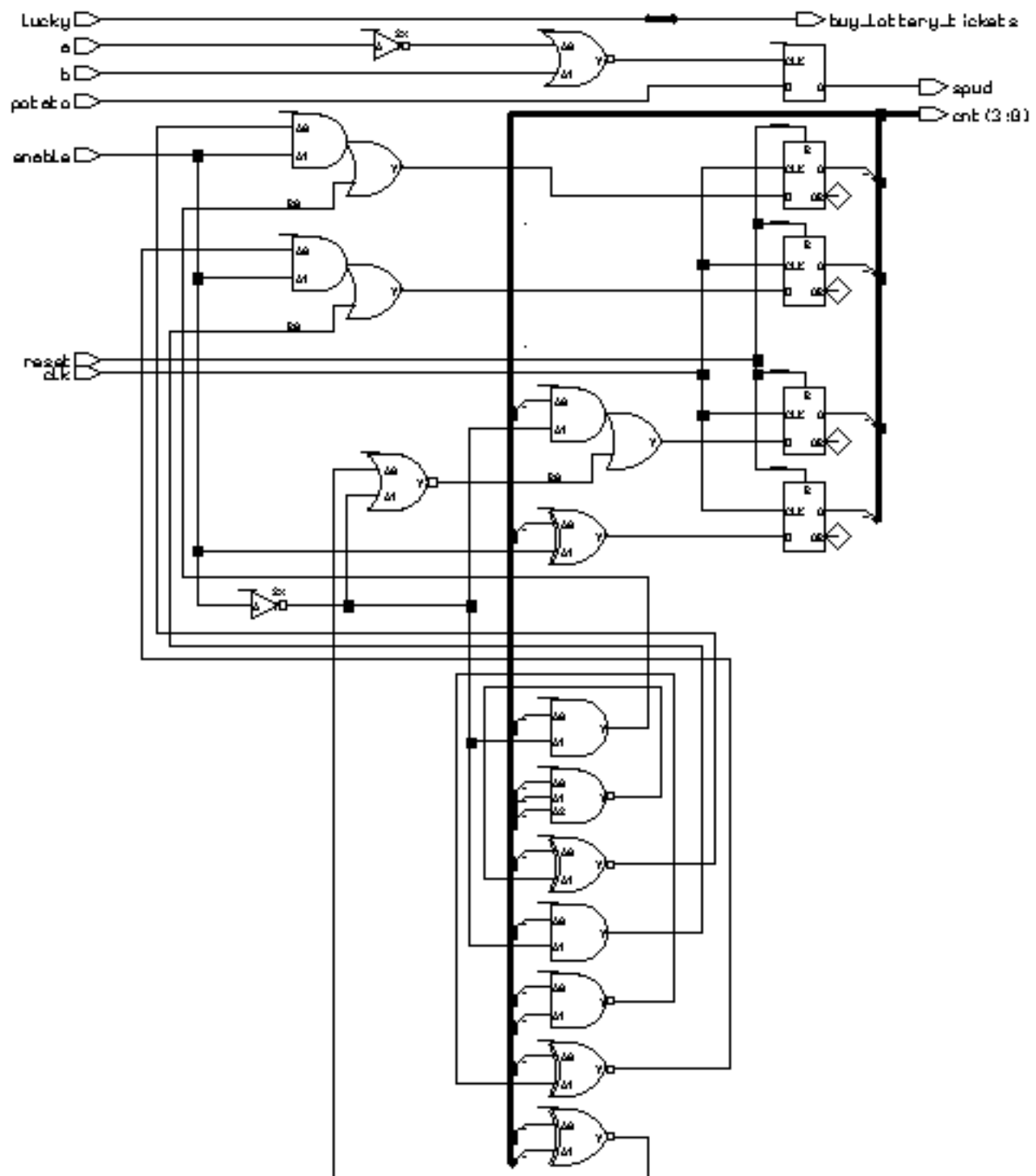

IF Implies Priority

The if statement implies a priority in how signals are assigned to the logic synthesized. See the code segment below and the synthesized gates.

```
ARCHITECTURE tuesday OF example IS
BEGIN
  wow: PROCESS (a, b, c, d, potato, carrot, beet, spinach, radish)
  BEGIN
    IF (a = '1') THEN
      vegatable <= potato;
    ELSIF (b = '1') THEN
      vegatable <= carrot;
    ELSIF (c = '1') THEN
      vegatable <= beet;
    ELSIF (d = '1') THEN
      vegatable <= spinach;
    ELSE
      vegatable <= radish;
    END IF;
  END PROCESS wow;
END ARCHITECTURE tuesday;
```

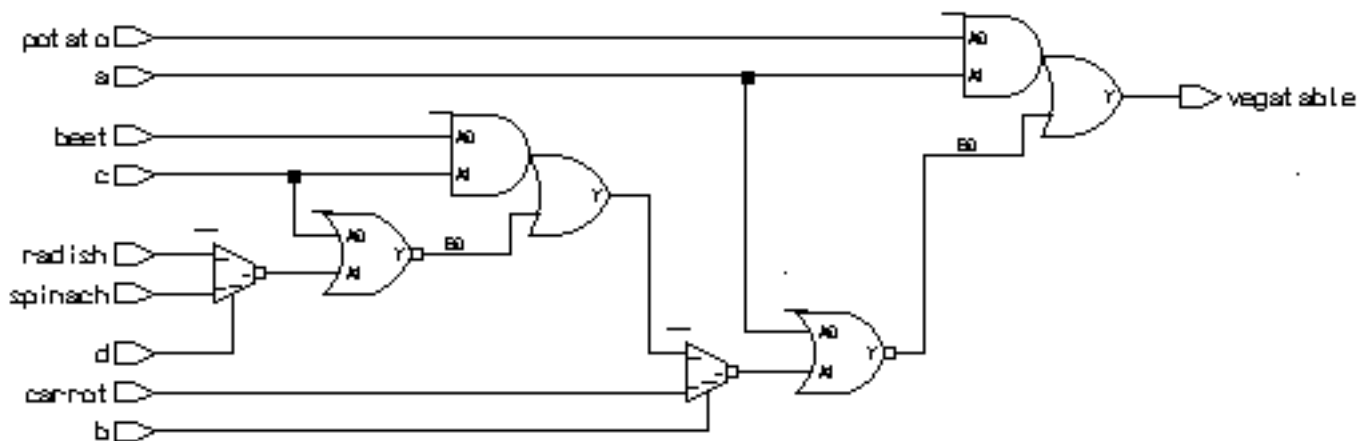

what are the delays for each path?

Note how signal with the smallest gate delay through the logic was the first one listed. You can use such behavior to your advantage. Note that use of excessively nested **IF** statements can yield logic with lots of gate delay.

Beyond about four levels of **IF** statement, the **CASE** statement will typically yield a faster implementation of the circuit.

Area and delay of nested IF statement

We can put reporting statements in our synthesis script to tell us the number of gate equivalents and the delays through all the paths in the circuit. For this example, we included the two statements:

```
report_area -cell area_report.txt
report_delay -show_nets delay_report.txt
```

In *area_report.txt*, we see:

```
*****
Cell: example      View: tuesday      Library: work
*****
Cell      Library  References      Total Area
ao21      ami05_typ  2 x      1      2 gates
mux21      ami05_typ  2 x      2      4 gates
nor02      ami05_typ  2 x      1      2 gates

Number of gates :                      8
```

The *delay_report.txt* has the delay information:

```
          Critical Path Report
Critical path #1  spinach to  vegetable  3.42ns
Critical path #2  radish  to  vegetable  3.41ns
Critical path #3  d       to  vegetable  3.31ns
Critical path #4  c       to  vegetable  2.88ns
Critical path #5  c       to  vegetable  2.57ns
Critical path #6  beet    to  vegetable  2.48ns
Critical path #7  carrot  to  vegetable  1.63ns
Critical path #8  b       to  vegetable  1.52ns
Critical path #9  a       to  vegetable  1.08ns
Critical path #10 a       to  vegetable  1.46ns
```

If implies priority (cont.)

The order in which the IF's conditional statement are evaluated also makes a difference in how the outputs value is assigned. For example, the first check is for (a = '1'). If this statement evaluates true, the output vegetable is assigned "potato" for any input combination where a= '1'.

If the first check fails, the possibilities narrow. If the second check (b= '1') is true, then any combination where a is '0' and b is '1' will assign carrot to vegetable.

If all prior checks fail, an ending ELSE catches all other possibilities.

Relational Operators

The IF statement uses relational operators extensively.

Relational operators return Boolean values (true, false) as their result.

OperatorOperation

=	equal
/=	not equal
<	less than
<=	less than or equal
>	greater than
>=	greater than or equal

The expression for signal assignment and less than or equal are the same. They are distinguished by the usage context.