

GENERATE

VHDL provides the GENERATE statement to create well-patterned structures easily.

Any VHDL concurrent statement can be included in a GENERATE statement, including another GENERATE statement.

Two ways to apply

- **FOR scheme**
- **IF scheme**


FOR Scheme Format:

```
label : FOR identifier IN range GENERATE  
    concurrent_statements;  
END GENERATE [label];
```

Generate Statement - FOR scheme

```
ARCHITECTURE test OF test IS
COMPONENT and02
  PORT( a0 : IN  std_logic;
        a1 : IN  std_logic;
        y  : OUT std_logic);
END COMPONENT and02;

 BEGIN
  G1 : FOR n IN (length-1) DOWNTO 0 GENERATE
    and_gate:and02
      PORT MAP( a0 => sig1(n),
                a1 => sig2(n),
                y  => z(n));
    END GENERATE G1;
END test;
```



With the FOR scheme

- All objects created are similar.
- The GENERATE parameter must be discrete and is undefined outside the GENERATE statement.
- Loop cannot be terminated early

Note: This structure could have been created by:

```
sig3 <= sig1 AND sig2;
```

provided the AND operator was overloaded for vector operations.

Generate Statement - IF scheme

Allows for conditional creation of components.

Can't use ELSE or ELSIF clauses.


IF Scheme Format:

```
label : IF (boolean_expression) GENERATE  
    concurrent_statements;  
END GENERATE [label];
```

The next slide will show how we can use both FOR and IF schemes.

Use of GENERATE - An example

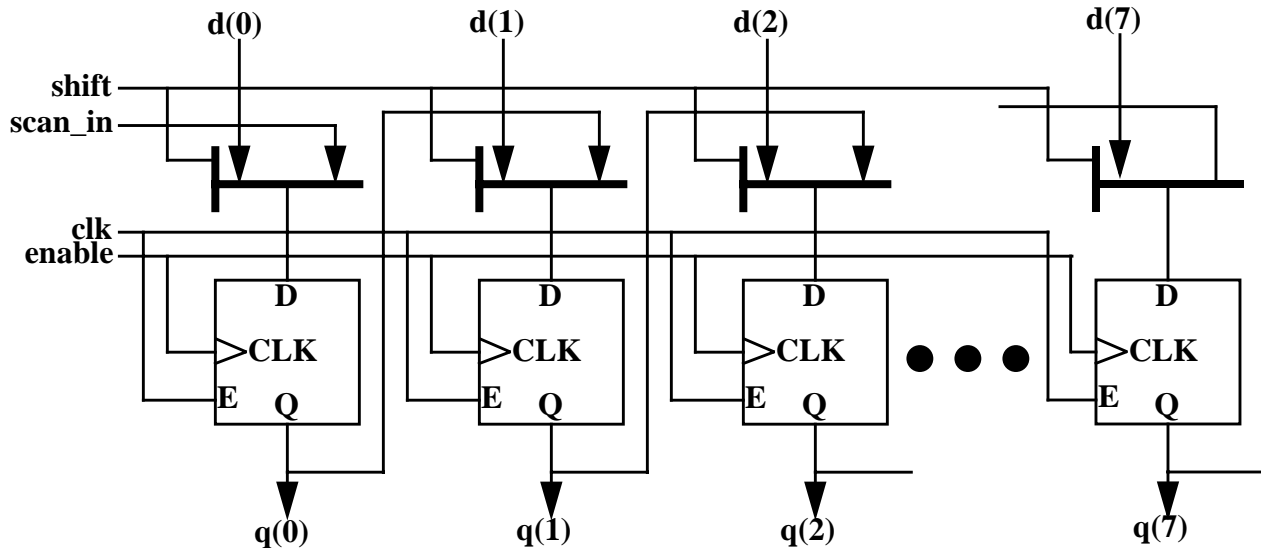Suppose we want to build an 8-bit shift register.



Suppose furthermore that we had previously defined the following components:

```
ENTITY dff IS
  PORT(d, clk, en      : IN    std_logic;
        q, qn          : OUT   std_logic);
END ENTITY dff;
```

```
ENTITY mux21 IS
  PORT(a, b, sel      : IN    std_logic;
        z              : OUT   std_logic);
END ENTITY mux21;
```

GENERATE

From the block diagram we know what the entity should look like.

```
ENTITY sr8 IS
  PORT(
    din      : IN  std_logic_vector(7 DOWNTO 0);
    sel      : IN  std_logic;
    shift    : IN  std_logic;
    scan_in  : IN  std_logic;
    clk      : IN  sed_logic;
    enable   : IN  std_logic;
    dout     : OUT std_logic_vector(7 DOWNTO 0));
```

Within the architecture statement we have to declare the components within the declaration region before using them. This is done as follows:

```
ARCHITECTURE example OF sr8 IS
  --declare components in declaration area
  COMPONENT dff IS
    PORT(d, clk, en  : IN  std_logic;
         q, qn      : OUT std_logic);
  END COMPONENT;
  COMPONENT mux21 IS
    PORT(a, b, sel : IN  std_logic;
         z         : OUT std_logic);
  END COMPONENT;
```

Component declarations look just like entity clauses, except COMPONENT replaces ENTITY. Use cut and paste to prevent mistakes!

Generate

After the component declarations, we declare the internal signal.

```
SIGNAL mux_out : std_logic_vector(7 DOWNTO 0);
```

With loop and generate statements, instantiate muxes and dff's.

```
BEGIN
  OUTERLOOP: FOR i IN 0 TO 7 GENERATE
    INNERLOOP1: IF (i = 0) GENERATE
      MUX: mux21 PORT MAP(a => d(i),
                          b => scan_in,
                          z => mux_out(i));
      FLOP: dff PORT MAP(d => mux_out(i),
                        clk => clk,
                        en => enable,
                        q  => dout(i)); --qn not listed
    END GENERATE INNERLOOP1;
    INNERLOOP2: IF (i > 0) GENERATE
      MUX: mux21 PORT MAP(a => d(i),
                          b => dout(i-1),
                          z => mux_out(i));
      FLOP: dff PORT MAP(d => mux_out(i),
                        clk => clk,
                        en => enable,
                        q  => dout(i),
                        qn => OPEN); --qn listed as OPEN
    END GENERATE INNERLOOP2;
  END GENERATE OUTERLOOP;
END example;
```