

SECTION 2: BIPOLAR JUNCTION TRANSISTORS

ECE 322 – Electronics I





2

Introduction

Transistors

3

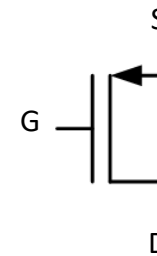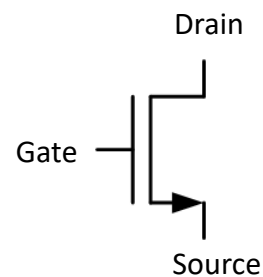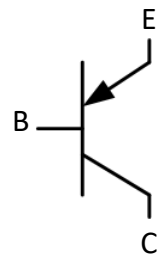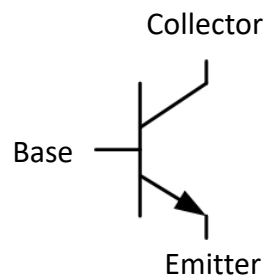
- So far, we have only dealt with **two-terminal** Electrical components
- We now look at **transistors**
 - ▣ **Three-terminal** components
 - ▣ Third terminal makes for very useful, though more complicated, device
- **Semiconductor** devices
 - ▣ Typically silicon, Si
 - ▣ Differently doped (N-type/P-type) Si at each terminal of the device



Transistors

4

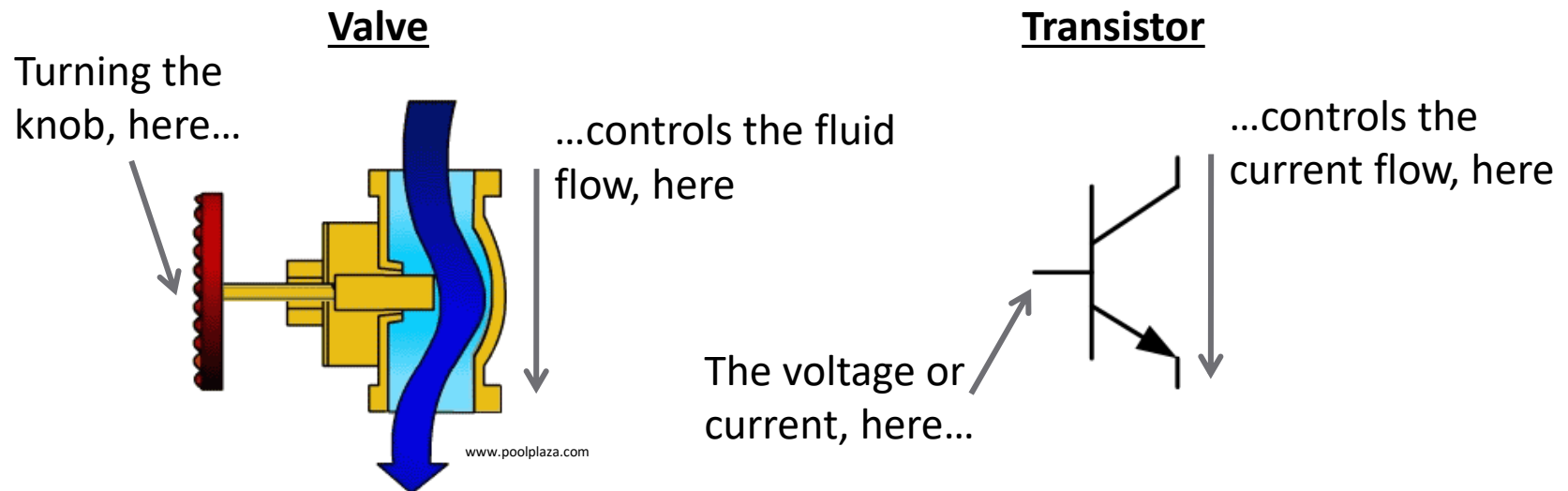- Three terminals:
 - ▣ Current or voltage (possibly small) at one terminal controls current (possibly large) flowing between the other two terminals
- Analogous to **valves**:




- Useful as **switches** or **amplifiers**

Types of Transistors


5

- Two primary classes of transistors:
 - ▣ ***Bipolar Junction Transistors*** – BJTs
 - ▣ ***Metal-Oxide-Semiconductor Field-Effect Transistors*** – MOSFETs

BJTs

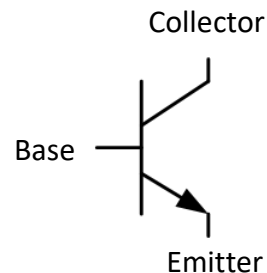


NPN

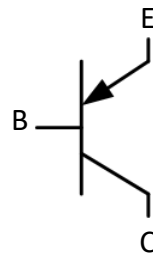


PNP

MOSFETs

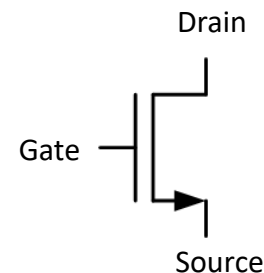

**N-Channel
(NMOS)**

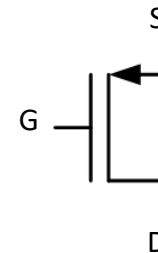


**P-Channel
(PMOS)**


Types of Transistors

6

BJTs

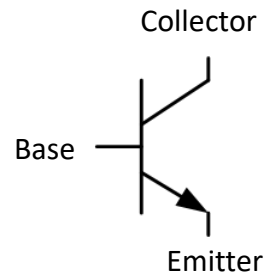


NPN

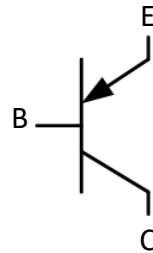


PNP

MOSFETs

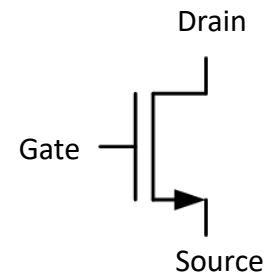

**N-Channel
(NMOS)**

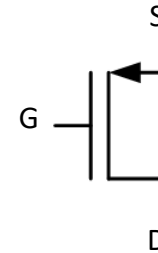

**P-Channel
(PMOS)**


- Difference between NPN/PNP and NMOS/PMOS is the type of semiconductor (N-type/P-type) used at each terminal
- We will learn about both BJTs and MOSFETs:
 - Sections 2, 3: BJTs
 - Sections 4, 5: MOSFETs

Transistor Amplifier Circuits – Preview

7


- Over the next two sections, you will learn to analyze and design circuits like the following

Common-Emitter Amplifier:

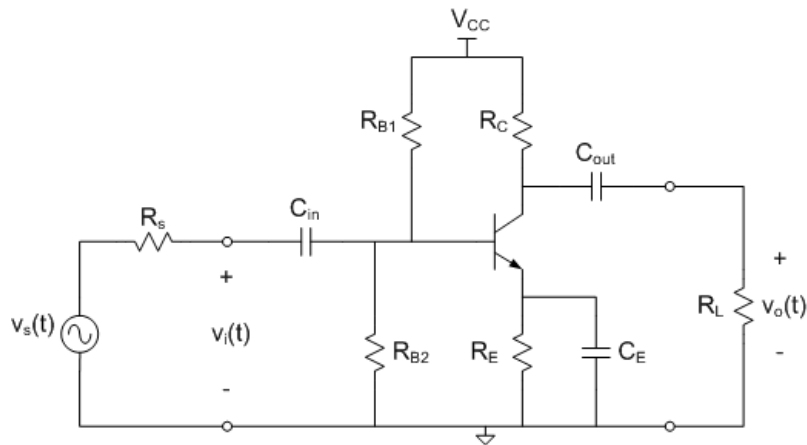

- High voltage gain
- An amplifier

Emitter-Follower Amplifier:

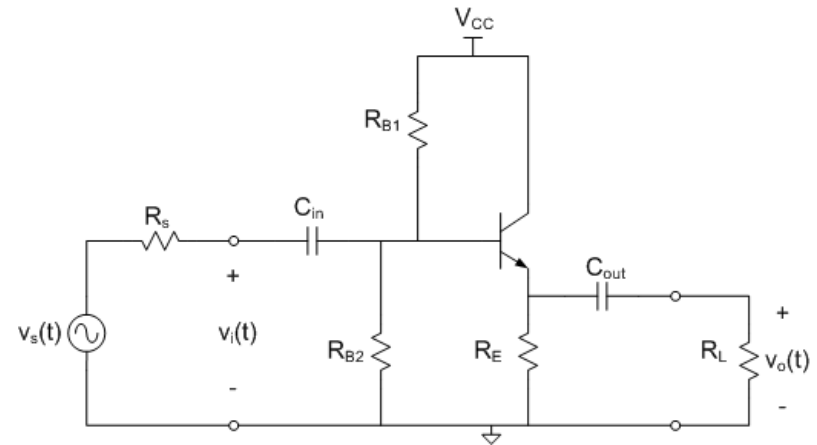

- Near unity gain
- A buffer

8


BJT Fundamentals

Bipolar Junction Transistors


9

- We have seen that diodes are constructed as PN-junctions
 - ▣ BJTs are essentially two back-to-back PN-junctions
- Two types: ***NPN*** and ***PNP***

NPN:

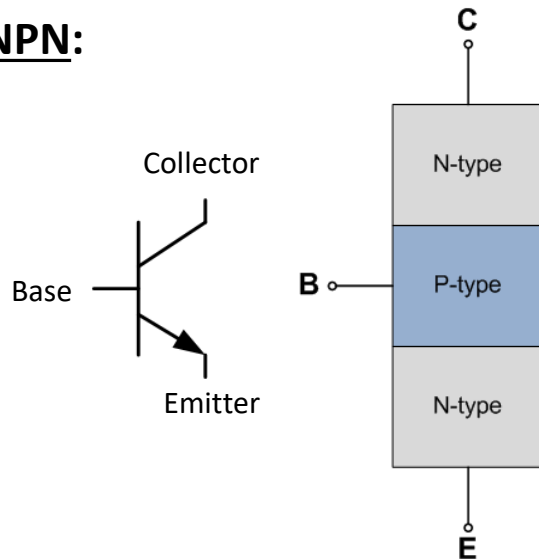

PNP:

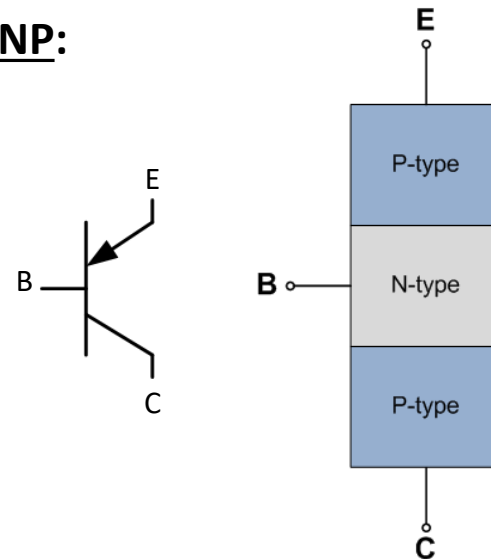


- Symbol mnemonics:
 - ▣ ***NPN***: Not Pointing in
 - ▣ ***PNP***: Point in Please

Terminal Voltages and Currents

10

- Terminal voltages and currents named as shown
- First letter in subscript is the *assumed* higher-potential terminal
 - E.g., $v_{CE} > 0$ if $v_C > v_E$
- Currents positive in direction shown, e.g.,
 - Positive collector current flows into the collector
 - Positive emitter current flows out of the emitter
- ***Lower-case* v or i with *upper-case subscript* denotes **both DC and AC** signal components**

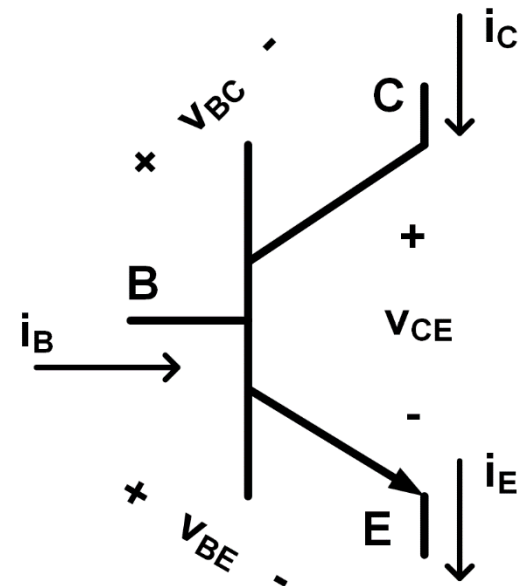

Kirchhoff's Laws


11

- KVL and KCL apply to a transistor, just as they do to any electrical network
- **KVL**
 - ▣ Voltages around the transistor sum to zero:

$$v_{BE} - v_{BC} - v_{CE} = 0$$

- **KCL**
 - ▣ Transistor terminal currents sum to zero:


$$i_B + i_C - i_E = 0$$

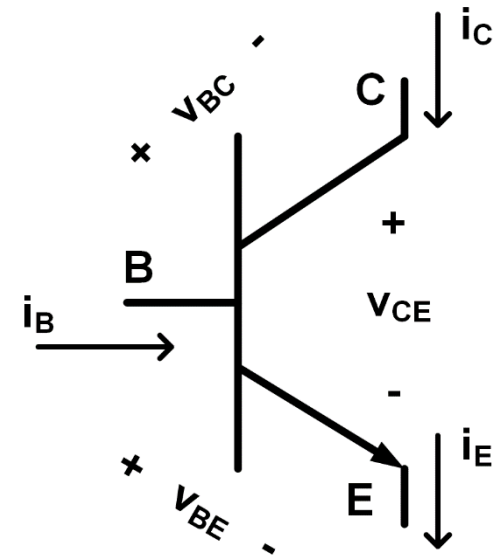

BJT Operating Regions

12

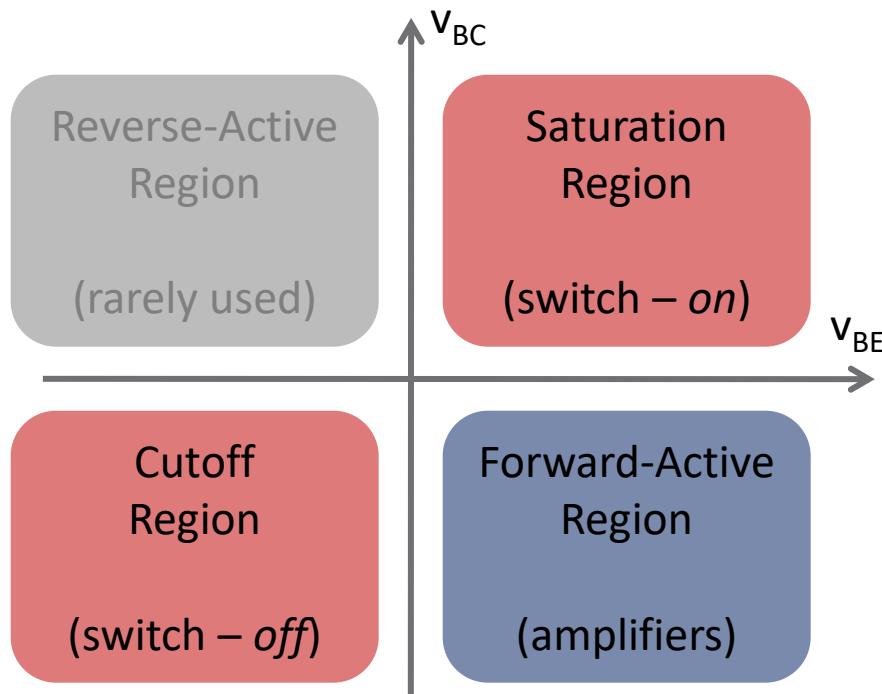- Four operating regions
 - ▣ Defined by polarities of the junction voltages



- **Forward active region**
 - ▣ $v_{BC} < 0$
 - ▣ $v_{BE} > 0$
 - ▣ Linear region – **amplifiers**
- **Saturation region**
 - ▣ $v_{BC} > 0$
 - ▣ $v_{BE} > 0$
 - ▣ C-E looks like a **closed switch**
- **Cutoff region**
 - ▣ $v_{BC} < 0$
 - ▣ $v_{BE} < 0$
 - ▣ C-E looks like an **open switch**


BJT Operating Regions

13

- Transistors used in electronic circuits fall into one of two categories:


- **Linear amplifier**

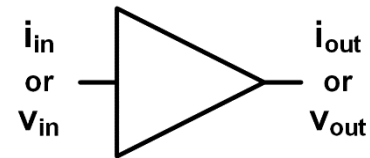- Forward active region
- Transistor provides **linear gain**
- Voltage or current gain
- Greater than or less than unity
- Type/value of gain depends on surrounding circuitry



- **Non-linear switch**

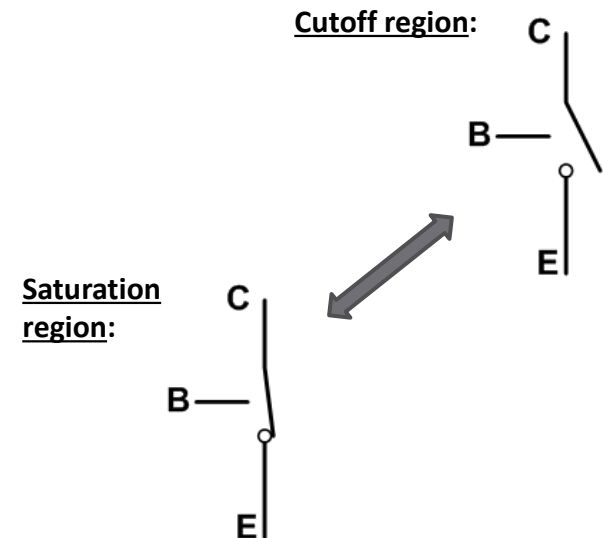- Open or closed switch between collector and emitter
- Cutoff (open) and saturation (closed) regions
- Switching large currents, e.g., controlling a fan
- Digital logic




14

BJTs in the Forward-Active Region

Forward Active Region


15

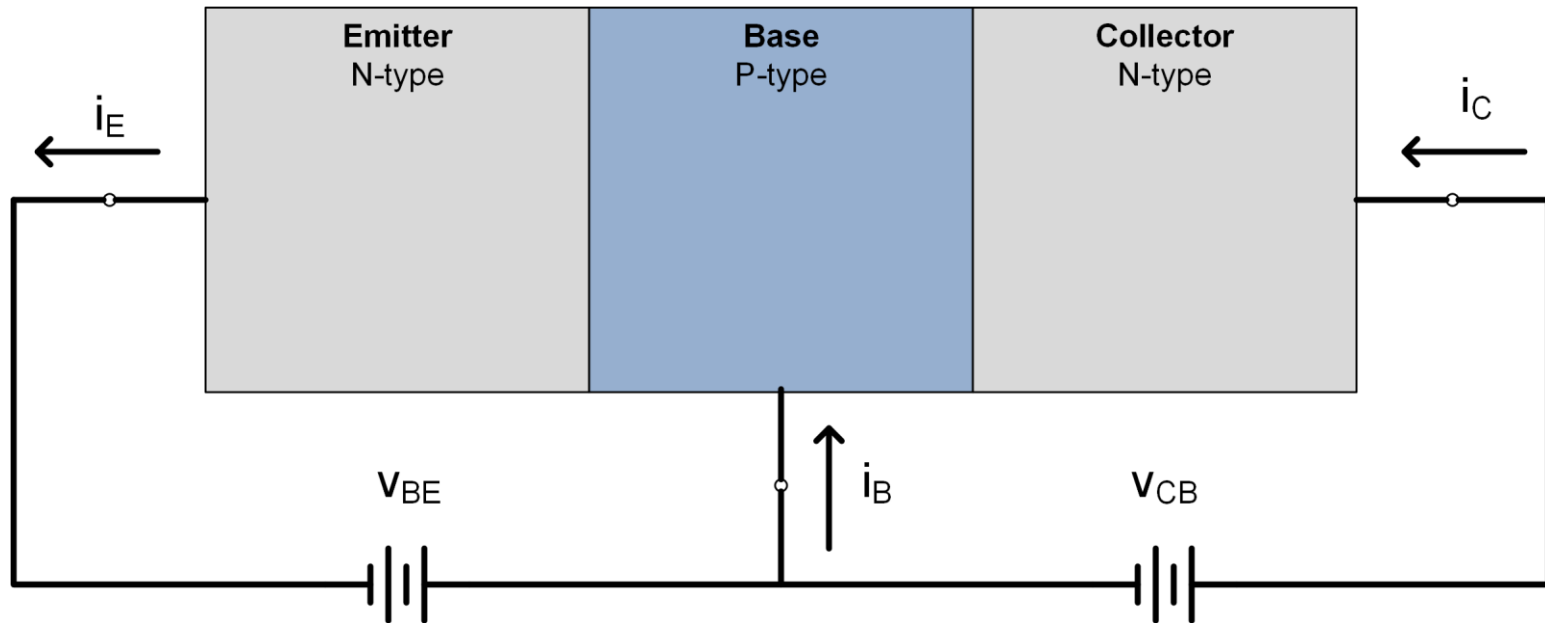

- B-E junction forward biased
 - Forward-biased P-N junction – current, i_E , will flow
- Reverse-biased C-B junction
 - Depletion region surrounding junction

Forward Active Region – Emitter Current


16

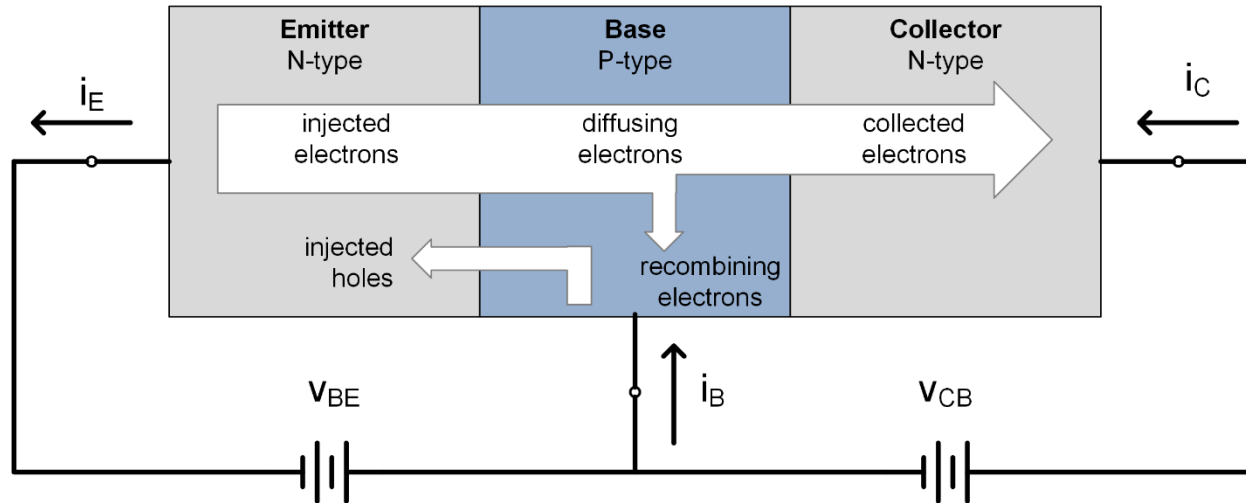

- Two components of emitter current, i_E :
 - ▣ Electrons injected (emitted) from the emitter into the base
 - Large – emitter is heavily-doped – large electron concentration
 - ▣ Holes injected from the base into the emitter
 - Small – base is lightly-doped – small hole concentration

Forward Active Region – Collector Current


17

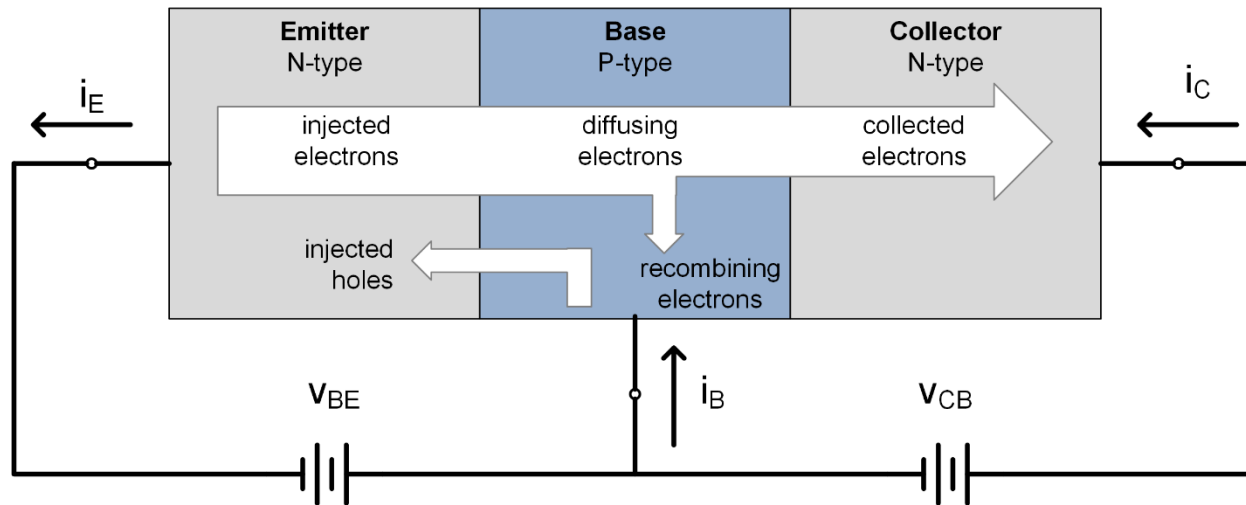

- Electrons – minority carriers – injected from emitter into the base
 - Concentration gradient across base
 - Highest at emitter junction
 - Zero at the C-B depletion region
- Electrons **diffuse** from emitter to collector
 - Swept across C-B depletion region to be **collected** at the collector
 - This is **collector current**, i_C

Forward Active Region – Base Current

18

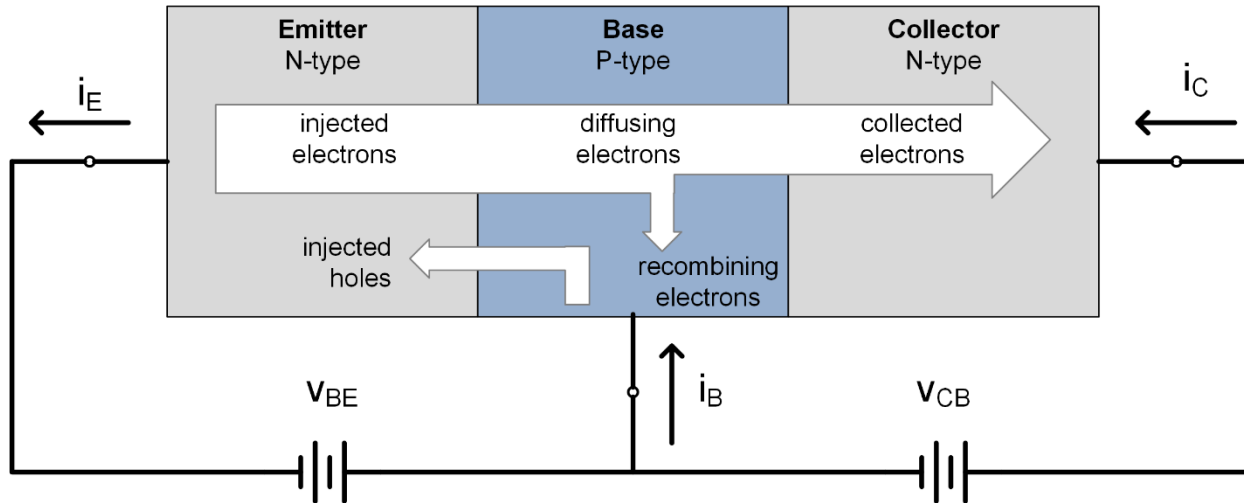

- Two components of base current, i_B
 - ▣ Holes injected from the base into the emitter
 - ▣ Holes recombining with diffusing electrons
- Both are small, due to lightly-doped base
 - ▣ ***Base current is relatively small***

Collector Current


19

- **Collector current** has an **exponential** dependence on base-emitter voltage:

$$i_C = I_S e^{\frac{v_{BE}}{V_{th}}}$$

where:

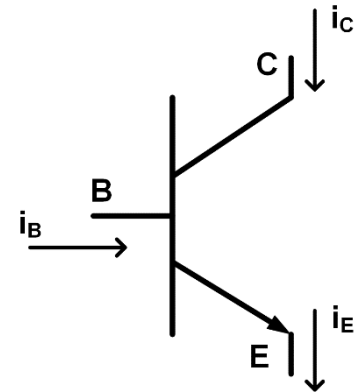- I_S is the transistor's **saturation** or **scale current**
 - $V_{th} = \frac{kT}{q}$ is the **thermal voltage**
- Saturation current, I_S
 - **Scales** with emitter area
 - Strongly depends on temperature



Base Current

20


- **Base current** also has an **exponential** dependence on v_{BE}
- Much smaller than collector current
 - ▣ Base is lightly-doped
 - ▣ Hole currents are small
- Can express base current in terms of collector current:

$$i_B = \frac{i_C}{\beta} = \frac{1}{\beta} I_s e^{\frac{v_{BE}}{V_{th}}}$$

- β is the **common-emitter current gain**:

$$\beta = \frac{i_C}{i_B}$$

- ▣ Typical β values: 50...200

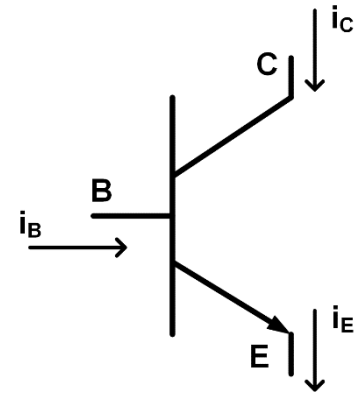

Emitter Current


21

- Applying KCL gives the **emitter current**:

$$i_E = i_C + i_B = i_C + \frac{1}{\beta} i_C$$

$$i_E = \frac{\beta + 1}{\beta} i_C = \frac{\beta + 1}{\beta} I_s e^{\frac{v_{BE}}{V_{th}}}$$

$$i_E = \frac{1}{\alpha} i_C$$

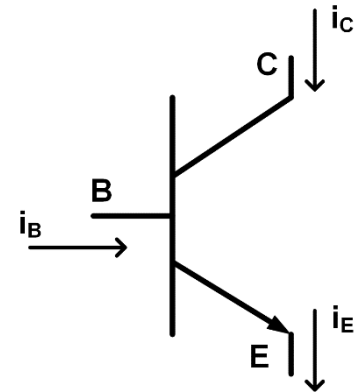

- α is the **common-base current gain**:

$$\alpha = \frac{\beta}{\beta + 1} = \frac{i_C}{i_E}$$

- Typical α values: 0.98...0.998

BJT Current-Voltage Relationships

22

- A few key points:
- Base current is very small compared to collector and emitter currents

$$i_B \ll i_E, i_B \ll i_C$$

- Collector current and emitter current are approximately equal

$$i_C \approx i_E$$

- Small changes in i_B yield large changes in i_C

$$i_C = \beta i_B$$


- i_C is exponentially dependent on v_{BE}
 - Small changes in v_{BE} yield large changes in i_C
 - A potential (transconductance) amplifier
- Collector current is independent of collector voltage (v_{CE})

Plotting I-V Characteristics

23


- BJTs are three-terminal devices
- Plot two different I-V characteristics:
 - ▣ **Input I-V characteristic**
 - ▣ **Output I-V characteristic**

Input I-V Characteristic:

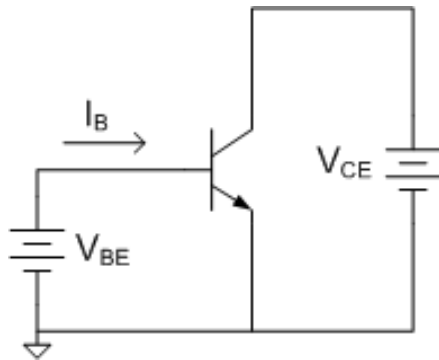

- Single curve:
 - ▣ i_B (or i_C) as a function of v_{BE}

Output I-V Characteristic:

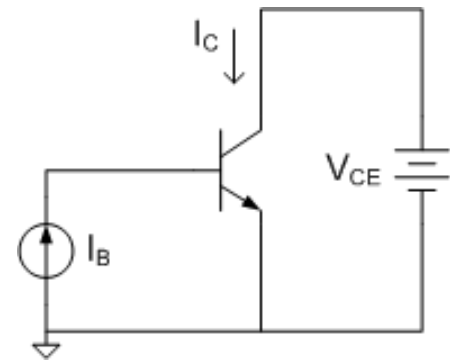

- Family of curves:
 - ▣ i_C as a function of v_{CE}
parameterized by i_B (or v_{BE})

Input I-V Characteristic


24

- Governed by a form of the Shockley equation:

$$i_B = \frac{1}{\beta} I_s e^{\frac{v_{BE}}{V_{th}}}$$


- In the forward-active region:

$$V_{BE} \approx 700 \text{ mV}$$

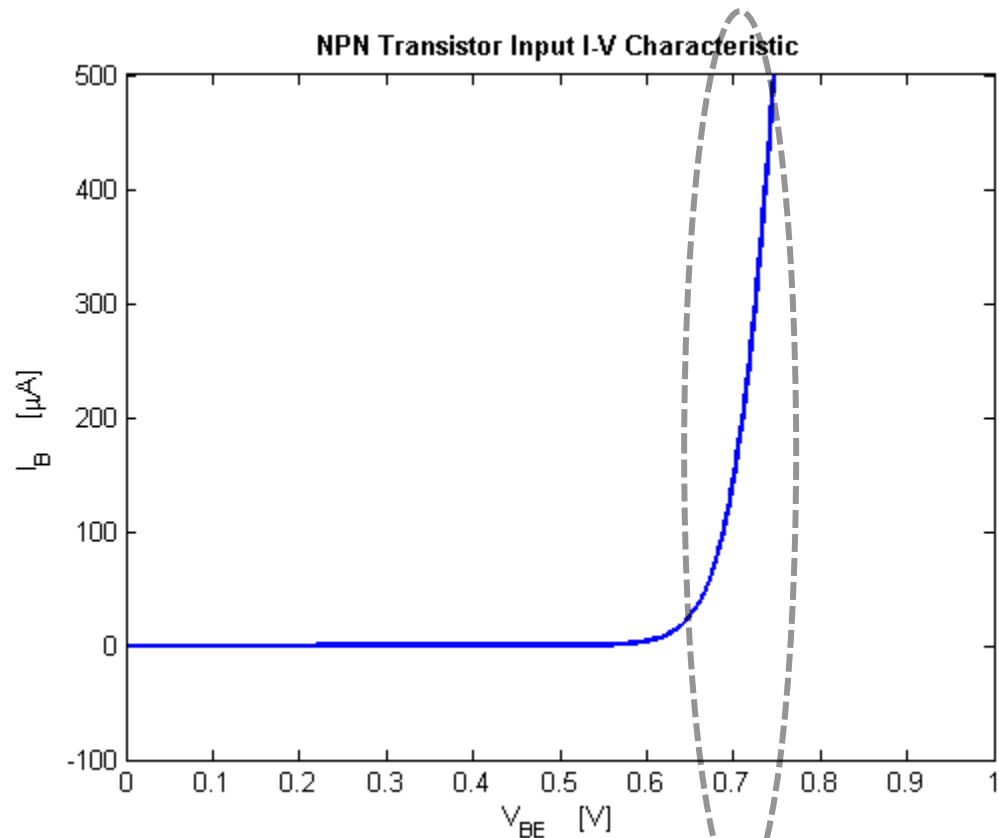

BJT Output I-V Characteristic


25

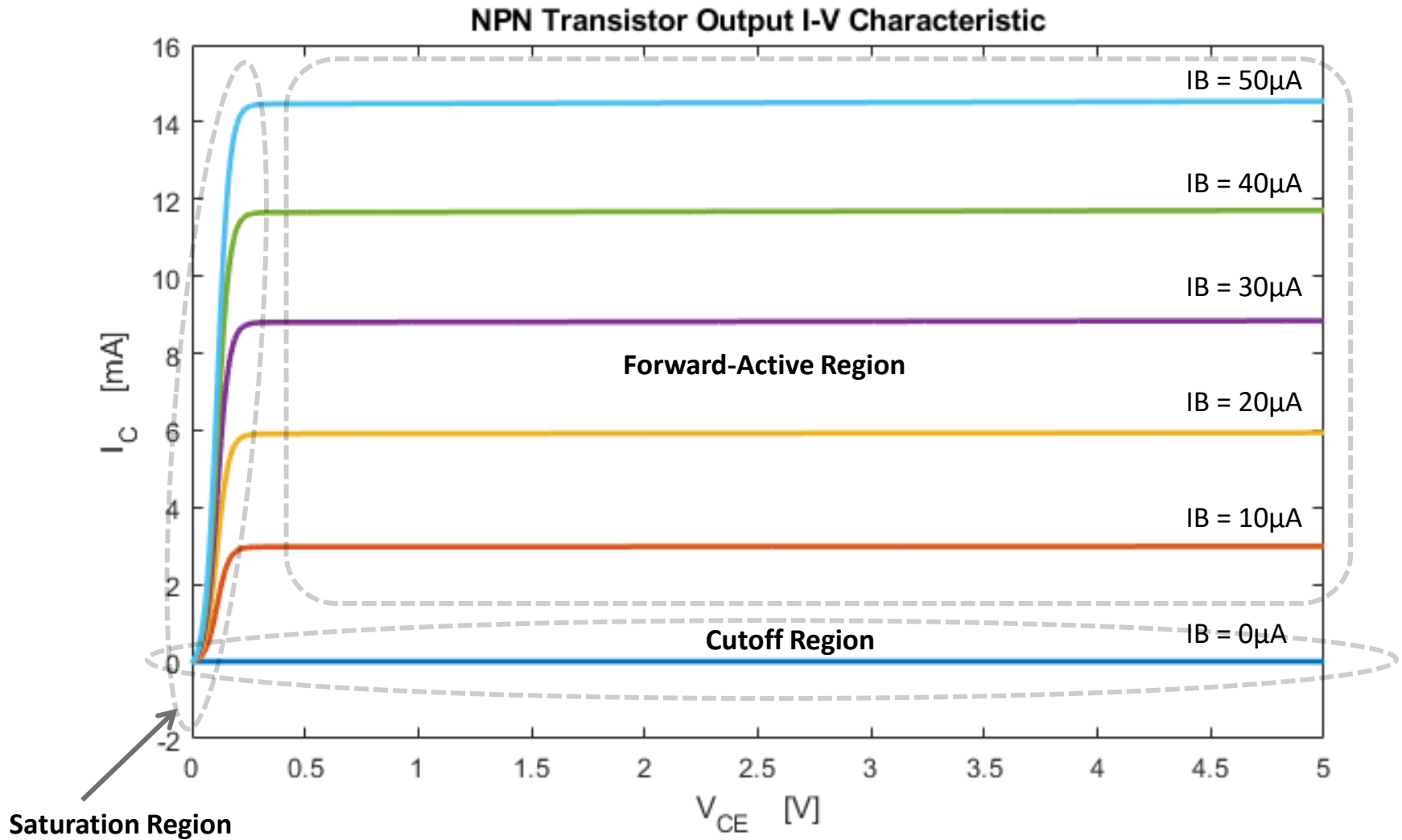

Active Region I-V Relationships – Summary

26

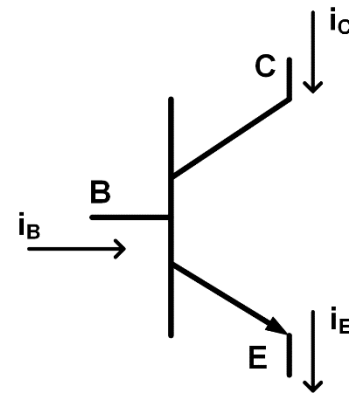
- $i_C = I_S e^{\frac{v_{BE}}{V_{th}}}$
- $i_B = \frac{i_C}{\beta} = \frac{1}{\beta} I_S e^{\frac{v_{BE}}{V_{th}}}$
- $i_E = \frac{1}{\alpha} i_C = \frac{1}{\alpha} I_S e^{\frac{v_{BE}}{V_{th}}}$
- $\beta = \frac{i_C}{i_B}, \quad \alpha = \frac{i_C}{i_E}$
- $\beta = \frac{\alpha}{1-\alpha}, \quad \alpha = \frac{\beta}{\beta+1}$



The Early Effect

27

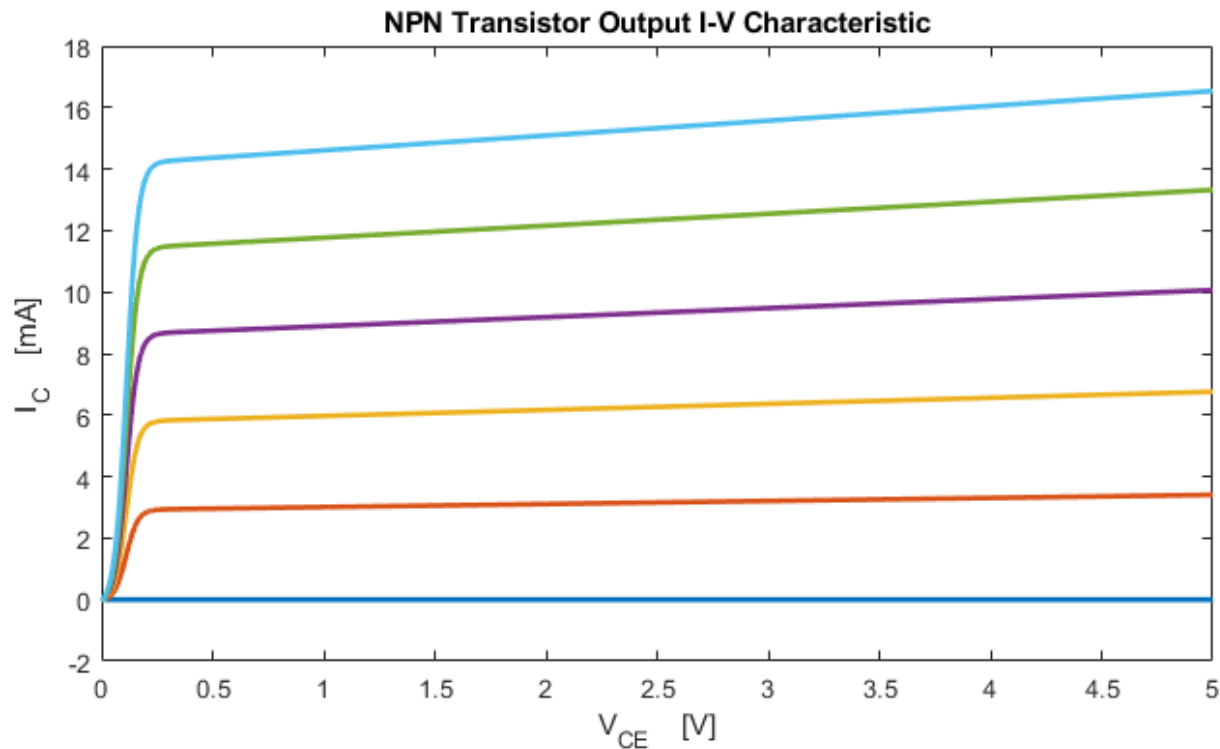- Our simple qualitative description and models for the BJT so far yield the I-V curves on the previous page
 - ▣ Collector current, i_C , is independent of v_{CE}
- Really, we observe something like this:



The Early Effect


28

- As v_{CE} increases:
 - ▣ C-B junction gets more reverse-biased
 - ▣ C-B depletion region increases
 - ▣ ***Effective base width shrinks***
- Saturation current, I_S , is inversely proportional to base width
- As base width shrinks:
 - ▣ Saturation current increases
 - ▣ Collector current, i_C , increases
- This is known as the ***Early effect*** or ***base-width modulation***

The Early Effect

29

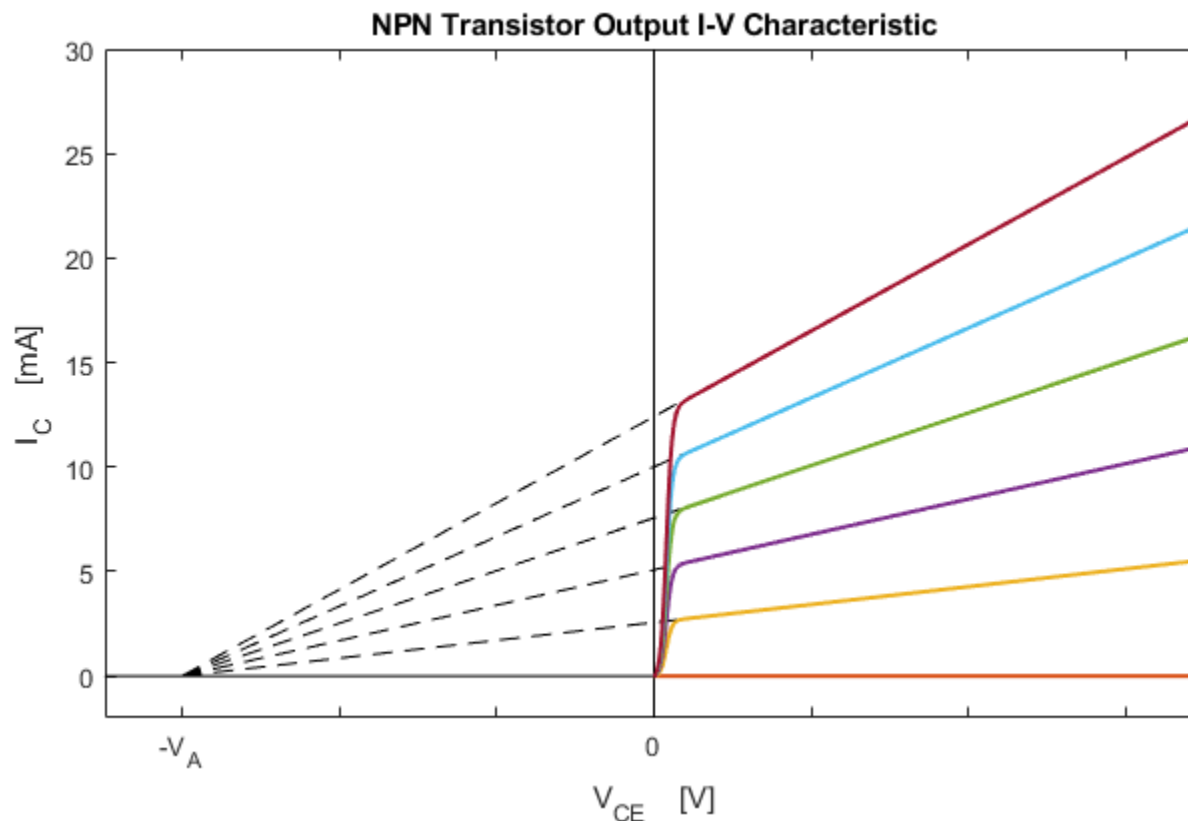- Extrapolations of the forward-active regions of the I-V curves intersect at a single point on the V_{CE} axis
 - ▣ The **Early voltage**, V_A




The Early Effect

30

- We can adjust our collector-current model to account for the Early effect:
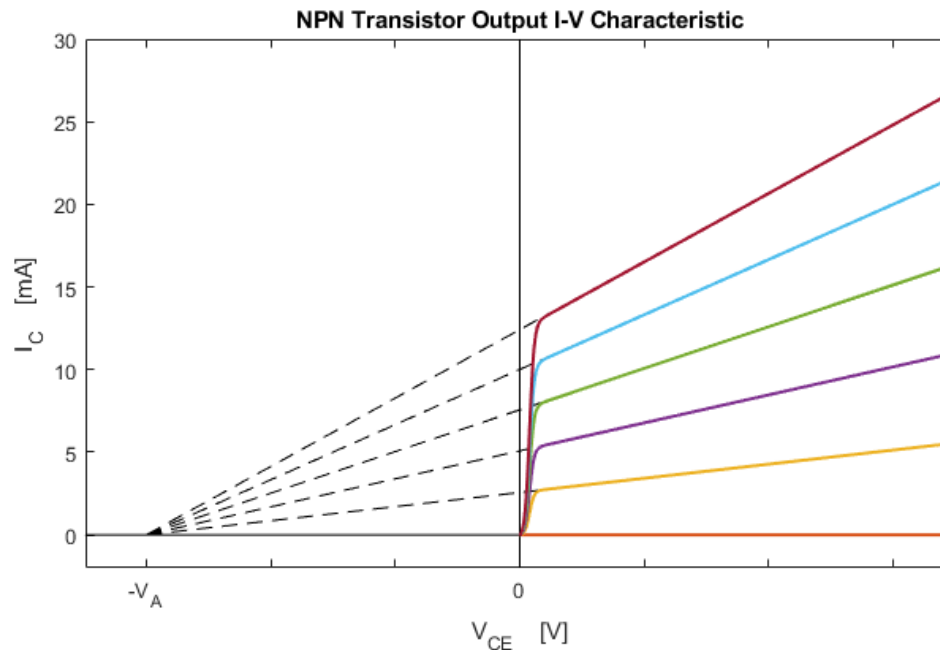
$$i_C = I_S e^{\frac{v_{BE}}{V_{th}}} \left(1 + \frac{v_{CE}}{V_A} \right)$$




31

PNP Transistors

PNP Transistors

32

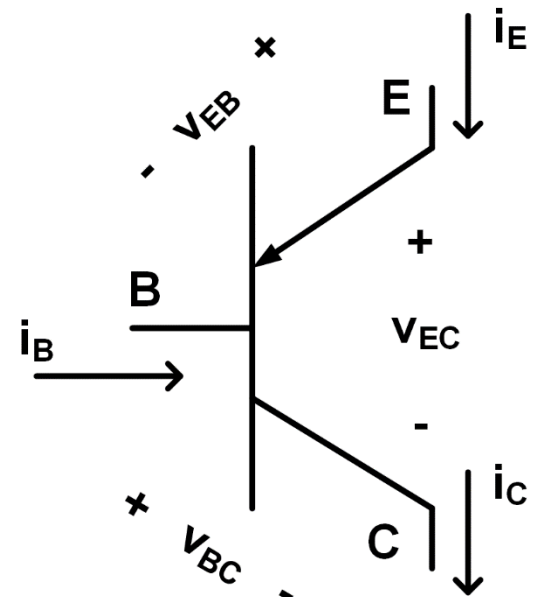- Our focus has been on NPN transistors
- With the necessary adjustments, all descriptions and models apply equally to PNP transistors
- A PNP biased in the forward-active region:
 - E-B junction forward-biased
 - $v_{EB} > 0$
 - C-B junction reverse-biased
 - $v_{BC} > 0$




BJT Operating Regions – PNP

33

- Junction voltages change signs for PNPs

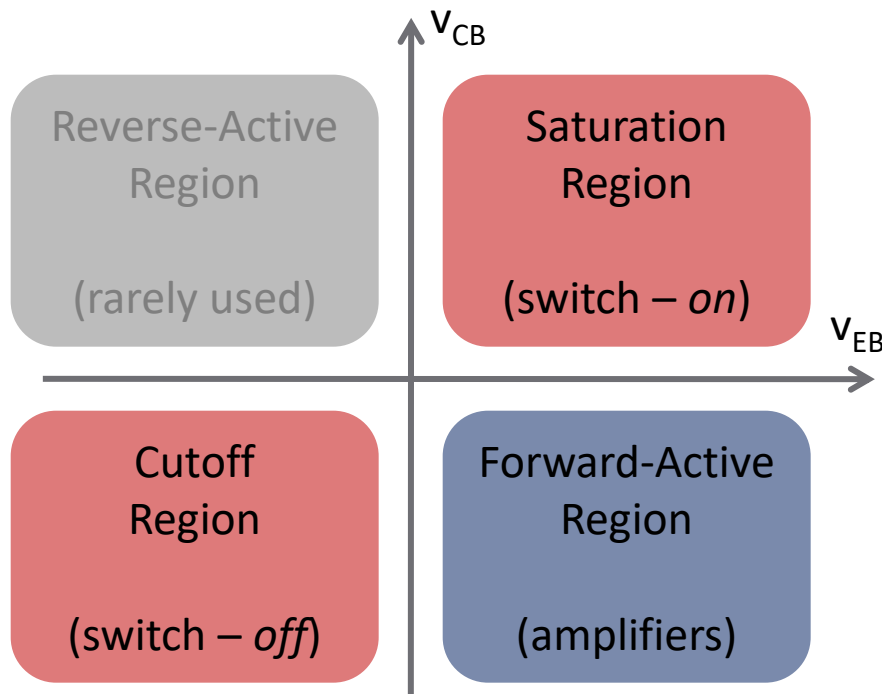- $v_{BC} \rightarrow v_{CB}$
- $v_{BE} \rightarrow v_{EB}$



- **Forward active region**

- $v_{CB} < 0$
- $v_{EB} > 0$
- Linear region – **amplifiers**

- **Saturation region**

- $v_{CB} > 0$
- $v_{EB} > 0$
- E-C looks like a **closed switch**


- **Cutoff region**

- $v_{CB} < 0$
- $v_{EB} < 0$
- E-C looks like an **open switch**

PNP Transistors

34

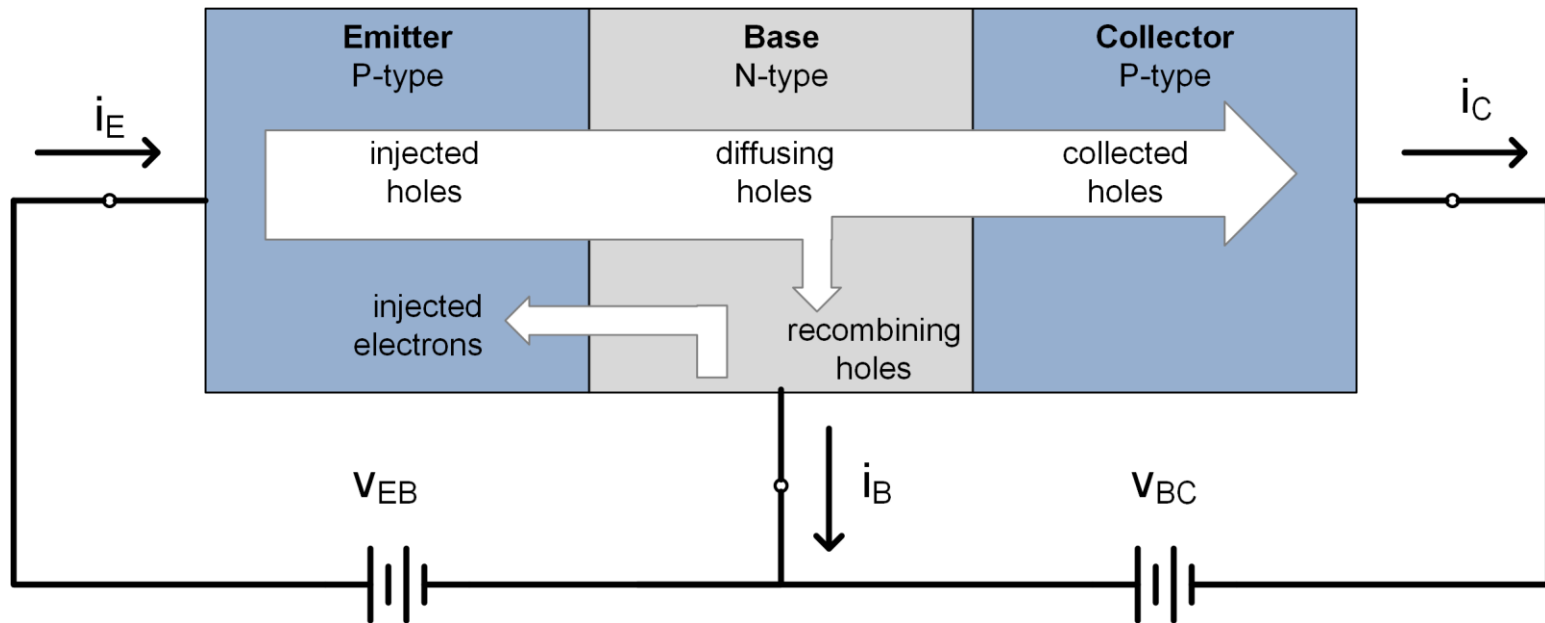- NPN current primarily due to diffusion of **minority carriers – electrons** – across the base region
- Same is true in PNP transistors, but now the minority carriers are **holes**



35

Equivalent Circuit Models

Equivalent Circuit Models

36

- We have seen that BJTs have an exponential current-voltage relationship
 - ▣ Small inputs, v_{BE} , can produce large outputs, i_C
 - ▣ BJTs are useful as ***amplifiers***
- Our goal is the analysis and design of ***transistor amplifier circuits***
- To do so, we first need ***equivalent circuit models*** for the transistors

BJT Amplifier Circuits


37

- Two functional pieces of a BJT amplifier:
 - ▣ **Bias network**
 - Sets the DC operating point of the transistor
 - Ensures the BJT remains in the forward-active region

- ▣ **Signal path**

- Sets the gain of the amplifier circuit

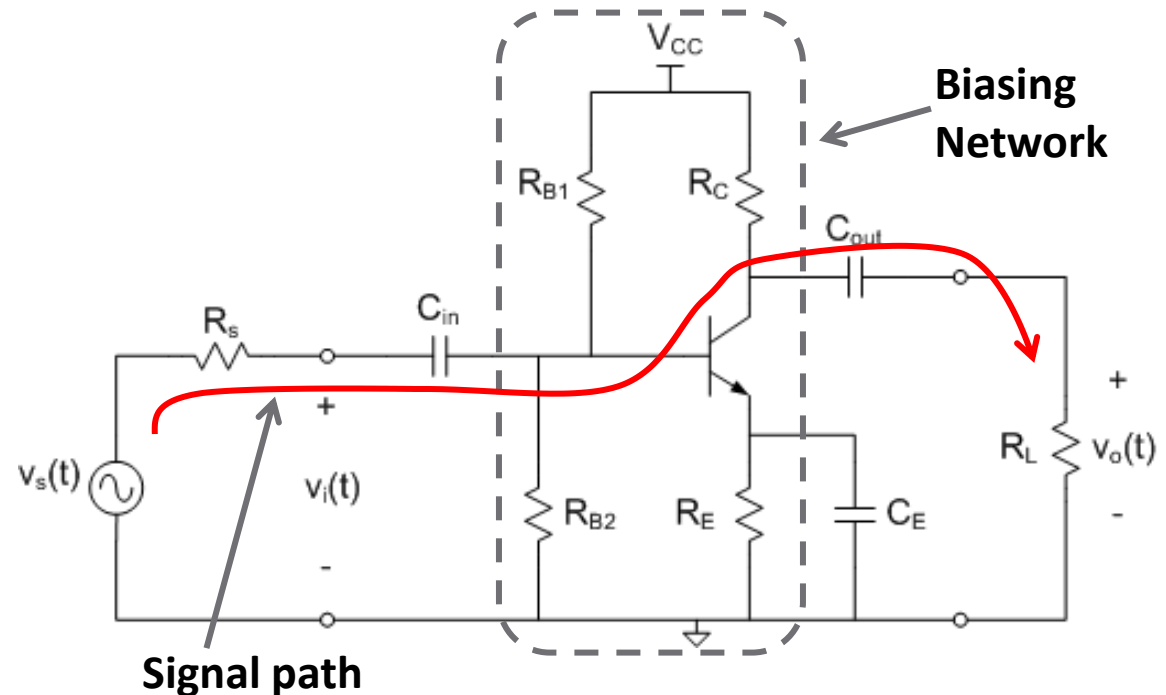- Significant overlap between the two parts



Equivalent Circuit Models

38

- We use two types of equivalent-circuit transistor models:
 - ***Large-signal model***
 - ▣ Models the transistor's behavior to DC signals
 - ▣ Used to determine the transistor's DC operating point
 - ***Small-signal model***
 - ▣ Models the behavior in response to small signals (w.r.t V_{th})
 - ▣ Describes the response to the AC signals to be amplified
 - ▣ Properties of the small-signal model determined by the DC operating point

39


Large-Signal Models

Large-Signal Model – Forward-Active


40

- Large-signal behavior in the forward-active region modeled by the following circuits:

NPN:

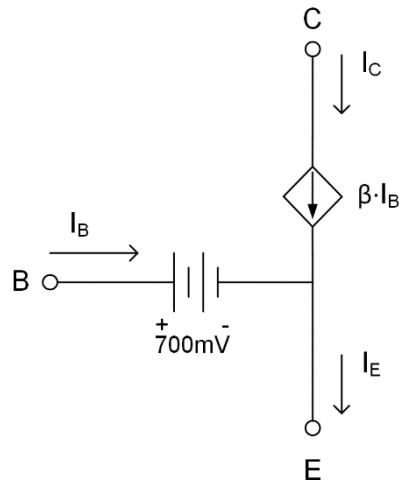

PNP:


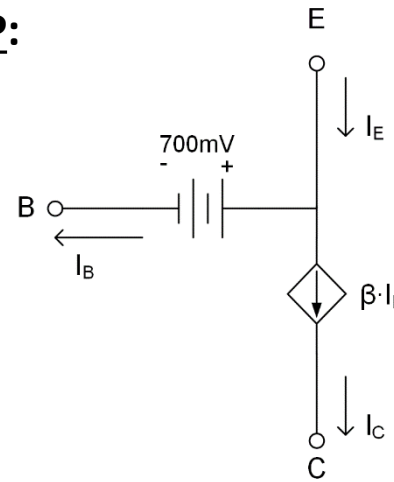


- Replace the transistor with the appropriate model to determine the DC operating point (Q-point)
- Forward-active-region bias assumed
 - If incorrect, model will say otherwise
- Note the use of upper-case I/V, and subscripts for DC signals

DC Operating Point – Example 1

41

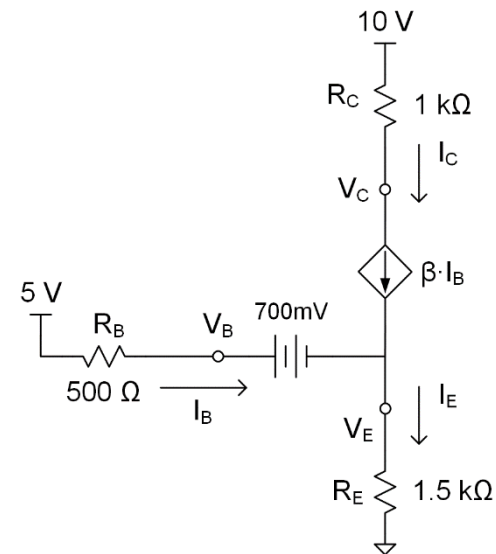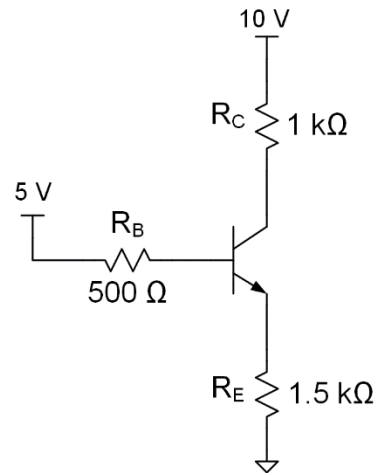- Determine the DC operating point (i.e., all terminal voltages and currents) for the following transistor
 - ▣ Assume $\beta = 100$
- First, replace transistor with its large-signal equivalent-circuit model



DC Operating Point – Example 1

42

- Apply KVL around the B-E loop:

$$5 V - I_B R_B - 700 mV - I_E R_E = 0$$

- Express emitter current in terms of base current


$$I_E = (\beta + 1)I_B$$

$$5 V - I_B R_B - 700 mV - I_B (\beta + 1)R_E = 0$$

- Solve for base current

$$I_B [R_B + (\beta + 1)R_E] = 4.3 V$$
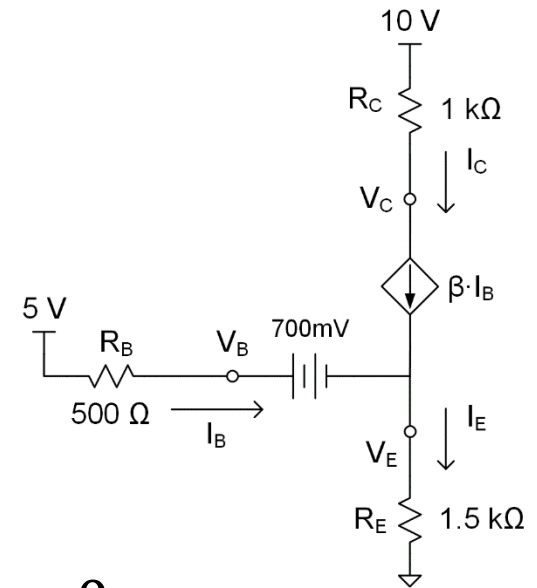
$$I_B = \frac{4.3 V}{[R_B + (\beta + 1)R_E]}$$



DC Operating Point – Example 1

43

- The base current is

$$I_B = \frac{4.3 \text{ V}}{[R_B + (\beta + 1)R_E]}$$


$$I_B = \frac{4.3 \text{ V}}{500 \Omega + 101 \cdot 1.5 \text{ k}\Omega} = 28.29 \mu\text{A}$$

- Calculate I_C and I_E from I_B

$$I_C = \beta I_B = 100 \cdot 28.29 \mu\text{A} = 2.829 \text{ mA}$$

$$I_E = (\beta + 1)I_B = 101 \cdot 28.29 \mu\text{A} = 2.857 \text{ mA}$$
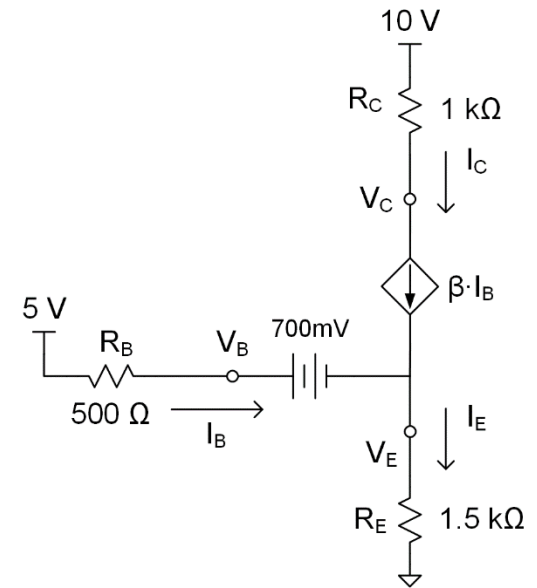
$$I_B = 28.29 \mu\text{A}, I_C = 2.829 \text{ mA}, I_E = 2.857 \text{ mA}$$



DC Operating Point – Example 1

44

- Use terminal currents to calculate terminal voltages

$$V_B = 5 V - I_B R_B$$

$$V_B = 5 V - 28.29 \mu A \cdot 500 \Omega$$

$$V_B = 4.986 V$$

- Collector voltage


$$V_C = 10 V - I_C R_C = 10 V - 2.829 mA \cdot 1 k\Omega$$

$$V_C = 7.171 V$$

- Emitter voltage

$$V_E = I_E R_E = 2.857 mA \cdot 1.5 k\Omega$$

$$V_E = 4.286 V$$

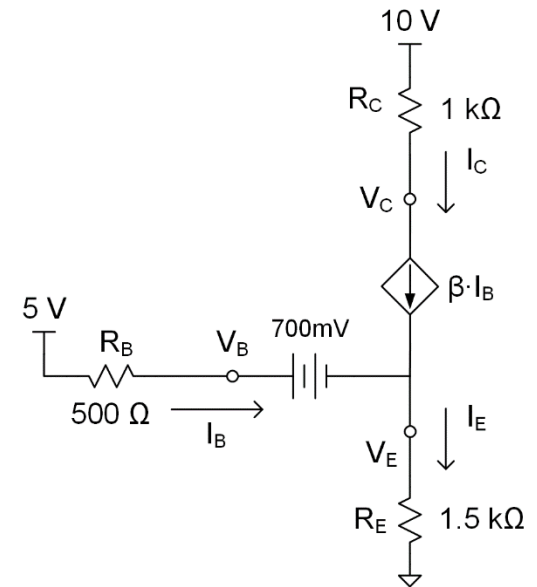


DC Operating Point – Example 1

45

- We now know the complete DC operating point for the transistor
 - ▣ All voltages and currents

| | |
|---------------------|-----------------|
| $I_B = 28.29 \mu A$ | $V_B = 4.986 V$ |
| $I_C = 2.829 mA$ | $V_C = 7.171 V$ |
| $I_E = 2.857 mA$ | $V_E = 4.286 V$ |


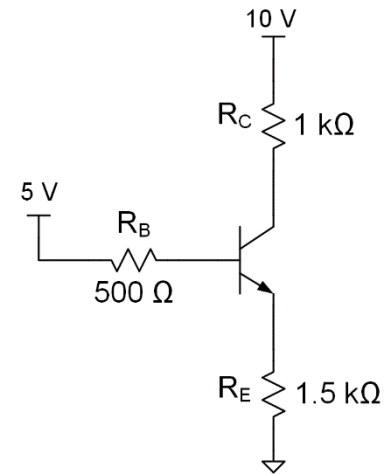


- Use of this model assumed forward-active region operation – verify
 - ▣ $V_B > V_E, V_{BE} > 0$
 - ▣ $V_C > V_B, V_{BC} < 0$
 - ▣ Transistor *is* biased in the forward active region

DC Operating Point – Example 2

46

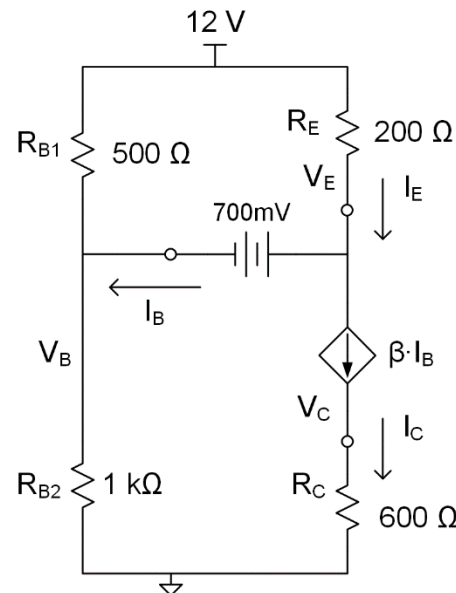
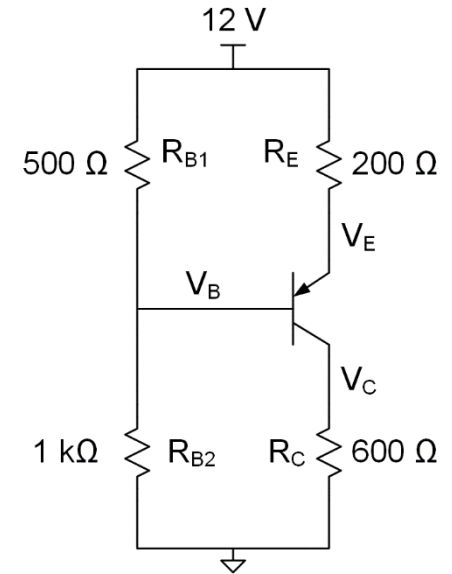
- Next, find the DC operating point of the following PNP transistor
- Again, begin by replacing the transistor with its large-signal equivalent circuit:



DC Operating Point – Example 2

47

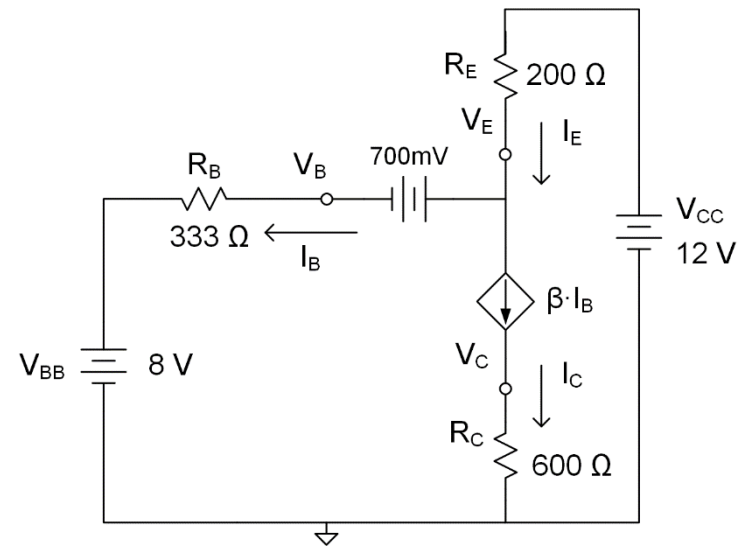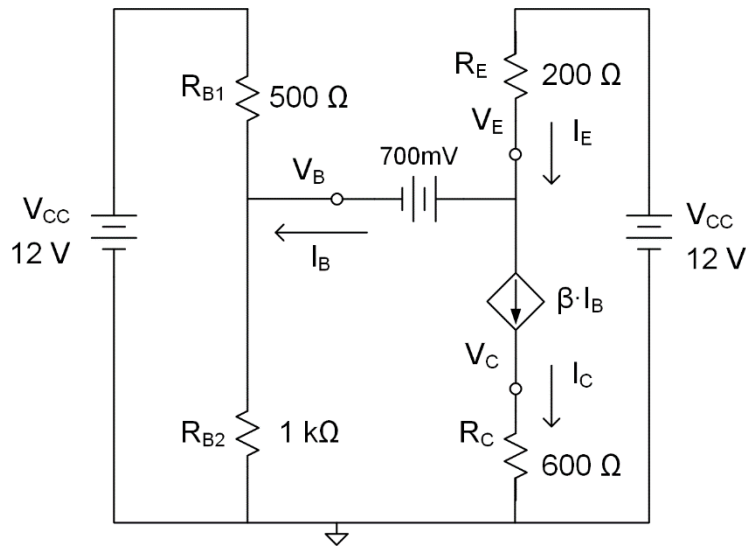- We can simplify the circuit by replacing the base bias circuit with its Thevenin equivalent



$$V_{BB} = V_{CC} \frac{R_{B2}}{R_{B1} + R_{B2}} = 12 \text{ V} \frac{1 \text{ k}\Omega}{500 \Omega + 1 \text{ k}\Omega} = 8 \text{ V}$$

$$R_B = \frac{R_{B1} R_{B2}}{R_{B1} + R_{B2}} = \frac{500 \Omega \cdot 1 \text{ k}\Omega}{500 \Omega + 1 \text{ k}\Omega} = 333.3 \Omega$$


DC Operating Point – Example 2

49

- The base current is

$$I_B = \frac{V_{CC} - V_{BB} - 700 \text{ mV}}{[R_B + (\beta + 1)R_E]}$$
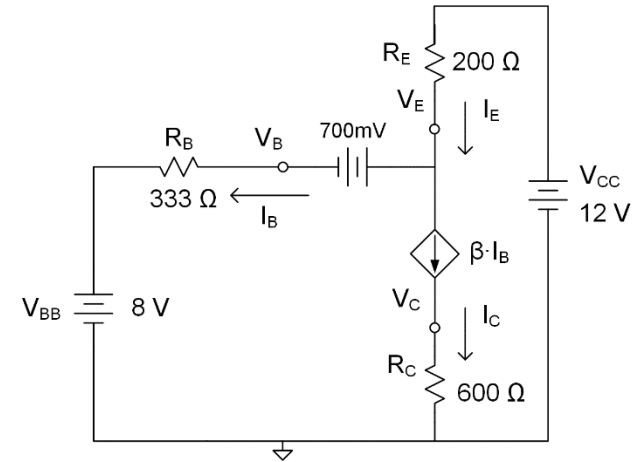
$$I_B = \frac{3.3 \text{ V}}{333\Omega + 101 \cdot 200 \Omega} = 160.7 \mu\text{A}$$



- Calculate I_C and I_E from I_B

$$I_C = \beta I_B = 100 \cdot 160.7 \mu\text{A} = 16.07 \text{ mA}$$

$$I_E = (\beta + 1)I_B = 101 \cdot 160.7 \mu\text{A} = 16.23 \text{ mA}$$

$$I_B = 160.7 \mu\text{A}, I_C = 16.07 \text{ mA}, I_E = 16.23 \text{ mA}$$

DC Operating Point – Example 2

50

□ Base voltage

$$V_B = V_{BB} + I_B R_B$$

$$V_B = 8\text{ V} + 160.7\ \mu\text{A} \cdot 333\ \Omega$$

$$V_B = 8.054\text{ V}$$

□ Collector voltage


$$V_C = I_C R_C = 16.07\text{ mA} \cdot 600\ \Omega$$

$$V_C = 6.429\text{ V}$$

□ Emitter voltage

$$V_E = V_{CC} - I_E R_E = 12\text{ V} - 16.23\text{ mA} \cdot 200\ \Omega$$

$$V_E = 8.754\text{ V}$$

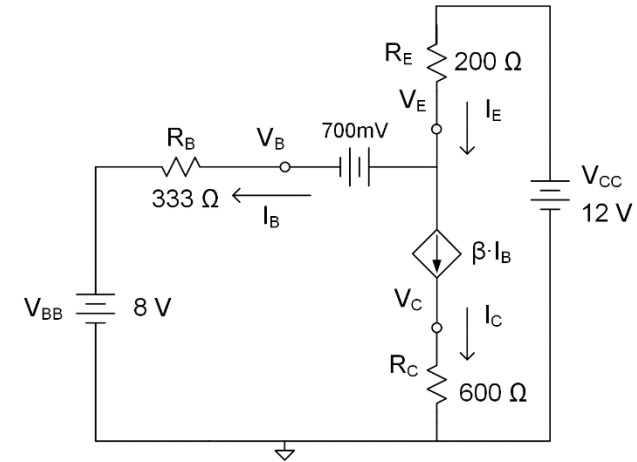

DC Operating Point – Example 2


51

- The DC operating point:

| | |
|---------------------|-----------------|
| $I_B = 160.7 \mu A$ | $V_B = 8.054 V$ |
| $I_C = 16.07 mA$ | $V_C = 6.429 V$ |
| $I_E = 16.23 mA$ | $V_E = 8.754 V$ |

- Terminal voltages confirm that the transistor is biased in the forward active region:


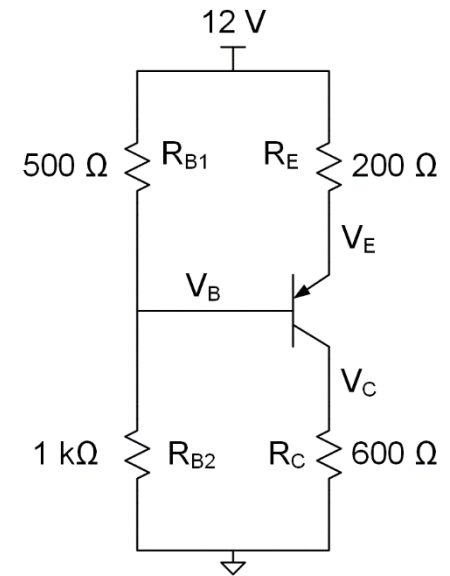
- $V_B < V_E, V_{EB} > 0$
- $V_C < V_B, V_{CB} < 0$



DC Operating Point – Example 3

52

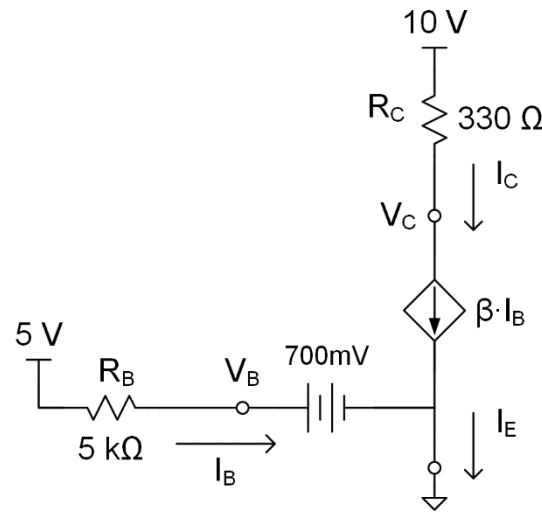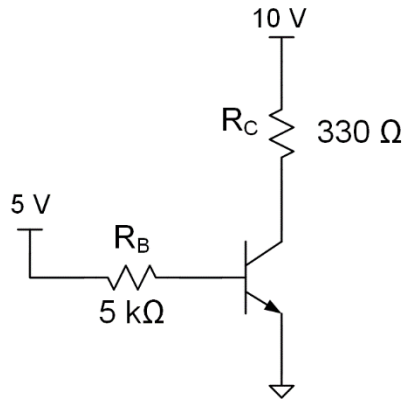- Next, find the DC operating point for the following circuit



- Here, the emitter is grounded, so base current is given by

$$I_B = \frac{5\text{ V} - 700\text{ mV}}{R_B} = \frac{4.3\text{ V}}{5\text{ k}\Omega}$$

$$I_B = 860\ \mu\text{A}$$

DC Operating Point – Example 3

53

- Use β to get collector and emitter currents:

$$I_C = \beta I_B = 100 \cdot 860 \mu A = 86 \text{ mA}$$

$$I_E = (\beta + 1)I_B = 101 \cdot 860 \mu A = 86.9 \text{ mA}$$

- Base and emitter voltages are known:

$$V_E = 0 \text{ V}$$

$$V_B = 700 \text{ mV}$$

- The collector voltage:

$$V_C = 10 \text{ V} - I_C R_C = 10 \text{ V} - 86 \text{ mA} \cdot 330 \Omega$$

$$V_C = -18.4 \text{ V (!)}$$

- B-C junction is not reverse biased
 - Transistor is not in the forward active region - **saturated**
 - Inappropriate large-signal model used
 - Need to use a model for the saturation region


Saturation/Cutoff Region Models

54

- Transistors used as **switches** operate alternately in the **saturation** (closed) and **cutoff** (open) regions
- Equivalent circuit models:

Saturation Region:

- Both junctions forward biased

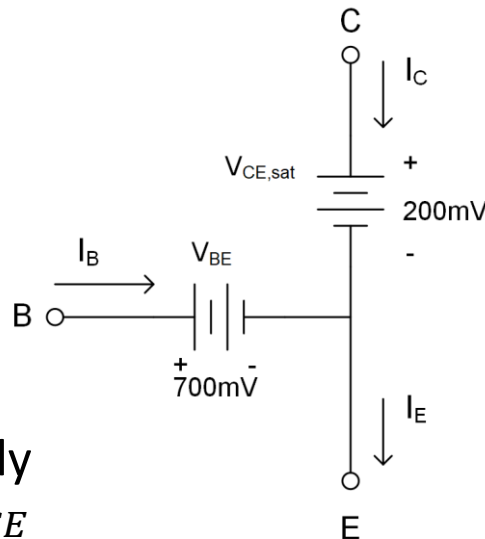


- Small, nearly constant V_{CE}

$$V_{CE,sat} \approx 200 \text{ mV}$$

Cutoff Region:

- Both junctions reverse biased

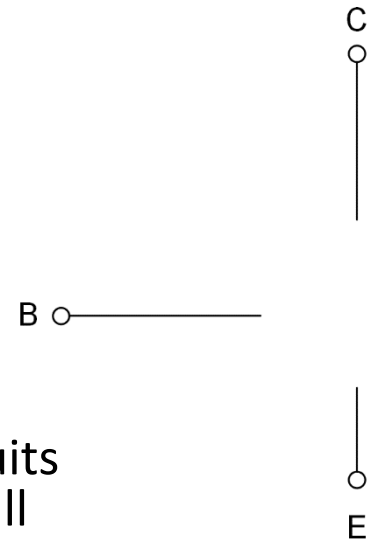

- Open circuits between all terminals

DC Operating Point – Example 3

55

- Returning to our example, now use the transistor model for saturation
- Base current does not change:


$$I_B = \frac{4.3 \text{ V}}{5 \text{ k}\Omega} = 860 \mu\text{A}$$

- But, collector current is now:

$$I_C = \frac{10 \text{ V} - V_{CE,sat}}{R_C} = \frac{9.8 \text{ V}}{330 \Omega}$$

$$I_C = 29.7 \text{ mA}$$

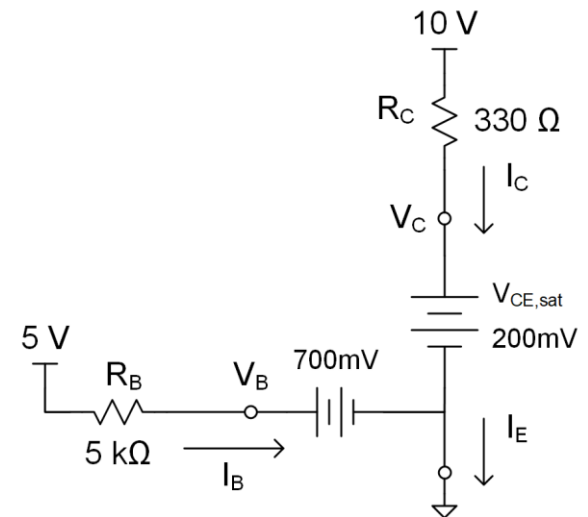- Much less than would be predicted by β
- β does not apply in the saturation region



DC Operating Point – Example 3

56

- The transistor is in the saturation region
 - ▣ Looks like a ***closed switch*** between collector and emitter

- Operating point:

$$I_B = 860 \mu A$$


$$V_B = 700 mV$$

$$I_C = 29.7 mA$$

$$V_C = 200 mV$$

$$I_E = 30.6 mA$$

$$V_E = 0 V$$

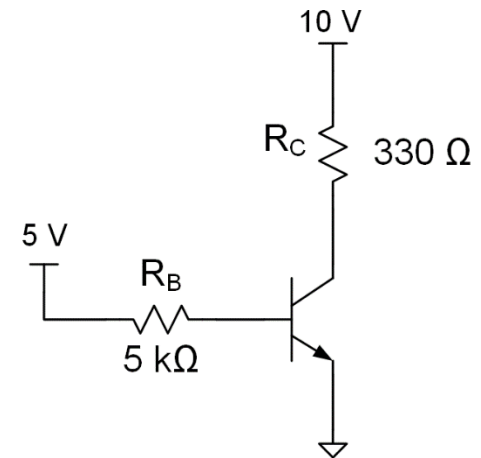

Large-Signal Models – Early Effect

57

- We have seen that, due to **base-width modulation**, or the **Early effect**, I_C is dependent on V_{CE}
- We can modify the large-signal model to account for this
- Add **output resistance**, r_o


$$r_o = \frac{V_A}{I'_C}$$

where

- V_A is the Early voltage
- I'_C is the collector current with the Early effect neglected

$$I'_C = I_s e^{\frac{V_{BE}}{V_{th}}}$$

- No longer an ideal current source

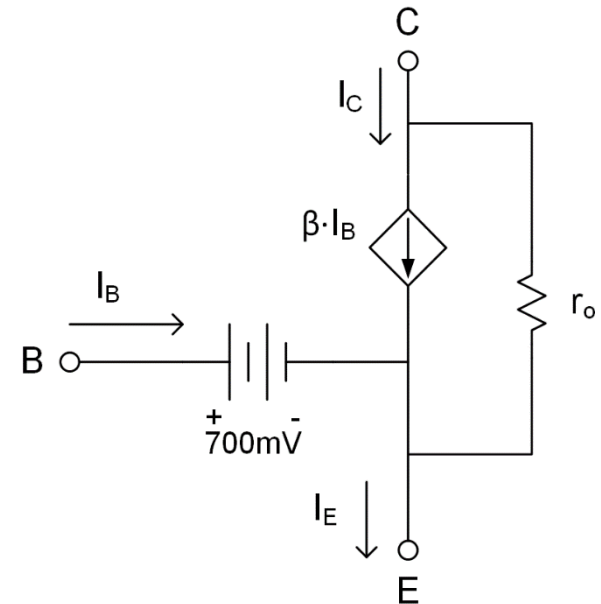

58

Small-Signal Models

BJT – Small-Signal Models

59


- Large-signal model allows us to determine the ***DC operating point***
 - ▣ DC terminal voltages and currents
- Remember, our objective is to ***amplify small signals***
 - ▣ Want to know how a transistor circuit responds to small AC signals
 - ▣ Need a ***small-signal model***
- ***Small-signal behavior is defined by the DC operating point***
 - ▣ Values of small-signal model parameters determined by the DC operating point
 - ▣ DC bias applied to the transistor serves to put the transistor in a state where it will behave as an amplifier
- We will look at two small-signal models:
 - ▣ Hybrid- π model
 - ▣ T model

Hybrid- π Model – β

60

- Two variations of the hybrid- π model
 - ▣ First one uses a **CCCS**
- Same collector current relationship as in large-signal model:

$$i_c = \beta i_b$$

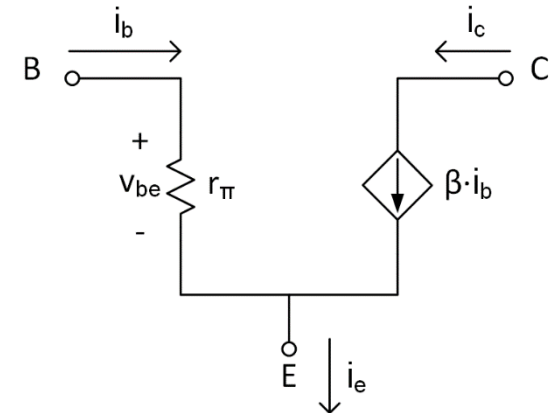

- Base input resistance, r_π , set by the DC collector current:

$$r_\pi = \frac{\beta V_{th}}{I_C}$$

- Note that we now use **small-signal notation**
 - ▣ Lower-case i and v and lower-case subscripts
 - ▣ These denote **AC signals**

Hybrid- π Model – g_m

61

- Second hybrid- π model uses a **VCCS**
- **Transconductance** parameter sets collector current as a function of v_{be}

$$i_c = g_m v_{be}$$


- **Transconductance, g_m**
 - ▣ Voltage one place, v_{be} , causes current somewhere else, i_c
 - ▣ Determined by DC collector current

$$g_m = \frac{I_C}{V_{th}} = \frac{I_C q}{kT} \approx \frac{I_C}{26 \text{ mV}}$$

- g_m is related to β :

$$g_m = \frac{i_c}{v_{be}} = \frac{i_c}{i_b r_\pi} = \frac{\beta}{r_\pi}$$

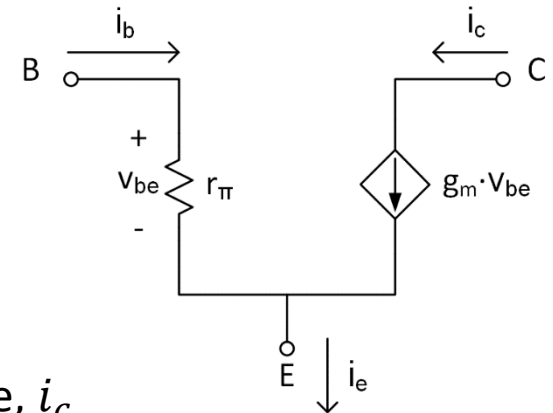- Note that, while g_m and r_π are dependent on bias, β is not
 - ▣ β is a device property



T-Model

62

- An alternative to the hybrid- π model is the T-model
 - ▣ Simplifies the analysis of some circuits
 - ▣ Again, either with a CCCS, using β , or a VCCS, using g_m
- Here, the resistance is the emitter resistance, r_e


$$r_e = \frac{V_{th}}{I_E} = \frac{\alpha}{g_m} \approx \frac{1}{g_m}$$

- Note the relationship to r_π

$$r_e = \frac{\alpha}{g_m} = \frac{\beta}{\beta + 1} \cdot \frac{1}{g_m}$$

$$r_e = \frac{1}{\beta + 1} \cdot \frac{\beta}{g_m} = \frac{r_\pi}{\beta + 1}$$

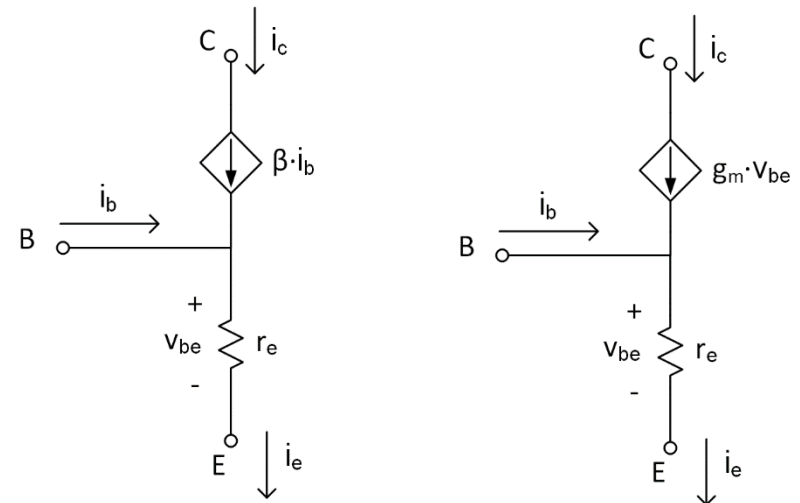
- ▣ The same resistance referred to one terminal or the other




Small-Signal Models – Early Effect

63

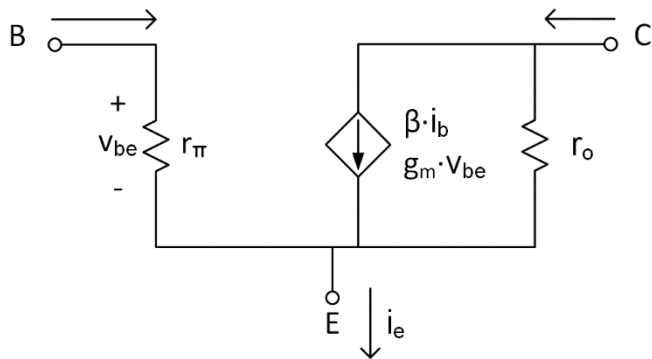- We have seen that we can add output resistance to the large-signal model to model the Early effect
 - ▣ Can do the same for the small-signal model
 - ▣ Will rarely, if ever, do this for the large signal model, but often will for the small-signal model



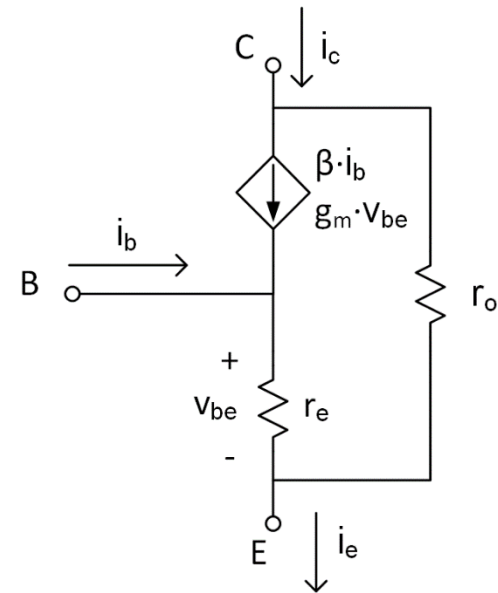
$$r_o = \frac{V_A}{I'_C} \approx \frac{V_A}{I_C}$$



BJT – Small-Signal Models

64

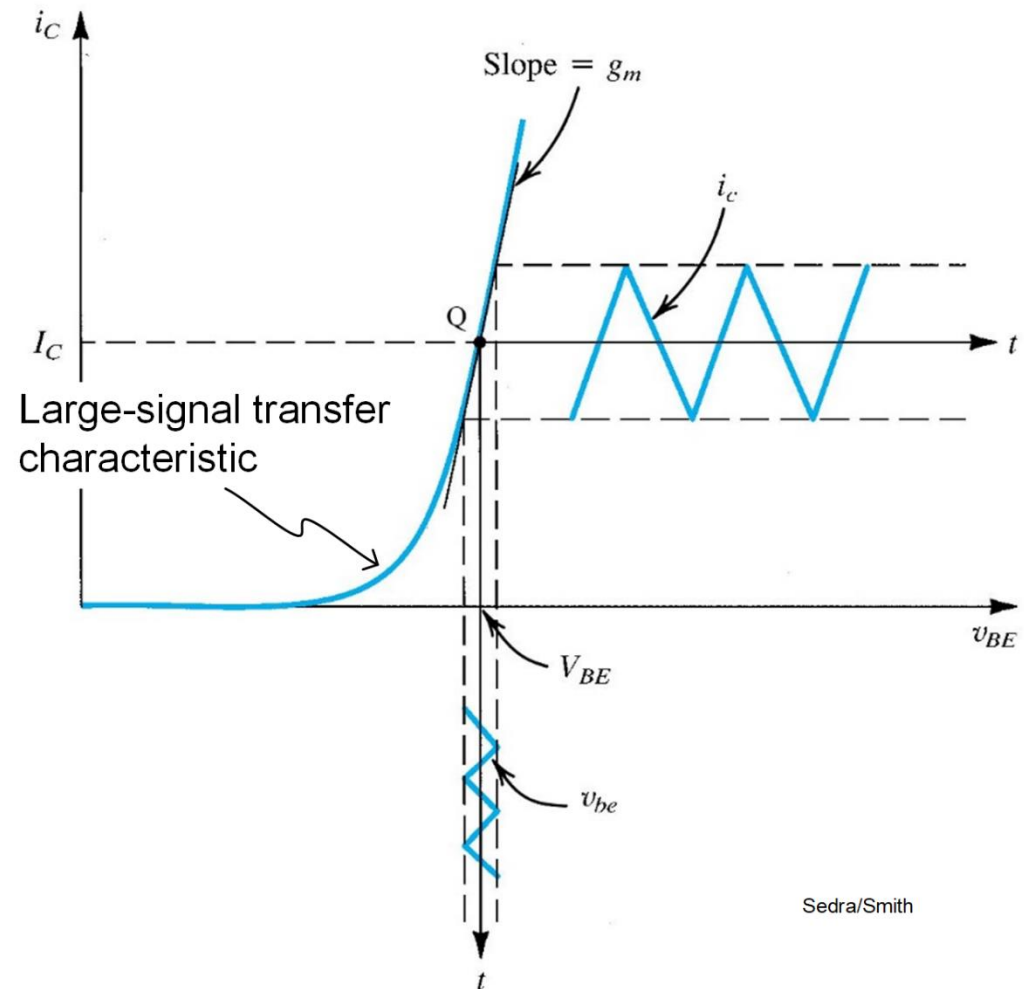- **Large-signal transfer characteristic**
 - Set of all possible Q-points
 - Very nonlinear
- As an amplifier, a transistor is operated **near its Q-point**
 - Closer to linear
 - **Small signal model** describes behavior here
 - Valid for small signal excursions about the Q-point



Sedra/Smith

Using the BJT Models

65

- In the next section of the course, we will look at the analysis and design of transistor amplifiers
 - ▣ Bias network and DC operating point
 - ▣ Signal-path

- Much more detail in the next section, but our general procedure will be:
 - ▣ ***Large-signal analysis***
 - DC operating point
 - Small-signal model parameters
 - ▣ ***Small-signal analysis***
 - Circuit gain