

# SECTION 5: MOSFET AMPLIFIERS

2


# MOSFET Amplifier Circuits

# MOSFET Amplifier Circuits – Preview

3


- In this section of the course, we will look at three MOSFET amplifiers, with a focus on the following two circuits:

## Common-Source Amplifier:

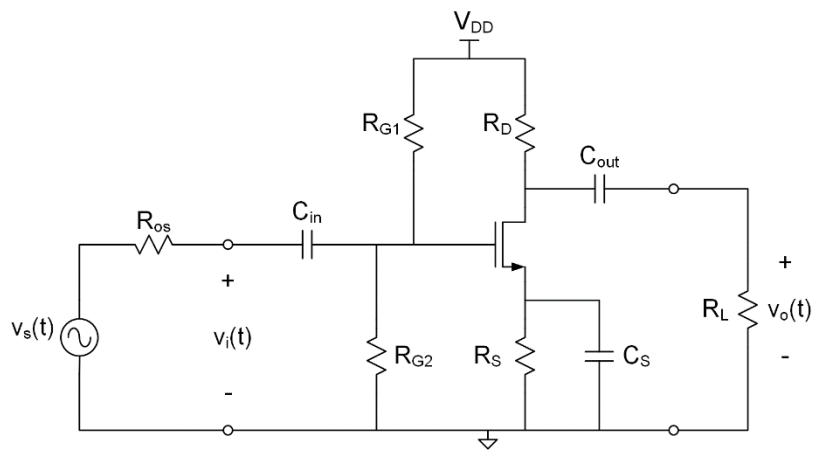

- High voltage gain
- An amplifier

## Source-Follower Amplifier:

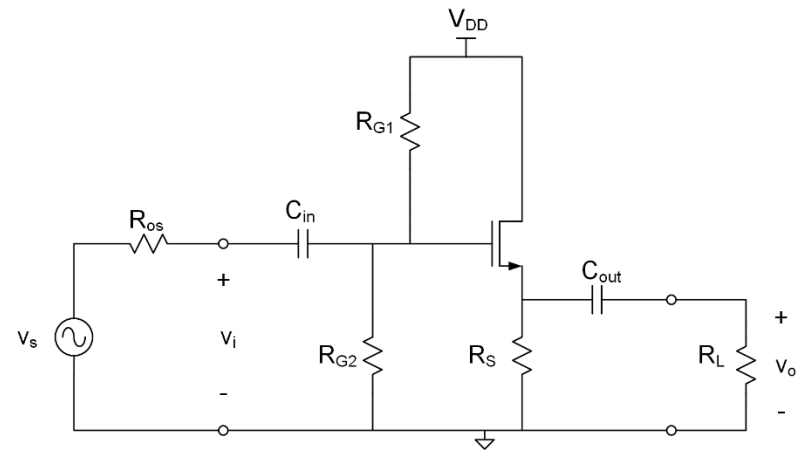

- Near unity gain
- A buffer

4

# MOSFET Amplifier Biasing

# MOSFET Amplifier Biasing


5

- To function as an amplifier, a MOSFET must be biased in the ***saturation region***
- DC operating point set by the ***bias network***
  - ▣ Resistors and power supply voltages
  - ▣ Sets the transistor's ***DC terminal voltages and currents*** – its DC bias
- How a transistor is ***biased*** determines:
  - ▣ Small-signal characteristics
  - ▣ Small-signal model parameters
  - ▣ How it will behave as an amplifier
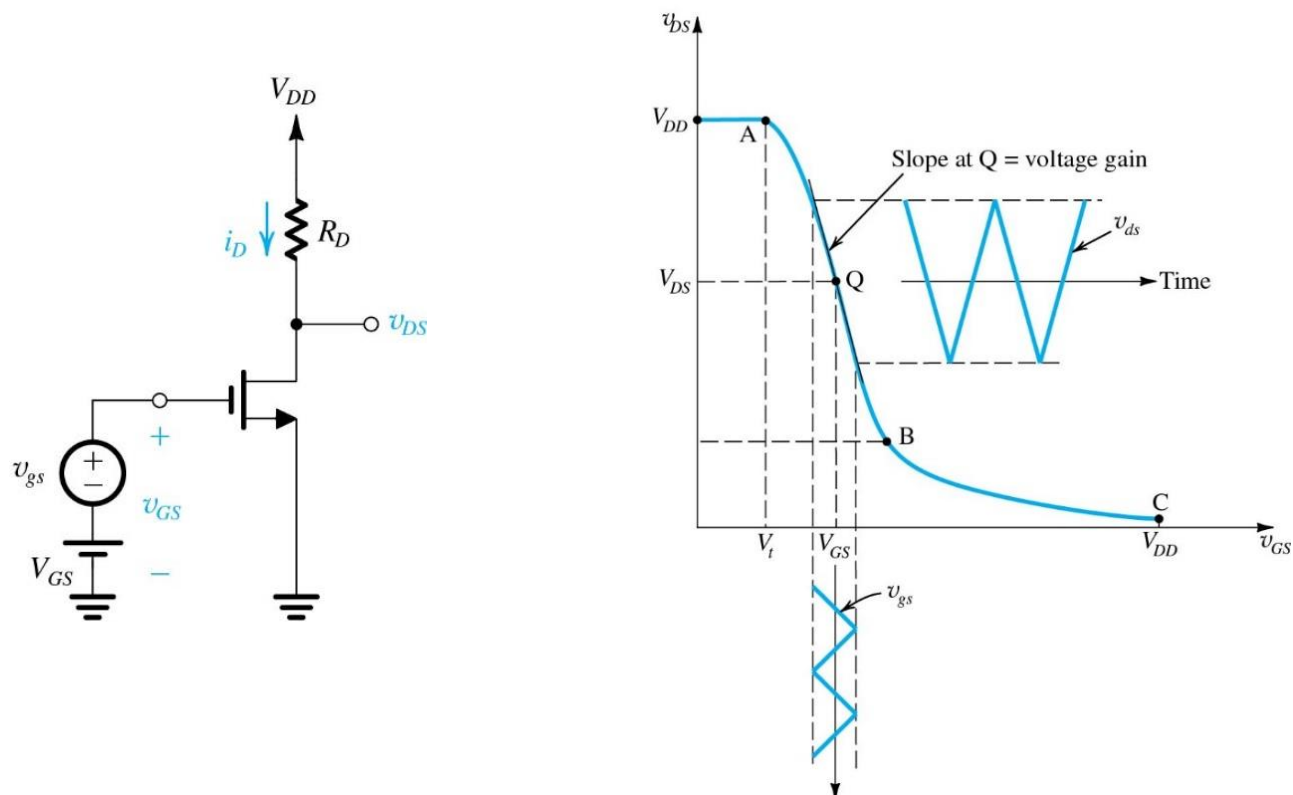
# Voltage Transfer Characteristic

6


- MOSFET amplifier biased in the middle of its saturation region
- Slope of the large-signal transfer characteristic gives the amplifier gain
  - Negative slope – gain is inverting
  - Small input signals yield larger output signals
  - Slope is nearly linear in this region


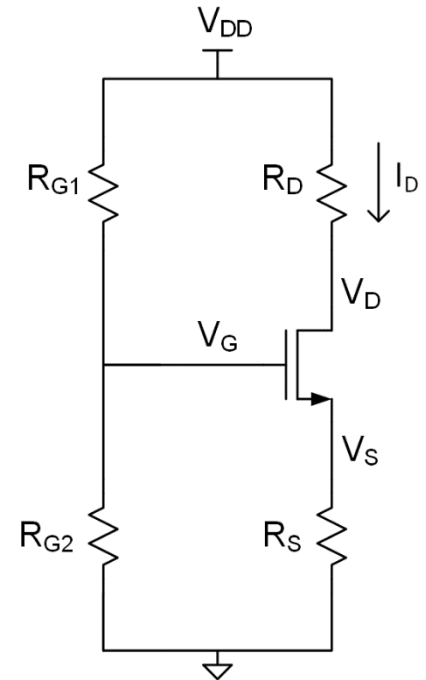
# MOSFET Biasing – Four-Resistor Bias Circuit

7

- We can use a similar four-resistor bias network for MOSFET amplifiers
- Commonly-used for both **common-source** amplifiers and **source-followers**
  - ▣ Single power supply or bipolar supply
- Stable biasing over device parameter variations
  - ▣ Insensitive to variations in  $V_t$ ,  $k'_n$ ,  $\frac{W}{L}$



# Analysis of the Four-Resistor Bias Circuit

- Since  $I_G = 0$ , gate voltage is simply set by the voltage divider

$$V_G = V_{DD} \frac{R_{G2}}{R_{G1} + R_{G2}}$$

- Drain current is given by

$$I_D = \frac{1}{2} k'_n \left( \frac{W}{L} \right) V_{OV}^2 = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$I_D = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (V_G - V_S - V_t)^2 = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (V_G - I_D R_S - V_t)^2$$

- After some rearranging, we arrive at a quadratic equation, which we can solve for  $I_D$ :

$$R_S^2 I_D^2 - \left[ 2R_S(V_G - V_t) + \frac{1}{\frac{1}{2} k'_n \left( \frac{W}{L} \right)} \right] I_D + (V_G - V_t)^2 = 0$$



# Four-Resistor Bias Circuit – Example

9

- Determine terminal voltages and drain current for the following circuit
- Gate voltage:

$$V_G = 12 V \cdot \frac{30 k\Omega}{50 k\Omega + 30 k\Omega} = 4.5 V$$

- Drain current:


$$I_D = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (V_G - V_S - V_t)^2$$

$$I_D = 1 \frac{mA}{V^2} (4.5 V - I_D \cdot 8k\Omega - 700 mV)^2$$

$$I_D = 1 \frac{mA}{V^2} (-8 k\Omega \cdot I_D + 3.8 V)^2$$

$$1 \frac{mA}{V^2} (64e6 \cdot I_D^2 - 60.8e3 \cdot I_D + 14.44) - I_D = 0$$
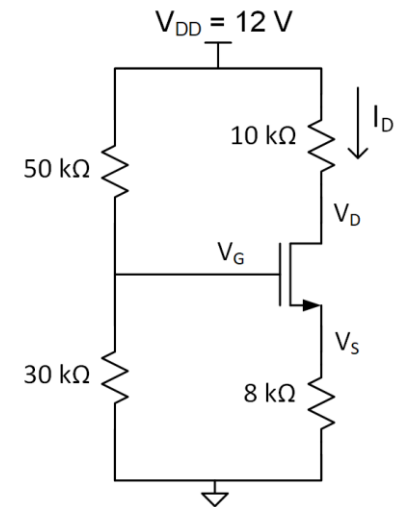
$$64e6 \cdot I_D^2 - 61.8e3 \cdot I_D + 14.44 = 0$$



$$V_t = 700 mV$$

$$k'_n \left( \frac{W}{L} \right) = 2 \frac{mA}{V^2}$$

# Four-Resistor Bias Circuit – Example

10

$$64e6 \cdot I_D^2 - 61.8e3 \cdot I_D + 14.44 = 0$$

- Solving the quadratic equation for  $I_D$  gives

$$I_D = 569 \mu A \text{ or } I_D = 396 \mu A$$

- For  $I_D = 569 \mu A$

$$V_S = I_D R_S = 569 \mu A \cdot 8 \text{ k}\Omega = 4.55 \text{ V}$$

$$V_{GS} = -50 \text{ mV} < V_t$$

- The transistor would be cut-off, so this is not a valid solution

- DC operating point:


$$I_D = 396 \mu A$$

$$V_S = 396 \mu A \cdot 8 \text{ k}\Omega = 3.17 \text{ V}$$

$$V_{GS} = 1.33 \text{ V}$$

$$V_{OV} = 630 \text{ mV}$$
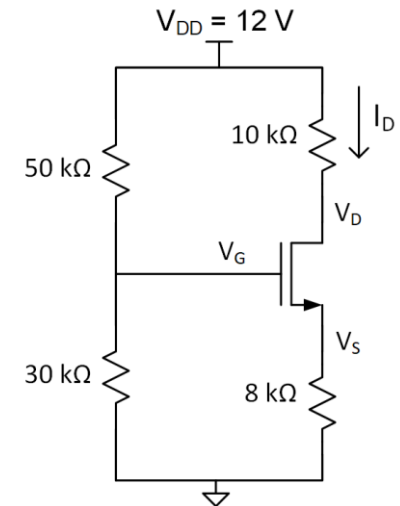
$$V_D = V_{DD} - I_D R_D = 8.04 \text{ V}$$



$$V_t = 700 \text{ mV}$$

$$k'_n \left( \frac{W}{L} \right) = 2 \frac{\text{mA}}{\text{V}^2}$$

# Design of the Four-Resistor Bias Circuit

11

- To design a bias network to provide a desired drain current:
  - Select  $R_D$  and  $R_S$  to each drop approximately one third of the supply voltage
    - That will leave approximately one third of the supply voltage across  $V_{DS}$
  - Calculate the required  $V_{OV}$ ,  $V_{GS}$ , and  $V_G$
  - Select the voltage divider resistors at the gate to provide the required gate voltage

# Bias Circuit Design - Example

12

- Design the bias network to provide  $I_D = 800 \mu A$
- Calculate  $R_D$  and  $R_S$  to each drop  $V_{DD}/3$

$$R_D = R_S = \frac{V_{DD}/3}{I_D} = \frac{5 V}{800 \mu A} = 6.25 k\Omega$$


- The required overdrive voltage is

$$V_{OV} = \sqrt{\frac{2I_D}{k'_n \left(\frac{W}{L}\right)}} = \sqrt{\frac{1.6 mA}{1 \frac{mA}{V^2}}} = 1.26 V$$

- The gate-source voltage

$$V_{GS} = V_{OV} + V_t = 1.26 V + 800 mV$$

$$V_{GS} = 2.06 V$$

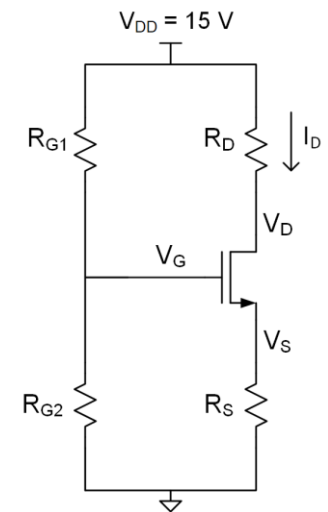

$$V_t = 800 mV$$

$$k'_n \left(\frac{W}{L}\right) = 1 \frac{mA}{V^2}$$

# Bias Circuit Design - Example

13

- Determine the required gate voltage

$$V_G = V_S + V_{GS} = I_D R_S + V_{GS}$$


$$V_G = 800 \mu\text{A} \cdot 6.25 \text{ k}\Omega + 2.06 \text{ V}$$

$$V_G = 7.06 \text{ V}$$

- Finally, select  $R_{G1}$  and  $R_{G2}$  to provide the required  $V_G$

$$R_{G1} = 100 \text{ k}\Omega$$

$$R_{G2} = 89 \text{ k}\Omega$$

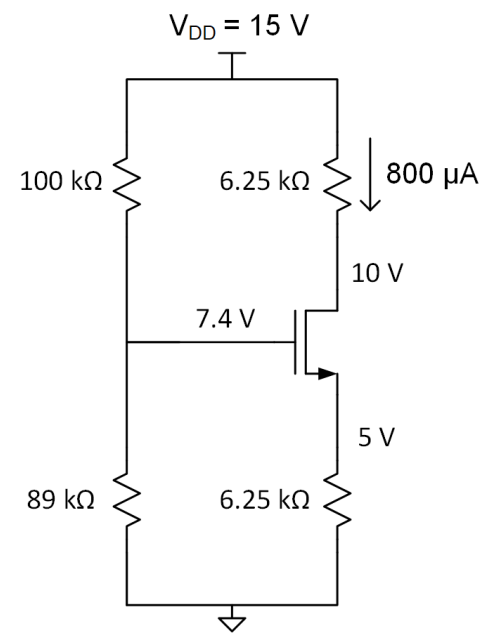

$$V_t = 800 \text{ mV}$$

$$k'_n \left( \frac{W}{L} \right) = 1 \frac{\text{mA}}{\text{V}^2}$$


14

# Common-Source Amplifier
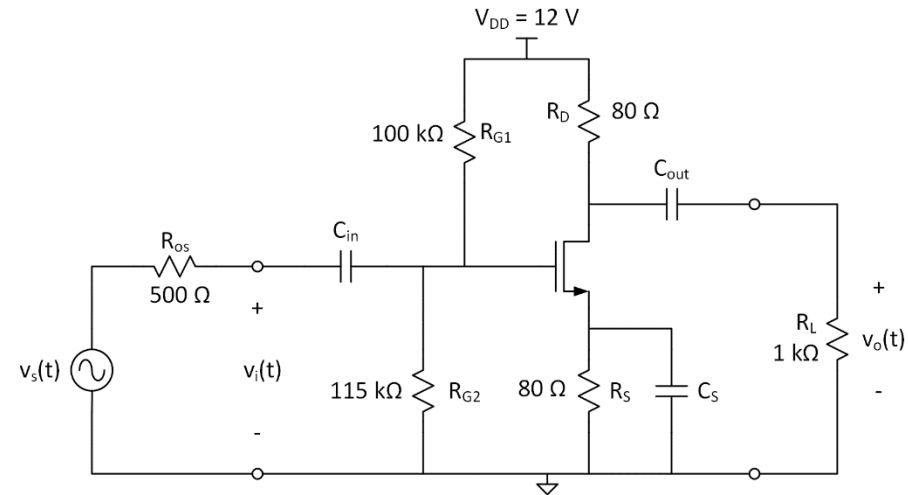
# Common-Source Amplifier

15

- Common-source amplifier
- All capacitors are **AC-coupling/DC blocking capacitors**
  - ▣ Open at DC
  - ▣ Shorts at signal frequencies
  - ▣ Isolate transistor bias from source/load



$$V_t = 1.6 V \quad k'_n \left( \frac{W}{L} \right) = 170 \frac{mA}{V^2}$$

- Called *common*-source, because source is connected to common – i.e., ground or a power supply
  - ▣  $C_S$  is a small-signal short to ground
  - ▣ Source is at small-signal ground

# Common-Source Amplifier

16


- Analyze the amplifier to find:
  - ▣ DC operating point
  - ▣ Small-signal voltage gain

- DC operating point:
  - ▣ The gate voltage is given by

$$V_G = V_{DD} \frac{R_{G2}}{R_{G1} + R_{G2}}$$

$$V_G = 12 \text{ V} \frac{115 \text{ k}\Omega}{100 \text{ k}\Omega + 115 \text{ k}\Omega}$$

$$V_G = 6.4 \text{ V}$$

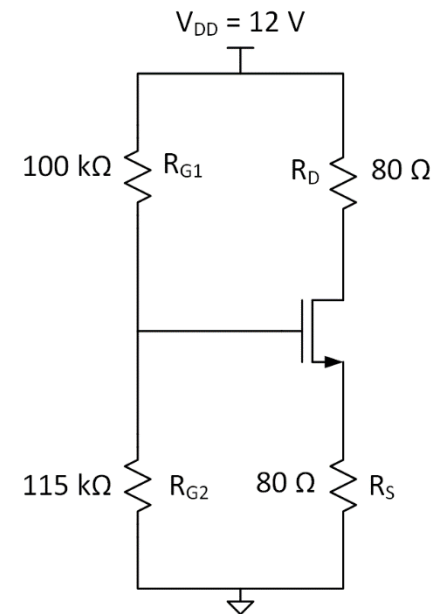



# C-S Amplifier – Large-Signal Analysis

17

- Drain current is given by

$$I_D = \frac{1}{2} k'_n \left( \frac{W}{L} \right) V_{OV}^2 = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (V_G - I_D R_S - V_t)^2$$

- As we have seen, solving for  $I_D$  results in the following quadratic

$$R_S^2 I_D^2 - \left[ 2R_S(V_G - V_t) + \frac{1}{\frac{1}{2} k'_n \left( \frac{W}{L} \right)} \right] I_D + (V_G - V_t)^2 = 0$$

$$6.4e3 \cdot I_D^2 - 779.8 \cdot I_D + 23.0 = 0$$

- This has two solutions

$$I_D = 72 \text{ mA} \quad \text{or} \quad I_D = 51 \text{ mA}$$

- The first solution would put the transistor in cutoff, so  $I_D = 51 \text{ mA}$

# C-S Amplifier – Large-Signal Analysis

18

- Use the drain current to determine terminal voltages

$$V_D = V_{DD} - I_D R_D$$

$$V_D = 12 \text{ V} - 51 \text{ mA} \cdot 80 \Omega = 7.95 \text{ V}$$

$$V_S = I_D R_S = 51 \text{ mA} \cdot 80 \Omega$$


$$V_S = 4.05 \text{ V}$$

- The complete DC operating point:

$$V_G = 6.42 \text{ V} \qquad I_D = 51 \text{ mA}$$

$$V_{GS} = 2.37 \text{ V} \qquad V_D = 7.95 \text{ V}$$
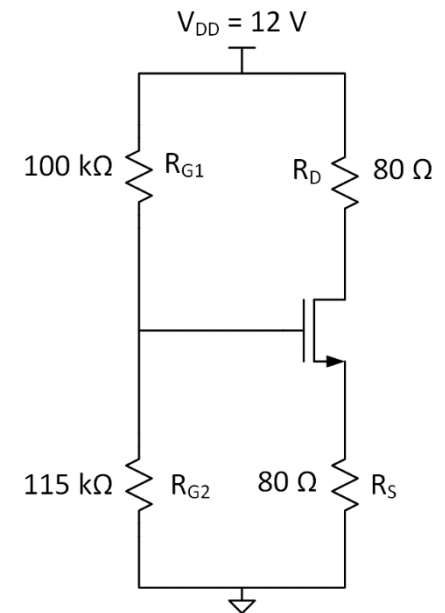
$$V_{OV} = 0.77 \text{ V} \qquad V_S = 4.05 \text{ V}$$



# C-S Amplifier – Small-Signal Analysis

19

- The DC operating point allows us to determine the transconductance for the transistor's small-signal model


$$g_m = k'_n \left( \frac{W}{L} \right) V_{OV} = 170 \frac{mA}{V^2} \cdot 0.77 V = 131 mS$$

- Next, create the ***small-signal equivalent circuit*** for the amplifier and perform a ***small-signal analysis***:
  1. Replace all AC coupling capacitors with shorts
    - Large enough to look like shorts at signal frequencies
  2. Connect all DC supply voltages to ground
    - From a small-signal perspective these are all constant voltages
    - Small-signal ground
  3. Replace the transistor with its small-signal model
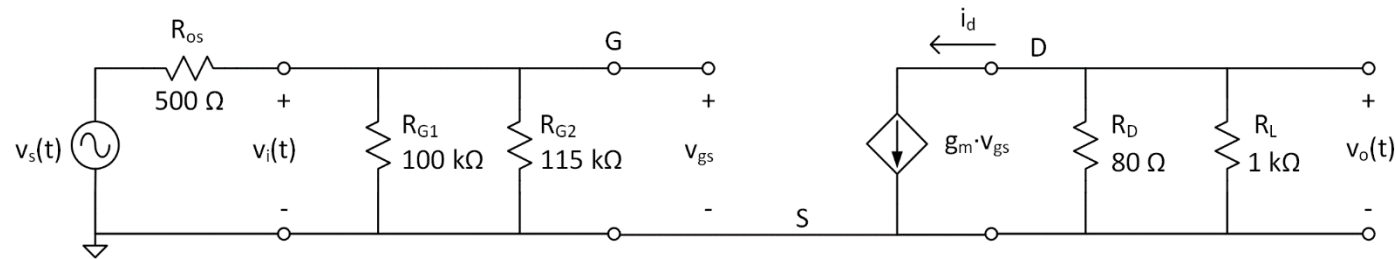
# C-S Amplifier – Small-Signal Analysis

20

- Small-signal equivalent circuit
  - ▣ Use to determine small-signal voltage gain



- Source is connected to small signal ground through  $C_S$
- $R_{G1}$  and  $R_{G2}$  appear in parallel at the gate

$$R_i = R_{G1} || R_{G2} = 53.5 \text{ k}\Omega$$


- $R_D$  and  $R_L$  are in parallel at the output

$$R_o = R_D || R_L = 74 \Omega$$

- Input voltage,  $v_i(t)$ , is the gate-source voltage,  $v_{gs}$

# C-S Amplifier – Small-Signal Analysis

21

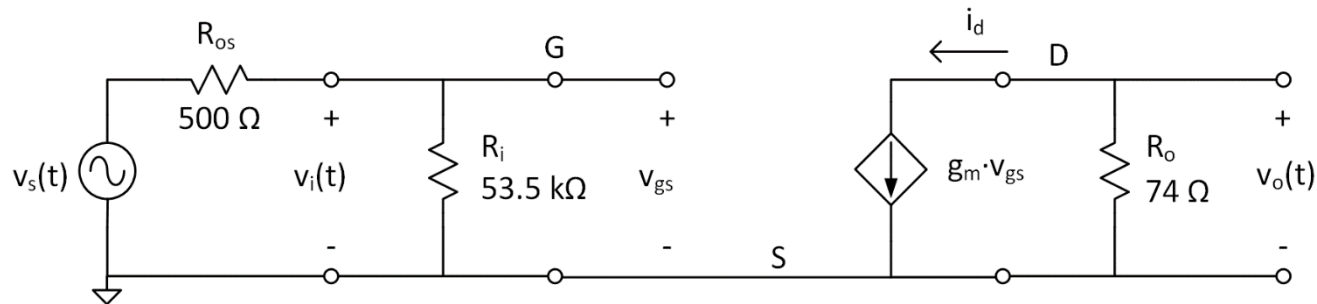

- Determine the small-signal voltage gain:

$$A_v = \frac{v_o}{v_i} \quad (1)$$

- The input is applied across the G-S junction, so


$$v_i = v_{gs} \quad (2)$$

- The output is the drain current applied across the output resistance

$$v_o = -i_d R_o = -g_m v_{gs} R_o \quad (3)$$

# C-S Amplifier – Small-Signal Analysis

22

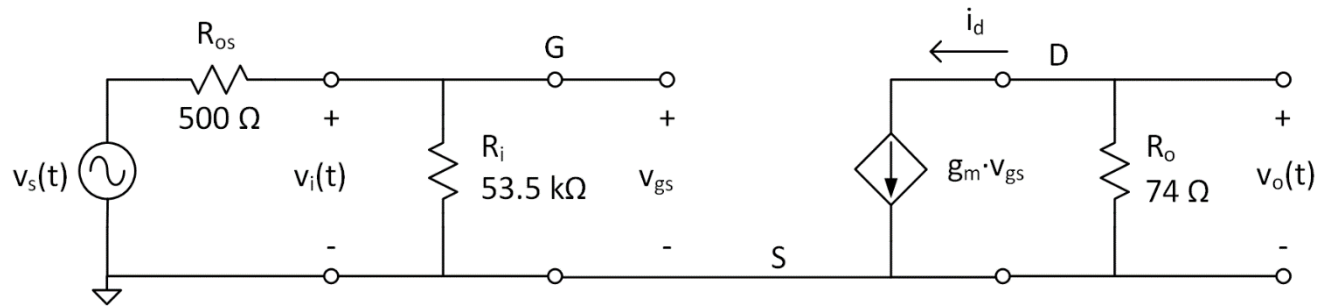

- Substituting (3) and (2) into (1) gives the gain:

$$A_v = \frac{v_o}{v_i} = -\frac{g_m v_{gs} R_o}{v_{gs}} = -g_m R_o$$


- This is the gain for *any* common-source amplifier

$$A_v = -g_m R_o$$

- The negative sign indicates that the amplifier has ***inverting*** gain

# C-S Amplifier – Small-Signal Analysis

23

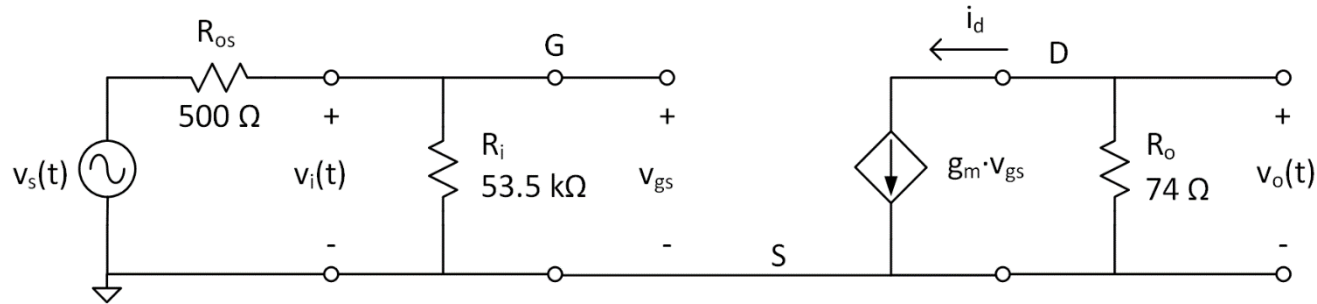

- For this circuit, the gain (from  $v_i$  to  $v_o$ ) is

$$A_v = \frac{v_o}{v_i} = -131 \text{ mS} \cdot 74 \text{ } \Omega = -9.7$$

- For the gain from  $v_s$  to  $v_o$ , account for attenuation due to source loading


$$A_v = \frac{v_o}{v_s} = \frac{v_i}{v_s} \cdot \frac{v_o}{v_i} = \frac{R_i}{R_s + R_i} \cdot (-g_m R_o)$$

- Here,


$$A_v = \frac{v_o}{v_s} = \frac{53.5 \text{ k}\Omega}{500 \text{ } \Omega + 53.5 \text{ k}\Omega} \cdot (-9.7) = -9.6$$

# C-S Amplifier – Small-Signal Analysis

24

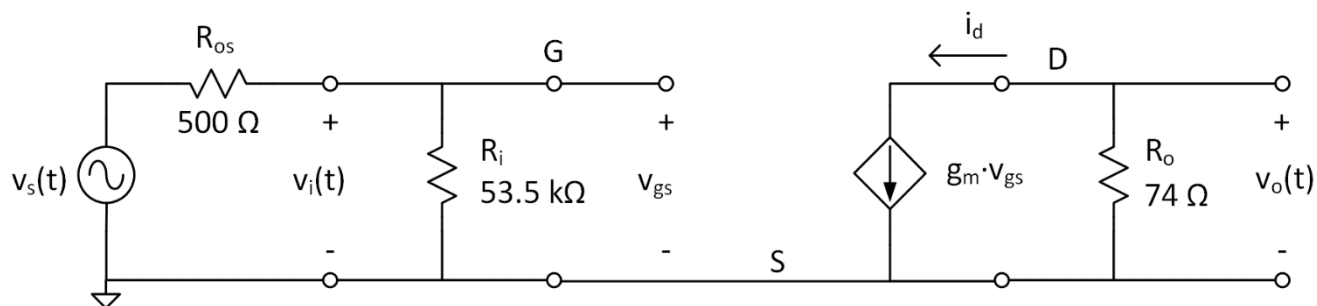

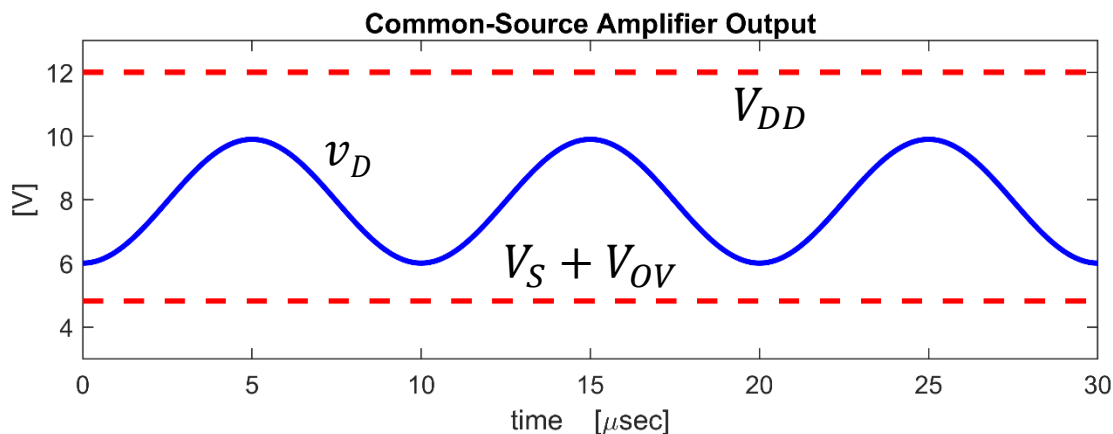- The output for a  $200 \text{ mV}_{pp}$ ,  $100 \text{ kHz}$  input:





# C-S Amplifier – Dynamic Range

25

## □ **Dynamic range**

- Range of input or output signal for which the transistor remains in the **saturation region**

- The amplifier's **linear range**


## □ For saturation bias:

- D-S voltage must remain greater than the overdrive voltage

$$v_{DS} > V_{OV}$$

- G-S voltage must remain greater than the threshold voltage

$$v_{GS} > V_t$$

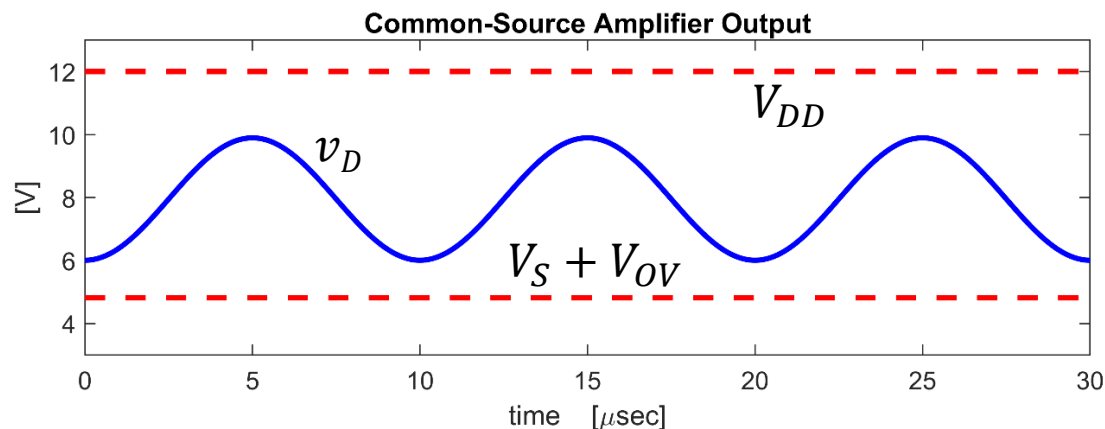

# C-S Amplifier – Input & Output Resistance

26

- Gate resistance is infinite, so amplifier input resistance is


$$R_i = R_{G1} || R_{G2}$$

- Output resistance is the drain resistance:

$$R_o = R_D$$

- ▣ Or, if accounting for channel-length modulation:

$$R_o = R_D || r_o$$

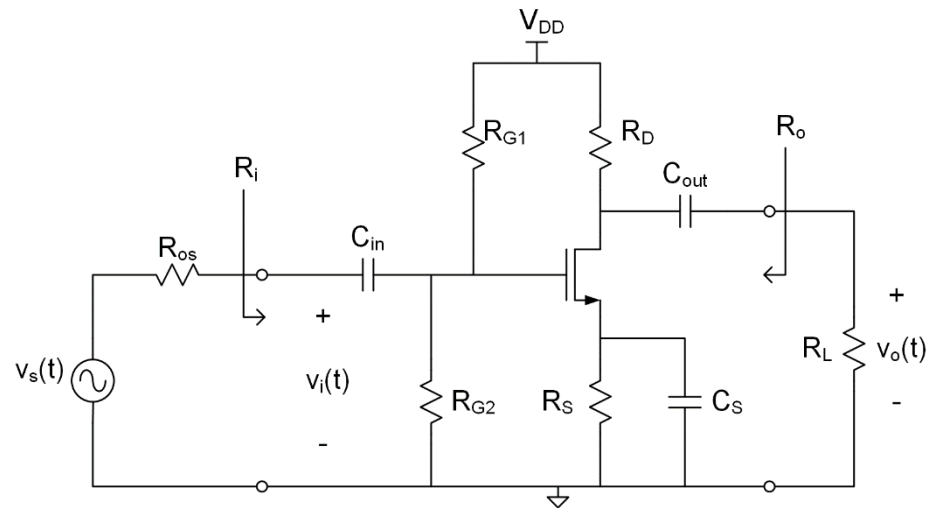

# C-S Amplifier – Gain

27

$$A_v = -g_m R_o$$

- C-S gain is **determined by  $g_m$  and  $R_o$** 
  - Select  $R_o$  ( $R_D$ ) and set  $g_m$  for desired gain
  - Transconductance is proportional to the square root of bias current

$$g_m = \sqrt{k'_n \left(\frac{W}{L}\right) I_D}$$


- Therefore, **gain is proportional to the square root of bias current**

28

# Source Degeneration

# C-S Amplifier – Source Degeneration


29

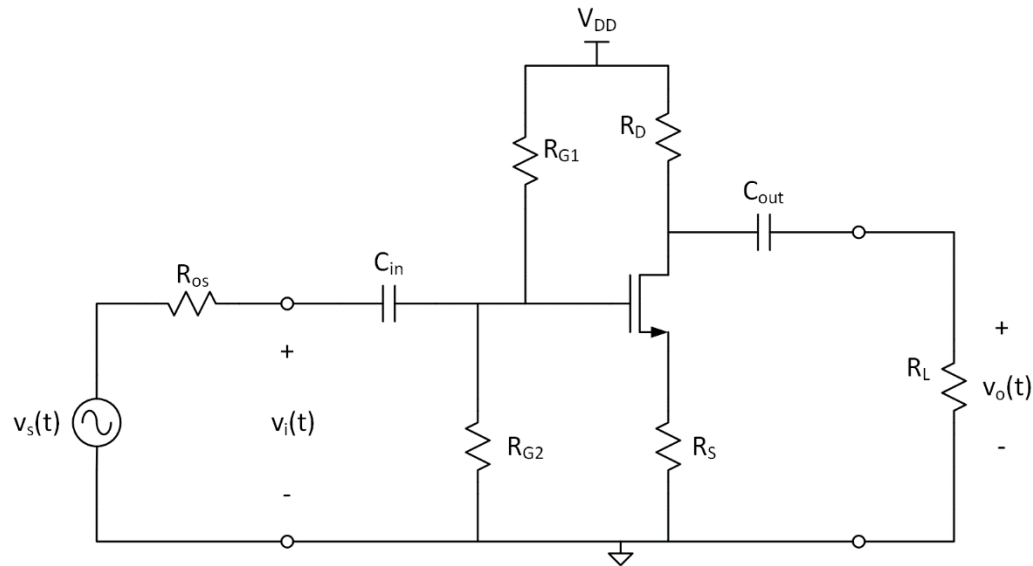

- The C-S amplifier we have looked at so far had its source grounded (small-signal ground)
  - Due to bypass capacitor,  $C_S$ , around  $R_S$
- What if we remove  $C_S$ ?
  - Or add another source resistor not bypassed by  $C_S$
  - **Source degeneration**

# C-S Amplifier – Source Degeneration

30

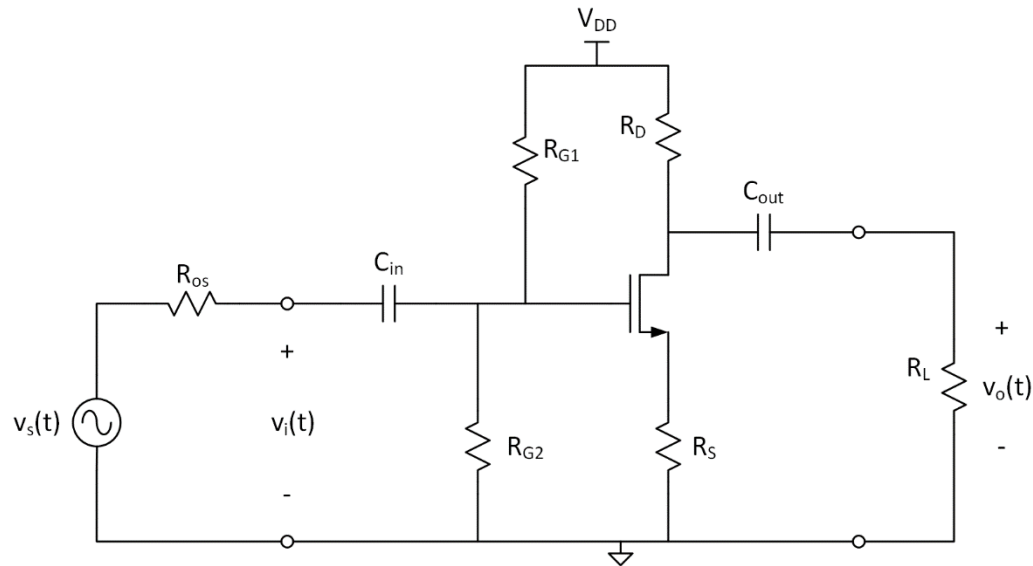

- Now,  $R_S$  is included in the small signal equivalent circuit
  - ▣ Source is no longer connected to small-signal ground
- Analysis will be simplified if we use the T-model
  - ▣ Usually the case whenever we have source resistance
  - ▣  $R_S$  will be in series with resistance in the model

# C-S Amplifier – Source Degeneration

31

- The output is still given by

$$v_o = -i_d R_o = -g_m v_{gs} R_o$$


- But, now,  $v_{gs}$  is the portion of  $v_i$  that appears across the  $1/g_m$  resistance

$$v_{gs} = v_i \frac{1/g_m}{1/g_m + R_S}$$

$$v_{gs} = v_i \frac{1}{1 + g_m R_S}$$

- The output is
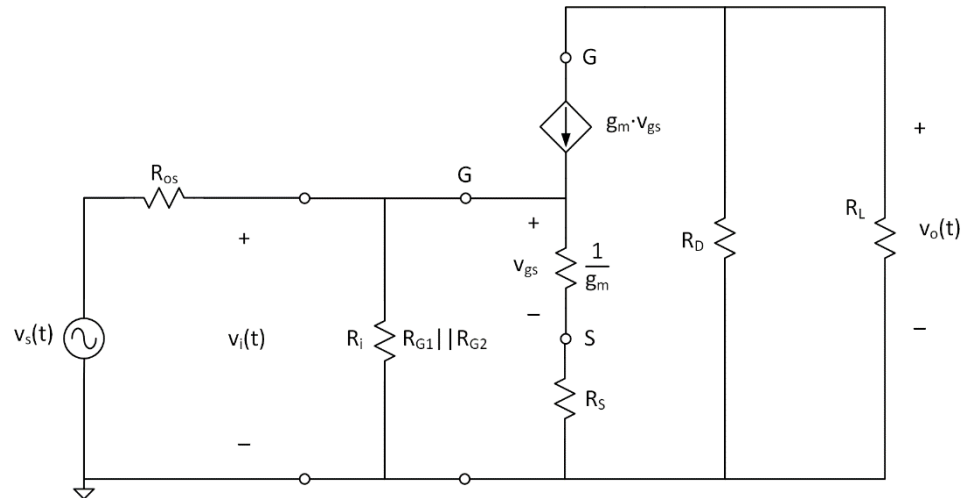
$$v_o = v_i \left( -g_m R_o \frac{1}{1 + g_m R_S} \right)$$




# Source Degeneration – Gain

32

- Rearranging the expression for the output gives the gain

$$A_v = -\frac{g_m R_o}{1 + g_m R_S}$$

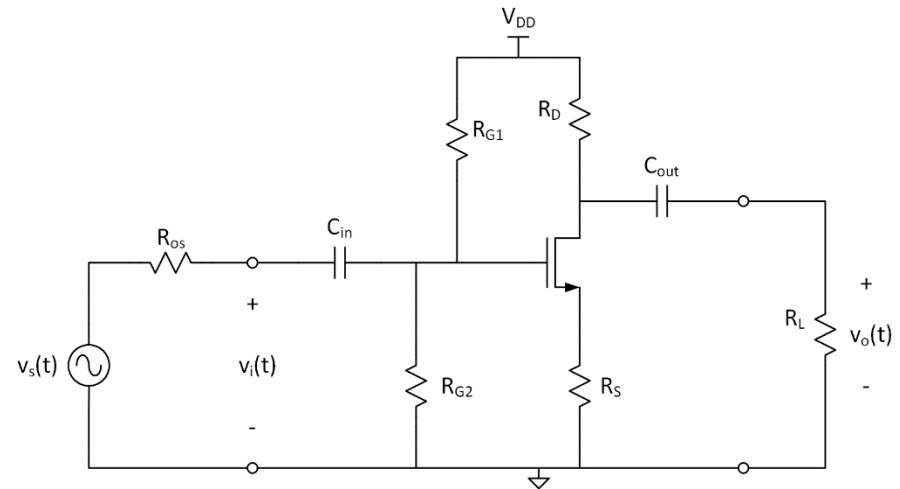

- **Source degeneration reduces the gain by a factor of  $(1 + g_m R_S)$**
- If  $R_S \gg 1/g_m$ , then  $g_m R_S \gg 1$ , and

$$A_v = -\frac{R_o}{R_S}$$



# Source Degeneration – Transconductance

33

$$A_v = -\frac{g_m R_o}{1 + g_m R_S}$$


- We can rewrite the gain as

$$A_v = -G_m R_o$$

- $G_m$  is the **effective transconductance of the amplifier**

$$G_m = \frac{g_m}{1 + g_m R_S}$$

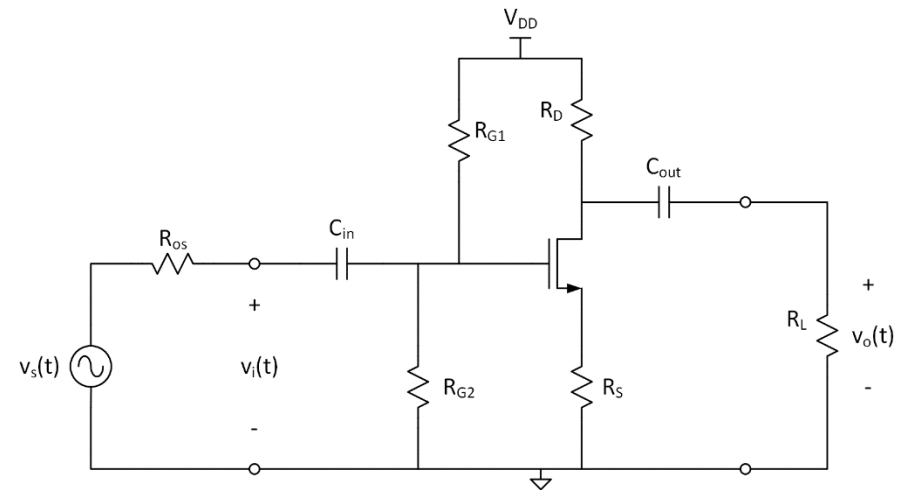- **Source degeneration reduces the transconductance by a factor of  $(1 + g_m R_S)$** 
  - This is why we see a reduction in gain by the same factor




34

# Source Follower

# Source-Follower


35

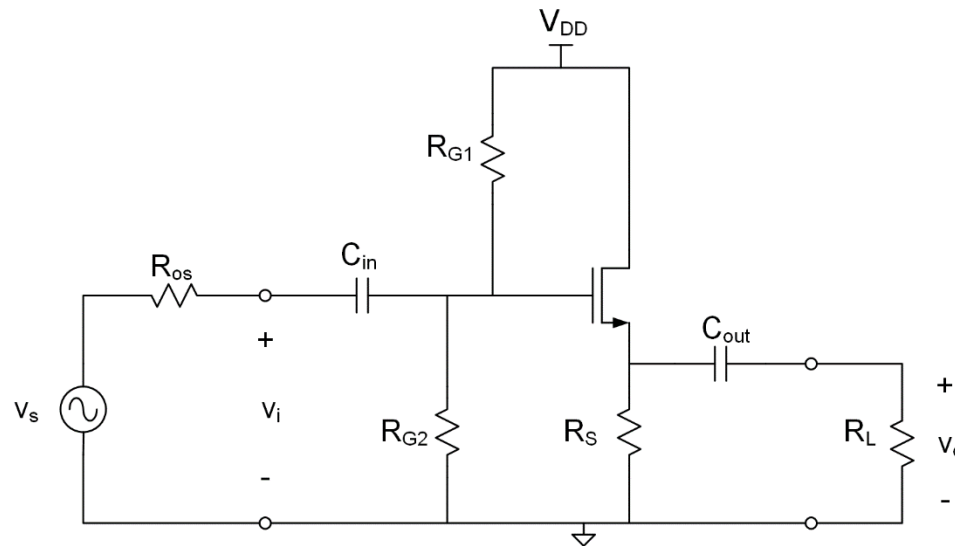

- **Source-follower amplifier**
  - ▣ Input applied to the gate
  - ▣ Output at the source
  - ▣ Source *follows* the gate
- Also called a **common-drain** amplifier (CD)
  - ▣ Drain is connected to small-signal ground

# Source-Follower – Small-Signal Analysis

36

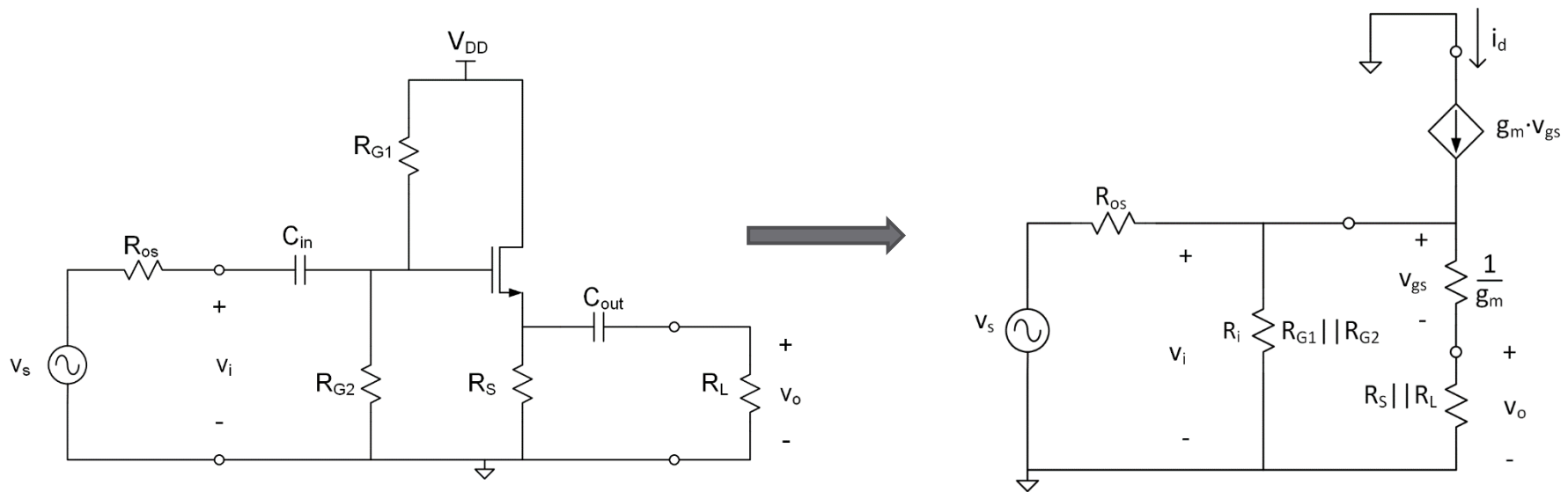

- Replace the MOSFET with small-signal model
  - Source resistance, so use T-model
  - Short coupling caps
  - DC voltages connect to ground
  - Simplify parallel resistances

# Source-Follower – Small-Signal Analysis

37

- Determine the gain from  $v_i$  to  $v_o$

$$A_v = \frac{v_o}{v_i}$$


Applying voltage division gives the output

$$v_o = v_i \frac{R_S \parallel R_L}{\left(R_S \parallel R_L + \frac{1}{g_m}\right)}$$

Rearrange to get the gain

$$A_v = \frac{R_S \parallel R_L}{\left(R_S \parallel R_L + \frac{1}{g_m}\right)}$$

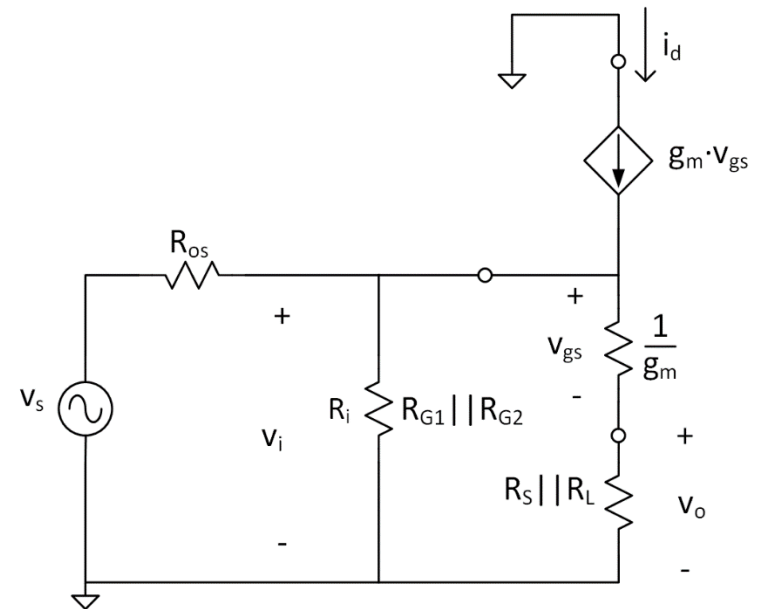- Clearly,  $A_v < 1$
- But, for  $R_S \parallel R_L \gg 1/g_m$ ,  $A_v \approx 1$



# Source Follower – Input & Output Resistance



38

- Gate resistance is infinite, so amplifier input resistance is

$$R_i = R_{G1} || R_{G2}$$

- The output resistance is the source resistance in parallel with  $1/g_m$ :

$$R_o = R_S || \frac{1}{g_m}$$

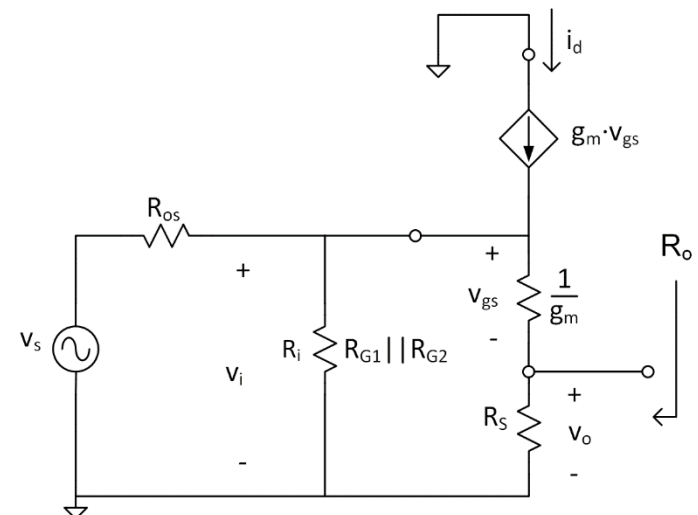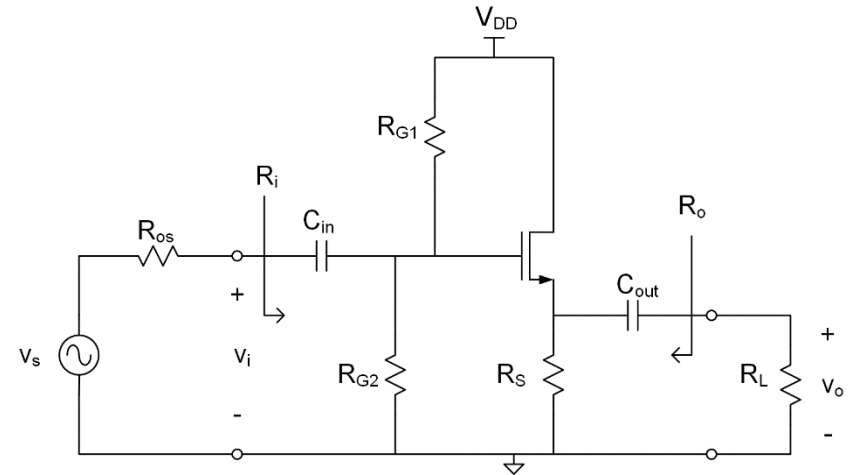


39

# Common-Gate Amplifier

# Common-Gate Amplifier

40

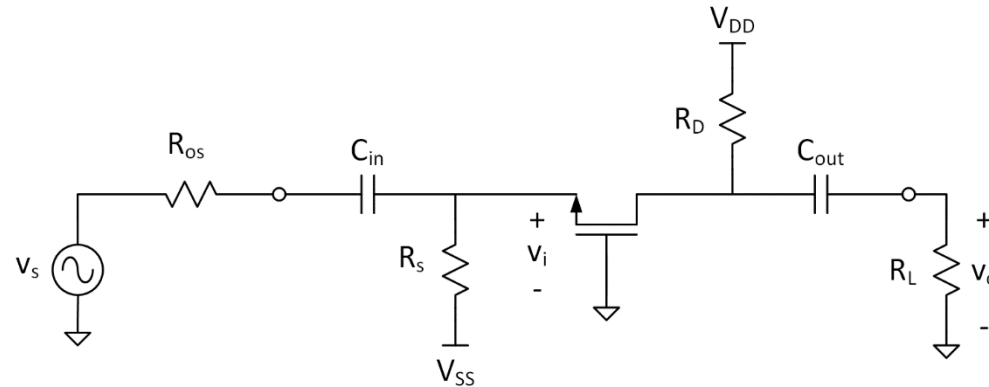

- The third MOSFET amplifier configuration we will look at is the ***common-gate amplifier***
  - ▣ Input applied to the source
  - ▣ Output taken from the drain
  - ▣ Gate is connected to small-signal ground
  - ▣ The least common of the three amplifiers



# Common-Gate Amplifier – Gain


41

- There is source resistance, so use the T-model for small-signal analysis
- The output is given by

$$v_o = -i_d R_D || R_L$$

$$v_o = -g_m v_{gs} R_D || R_L$$

$$v_o = g_m v_i R_D || R_L$$

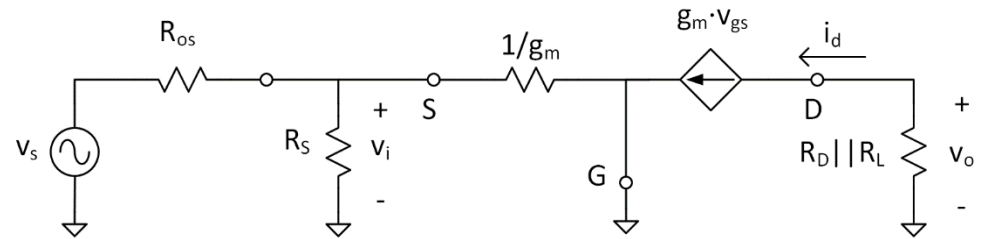


- Common-gate voltage gain is

$$A_v = g_m R_D || R_L$$

# Common-Gate – Input Resistance

42

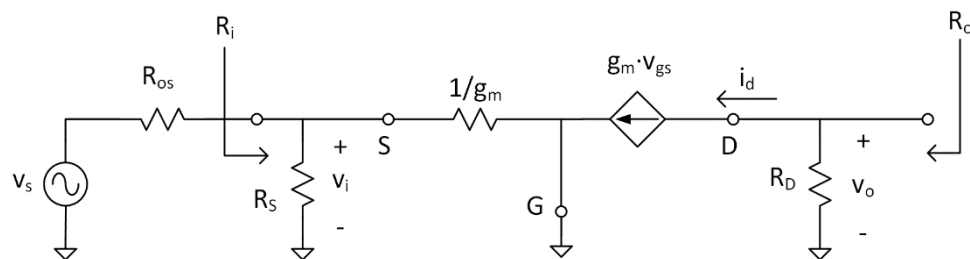

- $R_i$  is the parallel combination of the resistance connected to the source and the resistance looking into the source


$$R_i = R_S \parallel \frac{1}{g_m}$$

- If  $1/g_m \ll R_S$ , then

$$R_i \approx \frac{1}{g_m}$$

# Common-Gate – Output Resistance

43

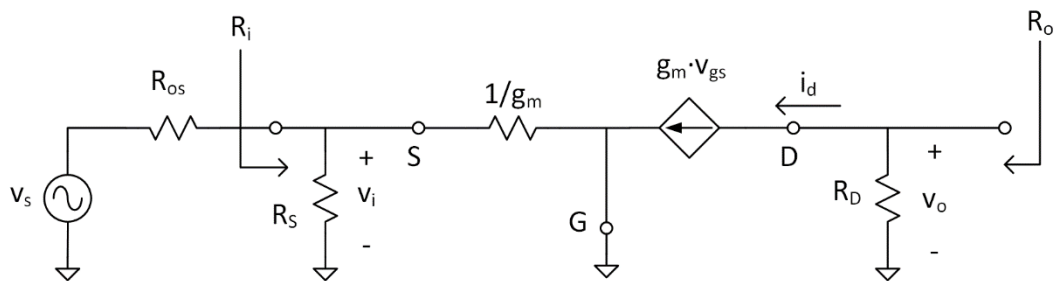

- If we neglect the transistor's output resistance,  $r_o$ , the common-gate output resistance is

$$R_o = R_D$$

- Entirely determined by the drain resistor

# Common-Gate Amplifier

44

- Low input resistance

$$R_i \approx \frac{1}{g_m}$$

- For  $R_{os} \gg 1/g_m$ , there will be significant attenuation from  $v_s$  to  $v_i$

$$v_i \ll v_s$$

- The overall gain from  $v_s$  to  $v_o$  may be small
- Like the common-base amplifier, useful in specific applications:
  - Low source resistance
    - E.g., amplifiers driven by cables
    - $R_i$  matched to  $Z_0$  (e.g.  $50 \Omega$  or  $75 \Omega$ ) to avoid reflections
  - Current buffers
    - E.g., in ***cascode*** amplifiers

45

# MOSFETs as Switches

# MOSFETs as Switches


46

- MOSFETs used as **switches** operate alternately in the **triode** (closed) and **cutoff** (open) regions
- Equivalent circuit models:
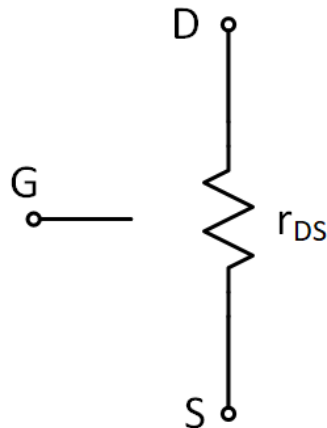
## Triode Region (ON):

- $V_{GS} > V_t$ 
  - $V_{GS} = V_{DD}$


- Switch is on
- $I_D \geq 0$
- $V_{DS} = I_D r_{DS} < V_{OV}$


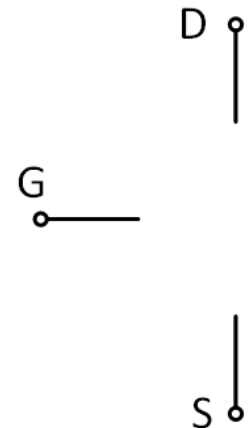
## Cutoff Region (OFF):

- $V_{GS} < V_t$ 
  - $V_{GS} = 0$


- Switch is off
- $I_D = 0$
- $V_{DS} = V_{DD}$


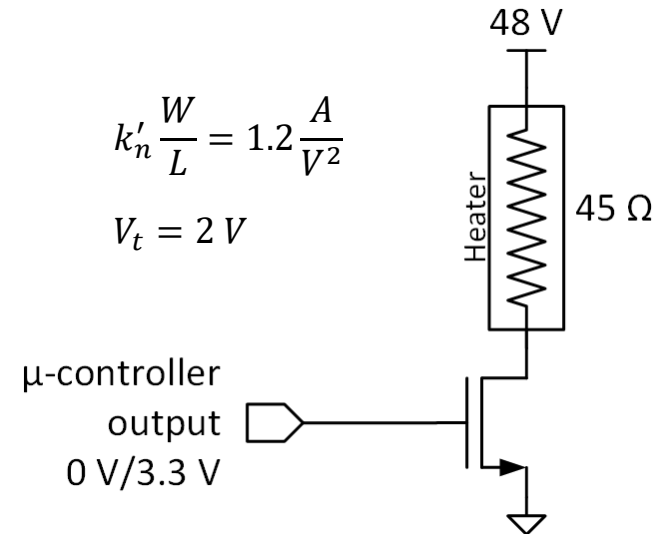
# Using a MOSFET as a Switch - Example

47


- Turn resistance heater on and off using a microcontroller
  - Heater may require amperes of current
  - Microcontroller output may be limited to tens of mA
- 
- Control a MOSFET switch with the microcontroller output
    - Low-current control signal from the microcontroller
      - Gate draws no DC current
    - MOSFET switches the large current required by the heater


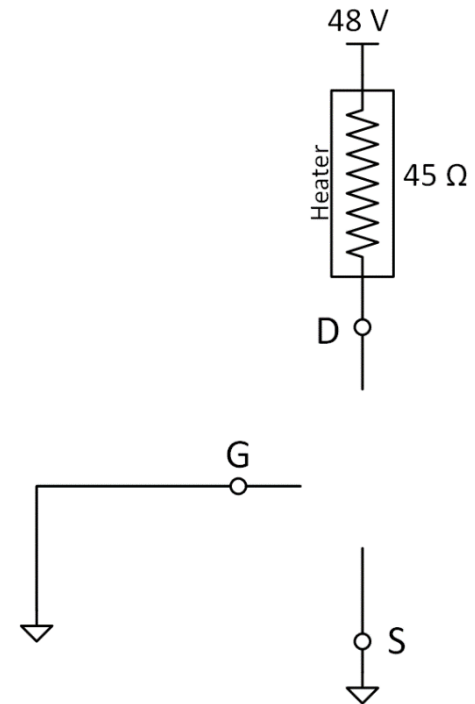
# Using a MOSFET as a Switch - Example

48

- When the  $\mu$ -controller's output is low (0 V)
  - $V_{GS} = 0\text{ V}$
  - Transistor is in the cutoff region
  - Switch is off
  - No current flows
  - The heater is off





# Using a MOSFET as a Switch - Example

49

- When the  $\mu$ -controller's output is high (3.3 V)
  - ▣  $V_{GS} = 3.3\text{ V}$ ,  $V_{OV} = 1.3\text{ V}$
  - ▣ Transistor is in triode
  - ▣ Switch and heater are on


- Drain current in triode is:

$$I_D = k'_n \frac{W}{L} \left[ V_{OV} - \frac{1}{2} V_{DS} \right] V_{DS}$$

$$I_D = k'_n \frac{W}{L} \left[ V_{OV} - \frac{1}{2} (48\text{ V} - I_D R_h) \right] (48\text{ V} - I_D R_h)$$

- Can solve the above quadratic, or, assuming  $V_{DS}$  is small, approximate switch on-resistance as:
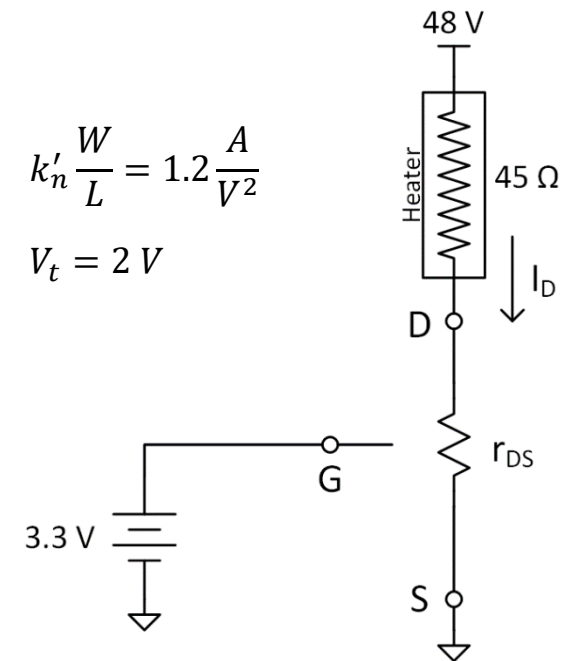
$$r_{DS} \approx \frac{1}{k'_n \frac{W}{L} V_{OV}} = \frac{1}{1.2 \frac{\text{A}}{\text{V}^2} \cdot 1.3\text{ V}} = 641\text{ m}\Omega$$



$$k'_n \frac{W}{L} = 1.2 \frac{\text{A}}{\text{V}^2}$$

$$V_t = 2\text{ V}$$

# Using a MOSFET as a Switch - Example

50

- Voltage division gives approximate drain voltage

$$V_D = 48 V \cdot \frac{r_{DS}}{R_h + r_{DS}} = 48 V \cdot \frac{641 m\Omega}{45 \Omega + 641 m\Omega}$$

$$V_D = 674 mV$$

- Drain current is approximately


$$I_D = \frac{48 V}{R_h + r_{DS}} = \frac{48 V}{45 \Omega + 641 m\Omega}$$

$$I_D = 1.05 A$$

- Heater power is

$$P_h = I_D^2 R_h = (1.05 A)^2 \cdot 45 \Omega$$

$$P_h = 49.75 W$$

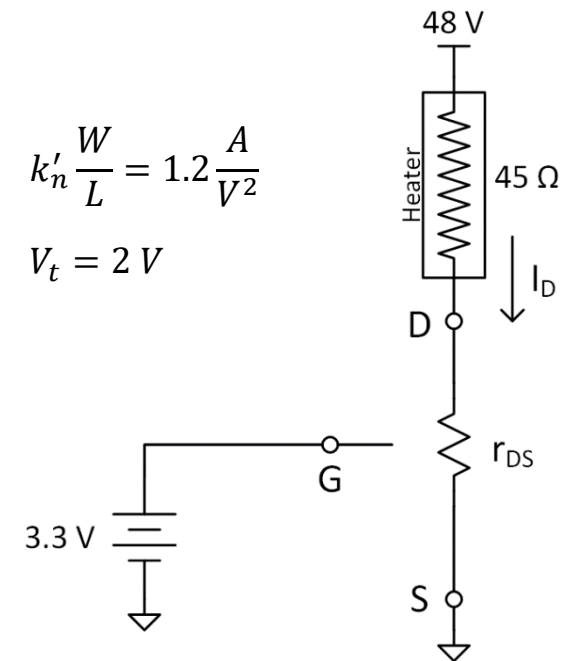

$$k'_n \frac{W}{L} = 1.2 \frac{A}{V^2}$$

$$V_t = 2 V$$