

# SECTION 6: INTEGRATED CIRCUIT BUILDING BLOCKS

ECE 322 – Electronics I

# Integrated Circuit Design Principles

2

- On-chip real estate is at a premium
  - ▣ Chip area is costly
- High-value resistors consume too much area and are avoided
  - ▣ Use transistor current sources for loads and biasing
- High-value capacitors consume too much area
  - ▣ Amplifier stages typically directly coupled
- Must account for transistor output resistance
  - ▣ Device dimensions are smaller
- Do not have precise control over device parameters
  - ▣ But, precise matching of devices is attainable
- Designers have control over transistor dimensions
  - ▣ Gate/channel aspect ratio:  $W, L$  for CMOS devices
  - ▣ Emitter area:  $W, L$  for BJTs

# Building Blocks of Integrated Circuits

3

- Analog integrated circuits make use of several very common building blocks:
- ***Amplifiers***
  - The amplifiers we have already learned about, with some modifications
  - ***Cascode amplifiers*** employ current buffers between transconductance devices and loads
- ***Current sources/current mirrors***
  - Active loads for amplifiers
  - Biasing for amplifiers and other circuits


4

# Current Mirrors
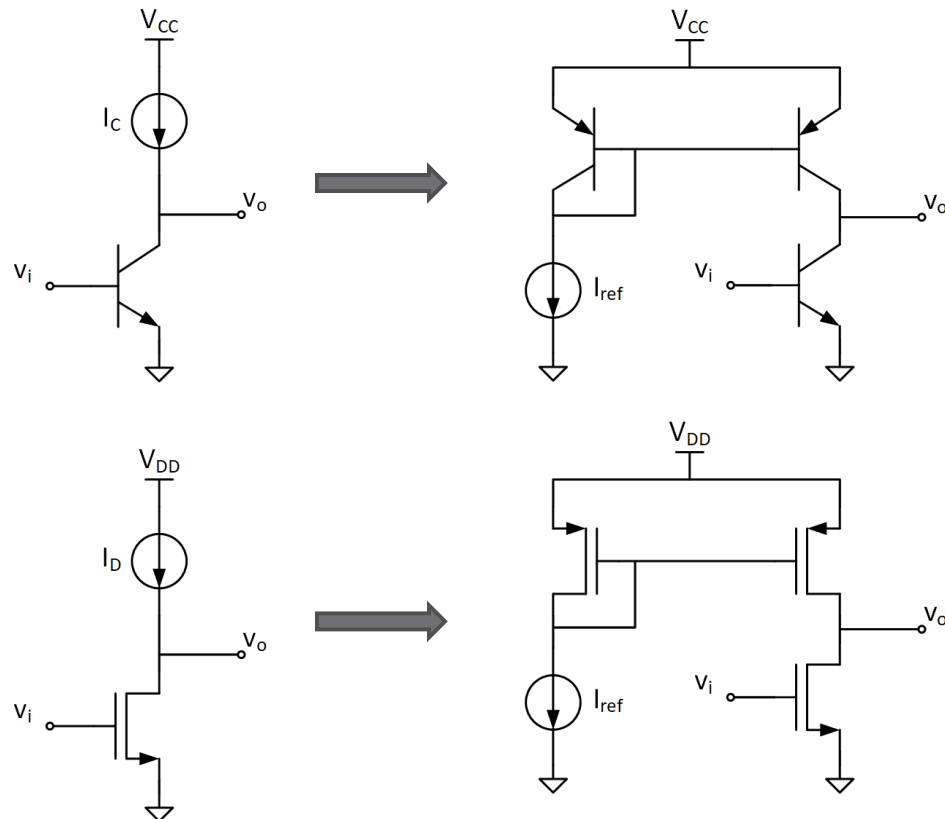
# Active Loads

5

- Transistor current sources are typically used as amplifier loads instead of resistors
  - ▣ Higher resistance, higher gain
  - ▣ Smaller area



# Current Mirrors


6

- Current sources are used everywhere on ICs
  - ▣ Amplifier loads
  - ▣ Transistor biasing
- Single circuit used to generate a reference current
  - ▣ Often a single bias generator circuit on a chip
- Reference current is replicated, and scaled, as needed at various circuits across the chip
  - ▣ ***Current steering***
- Replication of current accomplished by ***current mirrors***
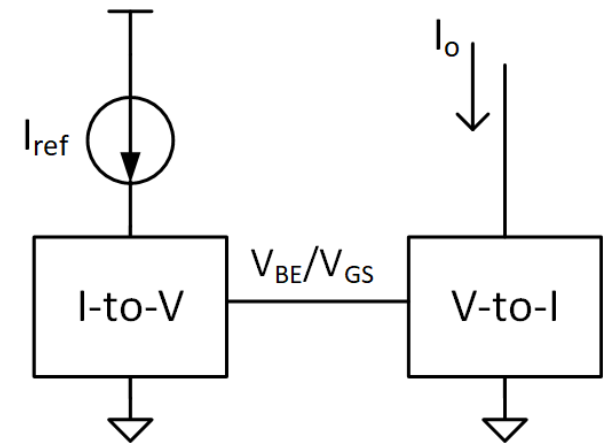
# Current Mirror – Basic Principles

7


- Current mirrors have two components:
- **Transresistance** stage
  - ▣ Current-to-voltage conversion
  - ▣ Low input resistance
  - ▣ Generates a voltage ( $V_{BE}$  or  $V_{GS}$ ) proportional to the input current ( $I_C$  or  $I_D$ )
- **Transconductance** stage
  - ▣ Voltage-to-current conversion
  - ▣ High output resistance (a current source)
  - ▣ Generates a current ( $I_C$  or  $I_D$ ) proportional to the input voltage ( $V_{BE}$  or  $V_{GS}$ )



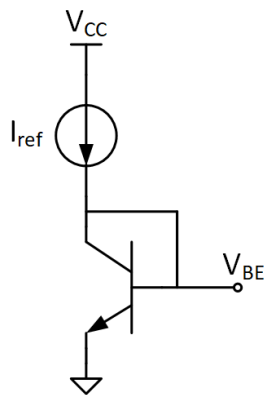
# Current Mirror – Transresistance Stage

8

- Current-to-voltage conversion
- **Diode-tied transistor**
  - ▣ Base/collector or gate/drain connected together
  - ▣ Looks like a diode
- Reference current applied to collector or drain
- Base-emitter or gate-source voltage generated proportional to collector or drain current


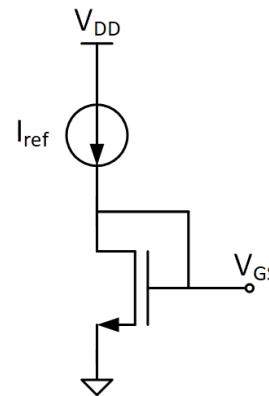
$$V_{BE} = V_{th} \ln \left( \frac{I_C}{I_S} \right)$$



$$V_{GS} = \sqrt{\frac{2I_D}{k'_n \left( \frac{W}{L} \right)}} + V_t$$



# Simple MOS Transresistance Stage

9

- Drain current


$$I_{ref} = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (V_{DD} - I_D R - V_t)^2$$

- A quadratic equation for  $I_{ref}$

$$R^2 I_{ref}^2 - \left[ 2(V_{DD} - V_t)R + \frac{2}{k'_n \left( \frac{W}{L} \right)} \right] I_{ref} + (V_{DD} - V_t)^2 = 0$$

- Solve to determine  $I_{ref}$
- Or, to determine  $R$  for desired  $I_{ref}$ :
  - Calculate overdrive voltage,  $V_{OV}$
  - Determine gate voltage
  - Apply Ohm's law:

$$R = \frac{V_{DD} - V_G}{I_{ref}}$$

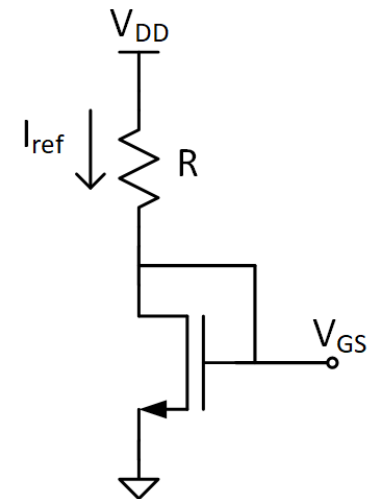

# Simple BJT Transresistance Stage

10

- Resistor in series with a diode-tied transistor
- Current through the resistor


$$I_{ref} = \frac{V_{CC} - V_{BE}}{R}$$

- Using the large-signal BJT model, where  $V_{BE} = 700 \text{ mV}$ :

$$I_{ref} = \frac{V_{CC} - V_{BE}}{R}$$

$$I_{ref} = \frac{V_{CC} - 700 \text{ mV}}{R}$$

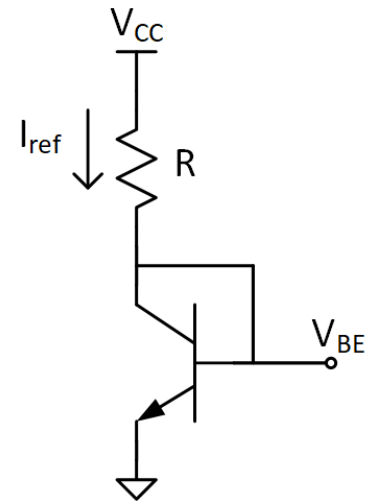
- $V_{BE}$  is inversely proportional to temperature
  - $I_{ref}$  increases with increasing temperature
  - A proportional-to-absolute-temperature (PTAT) current



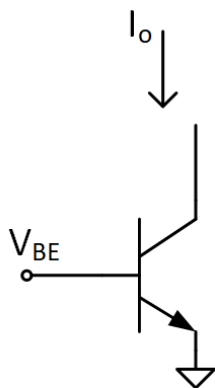
# Current Mirror – Transconductance Stage

11

- Voltage-to-current conversion
- Transresistance device's output voltage applied to the base or gate of the transconductance device
- Transistor must remain in the forward active (BJT) or saturation region (MOS)
- Output current proportional to the applied voltage
- High output resistance



$$I_o = I_s e^{\frac{V_{BE}}{V_{th}}}$$

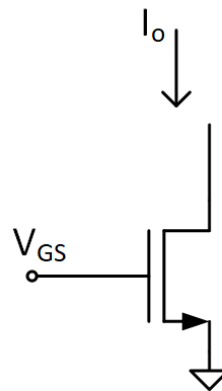

$$I_o = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (V_{GS} - V_t)^2$$

# Simple MOS Current Mirror

12

- Gate-source voltages:

$$V_{GS} = \sqrt{\frac{2I_{ref}}{k'_n \left(\frac{W}{L}\right)_1}} + V_t$$


- Output current:

$$I_o = \frac{1}{2} k'_n \left(\frac{W}{L}\right)_2 (V_{GS} - V_t)^2$$

$$I_o = \frac{1}{2} k'_n \left(\frac{W}{L}\right)_2 \frac{2I_{ref}}{k'_n \left(\frac{W}{L}\right)_1}$$

$$I_o = I_{ref} \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1}$$

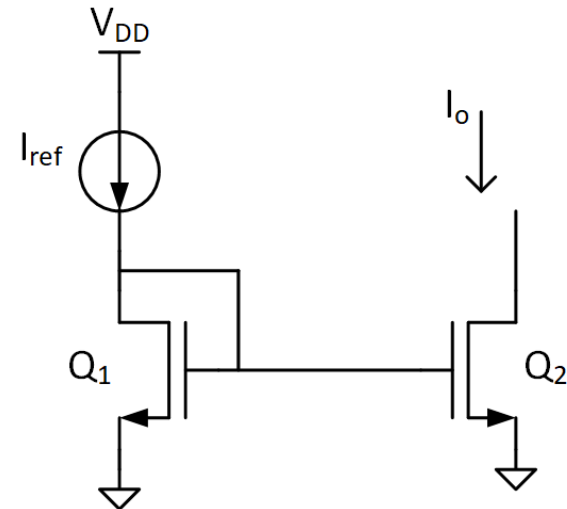- Output current scaled by the device aspect ratios
  - The **current transfer ratio** or current gain of the mirror



# Simple BJT Current Mirror

13

- First, assume  $\beta \approx \infty$
- Base-emitter voltages:

$$V_{BE} = V_{th} \ln\left(\frac{I_{ref}}{I_{S1}}\right)$$


- Output current:

$$I_o = I_{S2} e^{\frac{V_{BE}}{V_{th}}} = I_{S2} e^{\ln\left(\frac{I_{ref}}{I_{S1}}\right)}$$

$$I_o = I_{ref} \frac{I_{S2}}{I_{S1}} = I_{ref} \frac{A_{E2}}{A_{E1}}$$

- Output current is the reference current scaled by the emitter area ratios
  - ▣ The current transfer ratio:
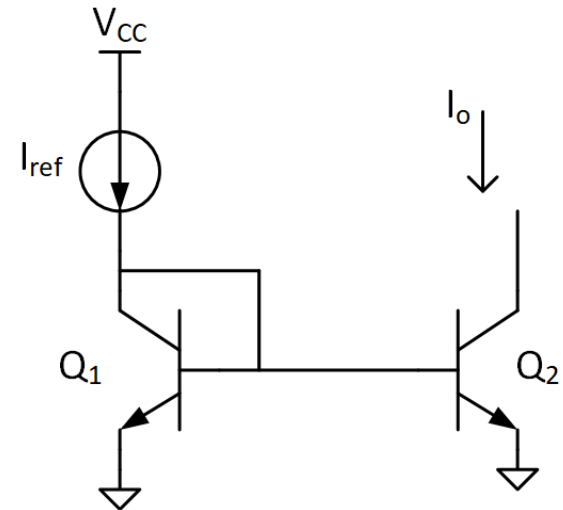
$$\frac{I_o}{I_{ref}} = \frac{A_{E2}}{A_{E1}} = m$$



# Simple BJT Current Mirror

14

- Now, accounting for finite  $\beta$
- Collector currents still scale with emitter area

$$I_o = I_{C_2} = I_{C_1} \frac{A_{E_2}}{A_{E_1}} = m \cdot I_{C_1}$$


- The current transfer ratio:

$$I_{ref} = I_{C_1} + \frac{I_{C_1}}{\beta} + \frac{I_o}{\beta} = \frac{I_o}{m} + \frac{I_o}{m\beta} + \frac{I_o}{\beta}$$

$$I_{ref} = I_o \left( \frac{1}{m} + \frac{1}{m\beta} + \frac{1}{\beta} \right)$$

$$I_{ref} = I_o \left( \frac{\beta + 1 + m}{m\beta} \right)$$
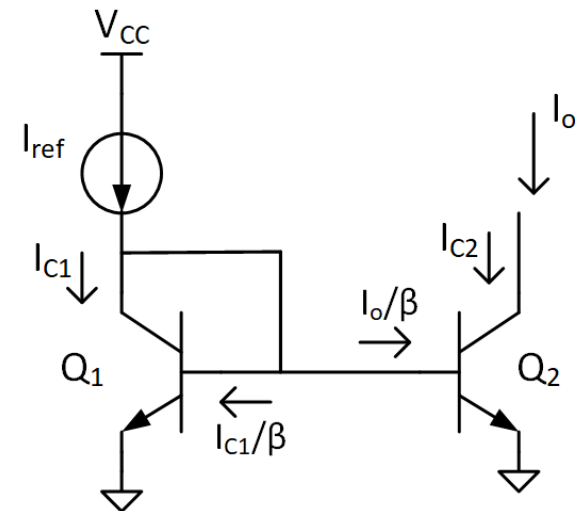
$$\frac{I_o}{I_{ref}} = \frac{m}{1 + \frac{m+1}{\beta}}$$



# BJT Current Mirror With $\beta$ Compensation

15

- Addition of a transistor can reduce the effect of base current on the current transfer ratio
- KCL at the collector of  $Q_1$ :

$$I_{ref} = I_{C1} + I_{B3} = \frac{I_o}{m} + \frac{I_{C3}}{\beta}$$


$$I_{ref} = \frac{I_o}{m} + \frac{\beta}{(\beta + 1)} \frac{I_{E3}}{\beta}$$

where

$$I_{E3} = \frac{I_{C1}}{\beta} + \frac{I_{C2}}{\beta} = \frac{I_o}{m\beta} + \frac{I_o}{\beta}$$

Substituting into the expression for  $I_{ref}$ :
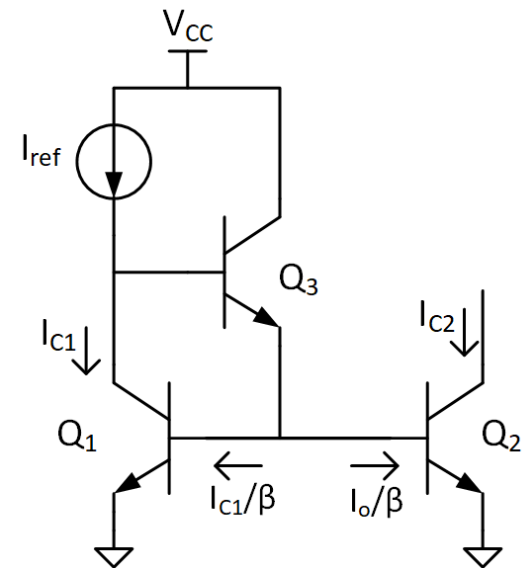
$$I_{ref} = \frac{I_o}{m} + \frac{I_o}{\beta(\beta + 1)} \left( \frac{1}{m} + 1 \right)$$



# BJT Current Mirror With $\beta$ Compensation

16

$$I_{ref} = \frac{I_o}{m} + \frac{I_o}{\beta(\beta + 1)} \left( \frac{1}{m} + 1 \right)$$


$$I_{ref} = I_o \left[ \frac{1}{m} + \frac{m + 1}{m\beta(\beta + 1)} \right]$$

- The current transfer ratio:

$$\frac{I_o}{I_{ref}} = \frac{1}{\frac{1}{m} + \frac{m + 1}{m\beta(\beta + 1)}}$$

$$\frac{I_o}{I_{ref}} = \frac{m}{1 + \frac{m + 1}{\beta(\beta + 1)}}$$

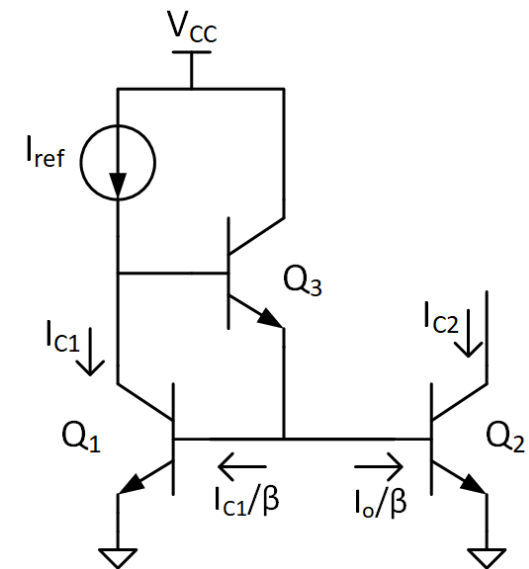- The error term has been improved by a factor of  $(\beta + 1)$







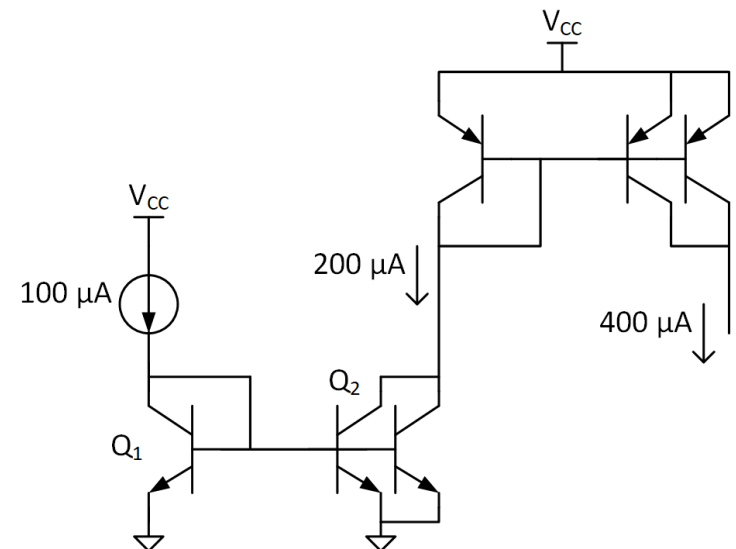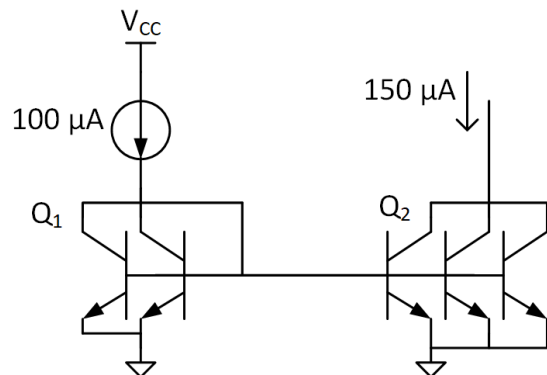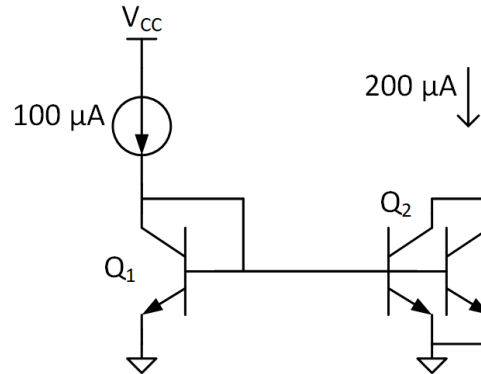
# BJT Current Scaling

17


- For BJTs emitter area scaling is typically accomplished by connecting multiple devices in parallel
  - ▣ For example ( $\beta = \infty$ ):



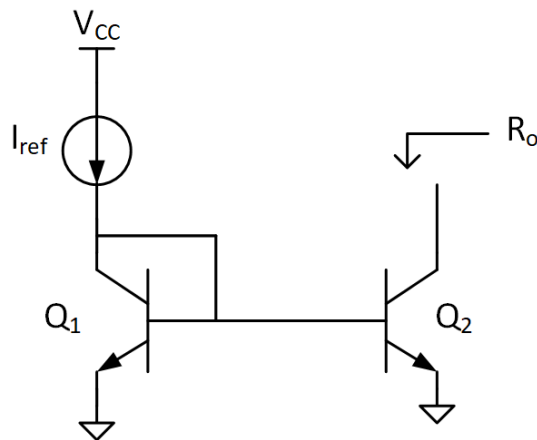
# Current Mirrors – Output Resistance

18

- An important figure of merit for any current source is its output resistance
  - ▣ For an ideal current source,  $R_o = \infty$
- For simple BJT and MOS current mirrors the output resistance is  $r_o$  of the transconductance transistor



$$R_o = r_o = \frac{V_A}{I_C}$$

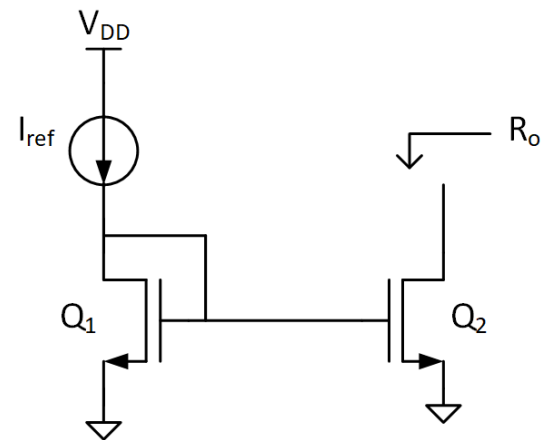

$$R_o = r_o = \frac{1}{\lambda I_D} = \frac{V_A}{I_D}$$

# Current Mirror – Example

19

- Determine the output current,  $I_o$
- Solve the quadratic for  $I_{ref}$ :

$$R^2 I_{ref}^2 - \left[ 2(V_{DD} - V_t)R + \frac{2}{k'_n \left(\frac{W}{L}\right)} \right] I_{ref} + (V_{DD} - V_t)^2 = 0$$

$$(47 \text{ k}\Omega)^2 I_{ref}^2 - \left[ 2(2.6 \text{ V})47 \text{ k}\Omega + \frac{2}{1.9 \frac{\text{mA}}{\text{V}^2}} \right] I_{ref} + (2.6 \text{ V})^2 = 0$$


$$2.248e9 \cdot I_{ref}^2 - 247,593 \cdot I_{ref} + 6.76 = 0$$

$$I_{ref} = 50.4 \mu\text{A}$$

- Output current scales with transistor aspect ratio

$$I_o = I_{ref} \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} = 50.4 \mu\text{A} \cdot \frac{15}{10}$$

$$I_o = 75.6 \mu\text{A}$$

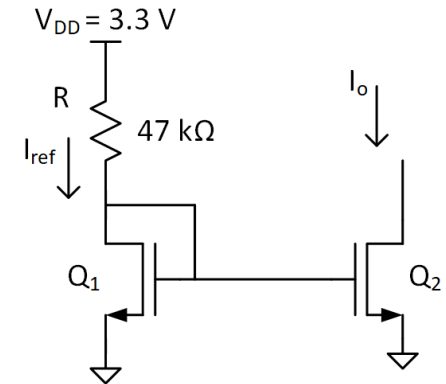

$$\mu_n C_{ox} = 190 \frac{\mu\text{A}}{\text{V}^2}$$

$$V_t = 700 \text{ mV}$$


$$\left(\frac{W}{L}\right)_1 = 10$$

$$\left(\frac{W}{L}\right)_2 = 15$$
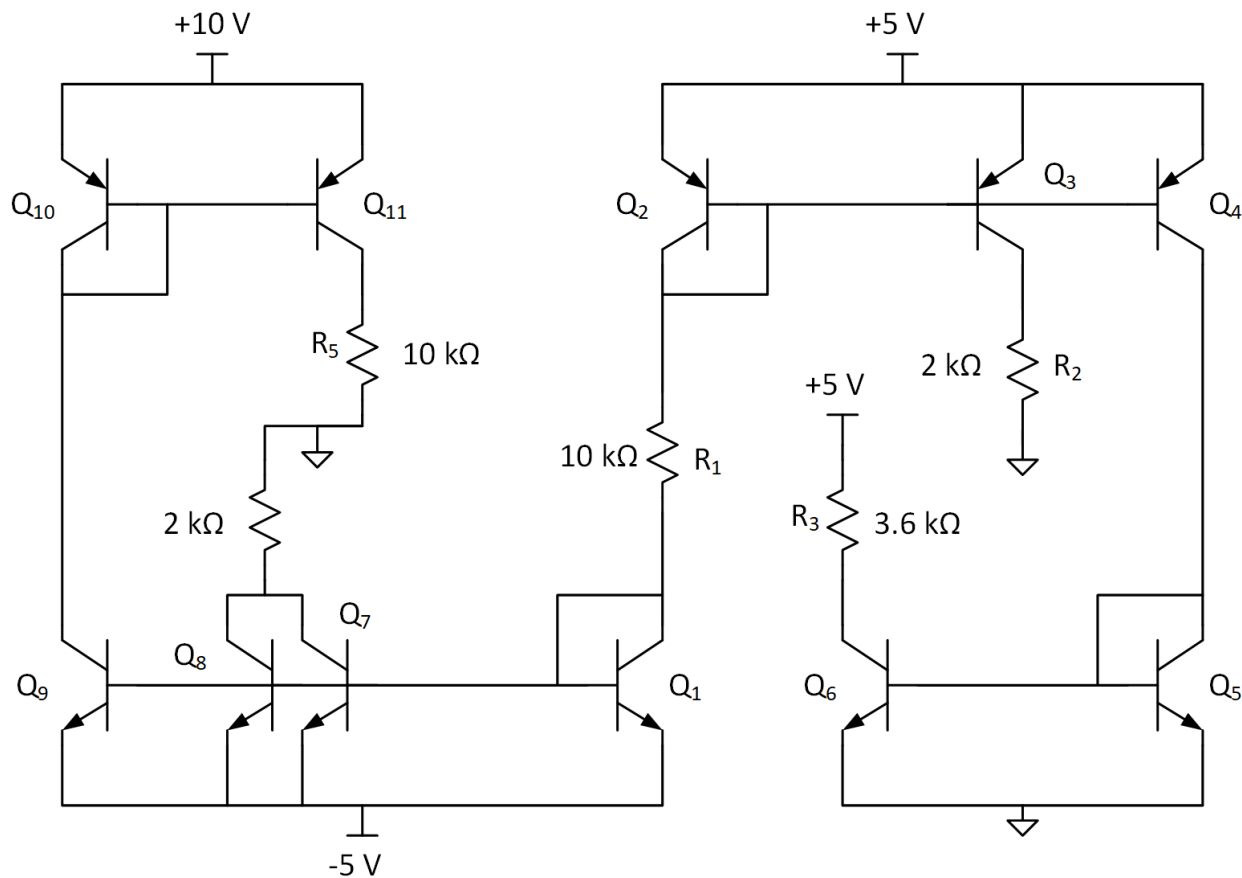
# Current Steering – Example

20

- Determine all collector currents and node voltages
  - ▣ Assume  $\beta = \infty$  and  $V_{BE} = 700\text{ mV}$



# Current Steering – Example

21

$$I_{C1} = I_{C2} = \frac{(+5\text{ V} - V_{BE}) - (-5\text{ V} + V_{BE})}{R_1} = \frac{8.6\text{ V}}{10\text{ k}\Omega} = 860\ \mu\text{A}$$

$$I_{C3} = I_{C2} = 860\ \mu\text{A}$$

$$V_{C3} = I_{C3}R_2 = 860\ \mu\text{A} \cdot 2\text{ k}\Omega = 1.72\text{ V}$$

$$I_{C4} = I_{C3} = 860\ \mu\text{A} = I_{C5} = I_{C6}$$

$$V_{C6} = +5\text{ V} - I_{C6}R_3 = +5\text{ V} - 860\ \mu\text{A} \cdot 3.6\text{ k}\Omega = 1.904\text{ V}$$

$$I_{C7} = I_{C8} = I_{C9} = I_{C1} = 860\ \mu\text{A}$$

$$V_{C7,8} = -(I_{C7} + I_{C8}) \cdot 2\text{ k}\Omega = -1.72\text{ mA} \cdot 2\text{ k}\Omega = -3.44\text{ V}$$

$$I_{C10} = I_{C11} = I_{C9} = 860\ \mu\text{A}$$

$$V_{C11} = I_{C11} \cdot 10\text{ k}\Omega = 860\ \mu\text{A} \cdot 10\text{ k}\Omega = 8.6\text{ V}$$



22

# The Basic Gain Cell
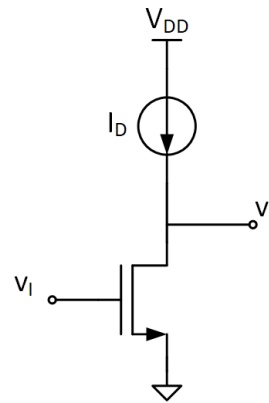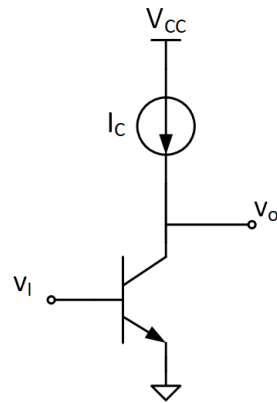
# Basic Gain Cell

23

- The basic gain cell used in integrated circuit (IC) amplifiers
  - ▣ Common-emitter or common-source amplifier
  - ▣ Load resistance replaced with a transistor current source – an **active load**



- Benefits of an active load
  - ▣ Provides both a high-resistance load and bias current
  - ▣ Consumes less chip area than a resistor
  - ▣ Enables higher gain

# Amplifier gain

24

- To understand why active loads can provide high gain, consider a resistively-loaded CS amplifier:
- Amplifier gain:

$$|A_v| = g_m R_D$$

where


$$g_m = k'_n \left( \frac{W}{L} \right) V_{OV}$$

And, since

$$I_D = \frac{1}{2} k'_n \left( \frac{W}{L} \right) V_{OV}^2$$

we can express  $g_m$  as

$$g_m = \frac{I_D}{\frac{1}{2} V_{OV}}$$

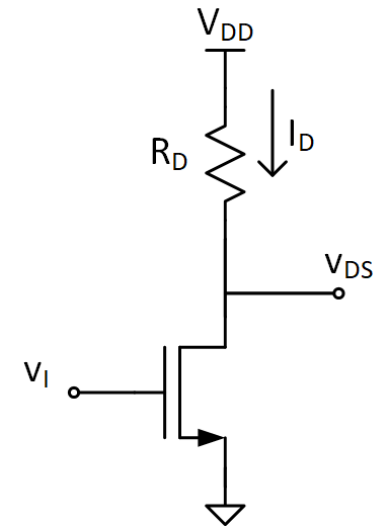



# Amplifier gain

25

- The amplifier gain becomes:


$$|A_v| = g_m R_D = \frac{I_D R_D}{\frac{1}{2} V_{OV}}$$

- The numerator represents the voltage drop across  $R_D$ :

$$|A_v| = \frac{V_{DD} - V_{DS}}{\frac{1}{2} V_{OV}}$$

- For active region operation,  $V_{DS} \geq V_{OV}$ , so the maximum gain is

$$|A_v|_{max} = \frac{V_{DD} - V_{OV}}{\frac{1}{2} V_{OV}}$$

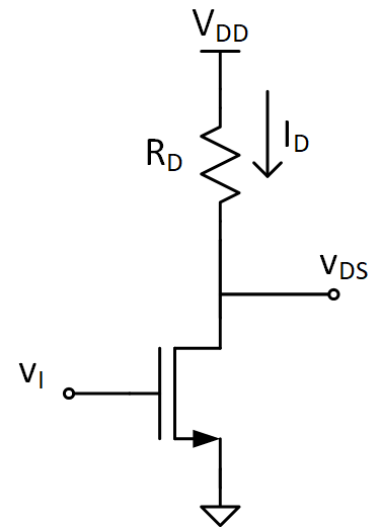


# Amplifier gain

26

- For an IC amplifier with  $V_{DD} = 3.3\text{ V}$  and  $V_{OV} = 200\text{ mV}$  max gain is only


$$|A_v|_{max} = \frac{1.1\text{ V}}{100\text{ mV}} = 11$$

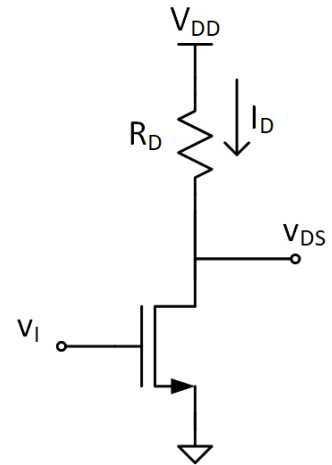- Note that at this bias point (i.e., the edge of triode,  $V_{DS} = V_{OV}$ ), the amplifier's dynamic range is zero
  - ▣ An absolute limit, not a usable gain
- Active loads allow for higher gain, because:
  - ▣ voltage drop across the load is decoupled from current and from high small-signal resistance
  - ▣ They are not resistors, so are not constrained by Ohm's law



# Active Loads and Biasing

27


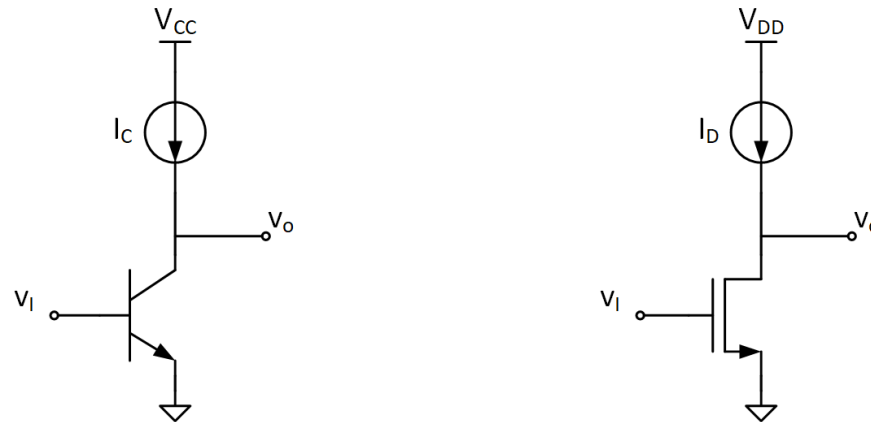


- Note that, in order to remain in the active region,  $I_D$  or  $I_C$  set by  $V_{GS}$  or  $V_{BE}$  must exactly match that of the current-source load
- You are only getting part of the story here
  - In practice, additional circuitry, including negative feedback stabilizes the bias point
- For now, just assume that the DC component of the input is such that its bias current matches the current source
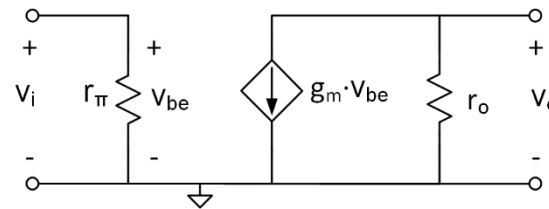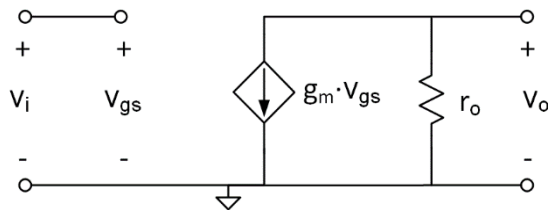
# Basic Gain Cell - Gain

28

- Small-signal models for the amplifiers:



- Treat the current sources as ideal
  - ▣ Infinite resistance – open circuit
  - ▣ In practice it would be a transistor output resistance
- Transistor  $r_o$  is the only load
- For both amplifiers, the gain is

$$A_v = -g_m r_o$$

- This is the maximum possible CS or CE gain
  - ▣ The *intrinsic gain*,  $A_0$

# Intrinsic Gain – MOSFET

29

- For the MOSFET,

$$A_0 = -g_m r_o$$

$$g_m = \frac{I_D}{V_{OV}/2}$$

$$r_o = \frac{V_A}{I_D}$$

- So, the intrinsic gain is

$$A_0 = -\frac{V_A}{V_{OV}/2}$$

- Proportional to the Early voltage
- Inversely proportional to channel length,  $L$
- Inversely proportional to the overdrive voltage,  $V_{OV}$
- Inversely proportional to drain current,  $I_D$

# Intrinsic Gain – BJT

30

$$A_0 = -g_m r_o$$

- For the BJT,

$$g_m = \frac{I_C}{V_t}$$

$$r_o = \frac{V_A}{I_C}$$

- So, the intrinsic gain is

$$A_0 = -\frac{V_A}{V_t}$$



- Proportional to the Early voltage
- Inversely proportional to collector current,  $I_C$
- BJT vs. MOSFETs
  - $V_t$  is much smaller than typical overdrive voltages (e.g. 150 – 300 mV)
  - $V_A$  is typically larger for BJTs
  - In comparable modern processes, BJT intrinsic gain is an order of magnitude higher than that of MOSFETs

# Finite Current-Source Resistance

31

- In practice, active loads are not ideal current sources
  - Transistor current sources
  - Resistance is the  $r_o$  of that transistor
  - Appears in parallel with the amplifier transistor's  $r_o$
  - Gain will be significantly lower than the intrinsic gain

$$A_v = -g_m r_{o1} || r_{o2}$$

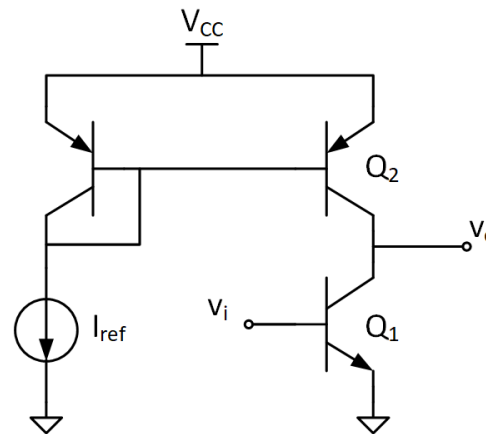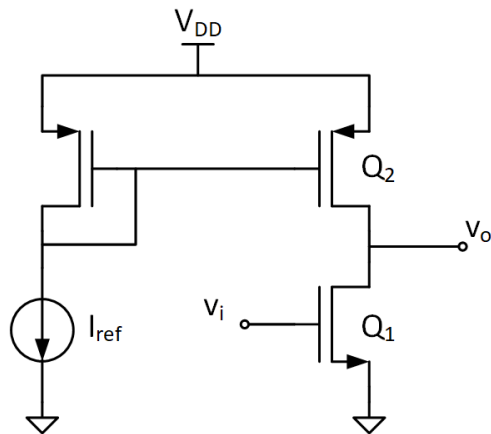

- Next, we'll see how we can increase gain by increasing the output resistance,  $r_{o1} || r_{o2}$

32



# CG/CB Amplifiers as Current Buffers



# Increasing the Gain

33


- If we can increase  $r_{o1} || r_{o2}$ , we can increase gain
- For now, we'll focus on increasing  $r_{o1}$ 
  - I.e., the resistance seen looking back toward the amplifier transistor

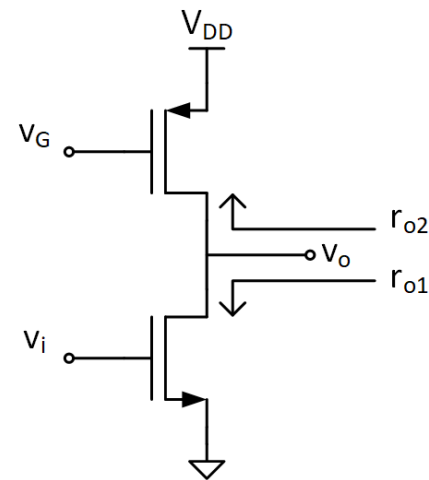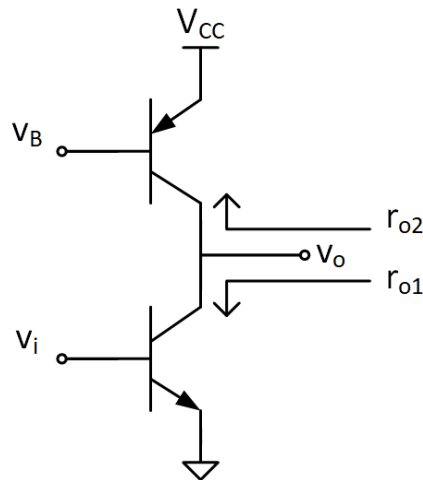
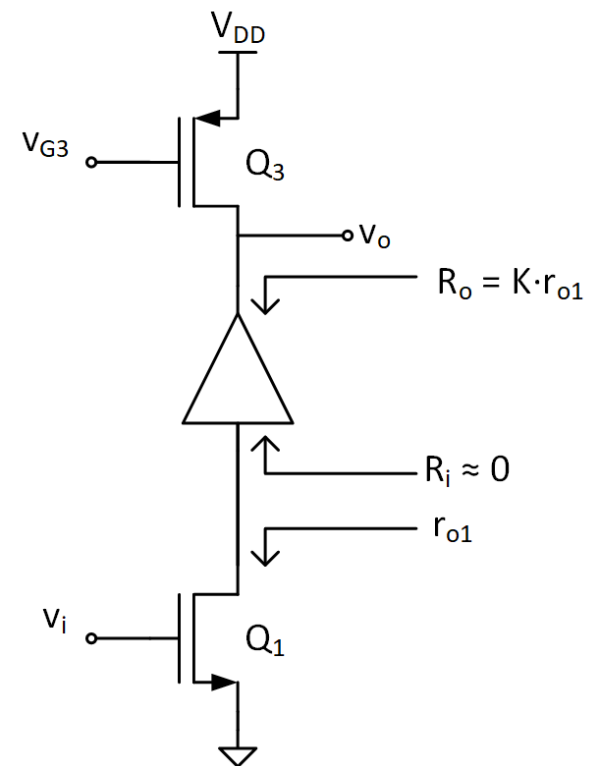
# Current Buffers

34

- The amplifier transistor's output current is applied to the active load transistor, where it is converted to a voltage
- Want a device that will:
  - Replicate that current
  - Apply it to the active load
  - Do so with a higher  $r_o$
- **A *current buffer***
  - Low input resistance
    - Input current unaffected
  - High output resistance
    - Approximating an ideal current source
    - Gain will be increased



# Current Buffers




35

- We have already seen transistor circuits that fit this description of a current buffer
  - ▣ ***Common-base*** amplifier
  - ▣ ***Common-gate*** amplifier
- We now revisit these circuits, looking more closely at the characteristics that make them suitable current buffers:
  - ▣ Current gain
  - ▣ Input resistance
  - ▣ Output resistance
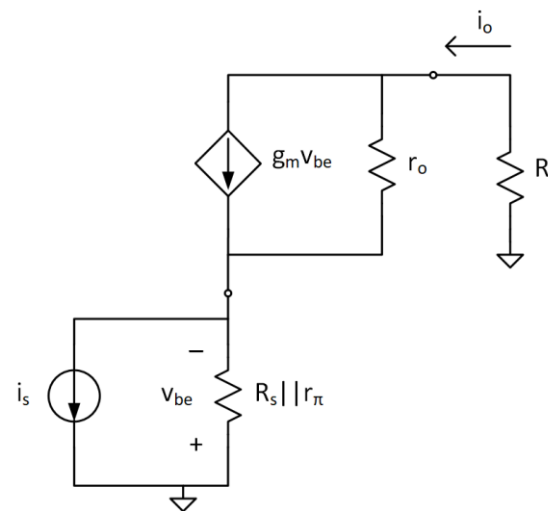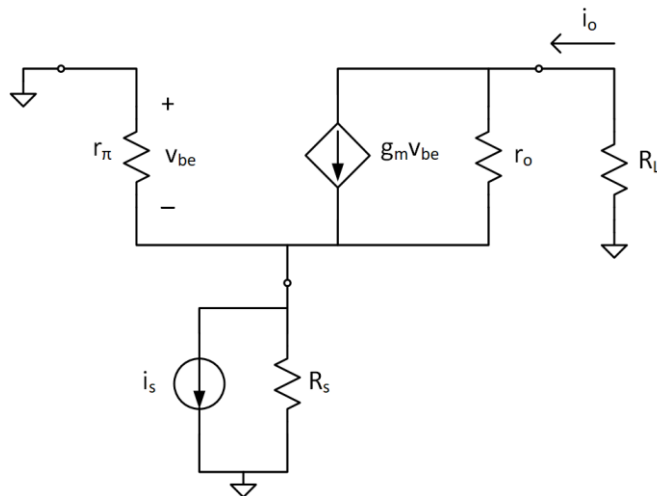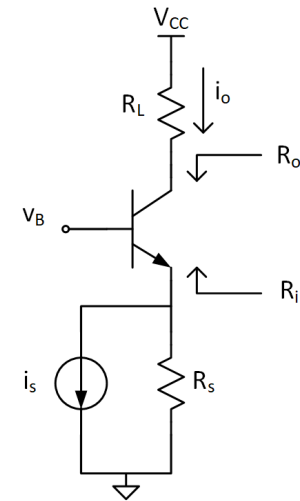
# Common-Base – Small-Signal Circuit

36

- Consider the following CB amplifier
  - ▣ Current source input with finite source resistance,  $R_S$
  - ▣ Load resistance,  $R_L$
- The small-signal equivalent circuit:




# Common-Base – Current Gain

37

- First, we will determine the **short-circuit current gain** for the CB amplifier

$$A_{i_s} = \frac{i_o}{i_s}$$

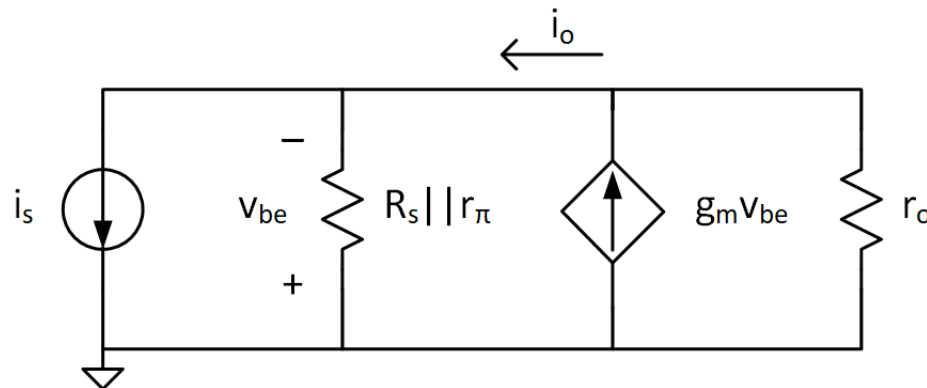
- For the short circuit-current gain, the output is shorted to ground
- The small-signal circuit simplifies to


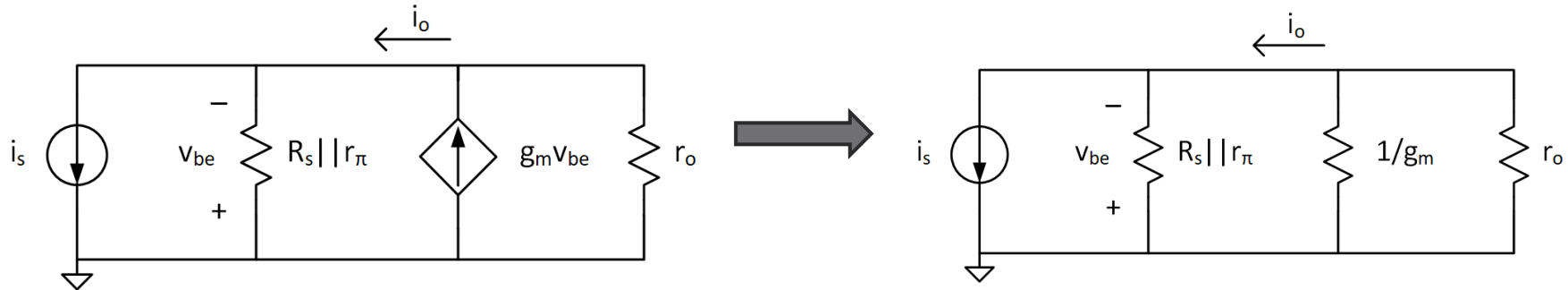
# Common-Base – Current Gain

38

- Note that the voltage across the VCCS is the source's controlling voltage,  $v_{be}$ 
  - ▣ The VCCS, therefore, can be replaced by a resistance:



- Output current is given by current division:

$$i_o = i_s \frac{g_m + \frac{1}{r_o}}{g_m + \frac{1}{r_o} + \frac{1}{R_s || r_\pi}}$$

# Common-Base – Current Gain

39

- The short-circuit current gain is

$$A_{is} = \frac{i_o}{i_s} = \frac{g_m + \frac{1}{r_o}}{g_m + \frac{1}{r_o} + \frac{1}{R_S || r_\pi}}$$

- If  $r_o \gg 1/g_m$  and  $R_S || r_\pi \gg 1/g_m$ , then the current gain is approximately unity

$$A_{is} \approx 1$$

- As would be desired for a current buffer

# Common-Base – Input Resistance

40

- To determine the input resistance, apply a test voltage source,  $v_t$ , and determine the resulting current,  $i_t$
- KVL around the loop:

$$v_t - i_2 r_o - i_c R_L = 0 \quad (1)$$

- KCL at the input node:


$$i_t + g_m v_{be} - i_1 - i_2 = 0$$

$$i_t + g_m v_{be} - \frac{v_t}{r_\pi} - i_2 = 0$$

- Note that  $v_{be} = -v_t$ , so

$$i_t - g_m v_t - \frac{v_t}{r_\pi} - i_2 = 0$$
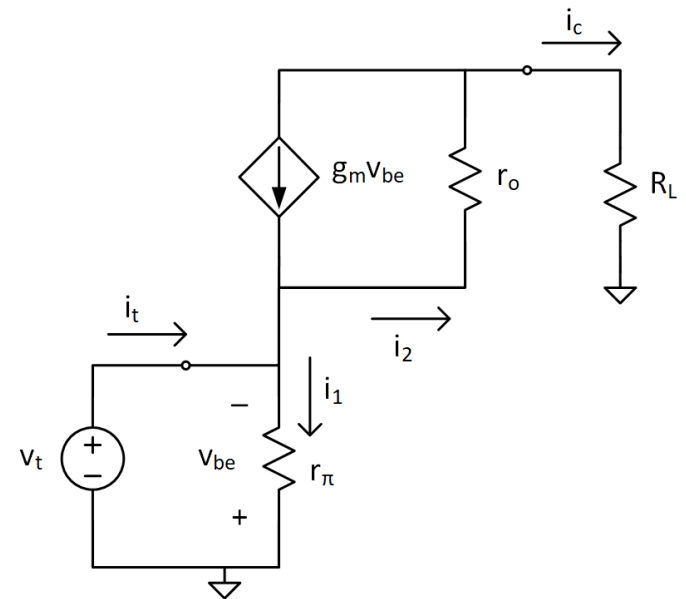
$$i_2 = i_t - g_m v_t - \frac{v_t}{r_\pi} \quad (2)$$





# Common-Base – Input Resistance

41

- KCL at the collector gives the collector current

$$i_c = i_2 - g_m v_{be} = i_2 + g_m v_t$$


$$i_c = i_t - g_m v_t - \frac{v_t}{r_\pi} + g_m v_t$$

$$i_c = i_t - \frac{v_t}{r_\pi} \quad (3)$$

- Substituting (2) and (3) into (1):

$$v_t - i_t r_o + g_m r_o v_t + \frac{v_t}{r_\pi} r_o - i_t R_L + \frac{v_t R_L}{r_\pi} = 0$$
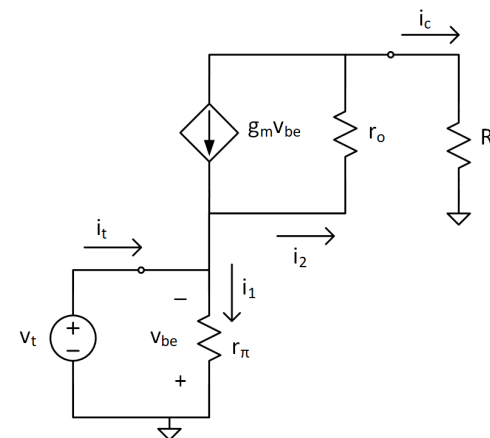
$$v_t \left( 1 + g_m r_o + \frac{r_o}{r_\pi} + \frac{R_L}{r_\pi} \right) = i_t (r_o + R_L) \quad (4)$$



# Common-Base – Input Resistance

42

- The input resistance is

$$R_i = \frac{v_t}{i_t} = \frac{r_o + R_L}{1 + g_m r_o + \frac{r_o}{r_\pi} + \frac{R_L}{r_\pi}} \quad (5)$$

- We can simplify (5) by noting the following


$$g_m r_o \gg 1$$

$$\frac{r_o}{r_\pi} = \frac{g_m r_o}{\beta} \ll g_m r_o$$

$$\frac{R_L}{r_\pi} = \frac{g_m R_L}{\beta} \ll g_m r_o$$

- The input resistance simplifies to
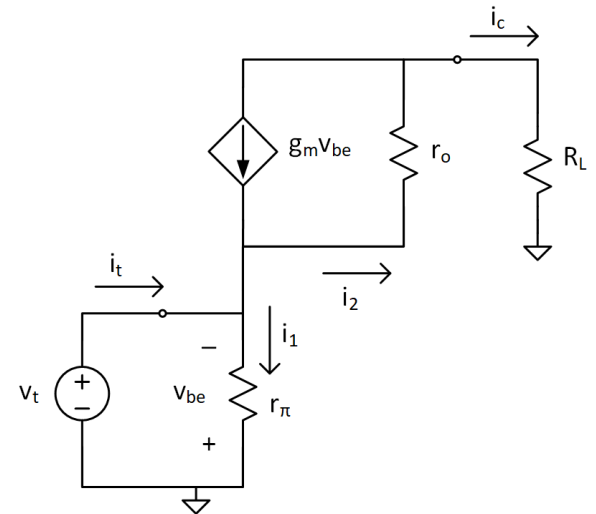
$$R_i \approx \frac{r_o + R_L}{g_m r_o} = \frac{1}{g_m} + \frac{R_L}{g_m r_o} = r_e + \frac{R_L}{g_m r_o} \quad (6)$$



# Common-Base – Input Resistance


43

- Common-base input resistance:

$$R_i \approx \frac{1}{g_m} + \frac{R_L}{g_m r_o} = r_e + \frac{R_L}{g_m r_o}$$

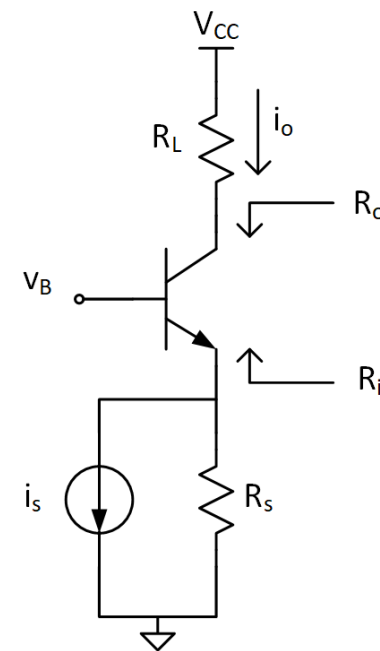(6)

- Two components to  $R_i$ :
  - ▣ Emitter resistance,  $r_e$ 
    - Typically small
  - ▣ Load resistance,  $R_L$ , **reduced by the transistor's intrinsic gain**
    - Effect of  $R_L$  reduced
- $R_i$  is typically small, as desired from a current buffer



# Common-Base – Output Resistance

44

- To determine output resistance,  $R_o$ , apply a test voltage to the output
- Applying KVL

$$v_t - i_1 r_o - i_2 (R_E || r_\pi) = 0 \quad (7)$$

- Applying KCL gives

$$i_1 = i_t - g_m v_{be} \quad (8)$$


$$i_2 = i_1 + g_m v_{be} = i_t \quad (9)$$

- The base-emitter voltage is

$$v_{be} = -i_2 (R_E || r_\pi) = -i_t (R_E || r_\pi) \quad (10)$$

- Substituting (8), (9), and (10) into (7) gives

$$v_t - i_t r_o - g_m i_t (R_E || r_\pi) r_o - i_t (R_E || r_\pi) = 0 \quad (11)$$

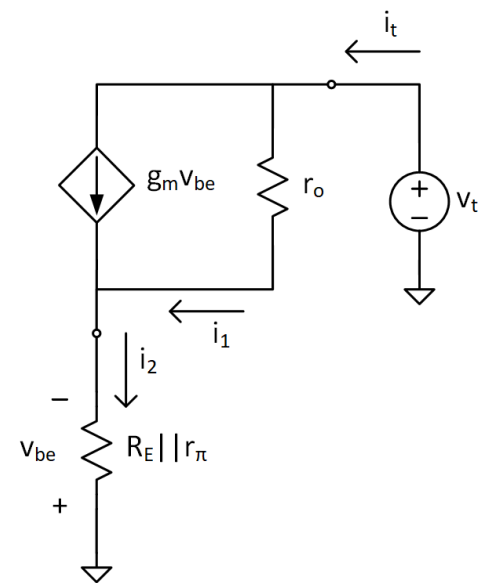

# Common-Base – Output Resistance

45

- Rearranging (11) gives the output resistance

$$R_o = \frac{v_t}{i_t} = r_o + (R_E || r_\pi) + g_m r_o (R_E || r_\pi)$$

$$R_o = r_o + (1 + g_m r_o)(R_E || r_\pi)$$


- We can simplify, assuming  $g_m r_o \gg 1$

$$R_o \approx r_o + g_m r_o (R_E || r_\pi)$$

- And, if  $g_m (R_E || r_\pi) \gg 1$ , then

$$R_o \approx g_m r_o (R_E || r_\pi)$$


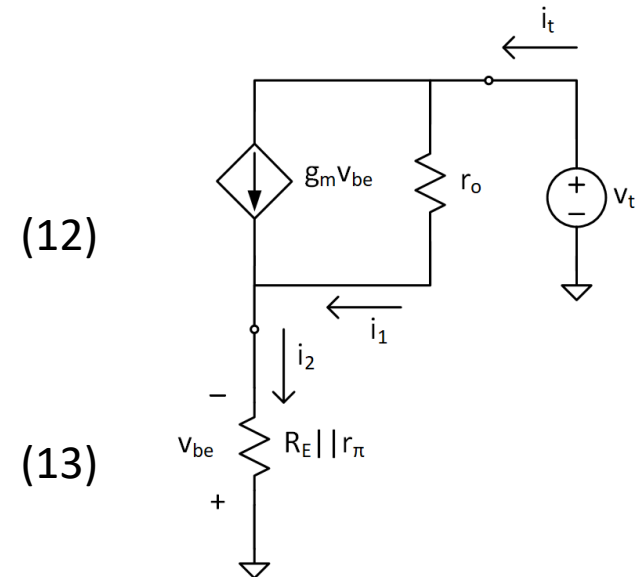
- Here, the resistance at the input is **increased by the transistor's intrinsic gain**
- $R_o$  will typically be a large resistance, as would be desired


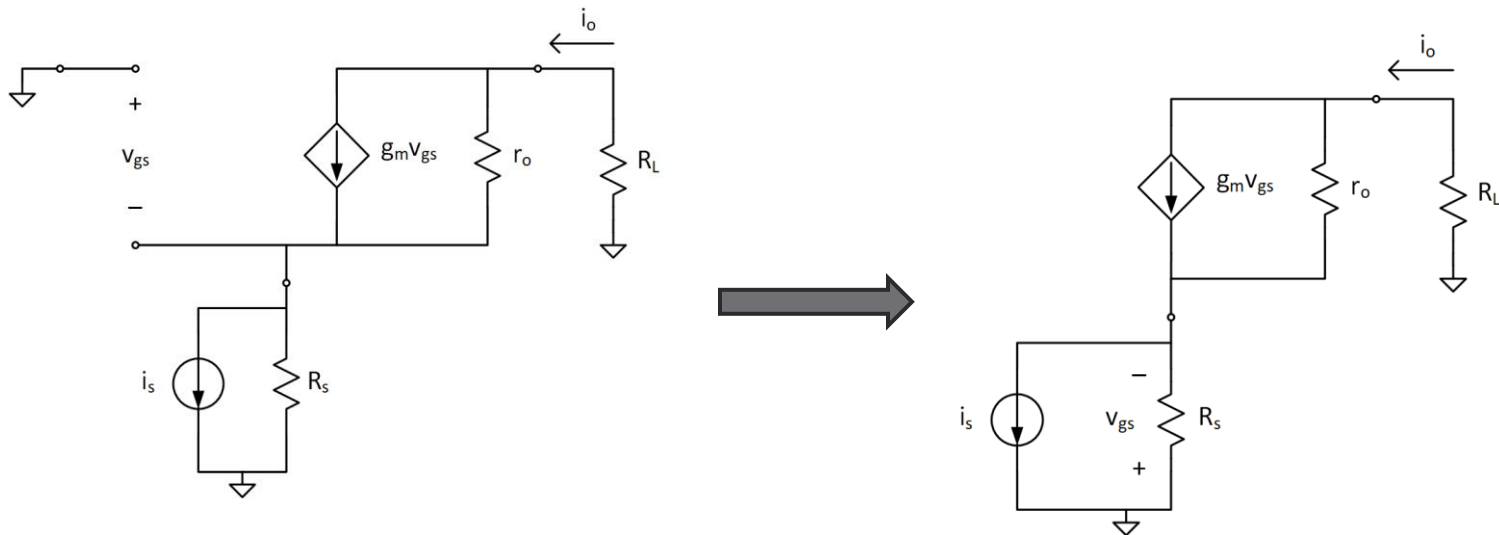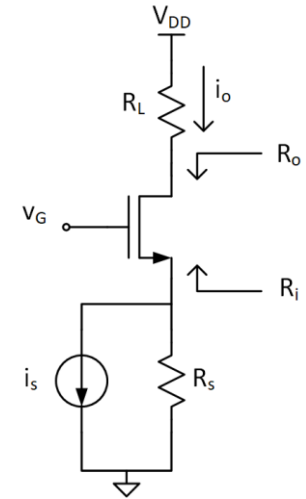
# Common-Gate – Small-Signal Circuit

46


- Consider the following CG amplifier
  - ▣ Current source input with finite source resistance,  $R_S$
  - ▣ Load resistance,  $R_L$
- The small-signal equivalent circuit:


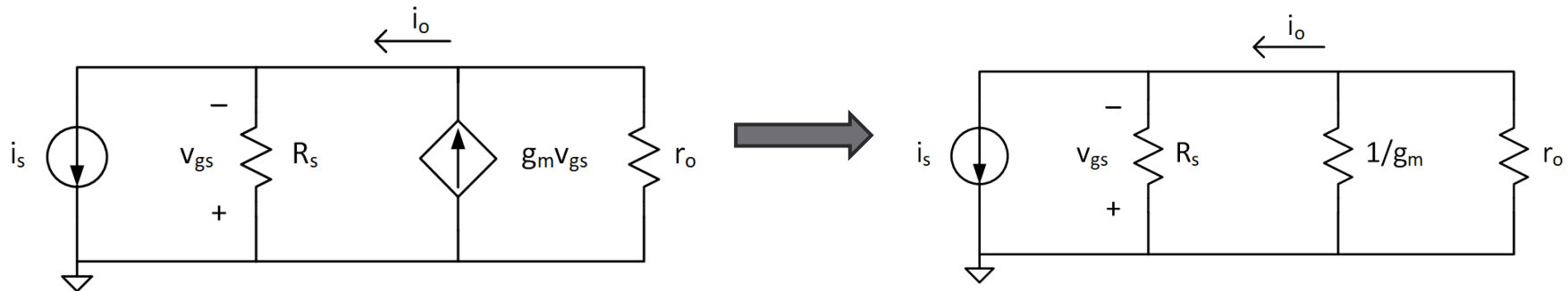
# Common-Gate – Current Gain

47

- To determine short-circuit current gain,  $A_{i_s}$ , we can simplify the small-signal circuit just as we did for the CB circuit:



- Output current is given by current division:

$$i_o = i_s \frac{g_m + \frac{1}{r_o}}{g_m + \frac{1}{r_o} + \frac{1}{R_s}}$$

# Common-Gate – Current Gain

48

- The short-circuit current gain is

$$A_{is} = \frac{i_o}{i_s} = \frac{g_m + \frac{1}{r_o}}{g_m + \frac{1}{r_o} + \frac{1}{R_S}}$$

- If  $r_o \gg 1/g_m$  and  $R_S \gg 1/g_m$ , then the current gain is approximately unity

$$A_{is} \approx 1$$

- As desired, and similar to the CB amplifier



# Common-Gate – Input Resistance

49

- To determine the input resistance, apply a test voltage source,  $v_t$ , and determine the resulting current,  $i_t$

- KVL around the loop:

$$v_t - i_1 r_o - i_d R_L = 0 \quad (14)$$

- KCL at the input node:

$$i_1 = i_t + g_m v_{gs} = 0$$


- Note that  $v_t = -v_{gs}$ , so

$$i_1 = i_t - g_m v_t \quad (15)$$

- Substituting (15) into (14) and noting that drain and source currents are equal

$$v_t - i_t r_o + g_m r_o v_t - i_t R_L = 0$$
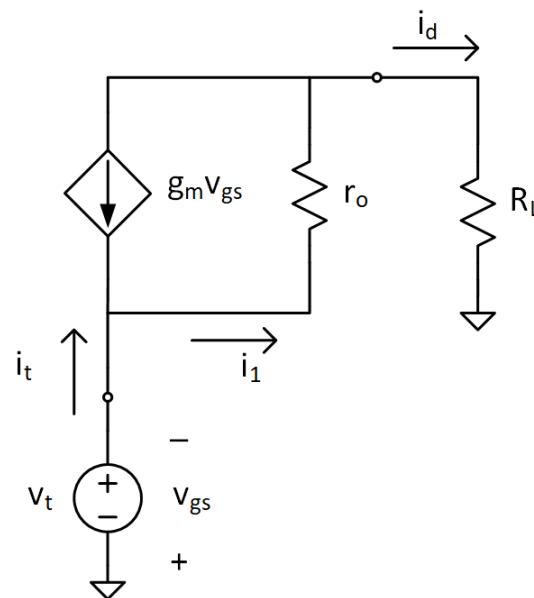
$$v_t(1 + g_m r_o) = i_t(r_o + R_L) \quad (16)$$



# Common-Gate – Input Resistance

50


- Solving (16) gives the input resistance:

$$R_i = \frac{v_t}{i_t} = \frac{r_o + R_L}{1 + g_m r_o} \quad (17)$$

- For  $g_m r_o \gg 1$ ,  $R_i$  simplifies to

$$R_i \approx \frac{1}{g_m} + \frac{R_L}{g_m r_o} \quad (18)$$

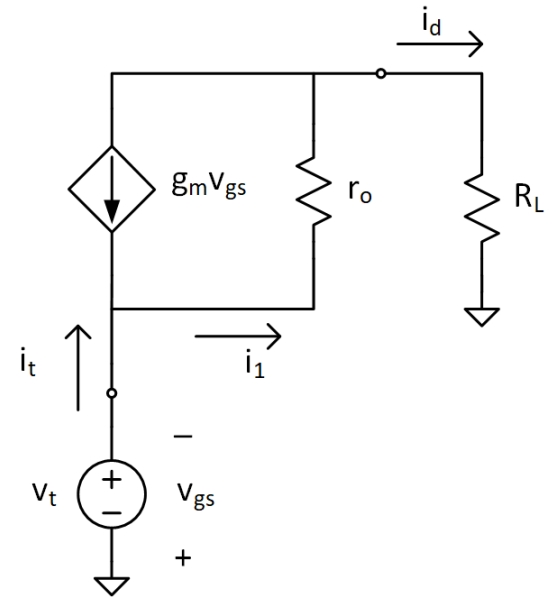- Two components to  $R_i$ 
  - ▣ The input resistance when neglecting  $r_o$
  - ▣ The load resistance **reduced by the intrinsic gain**



# Common-Gate – Output Resistance

51

- To determine output resistance,  $R_o$ , apply a test voltage to the output
- Applying KVL

$$v_t - i_1 r_o - i_s R_S = 0 \quad (19)$$

- Applying KCL gives


$$i_1 = i_t - g_m v_{gs} \quad (20)$$

- The gate-source voltage is

$$v_{gs} = -i_s R_S = -i_t R_S \quad (21)$$

- Substituting (20) and (21) into (19) gives
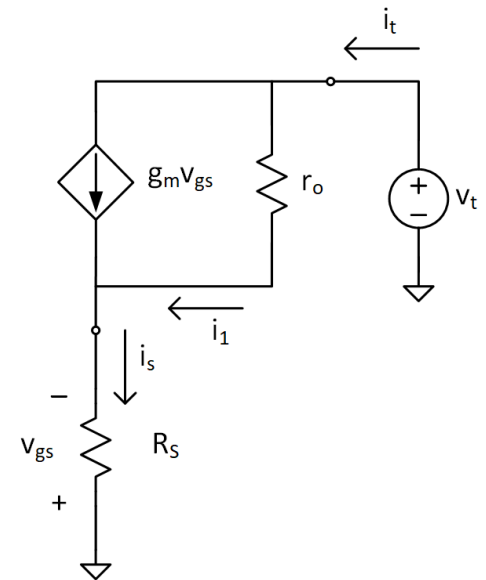
$$v_t - i_t r_o - g_m i_t R_S r_o - i_t R_S = 0 \quad (22)$$



# Common-Gate – Output Resistance

52

- Rearranging (22) gives the output resistance

$$R_o = \frac{v_t}{i_t} = r_o + R_S + g_m r_o R_S$$

$$R_o = r_o + (1 + g_m r_o) R_S$$


- We can simplify, assuming  $g_m r_o \gg 1$

$$R_o \approx r_o + g_m r_o R_S$$

- If we assume  $g_m r_o \gg 1$ , we can simplify further

$$R_o \approx g_m r_o R_S$$

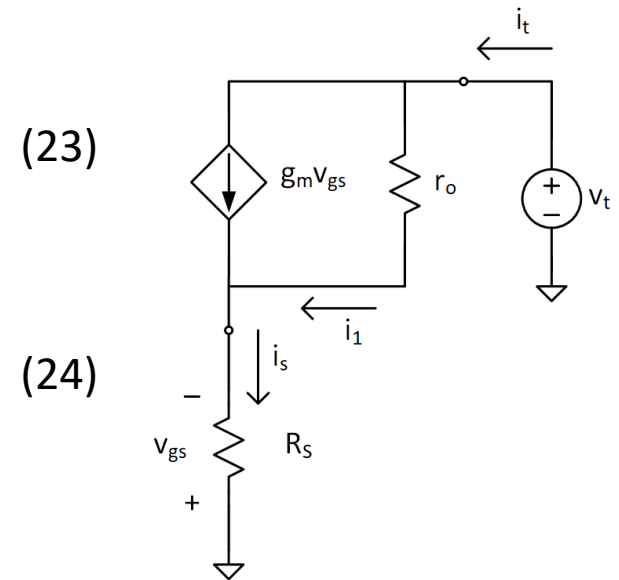- Here, the resistance at the input is **increased by the transistor's intrinsic gain**
- $R_o$  will typically be a relatively large resistance



# Common-Base/Common-Gate - Summary

53

$$A_{is} = \frac{g_m + \frac{1}{r_o}}{g_m + \frac{1}{r_o} + \frac{1}{R_S || r_{\pi}}} \approx 1$$


$$R_i = \frac{r_o + R_L}{1 + g_m r_o + \frac{r_o}{r_{\pi}} + \frac{R_L}{r_{\pi}}}$$

$$R_i \approx \frac{1}{g_m} + \frac{R_L}{g_m r_o} = r_e + \frac{R_L}{g_m r_o}$$

$$R_o = r_o + (1 + g_m r_o)(R_E || r_{\pi})$$

$$R_o \approx r_o + g_m r_o (R_E || r_{\pi})$$

$$R_o \approx g_m r_o (R_E || r_{\pi})$$

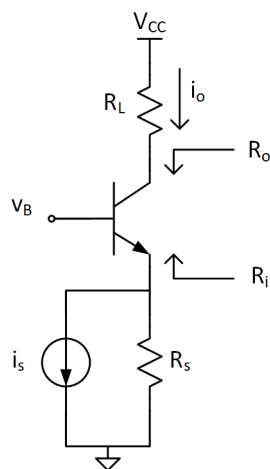

$$A_{is} = \frac{g_m + \frac{1}{r_o}}{g_m + \frac{1}{r_o} + \frac{1}{R_S}} \approx 1$$


$$R_i = \frac{r_o + R_L}{1 + g_m r_o}$$

$$R_i \approx \frac{1}{g_m} + \frac{R_L}{g_m r_o}$$

$$R_o = r_o + (1 + g_m r_o)R_S$$

$$R_o \approx r_o + g_m r_o R_S$$

$$R_o \approx g_m r_o R_S$$

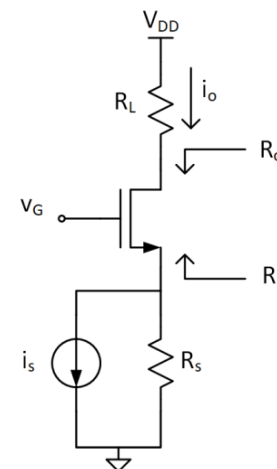

54

# Cascode Amplifiers

# Cascode Amplifier – MOSFET

55

- Recall the gain of a basic gain cell with an active load

$$A_v = -g_{m1}R_o = -g_{m1}(r_{o1}||r_{o2})$$

- We can increase this gain by increasing  $r_{o1}$  or  $r_{o2}$
- First, we'll focus on  $r_{o1}$  by adding a **cascode** device
- Now,  $R_o$  becomes

$$R_o = R_{on}||R_{op} = R_{on}||r_{o3}$$

where


$$R_{on} = g_{m2}r_{o2}(r_{o1})$$

- The gain is then

$$A_v = -g_{m1}(R_{on}||r_{o3})$$

$$A_v = -g_{m1}[(g_{m2}r_{o2}r_{o1})||r_{o3}]$$

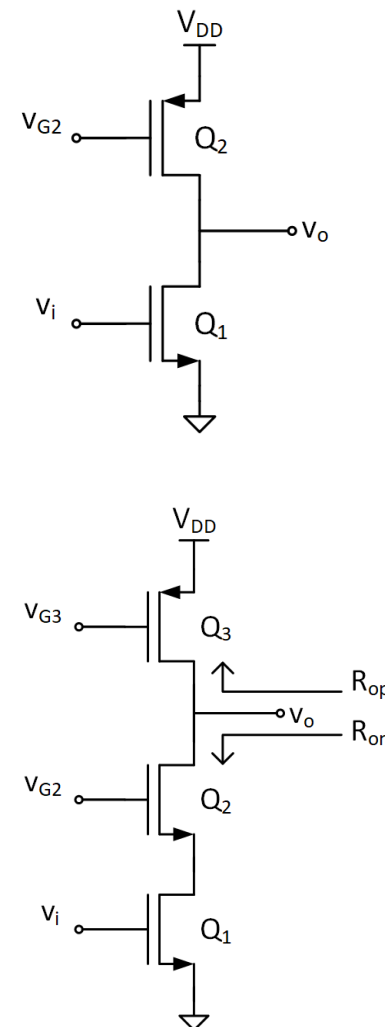- $r_{o1}$  has been increased by a factor of  $g_{m2}r_{o2}$ 
  - ▣ Gain is increased significantly



# Cascode Amplifier – BJT

56

- For the BJT cascode,  $R_{on}$  is



$$R_{on} = g_{m2}r_{o2}(r_{o1}||r_{\pi2})$$

- And the gain is

$$A_v = -g_{m1}(R_{on}||r_{o3})$$

$$A_v = -g_{m1}[(g_{m2}r_{o2}(r_{o1}||r_{\pi2}))||r_{o3}]$$

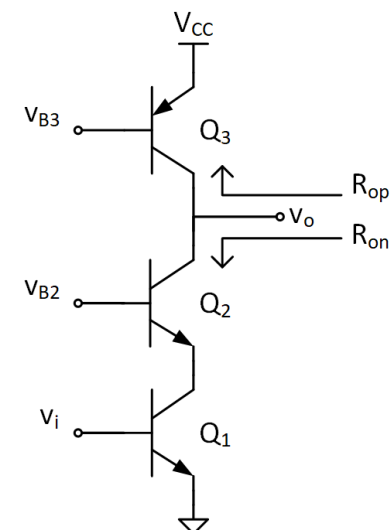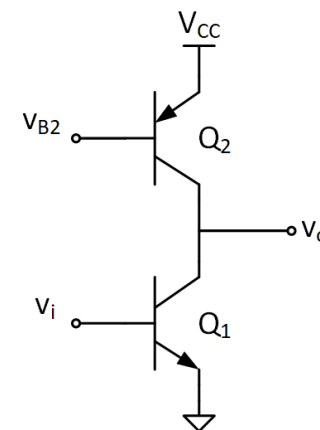- A bit more complicated result than for the MOS circuit
  - ▣ Gain still significantly increased
- Note that in both cases, we have only improved one component of  $R_o$ 
  - ▣ We can further increase gain by increasing  $r_{o3}$  as well





# Cascode Current Source – MOSFET

57

- We can further increase  $R_o$  and gain by adding a cascode device to the active load transistor

- ▣ Increases  $r_{o3}$  and  $R_{op}$

- Now,  $R_{op}$  is


$$R_{op} = g_{m3}r_{o3}(r_{o4})$$

- The gain is

$$A_v = -g_{m1}(R_{on} || R_{op})$$

$$A_v = -g_{m1}[(g_{m2}r_{o2}r_{o1}) || (g_{m3}r_{o3}r_{o4})]$$

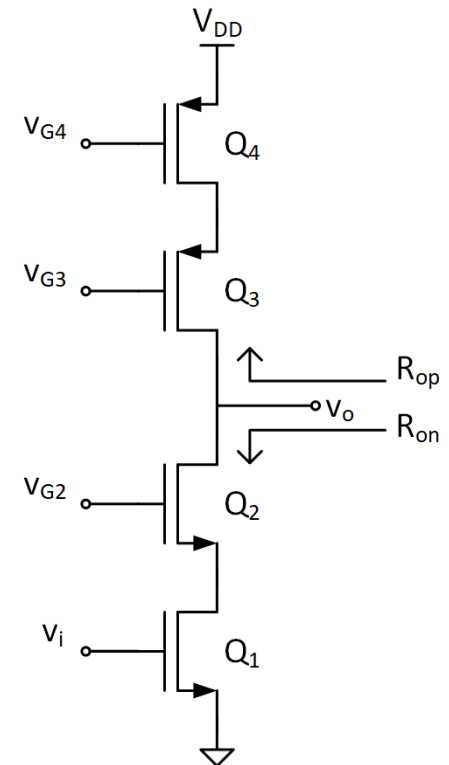- Now  $r_{o4}$  has been increased by a factor of  $g_{m3}r_{o3}$ 
  - ▣ Another significant gain increase



# Cascode Current Source – BJT

58

- For the BJT cascode amplifier, the cascode device on the active load increases  $R_{op}$  similarly


$$R_{op} = g_{m3}r_{o3}(r_{o4}||r_{\pi3})$$

- The gain is

$$A_v = -g_{m1}(R_{on}||R_{op})$$

$$A_v = -g_{m1}\{[g_{m2}r_{o2}(r_{o1}||r_{\pi2})]||[g_{m3}r_{o3}(r_{o4}||r_{\pi3})]\}$$

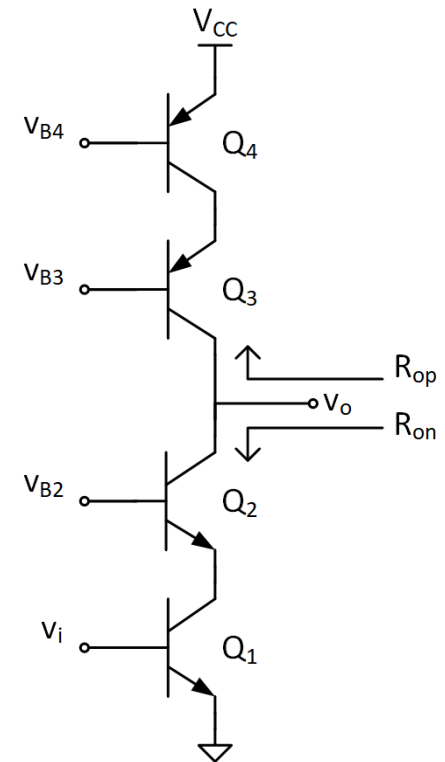- Again, the result is a bit more complicated than for the MOS circuit
  - ▣ Resulting increase of gain is similar



# Cascode Amplifier – Example 1

59

- Find the gain of the basic gain cell in a  $0.18 \mu\text{m}$  CMOS process with the given parameters
- Gain is given by


$$A_v = -g_{m1}R_o = -g_{m1}r_{o1}||r_{o2}$$

- The transistor transconductances:

$$g_{m1} = \sqrt{2k'_n \left(\frac{W}{L}\right)_n I_D}$$

$$g_{m1} = \sqrt{2 \cdot 387 \frac{\mu\text{A}}{\text{V}^2} \cdot 10 \cdot 100 \mu\text{A}}$$

$$g_{m1} = 880 \mu\text{S}$$

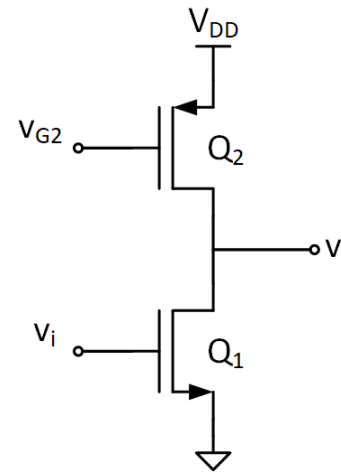

$$I_D = 100 \mu\text{A}$$

$$\mu_n C_{ox} = 387 \frac{\mu\text{A}}{\text{V}^2}$$

$$\mu_p C_{ox} = 86 \frac{\mu\text{A}}{\text{V}^2}$$

$$\left(\frac{W}{L}\right)_n = \frac{10 \mu\text{m}}{1 \mu\text{m}}$$

$$\left(\frac{W}{L}\right)_p = \frac{50 \mu\text{m}}{1 \mu\text{m}}$$

$$V_{An} = 5 \text{ V}$$

$$V_{Ap} = 6 \text{ V}$$

# Cascode Amplifier – Example 1

60

- The transistor output resistances:

$$r_{o1} = \frac{V_{An}}{I_D} = \frac{5 \text{ V}}{100 \mu\text{A}} = 50 \text{ k}\Omega$$

$$r_{o2} = \frac{V_{Ap}}{I_D} = \frac{6 \text{ V}}{100 \mu\text{A}} = 60 \text{ k}\Omega$$


- The gain:

$$A_v = -g_{m1} r_{o1} || r_{o2}$$

$$A_v = -880 \mu\text{S} \cdot 50 \text{ k}\Omega || 60 \text{ k}\Omega$$

$$A_v = -880 \mu\text{S} \cdot 27.3 \text{ k}\Omega$$

$$A_v = -24$$

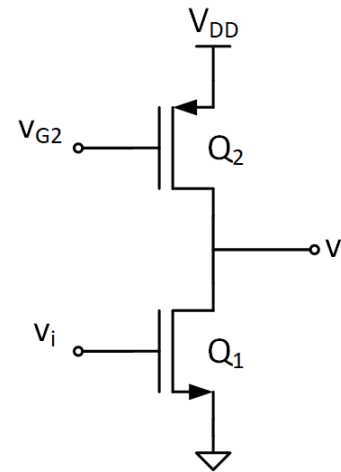

$$I_D = 100 \mu\text{A}$$

$$\mu_n C_{ox} = 387 \frac{\mu\text{A}}{\text{V}^2}$$

$$\mu_p C_{ox} = 86 \frac{\mu\text{A}}{\text{V}^2}$$

$$\left(\frac{W}{L}\right)_n = \frac{10 \mu\text{m}}{1 \mu\text{m}}$$

$$\left(\frac{W}{L}\right)_p = \frac{50 \mu\text{m}}{1 \mu\text{m}}$$

$$V_{An} = 5 \text{ V}$$

$$V_{Ap} = 6 \text{ V}$$

# Cascode Amplifier – Example 2

61

- Next, add a cascode device and determine the resulting gain
- Now, the gain is given by

$$A_v = -g_{m1}R_o = -g_{m1}R_{on} || r_{o3}$$


- Transconductance of the NMOS devices is unchanged:

$$g_{m1} = g_{m2} = 880 \mu S$$

- As are all output resistances

$$r_{o1} = r_{o2} = 50 k\Omega$$

$$r_{o3} = 60 k\Omega$$

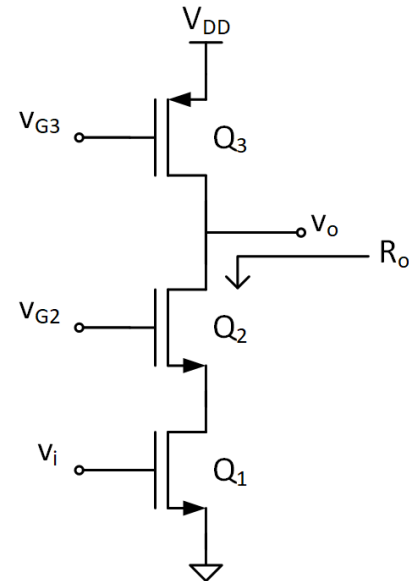

$$I_D = 100 \mu A$$

$$\mu_n C_{ox} = 387 \frac{\mu A}{V^2}$$

$$\mu_p C_{ox} = 86 \frac{\mu A}{V^2}$$

$$\left(\frac{W}{L}\right)_n = \frac{10 \mu m}{1 \mu m}$$

$$\left(\frac{W}{L}\right)_p = \frac{50 \mu m}{1 \mu m}$$

$$V_{An} = 5 V$$

$$V_{Ap} = 6 V$$

# Cascode Amplifier – Example 2

62

- The resistance looking into the drain of  $Q_2$  is

$$R_{on} = g_{m2}r_{o2} \cdot r_{o1}$$

$$R_{on} = 880 \mu S \cdot 50 k\Omega \cdot 50 k\Omega$$

$$R_{on} = 44 \cdot 50 k\Omega = 2.2 M\Omega$$


- The gain:

$$A_v = -g_{m1}R_{on} || r_{o3}$$

$$A_v = -880 \mu S \cdot 2.2 M\Omega || 60 k\Omega$$

$$A_v = -880 \mu S \cdot 58.4 k\Omega$$

$$A_v = -51.4$$

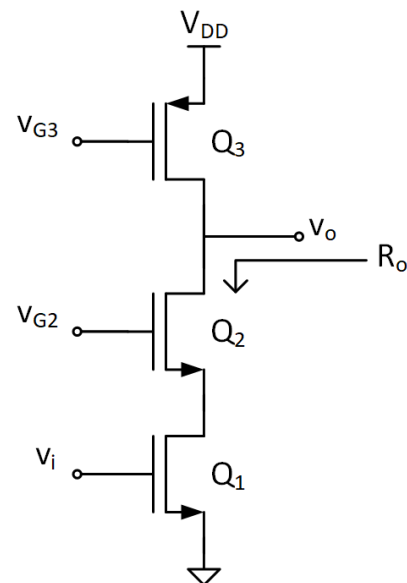

$$I_D = 100 \mu A$$

$$\mu_n C_{ox} = 387 \frac{\mu A}{V^2}$$

$$\mu_p C_{ox} = 86 \frac{\mu A}{V^2}$$

$$\left(\frac{W}{L}\right)_n = \frac{10 \mu m}{1 \mu m}$$

$$\left(\frac{W}{L}\right)_p = \frac{50 \mu m}{1 \mu m}$$

$$V_{An} = 5 V$$

$$V_{Ap} = 6 V$$

- The cascode transistor increased the gain from 24 to 51.4
  - A relatively small increase compared to the 44x increase in  $R_{on}$
  - $R_o$  dominated by  $r_{o3}$

# Cascode Amplifier – Example 3

63

- Finally, add a cascode device to the current-source load and determine the gain

- Now, the gain is given by

$$A_v = -g_{m1}R_o = -g_{m1}R_{on} || R_{op}$$


- Transconductance of the PMOS devices:

$$g_{m3} = g_{m4} = \sqrt{2k'_p \left(\frac{W}{L}\right)_p I_D}$$

$$g_{m3} = \sqrt{2 \cdot 86 \frac{\mu A}{V^2} \cdot 50 \cdot 100 \mu A}$$

$$g_{m3} = 927 \mu S$$

- All other quantities are the same

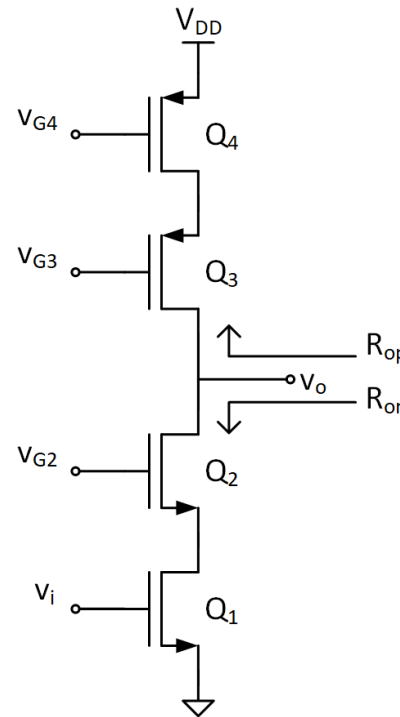

$$I_D = 100 \mu A$$

$$\mu_n C_{ox} = 387 \frac{\mu A}{V^2}$$

$$\mu_p C_{ox} = 86 \frac{\mu A}{V^2}$$

$$\left(\frac{W}{L}\right)_n = \frac{10 \mu m}{1 \mu m}$$

$$\left(\frac{W}{L}\right)_p = \frac{50 \mu m}{1 \mu m}$$

$$V_{An} = 5 V$$

$$V_{Ap} = 6 V$$

# Cascode Amplifier – Example 3

64

- The resistance looking into the drain of  $Q_3$  is

$$R_{op} = g_{m3}r_{o3} \cdot r_{o4}$$

$$R_{op} = 927 \mu S \cdot 60 k\Omega \cdot 60 k\Omega$$

$$R_{op} = 55.6 \cdot 60 k\Omega = 3.34 M\Omega$$


- The gain:

$$A_v = -g_{m1}R_{on} || R_{op}$$

$$A_v = -880 \mu S \cdot 2.2 M\Omega || 3.34 M\Omega$$

$$A_v = -880 \mu S \cdot 1.33 M\Omega$$

$$A_v = -1167$$

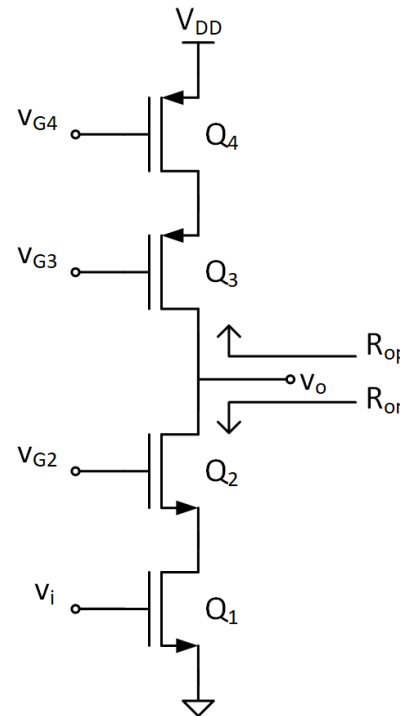

$$I_D = 100 \mu A$$

$$\mu_n C_{ox} = 387 \frac{\mu A}{V^2}$$

$$\mu_p C_{ox} = 86 \frac{\mu A}{V^2}$$

$$\left(\frac{W}{L}\right)_n = \frac{10 \mu m}{1 \mu m}$$

$$\left(\frac{W}{L}\right)_p = \frac{50 \mu m}{1 \mu m}$$

$$V_{An} = 5 V$$

$$V_{Ap} = 6 V$$

- Cascode current-source load results in a significant gain increase
  - ▣ Both components of  $R_o$  were increased by a factor of  $g_m r_o$



65

# Improved Current Mirrors

# Current Mirror Performance

66

- There are three main current-mirror figures of merit:
- ***Current transfer ratio***
  - How closely does the output current match the input/reference current?
  - A function of the Early effect and of  $\beta$  (BJTs)
- ***Output resistance***
  - Enables higher amplifier gain if used as an active load
  - Also affects current transfer ratio
    - How much is output current affected by output voltage?
- ***Overhead voltage***
  - What is the minimum voltage required at the output such that the transistors remain in the active region?
- We will now look at a few circuits that aim to improve on one or more of these characteristics

# Cascode Current Mirror – MOSFET

67

- As we have seen, a cascode device can improve output resistance
- A MOSFET cascode current mirror:
  - Assume matched devices (i.e.,  $m = 1$ )
- Output resistance:

$$R_o = g_{m3}r_{o3} \cdot r_{o2}$$

- Voltage at the gate of  $Q_3/Q_4$ :

$$V_{G3} = 2(V_t + V_{OV})$$


- To remain in the active region:

$$V_{D3} > V_t + 2V_{OV}$$

- If, for example,  $V_t = 500 \text{ mV}$  and  $V_{OV} = 200 \text{ mV}$

$$V_{D3} > 900 \text{ mV}$$

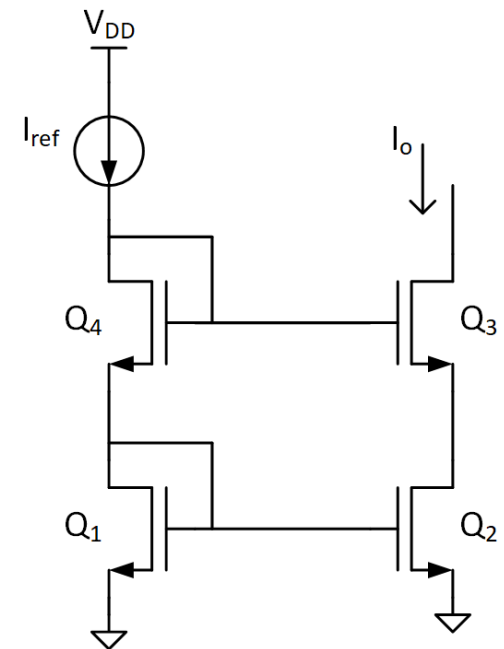- A significant portion of the total supply voltage



# Cascode Current Mirror – BJT

68

- The BJT cascode current mirror:
- Output resistance:

$$R_o = g_{m3}r_{o3}(r_{o2}||r_{\pi3})$$

- Voltage at the base of  $Q_3/Q_4$ :

$$V_{B3} = 2V_{BE}$$


- To remain in the active region:

$$V_{C3} > V_{B3} = 2V_{BE}$$

$$V_{C3} > \sim 1.4 V$$

- Again, a significant portion of the total supply voltage
- Cascode does not affect the current transfer ratio:
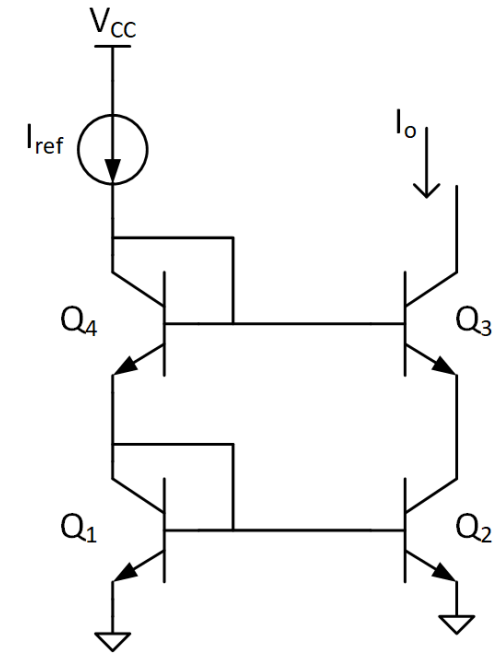
$$\frac{I_o}{I_{ref}} = \frac{1}{1 + \frac{2}{\beta}}$$



# Wilson Current Mirror – MOSFET

69


- The Wilson current mirror uses **negative feedback** to increase  $R_o$ 
  - Output current,  $I_o$ , is applied to the current mirror formed by  $Q_2$  and  $Q_1$
  - Mirrored  $I_o$  is fed back to the gate of  $Q_3$
  - $I_{G3} = 0$ , so  $I_o$  must be equal to  $I_{ref}$
  - If  $I_o > I_{ref}$ ,  $V_{G3}$  will drop, decreasing  $I_o$
  - If  $I_o < I_{ref}$ ,  $V_{G3}$  will rise, increasing  $I_o$

- Output resistance:

$$R_o = g_{m3}r_{o3} \cdot r_{o1} + r_{o3} + \frac{1}{g_{m2}}$$

$$R_o \approx g_{m3}r_{o3} \cdot r_{o1}$$

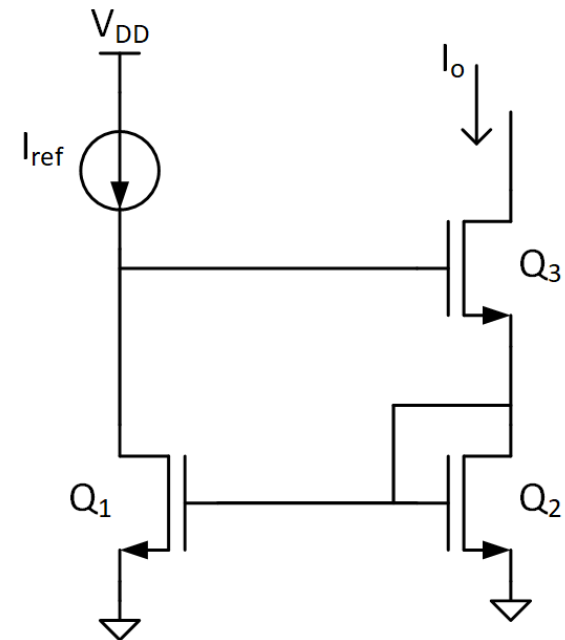
- Same  $R_o$  as for the cascode current mirror


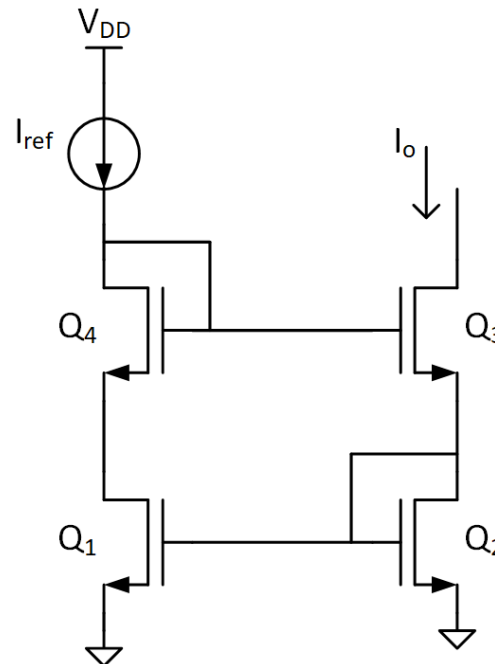
# Improved Wilson Mirror – MOSFET

70

- Wilson mirror can be improved by adding a fourth transistor
  - ▣  $Q_4$  helps to balance the drain-source voltages for  $Q_1$  and  $Q_2$
  - ▣ Reduces current-transfer-ratio errors



# Wilson Current Mirror – BJT

71

- Benefits of the Wilson mirror are greater for BJTs than for MOSFETs
  - ▣  $\beta$ -related current error reduced
- Current transfer ratio:


$$\frac{I_o}{I_{ref}} = \frac{1}{1 + \frac{2}{\beta(\beta + 2)}}$$

$$\frac{I_o}{I_{ref}} \approx \frac{1}{1 + \frac{2}{\beta^2}}$$

- ▣ Error significantly reduced compared to the simple mirror and cascode mirror
- Output resistance:

$$R_o = \left( \frac{\beta_3}{2} + 1 \right) r_{o3} + \frac{1}{2g_{m2}}$$


$$R_o \approx \frac{\beta_3}{2} r_{o3}$$

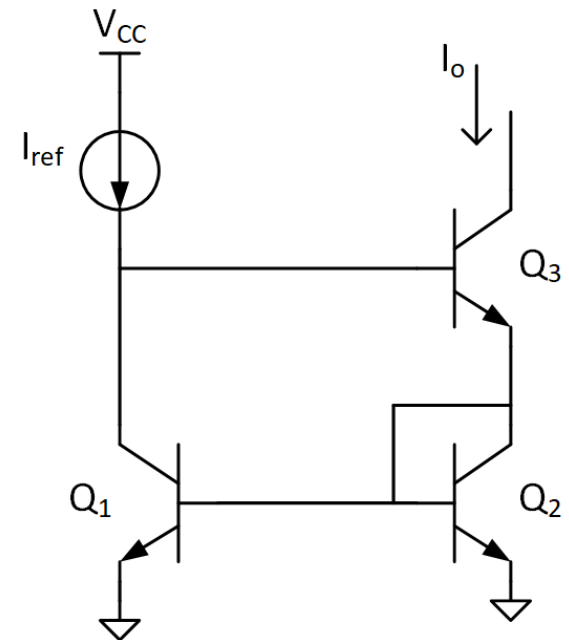
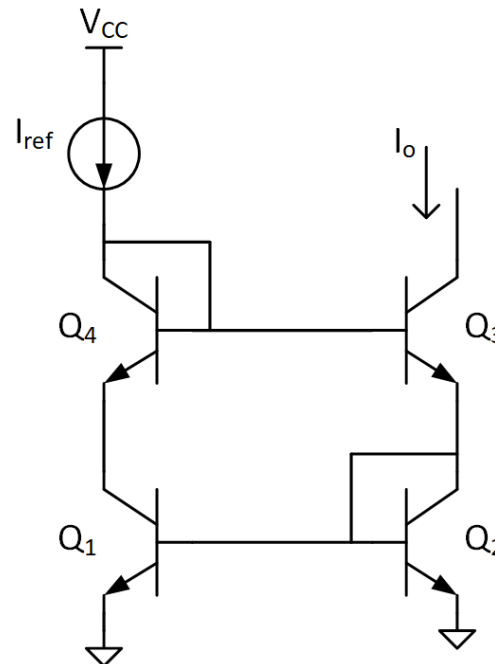
# Improved Wilson Mirror – BJT

72

- Similar to the MOSFET circuit, current-transfer-ratio error can be reduced by adding a fourth transistor to balance the  $Q_1$  and  $Q_2$  collector voltages






# Widlar Current Source – BJT

73

- Widlar current source adds an emitter resistor on the output transistor
- More of a *source* than a *mirror*
  - ▣ Current not replicated from one branch to the other
- Can generate small currents without the need for very large resistors
- Output resistance:



$$R_o \approx [1 + g_{m2}(R_{E2} || r_{\pi 2})]r_{o2}$$

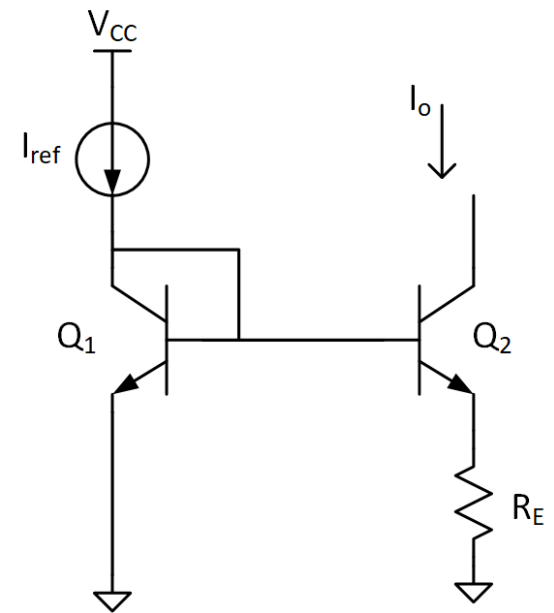
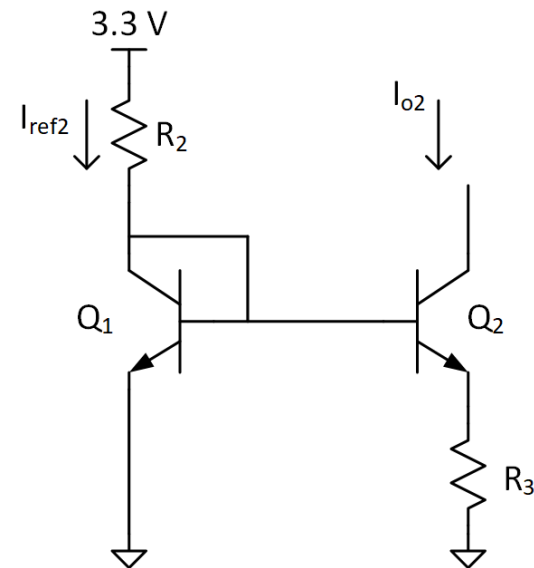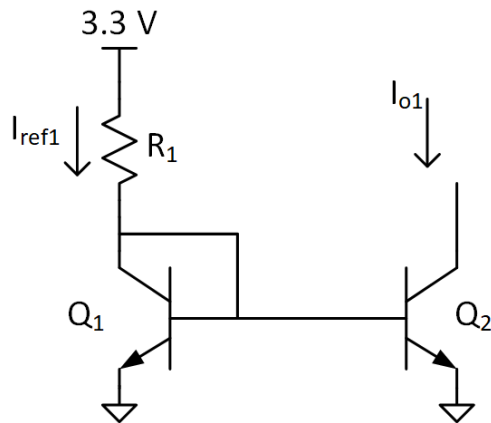
# Widlar Current Source – Example

74

- We can illustrate the function and benefit of a Widlar current source through an example
  - ▣ Compare the Widlar current source to a basic current mirror
- Design each source below for  $I_o = 10 \mu A$ 
  - ▣ Emitter areas are equal
  - ▣  $I_s = 2 \times 10^{-15} A = 2 fA$



# Widlar Current Source – Example

75

- First, design the basic current mirror
- The reference and output currents are equal

$$I_{ref1} = I_o = 10 \mu A$$

- Use  $I_{ref1}$  to determine  $V_{BE}$


$$V_{BE} = V_T \ln\left(\frac{I_{ref1}}{I_s}\right) = 26 \text{ mV} \ln\left(\frac{10 \mu A}{2 \text{ fA}}\right)$$

$$V_{BE} = 581 \text{ mV}$$

- Determine the value of  $R_1$

$$R_1 = \frac{V_{CC} - V_{BE1}}{I_{ref1}} = \frac{3.3 \text{ V} - 581 \text{ mV}}{10 \mu A}$$

$$R_1 = 272 \text{ k}\Omega$$

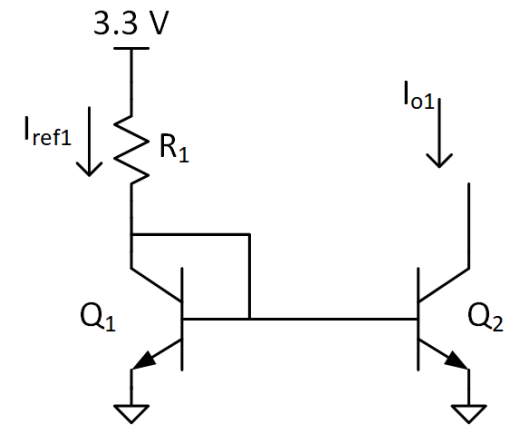

# Widlar Current Source – Example

76

- Next, design the Widlar source
- Here, we can choose the reference current

$$I_{ref2} = 1 \text{ mA}$$

- Use  $I_{ref2}$  to determine  $V_{BE1}$


$$V_{BE1} = V_T \ln\left(\frac{I_{ref2}}{I_s}\right) = 26 \text{ mV} \ln\left(\frac{1 \text{ mA}}{2 \text{ fA}}\right)$$

$$V_{BE1} = 700 \text{ mV}$$

- Determine the value of  $R_2$

$$R_2 = \frac{V_{CC} - V_{BE1}}{I_{ref1}} = \frac{3.3 \text{ V} - 700 \text{ mV}}{1 \text{ mA}}$$

$$R_2 = 2.6 \text{ k}\Omega$$

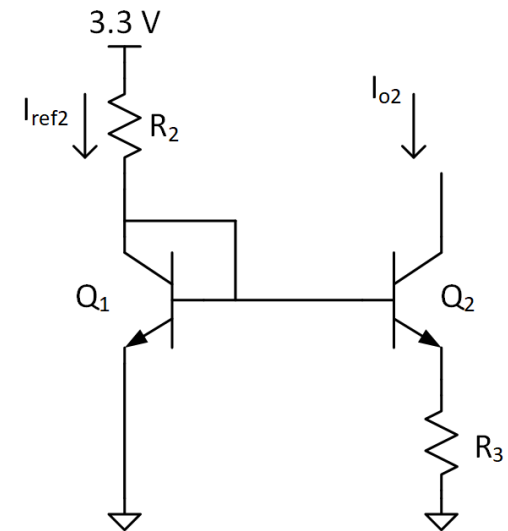

# Widlar Current Source – Example

77

- Next, determine  $R_3$ 
  - KVL around the B-E loop gives

$$V_{BE1} - V_{BE2} - I_{O2}R_3 = 0$$

$$R_3 = \frac{V_{BE1} - V_{BE2}}{I_{O2}}$$

- We already determined  $V_{BE2}$

$$V_{BE2} = 26 \text{ mV} \ln \left( \frac{10 \mu\text{A}}{2 \text{ fA}} \right) = 581 \text{ mV}$$

- So,  $R_3$  is

$$R_3 = \frac{700 \text{ mV} - 581 \text{ mV}}{10 \mu\text{A}} = 11.9 \text{ k}\Omega$$

$R_2 = 2.6 \text{ k}\Omega \quad \text{and} \quad R_3 = 11.9 \text{ k}\Omega$

- Both much smaller than required for the basic mirror ( $272 \text{ k}\Omega$ )

