

CLASS 3: ELECTRICAL FUNDAMENTALS

ENGR 102 – Introduction to Engineering

2

Fundamental Quantities

Fundamental Electrical Quantities

3

- **GOAL:** begin to understand the function of basic electrical circuits
- **REQUIREMENT:** become familiar with fundamental electrical concepts and quantities:
 - ***Voltage*** or ***potential***
 - ***Charge***
 - ***Current***

Electrical Charge

4

- Electrical energy results from ***charge differentials***
 - ▣ Different amounts of ***positive*** and ***negative electrical charge*** between two locations
 - E.g., between battery electrodes


- ***Negative electrical charge***
 - ▣ ***Electrons*** are the carriers of negative electrical charge

- ***Positive electrical charge***
 - ▣ ***Holes*** are the carriers of positive electrical charge
 - ▣ The absence of an electron

- ***Units of charge***: coulombs (C)
 - ▣ Charge of one electron: 1.6×10^{-19} C

Electrical Potential

5

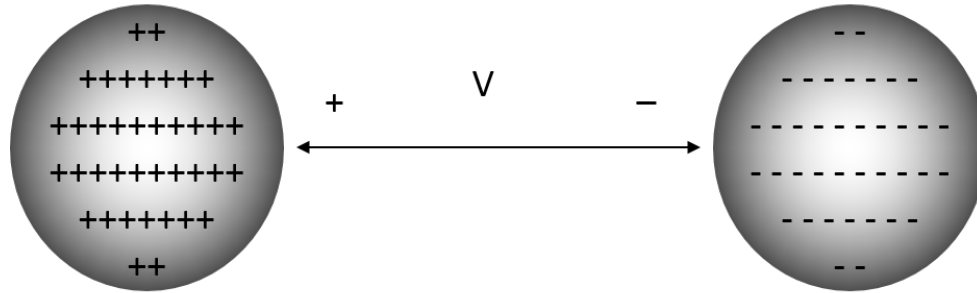

- **Potential** or **voltage** or **electromotive force** (emf)
 - A measure of electrical energy
 - The energy required to move one unit of electrical charge from one point to another
 - Units of potential: volts (V)
 - Units of electrical charge: coulombs (C)
 - Units of energy: joules (J)


$$1V = 1 \frac{J}{C}$$

Electrical Potential

6


- Electrical potential is a ***differential quantity***
 - Voltage ***between*** two points in a circuit
 - Voltage between a point and a ***ground reference***

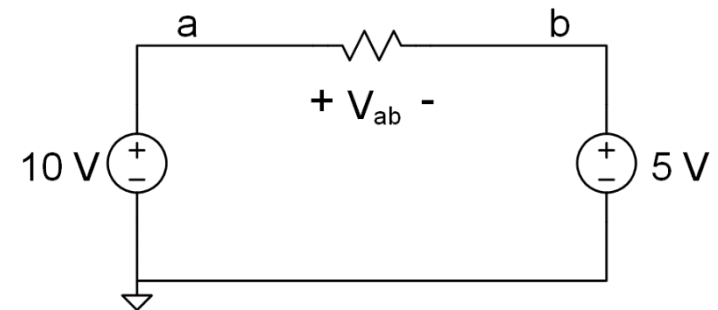- No such thing as an ***absolute*** voltage at a location, but...
 - We do talk about ***node voltages***
 - Always referenced to ground
 - For example,
 - Node voltages:
$$V_a = 10\text{ V}, \quad V_b = 5\text{ V}$$
 - Differential voltage:
$$V_{ab} = V_a - V_b = 5\text{ V}$$



Electrical Current

7

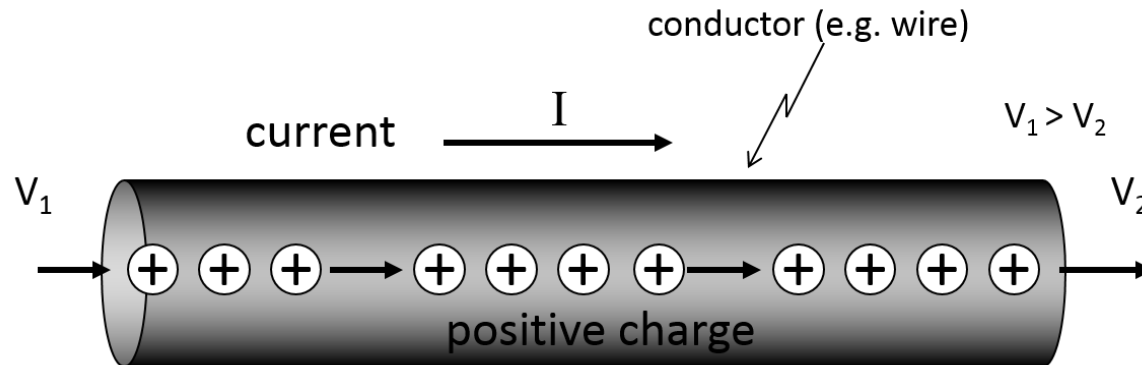


- **Current** (I) is the flow of positive charge
 - Voltage is the driving potential
 - Units: amperes or amps (A) – coulombs per second (C/s)
 - A **rate** of charge flow:

$$1A = 1 \frac{C}{s}$$

- Current wants to flow from high to low potential
- Analogous to fluid flow or heat flow
 - Fluid flows from high to low pressure
 - Heat flows from high to low temperature

Current – what's really flowing?

8

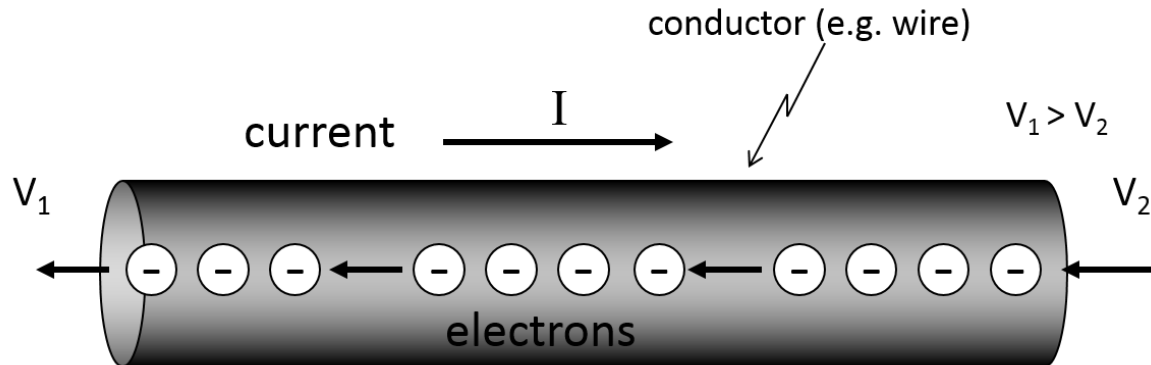

- Current is defined as the ***flow of positive charge***
- Really, current is the ***flow of negatively-charged electrons in the opposite direction***
 - ▣ Electrons flow from low potential to high potential
 - ▣ Negative charge flow in one direction is equivalent to positive charge flow in the opposite direction

Electrical-Mechanical Analogies

9

- Electrical systems are analogous to:
 - ***Fluid systems***
 - ***Thermal systems***

Domain	Driving potential	Flowing quantity	Flow	(units)
<i>Electrical</i>	Voltage	Positive charge	Current	(A)
<i>Fluid</i>	Pressure	Fluid	Flow rate	(m ³ /s)
<i>Thermal</i>	Temperature	Heat	Heat flux	(W)




10

Electrical Circuits

Electrical Networks – Schematics


11

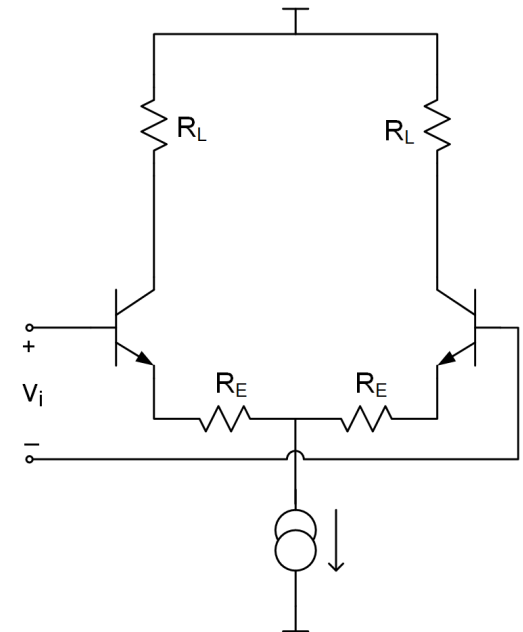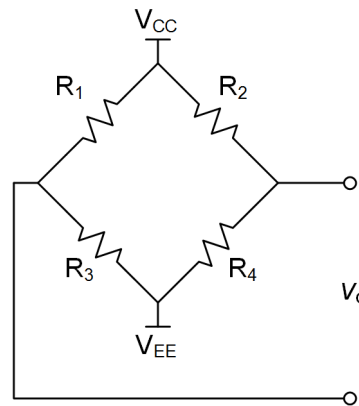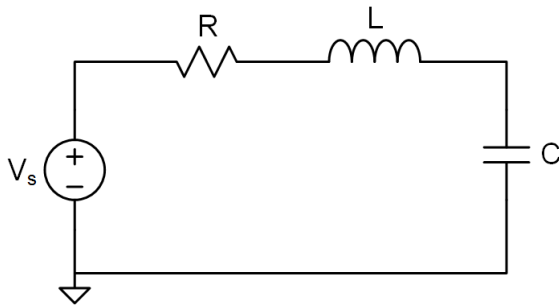- Electrical circuits represented graphically with **schematics**
 - ▣ Schematic symbols represent circuit elements
 - ▣ Schematics detail connections between circuit elements
 - ▣ Schematics describe paths for the flow of electrical current
- Some examples:



Electrical Networks – Branches & Nodes

12

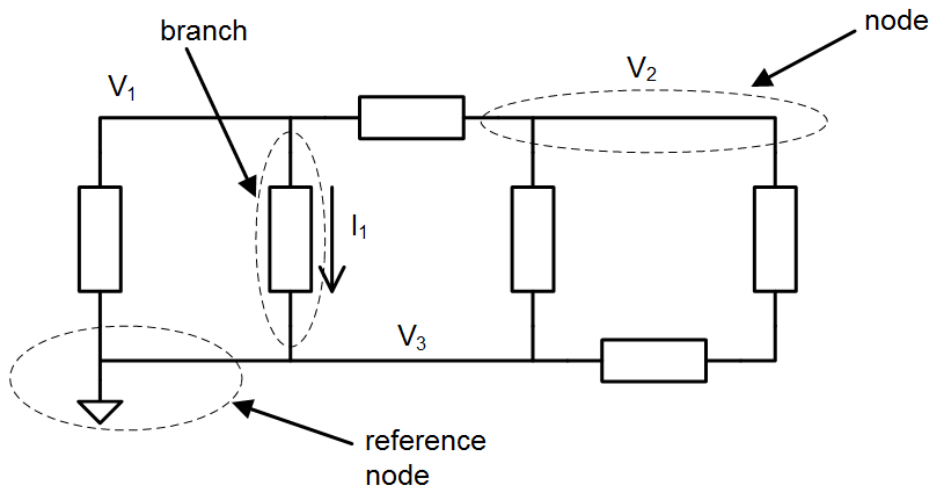

□ **Nodes**

- Connection points for circuit elements
- Node voltages given with respect to a reference node (0 V, ground)
 - E.g., $V_3 = 0$ V, here
- Current flows into and out of nodes

□ **Branches**

- Paths for current to flow
- Connections between nodes
- Branches are the components that comprise the circuit
- Voltage across a branch is the difference between node voltages at either end

Short Circuits & Open Circuits


13

□ **Short circuit**

- Direct connection between multiple nodes in a circuit
- A direct path for current to flow
- Often refers to an unintentional connection

□ **Open circuit**

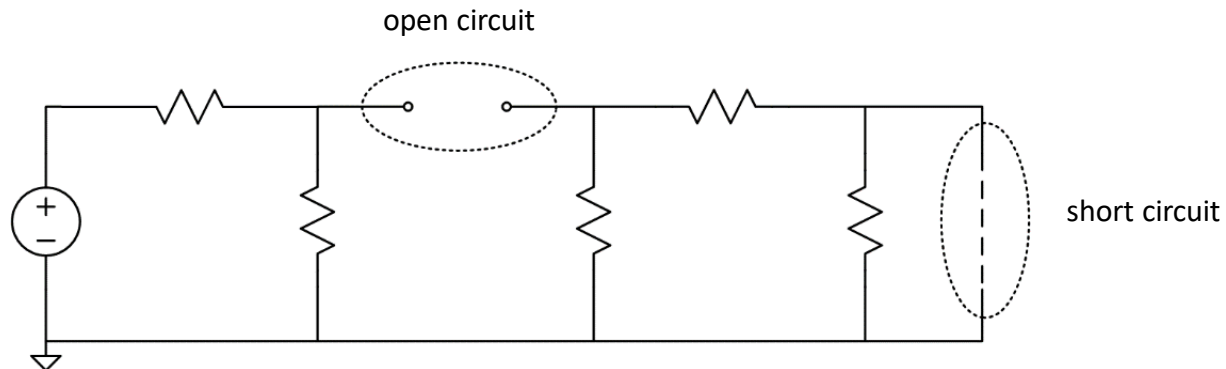- Lack of any electrical connection between two nodes in a circuit
- No path for current to flow
- Again, often used to refer to an unintended condition



Complete Circuits

14

- Electrical current always flows in a ***complete circuit***
 - A return current path must always exist for current to flow
 - Consider a simple lamp:
 - Two-conductor cord – line and neutral
 - Current flows from socket, down one conductor – line
 - Current flows through the bulb
 - Current returns back along the neutral conductor to the wall, and, ultimately, to the power plant
 - Ladder on a power line vs. bird on power line

15


Electrical Circuit Components

Circuit Components

16

□ ***Voltage source***

□ **Schematic symbol:**

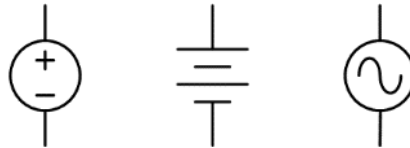


□ **Description:**

- Generates a fixed voltage between its terminals
- DC or AC

□ **Units:** volts (V)

□ ***Current source***

□ **Schematic symbol:**

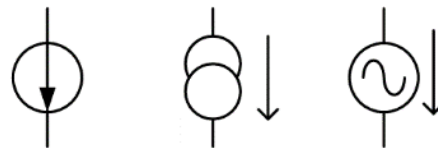

□ **Description:**

- Generates a fixed current
- DC or AC
- Current flows in one terminal and out the other

□ **Units:** amperes (A)

Circuit Components

17

□ **Resistor**

□ **Schematic symbol:**




□ **Description:**

- Circuit element that resists the flow of electrical current
- Intentional or parasitic resistance (even wires are resistive)

□ **Units:** ohms (Ω)

□ **Ground**

□ **Schematic symbol:**

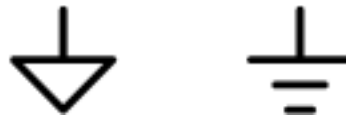

□ **Description:**

- Voltage reference for a circuit
- Ground node
- Potential of 0 V

Circuit Components

18

□ **Capacitor**

□ **Schematic symbol:**



□ **Description:**

- Stores energy in an electric field
- Two electrodes separated by a dielectric
- Stores a charge differential between the two electrodes

□ **Units:** farads (F)

□ **Inductor**

□ **Schematic symbol:**



□ **Description:**

- Stores energy in a magnetic field
- A coil of wire


□ **Units:** henries (H)

Circuit Components

19

□ **Switch**

□ **Schematic symbol:**

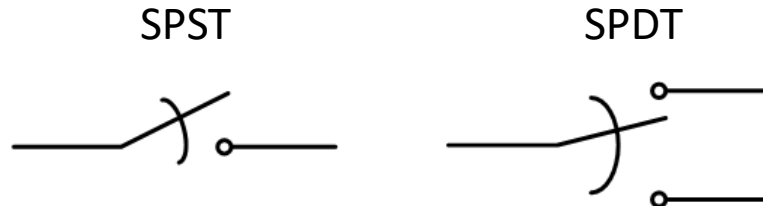

□ **Description:**

- Controls connections between multiple nodes in a circuit
- Single-pole single-throw (SPST) switch makes/breaks connection between two nodes
- Single-pole double-throw (SPDT) switch connects one node to one of two other nodes
- Many other configurations, e.g. DPDT, 3PDT, 6P3T, etc.

Circuit Components

20

□ **Diode**

□ **Schematic symbol:**




□ **Description:**

- Two-terminal semiconductor device
- Junction of p-type and n-type semiconductor – a p-n junction
- Allows current to flow in one direction only (anode to cathode)
- Analogous to a check valve

□ **Light-emitting diode (LED)**

□ **Schematic symbol:**

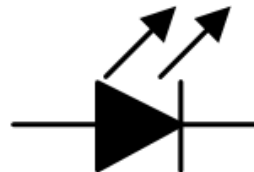

□ **Description:**


- Diode that emits photons in response to current flowing through it

Circuit Components

21

□ **Transistor**

▣ **Schematic symbol:**

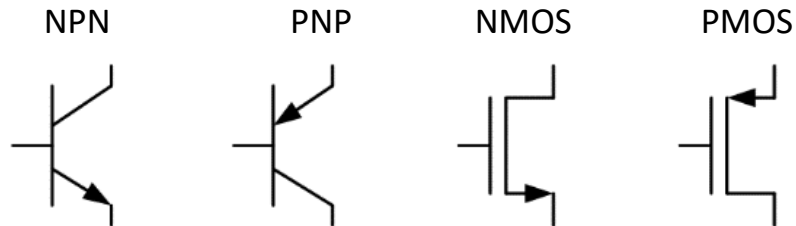

▣ **Description:**

- Three-terminal semiconductor device
- Small voltage on/current into one terminal controls current flow between the other two terminals
- Primary building block of integrated circuits
- Can be used as **switches** or **amplifiers**
- Analogous to **valves**:

