

CLASS 4: ELECTRICAL RESISTANCE

ENGR 102 – Introduction to Engineering

2

Resistance & Conductance

Resistance

3

□ **Resistance**

- The degree to which a circuit element opposes the flow of electrical current

□ Schematic symbol:




- Units: ohms (Ω)
- May be discrete, intentional circuit components, or parasitic resistance of wires, cables, interconnects, etc.

Resistance – Fluid Analogy

4

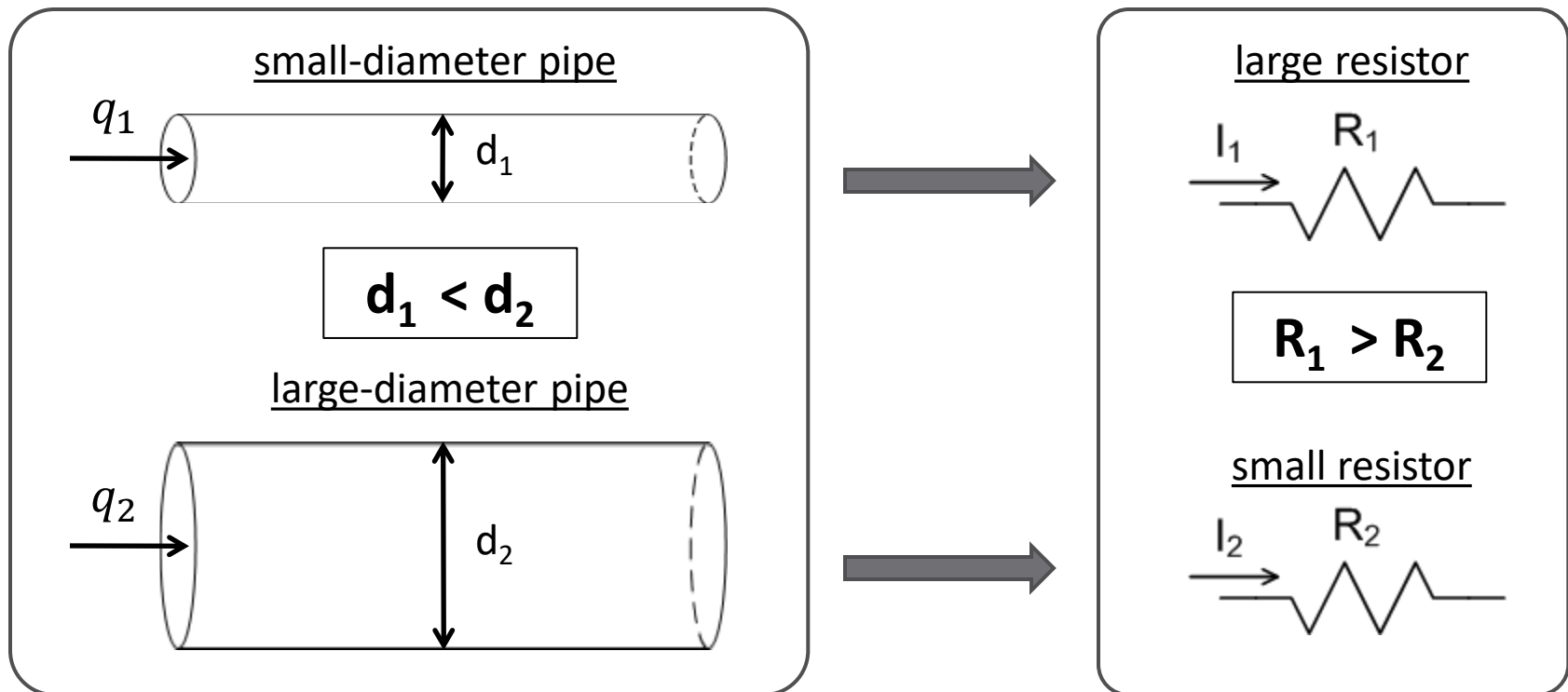
- Electrical resistance is analogous to the resistance of a pipe to fluid flow due to friction



Resistance – Thermal Analogy

5

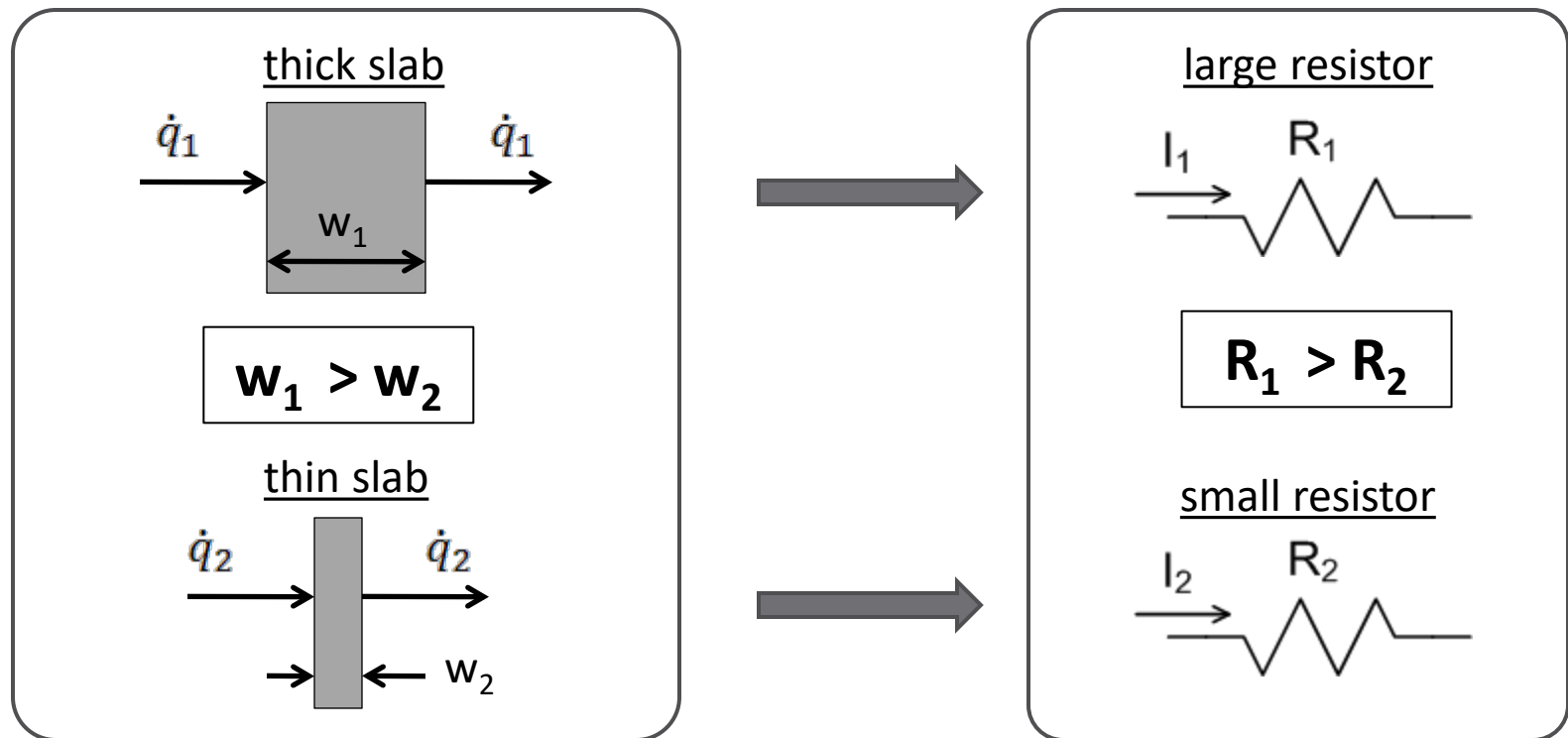- Electrical resistance is analogous to the resistance of heat conduction through a solid




Conductance

6

- Electrical **conductance** is the degree to which a circuit element allows the flow of electrical current
- Conductance is the **inverse of resistance**

$$G = \frac{1}{R}$$

- Schematic symbol:

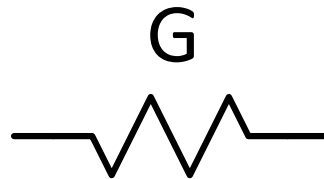

- Units: **siemens** or **mhos** (S or Ω^{-1})

Real Resistors





7

- Resistors for use in electronic circuits come in many shapes and sizes depending on their target application
- Size primarily determined by power handling capability
 - ▣ Larger resistors can dissipate more power
- Two primary form factors:
 - ▣ ***Axial lead*** resistors
 - ▣ ***Chip*** resistors


Axial Lead resistors

8

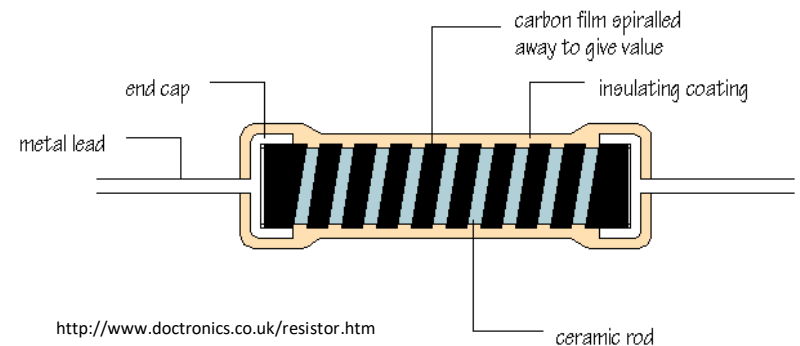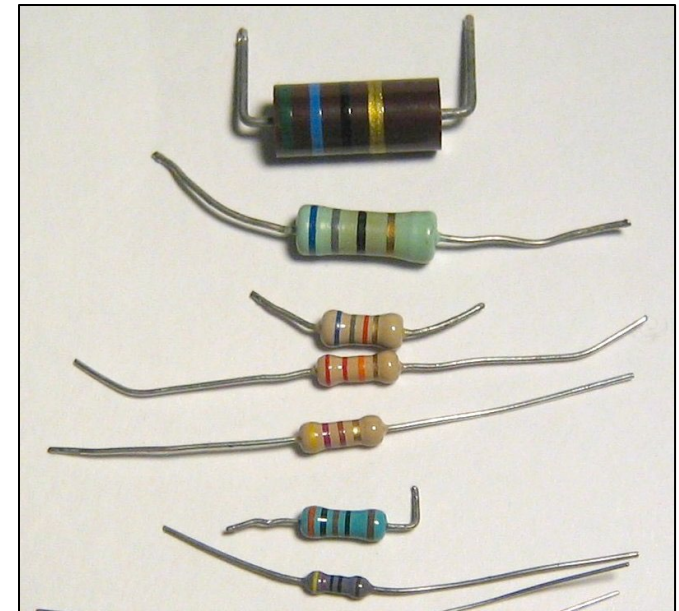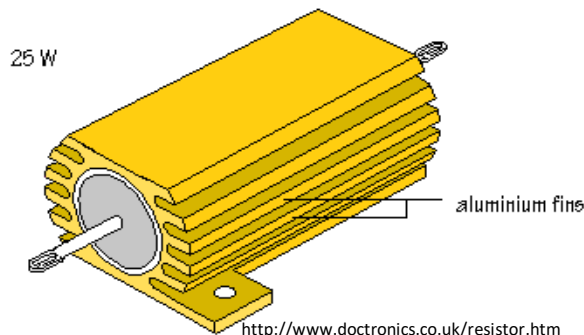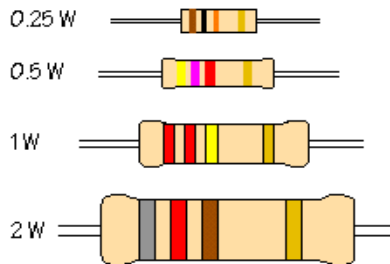- Cylindrical resistive component with wire leads extending from each end
- Used with **through-hole technology** printed circuit boards (PCB's)
 - ▣ Useful for prototyping
 - ▣ Size varies with power handling capacity



Resistor Color Code

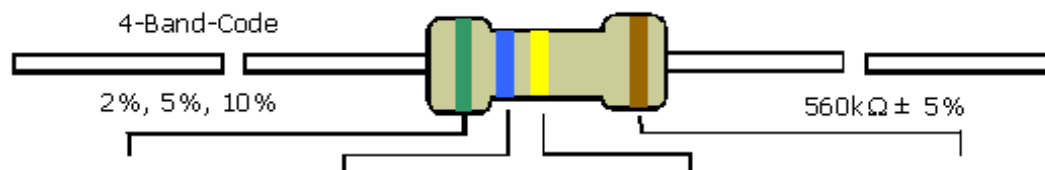

COLOR	1st BAND	2nd BAND	3rd BAND	MULTIPLIER	TOLERANCE
Black	0	0	0	1Ω	
Brown	1	1	1	10Ω	± 1% (F)
Red	2	2	2	100Ω	± 2% (G)
Orange	3	3	3	1KΩ	
Yellow	4	4	4	10KΩ	
Green	5	5	5	100KΩ	±0.5% (D)
Blue	6	6	6	1MΩ	±0.25% (C)
Violet	7	7	7	10MΩ	±0.10% (B)
Grey	8	8	8		±0.05%
White	9	9	9		
Gold				0.1	± 5% (J)
Silver				0.01	± 10% (K)




http://www.elexp.com/t_resist.htm

Chip Resistors

10

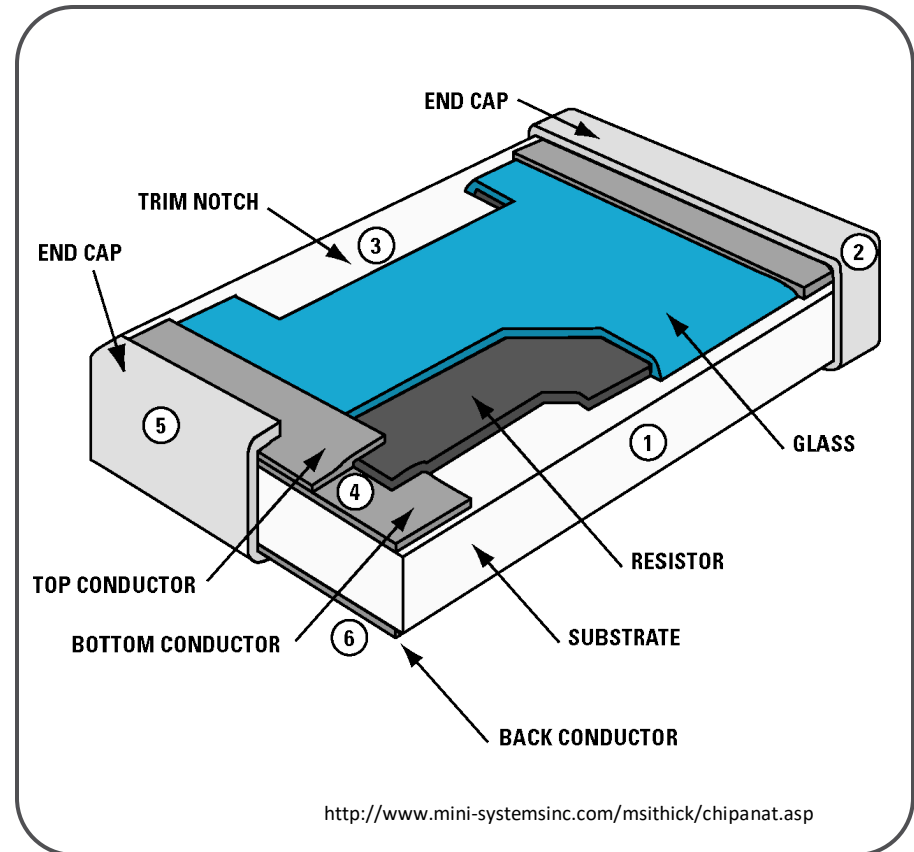- Small rectangular footprint
 - ▣ 0805 – 0.080" x 0.050"
 - ▣ 0603 – 0.060" x 0.030"
 - ▣ 0402 – 0.040" x 0.020"
 - ▣ 0201 – 0.020" x 0.010"
- Used with **surface-mount technology** PCB's
- More common than axial lead in modern electronics



11

Ohm's Law


Ohm's Law

12



Georg Simon Ohm, 1789 – 1854

$$I = \frac{V}{R}$$

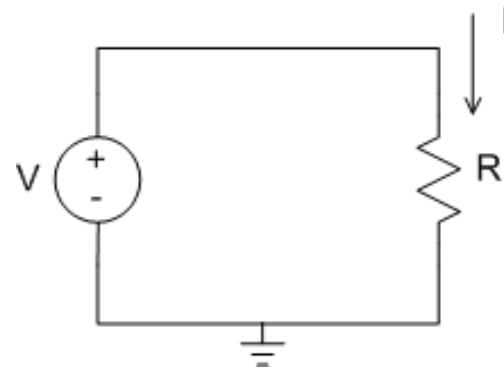


“The current through a resistor is proportional to the voltage across the resistor and inversely proportional to the resistance.”

Ohm's Law – said differently

13

$$V = I \cdot R$$

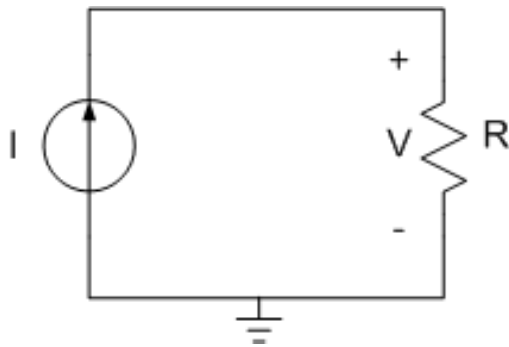



Georg Simon Ohm, 1789 – 1854

“The voltage across a resistor is proportional to the current through the resistor and proportional to the resistance.”

Ohm's Law – fluid analogy

14


- **Voltage** is analogous to **pressure**
 - ▣ Driving potentials
- Electrical **current** is analogous to **flow rate**
- A pipe carrying fluid has some resistance determined by physical characteristics (length, diameter, roughness, etc.)
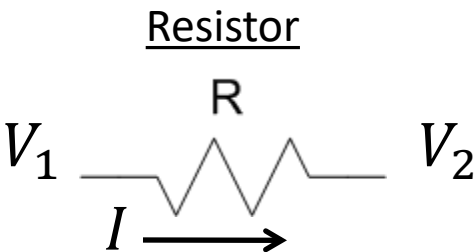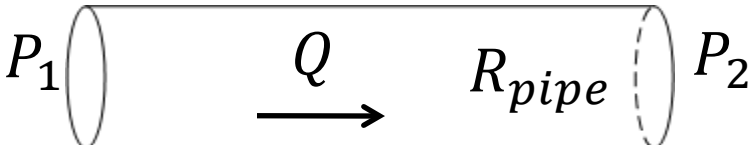
<p><u>Resistor</u></p> 	$I \propto (V_1 - V_2),$ $(V_1 - V_2) \propto I,$	$I \propto \frac{1}{R}$ $(V_1 - V_2) \propto R$
<p><u>Section of pipe</u></p> 	$Q \propto (P_1 - P_2),$ $(P_1 - P_2) \propto Q,$	$Q \propto \frac{1}{R_{pipe}}$ $(P_1 - P_2) \propto R_{pipe}$


Ohm's Law – thermal analogy

15

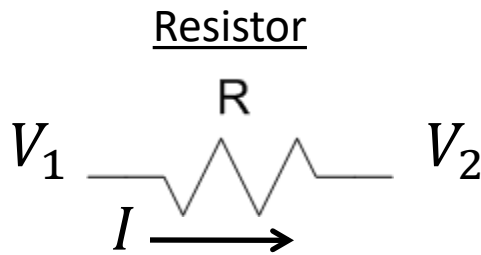- **Voltage** is analogous to **temperature**
 - ▣ Driving potentials
- Electrical **current** is analogous to **heat flux**
- A solid slab or wall has some thermal resistance determined by physical characteristics (thickness, material properties, etc.)


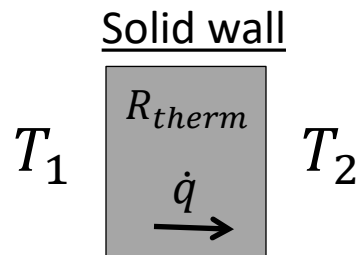
$$I \propto (V_1 - V_2), \quad I \propto \frac{1}{R}$$
$$(V_1 - V_2) \propto I, \quad (V_1 - V_2) \propto R$$



$$\dot{q} \propto (T_1 - T_2), \quad \dot{q} \propto \frac{1}{R_{therm}}$$
$$(T_1 - T_2) \propto \dot{q}, \quad (T_1 - T_2) \propto R_{therm}$$

Resistor Color Code

16

Exercise

- What are the values of the following resistors?



Ohm's Law

17

Exercise



- A 1 kW space heater is plugged into a 120 V wall outlet. The resistive heating element in the heater has a resistance of 14 Ω .
 - ▣ How much current does the heater draw?

Diodes & LEDs

18

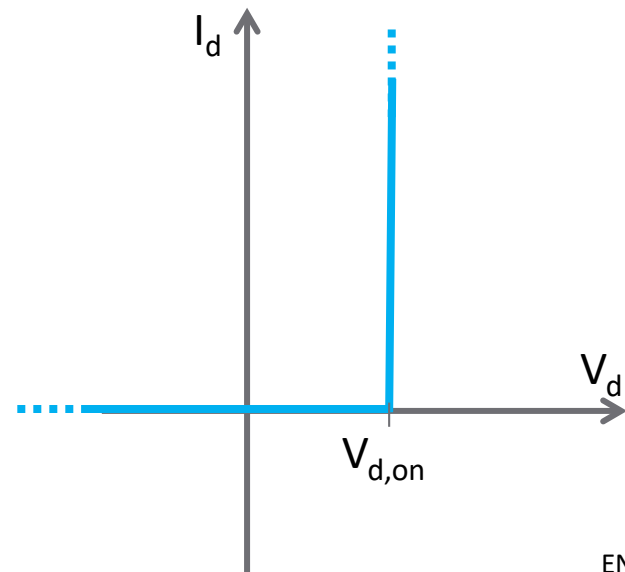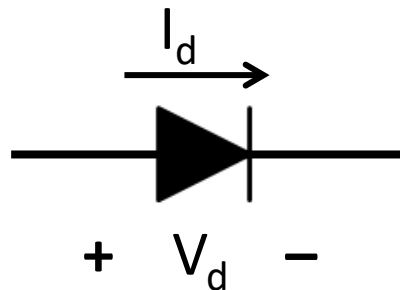Exercise

- **Diodes** allow current to flow in one direction only
 - Diode is off ($I_d = 0$) when voltage is less than the **turn-on voltage** ($V_d < V_{d,on}$)
 - Typically, $V_{d,on} \approx 600 - 700 \text{ mV}$
 - When the diode is on ($I_d > 0$), diode voltage is approximately constant, independent of current ($V_d = V_{d,on}$)




Diodes & LEDs

19

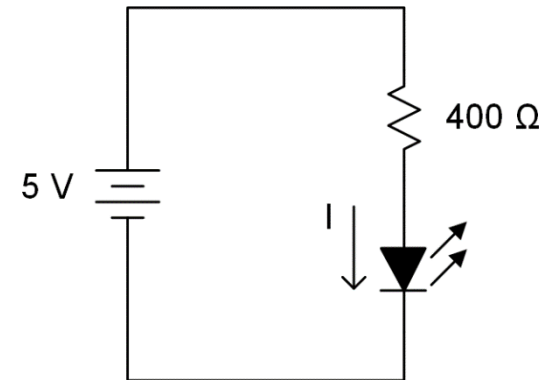Exercise

- Light-emitting diodes (LEDs) behave the same way
- LED turn-on voltage depends on color
 - ▣ $V_{d,on} \approx 1.8 V \dots 3.6 V$
- Determine the LED current in the circuit below
 - ▣ Assume $V_{d,on} = 2 V$



Diodes & LEDs

20

Exercise

- Determine the value of the current-limiting resistor, R , below, such that $I = 18 \text{ mA}$
 - ▣ Assume $V_{d,on} = 2 \text{ V}$

