

# CLASS 5: VOLTAGE & CURRENT DIVIDERS


2

# Series & Parallel Circuits
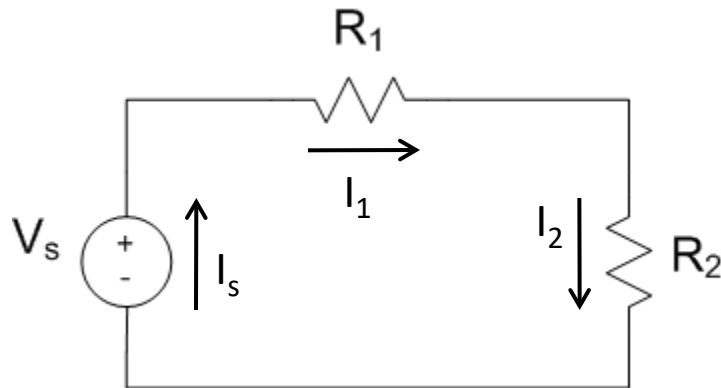
# Series Circuits

3

- Series-connected components
  - ▣ Share **one common node**
    - Nothing else connected to that node
  - ▣ Connected end-to-end
  - ▣ **Equal current** through each component




Resistors,  $R_1$  and  $R_2$ , and voltage source,  $V_s$ , are all connected in **series**

$$I_s = I_1 = I_2$$
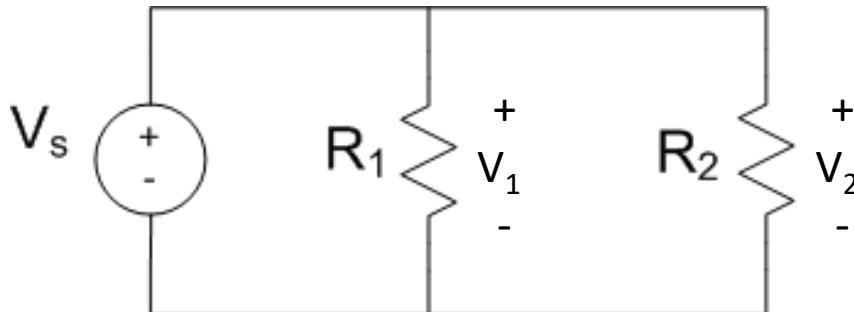
# Parallel Circuits

4

- Components in **parallel**
  - ▣ Share **two common nodes**
  - ▣ Connected side-by-side
  - ▣ **Equal voltage** across each component




Resistors,  $R_1$  and  $R_2$ , and voltage source,  $V_s$ , are all connected in **parallel**

$$V_s = V_1 = V_2$$

# Series Resistance

5

- **Resistances in series add**

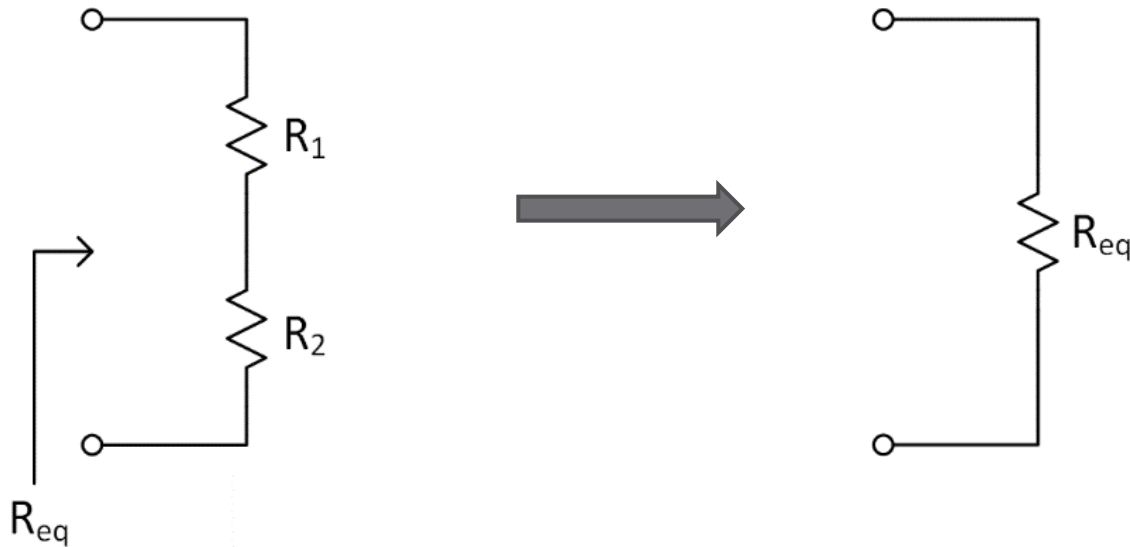

$$R_{eq} = R_1 + R_2$$


- In general,

$$R_{eq} = \sum R_i$$

# Parallel Resistance

6

## □ *Conductances in parallel add*

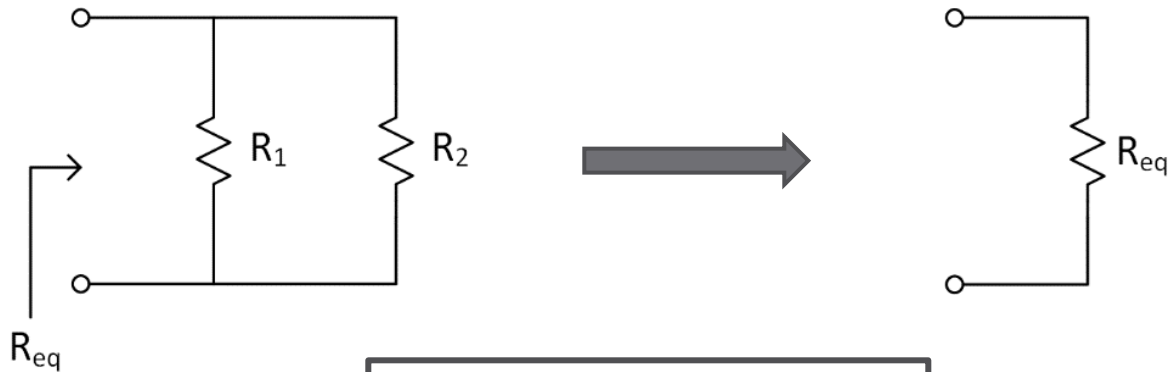

$$R_{eq} = \left( \sum \frac{1}{R_i} \right)^{-1}$$

## □ For **two** parallel resistors (only):


$$R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \frac{R_1 R_2}{R_1 + R_2}$$

# Equivalent Resistance

7
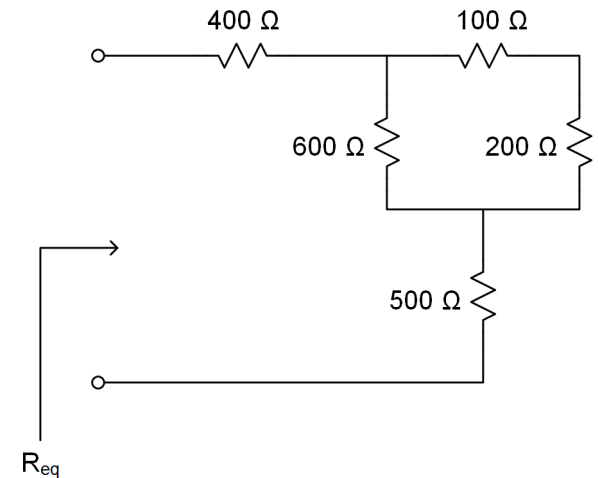
## Exercise

- Determine the equivalent resistance seen looking into the terminals of the following network



8

# Voltage & Current Dividers




# Voltage Dividers

9

- Voltage across series resistors divides proportional to resistance
- Consider two series resistors:
  - ▣ Current through the resistors

$$I = \frac{V_s}{R_1 + R_2}$$

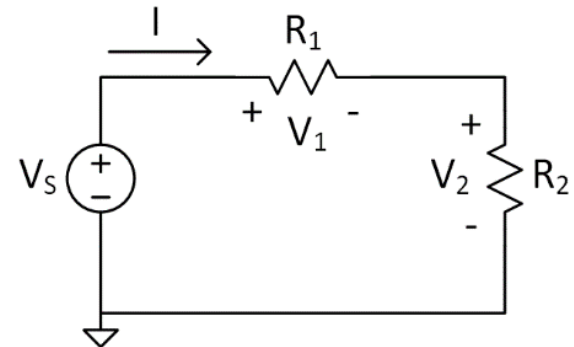

- ▣ Ohm's law gives the voltage across either resistor

$$V_n = IR_n$$

$$V_1 = \frac{V_s}{R_1 + R_2} R_1 = V_s \frac{R_1}{R_1 + R_2}$$

$$V_2 = \frac{V_s}{R_1 + R_2} R_2 = V_s \frac{R_2}{R_1 + R_2}$$

# Voltage Dividers

10


- In general, the voltage across one in a series of resistors is given by

$$V_n = V_{total} \cdot \frac{R_n}{\sum R_i}$$

- For example:

$$V_3 = 16 V \frac{300 \Omega}{1 k\Omega + 200 \Omega + 300 \Omega + 100 \Omega}$$
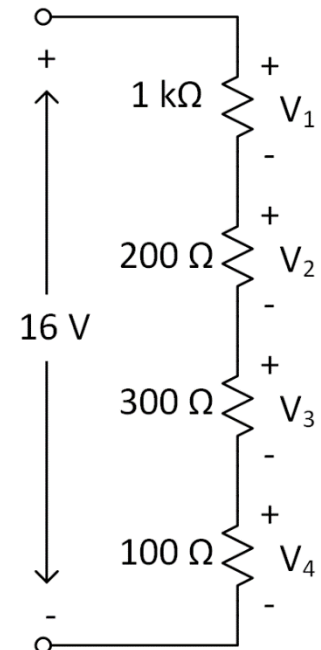
$$V_3 = 16 V \frac{300 \Omega}{1.6 k\Omega} = 3 V$$




# Current Dividers

11

- Current through parallel-connected resistances divides proportional to conductance
- Consider two parallel resistors:
  - Voltage across the resistors
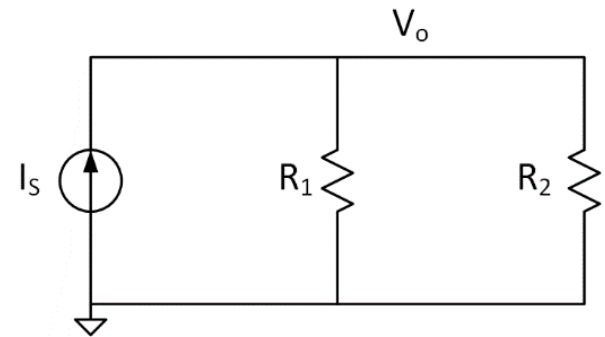
$$V_o = \frac{I_S}{G_1 + G_2} = \frac{I_S}{\frac{1}{R_1} + \frac{1}{R_2}} = I_S \frac{R_1 R_2}{R_1 + R_2}$$



- Ohm's law gives the current through either resistor

$$I_n = \frac{V_o}{R_n}$$

$$I_1 = \frac{I_S}{R_1} \frac{R_1 R_2}{R_1 + R_2} = I_S \frac{R_2}{R_1 + R_2}$$

$$I_2 = \frac{I_S}{R_2} \frac{R_1 R_2}{R_1 + R_2} = I_S \frac{R_1}{R_1 + R_2}$$

# Current Dividers

12

- Current through one of **two** parallel resistors is given by

$$I_1 = I_{total} \cdot \frac{R_2}{R_1 + R_2}$$

$$I_2 = I_{total} \cdot \frac{R_1}{R_1 + R_2}$$

- ▣ One of the two resistors may be a parallel combination of multiple resistors
- More generally, expressed in terms of **conductance**
  - ▣ Applies to any number of parallel resistances

$$I_n = I_{total} \cdot \frac{G_n}{\Sigma G_i}$$

# Current Dividers

13

- For example, determine  $I_1$
- First, combine the  $300\ \Omega$  and  $100\ \Omega$  resistors in parallel

$$R_{eq} = \left( \frac{1}{300\ \Omega} + \frac{1}{100\ \Omega} \right)^{-1} = 75\ \Omega$$



- Next, apply the current divider equation:

$$I_1 = I_{total} \frac{R_2}{R_1 + R_2}$$

$$I_1 = 22\ A \frac{75\ \Omega}{200\ \Omega + 75\ \Omega}$$


$$I_1 = 6\ A$$

# Current Dividers

14

□ Or, using conductances:
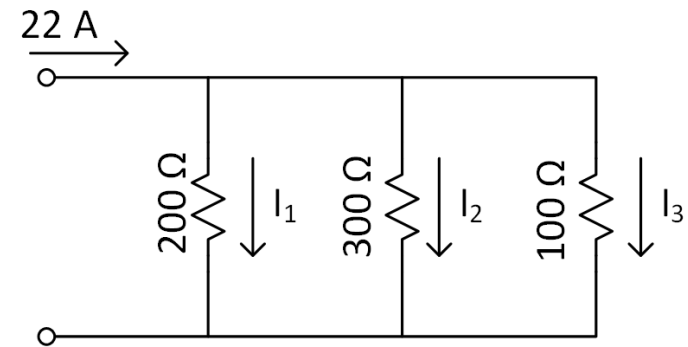
$$I_1 = 22 A \frac{\frac{1}{200 \Omega}}{\frac{1}{200 \Omega} + \frac{1}{300 \Omega} + \frac{1}{100 \Omega}}$$



$$I_1 = 22 A \cdot \frac{5 mS}{5 mS + 3.33 mS + 10 mS}$$

$$I_1 = 22 A \cdot 0.2727$$


$$I_1 = 6 A$$

# Voltage Division

15
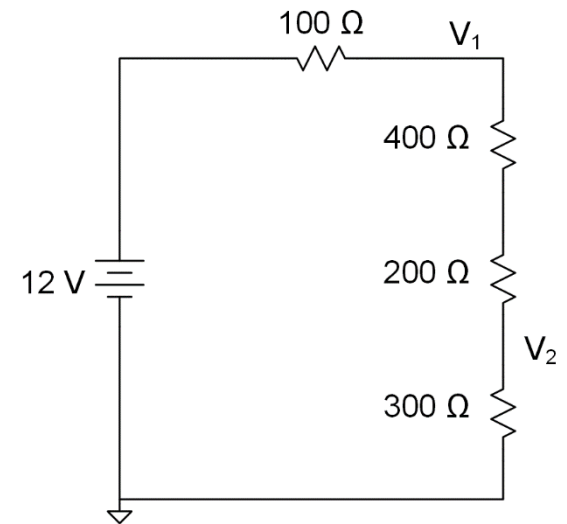
## Exercise

- Apply the principle of voltage division to determine  $V_1$  and  $V_2$  in the circuit below.



# Current Division

16

## Exercise

- Apply the principle of current division to determine  $V_o$  in the circuit below.

