

CLASS 6:  
ELECTRICAL SIGNALS &  
KIRCHHOFF'S LAWS

2

# Electrical Signals & Waveforms

# Electrical Signals


3

- ***Voltage*** and ***current*** are the two properties of electrical circuits that we are most often concerned with
  - Voltages and currents may be ***constant as functions of time***
    - Direct current, ***DC***
  - Or they may be ***time-varying***
    - Alternating current, ***AC***
  - We can refer to these quantities as electrical ***signals***
    - They carry information
    - More appropriate terminology in the world of electronics than power systems
- Voltages and currents can be plotted as functions of time – ***waveforms***

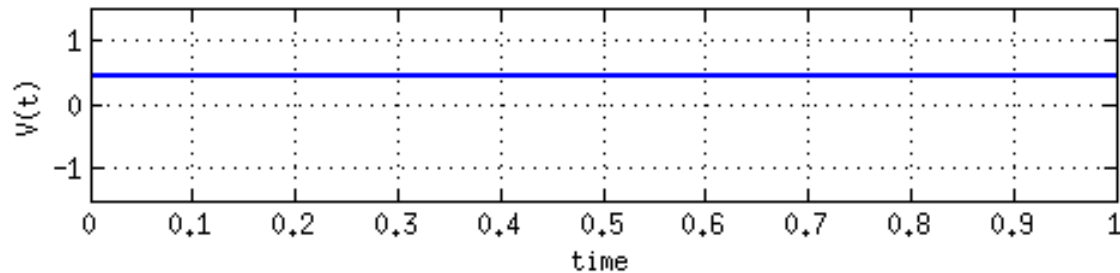
# DC vs. AC

4

- **DC** (direct current) electrical signals (voltages, currents) are ***time-invariant***
  - ▣ In ENGR 201, we will primarily focus on DC signals



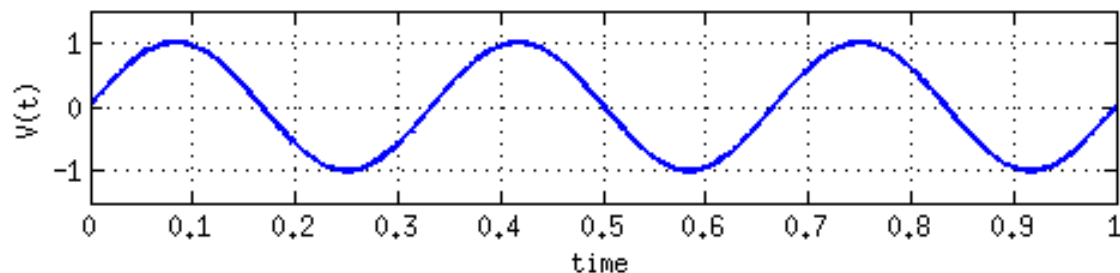
- **AC** (alternating current) electrical signals are ***time-varying***
  - ▣ Possibly ***periodic***




# Some Typical Waveforms

5


***Sinusoid:***

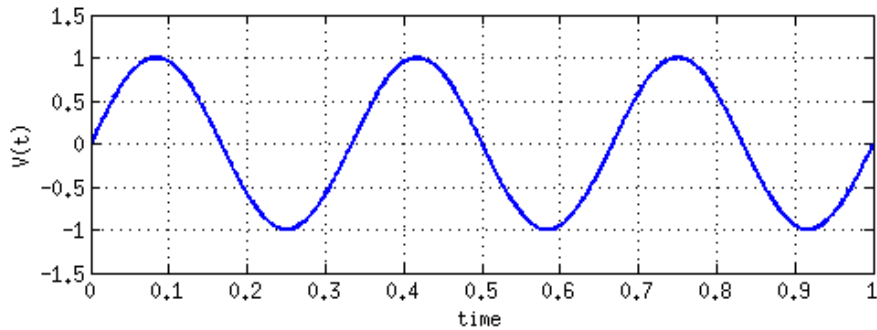


***Square wave:***

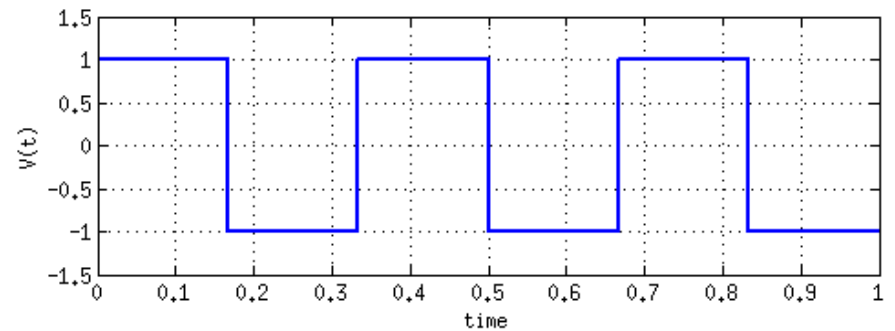

***Triangle wave:***

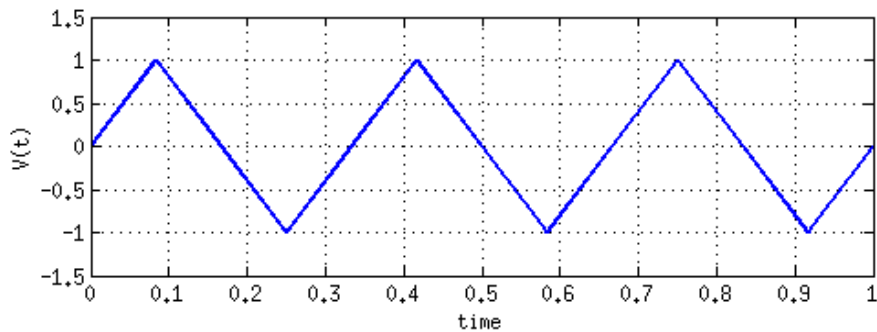

***Noise:***

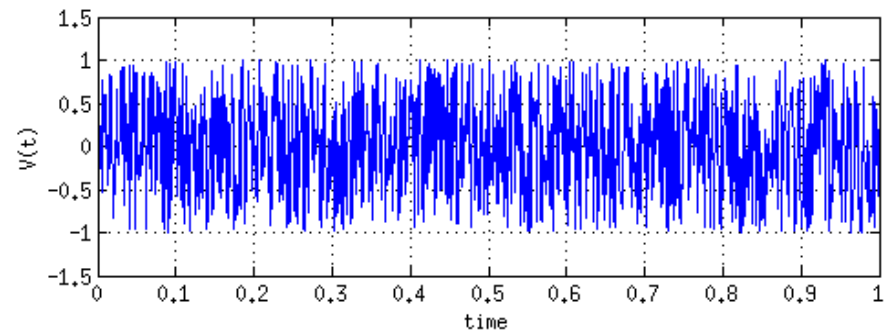


6

# Kirchhoff's Laws

# Kirchhoff's Current Law - KCL


7

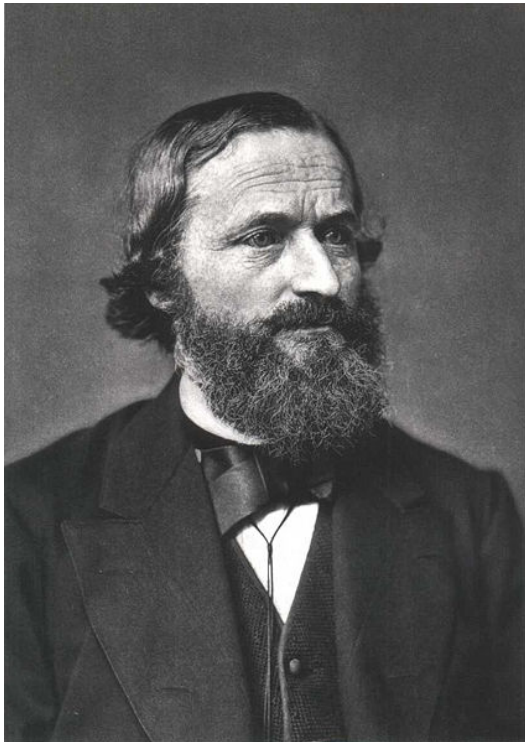

Gustav Kirchhoff, 1824 – 1887

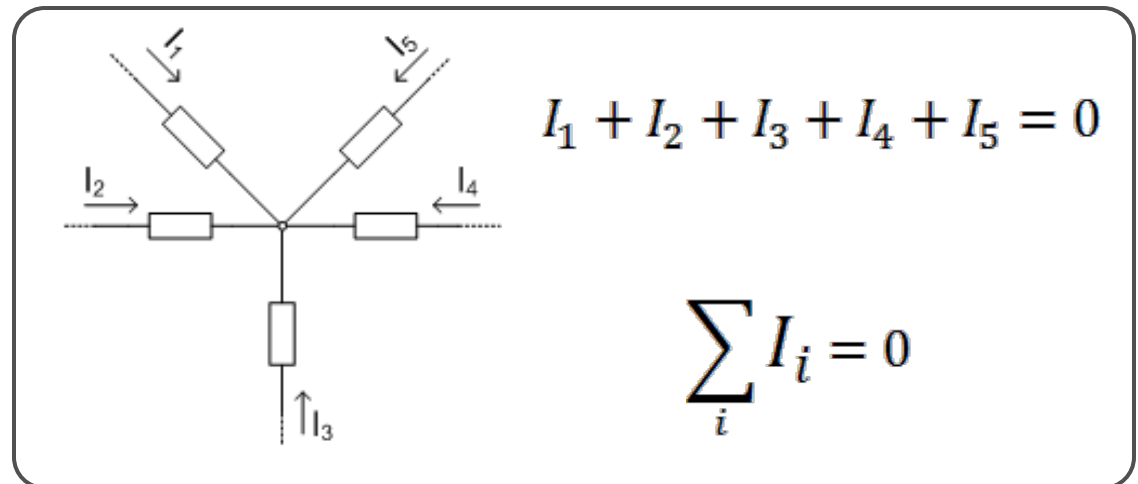**“The algebraic sum of currents entering any node must be zero.”**

- Charge cannot accumulate in a node
- What flows in, must flow out




- Analogous to the conservation of mass
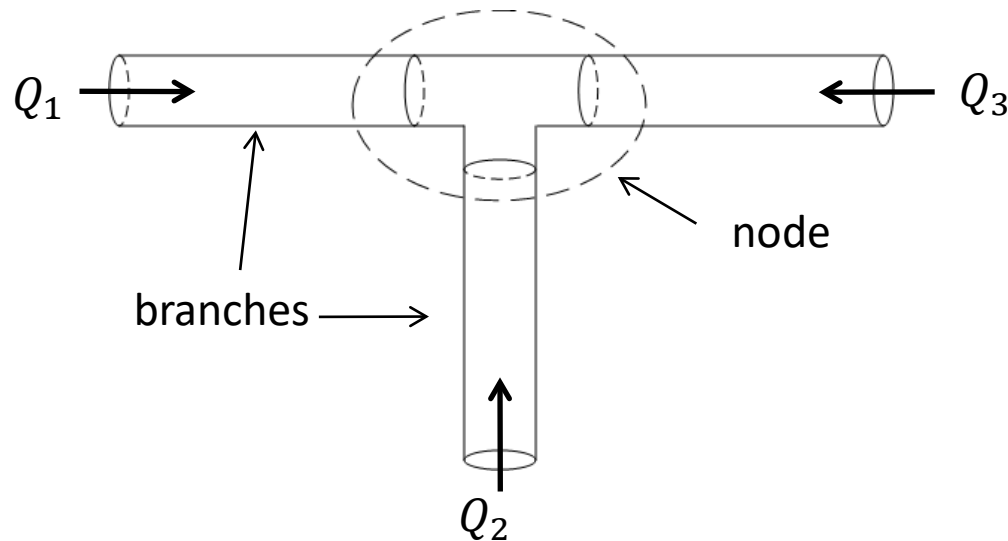
# KCL & the Conservation of Mass

8

- Consider fluid-carrying pipes connected in a Tee
  - ▣ Tee connector is analogous to electrical **node**
  - ▣ Pipes analogous to **branches**
- According to the conservation of mass, what flows in must flow out
  - ▣ ***Sum of the flow rates must be zero***



$$\sum_i Q_i = 0$$



# KCL - Example

9

- Determine the current through the  $1\text{ k}\Omega$  resistor,  $I_3$
- Applying KCL

$$I_1 + I_2 + I_3 = 0$$

$$I_3 = -I_1 - I_2$$

- $I_1$  and  $I_2$  are known:


$$I_1 = 10\text{ mA}, \quad I_2 = -1\text{ mA}$$

- Solving for  $I_3$ :

$$I_3 = -10\text{ mA} + 1\text{ mA}$$


$$I_3 = -9\text{ mA}$$

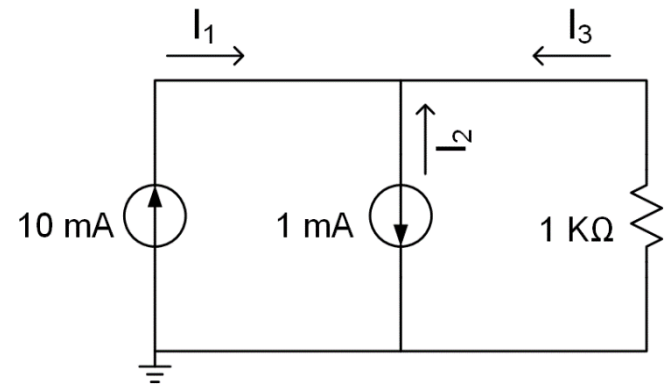- The negative sign indicates that  $I_3$  flows in the opposite direction of what was assumed




# Kirchhoff's Voltage Law - KVL

10

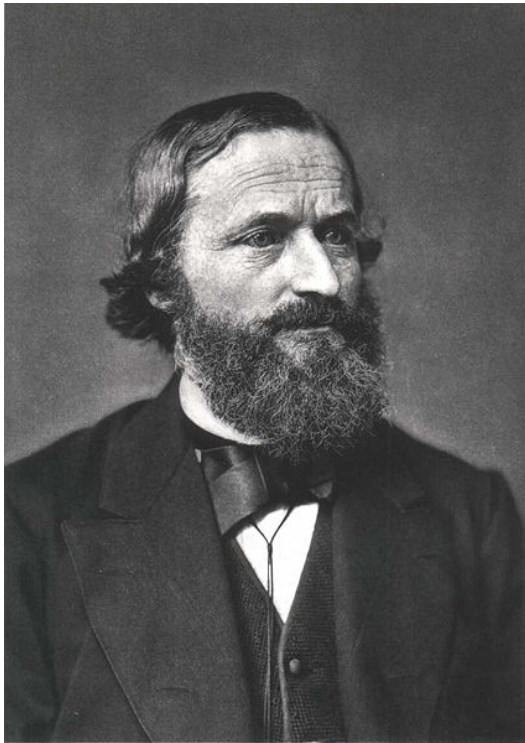

Gustav Kirchhoff, 1824 – 1887

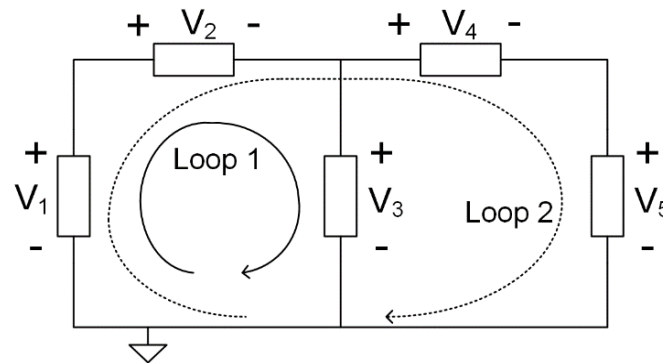**“The algebraic sum of voltage changes taken around any loop in a network is equal to zero.”**



KVL around Loop 1

$$V_1 - V_2 - V_3 = 0$$

KVL around Loop 2

$$V_1 - V_2 - V_4 - V_5 = 0$$


- Conservation of energy applied to electric circuits
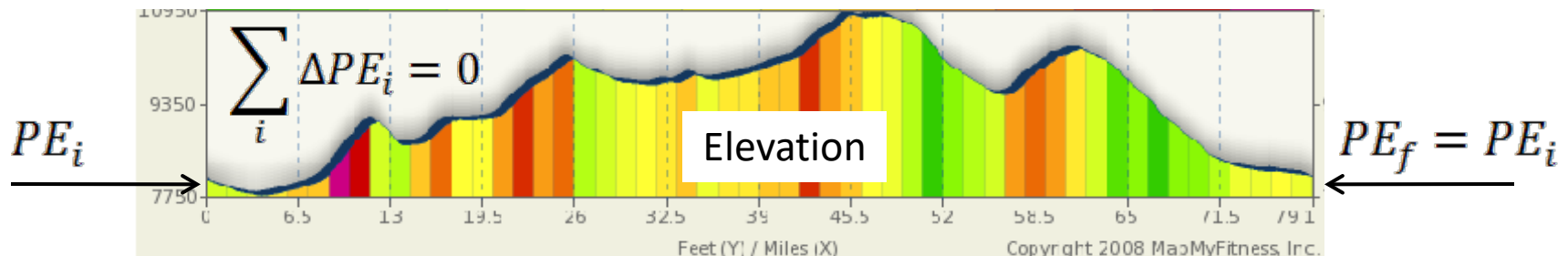
# KVL & the Conservation of Energy

11



- Voltage drops around a circuit are analogous to changes in potential energy while traversing a loop
- PE varies with elevation
  - Increases with each climb
  - Decreases with each descent
- Initial/final elevation & PE are the same
  - Sum of PE rises/drops around the loop is zero
  - Just like voltage drops around a circuit



# KVL – Example

12

- Determine the voltage,  $V_2$ , across the  $3.3\text{ k}\Omega$  resistor
- Applying KVL

$$V_1 - V_2 - V_3 = 0$$

$$V_2 = V_1 - V_3$$

- $V_1$  and  $V_3$  are known:


$$V_1 = 4\text{ V}, \quad V_3 = 12\text{ V}$$

- Solving for  $V_2$ :

$$V_2 = 4\text{ V} - 12\text{ V}$$

$$V_2 = -8\text{ V}$$

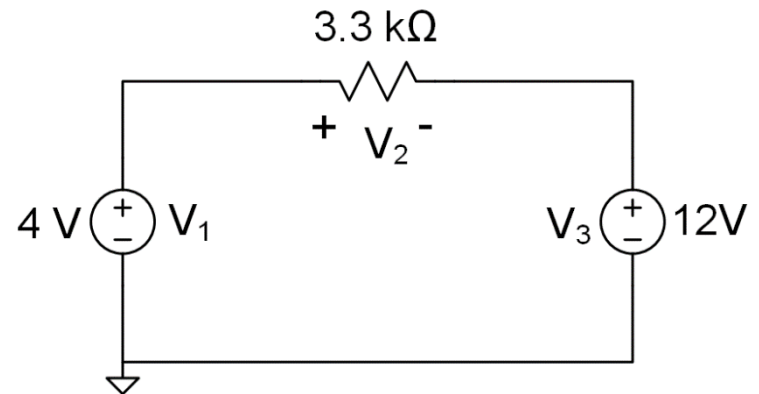- The negative sign indicates that the polarity of  $V_2$  is the opposite of what was assumed




# Kirchhoff's Voltage Law - KVL

13
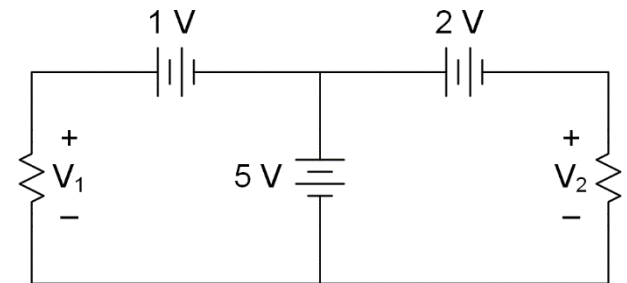
## Exercise

- Apply KVL to determine  $V_1$  and  $V_2$  in the following circuit.



# Kirchhoff's Current Law - KCL

14

## Exercise

- Apply KCL to determine all unknown branch currents and node voltages in the following circuit.

