

SECTION 2: RESISTIVE CIRCUIT ANALYSIS I

ENGR 201 – Electrical Fundamentals I

2

Resistance & Conductance

Resistance

3

□ **Resistance**

- The degree to which a circuit element opposes the flow of electrical current

□ Schematic symbol:




- Units: ohms (Ω)
- May be discrete, intentional circuit components, or parasitic resistance of wires, cables, interconnects, etc.

Resistance – Fluid Analogy

4

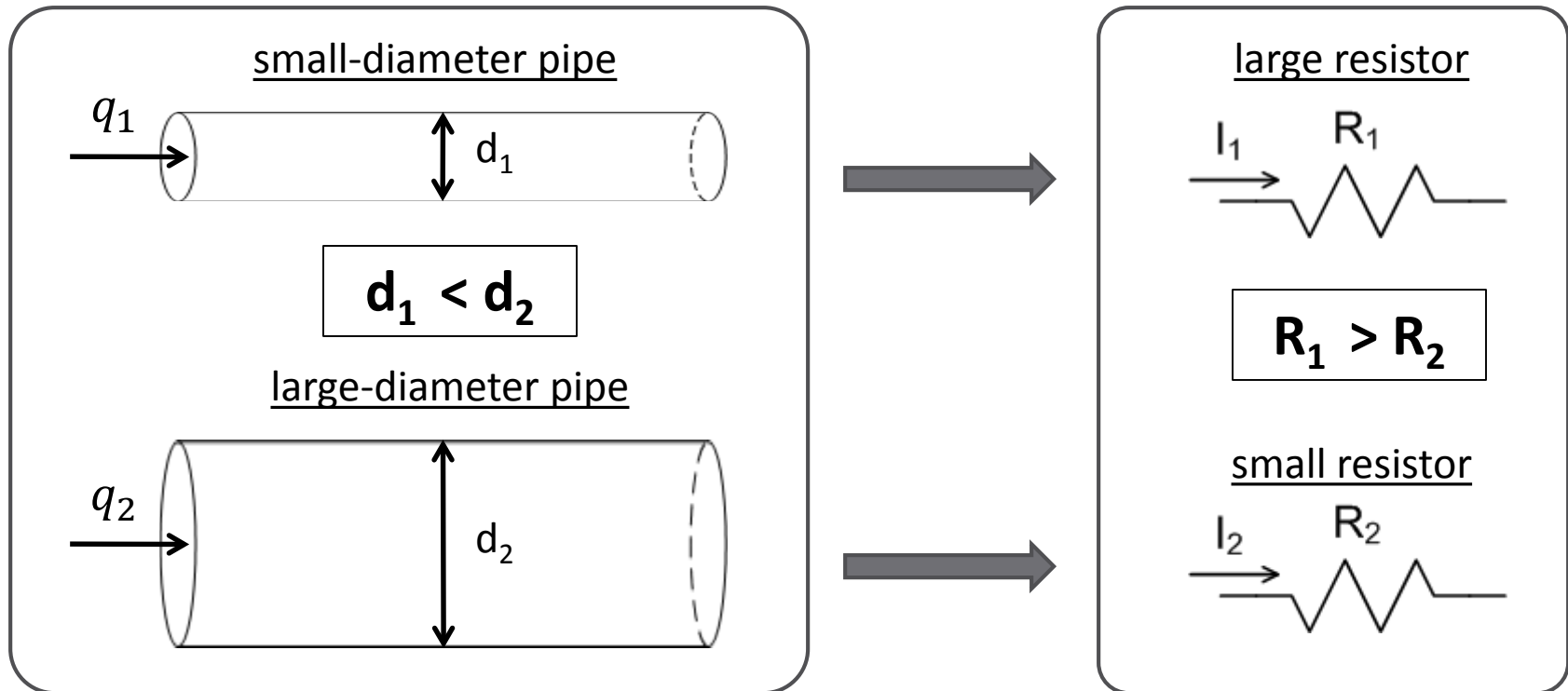
- Electrical resistance is analogous to the resistance of a pipe to fluid flow due to friction



Resistance – Thermal Analogy

5

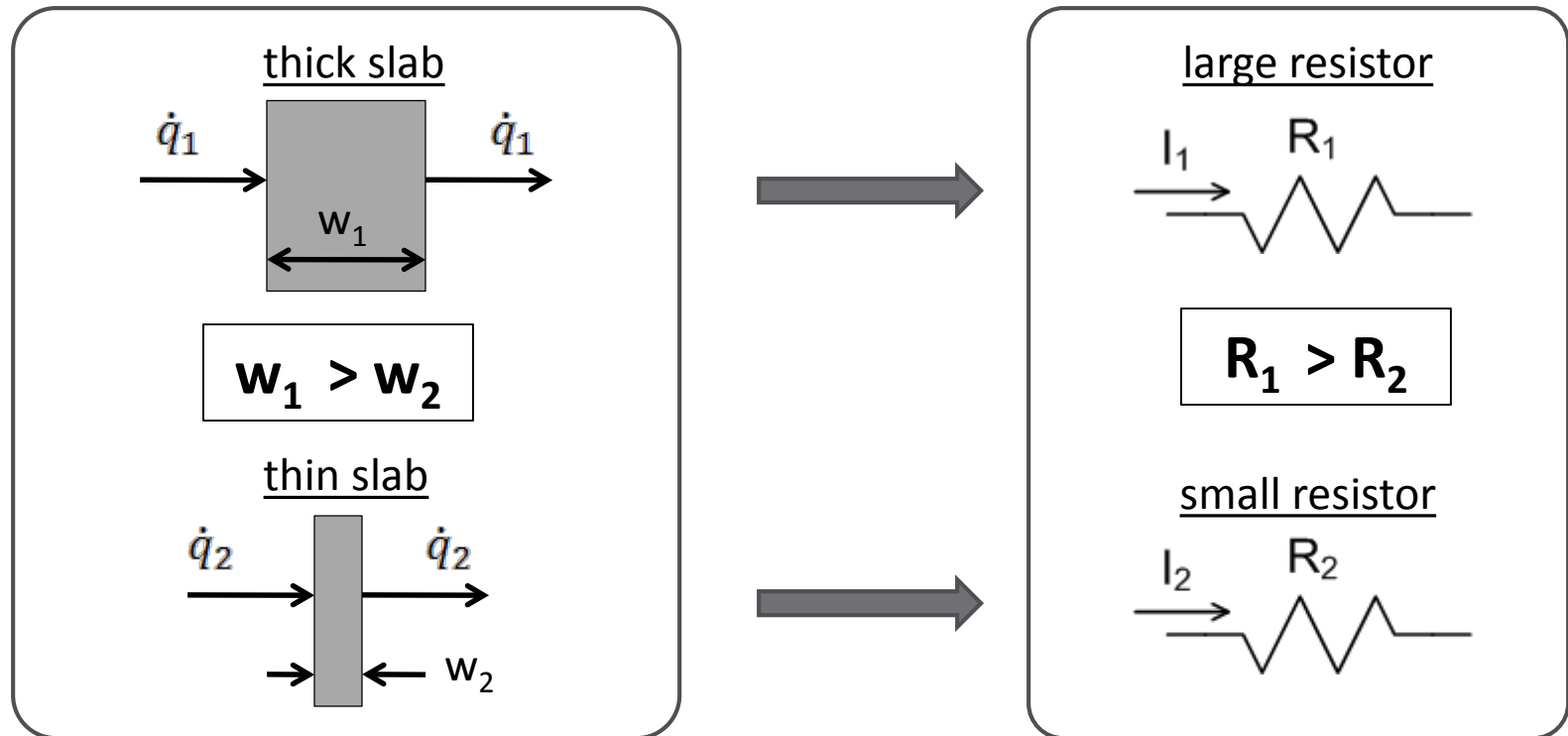- Electrical resistance is analogous to the resistance of heat conduction through a solid




Conductance

6

- Electrical **conductance** is the degree to which a circuit element allows the flow of electrical current
- Conductance is the **inverse of resistance**

$$G = \frac{1}{R}$$

- Schematic symbol:

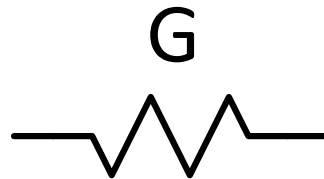

- Units: **siemens** or **mhos** (S or Ω^{-1})

Real Resistors





7

- Resistors for use in electronic circuits come in many shapes and sizes depending on their target application
- Size primarily determined by power handling capability
 - ▣ Larger resistors can dissipate more power
- Two primary form factors:
 - ▣ ***Axial lead*** resistors
 - ▣ ***Chip*** resistors


Axial Lead resistors

8

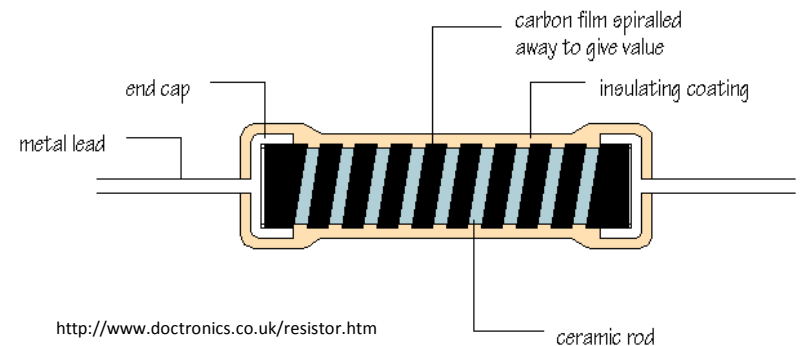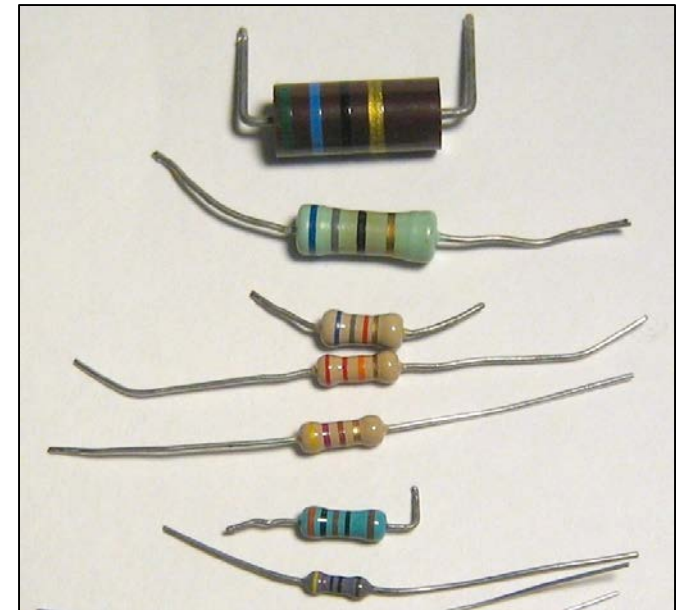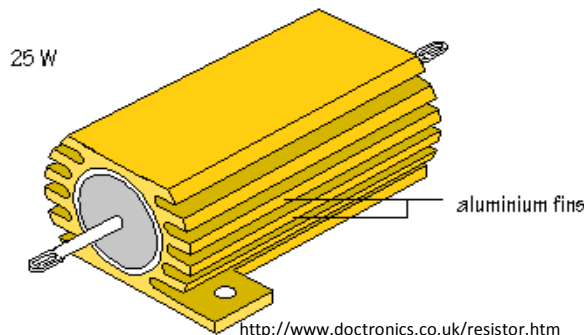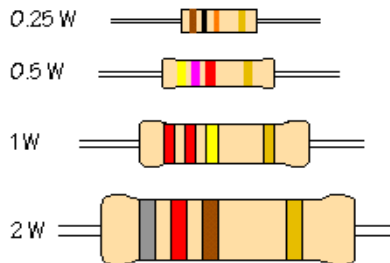- Cylindrical resistive component with wire leads extending from each end
- Used with **through-hole technology** printed circuit boards (PCB's)
 - ▣ Useful for prototyping
 - ▣ Size varies with power handling capacity



Resistor Color Code

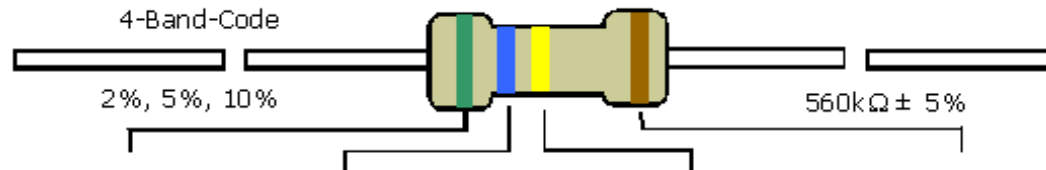

COLOR	1st BAND	2nd BAND	3rd BAND	MULTIPLIER	TOLERANCE
Black	0	0	0	1Ω	
Brown	1	1	1	10Ω	± 1% (F)
Red	2	2	2	100Ω	± 2% (G)
Orange	3	3	3	1KΩ	
Yellow	4	4	4	10KΩ	
Green	5	5	5	100KΩ	±0.5% (D)
Blue	6	6	6	1MΩ	±0.25% (C)
Violet	7	7	7	10MΩ	±0.10% (B)
Grey	8	8	8		±0.05%
White	9	9	9		
Gold				0.1	± 5% (J)
Silver				0.01	± 10% (K)




http://www.elexp.com/t_resist.htm

Chip Resistors

10

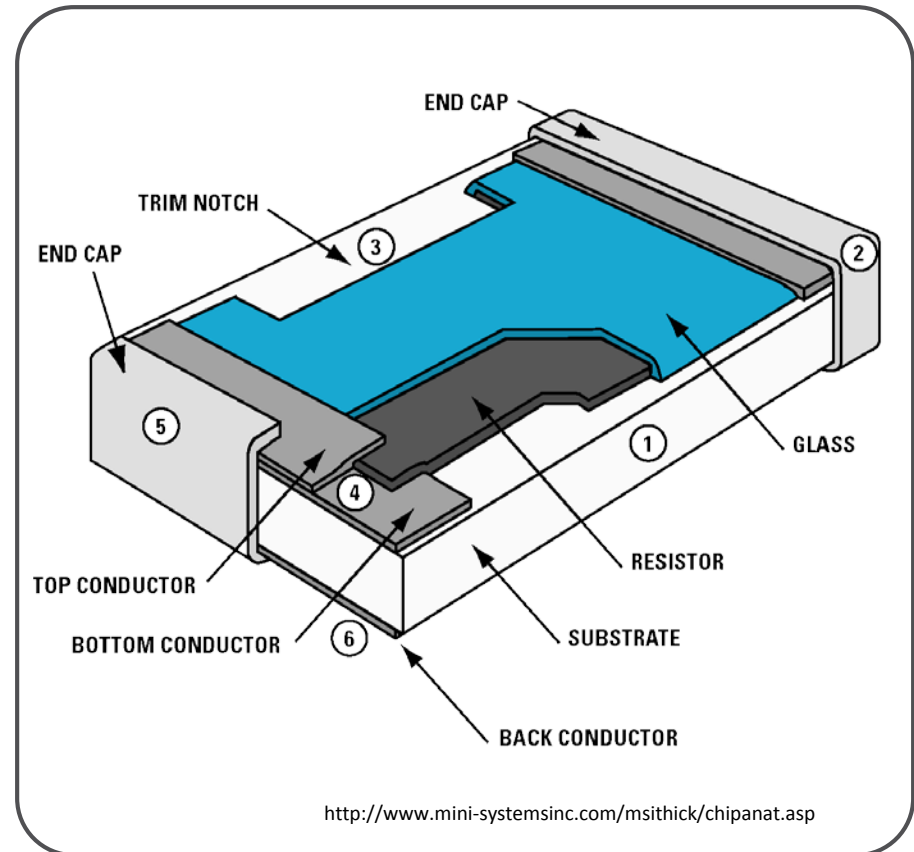- Small rectangular footprint
 - ▣ 0805 – 0.080" x 0.050"
 - ▣ 0603 – 0.060" x 0.030"
 - ▣ 0402 – 0.040" x 0.020"
 - ▣ 0201 – 0.020" x 0.010"
- Used with **surface-mount technology** PCB's
- More common than axial lead in modern electronics



11

Ohm's Law


Ohm's Law

12



Georg Simon Ohm, 1789 – 1854

$$I = \frac{V}{R}$$

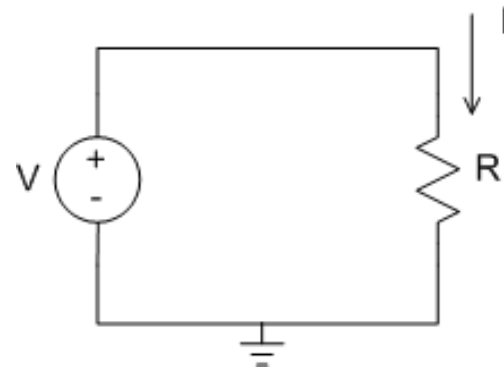


“The current through a resistor is proportional to the voltage across the resistor and inversely proportional to the resistance.”

Ohm's Law – said differently

13

$$V = I \cdot R$$

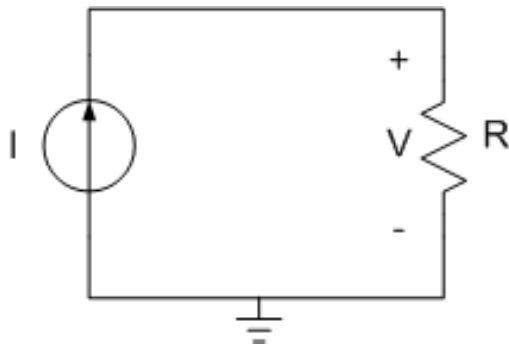


Georg Simon Ohm, 1789 – 1854

“The voltage across a resistor is proportional to the current through the resistor and proportional to the resistance.”


Ohm's Law – fluid analogy

14

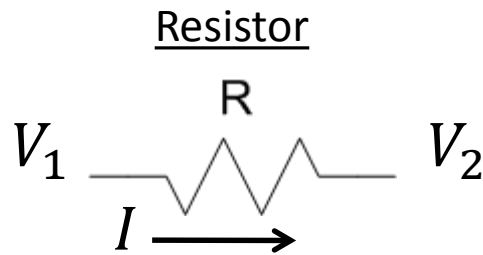- **Voltage** is analogous to **pressure**
 - ▣ Driving potentials
- Electrical **current** is analogous to **flow rate**
- A pipe carrying fluid has some resistance determined by physical characteristics (length, diameter, roughness, etc.)


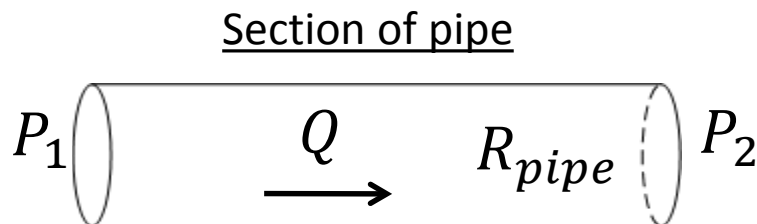
$$I \propto (V_1 - V_2), \quad I \propto \frac{1}{R}$$
$$(V_1 - V_2) \propto I, \quad (V_1 - V_2) \propto R$$




$$Q \propto (P_1 - P_2), \quad Q \propto \frac{1}{R_{pipe}}$$
$$(P_1 - P_2) \propto Q, \quad (P_1 - P_2) \propto R_{pipe}$$


Ohm's Law – thermal analogy

15

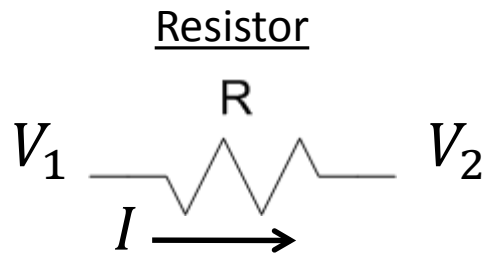- **Voltage** is analogous to **temperature**
 - ▣ Driving potentials
- Electrical **current** is analogous to **heat flux**
- A solid slab or wall has some thermal resistance determined by physical characteristics (thickness, material properties, etc.)


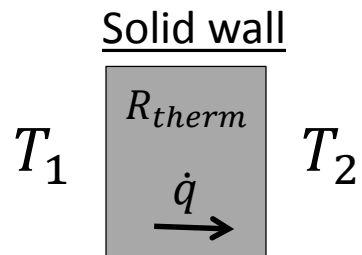
$$I \propto (V_1 - V_2), \quad I \propto \frac{1}{R}$$
$$(V_1 - V_2) \propto I, \quad (V_1 - V_2) \propto R$$



$$\dot{q} \propto (T_1 - T_2), \quad \dot{q} \propto \frac{1}{R_{therm}}$$
$$(T_1 - T_2) \propto \dot{q}, \quad (T_1 - T_2) \propto R_{therm}$$

Power in Resistors

16

- Resistors **dissipate** power
- Rate of power dissipation given by

$$P = V \cdot I$$

- According to Ohm's law


$$V = I \cdot R \quad \text{and} \quad I = V/R$$

- So **for resistors (only)**, power is given by

$$P = I^2 R$$

and

$$P = \frac{V^2}{R}$$

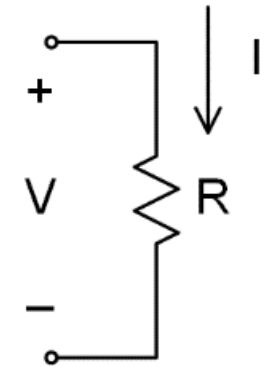


17

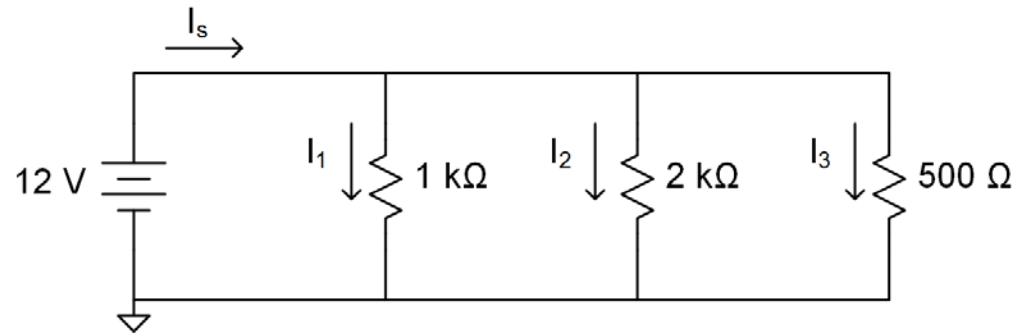Example Problems

Find:

- ▣ I_1 , I_2 , I_3 , and I_s .
- ▣ The power dissipated by each resistor three different ways.
- ▣ The power supplied by the source.




How much current does a 50 W incandescent lightbulb draw? What is its resistance?

The following circuit represents a battery connected to a load through a long wire.

How much current flows through the wire to the load?

How much power is delivered to the load?

How much power is lost in the wire?

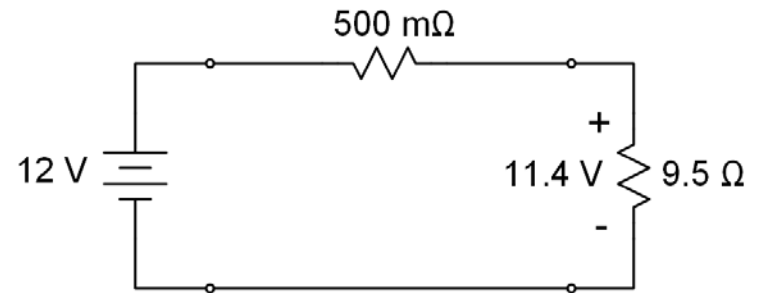

A 24 V source supplies 160 mA to a resistive load. How much power is delivered to the load? What is the equivalent resistance of the load?


23

Series & Parallel Circuits

Series Circuits

24

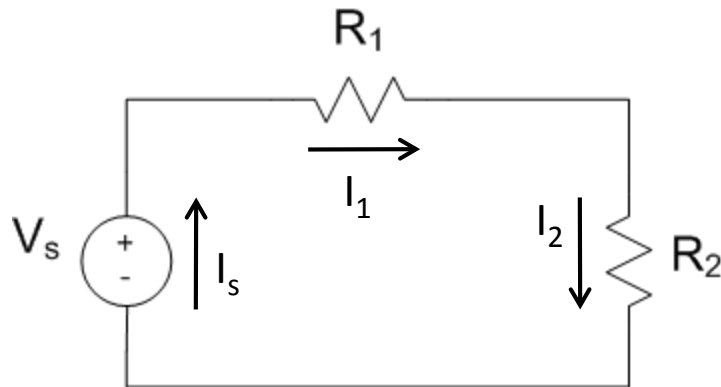- Series-connected components
 - ▣ Share **one common node**
 - Nothing else connected to that node
 - ▣ Connected end-to-end
 - ▣ **Equal current** through each component




Resistors, R_1 and R_2 , and voltage source, V_s , are all connected in **series**

$$I_s = I_1 = I_2$$

Parallel Circuits

25

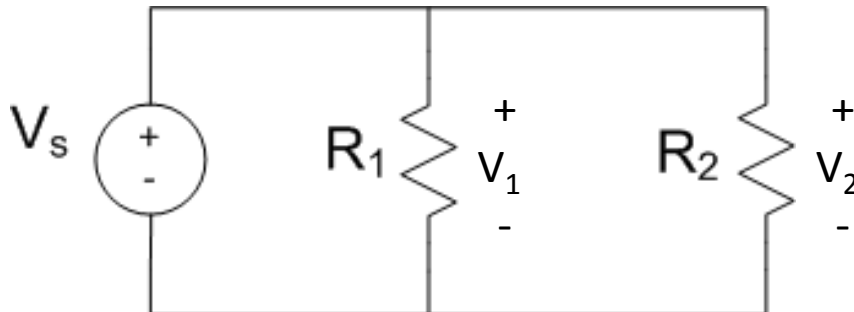- Components in **parallel**
 - ▣ Share **two common nodes**
 - ▣ Connected side-by-side
 - ▣ **Equal voltage** across each component




Resistors, R_1 and R_2 , and voltage source, V_s , are all connected in **parallel**

$$V_s = V_1 = V_2$$

Series Resistance

26

- **Resistances in series add**

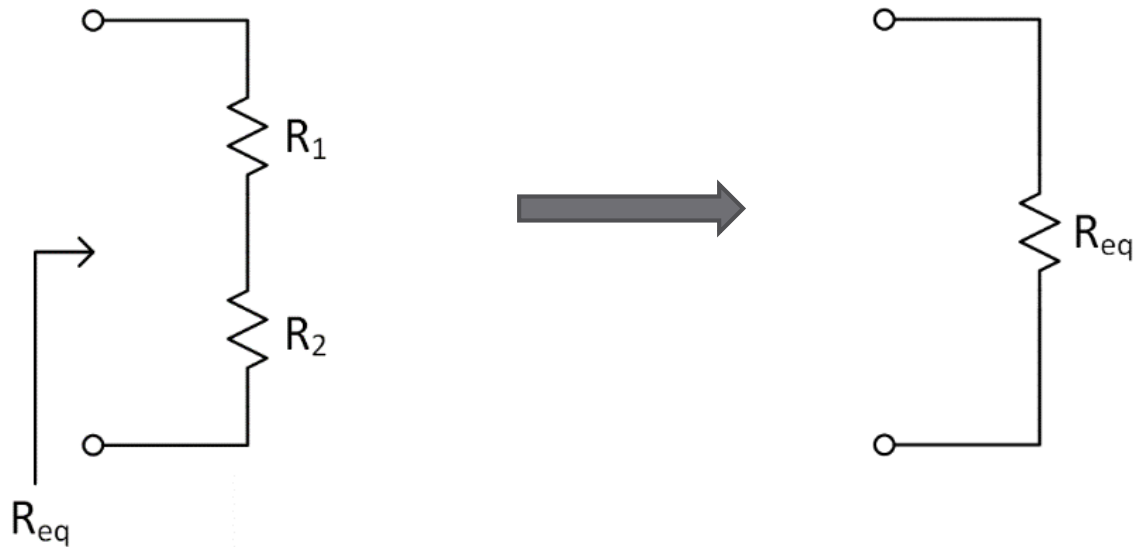

$$R_{eq} = R_1 + R_2$$


- In general,

$$R_{eq} = \sum R_i$$

Parallel Resistance

27

- **Conductances in parallel add**

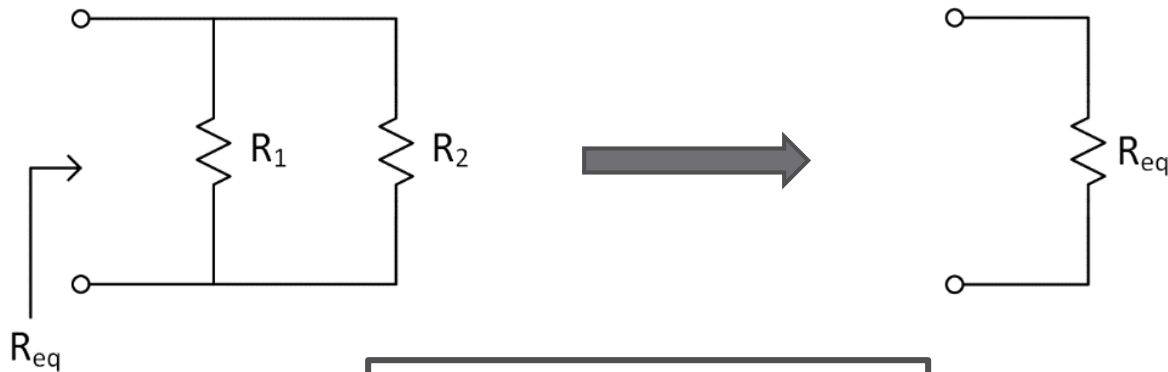

$$R_{eq} = \left(\sum \frac{1}{R_i} \right)^{-1}$$

- For **two** parallel resistors (only):

$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \frac{R_1 R_2}{R_1 + R_2}$$

28


Voltage & Current Dividers

Voltage Dividers

29

- Voltage across series resistors divides proportional to resistance
- Consider two series resistors:
 - ▣ Current through the resistors

$$I = \frac{V_s}{R_1 + R_2}$$

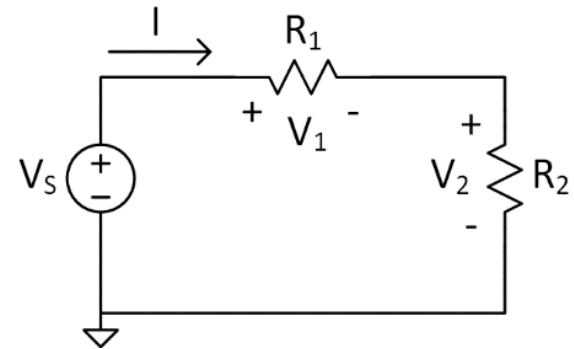

- ▣ Ohm's law gives the voltage across either resistor

$$V_n = IR_n$$

$$V_1 = \frac{V_s}{R_1 + R_2} R_1 = V_s \frac{R_1}{R_1 + R_2}$$

$$V_2 = \frac{V_s}{R_1 + R_2} R_2 = V_s \frac{R_2}{R_1 + R_2}$$

Voltage Dividers

30


- In general, the voltage across one in a series of resistors is given by

$$V_n = V_{total} \cdot \frac{R_n}{\sum R_i}$$

- For example:

$$V_3 = 16 V \frac{300 \Omega}{1 k\Omega + 200 \Omega + 300 \Omega + 100 \Omega}$$
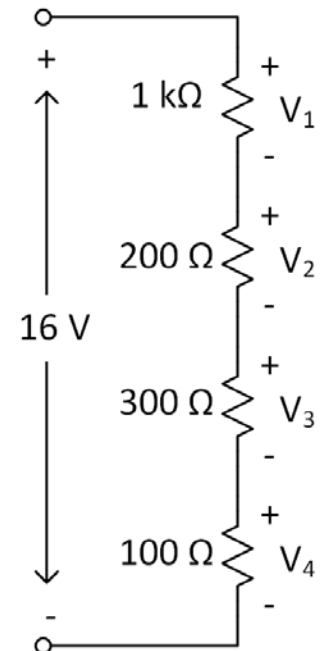
$$V_3 = 16 V \frac{300 \Omega}{1.6 k\Omega} = 3 V$$




Current Dividers

31

- Current through parallel-connected resistances divides proportional to conductance
- Consider two parallel resistors:
 - Voltage across the resistors
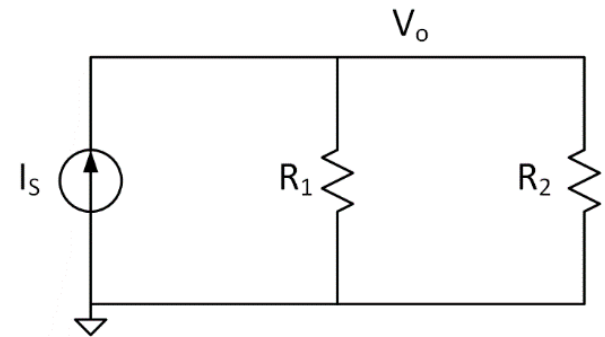
$$V_o = \frac{I_S}{G_1 + G_2} = \frac{I_S}{\frac{1}{R_1} + \frac{1}{R_2}} = I_S \frac{R_1 R_2}{R_1 + R_2}$$



- Ohm's law gives the current through either resistor

$$I_n = \frac{V_o}{R_n}$$

$$I_1 = \frac{I_S}{R_1} \frac{R_1 R_2}{R_1 + R_2} = I_S \frac{R_2}{R_1 + R_2}$$

$$I_2 = \frac{I_S}{R_2} \frac{R_1 R_2}{R_1 + R_2} = I_S \frac{R_1}{R_1 + R_2}$$

Current Dividers

32

- Current through one of **two** parallel resistors is given by

$$I_1 = I_{total} \cdot \frac{R_2}{R_1 + R_2}$$

$$I_2 = I_{total} \cdot \frac{R_1}{R_1 + R_2}$$

- ▣ One of the two resistors may be a parallel combination of multiple resistors
- More generally, expressed in terms of **conductance**
 - ▣ Applies to any number of parallel resistances

$$I_n = I_{total} \cdot \frac{G_n}{\Sigma G_i}$$

Current Dividers

33

- For example, determine I_1
- First, combine the $300\ \Omega$ and $100\ \Omega$ resistors in parallel

$$R_{eq} = \left(\frac{1}{300\ \Omega} + \frac{1}{100\ \Omega} \right)^{-1} = 75\ \Omega$$



- Next, apply the current divider equation:

$$I_1 = I_{total} \frac{R_2}{R_1 + R_2}$$

$$I_1 = 22\ A \frac{75\ \Omega}{200\ \Omega + 75\ \Omega}$$


$$I_1 = 6\ A$$

Current Dividers

34

□ Or, using conductances:
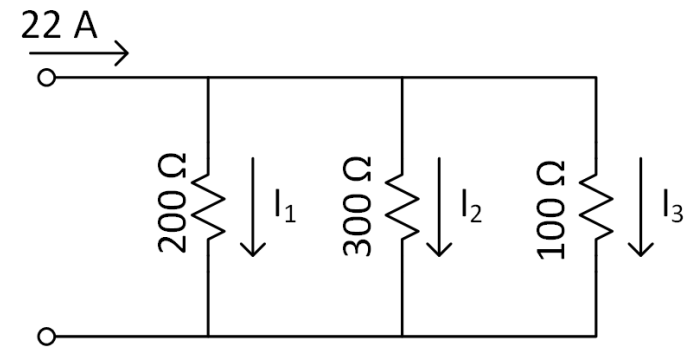
$$I_1 = 22 A \frac{\frac{1}{200 \Omega}}{\frac{1}{200 \Omega} + \frac{1}{300 \Omega} + \frac{1}{100 \Omega}}$$



$$I_1 = 22 A \cdot \frac{5 mS}{5 mS + 3.33 mS + 10 mS}$$


$$I_1 = 22 A \cdot 0.2727$$

$$I_1 = 6 A$$


35

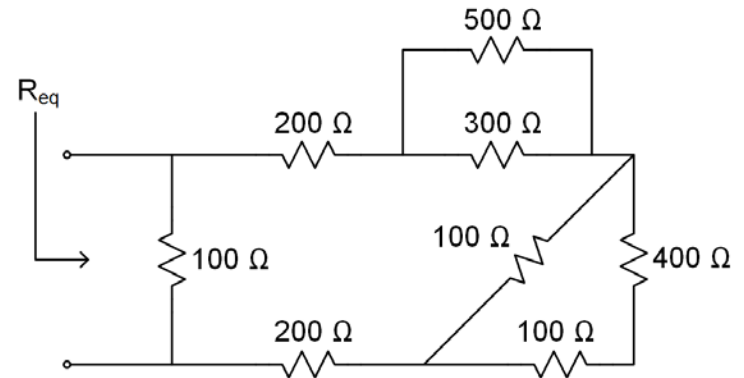Example Problems


Determine the equivalent input resistance, R_{eq} , for the following network.



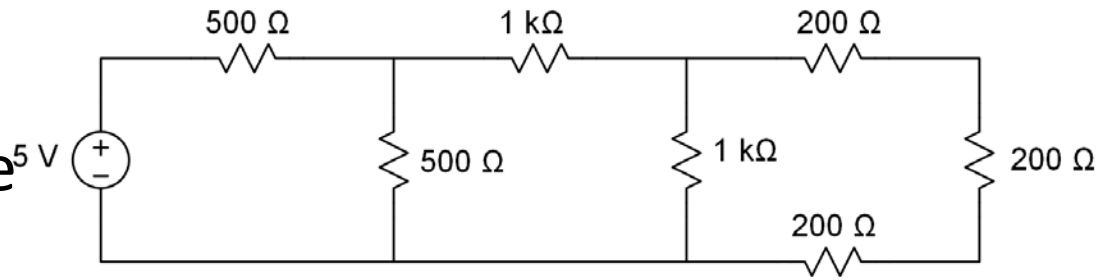
How much power is delivered by the voltage source in the following network?




Determine V_1 , V_2 , V_3 , and V_4

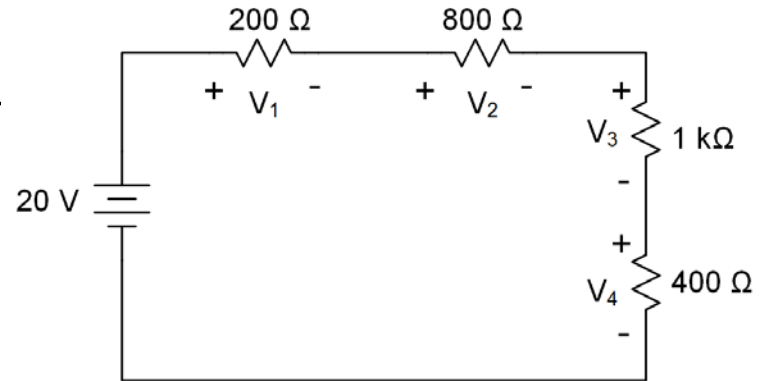

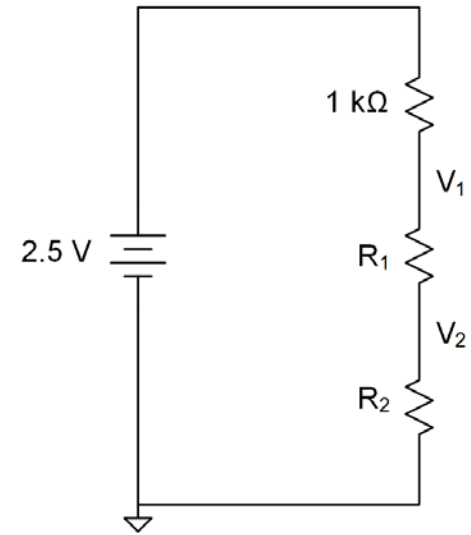Determine R_1 and R_2 , such that $V_1 = 2\text{ V}$, and $V_2 = 1.25\text{ V}$.



Determine V_o in the following circuit.

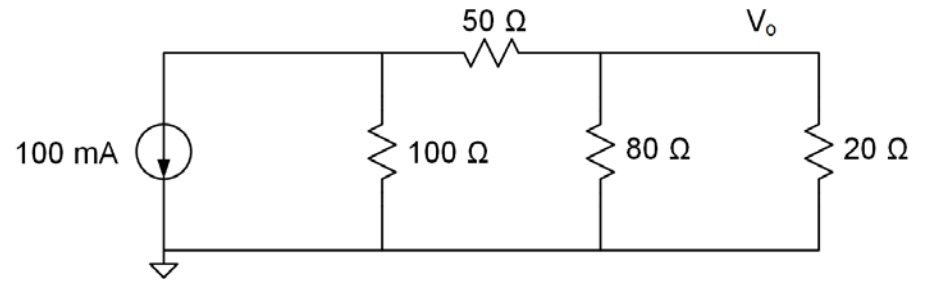


43

Kirchhoff's Laws

Kirchhoff's Current Law - KCL


44

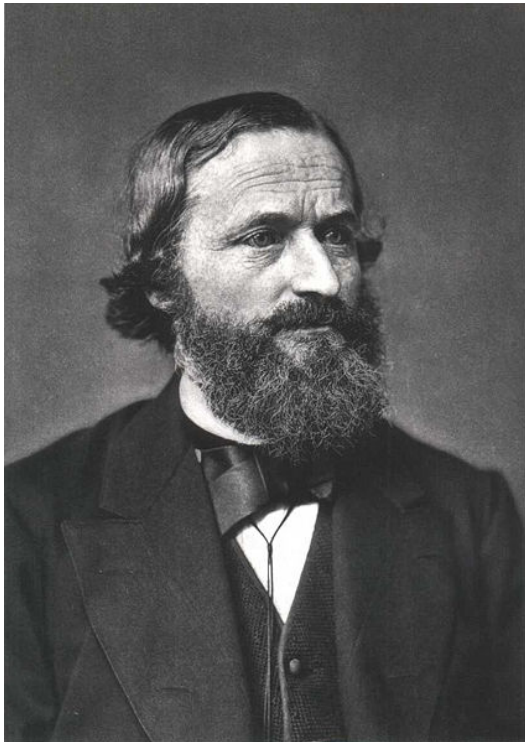

Gustav Kirchhoff, 1824 – 1887

“The algebraic sum of currents entering any node must be zero.”

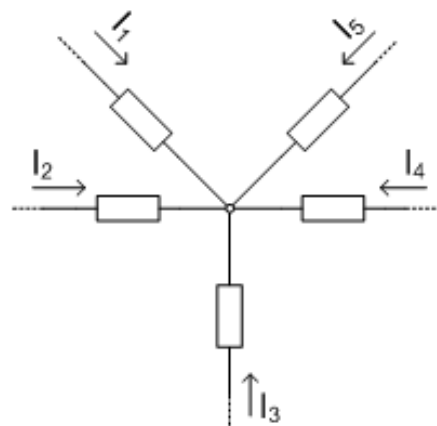- Charge cannot accumulate in a node
- What flows in, must flow out



$$I_1 + I_2 + I_3 + I_4 + I_5 = 0$$


$$\sum_i I_i = 0$$

- Analogous to the conservation of mass

KCL & the Conservation of Mass

45

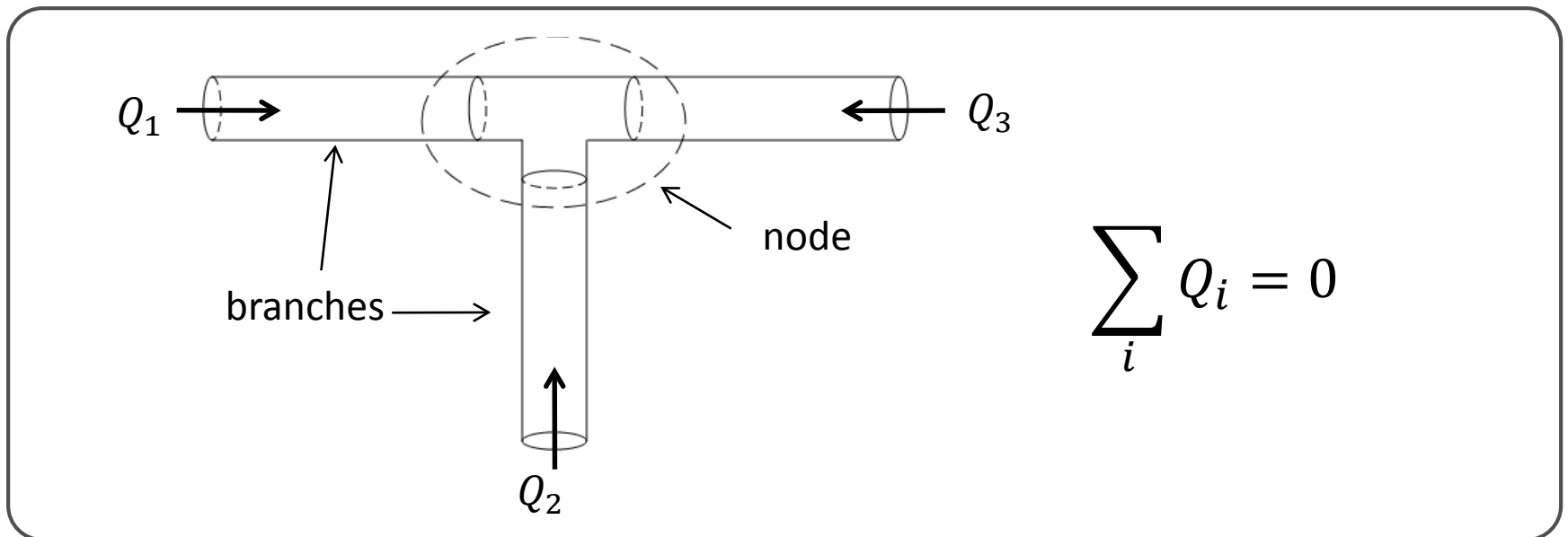- Consider fluid-carrying pipes connected in a Tee
 - ▣ Tee connector is analogous to electrical **node**
 - ▣ Pipes analogous to **branches**
- According to the conservation of mass, what flows in must flow out
 - ▣ ***Sum of the flow rates must be zero***



KCL - Example

46

- Determine the current through the $1\text{ k}\Omega$ resistor, I_3
- Applying KCL

$$I_1 + I_2 + I_3 = 0$$

$$I_3 = -I_1 - I_2$$

- I_1 and I_2 are known:


$$I_1 = 10\text{ mA}, \quad I_2 = -1\text{ mA}$$

- Solving for I_3 :

$$I_3 = -10\text{ mA} + 1\text{ mA}$$


$$I_3 = -9\text{ mA}$$

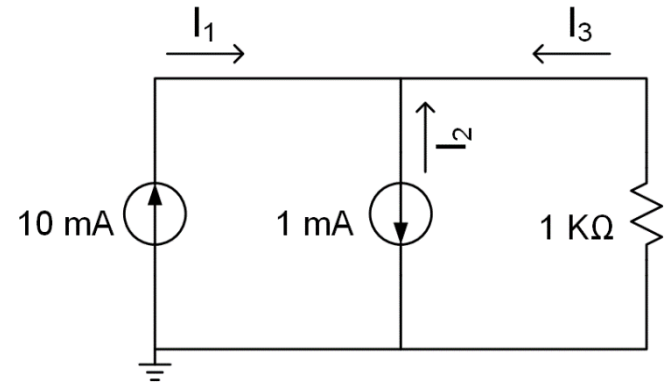- The negative sign indicates that I_3 flows in the opposite direction of what was assumed




Kirchhoff's Voltage Law - KVL

47

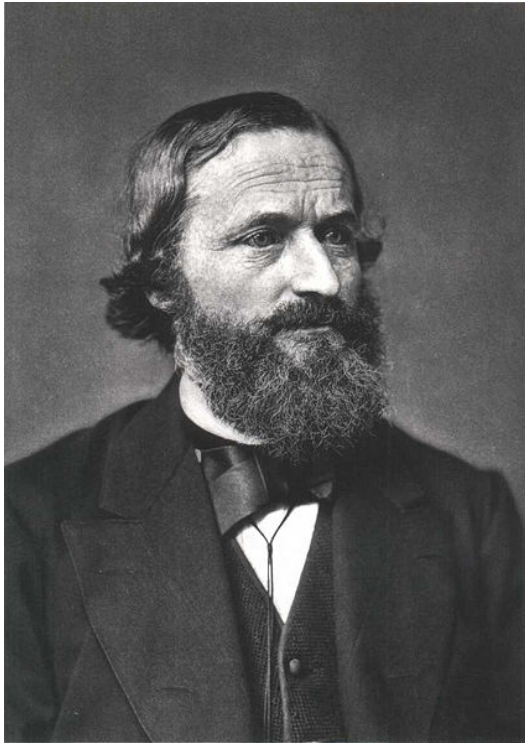

Gustav Kirchhoff, 1824 – 1887

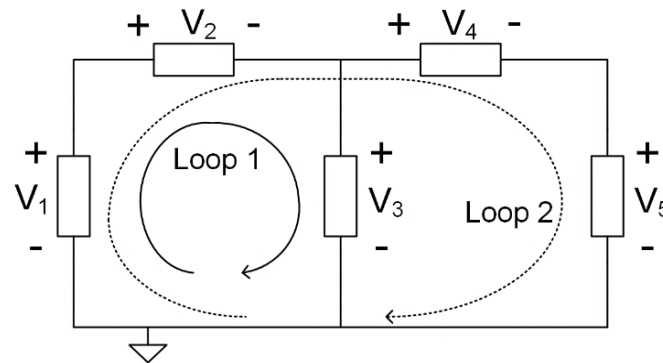“The algebraic sum of voltage changes taken around any loop in a network is equal to zero.”



KVL around Loop 1

$$V_1 - V_2 - V_3 = 0$$

KVL around Loop 2

$$V_1 - V_2 - V_4 - V_5 = 0$$


- Conservation of energy applied to electric circuits

KVL & the Conservation of Energy

48



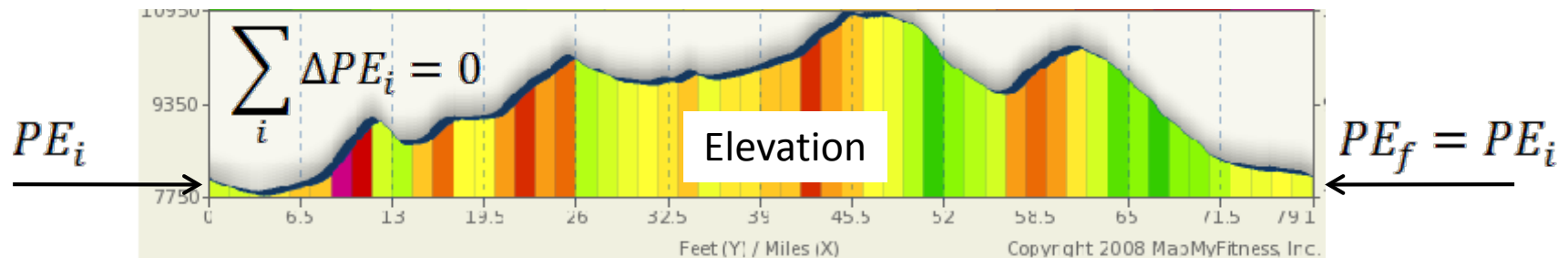- Voltage drops around a circuit are analogous to changes in potential energy while traversing a loop
- PE varies with elevation
 - Increases with each climb
 - Decreases with each descent
- Initial/final elevation & PE are the same
 - Sum of PE rises/drops around the loop is zero
 - Just like voltage drops around a circuit



KVL – Example

49

- Determine the voltage, V_2 , across the $3.3\text{ k}\Omega$ resistor
- Applying KVL

$$V_1 - V_2 - V_3 = 0$$

$$V_2 = V_1 - V_3$$

- V_1 and V_3 are known:


$$V_1 = 4\text{ V}, \quad V_3 = 12\text{ V}$$

- Solving for V_2 :

$$V_2 = 4\text{ V} - 12\text{ V}$$

$$V_2 = -8\text{ V}$$

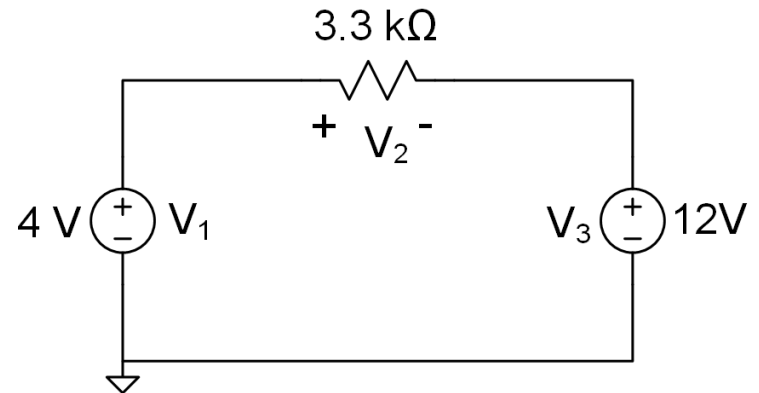- The negative sign indicates that the polarity of V_2 is the opposite of what was assumed



50


Delta and Wye Networks

Delta and Wye Networks


51

- Circuits may comprise components that are connected ***neither in series nor in parallel***, e.g.:
 - Wheatstone bridge circuit
 - Three-phase AC power systems
 - Motors
 - Generators
 - Transformers
- Often, these include ***wye*** and/or ***delta*** networks


Bridge network

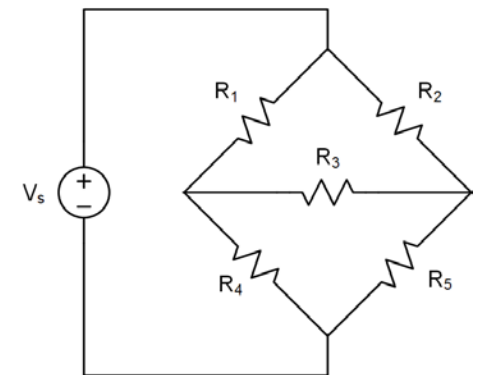

Wye network

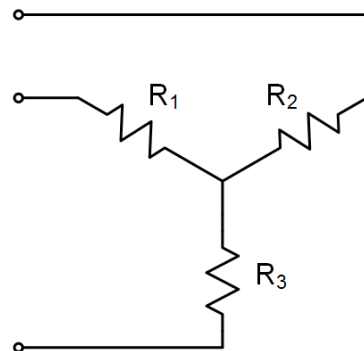


Delta network

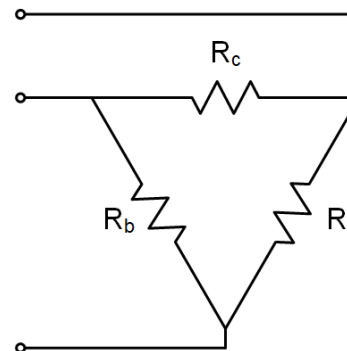


Y- Δ Transformations

52

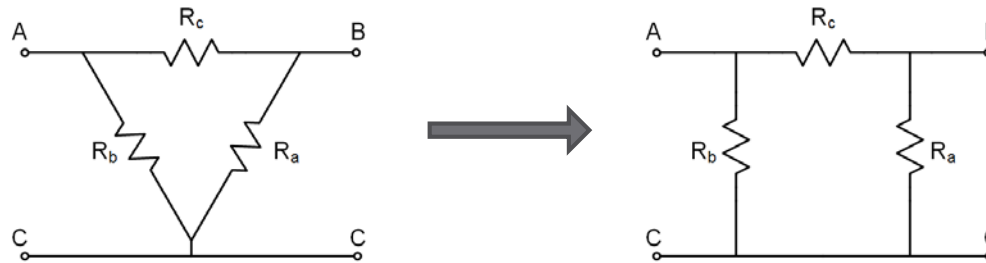- Circuit analysis is often simplified if we are able to convert between Y and Δ networks
- To aid in developing the Y- Δ conversion relationships, we can redraw the Δ network as a Π network:




- And the Y network as a T network:

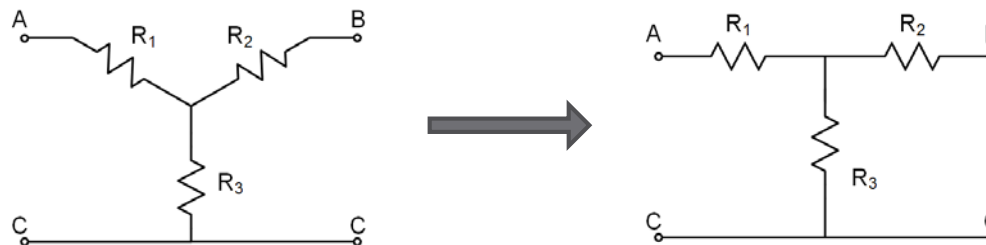

Δ -to-Y Conversion

53

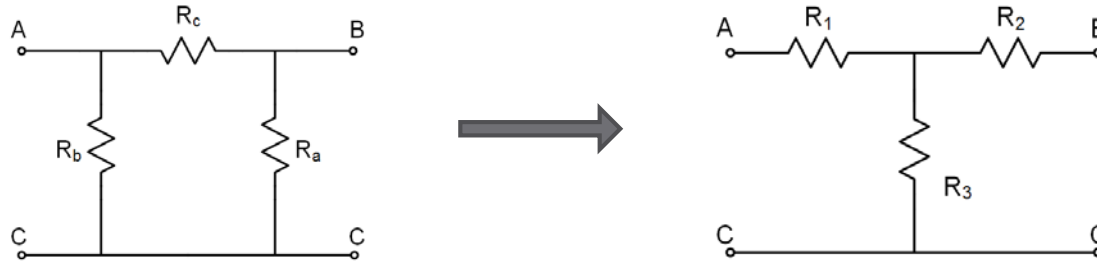

- For a Y network and Δ network to be equivalent, they must have equal resistance between corresponding terminals

- Between node A and node C:

$$R_{AC_Y} = R_1 + R_3 = R_{AC_\Delta} = R_b \parallel (R_a + R_c)$$

$$R_1 + R_3 = \frac{R_b(R_a + R_c)}{R_a + R_b + R_c} \quad (1)$$


- Between B and C:

$$R_{BC_Y} = R_2 + R_3 = R_{BC_\Delta} = R_a \parallel (R_b + R_c)$$

$$R_2 + R_3 = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c} \quad (2)$$

Δ -to-Y Conversion

54

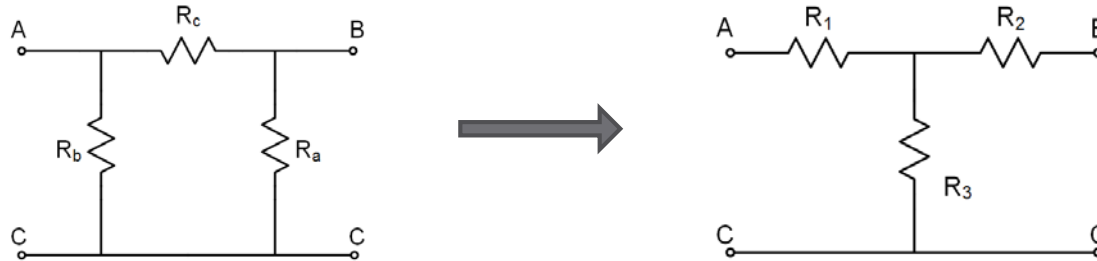

- ▣ Similarly, between nodes A and B:

$$R_{ABY} = R_1 + R_2 = R_{AB\Delta} = R_c \parallel (R_a + R_b)$$


$$R_1 + R_2 = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c} \quad (3)$$

- ▣ Subtracting (2) from (1) yields:

$$R_1 - R_2 = \frac{R_c(R_b - R_a)}{R_a + R_b + R_c} \quad (4)$$

Δ -to-Y Conversion

55

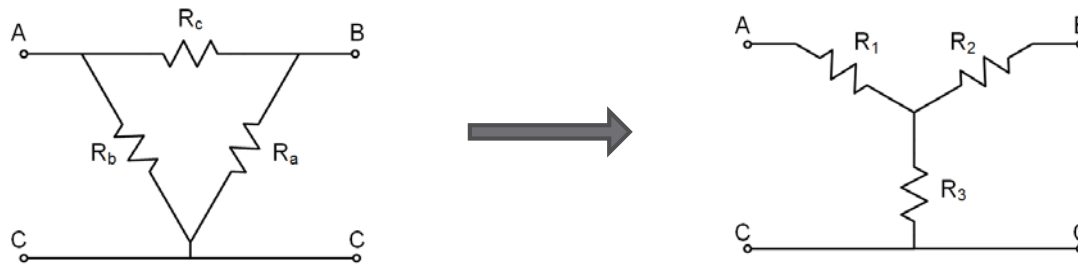

- Adding (4) to (3) gives an expression for R_1 :

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} \quad (5)$$

- Subtracting (4) from (3) gives


$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c} \quad (6)$$

- And, finally, subtracting (5) from (1) gives

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c} \quad (7)$$

Y-to-Δ Conversion

56

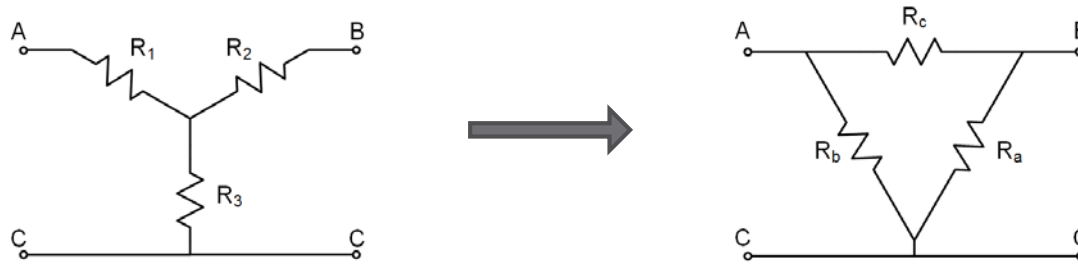

- We can derive a similar set of relationships for converting from a Y network to a Δ network

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

Y-Δ Transformations

57

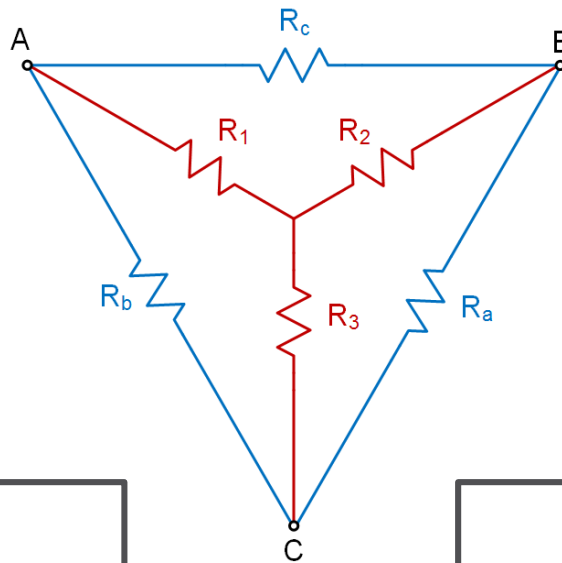Each resistor in the equivalent Y network is the product of the resistors in the two adjacent Δ branches, divided by the sum of the three Δ resistors



Each resistor in the equivalent Δ network is the sum of all possible products of Y resistors taken two at a time, divided by the opposite Y resistor

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$


58

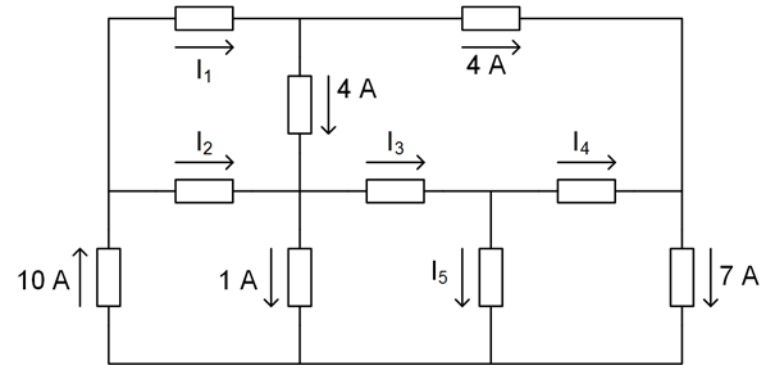Example Problems


Determine I_1 , I_2 , I_3 , I_4 , and I_5 .




Find V_1 , V_2 , and V_3 .

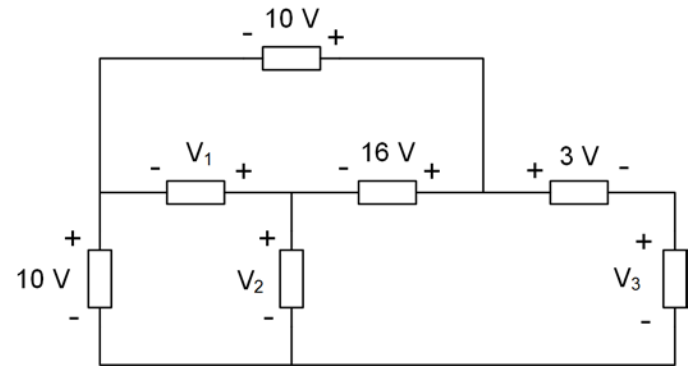

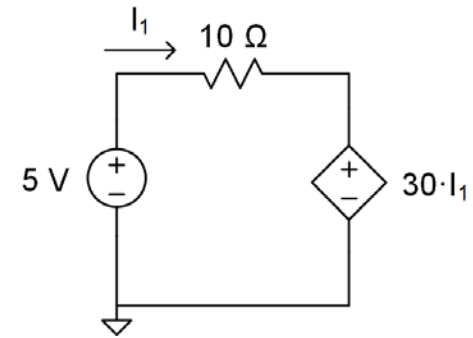
Determine the current through the circuit, I_1 .



Determine the voltage, V_1 .

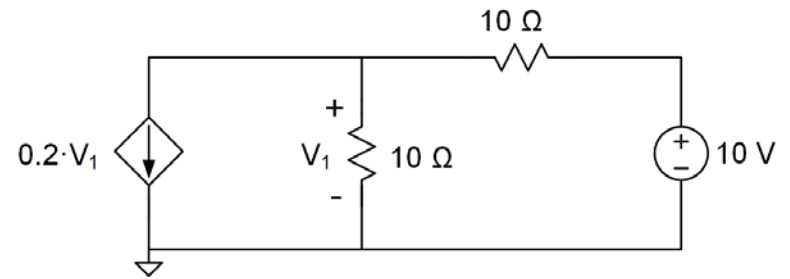

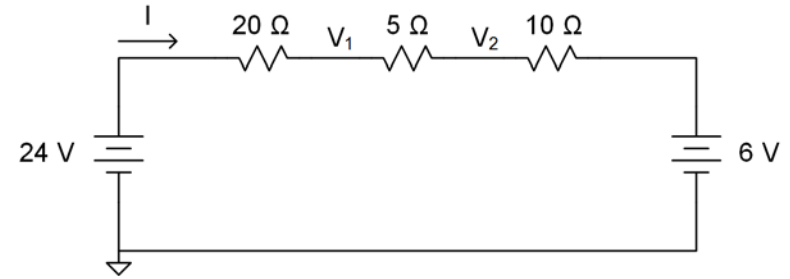Determine V_1 and V_2
in the following
circuit.



Determine I and V_1 in the following circuit.

