

SECTION 3: RESISTIVE CIRCUIT ANALYSIS II

ENGR 201 – Electrical Fundamentals I

2

Resistive Network Analysis

Circuit Analysis Methods

3

- Circuit analysis objective is to determine all:
 - ▣ ***Node voltages***
 - ▣ ***Branch currents***

- Circuit analysis tools:
 - ▣ Ohm's law
 - ▣ Kirchhoff's laws – KVL, KCL

- Circuit analysis methods:
 - ▣ ***Nodal analysis***
 - Systematic application of KCL
 - ▣ ***Mesh/loop analysis***
 - Systematic application of KVL

4

Nodal Analysis

Nodal Analysis

5

□ ***Nodal analysis***

- Systematic application of ***KCL***
- Generate a system of equations
 - Node voltages are the unknown variables
 - Number of equations equals number of unknown node voltages
- Solve equations to determine node voltages
- Apply Ohm's law to determine branch currents

Nodal Analysis – Step-by-Step Procedure


6

- 1) Identify and label all nodes in the circuit – distinguish known from unknown node voltages
- 2) Assign and label polarities of currents through all branches
- 3) Apply KCL at each node, using Ohm's Law to express branch currents in terms of node voltages
- 4) Solve the resulting simultaneous system of equations using substitution, calculator, Cramer's Rule, etc.
- 5) Use Ohm's Law and node voltages to determine branch currents

Nodal Analysis – Example


7

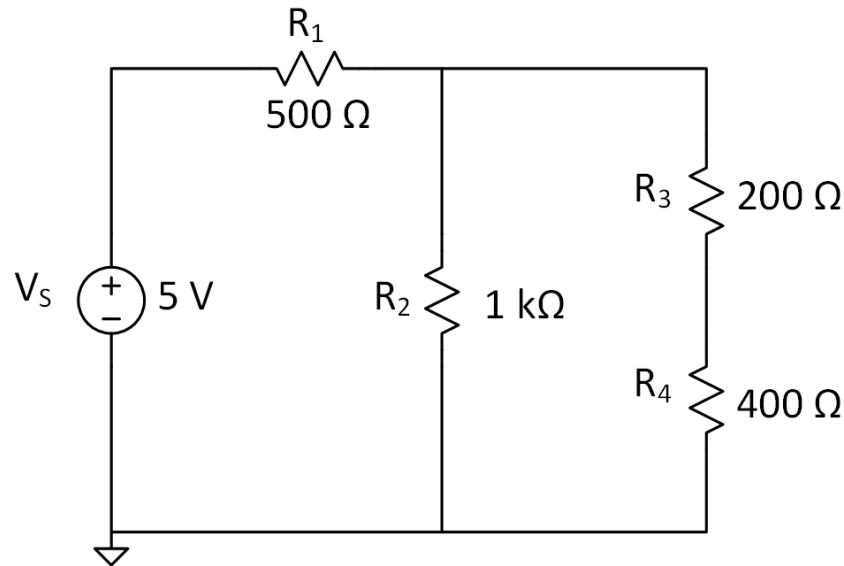- Apply nodal analysis to determine all node voltages and branch currents in the following circuit



Nodal Analysis – Step 1


8

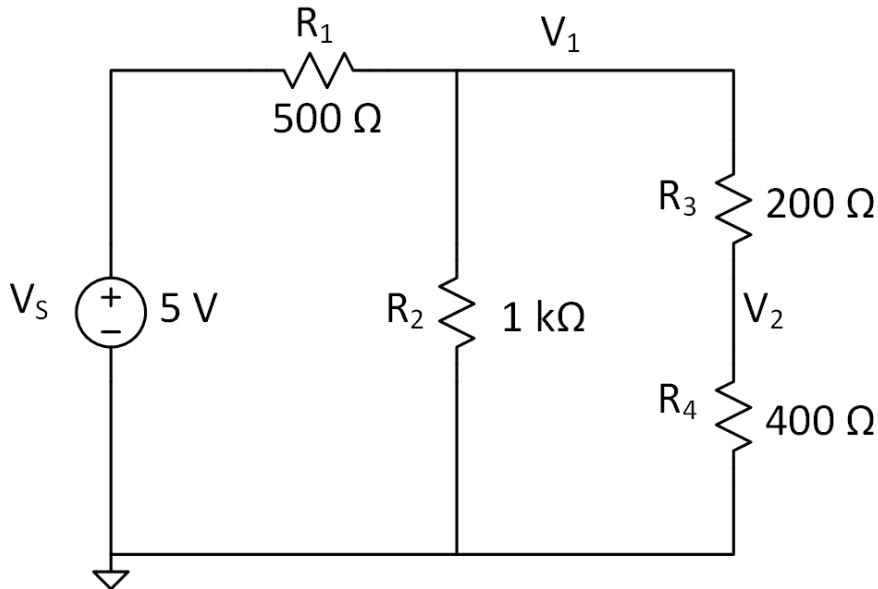

- **Step 1:** Identify and label all nodes in the circuit – distinguish known from unknown node voltages
 - V_s is a known node voltage (5 V)
 - V_1 and V_2 are unknown

Nodal Analysis – Step 2

9

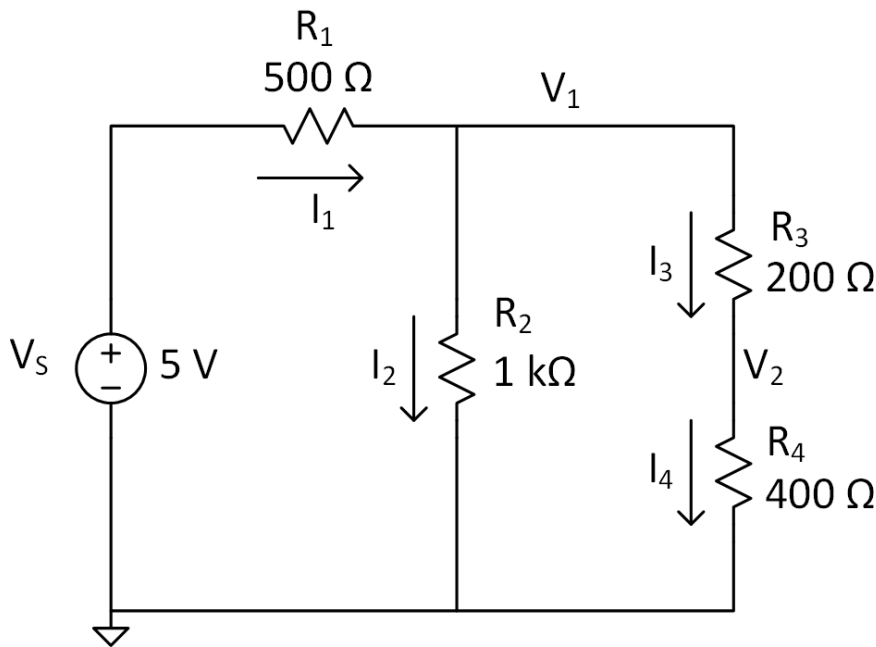


- **Step 2:** Assign and label polarities of currents through all branches
- ▣ Assumed polarities needn't be correct
 - Correct polarity given by the sign of the determined quantity

Nodal Analysis – Step 3

10

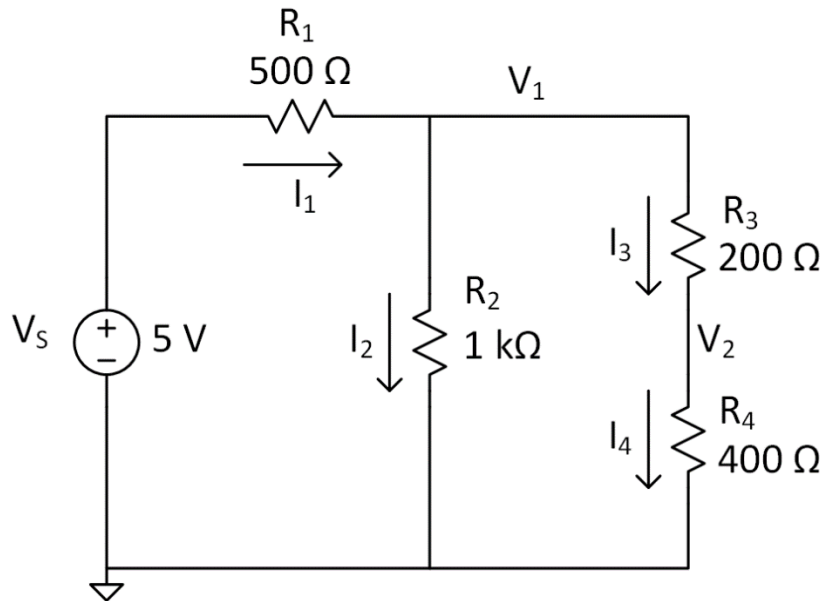- **Step 3:** Apply KCL at each node, using Ohm's Law to express branch currents in terms of node voltages



KCL at node 1

$$I_1 - I_2 - I_3 = 0$$

$$\frac{5V - V_1}{R_1} - \frac{V_1}{R_2} - \frac{V_1 - V_2}{R_3} = 0$$

KCL at node 2

$$I_3 - I_4 = 0$$

$$\frac{V_1 - V_2}{R_3} - \frac{V_2}{R_4} = 0$$

Nodal Analysis – Step 4

11

- **Step 4:** Solve the resulting system of equations
 - First, organize the equations

$$\begin{aligned} \frac{5V - V_1}{R_1} - \frac{V_1}{R_2} - \frac{V_1 - V_2}{R_3} &= 0 \\ \frac{V_1 - V_2}{R_3} - \frac{V_2}{R_4} &= 0 \end{aligned} \quad \longrightarrow \quad \begin{aligned} V_1 \left(-\frac{1}{R_1} - \frac{1}{R_2} - \frac{1}{R_3} \right) + V_2 \left(\frac{1}{R_3} \right) &= -\frac{5V}{R_1} \\ V_1 \left(\frac{1}{R_3} \right) + V_2 \left(-\frac{1}{R_3} - \frac{1}{R_4} \right) &= 0 \end{aligned}$$

- Solve using Gaussian elimination, Cramer's rule, or using calculator or computer
 - Put into matrix form for solution in calculator or MATLAB:

$$\begin{bmatrix} -\frac{1}{R_1} - \frac{1}{R_2} - \frac{1}{R_3} & \frac{1}{R_3} \\ \frac{1}{R_3} & -\frac{1}{R_3} - \frac{1}{R_4} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -\frac{5V}{R_1} \\ 0 \end{bmatrix} \quad \longrightarrow \quad \begin{bmatrix} -8mS & 5mS \\ 5mS & -7.5mS \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -10mA \\ 0 \end{bmatrix}$$

$$\mathbf{GV} = \mathbf{I}$$

Nodal Analysis – Step 5

12

- **Step 5:** Use Ohm's Law and node voltages to determine branch currents
 - ▣ Solution to system of equations yields node voltages:

$$V_1 = 2.14 V$$


$$V_2 = 1.43 V$$

- ▣ Branch currents are

$$I_1 = \frac{5V - V_1}{R_1} = \frac{5V - 2.14V}{500\Omega} = 5.71 mA$$

$$I_2 = \frac{V_1}{R_2} = \frac{2.14V}{1k\Omega} = 2.14 mA$$

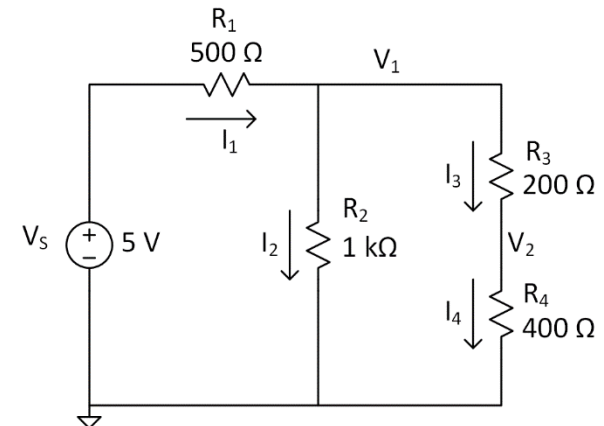
$$I_3 = I_4 = \frac{V_2}{R_4} = \frac{1.43V}{400\Omega} = 3.57 mA$$



Nodal Analysis

13

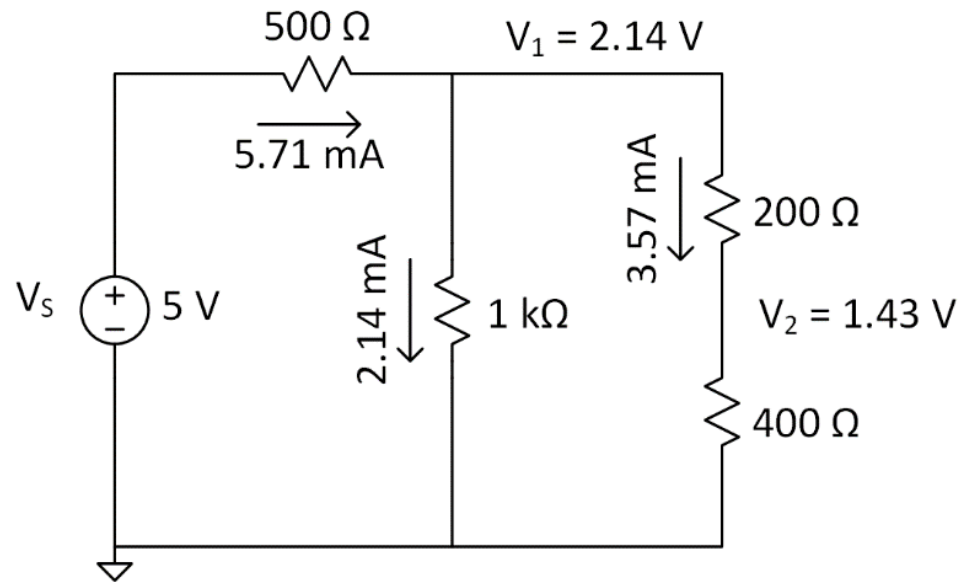- Nodal analysis yields all node voltages and branch currents




14

Supernodes

Nodal Analysis – Floating Voltage Sources

15

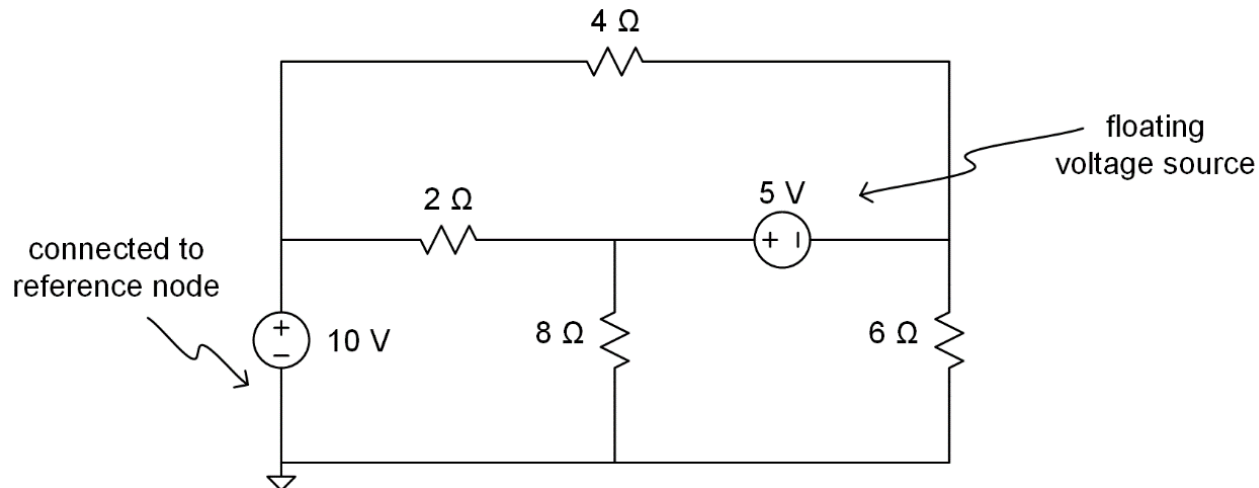- When performing nodal analysis on circuits with voltage sources, there are two possible scenarios:
 - ▣ Voltage source connected to the reference node
 - As in the last example
 - ▣ Voltage source is ***floating***
 - Both terminals connected to non-reference nodes



Nodal Analysis - Supernodes

16


- Floating voltage sources pose a problem
 - Cannot use Ohm's law to represent the current through the source
 - Ohm's law applies only to resistors

- Solution:
 - Form a ***supernode*** enclosing the source
 - Formed by two non-reference nodes
 - Apply KCL to the supernode
 - *One* equation for the *two* unknown nodes
 - Apply KVL to relate the voltages of the nodes forming the supernode
 - Providing the required additional equation

Supernode – Example

17

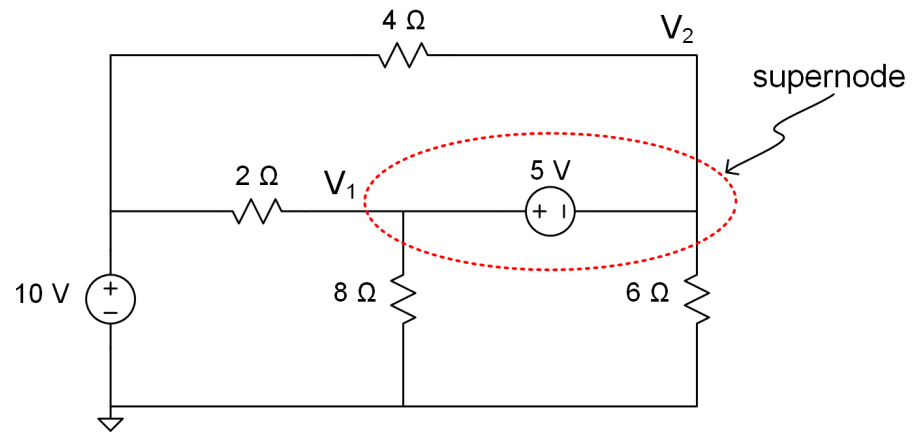- Nodes V_1 and V_2 form a supernode, enclosing the floating voltage source
- Circuit has two unknown node voltages, V_1 and V_2
 - System of two equations is required
- KCL will be applied at the supernode
 - Only one equation will result
- Additional required equation obtained by applying KVL to relate V_1 to V_2



Nodal Analysis with Supernodes – Step-by-Step


18

- 1) Identify and label all nodes in the circuit – distinguish known from unknown node voltages
- 2) Assign and label polarities of currents through all branches
- 3) Generate a system of equations
 - a) Apply KCL at each node and each supernode, using Ohm's Law to express branch currents in terms of node voltages
 - b) Apply KVL to relate the voltages of the nodes that form the supernodes
- 4) Solve the resulting simultaneous system of equations using substitution, calculator, Cramer's Rule, etc.
- 5) Use Ohm's Law and node voltages to determine branch currents

Supernode – Example

19

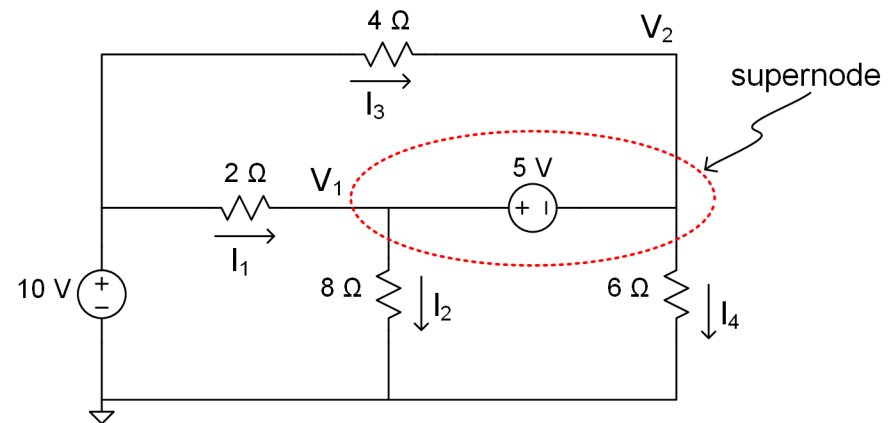- **Step 1:** Identify and label all nodes in the circuit
 - ▣ Any supernodes are identified and labeled in this step
- **Step 2:** Assign and label all branch currents
- **Step 3a:** Apply KCL at all nodes and all supernodes
 - ▣ Here we have only the one supernode:



$$I_1 - I_2 + I_3 - I_4 = 0$$

$$\frac{10V - V_1}{2\Omega} - \frac{V_1}{8\Omega} + \frac{10V - V_2}{4\Omega} - \frac{V_2}{6\Omega} = 0$$

$$V_1 \left(\frac{1}{2\Omega} + \frac{1}{8\Omega} \right) + V_2 \left(\frac{1}{4\Omega} + \frac{1}{6\Omega} \right) = 7.5A$$

Supernode – Example

20

- **Step 3b**: Apply KVL to relate the voltages of the nodes that form the supernode

$$V_1 - 5V - V_2 = 0$$

$$V_1 - V_2 = 5V$$

- **Step 4**: Solve the resulting system of equations

$$V_1 \cdot 625 \text{ mS} + V_2 \cdot 416.7 \text{ mS} = 7.5 \text{ A}$$

$$V_1 - V_2 = 5V$$

- Putting these into matrix form:

$$\begin{bmatrix} 625 \text{ mS} & 416.7 \text{ mS} \\ 1 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 7.5 \text{ A} \\ 5V \end{bmatrix}$$

Supernode – Example

21

$$\begin{bmatrix} 625 \text{ mS} & 416.7 \text{ mS} \\ 1 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 7.5 \text{ A} \\ 5 \text{ V} \end{bmatrix}$$

- Note that coefficient matrix on the left-hand side is no longer a conductance matrix
 - ▣ Second-row elements are dimensionless
 - ▣ Mix of KCL and KVL equations
- Solve using your method of choice
- Here, solved using MATLAB

$$V_1 = 9.2 \text{ V}$$

$$V_2 = 4.2 \text{ V}$$

```
Command Window
>> A = [0.625,0.41667;1,-1]

A =

    0.6250    0.4167
    1.0000   -1.0000

>> b = [7.5;5]

b =

    7.5000
    5.0000

>> V = A\b

V =

    9.2000
    4.2000
```

Supernode – Example

22

- **Step 5:** Use Ohm's law and branch currents to determine node voltages

$$I_1 = \frac{10\text{ V} - 9.2\text{ V}}{2\ \Omega} = \frac{0.8\text{ V}}{2\ \Omega} = 0.4\text{ A}$$

$$I_2 = \frac{9.2\text{ V}}{8\ \Omega} = 1.15\text{ A}$$

$$I_3 = \frac{10\text{ V} - 4.2\text{ V}}{4\ \Omega} = \frac{5.8\text{ V}}{4\ \Omega} = 1.45\text{ A}$$

$$I_4 = \frac{4.2\text{ V}}{6\ \Omega} = 0.7\text{ A}$$



$$I_1 = 0.4\text{ A}$$

$$I_2 = 1.15\text{ A}$$


$$I_3 = 1.45\text{ A}$$

$$I_4 = 0.7\text{ A}$$

23

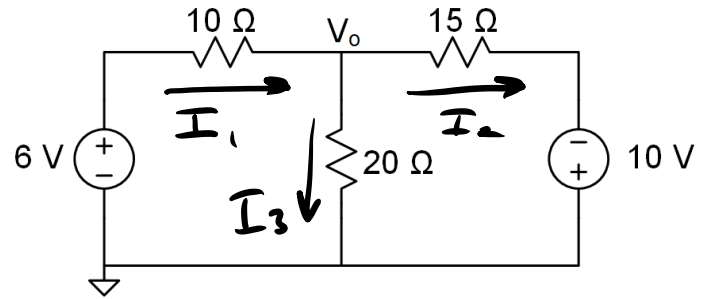Example Problems

Apply nodal analysis to determine V_o in the following circuit.



KCL at V_o :

$$I_1 - I_2 - I_3 = 0$$

$$\frac{6V - V_o}{10\Omega} - \frac{(V_o - (-10V))}{15\Omega} - \frac{V_o}{20\Omega} = 0$$


$$V_o \left(\frac{1}{10\Omega} + \frac{1}{15\Omega} + \frac{1}{20\Omega} \right) = \frac{6V}{10\Omega} - \frac{10V}{15\Omega}$$

$$V_o (216.7 \text{ mS}) = -66.7 \text{ mA}$$

$$V_o = \frac{-66.7 \text{ mA}}{216.7 \text{ mS}}$$

$$\underline{V_o = -307.7 \text{ mV}}$$

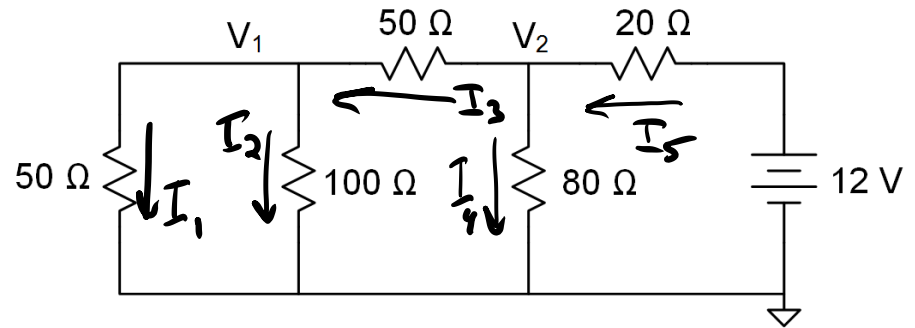Apply nodal analysis to determine V_1 and V_2 .



KCL at V_1 :

$$-I_1 - I_2 + I_3 = 0$$

$$-\frac{V_1}{50\Omega} - \frac{V_1}{100\Omega} + \frac{V_2 - V_1}{50\Omega} = 0$$

$$V_1 \left(\frac{1}{50\Omega} + \frac{1}{100\Omega} + \frac{1}{50\Omega} \right) + V_2 \left(-\frac{1}{50\Omega} \right) = 0$$

$$V_1 (30\text{mS}) + V_2 (-20\text{mS}) = 0 \quad (1)$$

KCL at V_2 :

$$-I_3 - I_4 + I_5 = 0$$

$$-\frac{(V_2 - V_1)}{50\Omega} - \frac{V_2}{80\Omega} + \frac{12V - V_2}{20\Omega} =$$

$$V_1\left(-\frac{1}{50\Omega}\right) + V_2\left(\frac{1}{50\Omega} + \frac{1}{80\Omega} + \frac{1}{20\Omega}\right) = \frac{12V}{20\Omega}$$

$$V_1(-20\text{mS}) + V_2(82.5\text{mS}) = 600\text{mA} \quad (2)$$


System of equations

$$\begin{bmatrix} 50\text{mS} & -20\text{mS} \\ -20\text{mS} & 82.5\text{mS} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 600\text{mA} \end{bmatrix}$$


Solving \rightarrow

$$\underline{V_1 = 3.22V}$$

$$\underline{V_2 = 8.05V}$$

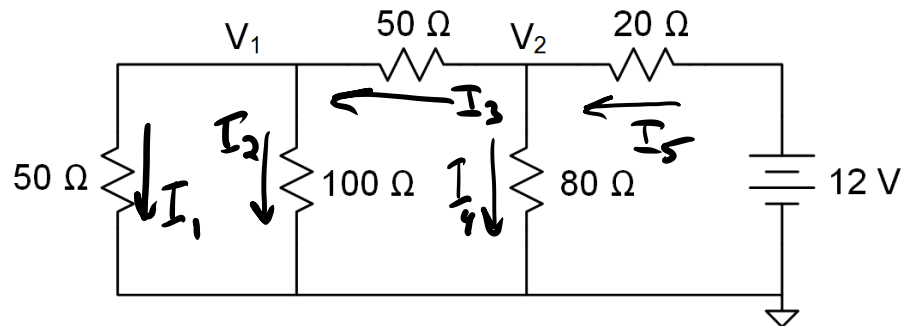

Apply nodal analysis
to determine V_o .

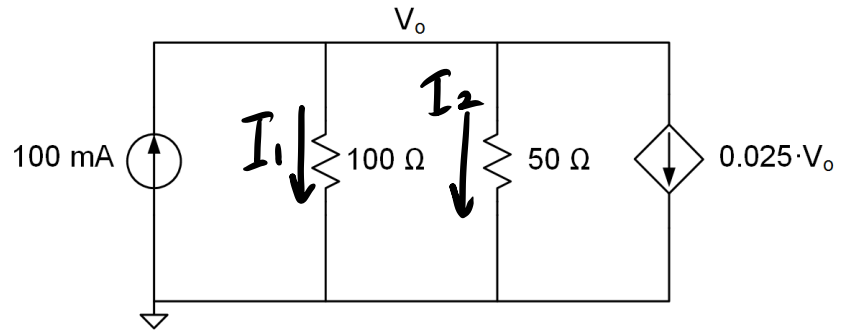

KCL at v_o :

$$100 \text{ mA} - I_1 - I_2 - 0.25 V_o = 0$$

$$100 \text{ mA} - \frac{V_o}{100 \Omega} - \frac{V_o}{50 \Omega} - 0.25 V_o = 0$$


$$V_o \left(\frac{1}{100 \Omega} + \frac{1}{50 \Omega} + 0.025 \text{ S} \right) = 100 \text{ mA}$$

$$V_o (55 \text{ mS}) = 100 \text{ mA}$$

$$V_o = \frac{100 \text{ mA}}{55 \text{ mS}}$$

$$\underline{V_o = 1.82 \text{ V}}$$

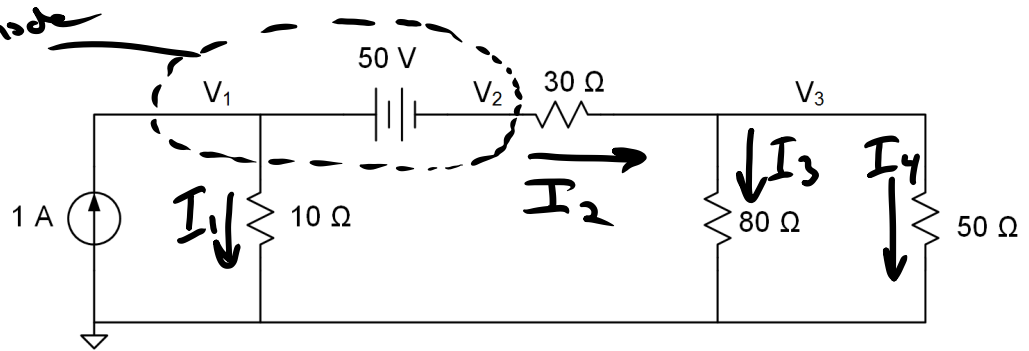Apply nodal analysis to determine V_1 , V_2 , and V_3 .



KCL at the Supernode :

$$1A - I_1 - I_2 = 0$$

$$1A - \frac{V_1}{10\Omega} - \frac{(V_2 - V_3)}{30\Omega} = 0$$

$$V_1 \left(\frac{1}{10\Omega} \right) + V_2 \left(\frac{1}{30\Omega} \right) + V_3 \left(-\frac{1}{30\Omega} \right) = 1A$$

$$V_1 (100mS) + V_2 (33.3mS) + V_3 (-33.3mS) = 1A \quad (1)$$

KCL at V_3

$$I_2 - I_3 - I_4 = 0$$

$$\frac{V_2 - V_3}{30\Omega} - \frac{V_3}{80\Omega} - \frac{V_3}{50\Omega} = 0$$

$$V_2 \left(\frac{1}{30\Omega} \right) + V_3 \left(-\frac{1}{30\Omega} - \frac{1}{80\Omega} - \frac{1}{50\Omega} \right) = 0$$

$$V_2 (33.3\text{mS}) + V_3 (-65.8\text{mS}) = 0 \quad (2)$$

KVL at the supernode


$$V_1 - V_2 = 50\text{V} \quad (3)$$

$$\begin{bmatrix} 100\text{mS} & 33.3\text{mS} & -33.3\text{mS} \\ 0 & 33.3\text{mS} & -65.8\text{mS} \\ 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 1\text{A} \\ 0 \\ 50\text{V} \end{bmatrix}$$




$$\begin{aligned} V_1 &= 15.65\text{V} \\ V_2 &= -34.35\text{V} \\ V_3 &= -17.39\text{V} \end{aligned}$$

Supernode

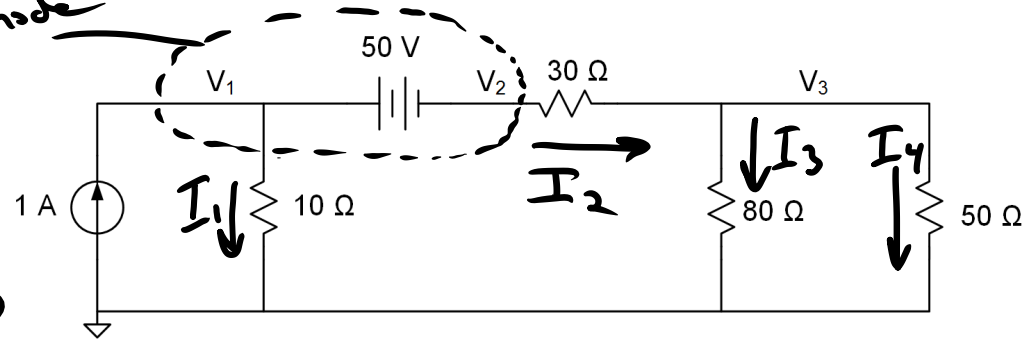

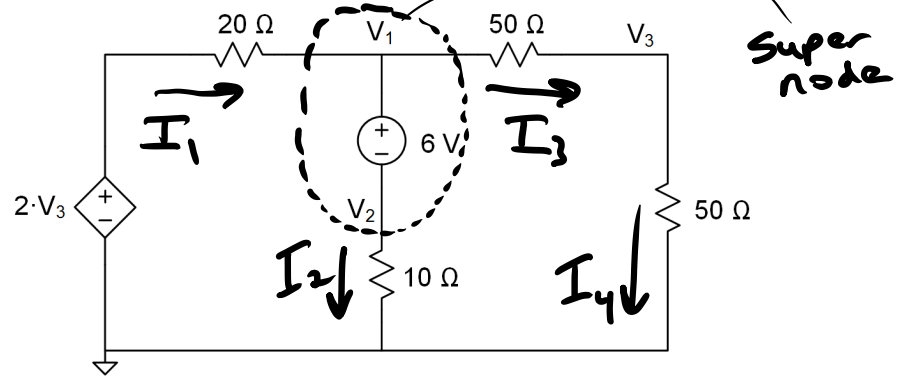Apply nodal analysis to determine V_1 , V_2 , and V_3 .



KCL at the supernode:

$$I_1 - I_2 - I_3 = 0$$

$$\frac{2V_3 - V_1}{20\Omega} - \frac{V_2}{10\Omega} - \frac{V_1 - V_3}{50\Omega} = 0$$

$$V_1 \left(-\frac{1}{20\Omega} - \frac{1}{50\Omega} \right) + V_2 \left(-\frac{1}{10\Omega} \right) + V_3 \left(\frac{2}{20\Omega} + \frac{1}{50\Omega} \right) = 0$$

$$V_1 (-70\text{mS}) + V_2 (-100\text{mS}) + V_3 (120\text{mS}) = 0 \quad (1)$$

KCL at V_3 :

$$I_3 - I_4 = 0$$

$$\frac{V_1 - V_3}{50\Omega} - \frac{V_3}{50\Omega} = 0$$


$$V_1(20mS) + V_3(-40mS) = 0 \quad (2)$$

KVL at supernode

$$V_1 - V_2 = 6V \quad (3)$$

$$\begin{bmatrix} -70mS & -100mS & 120mS \\ 20mS & 0 & -40mS \\ 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 6V \end{bmatrix}$$
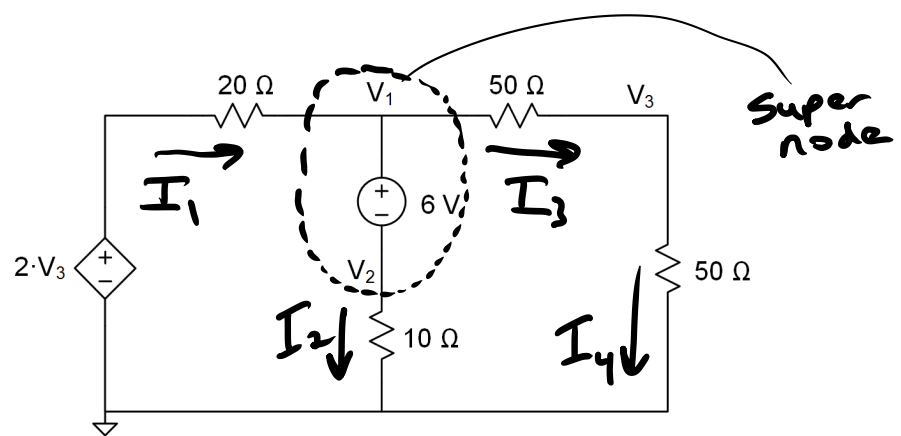
$$\longrightarrow \underline{V_1 = 5.45V}, \quad \underline{V_2 = -0.55V}, \quad \underline{V_3 = 2.73V}$$



32

Mesh Analysis

Mesh Analysis

33


□ ***Mesh analysis***

- Systematic application of ***KVL***
- Generate a system of equations
 - Mesh currents are the unknown variables
 - Number of equations equals number of unknown mesh currents
- Solve equations to determine mesh currents
- Determine branch currents as linear combinations of mesh currents
- Apply Ohm's law to determine node voltages

Meshes

34

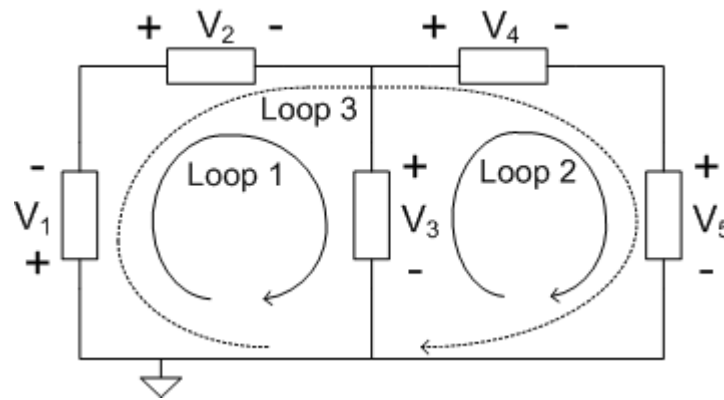- What is a *mesh*?
 - ▣ A mesh is a loop that does not contain any other loops



- ▣ Loop 1 and Loop 2 are meshes, Loop 3 is not

Mesh Currents

35


- What is a **mesh current**?
 - ▣ Fictitious circulating current in a mesh
 - ▣ Components of the branch currents
 - Branch currents are linear combinations of mesh currents, e.g.:

$$i_1 = I_1$$

$$i_3 = I_1 - I_2$$

$$i_4 = I_2$$

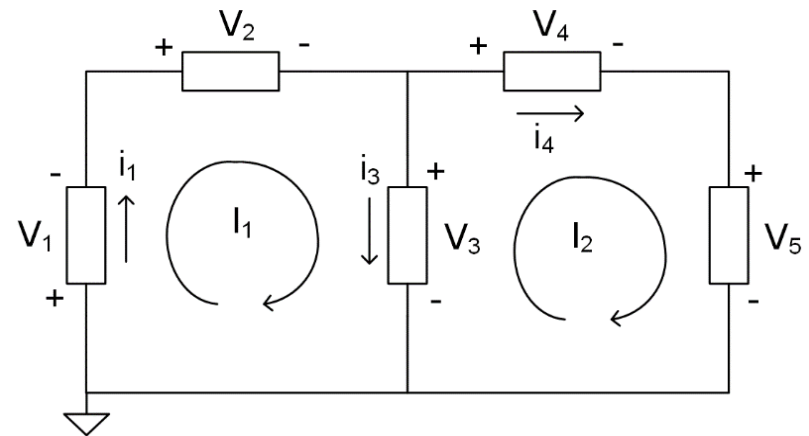- **Conventions:**
 - ▣ Denote mesh currents with uppercase I
 - ▣ Denote branch currents with lowercase i
 - ▣ Mesh current direction is clockwise



Mesh Analysis – step-by-step procedure


36

- 1) Identify and label all:
 - ▣ Mesh currents, I_n
 - ▣ Branch currents, i_n
 - ▣ Unknown node voltages
- 2) Apply KVL around each mesh
 - ▣ Follow CW direction of the mesh current
 - ▣ Use Ohm's law to express voltage drops in terms of mesh currents
- 3) Solve the resulting simultaneous system of equations using Gaussian elimination, calculator, MATLAB, etc.
- 4) Determine branch currents from the mesh currents
- 5) Use Ohm's Law and branch currents to determine node voltages


Mesh Analysis – Example

37

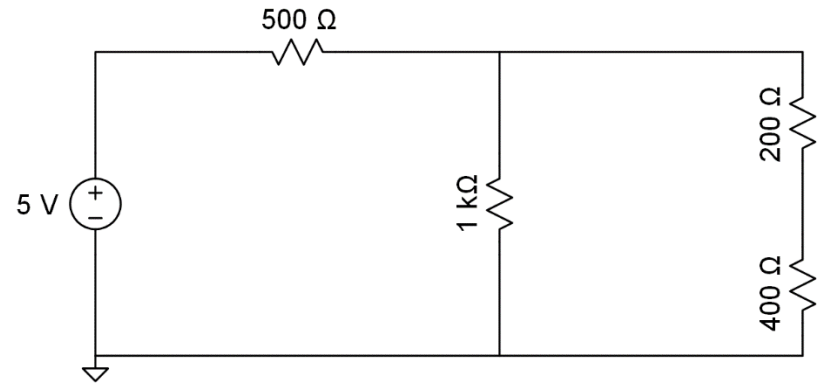- Use **mesh analysis** to determine all
 - ▣ Node voltages
 - ▣ Branch currents



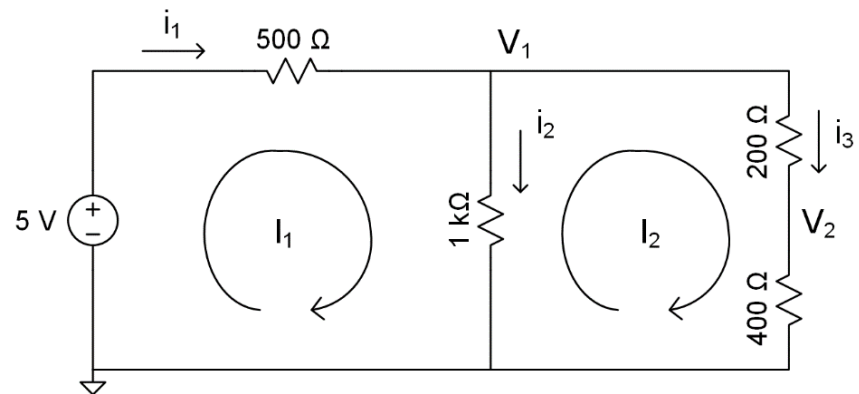- **Step 1:** Identify and label all mesh currents, branch currents, and unknown node voltages
 - ▣ Two unknown mesh currents
 - ▣ Three distinct branch currents
 - ▣ Two unknown node voltages



Mesh Analysis – Example

38

- **Step 2:** Apply KVL around each mesh

- KVL around mesh 1:

$$5\text{ V} - I_1 \cdot 500\ \Omega - I_1 \cdot 1\ \text{k}\Omega + I_2 \cdot 1\ \text{k}\Omega = 0$$


- Note that there are two components to the voltage across the $1\ \text{k}\Omega$ resistor

- A drop due to I_1
- A rise due to I_2

- KVL around mesh 2:

$$-I_2 \cdot 1\ \text{k}\Omega + I_1 \cdot 1\ \text{k}\Omega - I_2 \cdot 200\ \Omega - I_2 \cdot 400\ \Omega = 0$$

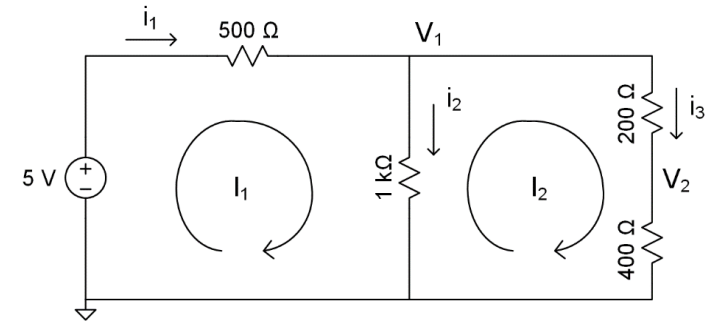- Again, note the two voltage components across the $1\ \text{k}\Omega$ resistor



Mesh Analysis – Example

39

- **Step 3:** Solve the resulting system of mesh equations

- Cleaning up the two equations:

$$I_1 \cdot 1.5 \text{ k}\Omega - I_2 \cdot 1 \text{ k}\Omega = 5 \text{ V}$$

$$-I_1 \cdot 1 \text{ k}\Omega + I_2 \cdot 1.6 \text{ k}\Omega = 0$$

- Organizing the system of two equations into matrix form:

$$\begin{bmatrix} 1.5 \text{ k}\Omega & -1 \text{ k}\Omega \\ -1 \text{ k}\Omega & 1.6 \text{ k}\Omega \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 5 \text{ V} \\ 0 \end{bmatrix}$$


$$\mathbf{R I} = \mathbf{V}$$

- Solving in MATLAB yields:

$$I_1 = 5.71 \text{ mA}$$

$$I_2 = 3.57 \text{ mA}$$

- **Mesh currents**, not branch currents

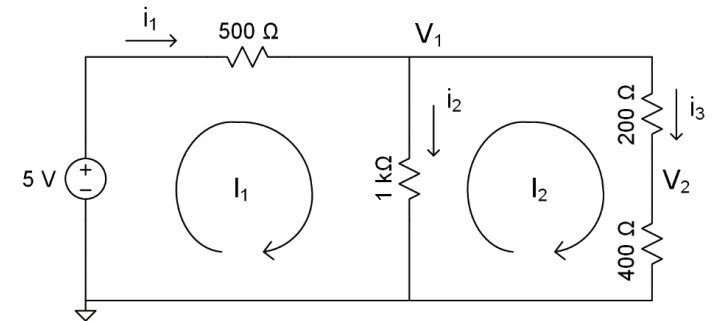

```
Command Window
>> R = [1.5e3,-1e3;-1e3,1.6e3]

R =

    1.5000e+003    -1.0000e+003
   -1.0000e+003     1.6000e+003

>> v = [5;0]

v =

    5.0000e+000
    0.0000e+000

>> I = R\v

I =

    5.7143e-003
    3.5714e-003
```

Mesh Analysis – Example

40

- **Step 4:** Determine branch currents from mesh currents
 - ▣ Branch current, i_1 , is the same as mesh current, I_1


$$i_1 = I_1 = 5.71 \text{ mA}$$

- ▣ Branch current, i_2 , is a combination of the two opposing mesh currents
 - In the same direction as I_1
 - In the opposite direction of I_2

$$i_2 = I_1 - I_2 = 5.71 \text{ mA} - 3.57 \text{ mA} = 2.14 \text{ mA}$$

- ▣ Branch current, i_3 , is the same as mesh current, I_2

$$i_3 = I_2 = 3.57 \text{ mA}$$

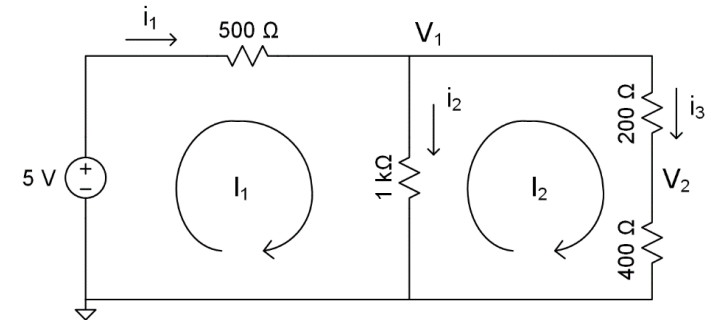


Mesh Analysis – Example

41

$$i_1 = 5.71 \text{ mA}$$

$$i_2 = 2.14 \text{ mA}$$

$$i_3 = 3.57 \text{ mA}$$

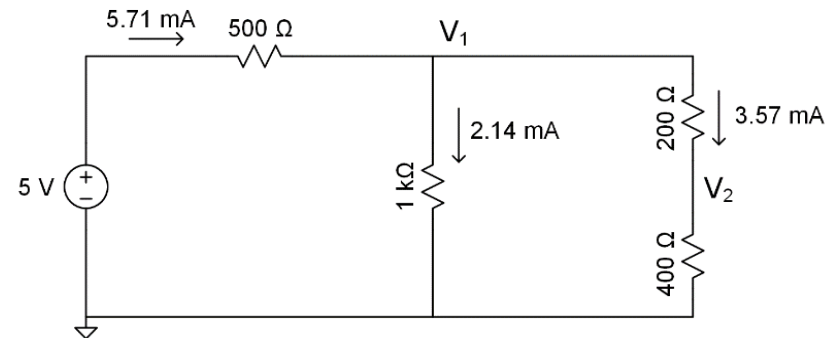

- **Step 5:** Use Ohm's law and branch currents to determine node voltages

$$V_1 = 2.14 \text{ mA} \cdot 1 \text{ k}\Omega = 2.14 \text{ V}$$

$$V_2 = 3.57 \text{ mA} \cdot 400 \Omega = 1.43 \text{ V}$$

$$V_1 = 2.14 \text{ V}$$

$$V_2 = 1.43 \text{ V}$$

- Note that these results agree with those obtained through nodal analysis

42


Supermeshes

Mesh Analysis – Current Sources

43


- Sometimes, we may want to perform **mesh analysis** on a circuit containing **current sources**
- Two possible scenarios:

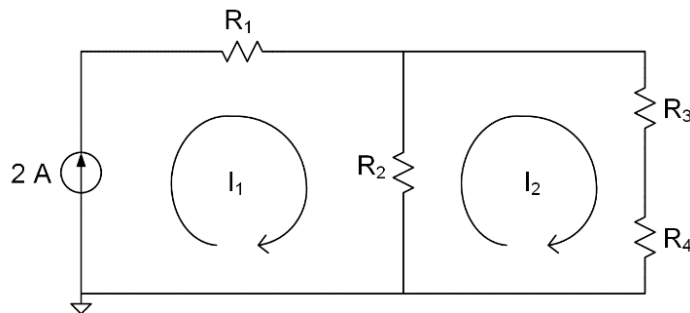- Current source is part of only one mesh



- Here, $I_1 = 2 A$
- Only one unknown mesh current, I_2
 - Only one mesh equation
- Mesh analysis proceeds as usual

- Current source is part of two meshes

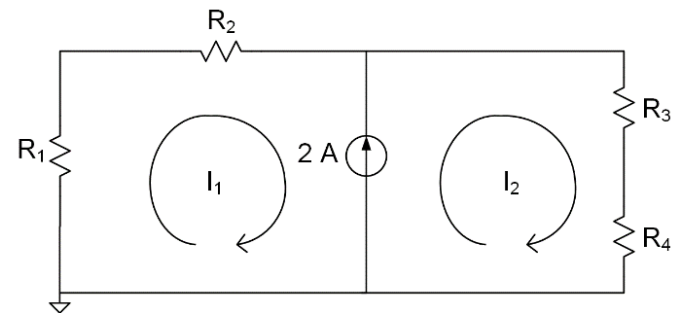

- Can't apply KVL around either mesh
 - Don't know the voltage drop across the current source

Supermesh

44


- Current source shared by two meshes poses a problem
 - Need to apply KVL around each mesh, but don't know the voltage across the current source

- Solution:
 - Form a ***supermesh*** around the periphery of the two meshes that share the current source
 - Apply KVL around the supermesh
 - One equation for the two unknown mesh currents
 - Apply KCL to a node on the branch common to the two meshes in the supermesh
 - This provides the second required equation for the two unknown mesh currents

Supermesh – Example

45

- Meshes 1 and 2 are combined to form a **supermesh**
- Circuit has two unknown mesh currents, I_1 and I_2
 - ▣ System of two equations is required
- KVL will be applied around the supermesh
 - ▣ Only one equation will result
- Additional required equation obtained by applying KCL to a node on the branch common to both meshes
- If multiple supermeshes intersect, they should be joined into a single supermesh

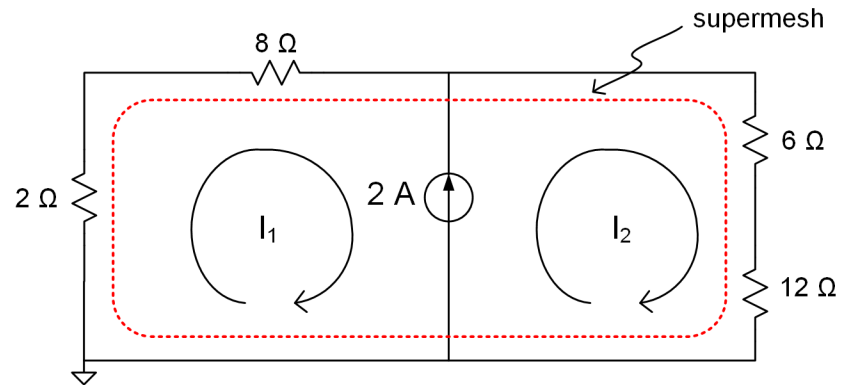

Mesh Analysis with Supermeshes – Step-by-Step


46

- 1) Identify and label all:
 - ▣ Mesh currents, I_n
 - ▣ Branch currents, i_n
 - ▣ Unknown node voltages
- 2) Generate a system of equations
 - a) Apply KVL around each supermesh and each mesh that is not part of a supermesh
 - b) Apply KCL at a node on each branch common to two meshes in each supermesh
- 3) Solve the resulting simultaneous system of equations using Gaussian elimination, calculator, MATLAB, etc.
- 4) Determine branch currents from the mesh currents
- 5) Use Ohm's Law and branch currents to determine node voltages

Supermesh – Example

47

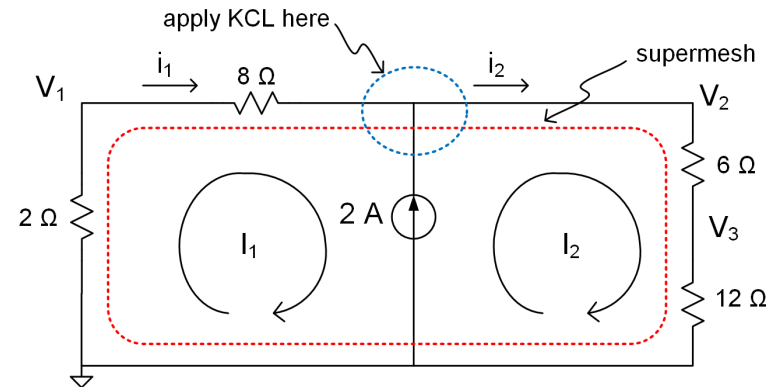- **Step 1:** Identify and label all mesh currents, branch currents, and unknown node voltages
 - Any supermeshes are identified and labeled in this step



- **Step 2a:** Apply KVL around each mesh and each supermesh
 - Only one supermesh, and no other meshes

$$-I_1 \cdot 2 \Omega - I_1 \cdot 8 \Omega - I_2 \cdot 6 \Omega - I_2 \cdot 12 \Omega = 0$$

- **Step 2b:** Apply KCL at a node on the branch common to the two meshes in the supermesh

$$I_1 - I_2 + 2A = 0$$

- These are the two equations needed to solve for the two unknown mesh currents, I_1 and I_2

Supermesh – Example

48

- **Step 3:** Solve the resulting system of equations

- Rearranging the equations:

$$I_1 \cdot 10 \Omega + I_2 \cdot 18 \Omega = 0$$

$$-I_1 + I_2 = 2 A$$

- In matrix form, the system of equations is


$$\begin{bmatrix} 10 \Omega & 18 \Omega \\ -1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 2 A \end{bmatrix}$$

- Note that, similar to the supernode analysis, the two equations now have different units

- Solving in MATLAB yields

$$I_1 = -1.29 A$$

$$I_2 = 0.714 A$$

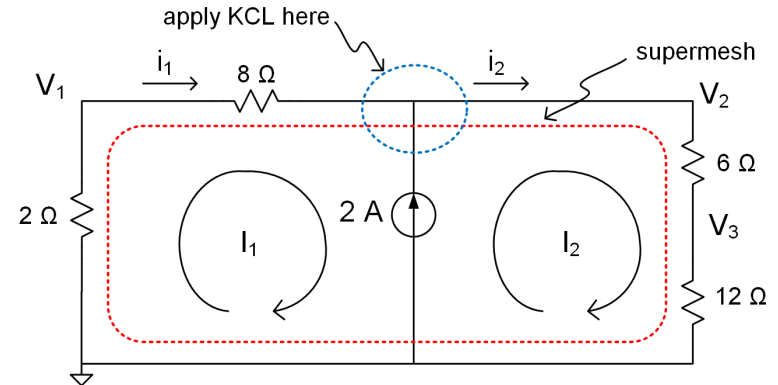

Supermesh – Example


49

- **Step 4:** Determine branch currents from the mesh currents

- Very simple in this example

$$i_1 = I_1 = -1.29 \text{ A}$$

$$i_2 = I_2 = 0.714 \text{ A}$$

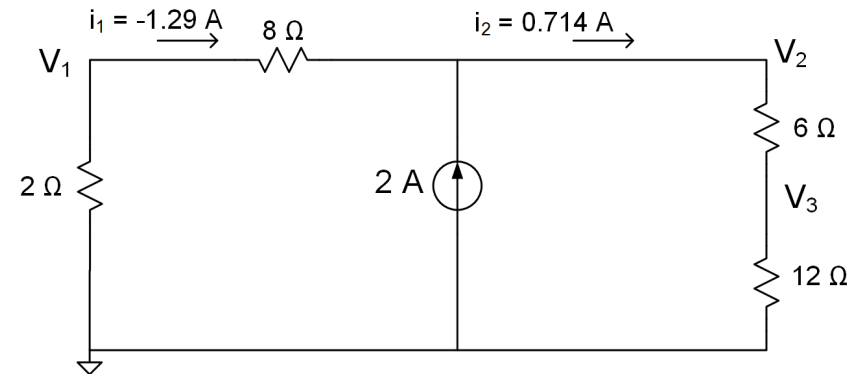

- **Step 5:** Use Ohm's law and branch currents to determine node voltages

$$V_1 = -i_1 \cdot 2 \Omega = 1.29 \text{ A} \cdot 2 \Omega = 2.57 \text{ V}$$

$$V_2 = i_2 \cdot 18 \Omega = 0.714 \text{ A} \cdot 18 \Omega = 12.86 \text{ V}$$

$$V_3 = i_2 \cdot 12 \Omega = 0.714 \text{ A} \cdot 12 \Omega = 8.57 \text{ V}$$

- Results of the mesh analysis:

$$i_1 = -1.29 \text{ A}$$

$$i_2 = 0.714 \text{ A}$$

$$V_1 = 2.57 \text{ V}$$


$$V_2 = 12.86 \text{ V}$$

$$V_3 = 8.57 \text{ V}$$

50

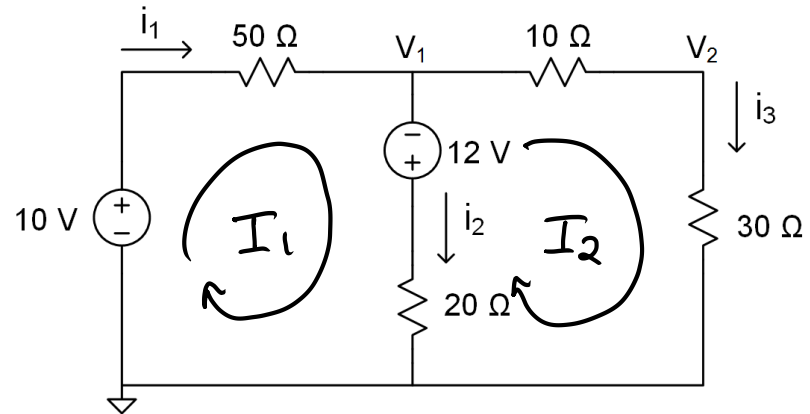Example Problems

Apply mesh analysis to determine V_1 , V_2 , i_1 , i_2 , and i_3 in the following circuit.



KVL around Mesh 1:

$$10V - I_1 \cdot 50\Omega + 12V - I_1 \cdot 20\Omega + I_2 \cdot 20\Omega = 0$$

$$I_1(50\Omega + 20\Omega) + I_2(-20\Omega) = 22V$$

$$I_1(70\Omega) + I_2(-20\Omega) = 22V \quad (1)$$

KVL around mesh 2:


$$-I_2 \cdot 20\Omega + I_1 \cdot 20\Omega - 12V - I_2 \cdot 10\Omega - I_2 \cdot 30\Omega = 0$$

$$I_1(20\Omega) + I_2(-20\Omega - 10\Omega - 30\Omega) = 12V$$

$$I_1(20\Omega) + I_2(-60\Omega) = 12V \quad (2)$$

I_n matrix form
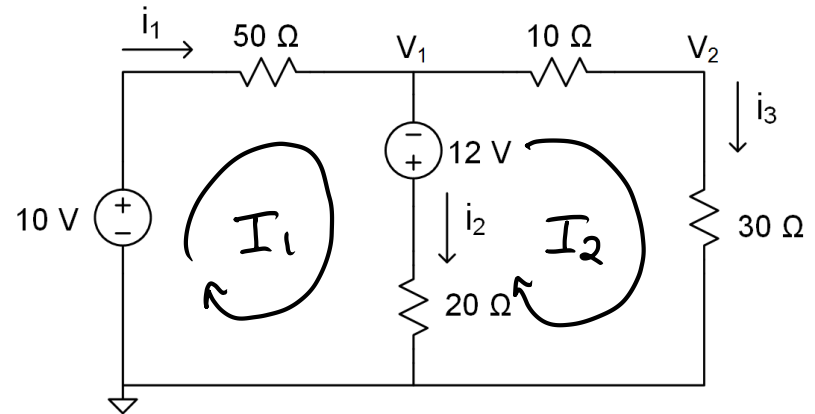
$$\begin{bmatrix} 70\Omega & -20\Omega \\ 20\Omega & -60\Omega \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 22V \\ 12V \end{bmatrix}$$



Solving yields

$$I_1 = 284.2 \text{ mA} \quad \text{and} \quad I_2 = -105.3 \text{ mA}$$

Branch currents are

$$i_1 = I_1 = 284.2 \text{ mA}$$

$$i_2 = I_1 - I_2 = 284.2 \text{ mA} + 105.3 \text{ mA} = 389.5 \text{ mA}$$

$$i_3 = I_2 = -105.3 \text{ mA}$$

Node voltages:


$$V_1 = 10V - i_1 \cdot 50\Omega$$

$$V_1 = 10V - 284.2mA \cdot 50\Omega$$

$$V_1 = -4.21V$$

$$V_2 = i_3 \cdot 30\Omega = -105.3mA \cdot 30\Omega$$

$$V_2 = -3.16V$$

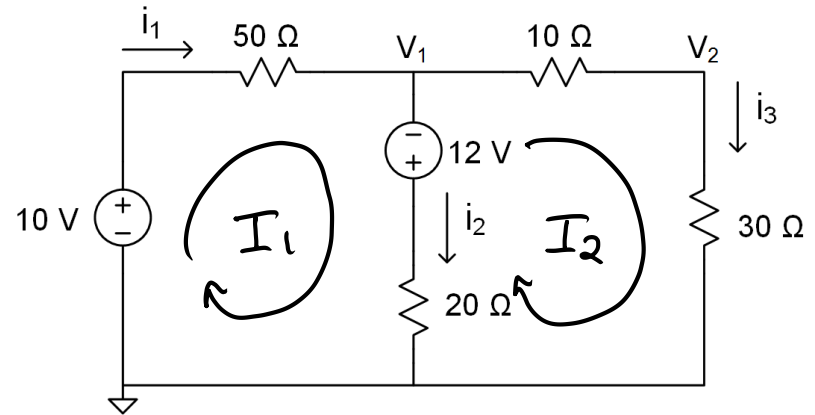

$$V_1 = -4.21V$$


$$V_2 = -3.16V$$

$$i_1 = 284.2mA$$

$$i_2 = 389.5mA$$

$$i_3 = -105.3mA$$

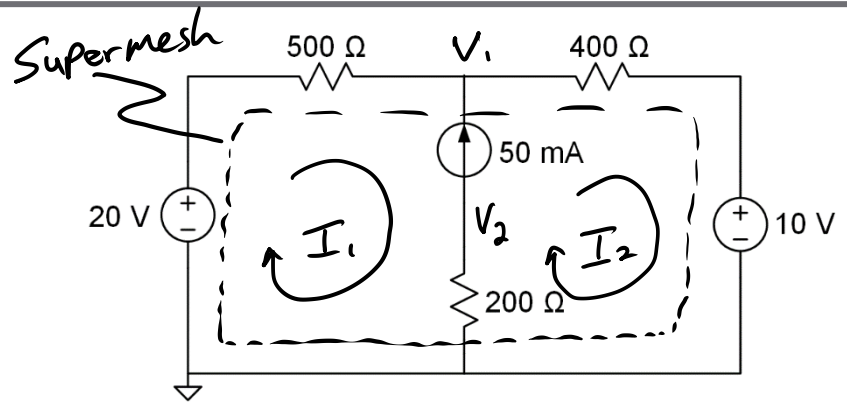Apply mesh analysis to determine the power supplied/absorbed by each of the sources in the following circuit.



KVL around super mesh:

$$20V - I_1 \cdot 500\Omega - I_2 \cdot 400\Omega - 10V = 0$$

$$I_1 \cdot 500\Omega + I_2 \cdot 400\Omega = 10V \quad (1)$$

KCL at V_1 :

$$I_1 + 50mA - I_2 = 0$$

$$I_1 - I_2 = -50mA \quad (2)$$

$$\begin{bmatrix} 500\Omega & 400\Omega \\ 1 & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10V \\ -50mA \end{bmatrix} \rightarrow \begin{aligned} I_1 &= -11.1mA \\ I_2 &= 38.9mA \end{aligned}$$

Node voltages

$$V_1 = 20\text{V} - I_1 \cdot 500\Omega$$

$$V_1 = 20\text{V} + 11.1\text{mA} \cdot 500\Omega$$

$$V_1 = 25.56\text{V}$$

$$V_2 = -50\text{mA} \cdot 200\Omega = -10\text{V}$$

Power of 20V source

$$P_{20\text{V}} = 20\text{V}(-I_1) = 20\text{V}(11.1\text{mA}) = \underline{222\text{mW}} \quad (\text{absorbed})$$


Power of 10V source

$$P_{10\text{V}} = 10\text{V}(I_2) = 10\text{V}(38.9\text{mA}) = \underline{389\text{mW}} \quad (\text{absorbed})$$


Power of 50mA source

$$P_{50\text{mA}} = (V_2 - V_1) \cdot 50\text{mA} = (-10\text{V} - 25.56\text{V}) \cdot 50\text{mA}$$
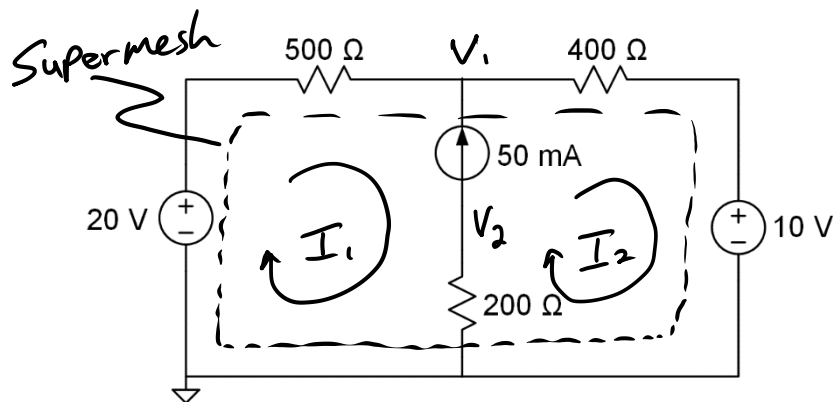
$$P_{50\text{mA}} = -35.56\text{V} \cdot 50\text{mA} = \underline{-1.78\text{W}} \quad (\text{supplied})$$



Apply mesh analysis
to determine V_x .

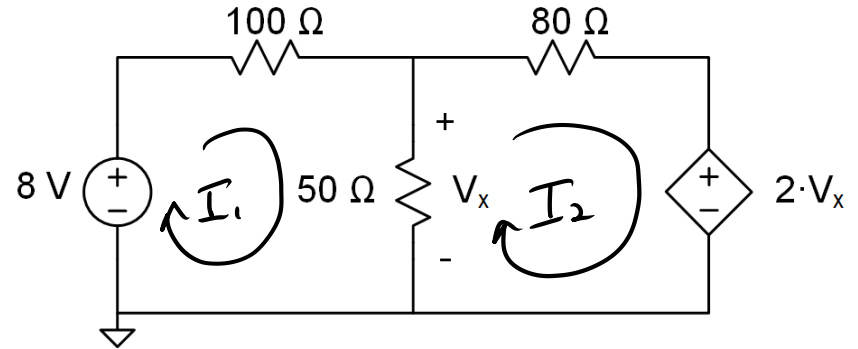

KVL around mesh 1

$$8V - I_1 \cdot 100\Omega - I_1 \cdot 50\Omega + I_2 \cdot 50\Omega = 0$$

$$I_1(100\Omega + 50\Omega) + I_2(-50\Omega) = 8V$$

$$I_1(150\Omega) + I_2(-50\Omega) = 8V \quad (1)$$

KVL around mesh 2

$$I_1 \cdot 50\Omega - I_2 \cdot 50\Omega - I_2 \cdot 80\Omega - 2V_x = 0$$

$$V_x = I_1 \cdot 50\Omega - I_2 \cdot 50\Omega$$

$$I_1 \cdot 50\Omega - I_2 \cdot 50\Omega - I_2 \cdot 80\Omega - 2 \cdot I_1 \cdot 50\Omega + 2I_2 \cdot 50\Omega = 0$$


$$I_1(-50\Omega) + I_2(-30\Omega) = 0 \quad (2)$$

In matrix form:

$$\begin{bmatrix} 150\Omega & -50\Omega \\ -50\Omega & -30\Omega \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 8V \\ 0 \end{bmatrix} \rightarrow \begin{aligned} I_1 &= 34.3 \text{ mA} \\ I_2 &= -57.1 \text{ mA} \end{aligned}$$

$$V_x = (I_1 - I_2) \cdot 50\Omega = (34.3 \text{ mA} + 57.1 \text{ mA}) 50\Omega$$

$$\underline{V_x = 4.57 \text{ V}}$$

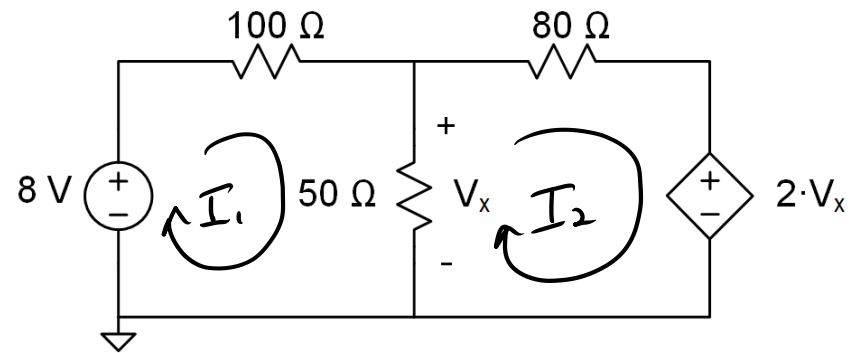

58

Linearity & Superposition


Systems

59

□ **System**


- Some entity – component, group of components – with inputs and outputs

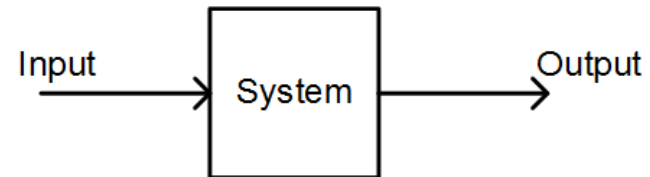- Electrical component
- Electrical circuit
- Motor, engine, robot, aircraft, etc. ...




- Can think of the system as a **mathematical function** that operates on the input to provide the output

$$y = f(x)$$

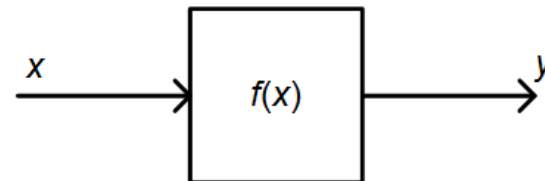

- A resistor is a system with voltage as the input and current as the output (or vice versa)

$$i = \frac{1}{R} v$$

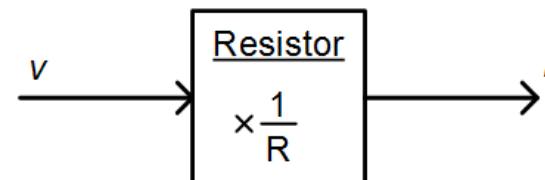

Linear Systems

60

□ **Linear system**

- A system whose **constitutive relationship is linear**
 - Function relating input to output is an **equation for a line**
- An ideal resistor is an example of a linear system
 - Voltage in, current out:



$$i = \frac{1}{R} \cdot v$$

- A line with slope $1/R$

- Current in, voltage out:

$$v = R \cdot i$$

- A line with slope R

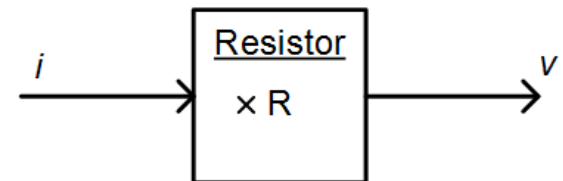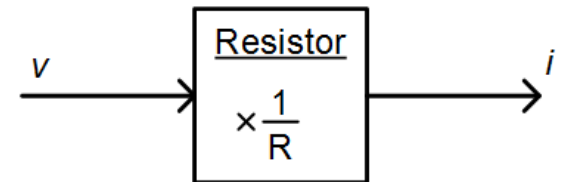


Superposition

61

- Linear systems obey the principle of ***superposition***
- Two components to the superposition principle:


- ***Additivity***

$$f(x_1 + x_2) = f(x_1) + f(x_2)$$

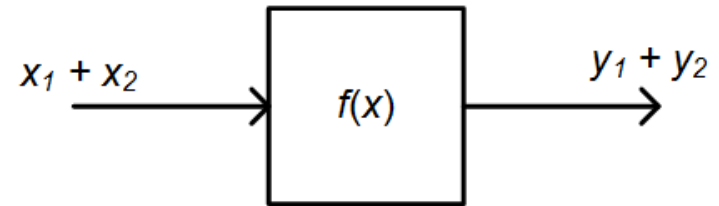

- ***Homogeneity***
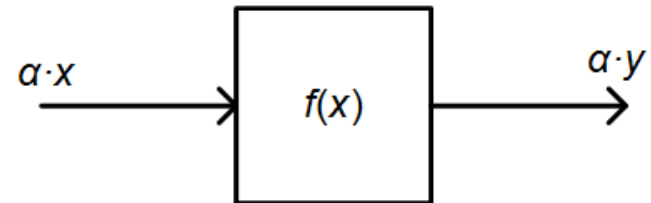
$$f(\alpha \cdot x) = \alpha \cdot f(x)$$



Superposition

62

- Consider an $4\ \Omega$ resistor

$$i = \frac{v}{R}$$

- $v_1 = 2\ V$



$$i_1 = \frac{2\ V}{4\ \Omega} = 0.5\ A$$

- $v_2 = 6\ V$

$$i_2 = \frac{3 \cdot 2\ V}{4\ \Omega} = 3 \cdot 0.5\ A = 1.5\ A$$

- $v_3 = 8\ V$
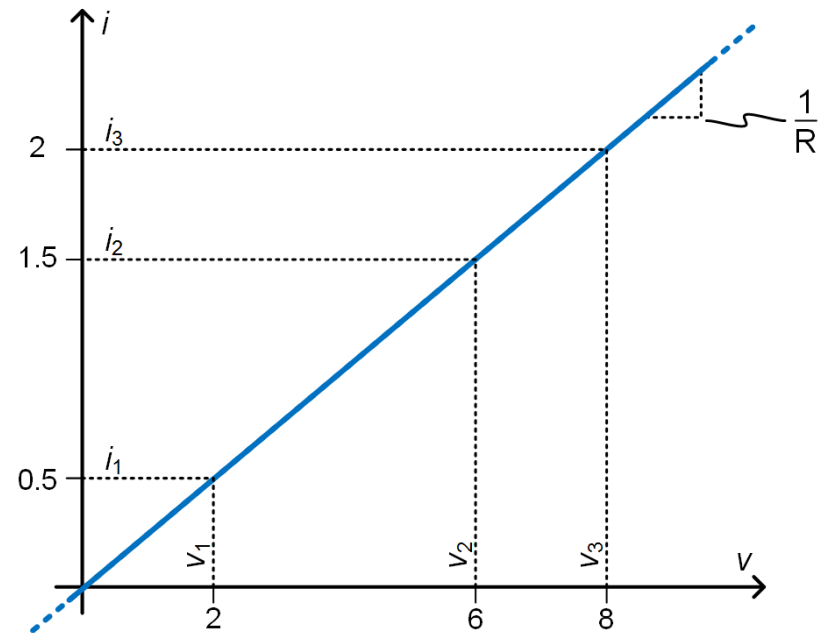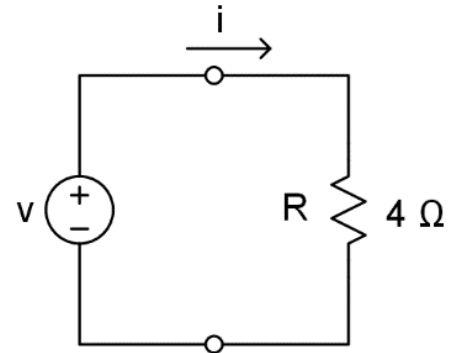
$$i_3 = \frac{2\ V + 6\ V}{4\ \Omega} = 0.5\ A + 1.5\ A = 2\ A$$



Superposition – Electrical Circuits

63


- Superposition applied to electrical circuits
 - Tool for analyzing networks with **multiple sources**

- For example:

- Output, V_{out} , is some linear combination of the inputs:

$$V_{out} = a_1 V_s + a_2 I_s$$

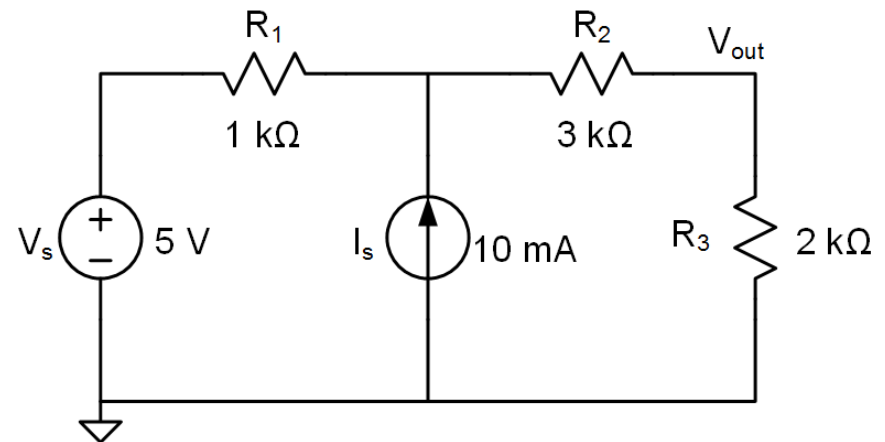- a_1 and a_2 are constants
 - If we know them, we know V_{out}
- To determine a_1
 - Set $I_s = 0$
 - Analyze the circuit to determine V_{out}
- To determine a_2
 - Set $V_s = 0$
 - Analyze the circuit to determine V_{out}



Superposition

64

The output of a multiple-input system is the sum of the outputs due to each independent source acting individually

- Circuit analysis using superposition:
 - ▣ Set all *independent* sources to zero, except for one
 - ▣ Determine the output component due to that source
 - ▣ Repeat for all independent sources
 - ▣ Sum all output components to find the total output

- Setting sources to zero:
 - ▣ Voltage sources become short circuits ($v = 0$)
 - ▣ Current sources become open circuits ($i = 0$)



Superposition - Example

65

- Apply superposition to determine the output voltage, V_{out}

- First, set the current source to zero
 - ▣ Replace it with an open circuit
 - ▣ Analyze the circuit to determine the output components due to the voltage source acting alone:

$$V_{out} \Big|_{V_s}$$

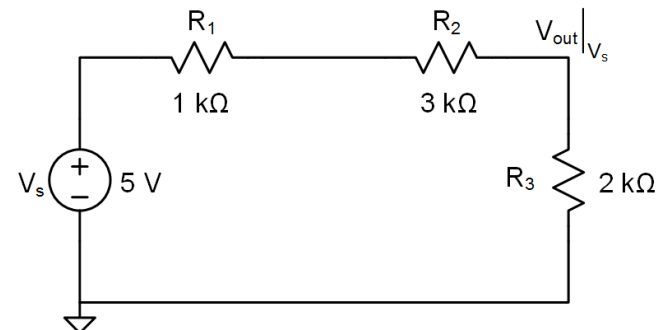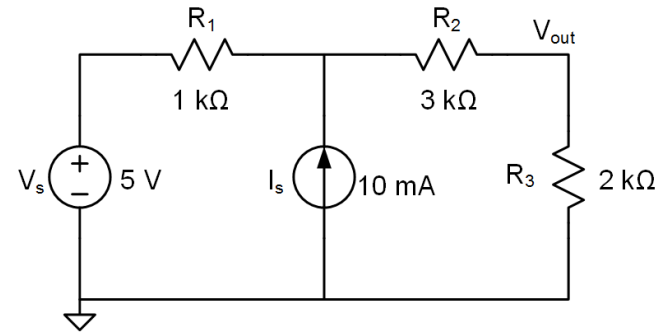

Superposition - Example


66

- A simple **voltage-divider** circuit

$$V_{out} \Big|_{V_s} = V_s \frac{R_3}{R_1 + R_2 + R_3}$$


$$V_{out} \Big|_{V_s} = 5 V \frac{2 k\Omega}{6 k\Omega}$$

$$V_{out} \Big|_{V_s} = 1.67 V$$

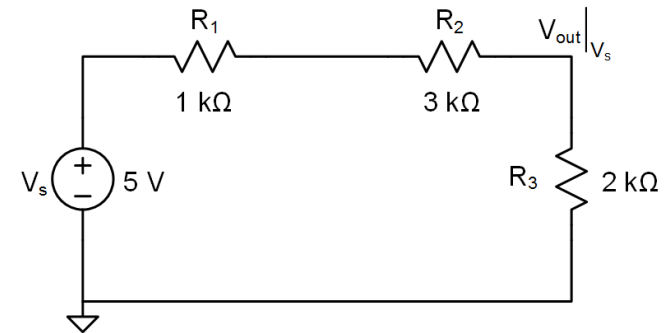

- Next, set the voltage source to zero
 - Replace it with a short circuit
 - Analyze the circuit to determine the output components due to the current source acting alone:

$$V_{out} \Big|_{I_s}$$

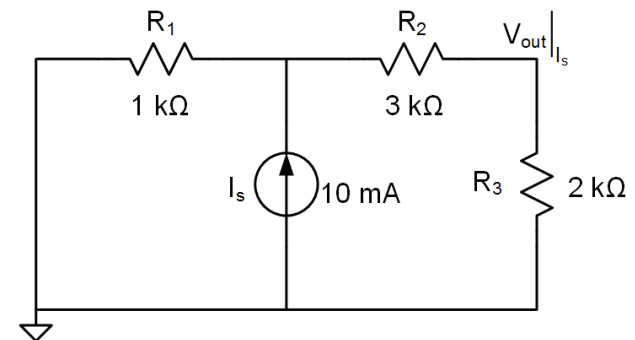

Superposition - Example


67

- In this case, we have a **current-divider** circuit
 - ▣ First, determine the current, I_3 , flowing through R_3

$$I_3 = I_s \frac{R_1}{R_1 + R_2 + R_3}$$

$$I_3 = 10 \text{ mA} \frac{1 \text{ k}\Omega}{6 \text{ k}\Omega}$$

$$I_3 = 1.67 \text{ mA}$$

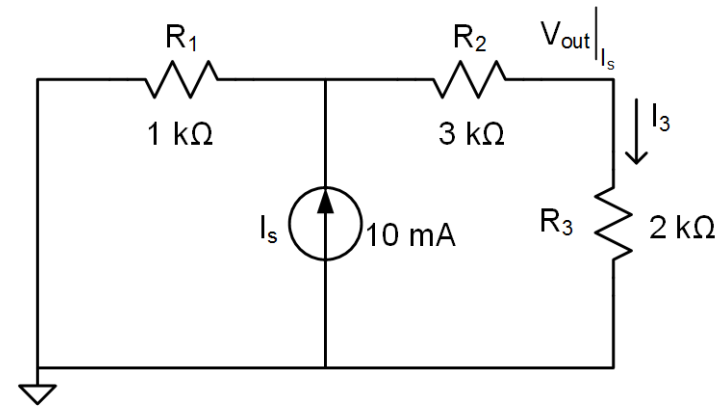

- Applying Ohm's law to R_3 gives the output voltage due to the current source

$$V_{out} \Big|_{I_s} = I_3 R_3 = 1.67 \text{ mA} \cdot 2 \text{ k}\Omega$$

$$V_{out} \Big|_{I_s} = 3.33 \text{ V}$$

Superposition - Example


68

- The total output due to both sources is the sum of the individual output components

$$V_{out} = V_{out} \Big|_{V_s} + V_{out} \Big|_{I_s}$$

$$V_{out} = 1.67 \text{ V} + 3.33 \text{ V}$$

$$V_{out} = 5 \text{ V}$$

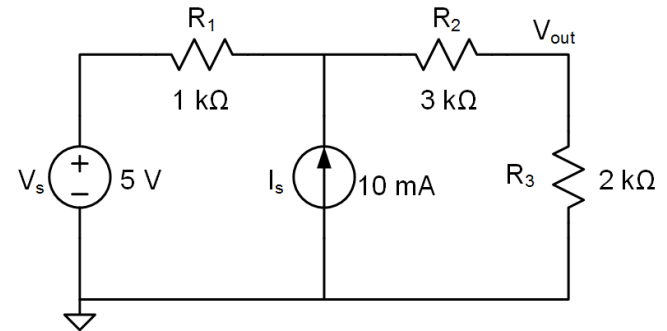


□ **Comments:**

- Superposition applies to circuits with any number of sources and any mix of voltage and/or current sources
- Becomes a more useful tool as circuits get more complex
- Applies to ***all types of linear systems*** – not just electrical

69

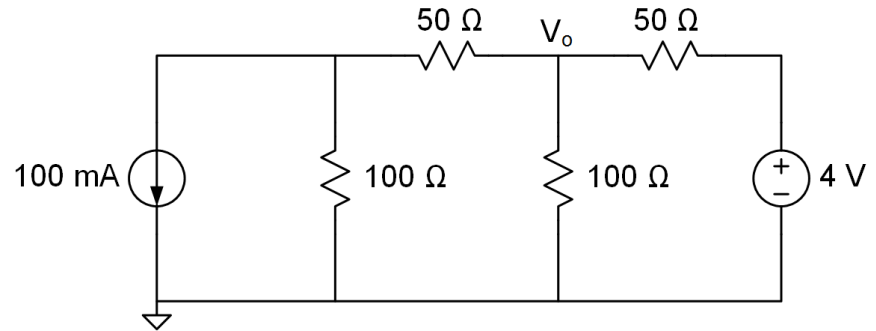
Example Problems

Apply superposition to determine V_o in the following circuit.



$$V_o = V_o|_{100\text{mA}} + V_o|_{4\text{V}}$$

First, set the 4V source to zero

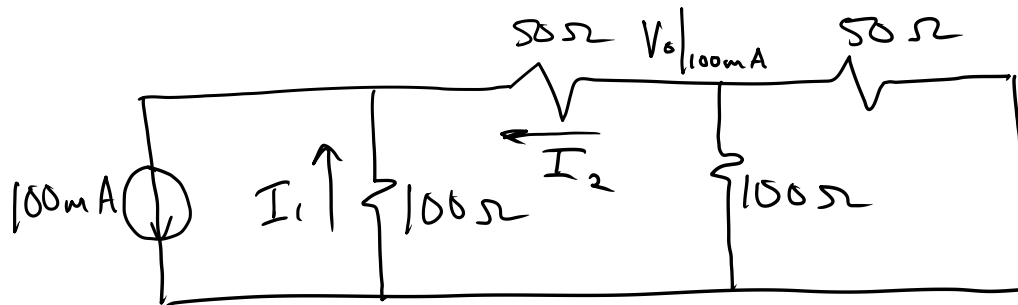

Output voltage is


$$V_o|_{100\text{mA}} = -I_2 (50\Omega || 100\Omega) = -I_2 \cdot 33.3\Omega$$

Apply Current division to get I_2

$$I_2 = 100\text{mA} \cdot \frac{100\Omega}{100\Omega + 50\Omega + 33.3\Omega} = 54.5\text{mA}$$

$$V_o|_{100\text{mA}} = -54.5\text{mA} \cdot 33.3\Omega = \underline{\underline{-1.82\text{V}}}$$

Next, set the 100mA source to zero

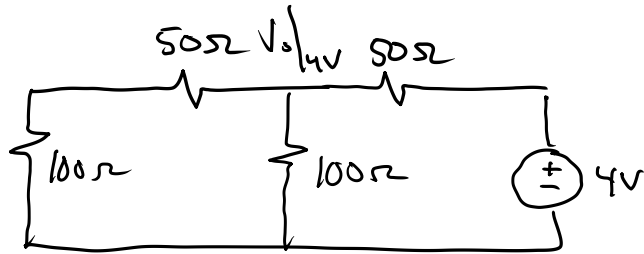

Applying voltage division

$$V_o|_{4\text{V}} = 4\text{V} \frac{(50\Omega + 100\Omega) \parallel 100\Omega}{50\Omega + (50\Omega + 100\Omega) \parallel 100\Omega} = 4\text{V} \frac{60\Omega}{90\Omega + 60\Omega}$$

$$V_o|_{4\text{V}} = 2.18\text{V}$$


Finally, applying superposition

$$V_o = V_o|_{100\text{mA}} + V_o|_{4\text{V}}$$


$$V_o = -1.82\text{ V} + 2.18\text{ V}$$

$$V_o = 364\text{ mV}$$

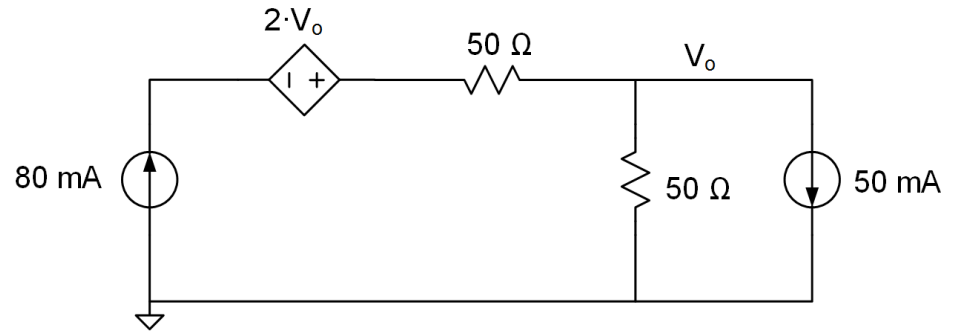Apply superposition to determine V_o in the following circuit.




First, set the 50 mA source to zero

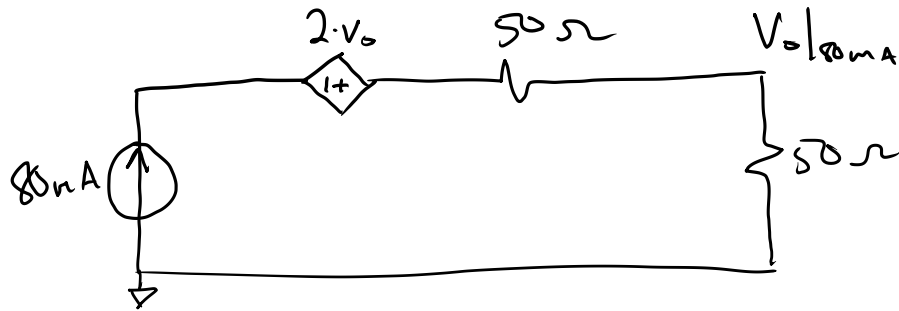

$$V_o|_{80mA} = 80mA \cdot 50 \Omega$$

$$V_o|_{80mA} = 4V$$

Next, set the 80mA source to zero

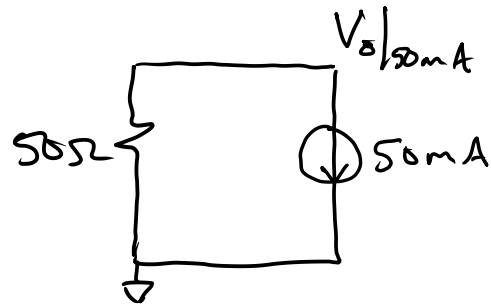


$$V_o|_{80mA} = -50mA \cdot 50\Omega = -2.5V$$

Apply superposition


$$V_o = V_o|_{80mA} + V_o|_{50mA} = 4V - 2.5V$$

$$V_o = 1.5V$$

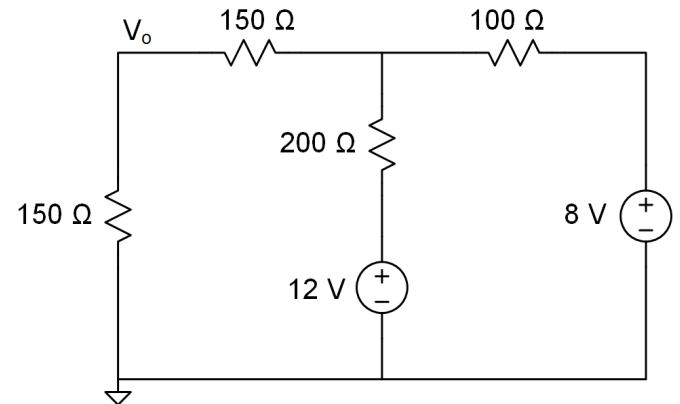Apply superposition to determine V_o in the following circuit.



First, set the 8V source to zero

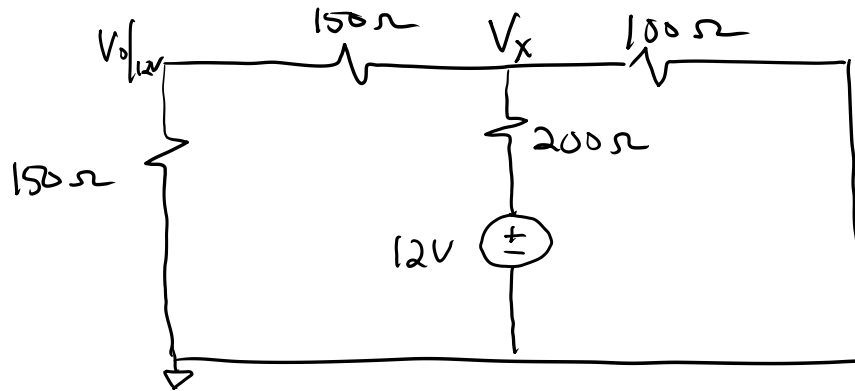


Apply voltage division twice. First, find V_x . Then

$$V_o|_{12V} = V_x \frac{150\ \Omega}{150\ \Omega + 150\ \Omega} = \frac{V_x}{2}$$

$$V_x = 12V \frac{100\Omega \parallel (150\Omega + 150\Omega)}{200\Omega + 100\Omega \parallel (150\Omega + 150\Omega)} = 12V \frac{75\Omega}{275\Omega} = 3.27V$$

$$V_o|_{12V} = \frac{V_x}{2} = \frac{3.27V}{2} = \underline{1.64V}$$

Next, set the 12V source to zero

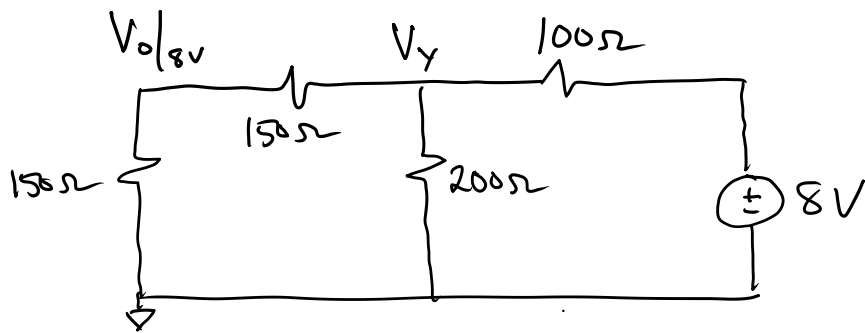

Again, apply voltage division twice. First, find V_y . The

$$V_o|_{8V} = V_y \frac{150\Omega}{150\Omega + 150\Omega} = \frac{V_y}{2}$$

$$V_y = 8V \frac{200\Omega // 300\Omega}{100\Omega + 200\Omega // 300\Omega} = 8V \frac{120\Omega}{220\Omega} = 4.36V$$

$$V_o|_{8V} = \frac{V_y}{2} = \frac{4.36V}{2} = 2.18V$$

Applying superposition

$$V_o = V_o|_{12V} + V_o|_{8V} = 1.64V + 2.18V$$

$$V_o = 3.82V$$

78

Thévenin & Norton Equivalents

Thévenin Equivalent Circuits

79

- Thévenin's theorem:

Any two-terminal linear network of resistors and sources can be represented as single resistor in series with a single independent voltage source

- The resistor is the ***Thévenin equivalent resistance, R_{th}***
- The voltage source is the ***open-circuit voltage, V_{oc}***



Léon Charles Thévenin, 1857 – 1926

Thévenin Equivalent Circuits


80

- Simplifies the analysis of complex networks
 - ▣ Quickly determine current, voltage, or power to any load connected to the network terminals

Complex network




Thévenin equivalent network

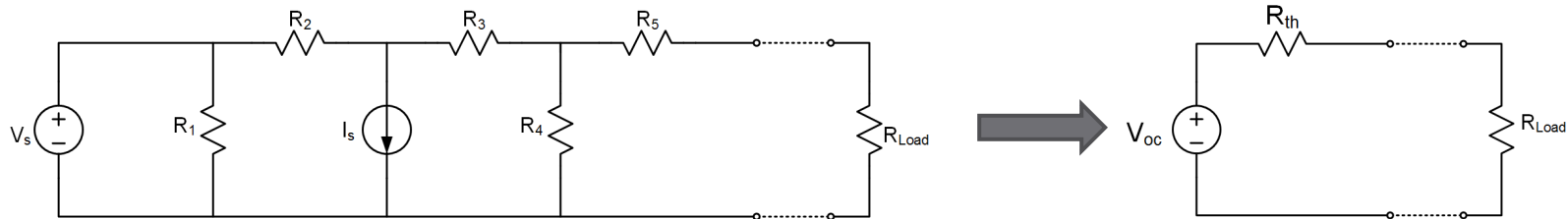

Open-Circuit Voltage - V_{oc}

81

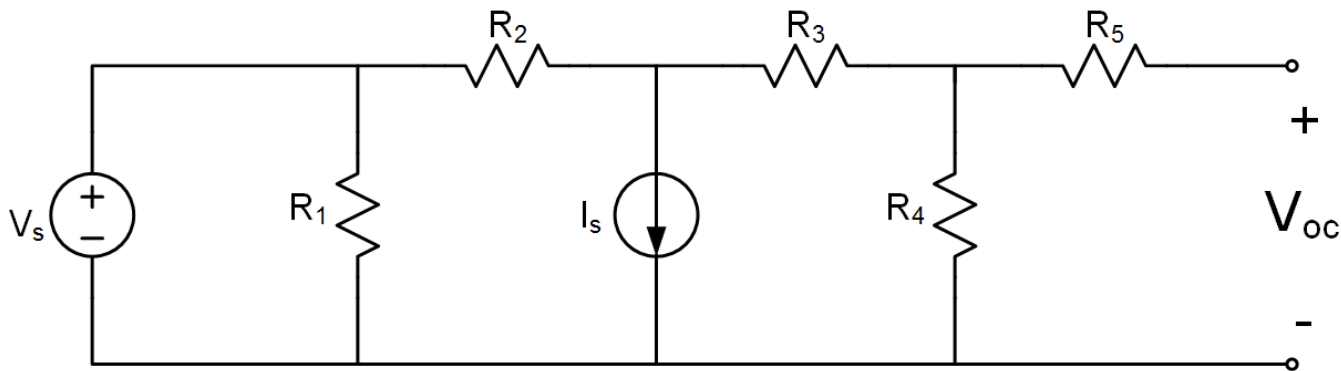
- **Open-circuit voltage, V_{oc}**
 - ▣ The terminal voltage with no load attached
- Determine V_{oc} by using most convenient method
 - ▣ Ohm's Law
 - ▣ Kirchhoff's Laws
 - ▣ Voltage or current divider
 - ▣ Nodal or mesh analysis



Thévenin Resistance - R_{th}

82

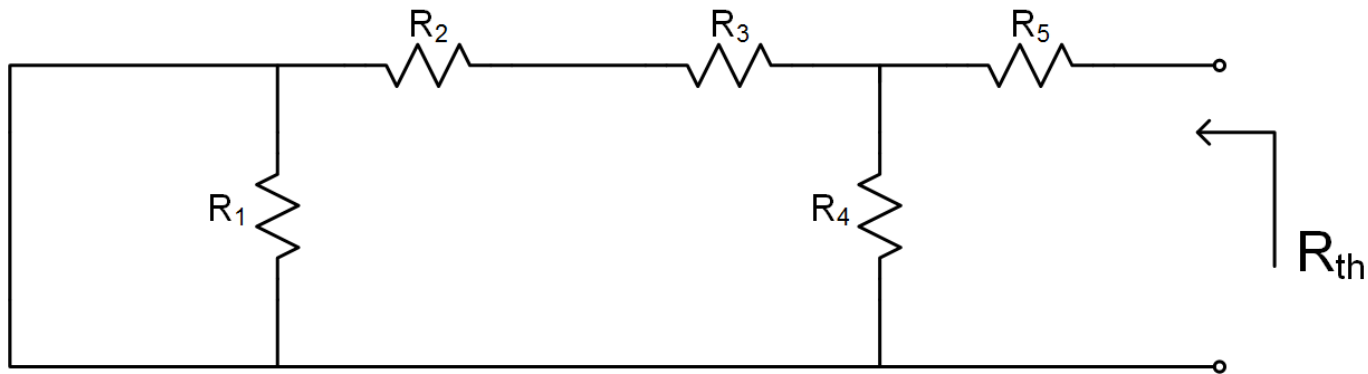
- ***Thévenin equivalent resistance, R_{th}***
 - Resistance seen between the two terminals with all independent sources set to zero
 - Voltage sources → short circuits
 - Current sources → open circuits



Thévenin Equivalent – Example

83

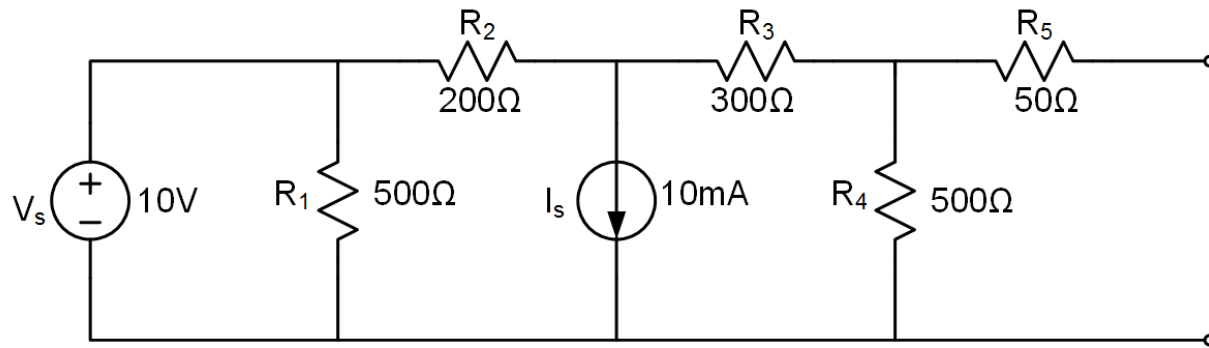- For a $100\ \Omega$ load connected to the following network, determine:
 - ▣ Load current, I_L
 - ▣ Load voltage, V_L





- Transform to a Thévenin equivalent circuit, then connect a $100\ \Omega$ load
 - ▣ I_L and V_L are then easily determined using Ohm's Law

Thévenin Equivalent – Example

84

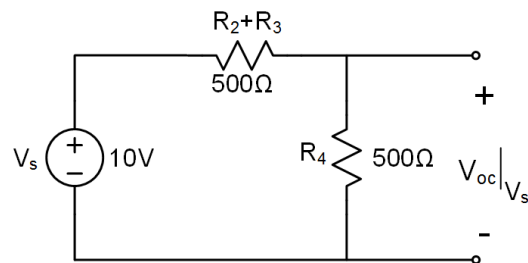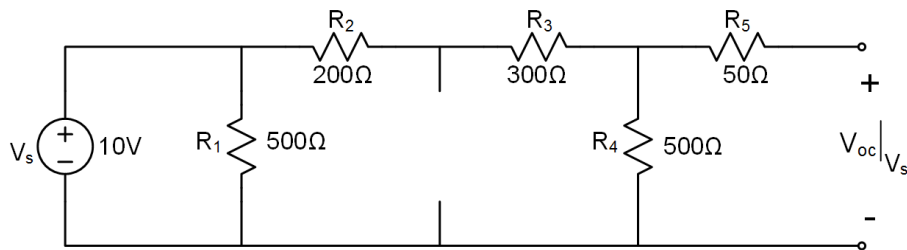- Analyze the circuit using any convenient technique
 - Nodal analysis would be a reasonable choice
 - Two independent sources – we'll use superposition




- First, find V_{OC} due to V_S
 - R_1 is in parallel with a voltage source, so it can be neglected
 - No current flows through R_5 so it can be neglected
 - Circuit reduces to a simple voltage divider

$$V_{oc} \Big|_{V_S} = 10 V \cdot \frac{500 \Omega}{1000 \Omega} = 5 V$$

Thévenin Equivalent – Example


85

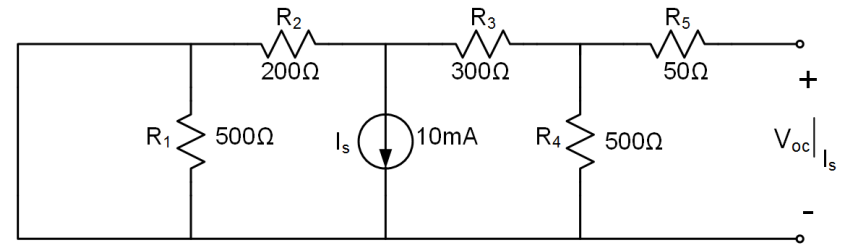- Next, find V_{oc} due to I_s
 - R_1 gets shorted, so it can be neglected
 - No current flows through R_5 so it can be neglected



- Circuit reduces to a simple current divider
 - Find I_3 to determine the terminal voltage
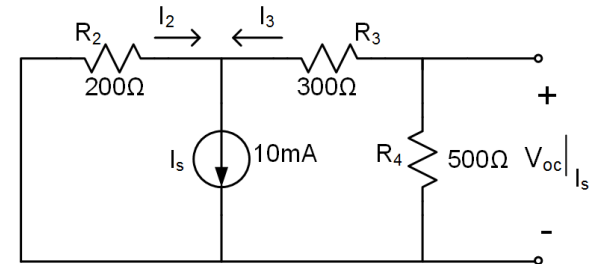
$$I_3 = 10 \text{ mA} \frac{200 \Omega}{1000 \Omega} = 2 \text{ mA}$$



- Terminal voltage is negative due to current direction

$$V_{oc} \Big|_{I_s} = -I_3 R_4 = -2 \text{ mA} \cdot 500 \Omega = -1 \text{ V}$$


- Open-circuit voltage is the sum of the individual components

$$V_{oc} = V_{oc} \Big|_{V_s} + V_{oc} \Big|_{I_s} = 5 \text{ V} - 1 \text{ V} = 4 \text{ V}$$

Thévenin Equivalent – Example

86

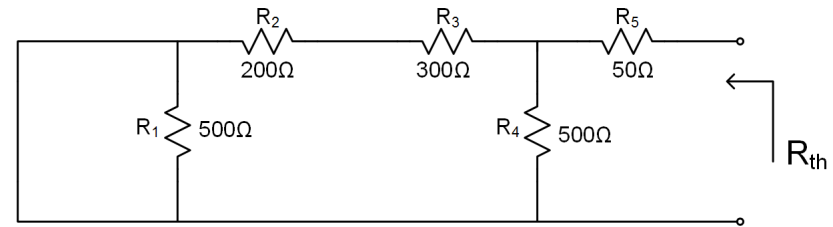
- Next, determine the Thévenin equivalent resistance, R_{th}
 - ▣ Set independent sources to zero
 - $V_s \rightarrow$ short circuit ($V = 0$)
 - $I_s \rightarrow$ open circuit ($I = 0$)
 - ▣ Determine equivalent resistance between the terminals
- R_1 is shorted
 - ▣ In parallel with a short circuit
- Combine other series and parallel resistors



$$R_{th} = R_5 + R_4 || (R_2 + R_3)$$

$$R_{th} = 50 \Omega + 500 \Omega || (200 \Omega + 300 \Omega)$$

$$R_{th} = 300 \Omega$$

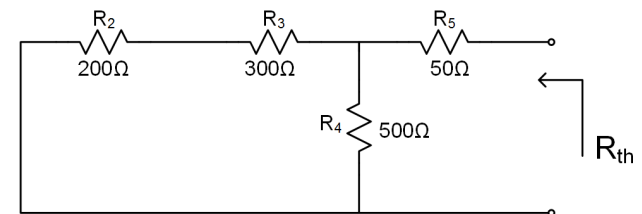

Thévenin Equivalent – Example

87

- The Thévenin equivalent circuit with a $100\ \Omega$ load connected:
- Voltage division gives the load voltage


$$V_L = V_{oc} \frac{R_L}{R_{th} + R_L} = 4\text{ V} \frac{100\ \Omega}{400\ \Omega}$$

$$V_L = 1\text{ V}$$

- Ohm's law gives the load current

$$I_L = \frac{V_L}{R_L} = \frac{1\text{ V}}{100\ \Omega}$$

$$I_L = 10\text{ mA}$$

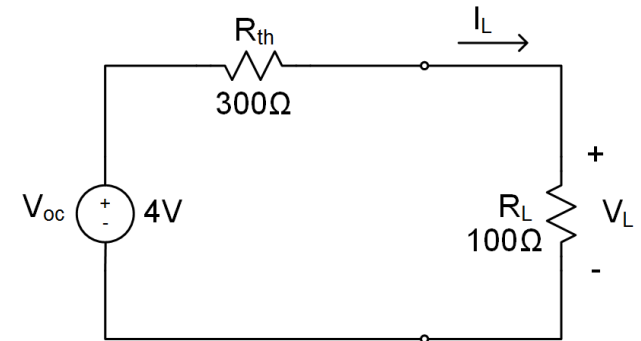

Norton Equivalent Circuits

88

- Norton's theorem:

Any two-terminal linear network of resistors and sources can be represented as single resistor in parallel with a single independent current source

- The resistor is the ***Thévenin equivalent resistance, R_{th}***
- The current source is the ***short-circuit current, I_{sc}***




Edward Lawry Norton, 1898 – 1983

Norton Equivalent Circuits

89

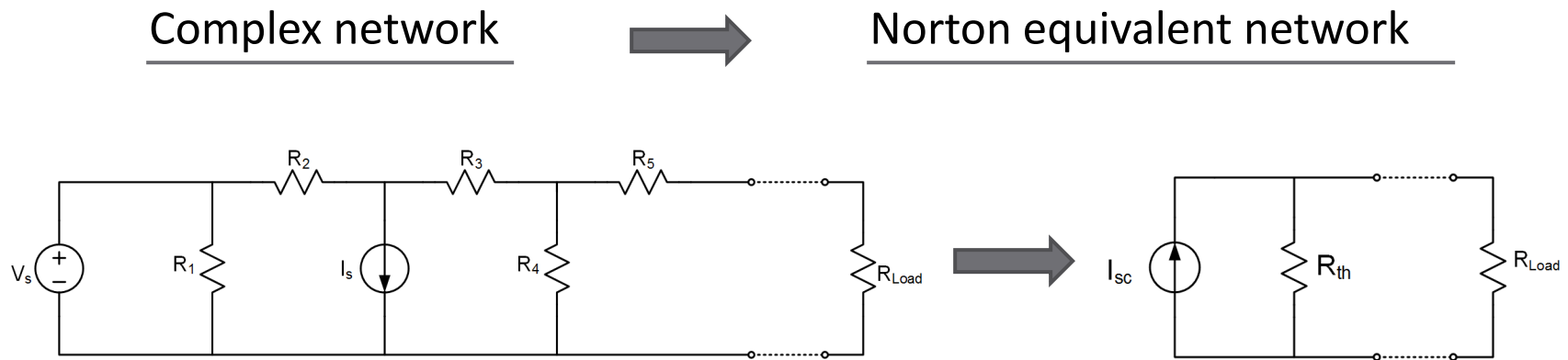
- An extension of Thévenin's Theorem
- Motivated by the development of vacuum tubes
 - ▣ More appropriately modeled with current sources
 - ▣ Same is true of the successors to tubes: transistors



Short-Circuit Current- I_{SC}

90

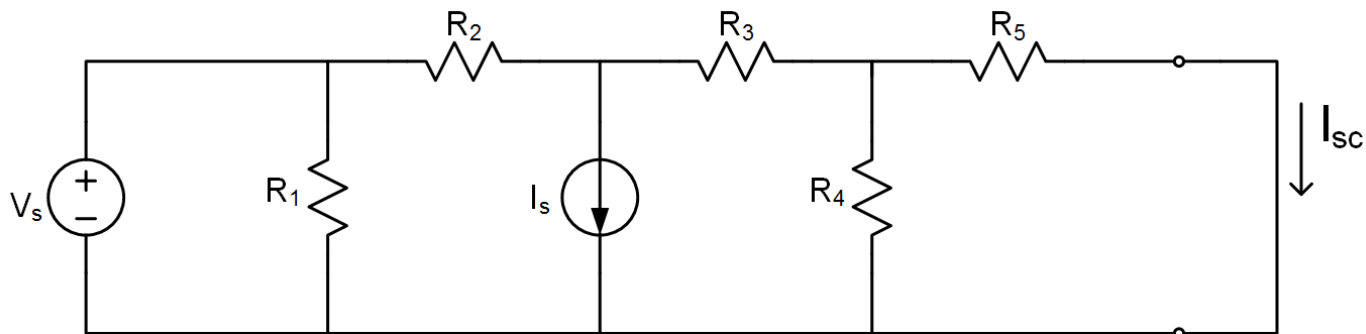
- **Short-circuit current, I_{SC}**
 - ▣ The current that flows between the **short-circuited** terminals
- Determine I_{SC} by using most convenient method
 - ▣ Ohm's Law
 - ▣ Kirchhoff's Laws
 - ▣ Voltage or current divider
 - ▣ Nodal or mesh analysis



Thévenin Resistance - R_{th}

91



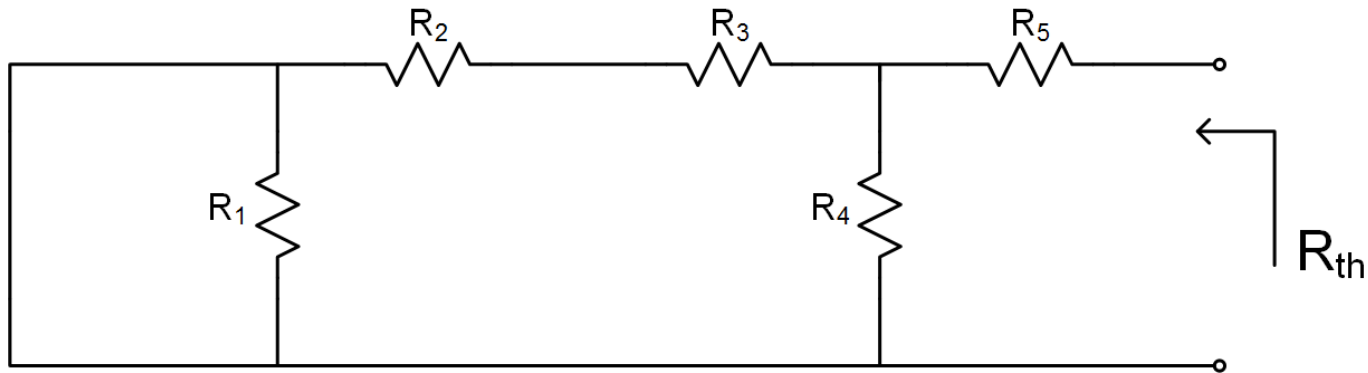
- **Thévenin equivalent resistance, R_{th} ,**
 - The same for a Norton equivalent circuit as for a Thévenin equivalent circuit
 - The resistance seen between the two terminals with all independent sources set to zero



Thévenin and Norton Equivalents

92

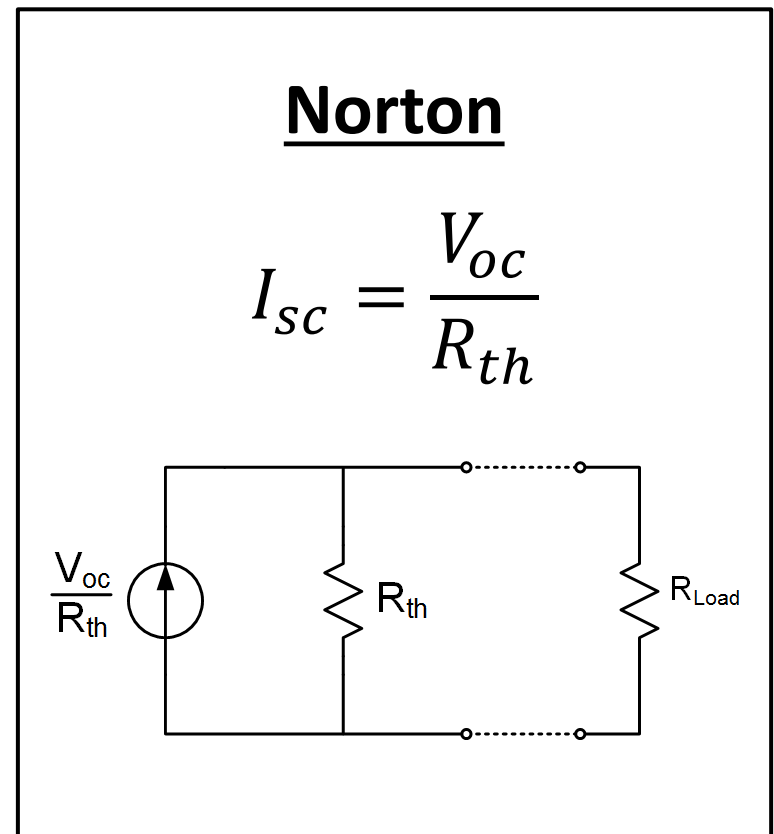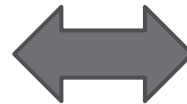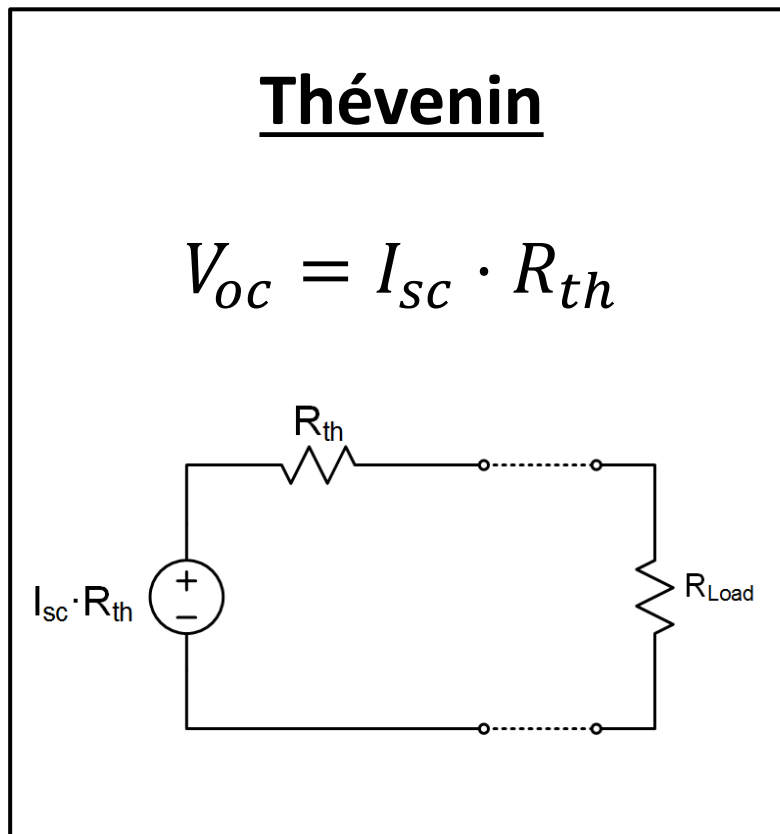
- Easily convert between Thévenin and Norton equivalent circuits



93

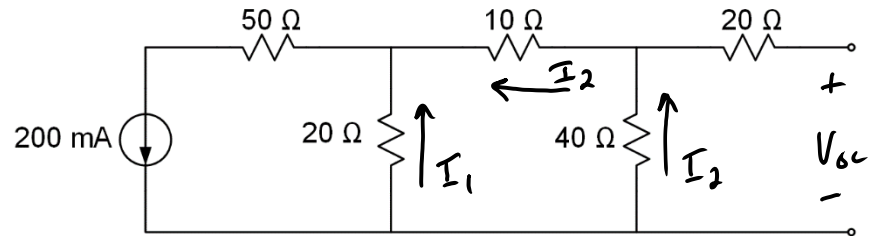Example Problems

Determine both the Thévenin and Norton equivalents for the following circuit.



First, find V_{oc}


$$V_{oc} = -I_2 \cdot 40\Omega$$

- No current through 20Ω resistor at terminals, so it has no impact on V_{oc} .
- Apply current division


$$I_2 = 200\text{ mA} \frac{20\Omega}{20\Omega + 10\Omega + 40\Omega} = 57.14\text{ mA}$$

$$V_{oc} = -57.14\text{ mA} \cdot 40\Omega = -2.29\text{ V}$$


Next, find R_{th}

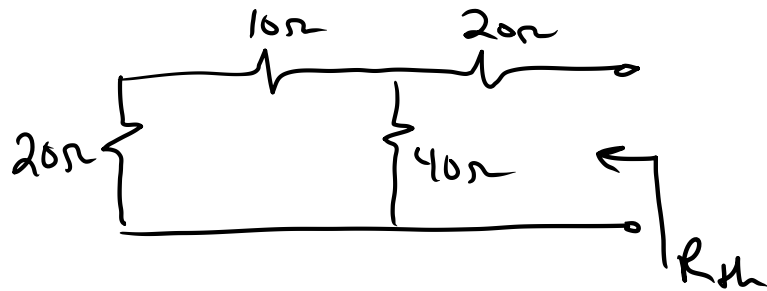

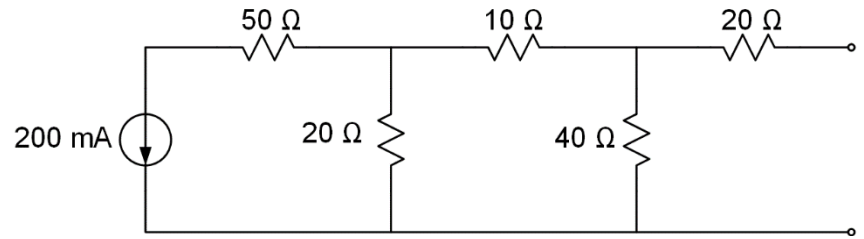
$$R_{th} = 20\Omega + 40\Omega // (10\Omega + 20\Omega) = \underline{37.1\Omega}$$



Theremin equivalent:

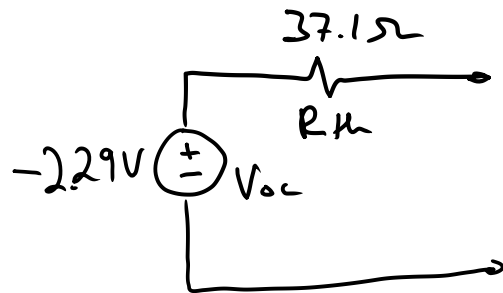


or

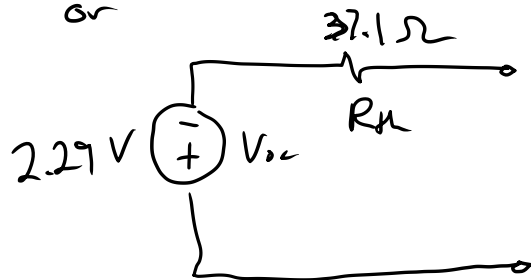


Norton equivalent

$$I_{sc} = \frac{V_{oc}}{R_{th}} = \frac{-2.29V}{37.1\Omega}$$

$$I_{sc} = -615\mu A$$

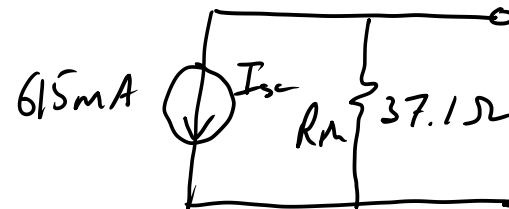

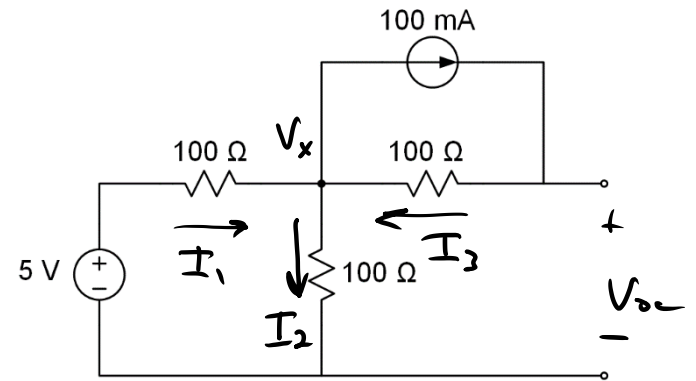Determine the Thévenin equivalent for the following circuit.



First, find V_{oc} . Apply KCL at V_x :

$$I_1 - I_2 + I_3 = 0$$

$$\frac{5V - V_x}{100\Omega} - \frac{V_x}{100\Omega} + \frac{V_{oc} - V_x}{100\Omega} - 100mA = 0$$

$$V_x \left(-\frac{1}{100\Omega} - \frac{1}{100\Omega} - \frac{1}{100\Omega} \right) + V_{oc} \left(\frac{1}{100\Omega} \right) = 100mA - \frac{5V}{100\Omega}$$

$$V_x (-30mA) + V_{oc} (10mA) = 50mA \quad (1)$$

KCL at V_{oc}

$$100mA - I_3 = 0$$

$$100mA - \frac{V_{oc} - V_x}{100\Omega} = 0$$

$$V_{oc} - V_x = 100 \text{ mA} \cdot 100 \Omega$$

$$V_{oc} = V_x + 10 \text{ V} \quad (2)$$

Substitute (2) \rightarrow (1)

$$V_x(-30 \text{ ms}) + V_x(10 \text{ ms}) + 10 \text{ V}(10 \text{ ms}) = 50 \text{ mA}$$


$$V_x(-20 \text{ ms}) = 50 \text{ mA} - 100 \text{ mA} = -50 \text{ mA}$$

$$V_x = \frac{-50 \text{ mA}}{-20 \text{ ms}} = 2.5 \text{ V}$$

Substitute V_x into (2)


$$V_{oc} = 2.5 \text{ V} + 10 \text{ V} = \underline{12.5 \text{ V}}$$

Finally, find R_{th} :

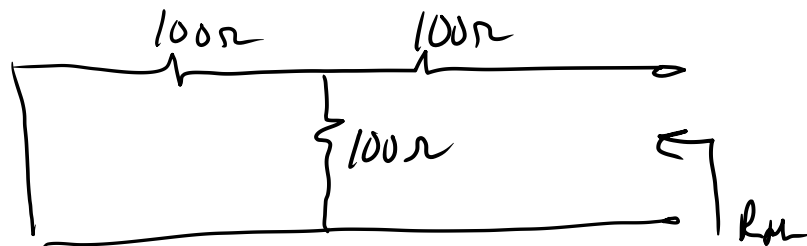


$$R_{th} = 100 \Omega + (100 \Omega \parallel 100 \Omega)$$



$$\underline{R_{th} = 50 \Omega}$$

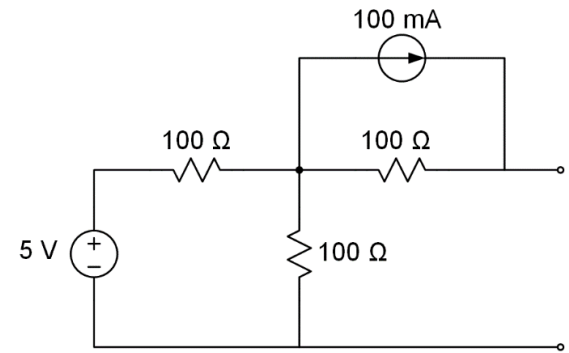

Thevenin equivalent:


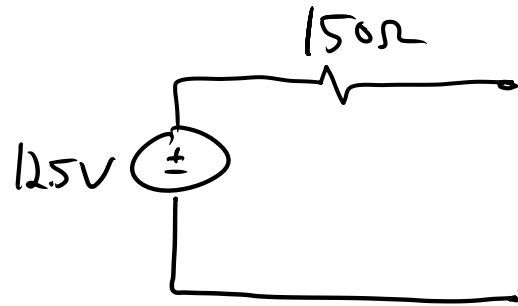


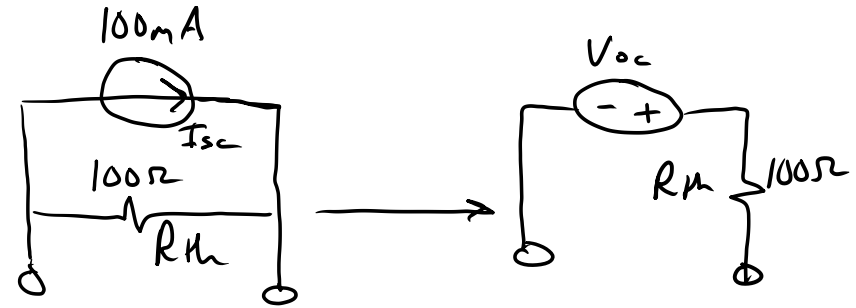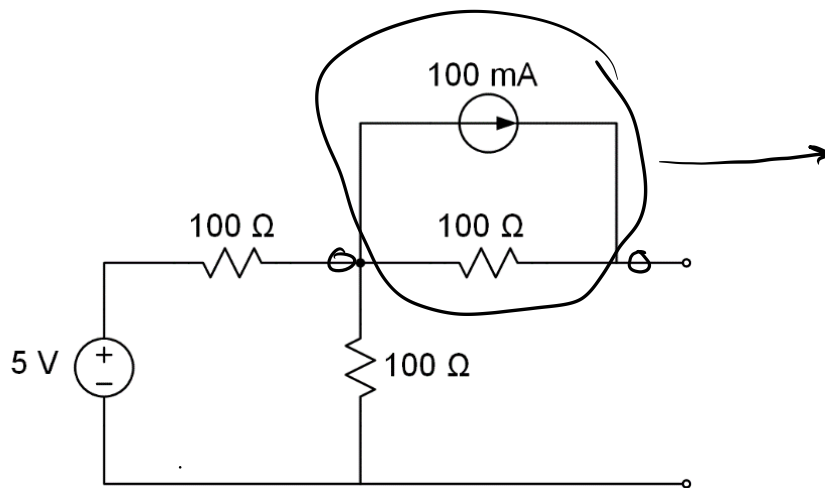Alternatively, could do a source transformation on the current source



$$V_{oc} = I_{sc} \cdot R_{th} = 100\text{mA} \cdot 100\Omega$$

$$V_{oc} = 10\text{V}$$

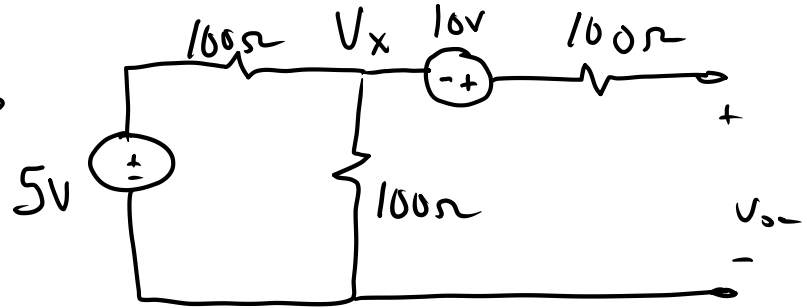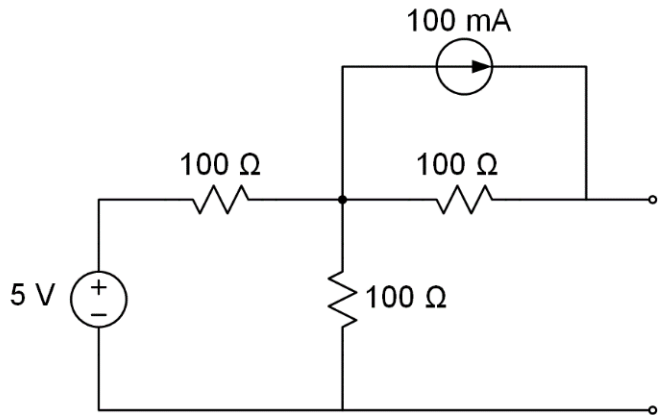


Now, apply voltage division to get V_x

$$V_x = 5V \frac{100\Omega}{100\Omega + 100\Omega} = 2.5V$$

And, clearly now, we have

$$V_{oc} = V_x + 10V = 12.5V \quad \rightarrow \quad \underline{V_{oc} = 12.5V}$$

R_{th} is the same as before

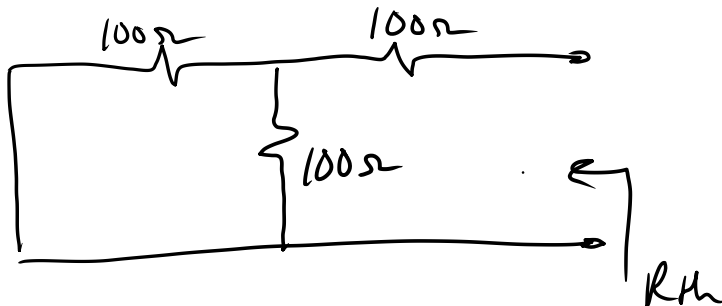

$$R_{th} = 100\Omega + 100\Omega \parallel 100\Omega$$

$$\underline{R_{th} = 150\Omega}$$