

# SECTION 4: OPERATIONAL AMPLIFIERS

ENGR 201 – Electrical Fundamentals I

2

# Introduction

# Amplification


3

## □ **Amplification**

### ▣ **Multiplication** of electrical signals

- Voltage or current
- Scaling factor: **gain**

### ▣ Performed by **amplifiers**

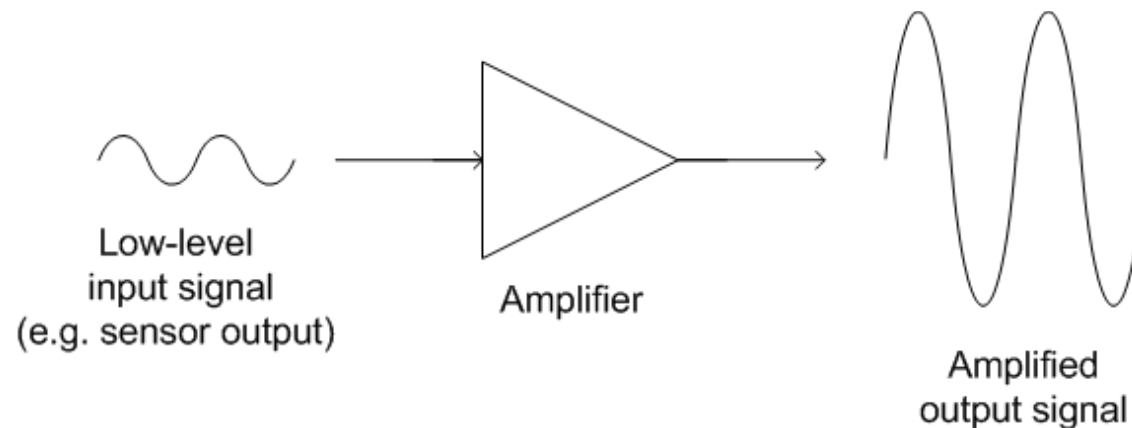

# Amplification – Why?

4

- Often want to ***increase the amplitude of small electrical signals***
  - Sensor outputs, e.g.:
    - Strain gauges
    - Pressure sensors
    - Flow meters
    - Temperature sensors
    - Photo-detectors, etc.
  - Wireless communication signals
  - Audio signals
- Larger signals are easier to measure
  - Utilize the full ***dynamic range*** of the measurement system
    - Higher accuracy

# Amplification – Why?

5

- Amplifiers are also useful for ***impedance conversion***
  - ▣ Make a high-resistance source look like a low resistance
  - ▣ Make a low-resistance load look like a high resistance
  - ▣ ***Buffering*** a high- resistance source from a low-resistance load
- A single amplifier circuit can provide amplification and impedance conversion

6

# Amplifier Fundamentals

# Amplifier Characteristics

7


## □ Key amplifier characteristics:

### ▣ ***Gain***

- May be designed for voltage, current, or power gain


### ▣ ***Input resistance***

### ▣ ***Output resistance***

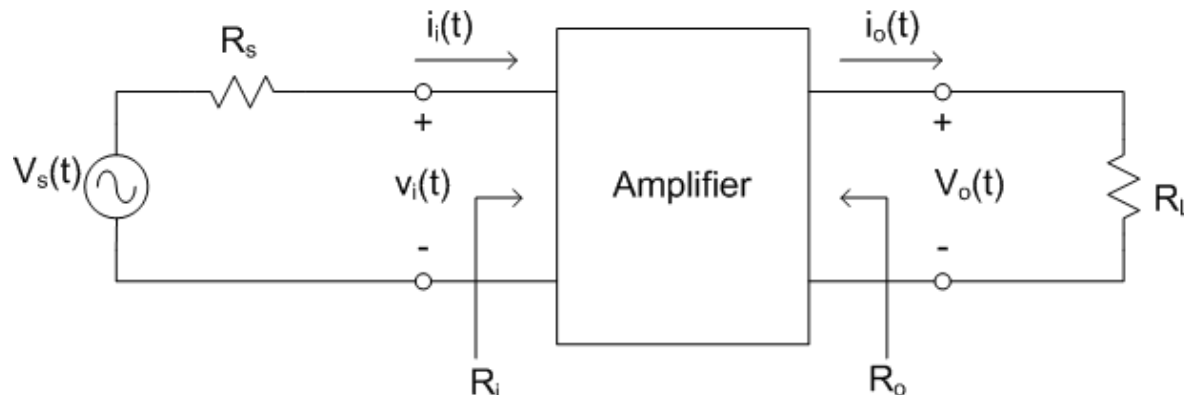

# Amplifier Characteristics - Gain

8

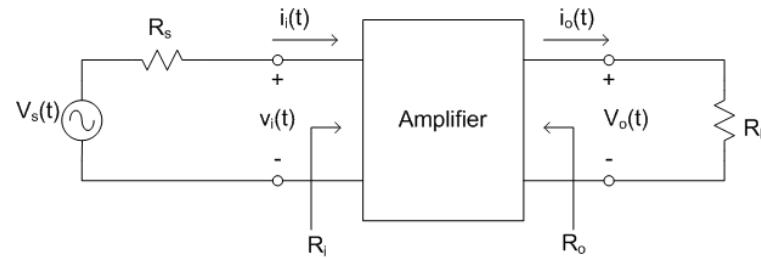

## □ **Voltage gain**

- ▣ Ratio of output to input voltage

$$A_V = \frac{v_o}{v_i}$$

## □ **Current gain**

- ▣ Ratio of output to input current

$$A_i = \frac{i_o}{i_i}$$

## □ **Power gain**


- ▣ Ratio of output to input power

$$G = \frac{P_o}{P_i}$$



# Amplifier Characteristics – Input Resistance


9

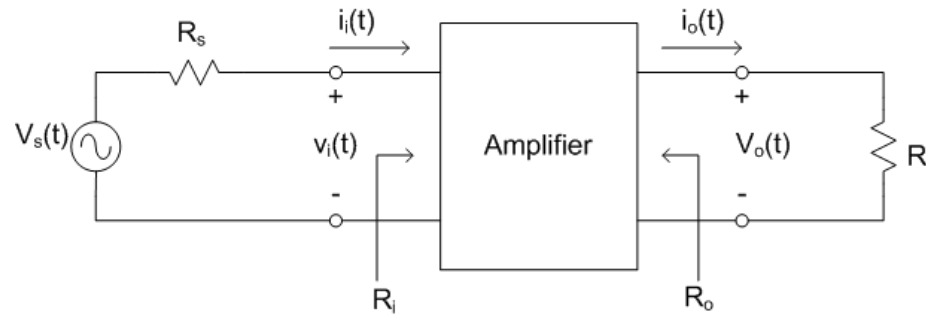

- **Input resistance,  $R_i$** 
  - ▣ Equivalent resistance seen looking into the amplifier
- Amplifier **loads** the source
  - ▣ Source appears to be connected to a resistance of  $R_i$
  - ▣ Possible voltage division between source resistance and input resistance

# Amplifier Characteristics – Output Resistance

10

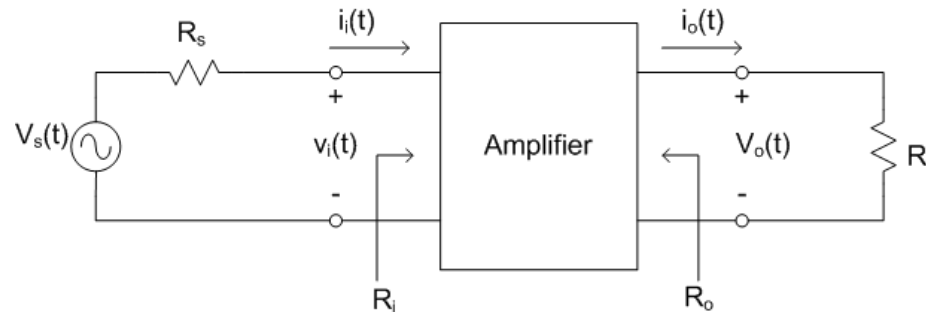


- **Output resistance,  $R_o$** 
  - Thévenin equivalent resistance of the amplifier output
- From the perspective of the load, amplifier output is the source
  - Modeled as Thévenin equivalent circuit, with resistance,  $R_o$
  - Possible voltage division between  $R_o$  and the load
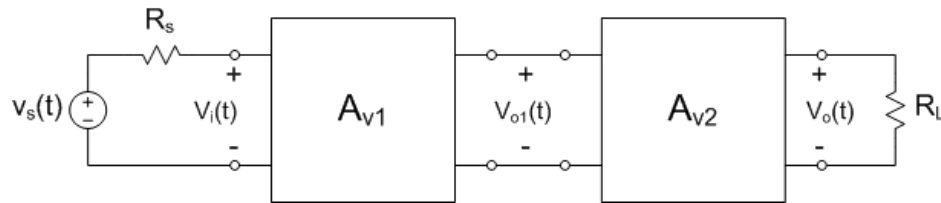
# Amplifier Characteristics – Cascaded Amplifiers

11

- Consider two amplifiers connected in ***cascade***



- Input to the second amplifier is the output from the first


$$v_{o1}(t) = A_{v1} \cdot v_i(t)$$

- Output of the second amplifier is the output of the cascade

$$v_o(t) = A_{v2} \cdot v_{o1}(t) = A_{v1} \cdot A_{v2} \cdot v_i(t)$$

- Overall gain is the ***product*** of the individual gains


$$A_v = A_{v1} \cdot A_{v2}$$

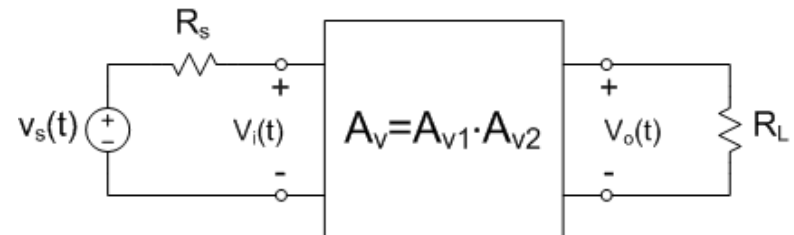

# Amplifier – Equivalent Circuit


12

- Amplifier equivalent circuit:

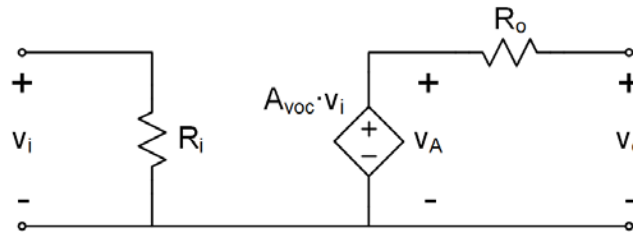

- $R_i$ : **input resistance**
- $R_o$ : **output resistance**
- $A_{voc}$ : **open-circuit voltage gain**
  - Note that, in general, due to loading:
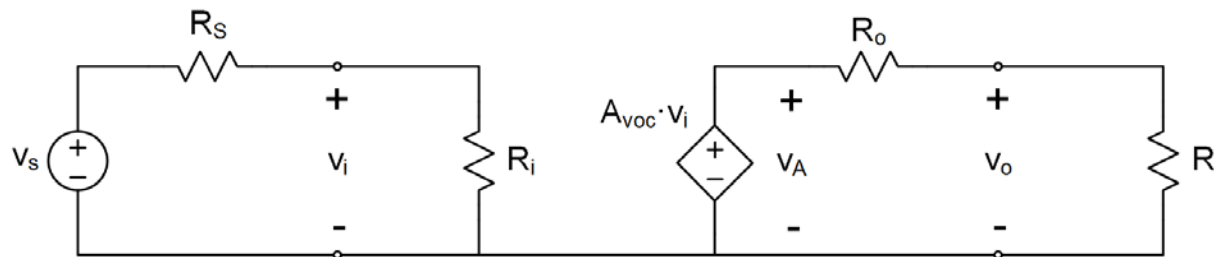
$$A_{voc} = \frac{v_A}{v_i} \neq A_v = \frac{v_o}{v_s}$$



13

# Opamp Fundamentals

# Operational Amplifiers - Opamps


14

- How do we get the amplification we need?
- Different requirements for different applications
  - ▣ High gain/low gain – Inverting/non-inverting gain
  - ▣ Accuracy
  - ▣ Adjustability
- Building amplifiers out of transistors is difficult, inconvenient
- Chip makers could make unique integrated circuits (ICs) for all possible applications
  - ▣ Impractical, not economical
- Instead: ***operational amplifiers (opamps)***
  - ▣ ***General-purpose*** amplifier ICs
  - ▣ Gain set by a few external components
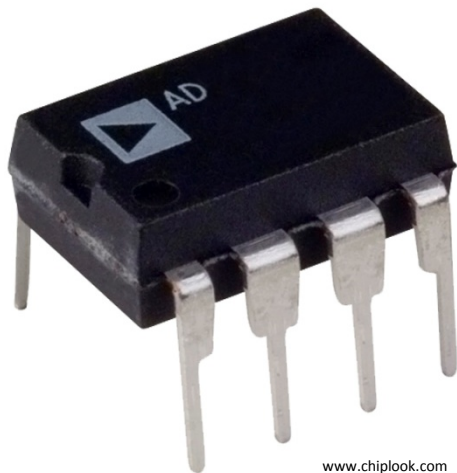
# Operational Amplifiers - Opamps

15

- High-gain amplifiers built from many transistors, resistors, and capacitors
- **Integrated circuits (ICs)**
  - All components fabricated on a single semiconductor (e.g. Si) chip
- Gain set by a few external resistors




[www.chiplook.com](http://www.chiplook.com)




# Ideal Opamps

16

- Schematic symbol:

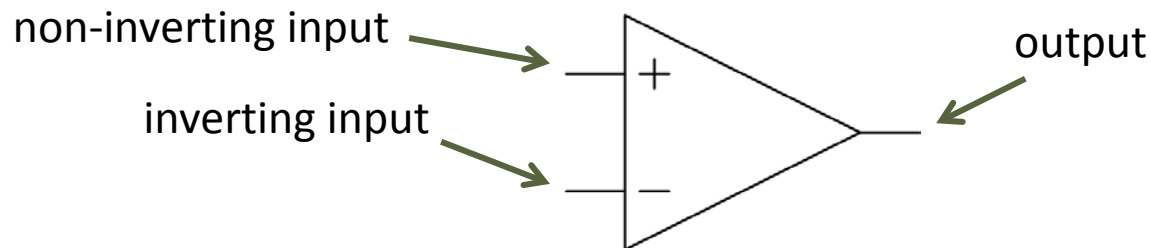

- Equivalent circuit:

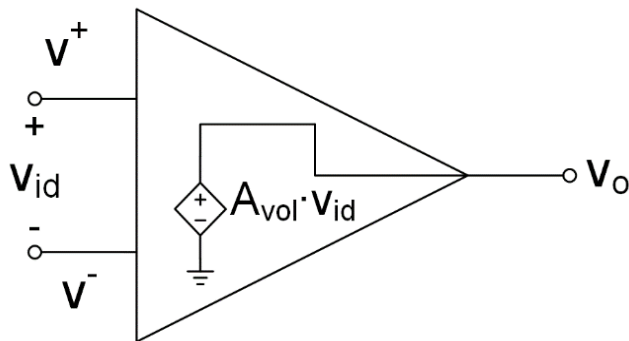

- Open-loop voltage gain,  $A_{vol}$ 
  - ▣ Gain of the opamp without feedback

- **Differential input,  $v_{id}$**

- ▣ Difference between the two input voltages

$$v_{id} = v^+ - v^-$$

- **Common-mode input,  $v_{icm}$**

$$v_{icm} = \frac{(v^+ + v^-)}{2}$$



# Ideal Opamp Characteristics

17

- Ideal opamp characteristics:
  - 1) ***Infinite input resistances*** – at  $v^+$  and  $v^-$ 
    - No current flows into either input terminal
  - 2) ***Infinite open-loop gain***
    - Any differential input will result in an infinite output
  - 3) **Zero output resistance**
    - Immune to the effect of loading

# Infinite Gain

18

- Ideal opamps have infinite gain
  - ▣ How do we get a gain of 2 or 9 or -3?

## ***Negative feedback***

- By enclosing the opamp in a ***feedback loop*** we can create an amplifier with useable gain
- Before applying feedback to opamp circuits, we'll first introduce the concept of feedback

19

# Introduction to Feedback

# Feedback

20

## □ **Feedback**

- A process in which a portion of the output of some system is *fed back* to the input of that system

## □ **Positive feedback**

- The **addition** of a portion of the output to the input
- Generally has a *destabilizing* effect

## □ **Negative feedback**

- The **subtraction** of portion of the output from the input
- Generally has a *stabilizing* effect
- All opamp *amplifiers* we will encounter in this course employ negative feedback

# Feedback

21

- Feedback is everywhere:
  - HVAC
  - Cruise control
  - Robotics
  - Amplifiers
  - Toilets
  - Ovens
  - Autonomous vehicles
  - Etc.
  
- A very important concept in many engineering fields, particularly ***controls*** and ***electronics***


# Signal Flow Diagrams

22

## □ **Signal flow diagrams**

- Block diagrams
- Show the flow of signals – energy, information, etc. – through a system
- Used for all types of engineering systems: electrical, mechanical, etc.
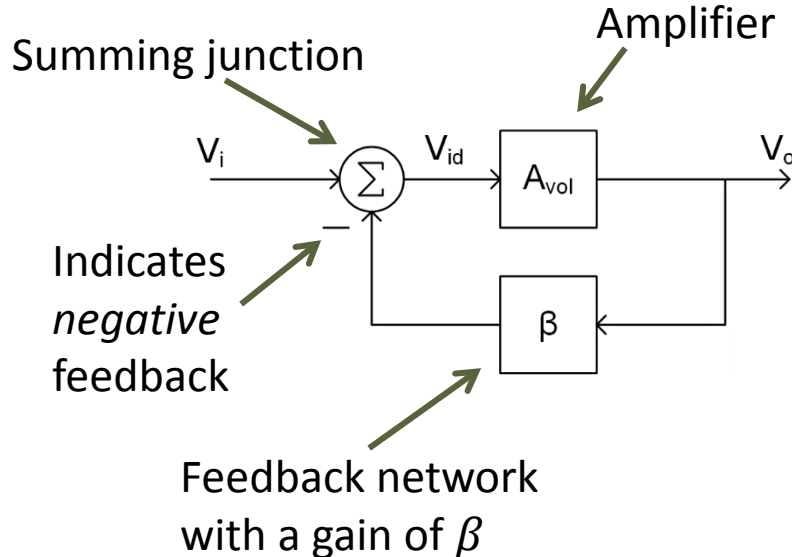
## □ Amplifier, with open-loop gain $A_{vol}$ , enclosed in a feedback loop:



- Amplifier is in a **closed-loop** configuration
- Feedback gain  $\beta$ , determines how much output is fed back
- Difference between input and feedback is amplifier input
- $\beta$  determines overall gain
  - Closed-loop gain

# Closed-Loop Gain

23

## □ **Open-loop gain**

- Gain of amplifier without feedback

$$A_{vol} = \frac{v_o}{v_{id}}$$

## □ **Closed-loop gain**

- Gain of the closed-loop amplifier

$$A_{vcl} = \frac{v_o}{v_i}$$


## □ Calculating the closed-loop gain:

$$v_o = v_{id} \cdot A_{vol} = (v_i - \beta v_o) A_{vol}$$

$$v_o + \beta \cdot v_o \cdot A_{vol} = v_i \cdot A_{vol}$$

$$v_o(1 + \beta \cdot A_{vol}) = v_i \cdot A_{vol}$$
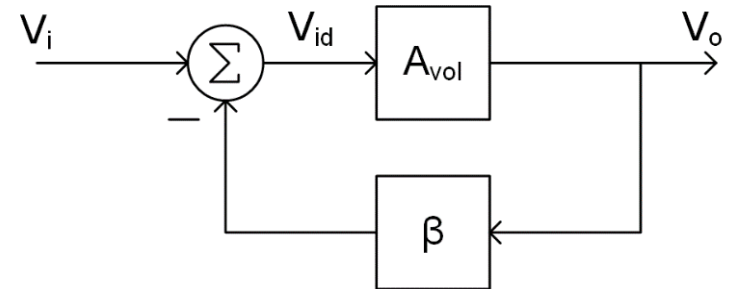
$$A_{vcl} = \frac{v_o}{v_i} = \frac{A_{vol}}{1 + \beta \cdot A_{vol}}$$




# Closed-Loop Gain

24

$$A_{vcl} = \frac{v_o}{v_i} = \frac{A_{vol}}{1 + \beta \cdot A_{vol}}$$

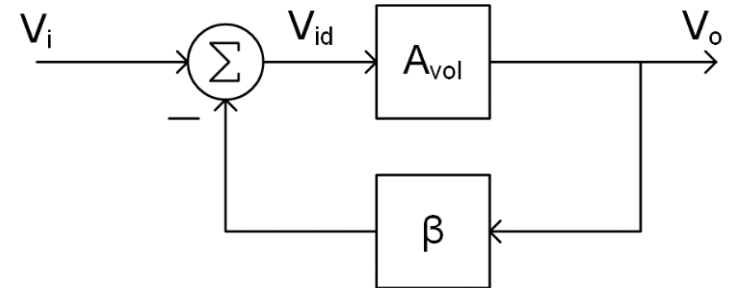- Consider the case of ***infinite open-loop gain***
  - ▣ E.g., an ideal opamp



$$\lim_{A_{vol} \rightarrow \infty} A_{vcl} = \lim_{A_{vol} \rightarrow \infty} \frac{A_{vol}}{1 + \beta \cdot A_{vol}}$$

$$\lim_{A_{vol} \rightarrow \infty} A_{vcl} = \lim_{A_{vol} \rightarrow \infty} \frac{A_{vol}}{\beta \cdot A_{vol}} = \frac{1}{\beta}$$

- Feedback gain, alone, determines the closed-loop gain
  - ▣ For example, to get a gain of four, feed back one quarter of the output signal



# Summing Point Constraint

25

- For  $A_{vol} = \infty$ , the differential input is

$$v_{id} = v_i - \beta v_o = v_i - \beta \frac{1}{\beta} v_i$$

$$v_{id} = v_i - v_i = 0$$

- A very important result, the ***summing-point constraint***:

***The input to an infinite-gain amplifier, enclosed in a negative feedback loop, is zero!***


- Any non-zero input would yield infinite output
- Along with the properties of ideal opamps, the summing-point constraint will be essential for analyzing opamp circuits

# Opamps as Feedback Systems

26


- **Any amplifier** enclosed in a negative feedback loop:

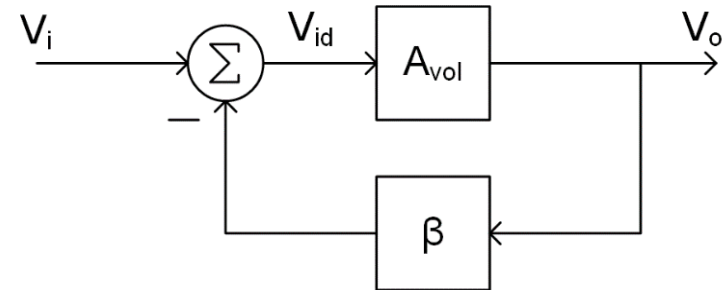- Output scaled by  $\beta$  and fed back
- Feedback signal subtracted from the input at a summing junction
- If  $A_{vol} = \infty$ , then  $v_{id} = 0$



- **Ideal opamp** enclosed in a negative feedback loop:

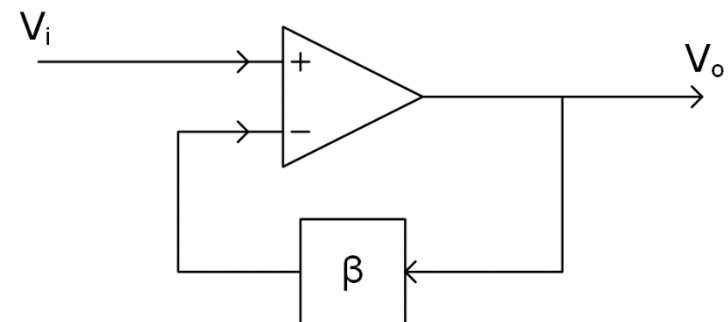- Output scaled by  $\beta$  and fed back
- Differential input is a built-in summing junction
- $v_{id} = 0$ , so  $v^+ = v^-$
- A **virtual short** between input terminals



27

# Example Problems

An amplifier with a gain of 4 is used to amplify the output of a sensor. The amplifier has an input resistance of  $1\text{ k}\Omega$  and an output resistance of  $100\ \Omega$ . The sensor has an open-circuit voltage of  $1\text{ V}$ , and an output resistance of  $50\ \Omega$ . The amplifier drives a  $5\text{ k}\Omega$  load. What is the amplifier's output voltage?



An amplifier is enclosed in a negative feedback loop with a feedback gain of 0.5. Determine the closed-loop gain for an amplifier with an open-loop gain of:

- a) 10
- b) 100E3



A 1 V input is applied to an opamp enclosed in a negative feedback loop with a feedback gain of 0.2. Determine the differential input voltage for an opamp with an open-loop gain of:

- a) 10
- b) 100E3





34

# Opamp Amplifiers

# Analysis of Ideal Opamp Circuits

35


- Key properties for analysis of opamp circuits:
  - 1) Infinite input resistance – no input current
  - 2) Virtual short between inverting and non-inverting input terminals (as long as there is negative feedback)
  - 3) Infinite open-loop gain
- If there is negative feedback, 1 and 2 are sufficient

# Opamp Amplifiers


36

- Two basic opamp amplifier configurations:

## Non-inverting amplifier:

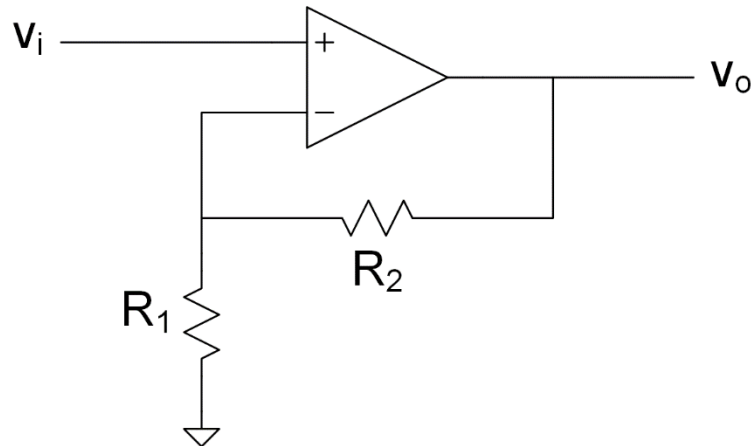

## Inverting amplifier:

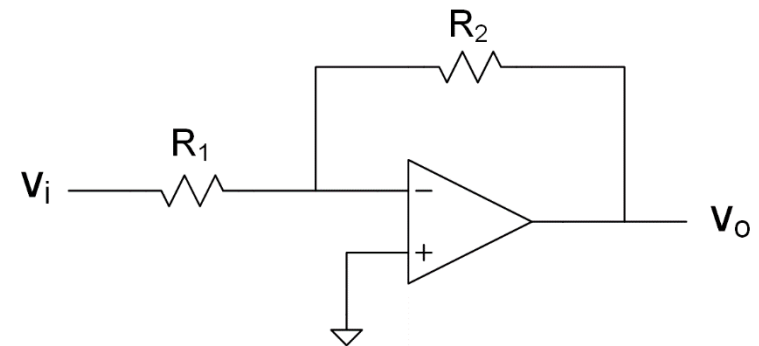

37

# Non-Inverting Amplifier

# Non-Inverting Amplifier – Gain

38

- **Non-inverting amplifier** gain:
- Negative feedback, so the **summing-point constraint** applies

$$v^- = v^+ = v_i$$


- **Zero opamp input current**, so KCL at the inverting terminal gives:

$$i_1 = i_2$$

$$\frac{v_o - v^-}{R_2} = \frac{v^-}{R_1}$$

- Applying the summing-point constraint
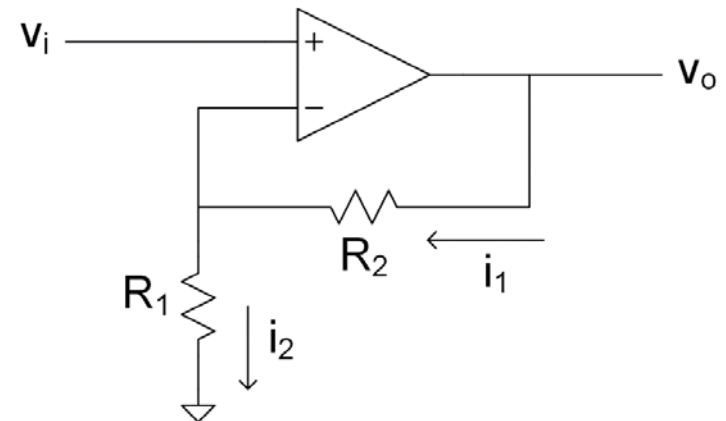
$$\frac{v_o - v_i}{R_2} = \frac{v_i}{R_1}$$



# Non-Inverting Amplifier – Gain

39

$$\frac{v_o - v_i}{R_2} = \frac{v_i}{R_1}$$

- Solving for the amplifier output


$$v_o = v_i \left( \frac{1}{R_1} + \frac{1}{R_2} \right) R_2$$

- Dividing both sides by  $v_i$  gives the non-inverting amplifier gain:

$$A_v = \frac{v_o}{v_i} = \frac{R_1 + R_2}{R_1}$$


- Note that this is the inverse of the feedback path gain
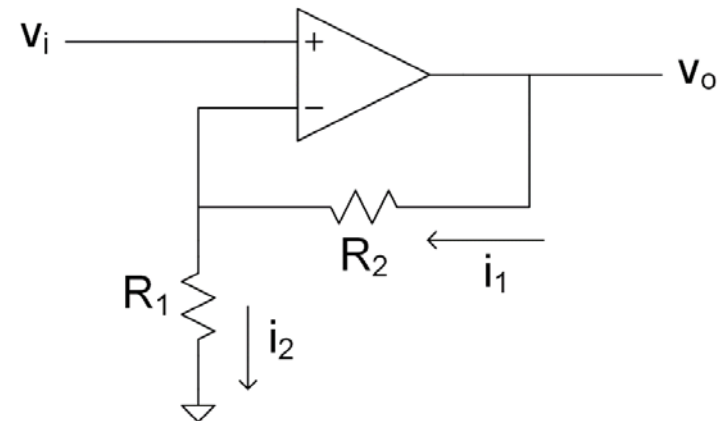
$$A_v = \frac{1}{\beta} = \frac{1}{\frac{R_1}{R_1 + R_2}}$$



# Non-Inverting Amplifier – Gain

40

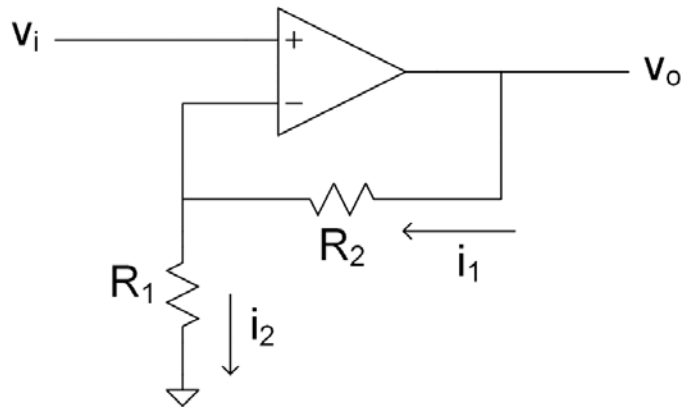


$$A_v = \frac{v_o}{v_i} = \frac{R_1 + R_2}{R_1}$$

- Gain determined entirely by the relative value of two external resistors
  - ▣ Any gain value is possible
  - ▣ Resistor tolerance sets amplifier gain tolerance
- Gain is **positive** (non-inverting)
  - ▣ As input goes up, output goes up
- Gain can never be less than one
  - ▣ Unity gain for  $R_2 = 0 \Omega$



# Non-Inverting Amplifier – $R_i$ and $R_o$

41

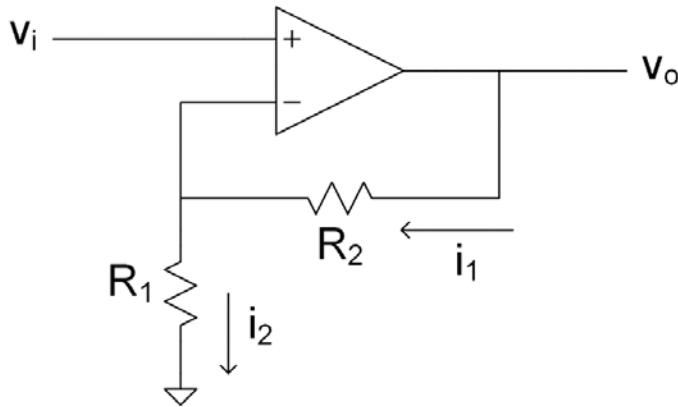

- Input resistance,  $R_i$ :
  - ▣ Input connected directly to input terminal of ideal opamp

$$R_i = \infty$$

- Output resistance,  $R_o$ :
  - ▣ Output is the output from an ideal opamp

$$R_o = 0 \Omega$$

42


# Inverting Amplifier

# Inverting Amplifier – Gain

43

- **Inverting amplifier** gain:
- Negative feedback, so the **summing-point constraint** applies

$$v^- = v^+ = 0$$

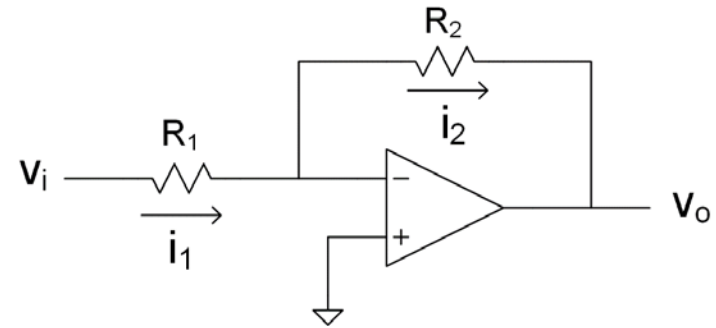

- **Zero opamp input current**, so KCL at the inverting terminal gives:

$$i_1 = i_2$$


$$\frac{v_i}{R_1} = \frac{-v_o}{R_2}$$

- Gain of the inverting amplifier:

$$A_v = \frac{v_o}{v_i} = -\frac{R_2}{R_1}$$

# Inverting Amplifier – Gain

44

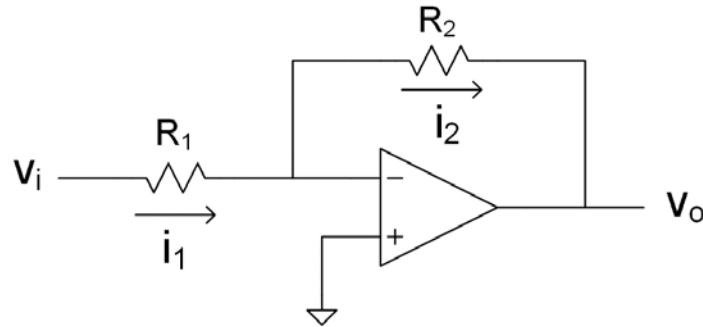

$$A_v = \frac{v_o}{v_i} = -\frac{R_2}{R_1}$$


- Again, gain determined entirely by external resistor values
- Gain is **negative** (inverting)
  - ▣ As input goes up, output goes down
- Gain can be any value
  - ▣  $A_v < 1$  for  $R_1 > R_2$

# Inverting Amplifier – $R_i$

45

- Input resistance,  $R_i$ :
  - ▣ Inverting terminal is a **virtual ground**, so

$$i_i = \frac{v_i}{R_1}$$

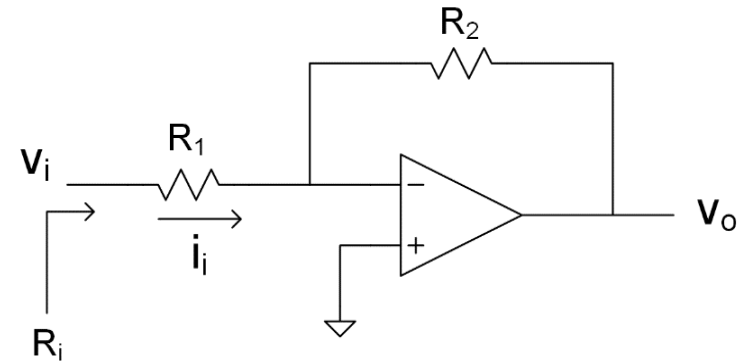

- By definition, input resistance is

$$R_i = \frac{v_i}{i_i} = v_i \frac{R_1}{V_i}$$

$$R_i = R_1$$


- ▣ Input is a resistance,  $R_1$ , to (*virtual*) ground

# Inverting Amplifier – $R_o$

46


- Output resistance,  $R_o$ :
  - ▣ Output is the output of an ideal opamp, so

$$R_o = 0 \Omega$$

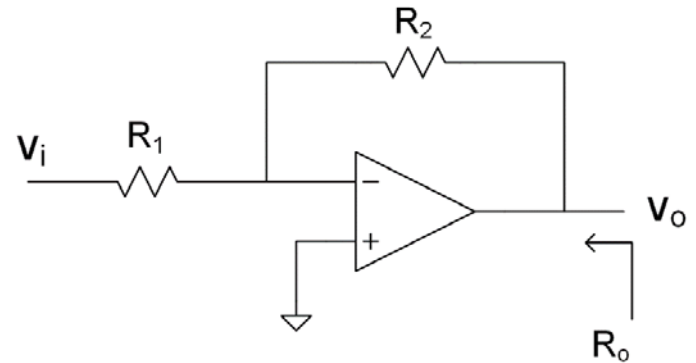

- Consider a non-ideal opamp with non-zero output resistance:

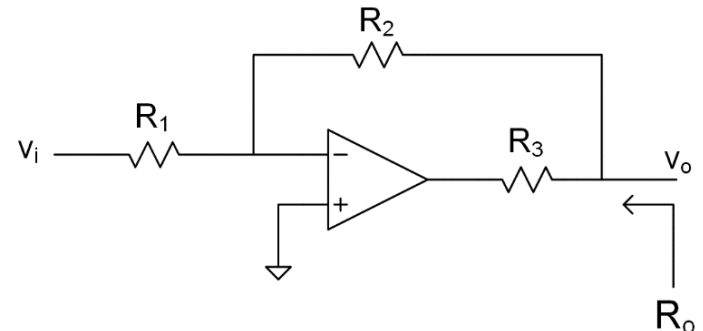
- ▣  $R_3$  is driven by a **dependent source**
  - ▣ Determining  $R_o$  is a bit trickier


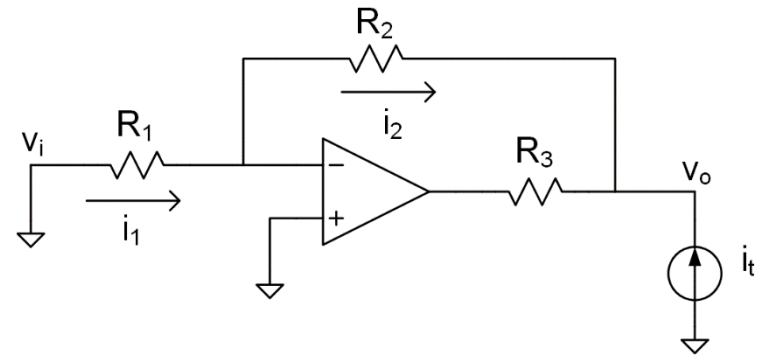
# Inverting Amplifier – $R_o$

47

- To determine a terminal resistance in the presence of ***dependent*** sources:
  - ▣ Set all *independent* sources to zero
    - Here, ground the input,  $v_i$
  - ▣ Apply a test current,  $i_t$ , to the terminal of interest
  - ▣ Analyze the circuit to determine the voltage at that terminal
  - ▣ Resistance at that terminal is given by



$$R_o = \frac{v_o}{i_t}$$

# Inverting Amplifier – $R_o$


48

- Still a virtual ground at the inverting terminal, so

$$i_1 = i_2 = \frac{v_i}{R_1} = \frac{0\text{ V}}{R_1} = 0$$

$$i_2 = -\frac{v_o}{R_1} = 0$$

$$v_o = 0$$

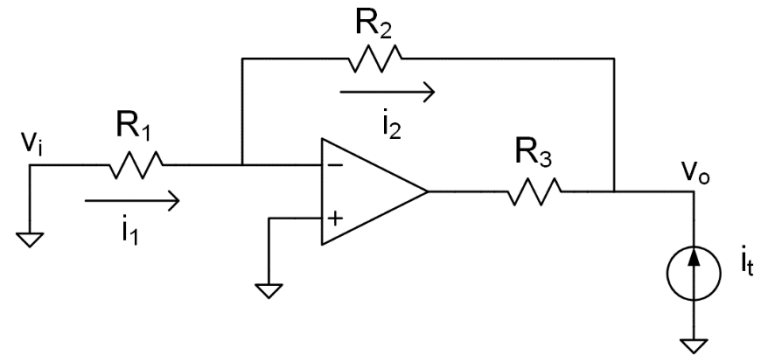

- The output is zero, independent of  $i_t$  (and independent of  $R_3$ ), so

$$R_o = 0\ \Omega$$



- **Feedback around an infinite gain amplifier forces the closed-loop output resistance to zero, even if the output resistance of the amplifier itself is non-zero**




49
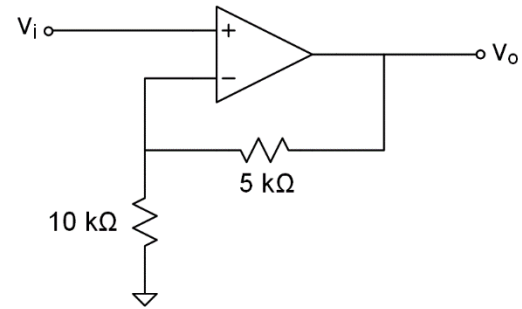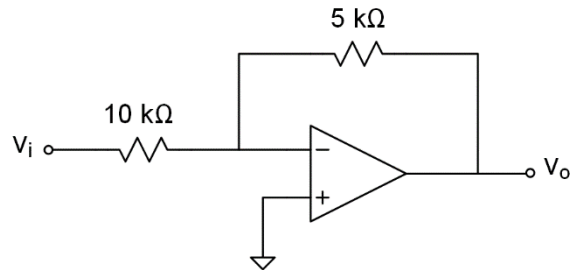
# Example Problems


Determine the gain of the following circuits.




Determine the output voltage,  $V_o$ .

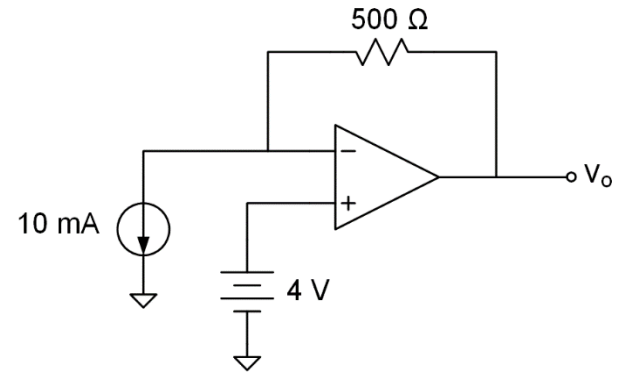


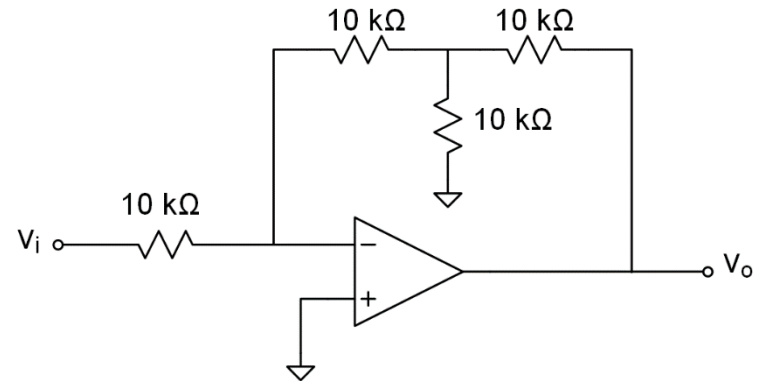
Determine the gain of the following circuit.



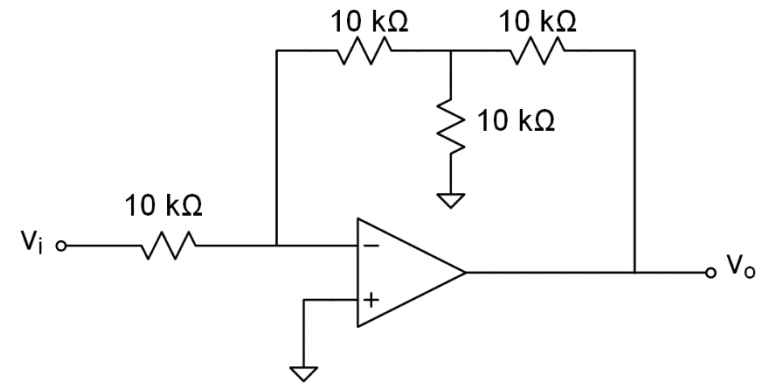


Determine the output voltage,  $V_o$ .

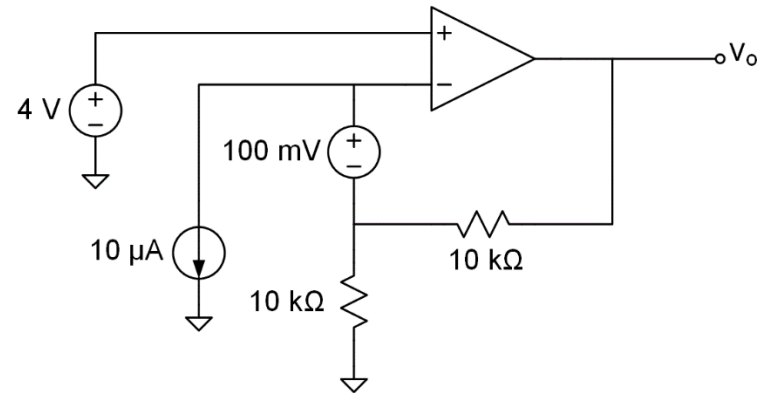

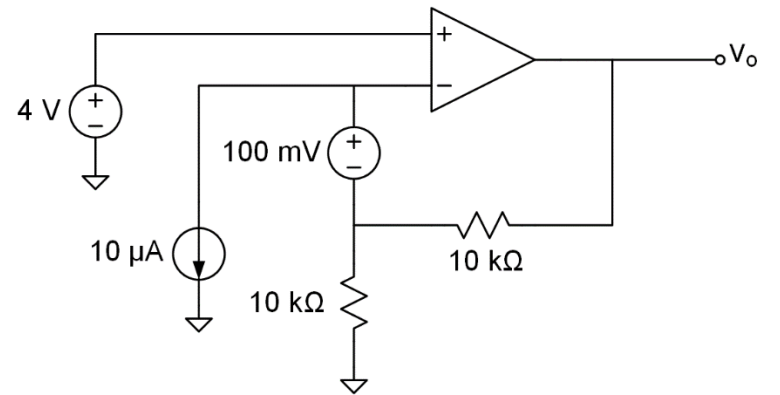

Determine the LED bias current,  $I_o$ .

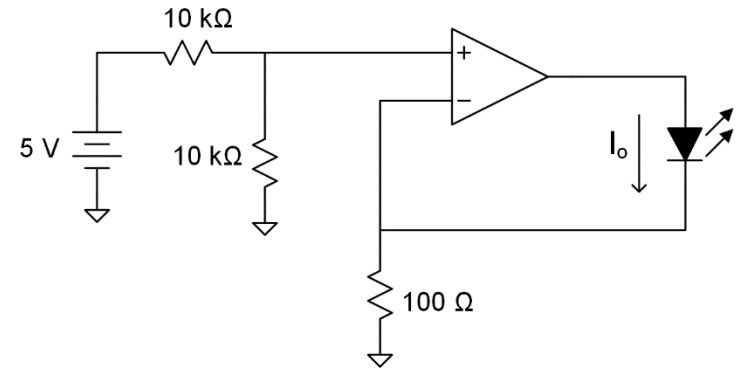




57

# Unity-Gain Buffer
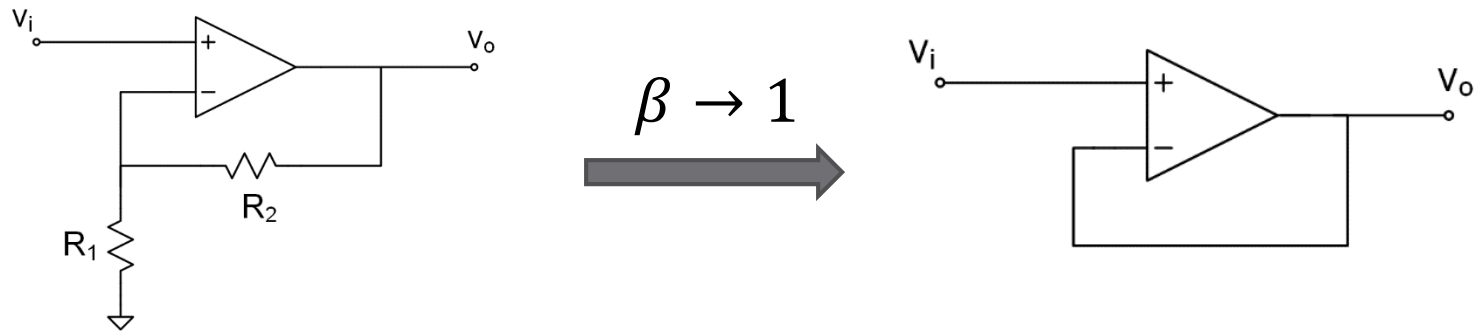
# Unity-Gain Buffer

58

- Start with a non-inverting amplifier, and let the feedback path gain go to unity



- Inverting terminal is connected directly to the output

$$v^- = v_o$$

- Virtual short at the input terminals

$$v^- = v^+ = v_i = v_o$$


- Closed-loop gain is **unity**

$$A_v = \frac{v_o}{v_i} = 1$$
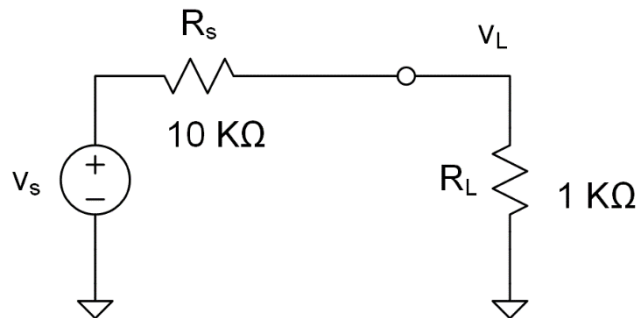
# Unity-Gain Buffer – Buffering

59

- What good is an amplifier with unity gain?
  - ▣ **Impedance conversion**
  - ▣ A **buffer** between a high-resistance source and a lower-resistance load
  - ▣ Eliminates loading effects
- Consider the following scenario:
  - ▣ Sensor with  $R_{th} = 10\text{ k}\Omega$  drives a load of  $R_L = 1\text{ k}\Omega$



- Signal measured at the load is attenuated


$$v_L = v_s \frac{R_L}{R_s + R_L} = v_s \frac{1\text{ k}\Omega}{11\text{ k}\Omega}$$

$$v_L = \frac{1}{11} v_s$$
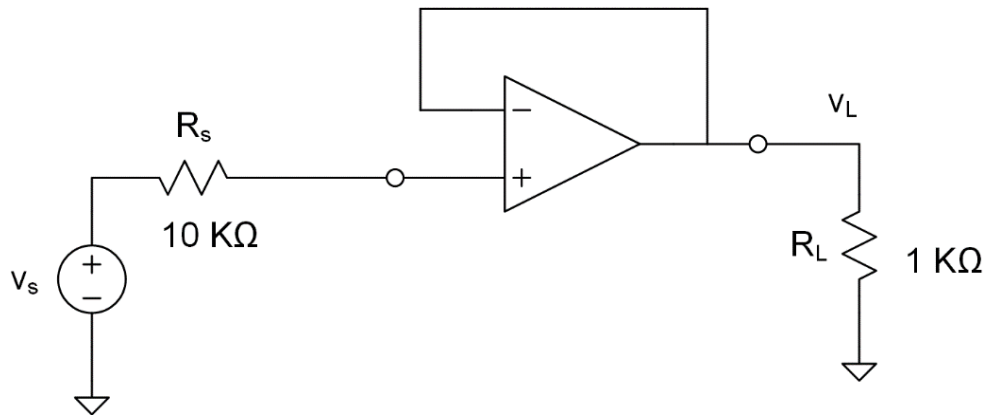
# Unity-Gain Buffer – Buffering

60

- To prevent signal attenuation due to loading:
  - ▣ Add a unity-gain buffer between the source and the load
- Buffer input is the load for the source
  - ▣  $R_i = \infty$
- Buffer output is the source for the load
  - ▣  $R_o = 0 \Omega$



- Now, full sensor signal appears across the load

$$v_L = v^+ = v_s$$

61

# Summing & Difference Amplifiers


# Summing Amplifier

62

- KCL at the inverting node:

$$i_A + i_B + i_C = i_f$$
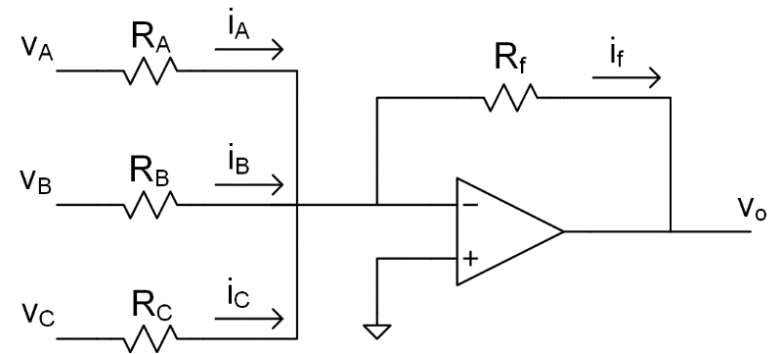
$$\frac{v_A}{R_A} + \frac{v_B}{R_B} + \frac{v_C}{R_C} = -\frac{v_O}{R_F}$$



- Output is the (inverted) **weighted sum** of all of the inputs

$$v_O = -R_F \left( \frac{v_A}{R_A} + \frac{v_B}{R_B} + \frac{v_C}{R_C} \right)$$

- For the special case of  $R_A = R_B = R_C = R_i$ :

$$v_O = -\frac{R_F}{R_i} (v_A + v_B + v_C)$$

# Difference Amplifier



63

- This looks a bit like a combination of a non-inverting and an inverting amplifier
- Analyze by applying **superposition**
- First, set  $v_2 = 0$ 
  - A non-inverting amplifier with a voltage divider at the input

$$v_o \Big|_{v_1} = v^+ \frac{R_1 + R_2}{R_1}$$

$$v^+ = v_1 \frac{R_4}{R_3 + R_4}$$

$$v_o \Big|_{v_1} = v_1 \frac{R_4}{R_3 + R_4} \frac{R_1 + R_2}{R_1}$$

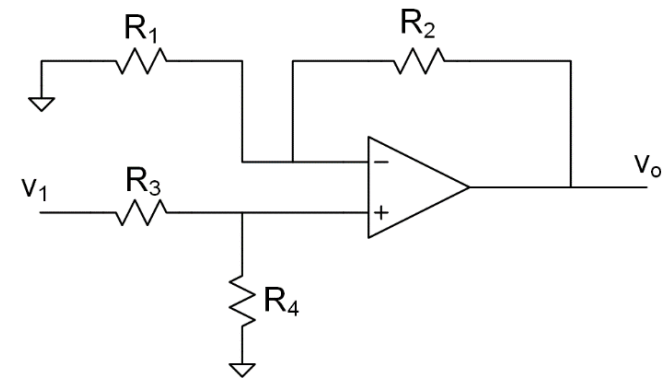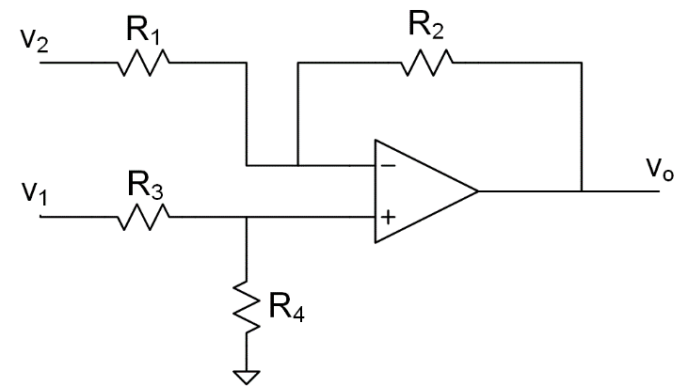

# Difference Amplifier

64

- Next, set  $v_1 = 0$ 
  - ▣ No current through  $R_3$  and  $R_4$

$$v^+ = 0 V$$


- ▣ An inverting amplifier

$$v_o \Big|_{v_2} = -v_2 \frac{R_2}{R_1}$$

- Summing the contributions from each output:

$$v_o = v_o \Big|_{v_1} + v_o \Big|_{v_2}$$
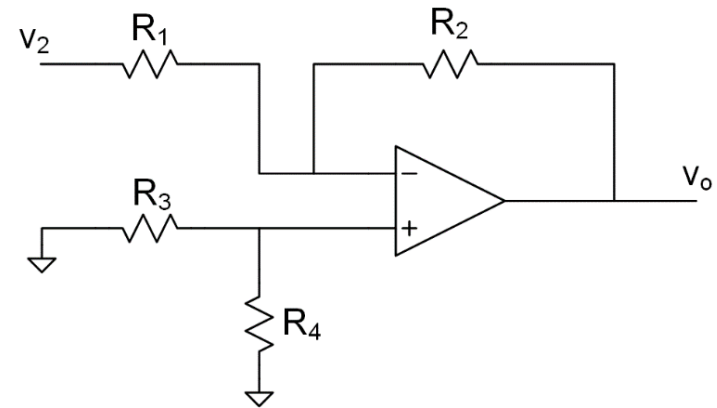
$$v_o = v_1 \frac{R_4}{R_3 + R_4} \frac{R_1 + R_2}{R_1} - v_2 \frac{R_2}{R_1}$$





# Difference Amplifier

65


- Restricting resistor values:

- $R_3 = R_1$  and  $R_4 = R_2$

$$v_o = v_1 \frac{R_2}{R_1 + R_2} \frac{R_1 + R_2}{R_1} - v_2 \frac{R_2}{R_1}$$

$$v_o = v_1 \frac{R_2}{R_1} - v_2 \frac{R_2}{R_1}$$

$$v_o = \frac{R_2}{R_1} (v_1 - v_2)$$

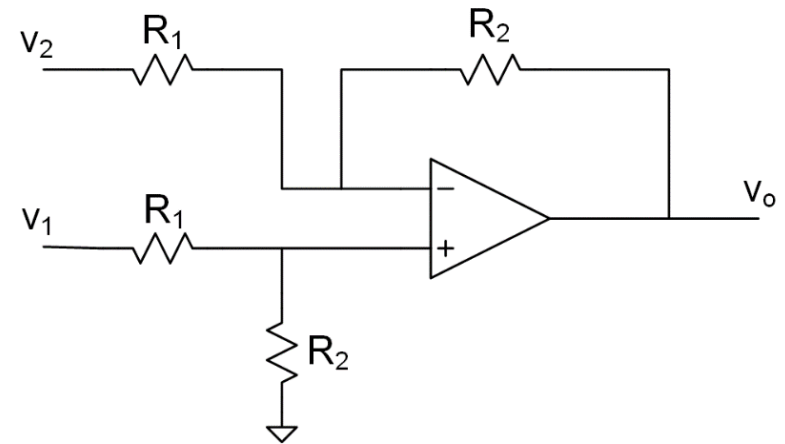


- Inverting and non-inverting amplifiers are special cases of the difference amplifier
  - Inverting amplifier:  $v_1$  is grounded
  - Non-inverting amplifier:  $v_2$  is grounded


66


# Example Problems

Determine the output voltage,  $V_o$ .

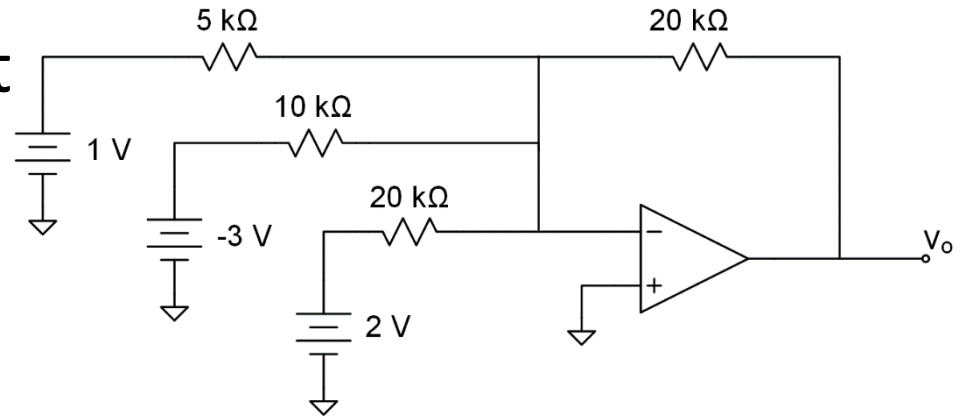

Determine the output voltage,  $V_o$ .

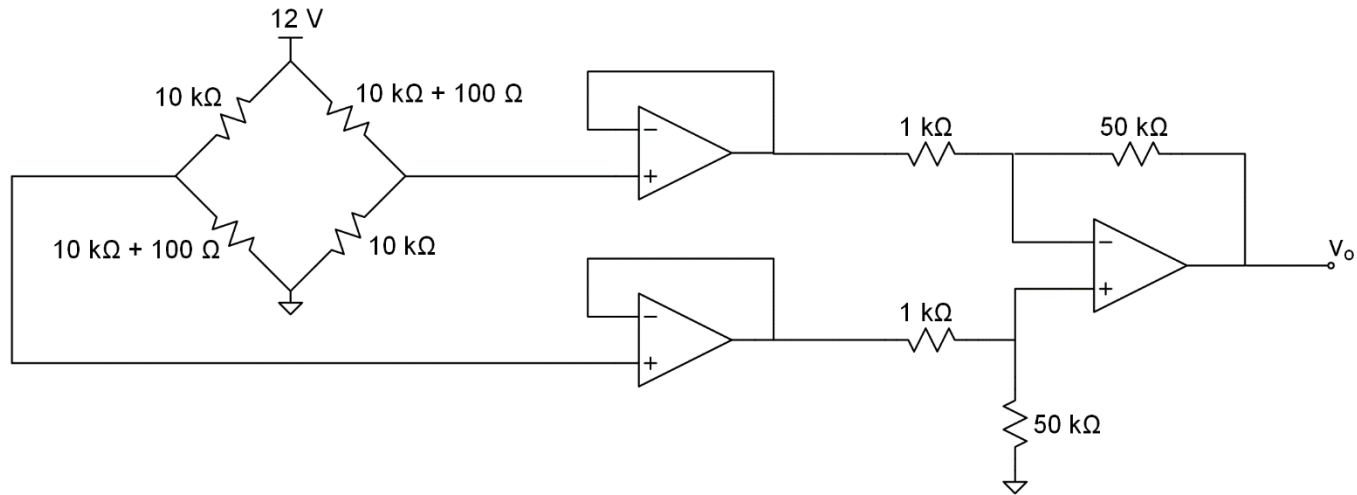

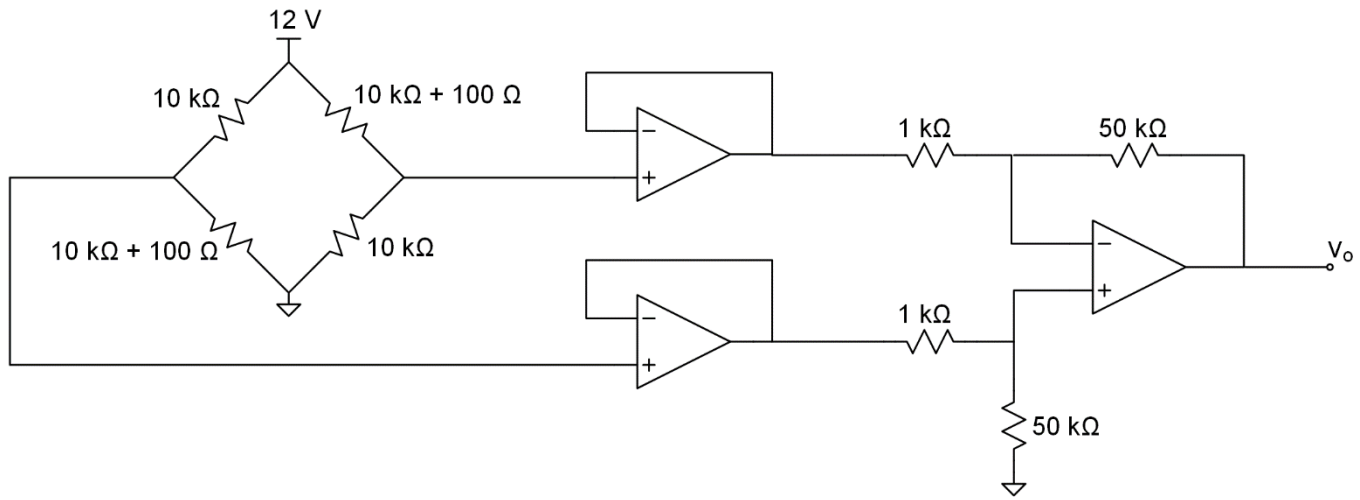


Design an opamp circuit to perform the following mathematical operation:

$$V_o = 3V_1 - 5V_2$$



Design an opamp circuit to perform the following mathematical operation:

$$V_o = 5V_1 - 3V_2$$

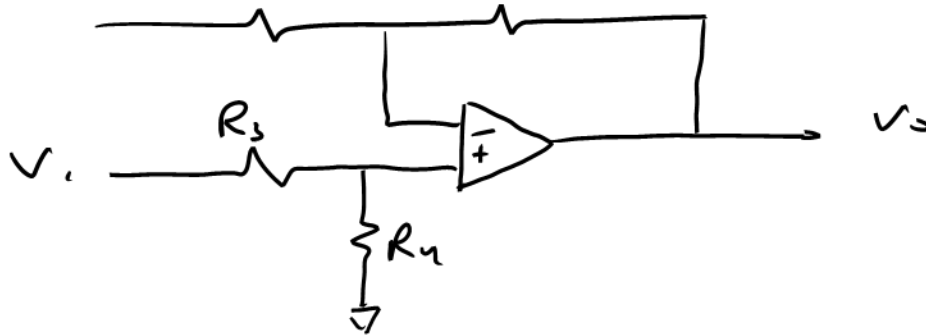







75

# Comparators

# Open-Loop Opamp Behavior


76

- So far, we've looked at opamp **amplifier** circuits
  - **Closed-loop** configuration
  - **Negative feedback**
  - Output remains within the opamp's **linear** output range
  
- We'll now consider using an opamp **open-loop** – without feedback – or with positive feedback
  - For ideal opamp,  $A_{vol} = \infty$
  - For any non-zero input,  $v_o \rightarrow \pm\infty$
  - But,  $v_o$  limits, or **saturates**, somewhere near the supply voltages,  $V_{o,max}$
  - In practice, the output of an open-loop opamp is always saturated at  $\pm V_{o,max}$
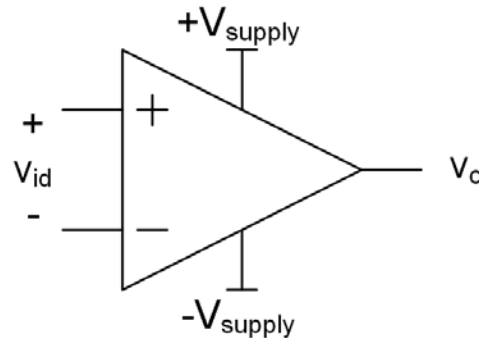
# Comparators

77

- Open-loop opamp's output determined by relative values of the two inputs, differential input




$v^+, v^-$	$V_{id}$	$V_o$
$v^+ > v^-$		
$v^+ < v^-$		

- An open-loop opamp acts as a **comparator**
  - ▣ **Compares** the two input voltages
  - ▣ Sets the output based on which input is higher

# Comparators


78

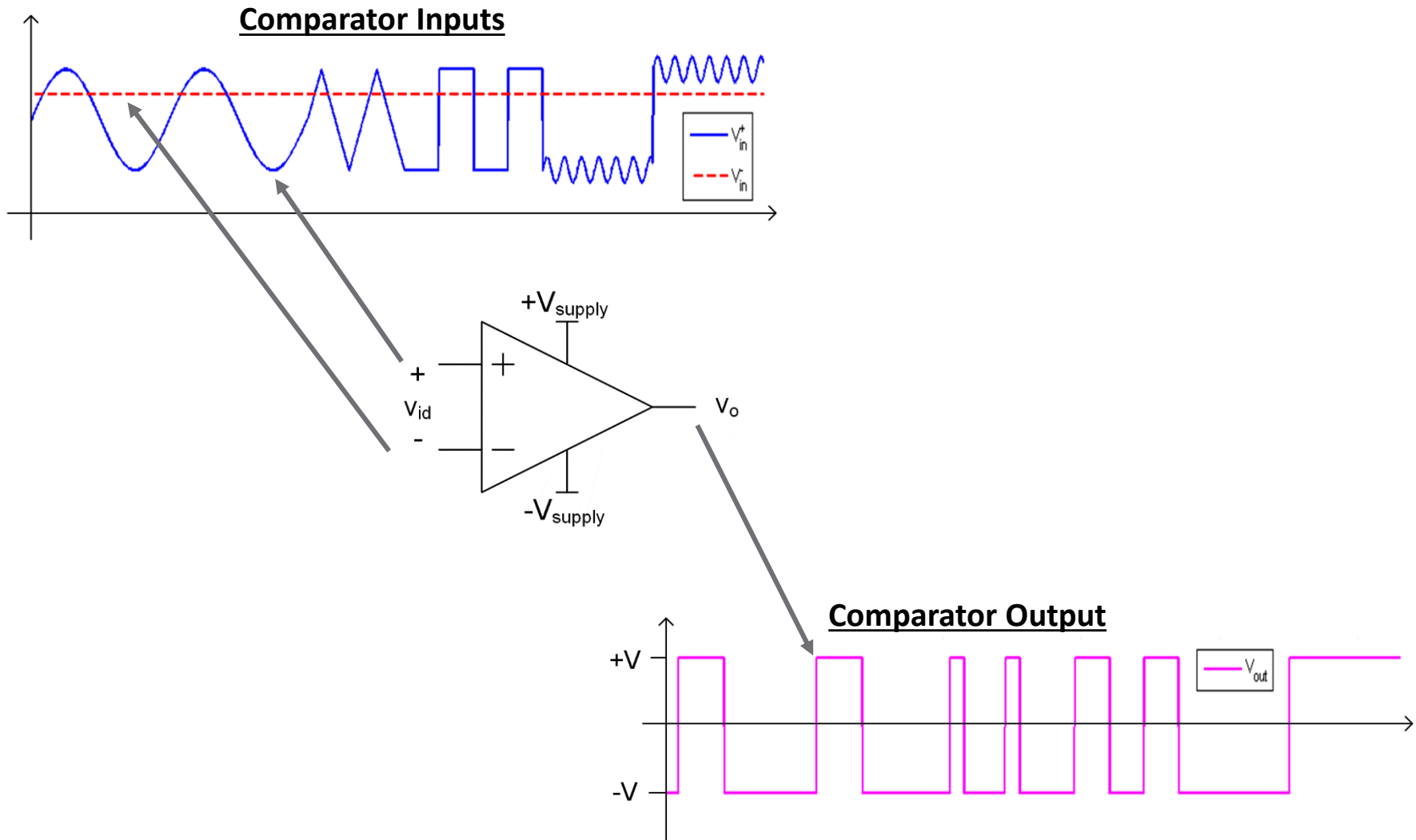
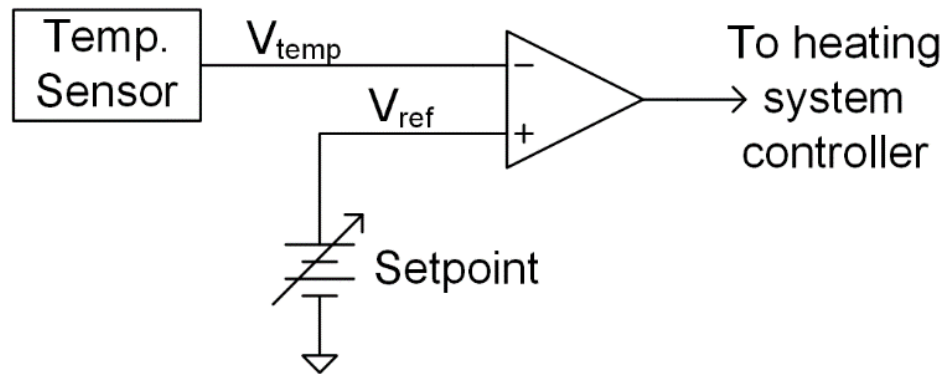
# Comparators – Applications

79

- Simple comparator application: **thermostat**
  - Inverting input connected to a temperature sensor
  - Non-inverting input connected to a variable reference voltage determined by the temperature setpoint



- If  $T_{room} < T_{set}$ 
  - $V_{temp} < V_{ref}$
  - Output is high
  - Heat turns on
- If  $T_{room} > T_{set}$ 
  - $V_{temp} > V_{ref}$
  - Output is low
  - Heat is off


- Another example application: **motion-sensing light**
  - One input from a motion sensor – variable analog voltage
  - Other input is a threshold voltage set by sensitivity setting
    - Want light to turn on for people and cars, not birds or insects

# Comparators and Noise


80

□ Consider the following comparator circuit:

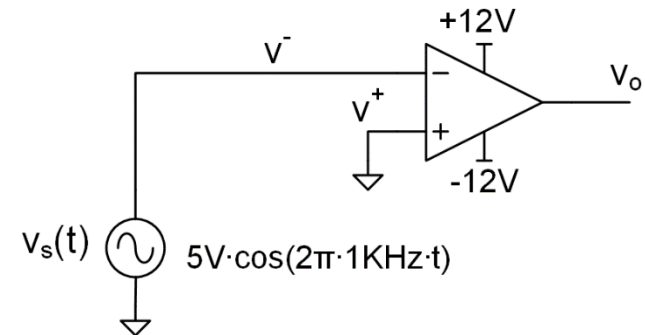
- Inverting input driven by sinusoidal voltage
- Non-inverting input is **threshold voltage** – connected to ground ( $0\text{ V}$ )
- Output switches cleanly at each input threshold crossing



Comparator Inputs and Output

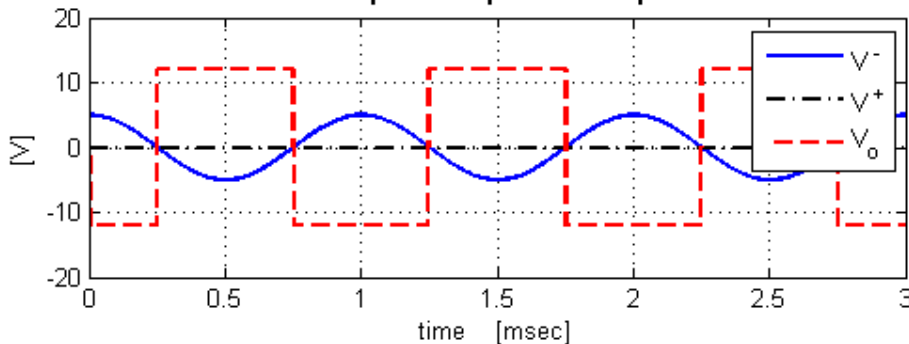

Comparator Inputs and Output



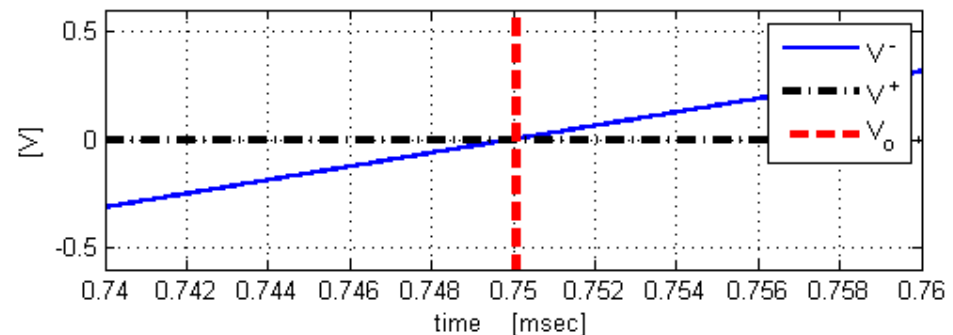



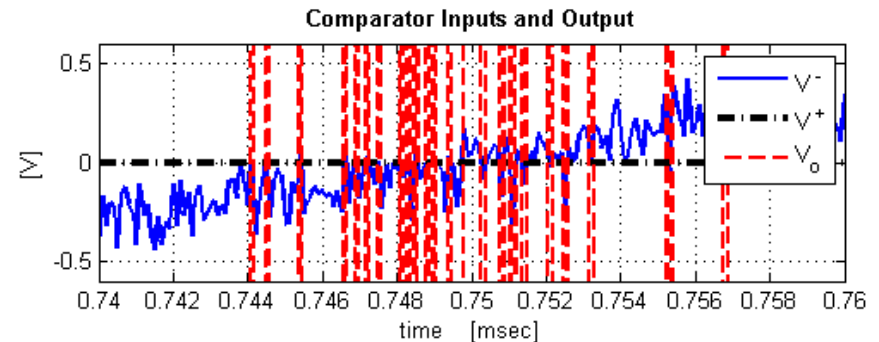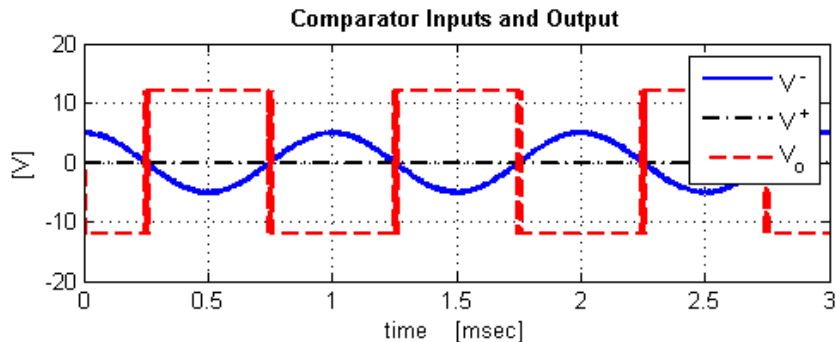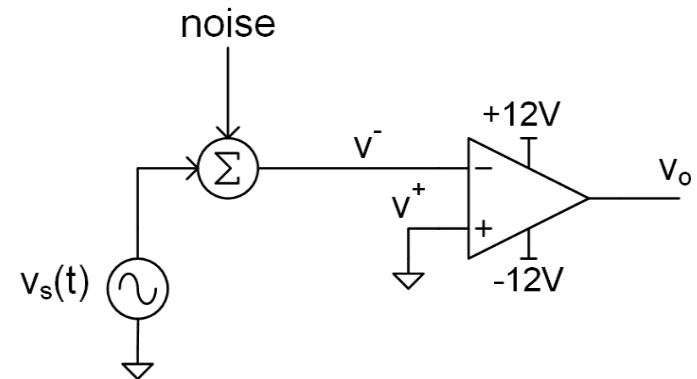
# Comparators and Noise

81

- Now, the sinusoidal input is corrupted by noise
  - ▣ Multiple input threshold crossings each time  $v_s(t)$  goes through  $0\text{ V}$
  - ▣ Multiple, unwanted, output transitions



- Would like to be able to reject this noise at the input:
  - ▣ **Schmitt trigger**

82

# Hysteresis

# Hysteresis – Schmitt Trigger


83

- Schmitt trigger employs ***hysteresis***
  - ▣ Characteristics of the circuit are dependent on its previous state
- Looks like a non-inverting amplifier, but it is not
  - ▣ ***Positive feedback***
- A comparator with a threshold voltage that depends on the output

$$v^+ = v_o \frac{R_2}{R_1 + R_2} = \beta v_o$$

- Threshold voltage switches between two values as the output switches between  $\pm V_{o,max}$

$$v^+ = \pm \beta V_{o,max}$$

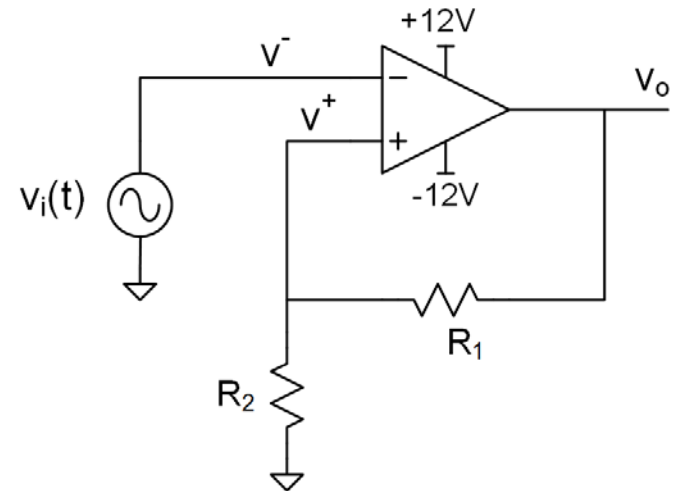

# Schmitt Trigger – Hysteresis voltage

84

- Consider the case where the input is low

$$v_i < v^+$$

- ▣ Output will be high

$$v_o = +V_{o,max}$$

- The input then increases and exceeds the threshold voltage

$$v_i > v^+$$

- ▣ The output will then switch low


$$v_o \rightarrow -V_{o,max}$$

- ▣ The threshold voltage will switch low

$$v^+ \rightarrow -\beta V_{o,max}$$

- ▣ **Threshold voltage switches away from the rising input**

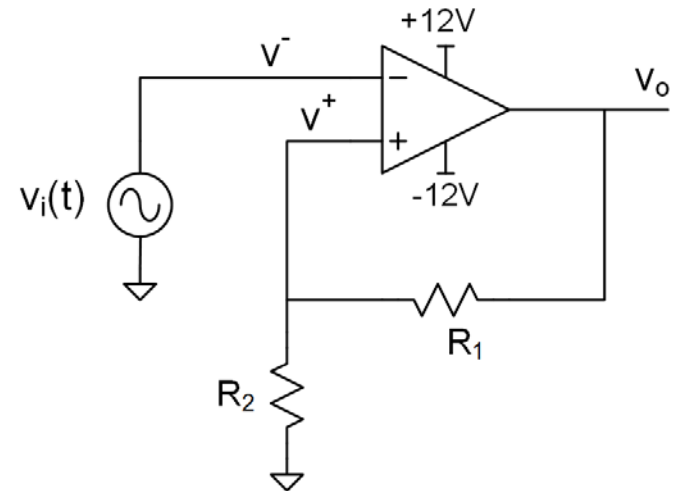- Similar thing is true for falling input




# Schmitt Trigger – Hysteresis voltage

85

- Output, and threshold voltage, always ***switches away from the input signal*** at the first threshold crossing
- ***Hysteresis voltage:***
  - ▣ Magnitude of the threshold voltage change

$$V_{hyst} = 2\beta V_{o,max}$$

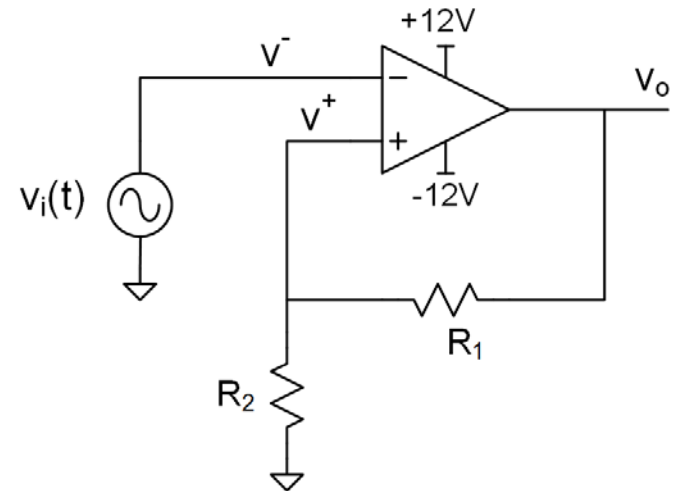- Hysteresis voltage set for the amount of noise that is present
  - ▣ Threshold must switch far enough away from the noisy input that it will not be crossed multiple times by noise alone
  - ▣  $V_{hyst}$  set greater than peak-to-peak noise on the input signal






# Comparators and Noise – Hysteresis

86


- Feedback gain,  $\beta$ , set to provide adequate hysteresis to reject the input noise
  - ▣ Noisy input crosses threshold
  - ▣ Threshold voltage switches away from the input by the hysteresis voltage

$$V_{hyst} > V_{n,pp}$$

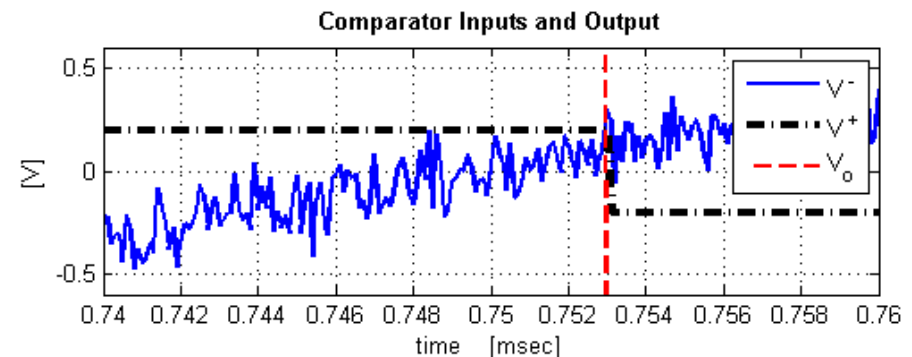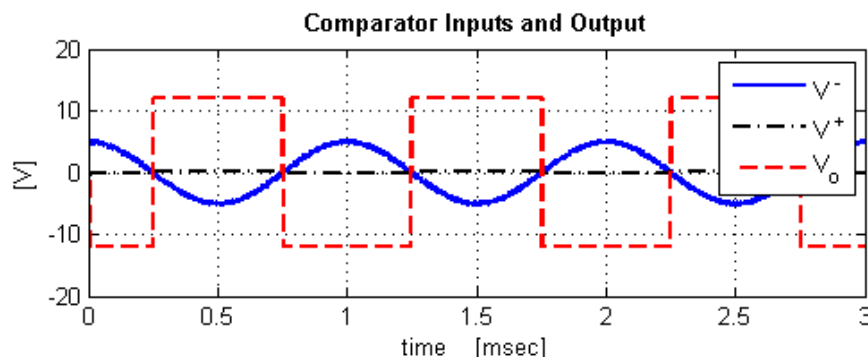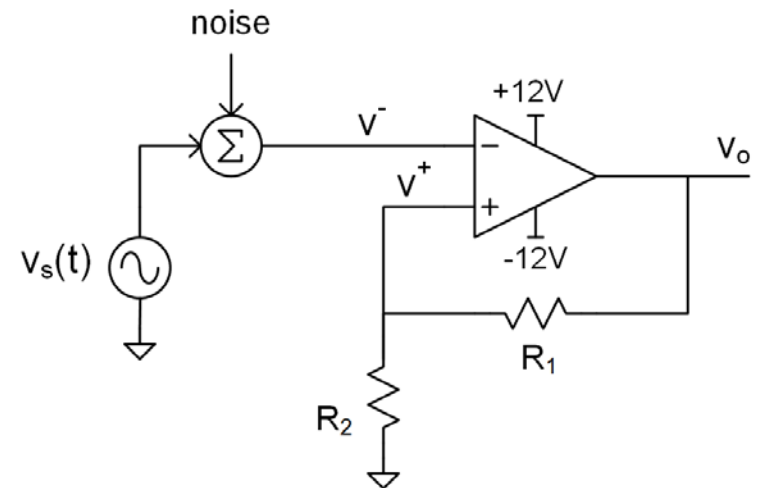

# Hysteresis Voltage

87

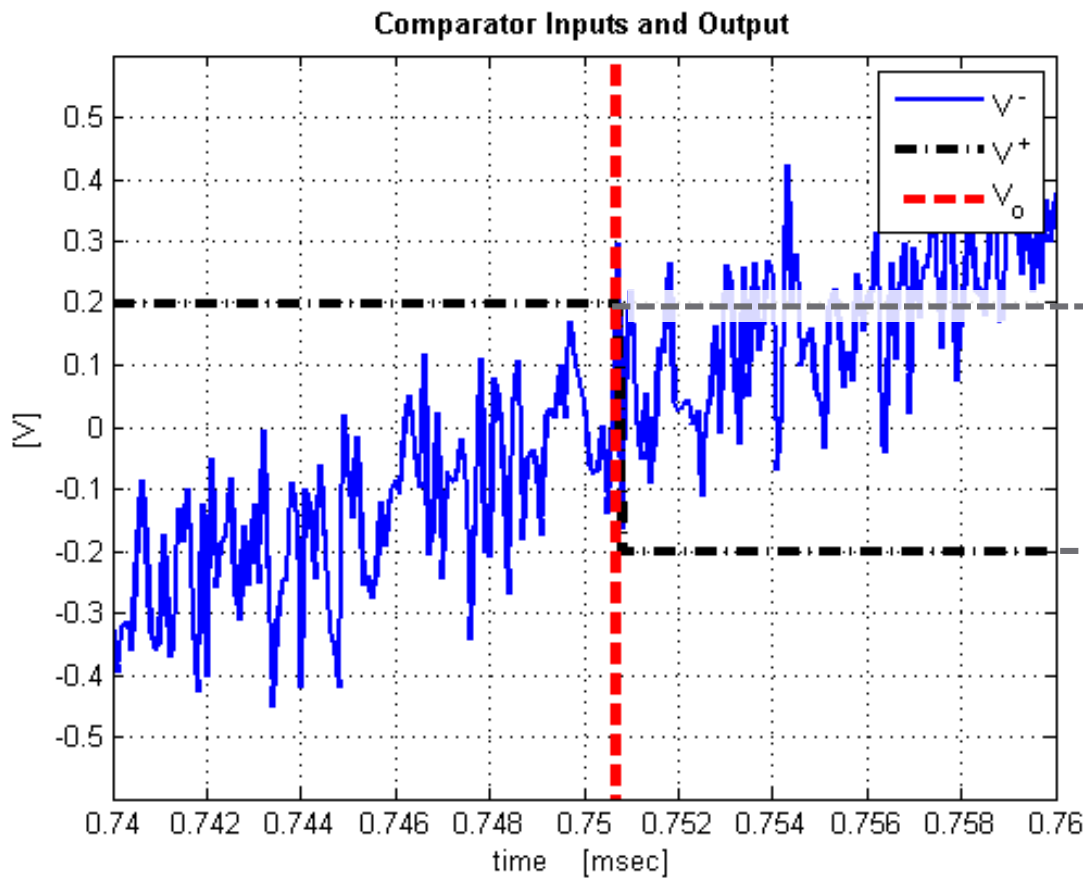

## □ **Hysteresis voltage**

- Full peak-to-peak swing of the threshold voltage

$$V_{hyst} = 400 \text{ mV}$$


- Twice the magnitude of the feedback signal

$$V_{hyst} = 2\beta V_{o,max}$$
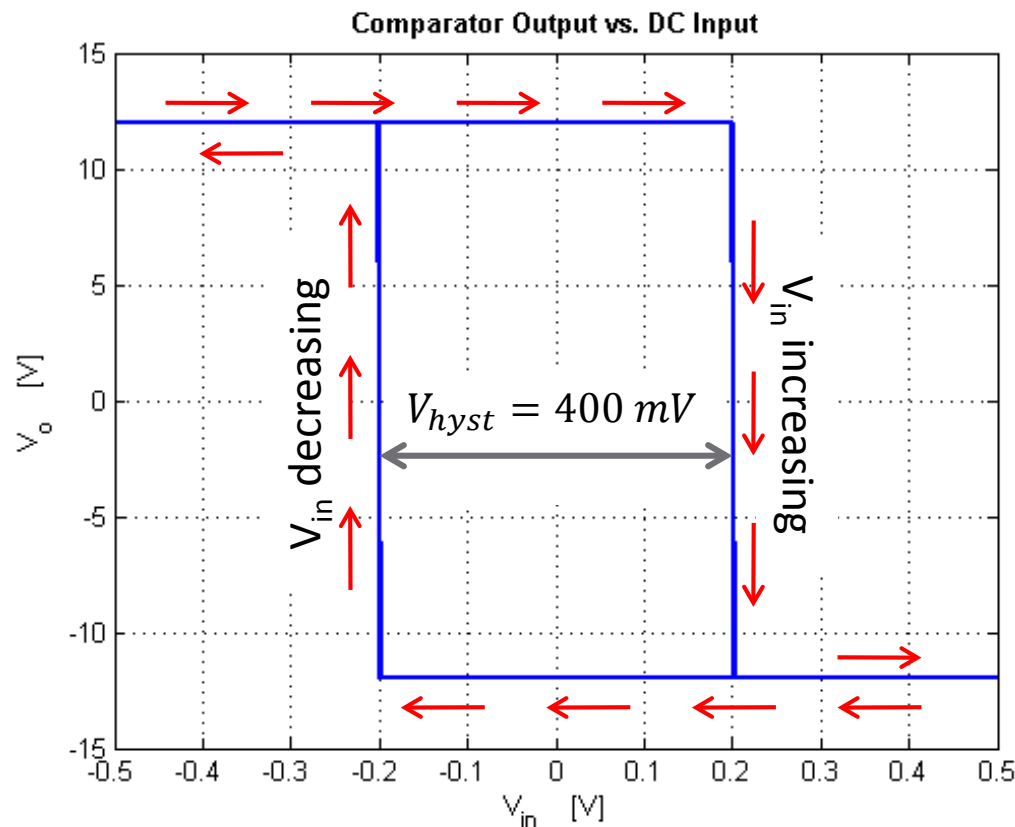
# Hysteresis Voltage

88

- Can also measure  $V_{hyst}$  by performing a bidirectional DC sweep of the input
  - ▣ Low-to-high, then high-to-low



- Output traces a different path depending on direction of  $v_{in}$ 
  - ▣ Vertical lines indicate threshold voltages
  - ▣  $V_{hyst}$  given by difference between upper and lower thresholds



# Adjustable Hysteresis

89

- If noise level is not known ahead of time
  - ▣ Use a potentiometer to get adjustable hysteresis
- $R_2$  adjustable from  $0 \Omega$  to  $R_{2,max}$
- Hysteresis varies as  $R_2$  varies


$$V_{hyst} = 2 \frac{R_2}{R_1 + R_2} V_{o,max}$$

- Max hysteresis at  $R_2 = R_{2,max}$

$$V_{hyst,max} = 2 \frac{R_{2,max}}{R_1 + R_{2,max}} V_{o,max}$$

- Minimum hysteresis for  $R_2 = 0 \Omega$
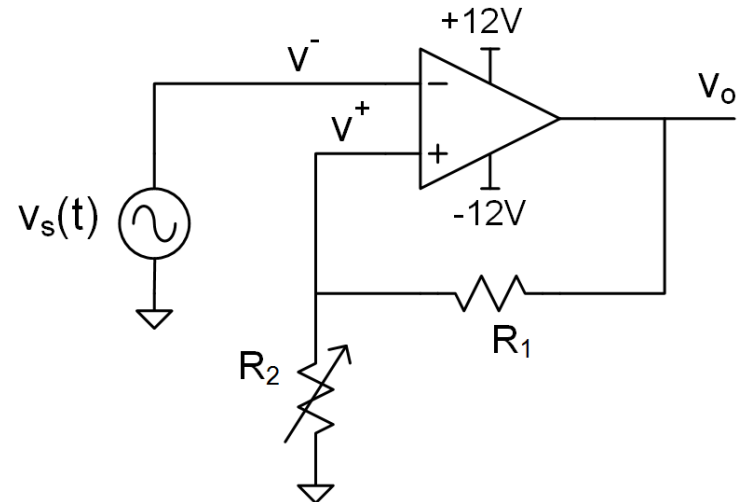
$$V_{hyst,min} = 2 \frac{0 \Omega}{R_1 + 0 \Omega} V_{o,max} = 0 V$$



# Schmitt Trigger – Example

90


- Consider the following scenario:
  - Test engine instrumented and running on a dynamometer
  - Want an engine temperature warning light (LED)
  - RTD (*resistive temperature detector* or *resistive thermal device*) installed to measure coolant temperature.
  - RTD is biased such that a  $0\text{ V}$  output corresponds to  $T_{max}$
  - Noise:  $V_{n,pp} \approx 100\text{ mV}$
  - Opamp available for use as a comparator:
    - $V_{supply} = \pm 5\text{ V}$
    - $V_{o,max} = \pm |V_{supply} - 500\text{ mV}|$
    - $I_{o,max} = \pm 10\text{ mA}$
  - $I_{LED} = 9\text{ mA}$

# Schmitt Trigger – Example

91

- When  $T > T_{max}$ 
  - ▣ RTD output exceeds 0 V
  - ▣ Schmitt trigger output goes low:  $v_o \rightarrow -4.5 V$
  - ▣ LED turns on:  $I_{LED} = 9 mA$
  - ▣ Opamp output sinks LED current and feedback network current
  - ▣ Feedback network current must not exceed 1 mA

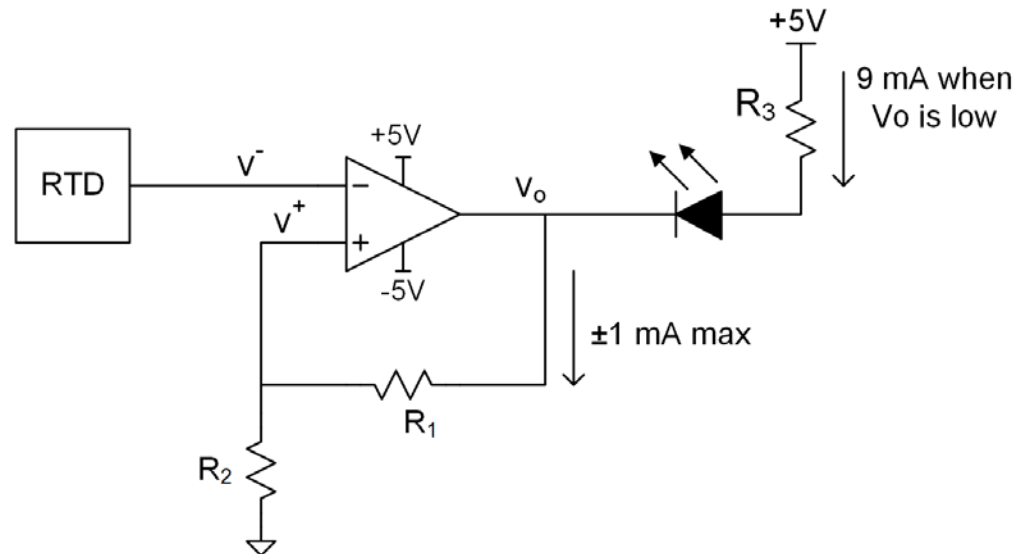- Determine  $R_1$  and  $R_2$  to:
  - ▣ Set required hysteresis voltage
  - ▣ Limit feedback path current



# Schmitt Trigger – Example

92

- Required hysteresis is *at least* the peak-to-peak noise voltage,  $V_{n,pp} \approx 100 \text{ mV}$ 
  - Design for  $V_{hyst} = 150 \text{ mV}$
  - The opamp saturates at  $\pm 4.5 \text{ V}$ , so

$$V_{hyst} = 2 \cdot 4.5 \text{ V} \frac{R_2}{R_1 + R_2} = 150 \text{ mV}$$

$$\frac{R_2}{R_1 + R_2} = \frac{150 \text{ mV}}{9 \text{ V}} = 16.67 \times 10^{-3}$$

- This specifies the ratio between the feedback resistors

$$R_2 = 16.95 \times 10^{-3} \cdot R_1$$

- Absolute values will be selected to limit feedback path current

# Schmitt Trigger – Example

93

- When the LED is on, the feedback path current flowing into the opamp output is

$$I_f = \frac{4.5 V}{R_1 + R_2} < 1 mA$$

- So, the total feedback path resistance is

$$R_1 + R_2 > 4.5 k\Omega$$

- Select a standard value for the larger resistor


$$R_1 = 5.1 k\Omega$$

- Calculate  $R_2$  using the previously derived ratio

$$R_2 = 16.95 \times 10^{-3} \cdot 5.1 k\Omega = 86.4 \Omega$$

- Select the next *larger* standard value:  $R_2 = 91 \Omega$

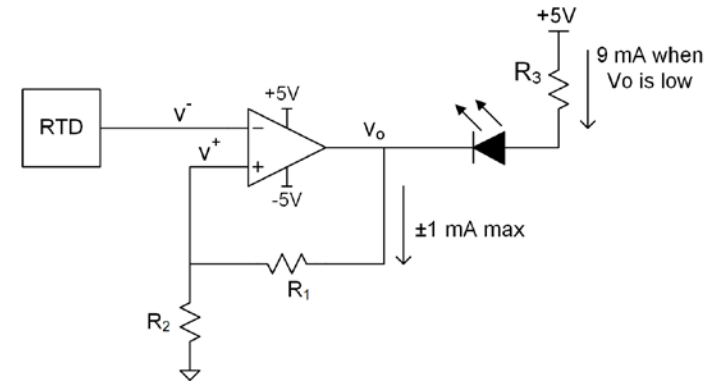
- ▣ *Larger*, so as not to decrease  $V_{hyst}$



# Schmitt Trigger – Example

94

□ The resulting circuit:

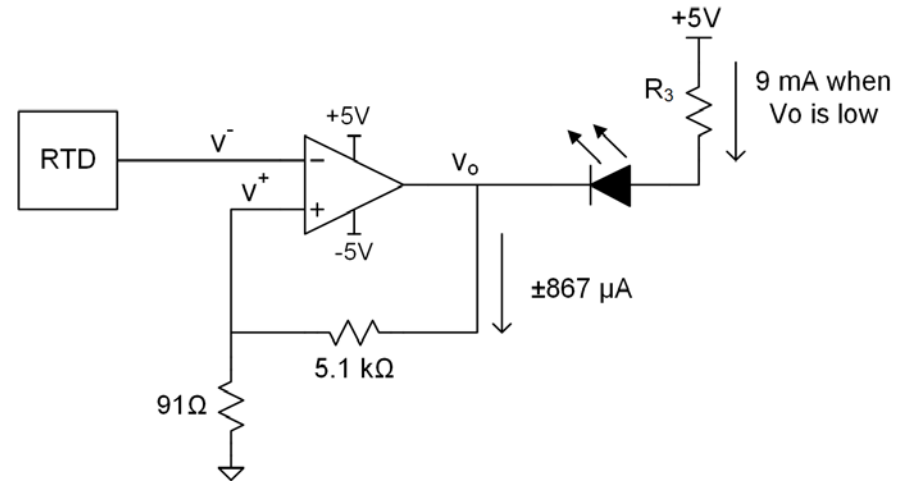

□ Verifying hysteresis:

$$V_{hyst} = 9 V \frac{91 \Omega}{5.1 k\Omega + 91 \Omega}$$

$$V_{hyst} = 157 mV$$

□ Feedback path current:

$$I_f = \frac{4.5 V}{5191 \Omega} = 867 \mu A$$