

SECTION 5: CAPACITANCE & INDUCTANCE

ENGR 201 – Electrical Fundamentals I


2

Fluid Capacitor

Fluid Capacitor

3

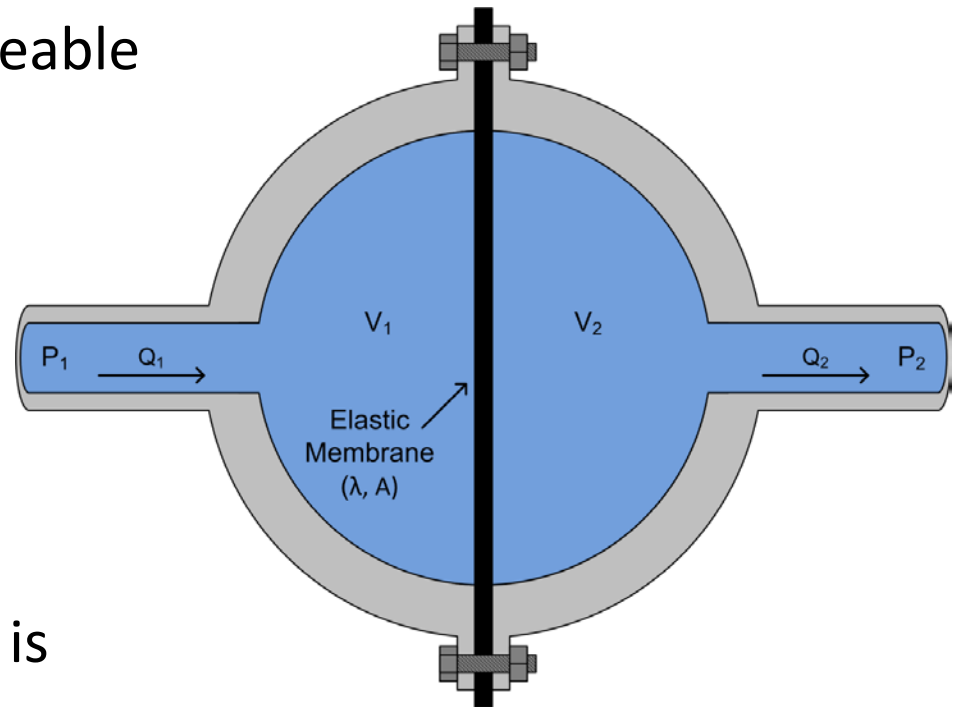- Consider the following device:
 - Two rigid hemispherical shells
 - Separated by an impermeable elastic membrane
 - Modulus of elasticity, λ
 - Area, A
 - Incompressible fluid
 - External pumps set pressure or flow rate at each port
 - Total volume inside shell is constant
 - Volume on either side of the membrane may vary



Fluid Capacitor – Equilibrium

4

- Equal pressures

$$\Delta P = P_1 - P_2 = 0$$


- No fluid flow

$$Q_1 = Q_2 = 0$$

- Membrane does not deform

- Equal volume on each side

$$V_1 = V_2 = \frac{V}{2}$$

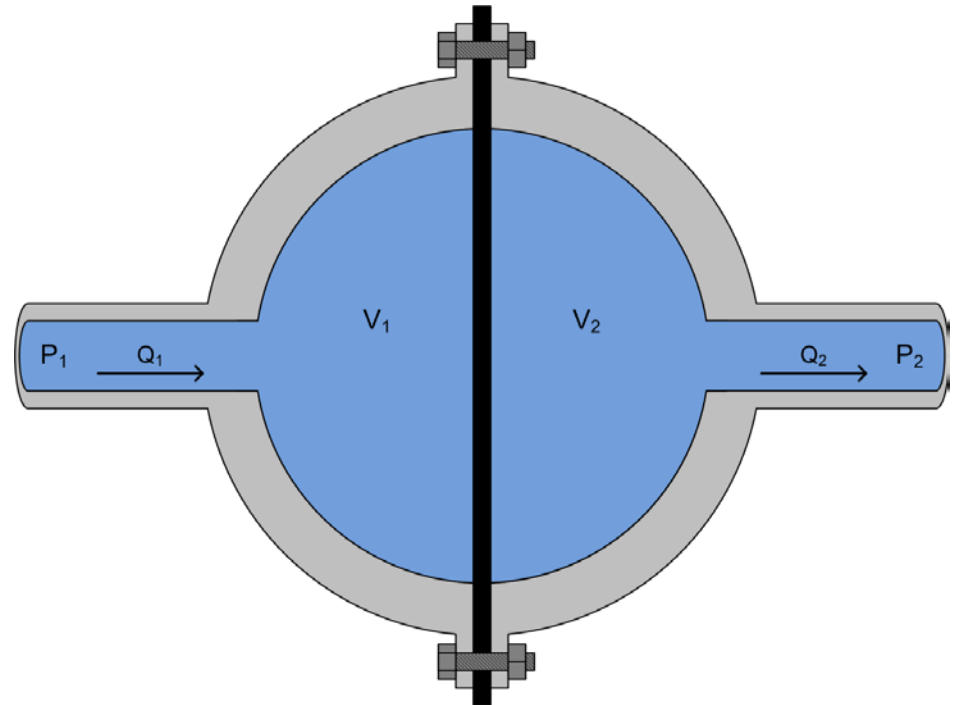

Fluid Capacitor – $P_1 > P_2$

5

- Pressure differential

$$\Delta P = P_1 - P_2 > 0$$

- Membrane deforms

- Volume differential


$$\Delta V = V_1 - V_2 > 0$$

- Transient flow as membrane stretches, but...

- No steady-state flow

- As $t \rightarrow \infty$

$$Q_1 = Q_2 = 0$$

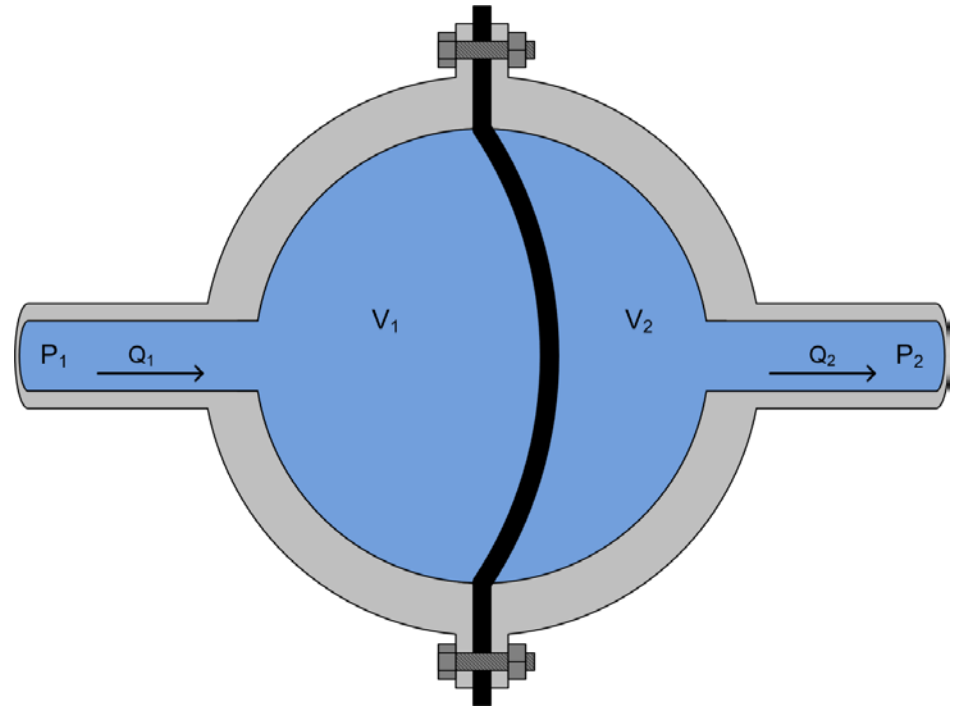

Fluid Capacitor – $P_1 < P_2$

6

- Pressure differential

$$\Delta P = P_1 - P_2 < 0$$

- Volume differential

$$\Delta V = V_1 - V_2 < 0$$


- ΔV proportional to:

- ▣ Pressure differential
- ▣ Physical properties, λ, A

- Total volume remains constant

$$V_1 + V_2 = V$$

- Again, no steady-state flow

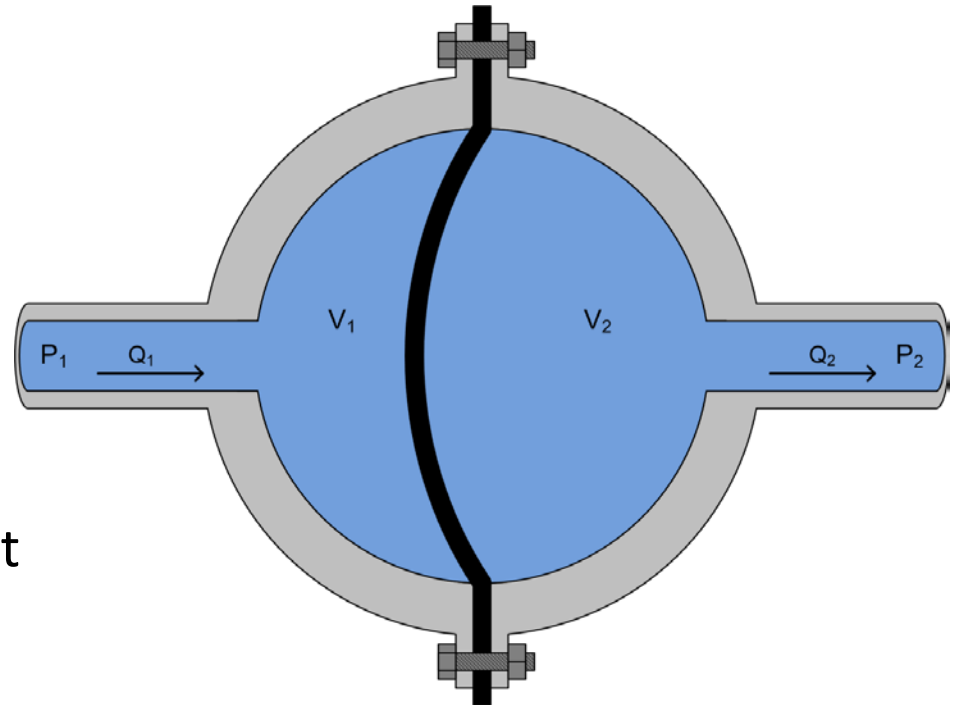

Fluid Capacitor – Constant Flow Rate

7

- Constant flow rate forced into port 1

$$Q_1 \neq 0$$

- Incompressible, so flows are equal and opposite

$$Q_1 = Q_2$$


- Volume on each side proportional to time

$$V_1 = \frac{V}{2} + Q_1 \cdot t$$

$$V_2 = \frac{V}{2} - Q_2 \cdot t = \frac{V}{2} - Q_1 \cdot t$$

- Volume differential proportional to time

$$\Delta V = V_1 - V_2 = 2Q_1 \cdot t$$

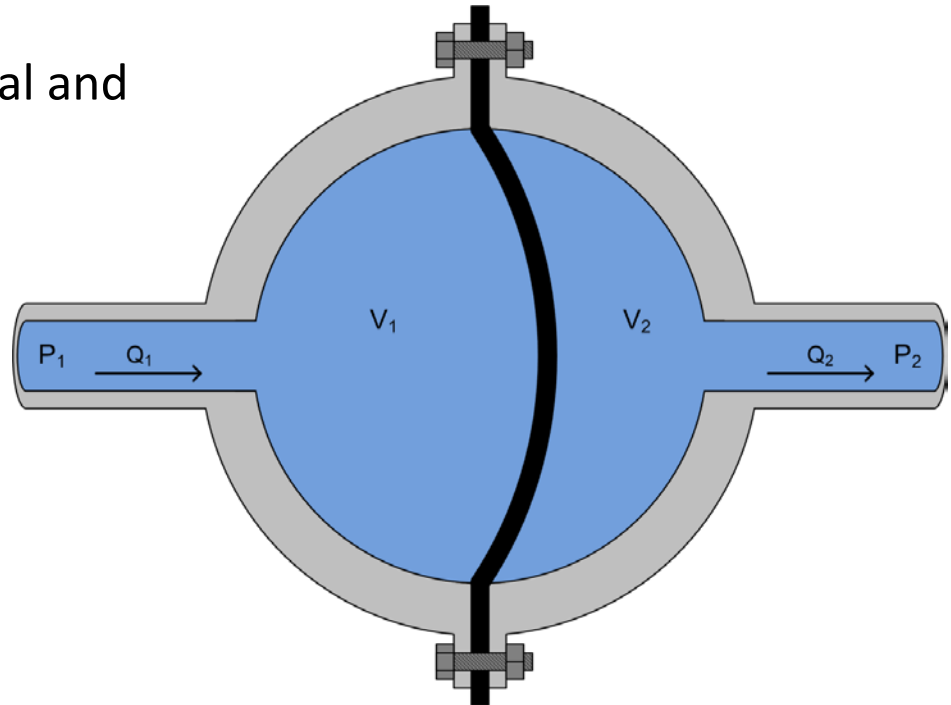

Fluid Capacitor – Capacitance


8

- Define a relationship between differential volume and pressure

- **Capacitance**

$$C = \frac{\Delta V}{\Delta P}$$

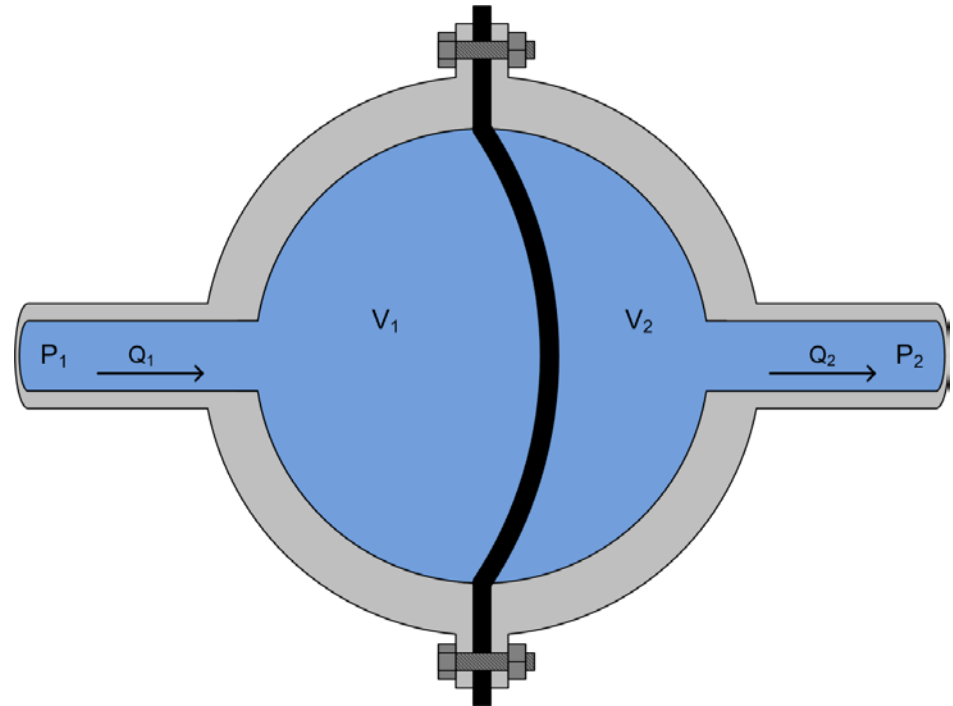- Intrinsic device property
- Determined by physical parameters:
 - ▣ Membrane area, A
 - ▣ Modulus of elasticity, λ



Fluid Capacitor – DC vs. AC

9

- In steady-state (DC), no fluid flows

$$Q_1 = Q_2 = 0$$


- Consider sinusoidal ΔP (AC):

$$\Delta P = P \sin(\omega t)$$

- Resulting flow rate is proportional to:

- ▣ Rate of change of differential pressure
- ▣ Capacitance
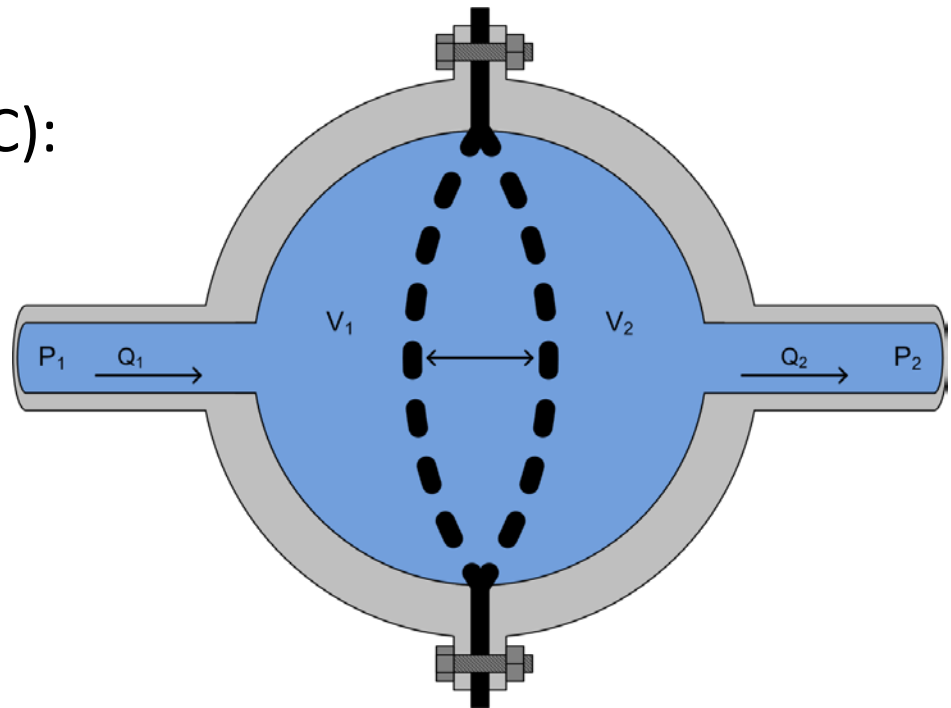
$$Q_1 = Q_2 = C \frac{dP}{dt} = \omega C P \cos(\omega t)$$



Fluid Capacitor – Time-Varying ΔP

10

- Equal and opposite flow at both ports

$$Q_1 = Q_2$$

- Not the same fluid flowing at both ports
 - ▣ Fluid cannot permeate the membrane

- **Fluid appears to flow through the device**


- ▣ Due to the displacement of the membrane
- ▣ A **displacement flow**

- The faster ΔP changes, the higher the flow rate

$$Q \propto \omega$$

- The larger the capacitance, the higher the flow rate


$$Q \propto C$$

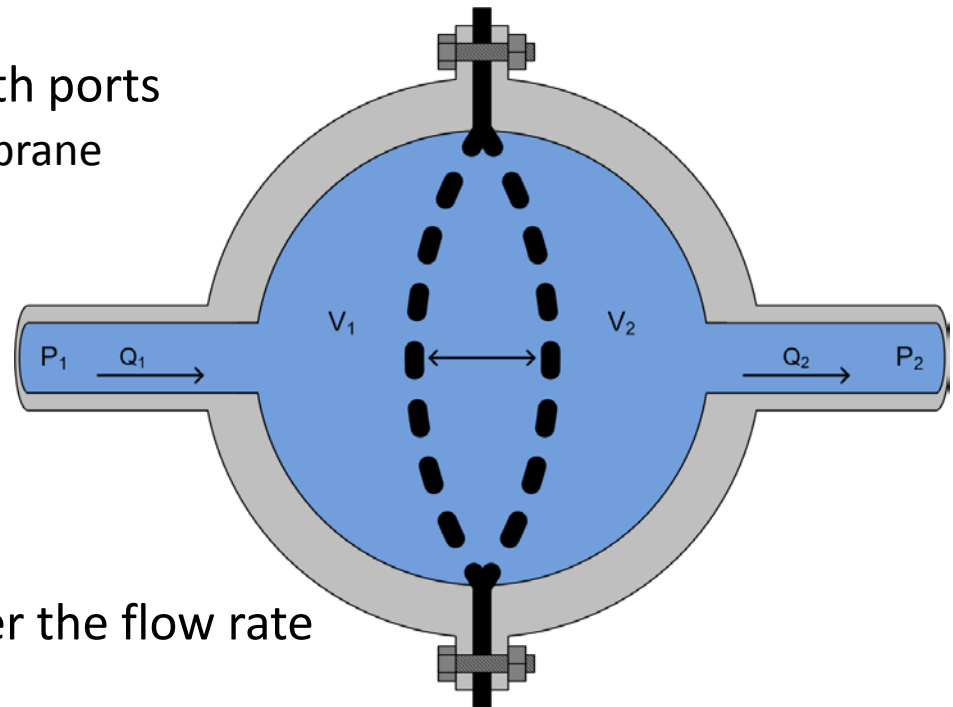

Fluid Capacitor – Changing ΔP

11

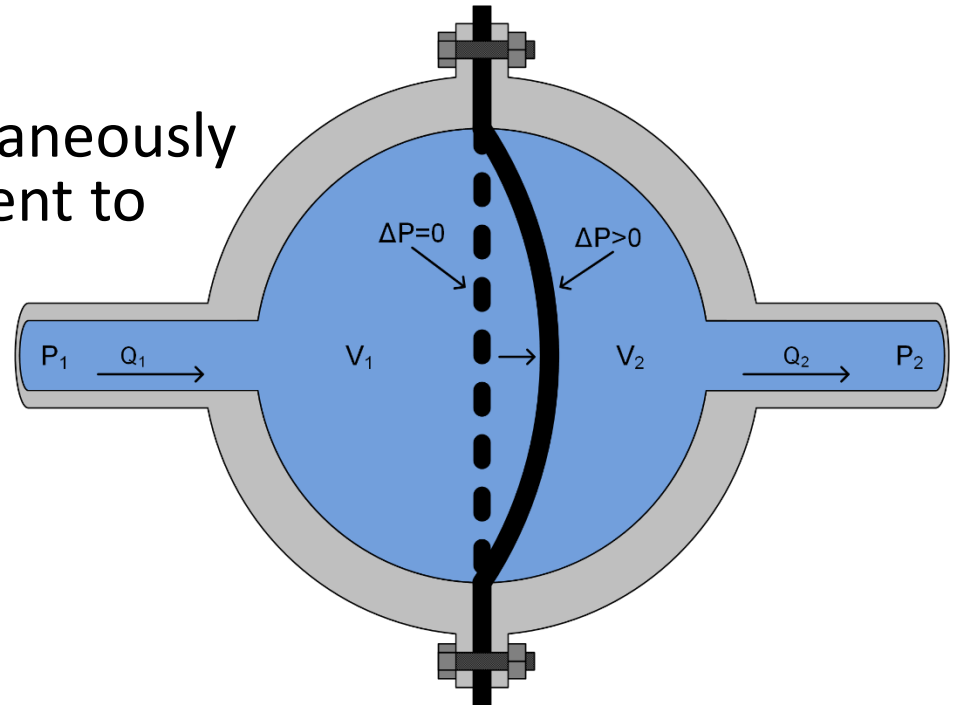
- A given ΔP corresponds to a particular membrane displacement
 - ▣ Forces must balance
- Membrane cannot instantaneously jump from one displacement to another
- Step change in displacement/pressure is impossible
 - ▣ Would require an infinite flow rate
- ***Pressure across a fluid capacitor cannot change instantaneously***



Fluid Capacitor – Energy Storage

12

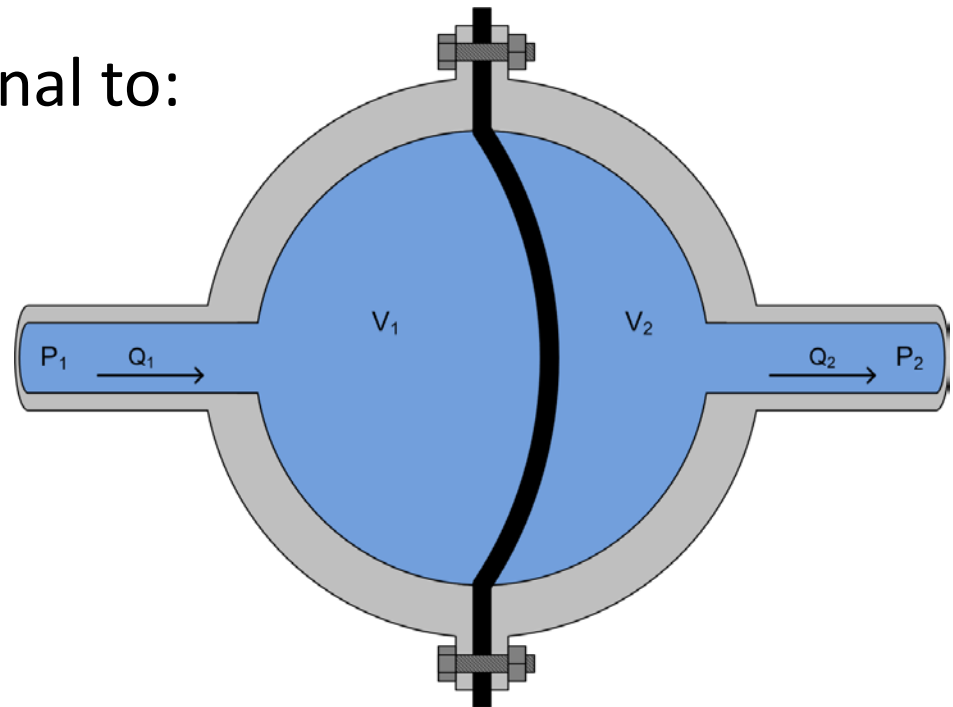- Stretched membrane **stores energy**
 - **Potential energy**
- Stored energy proportional to:
 - ΔP
 - ΔV
- Energy released as membrane returns
 - P and Q are supplied



13

Electrical Capacitors

Electrical Capacitor

14

- In the electrical domain, our “working fluid” is ***positive electrical charge***
- In either domain, we have a ***potential-driven flow***

Fluid Domain	Electrical Domain
Pressure – P	Voltage – V
Volumetric flow rate – Q	Current – I
Volume – V	Charge – Q

Electrical Capacitor

15


- Parallel-plate capacitor
 - ▣ Parallel metal plates
 - ▣ Separated by an insulator
- ***Applied voltage creates charge differential***
 - ▣ Equal and opposite charge


$$Q_1 = -Q_2$$

- ▣ Zero net charge
- Equal current

$$I_1 = I_2$$

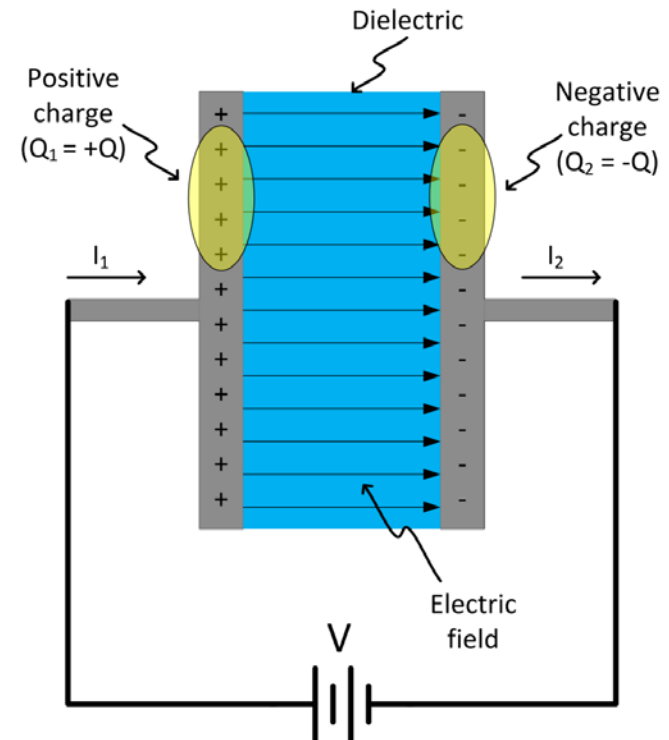- ▣ What flows in one side flows out the other




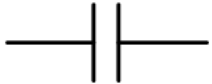- Schematic symbol: 
- Units: Farads (F)

Electrical Capacitor – Electric Field

16

- Charge differential results in an **electric field, E** , in the dielectric
 - ▣ Units: V/m
- $|E|$ is inversely proportional to dielectric thickness, d
- Above some maximum electric field strength, dielectric will **break down**
 - ▣ Conducts electrical current
 - ▣ Maximum capacitor voltage rating

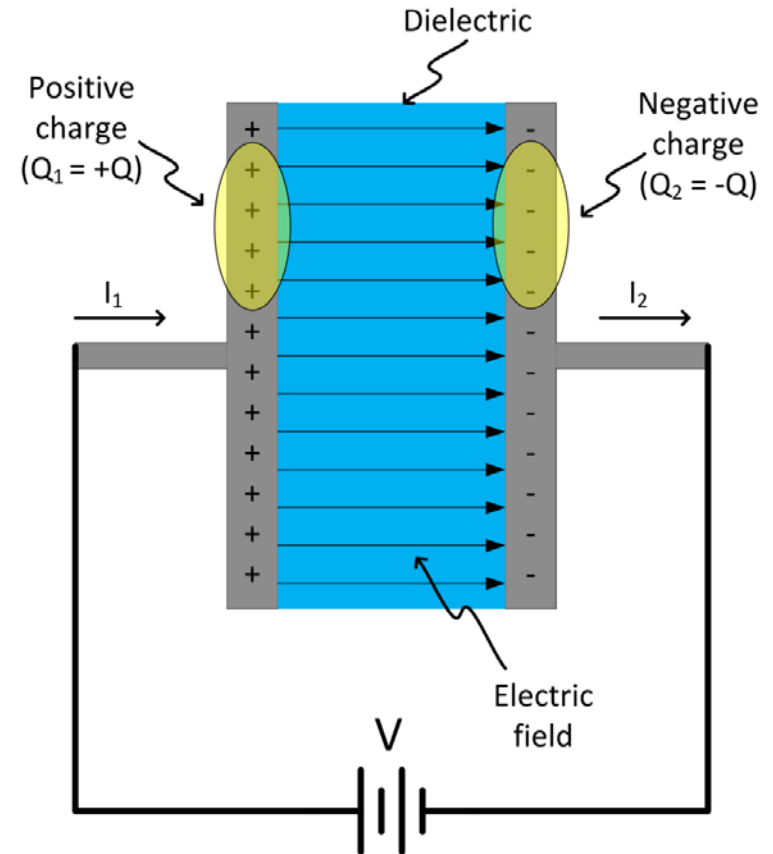

Electrical Capacitor - Capacitance


17

□ **Capacitance**

- ▣ Ratio of charge to voltage


$$C = \frac{Q}{V}$$

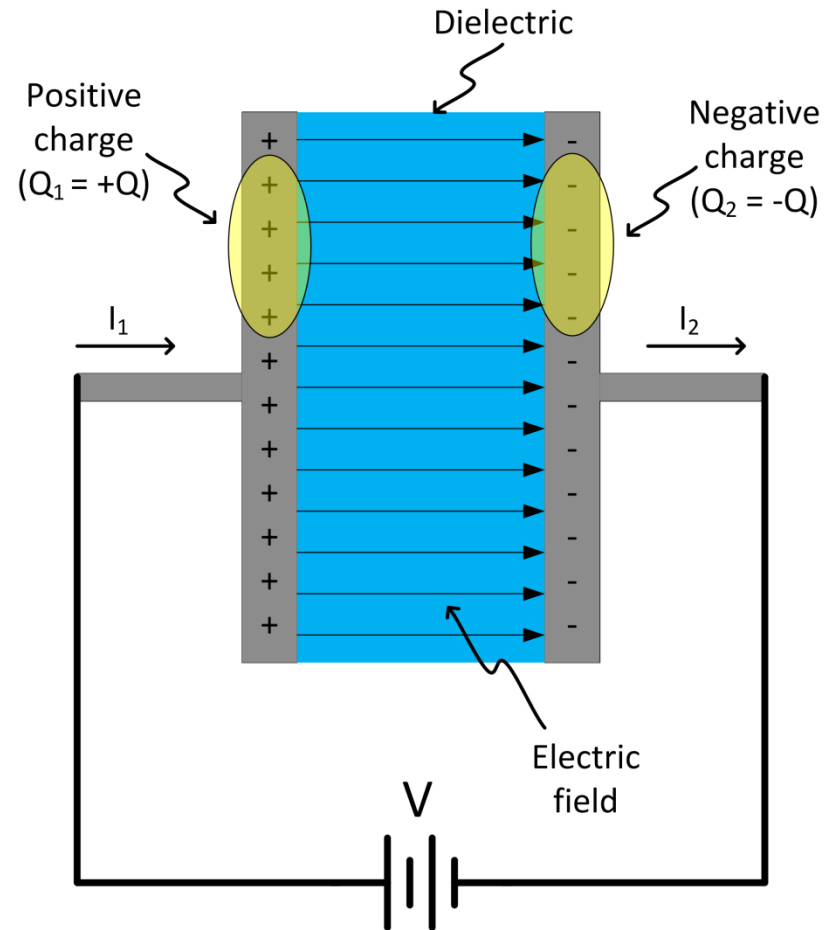- Intrinsic device property
- Proportional to physical parameters:
 - ▣ Dielectric thickness, d
 - ▣ Dielectric constant, ϵ
 - ▣ Area of electrodes, A



Parallel-Plate Capacitor

18

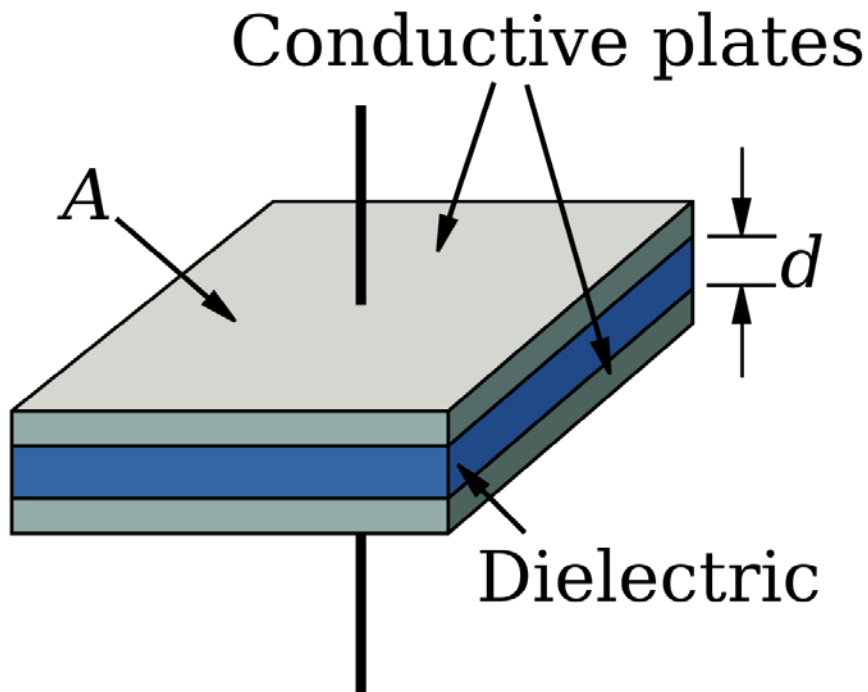

□ Capacitance

$$C = \frac{\epsilon A}{d}$$

- ϵ : dielectric permittivity
 - A : area of the plates
 - d : dielectric thickness
-
- Capacitance is maximized by using:
 - High-dielectric-constant materials
 - Thin dielectric
 - Large-surface-area plates

Capacitors – Voltage and Current


19

- Current through a capacitor is proportional to
 - ▣ Capacitance
 - ▣ Rate of change of the voltage

$$i(t) = C \frac{dv}{dt}$$

- Voltage across capacitor results from an accumulation of charge differential
 - ▣ Capacitor integrates current

$$v(t) = \frac{1}{C} \int i(t) dt$$

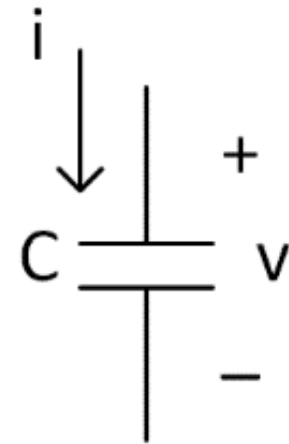

Voltage Change Across a Capacitor

20

- For a step change in voltage,

$$\frac{dv}{dt} = \infty$$

- The corresponding current would be *infinite*
- ***Voltage across a capacitor cannot change instantaneously***
- Current can change instantaneously, but voltage is the integral of current

$$\lim_{\Delta t \rightarrow 0} \Delta V = \lim_{\Delta t \rightarrow 0} \frac{1}{C} \int_{t_0}^{t_0 + \Delta t} i(t) dt = 0$$

Capacitors – Open Circuits at DC

21

- Current through a capacitor is proportional to the time rate of change of the voltage across the capacitor

$$i(t) = C \frac{dv}{dt}$$



- A DC voltage does not change with time, so

$$\frac{dv}{dt} = 0 \quad \text{and} \quad i(t) = 0$$

- ***A capacitor is an open circuit at DC***

Capacitors in Parallel

22

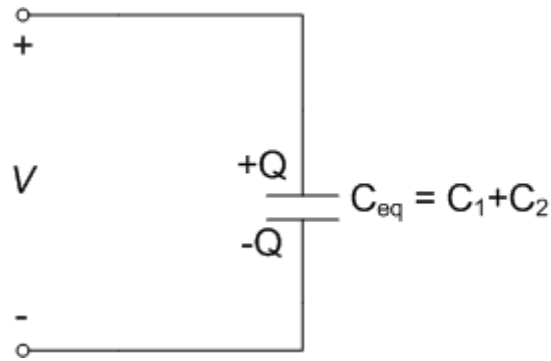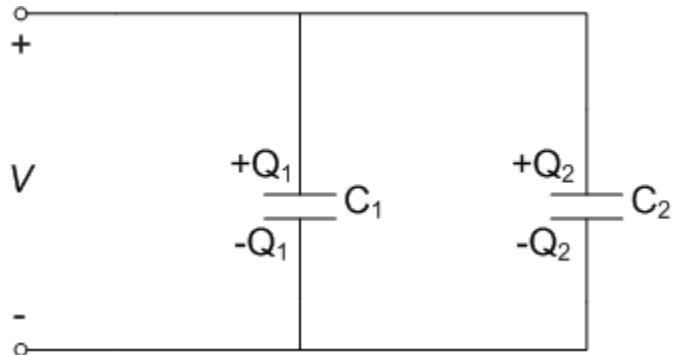

- Total charge on two parallel capacitors is

$$Q = Q_1 + Q_2$$

$$Q = C_1V + C_2V$$

$$Q = (C_1 + C_2)V$$


$$Q = C_{eq}V$$

- ***Capacitances in parallel add***

$$C_{eq} = C_1 + C_2$$

Capacitors in Series

23

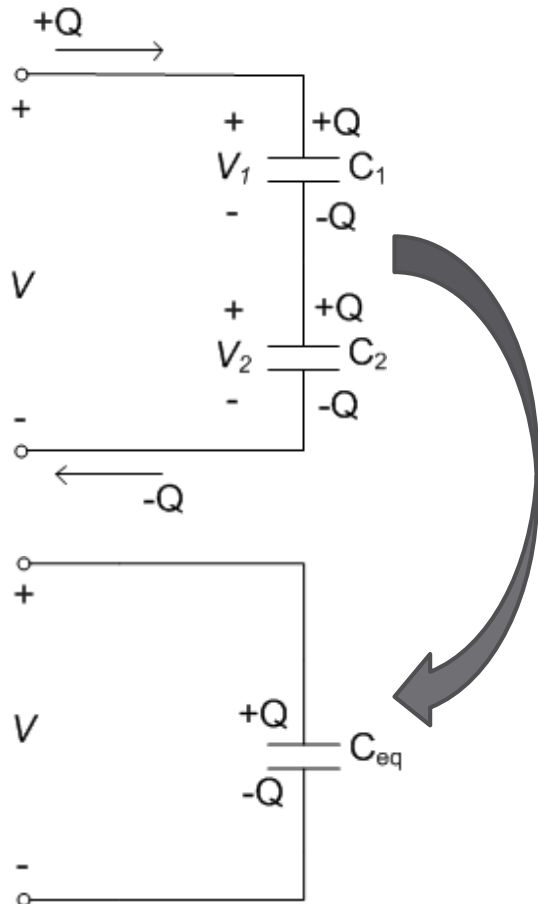

- Total voltage across the series combination is

$$V = V_1 + V_2$$

$$V = \frac{Q}{C_1} + \frac{Q}{C_2}$$



$$V = Q \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = \frac{Q}{C_{eq}}$$

- ***The inverses of capacitors in series add***

$$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1} = \frac{C_1 C_2}{C_1 + C_2}$$


Constant Current Onto a Capacitor

24

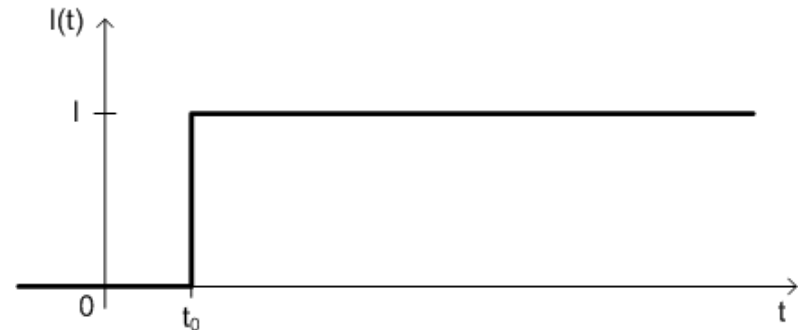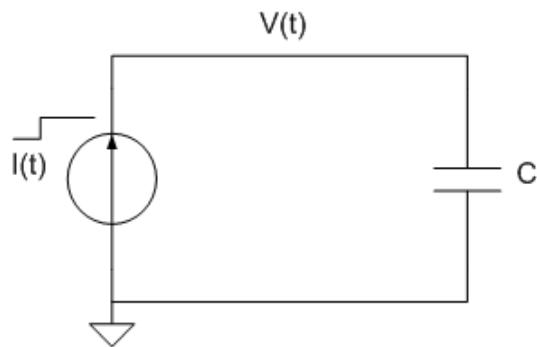

- Capacitor voltage increases linearly for constant current
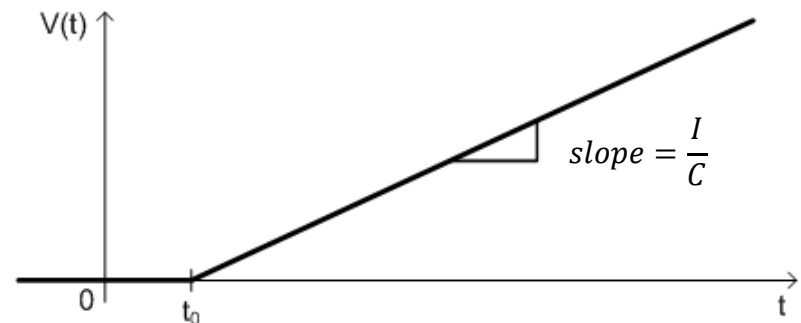
$$v(t) = \frac{I(t-t_0)}{C}, \quad t \geq t_0$$



Capacitor – Energy Storage

25


- Capacitors store **electrical energy**
 - ▣ Energy stored in the **electric field**

- Stored energy is proportional to:

- ▣ Voltage
- ▣ Charge differential

$$E = \frac{1}{2} QV = \frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C}$$

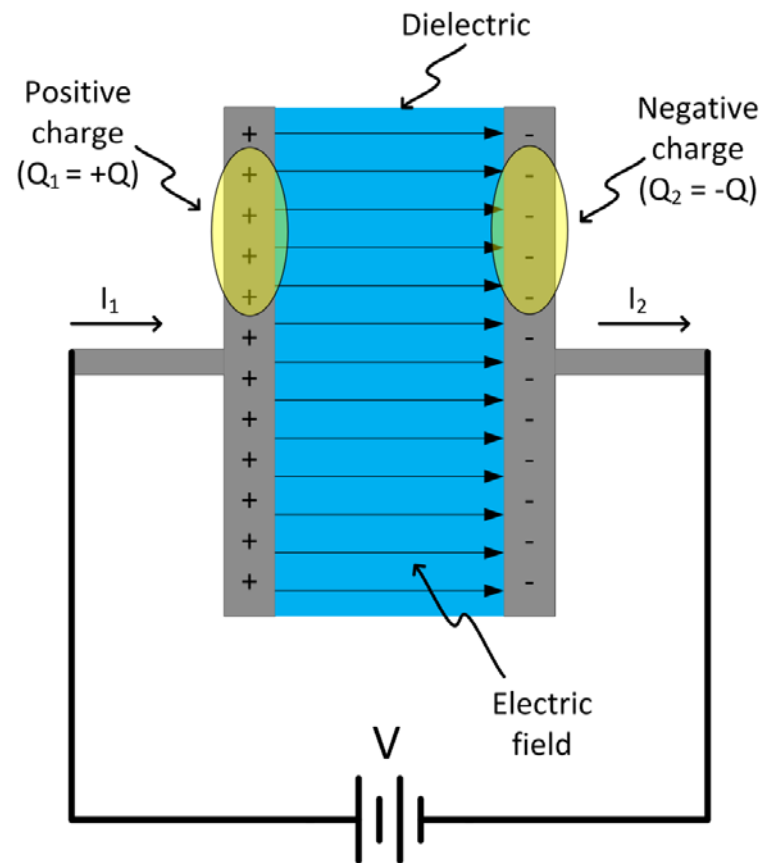- Energy released as E-field collapses
 - ▣ V and I supplied



26

Fluid Inductor

Fluid Inductor

27


□ Consider the following device:

- Lossless pipe
- Heavy paddle-wheel/turbine
 - Frictionless bearing
 - Moment of inertia, I

□ Incompressible fluid

$$Q_1 = Q_2$$

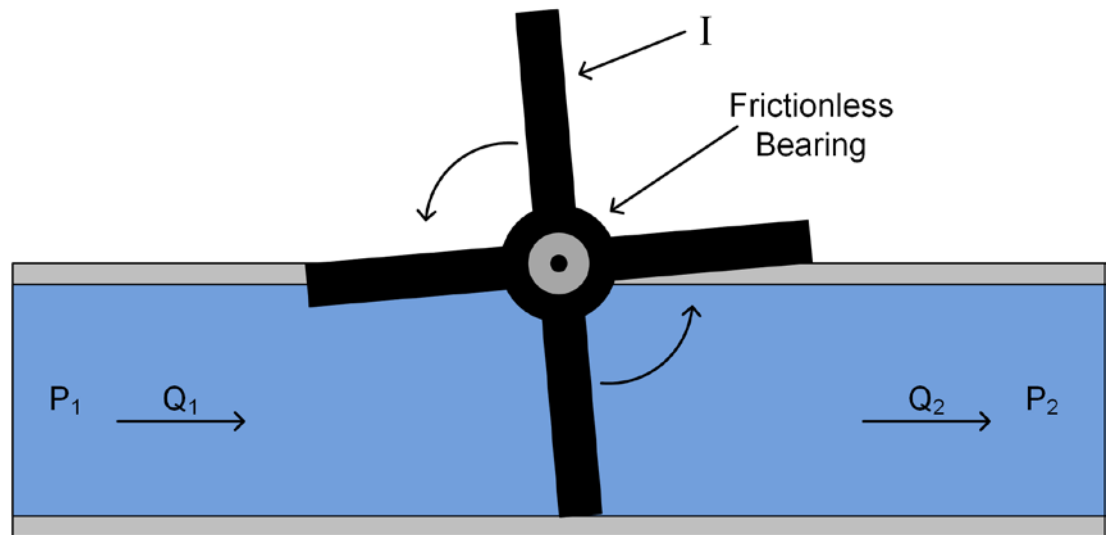□ Paddle wheel rotates at same rate as the flow



Fluid Inductor – Constant Flow Rate

28

- Constant flow rate

$$Q_1 = Q_2 = Q$$

- Constant paddle-wheel angular velocity


- ▣ Zero acceleration
- ▣ Zero net applied force

- Frictionless bearing

- ▣ No force required to maintain rotation

- Zero pressure differential

$$\Delta P = P_1 - P_2 = 0$$

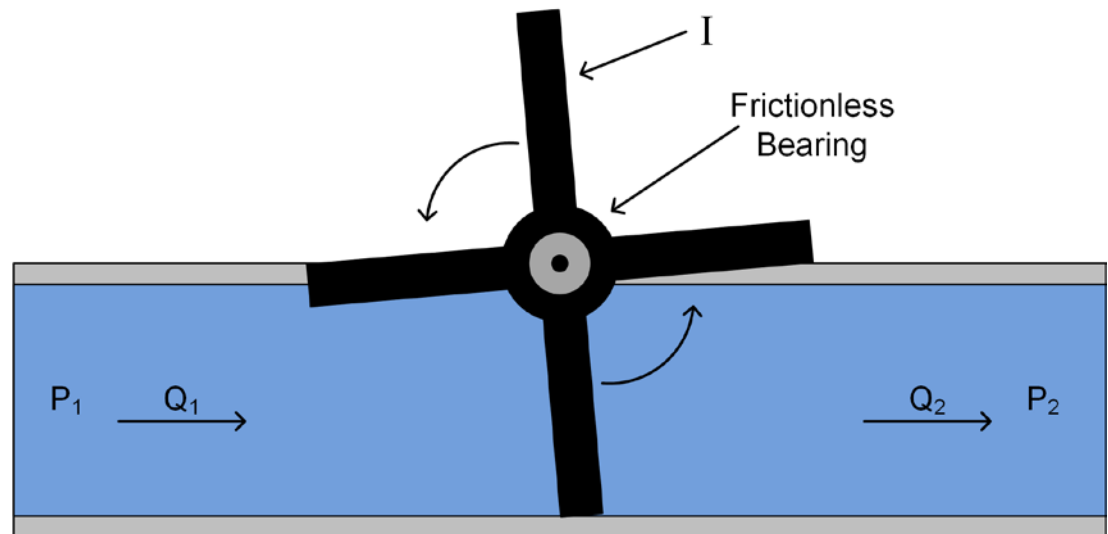

Fluid Inductor – Constant ΔP

29

- Constant pressure differential


$$\Delta P = P_1 - P_2 \neq 0$$

- Constant applied torque
 - ▣ Constant angular acceleration
- Flow rate increases linearly with time

$$Q_1(t) = Q_2(t) = \frac{\Delta P}{L} \cdot t + Q_0$$

- L is **inductance**
 - ▣ Intrinsic device property

$$L \propto I$$

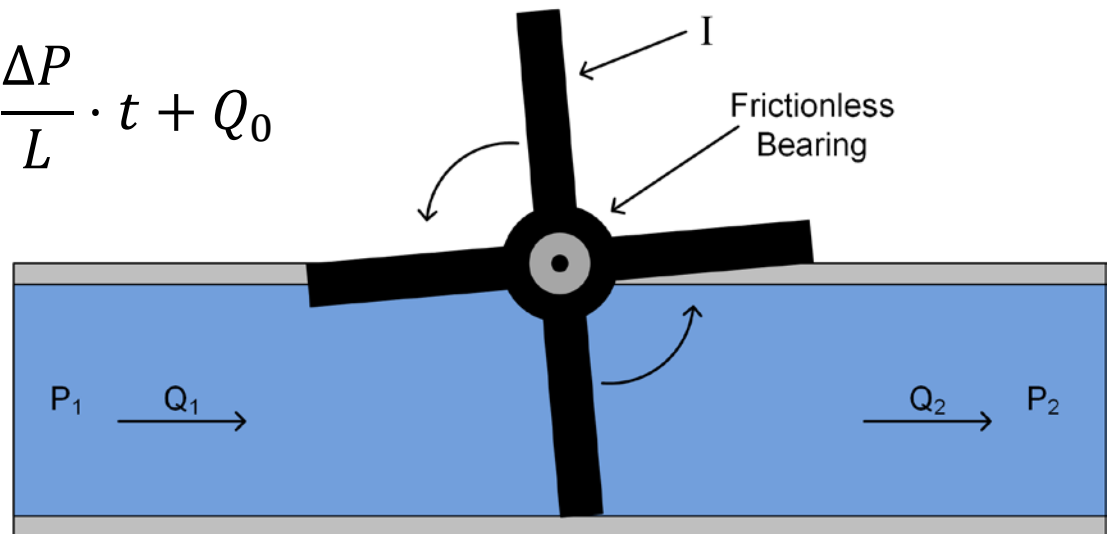


Fluid Inductor – Changing Flow Rate

30

- Paddle wheel has inertia (inductance)
 - ▣ Does not want to change angular velocity
- Changes in flow rate require:
 - ▣ Paddle-wheel acceleration
 - ▣ Torque
 - ▣ Pressure differential
- Pressure differential associated with changing flow rate:

$$\Delta P = L \frac{dQ}{dt}$$

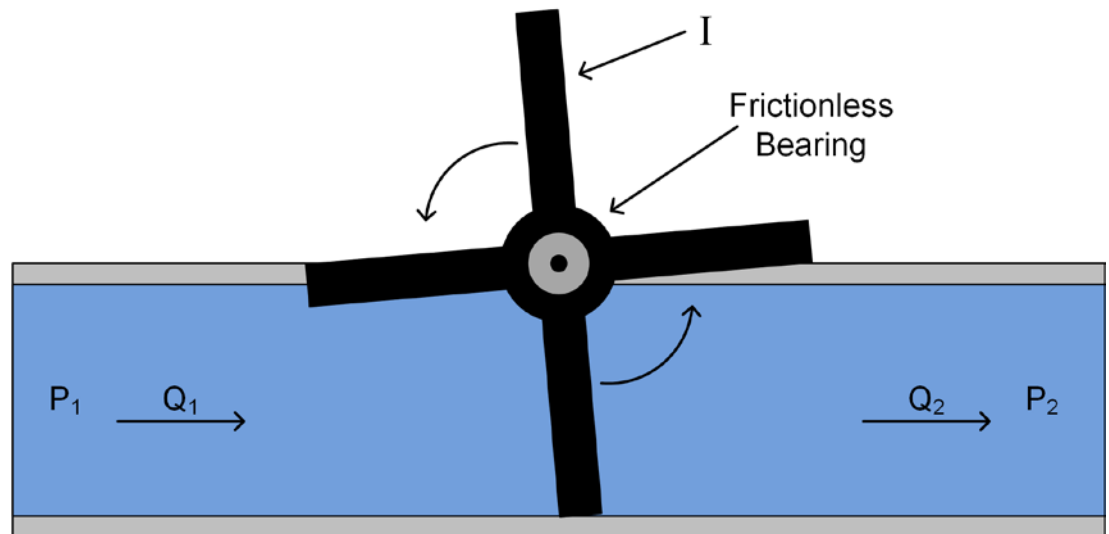

Fluid Inductor – AC vs. DC

31


- **Steady state (DC) flow**
 - No pressure differential
 $\Delta P = 0$
- Consider a **sinusoidal (AC)** flow rate:

$$Q_1 = Q_2 = Q \sin(\omega t)$$

- Sinusoidal acceleration
- Sinusoidal torque
- Sinusoidal pressure differential:

$$\Delta P = L \frac{dQ}{dt} = \omega L Q \cos(\omega t)$$

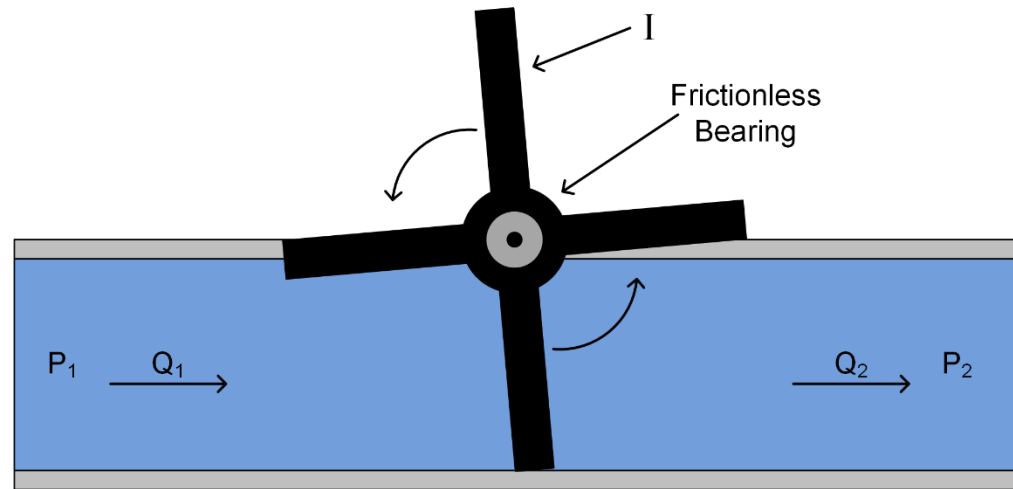
- ΔP proportional to:
 - Inductance
 - Frequency



Fluid Inductor – Changing Flow Rate

32

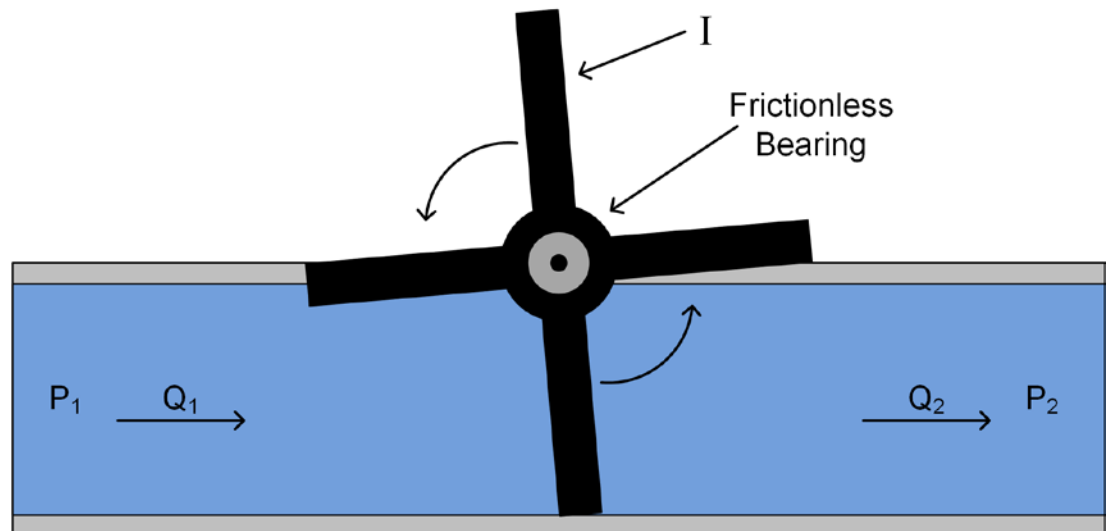- Each flow rate has a corresponding angular velocity
 - ▣ Changes in flow rate require changes in angular velocity
- Angular velocity cannot change instantaneously from one value to another:
 - ▣ Must accelerate continuously through all intermediate values
- ***Flow rate through a fluid inductor cannot change instantaneously***
 - ▣ Would require:
 - $dQ/dt = \infty$
 - $\Delta P = \infty$





33

Electrical Inductors

Electrical Inductors

34

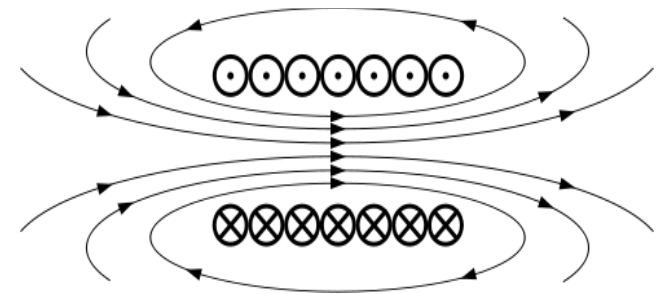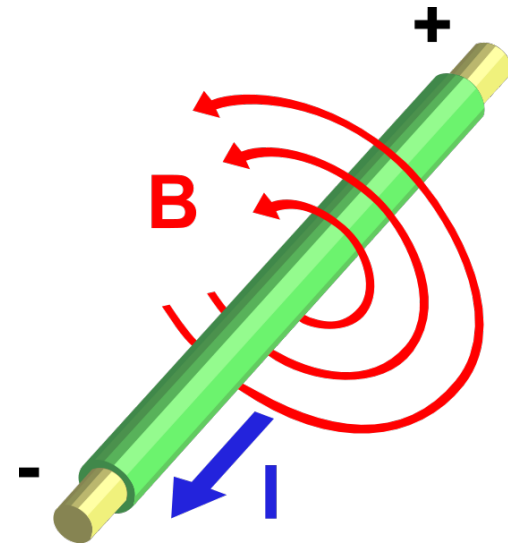- **Inductance**
 - ▣ Electrical property impeding changes in electrical current
- **Ampere's law**
 - ▣ Electrical current induces a magnetic field surrounding the conductor in which it flows
- **Electromagnetic induction**
 - ▣ As current changes, the changing magnetic field induces a voltage that **opposes the changing current**



Inductors

35


□ **Inductors**

- Electrical components that store energy in a magnetic field
- Coils of wire
- Often wrapped around a magnetic core
- Magnetic fields from current in adjacent turns sum
- Inductance is proportional to the number of turns

□ Schematic symbol:



□ Units: **henries** (H)

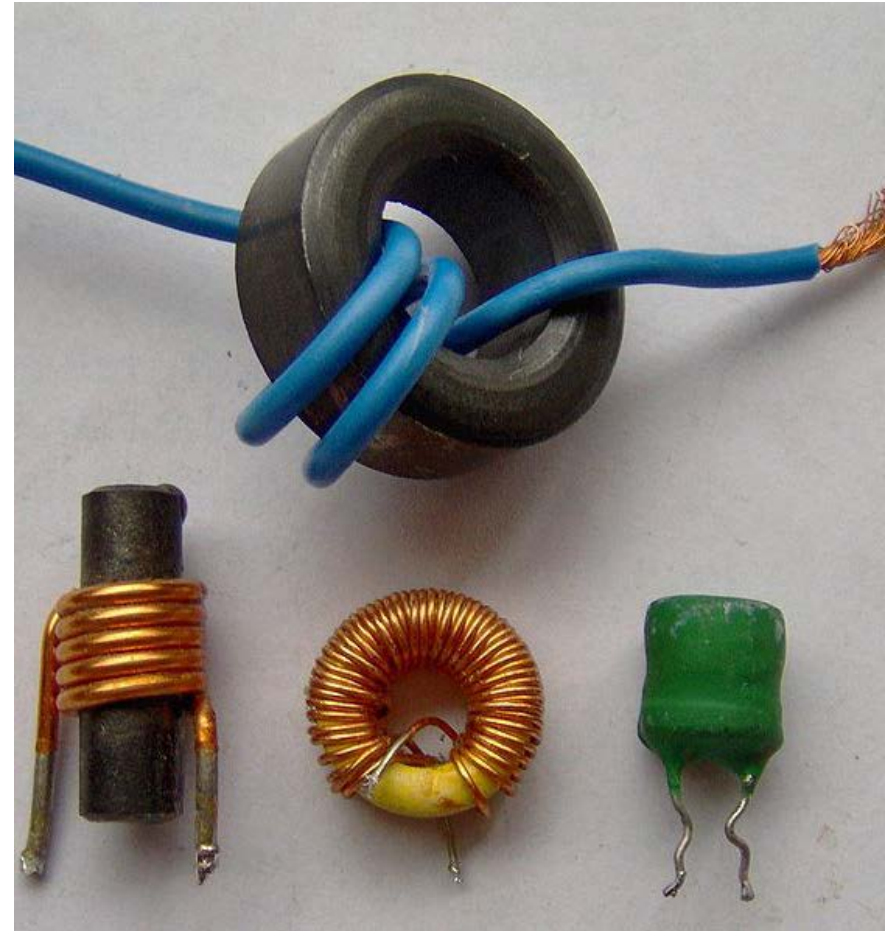


Inductors – Voltage and Current

36

- Voltage across an inductor is proportional to:
 - ▣ Inductance
 - ▣ Rate of change of the current

$$v(t) = L \frac{di}{dt}$$

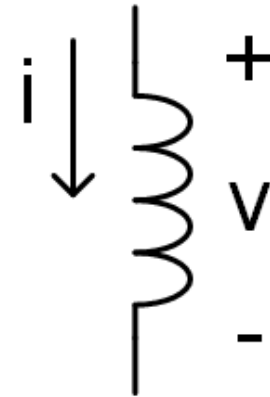

- Current through inductor builds gradually with applied voltage
 - ▣ Inductor integrates voltage

$$i(t) = \frac{1}{L} \int v(t) dt$$

Current Change Through an Inductor

37

- For a step change in current,

$$\frac{di}{dt} = \infty$$

- The corresponding voltage would be *infinite*
- ***Current through an inductor cannot change instantaneously***
- Voltage can change instantaneously, but current is the integral of voltage

$$\lim_{\Delta t \rightarrow 0} \Delta i = \lim_{\Delta t \rightarrow 0} \frac{1}{L} \int_{t_0}^{t_0 + \Delta t} v(t) dt = 0$$

Inductors – Short Circuits at DC

38

- Voltage across an inductor is proportional to the time rate of change of the current through the inductor

$$v(t) = L \frac{di}{dt}$$



- A DC current does not change with time, so

$$\frac{di}{dt} = 0 \quad \text{and} \quad v(t) = 0$$

- ***An inductor is a short circuit at DC***

Inductors in Series

39

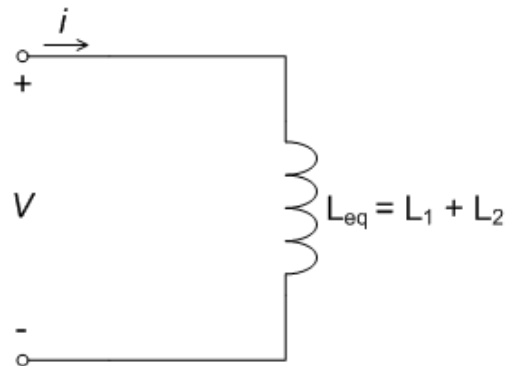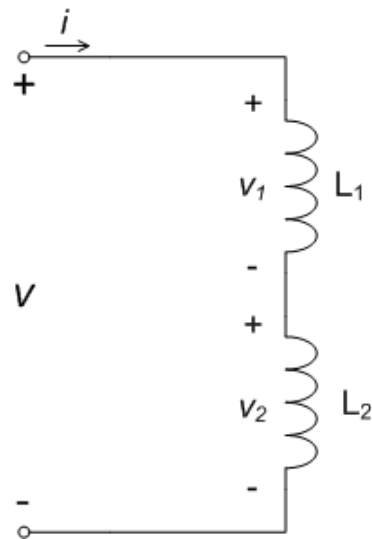

- Total voltage across the series combination is

$$V = V_1 + V_2$$

$$V = L_1 \frac{di}{dt} + L_2 \frac{di}{dt}$$



$$V = \frac{di}{dt} (L_1 + L_2) = L_{eq} \frac{di}{dt}$$

- ***Inductances in series add***

$$L_{eq} = L_1 + L_2$$

Inductors in Parallel

40

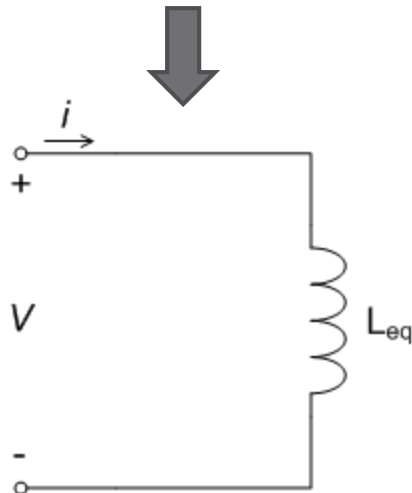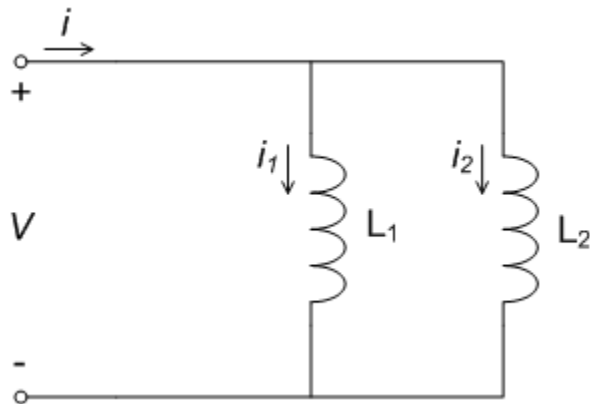

- Voltage across the two parallel inductors:

$$v = L_1 \frac{di_1}{dt} = L_2 \frac{di_2}{dt}$$

so

$$\frac{di_1}{dt} = \frac{v}{L_1}, \quad \frac{di_2}{dt} = \frac{v}{L_2}$$

- Voltage across the equivalent inductor:

$$v = L_{eq} \frac{di}{dt} = L_{eq} \left(\frac{di_1}{dt} + \frac{di_2}{dt} \right)$$

$$v = L_{eq} \left(\frac{v}{L_1} + \frac{v}{L_2} \right)$$

- ***Inverses of inductors in parallel add***

$$L_{eq} = \left(\frac{1}{L_1} + \frac{1}{L_2} \right)^{-1} = \frac{L_1 L_2}{L_1 + L_2}$$


Inductor – Energy Storage

41

- Inductors store ***magnetic energy***
 - ▣ Energy stored in the ***magnetic field***
- Stored energy is proportional to:
 - ▣ Current
 - ▣ Inductance
 - ▣ Magnetic flux: $\lambda = LI$

$$E = \frac{1}{2}LI^2$$

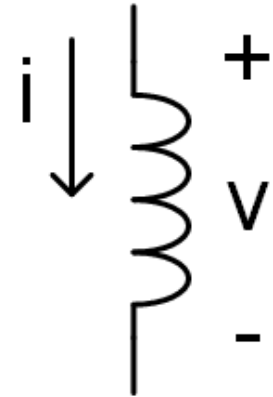- Energy released as magnetic field collapses
 - ▣ V and I supplied



42


Example Problems


A typical US home consumes about 1000 kWh/month.

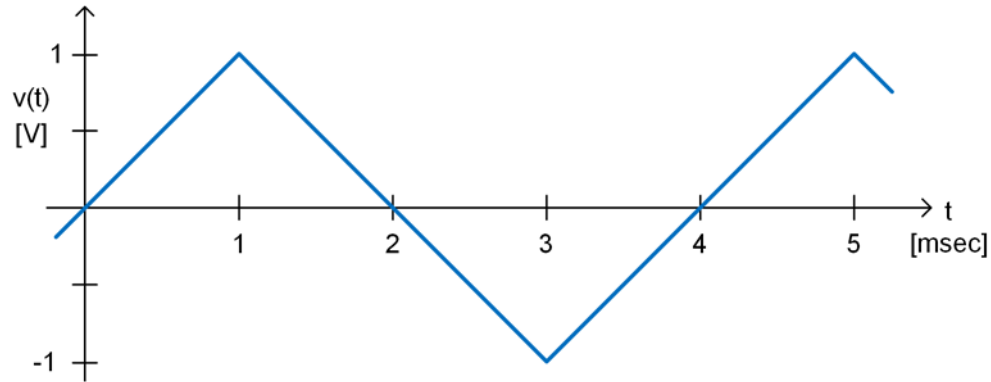- a) To what voltage would a 1 F capacitor need to be charged in order to store this amount of energy?
- b) If the fully-charged voltage is limited to 200 V, how much capacitance would be required to store this amount of energy?

A 10 V, 1 kHz, sinusoidal voltage is applied across a $1 \mu\text{F}$ capacitor. How much current flows through the capacitor?

The following voltage is applied across a $1\mu\text{F}$ capacitor. Sketch the current through the capacitor.



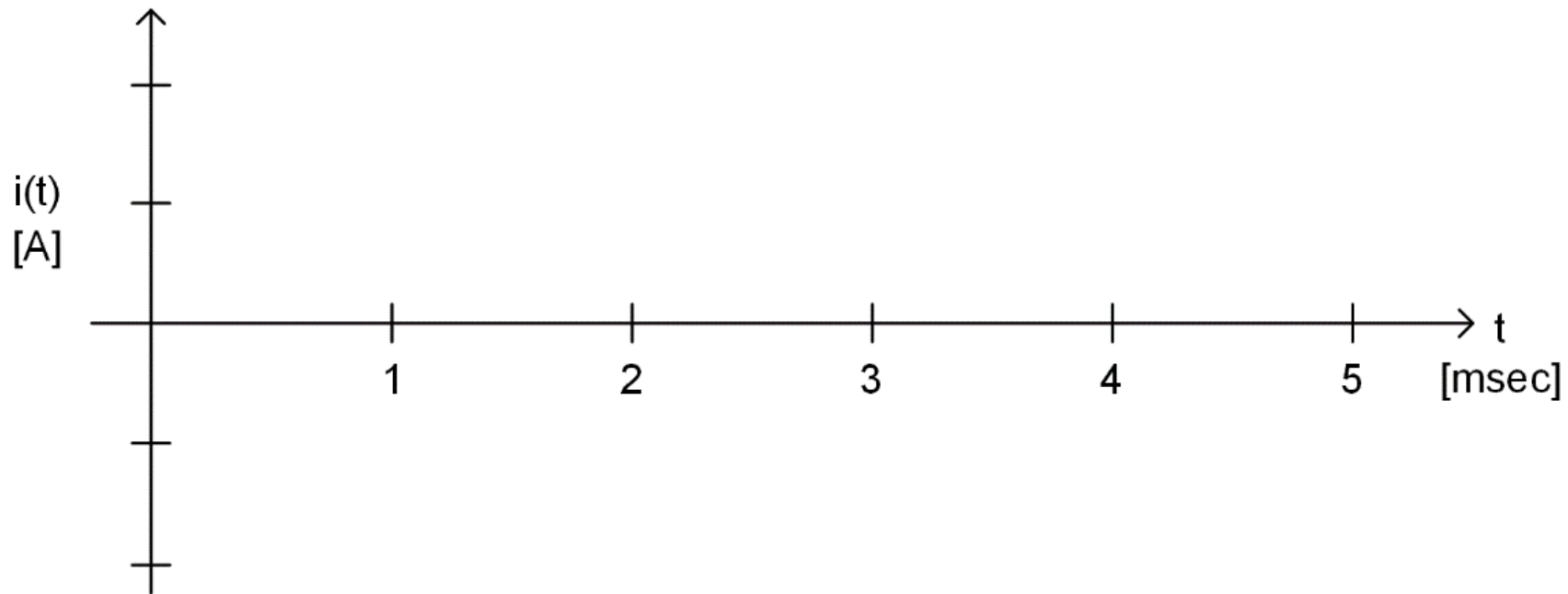

A typical US home consumes about 1000 kWh/month.

- a) How much current would be required in order to store this amount of energy in a 1 H inductor ?
- b) If the maximum current is limited to 200 A, how much inductance would be required to store this amount of energy?

If 10 VDC is applied across a 500 mH inductor, how long will it take the current to reach 10 A?

52

RC Circuits

Step Response


53

□ **Step response**

- Response of a dynamic system (not necessarily electrical) to a step function input

□ **Unit step function or Heaviside step function:**
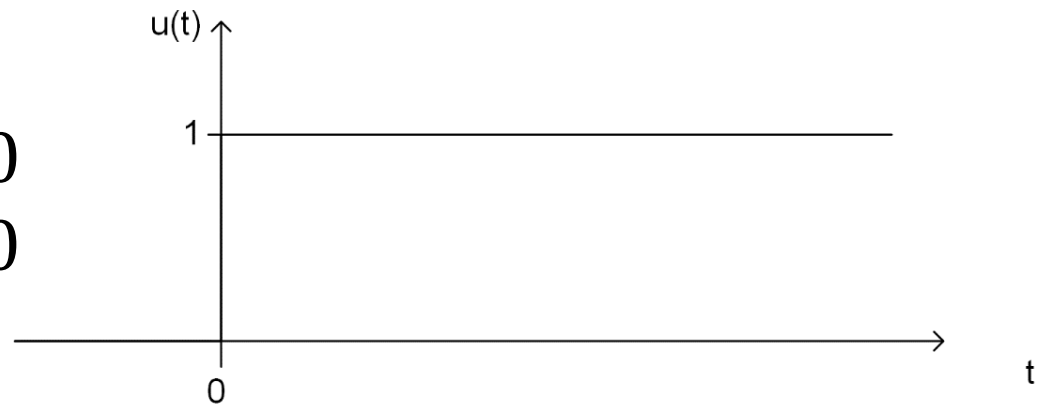
$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t \geq 0 \end{cases}$$





- To characterize an electrical network, a **voltage step** can be applied as an input

RC Circuit – Step Response

54

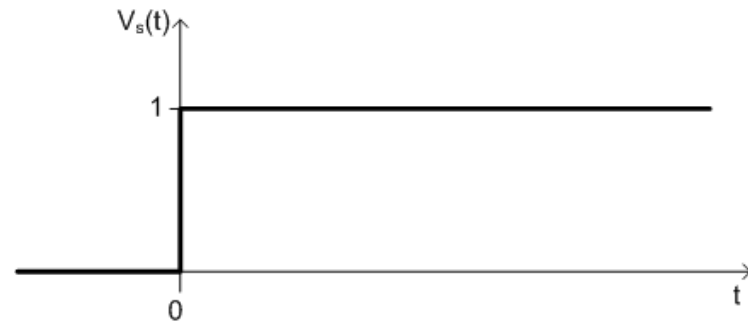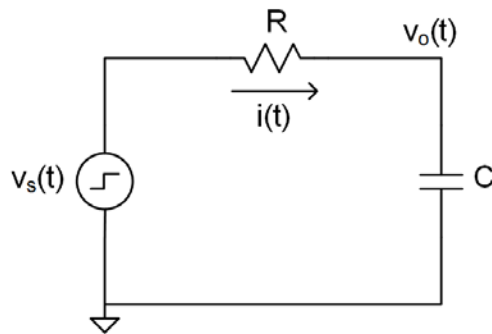
- Step response of this RC circuit is the output voltage in response to a step input: $v_s(t) = 1V \cdot u(t)$



How does $v_o(t)$ get from $v_o(0) = 0V$ to $v_o(\infty) = 1V$?

- For $t < 0$,
 - ▣ $v_s(t) = 0V$
 - ▣ $v_o(t) = 0V$

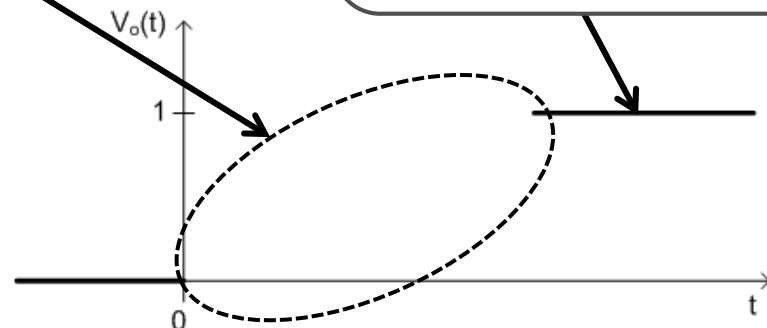- For $t \gg 0$,
 - ▣ $v_s(t) \rightarrow DC$
 - ▣ $C \rightarrow$ open circuit
 - ▣ $v_o(t) \rightarrow 1V$



RC Circuit – Step Response

55

- To determine the step response, apply KVL around the circuit

$$v_s(t) - i(t)R - v_o(t) = 0$$

- Current, $i(t)$, is the capacitor current


$$i(t) = C \frac{dv_o}{dt}$$

- Substituting in for $i(t)$ and $v_s(t)$

$$1 V \cdot u(t) - RC \frac{dv_o}{dt} - v_o(t) = 0$$

- Rearranging
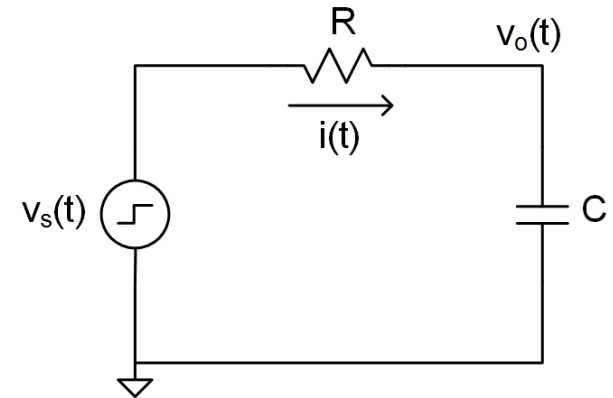
$$\frac{dv_o}{dt} + \frac{1}{RC} v_o(t) = \frac{1 V}{RC} \cdot u(t)$$




RC Circuit – Step Response

56

$$\frac{dv_o}{dt} + \frac{1}{RC}v_o(t) = \frac{1V}{RC} \cdot u(t)$$

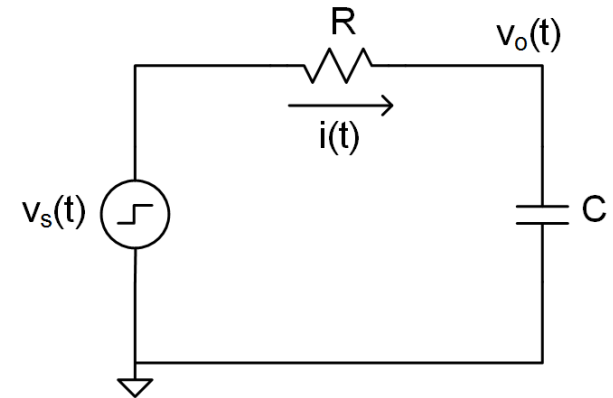- A **first-order linear, ordinary, non-homogeneous differential equation**
- Solution for $v_o(t)$ is the sum of two solutions:
 - ▣ **Complementary** solution
 - ▣ **Particular** solution
- The **complementary solution** is the solution to the homogeneous equation
 - ▣ Set the input (**forcing function**) to zero
 - ▣ The circuit's **natural response**



$$\frac{dv_o}{dt} + \frac{1}{RC}v_o(t) = 0$$

RC Step Response – Homogeneous Solution

57

$$\frac{dv_o}{dt} + \frac{1}{RC}v_o(t) = 0$$

- For a first-order ODE of this form, we assume a solution of the form

$$v_{o_c}(t) = K_0 e^{\lambda t}$$

then

$$\frac{dv_o}{dt} = \lambda K_0 e^{\lambda t}$$

and


$$\lambda K_0 e^{\lambda t} + \frac{1}{RC} K_0 e^{\lambda t} = 0$$

so

$$\lambda + \frac{1}{RC} = 0 \rightarrow \lambda = -\frac{1}{RC} = -\frac{1}{\tau}$$

and
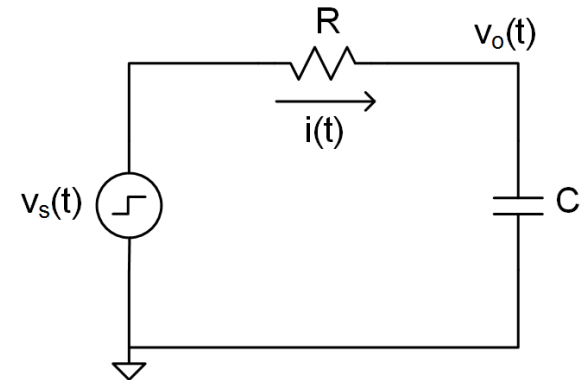
$$v_{o_c}(t) = K_0 e^{-\frac{t}{RC}} = K_0 e^{-\frac{t}{\tau}}$$



RC Step Response – Homogeneous Solution

58

$$v_{o_c}(t) = K_0 e^{-\frac{t}{\tau}}$$


□ The **complementary solution**

- τ is the circuit **time constant**

$$\tau = RC$$

- K_0 is an unknown constant
 - To be determined through application of **initial conditions**

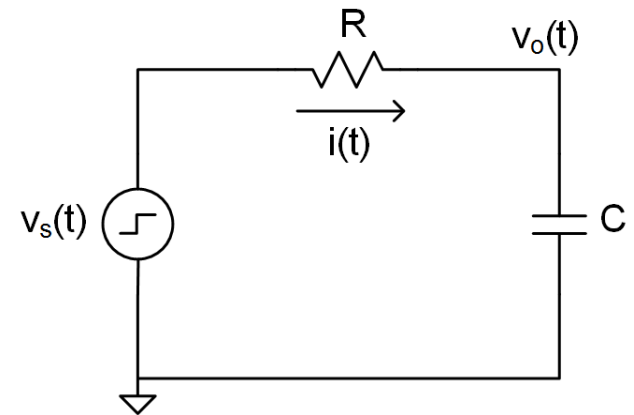□ Next, find the **particular solution**, $v_{o_p}(t)$



RC Step Response – Particular Solution

59

- For a step input, the ***particular solution*** is the circuit's ***steady-state response***


- As $t \rightarrow \infty$
- Long after the input step

- In steady state:

- $v_s(t) = 1\text{ V}$ (DC)
- Capacitor \rightarrow open circuit
- $i(t) = 0$
- $v_o(t) = v_s(t) = 1\text{ V}$

- The ***particular solution***:

$$v_{op}(t) = 1\text{ V}$$

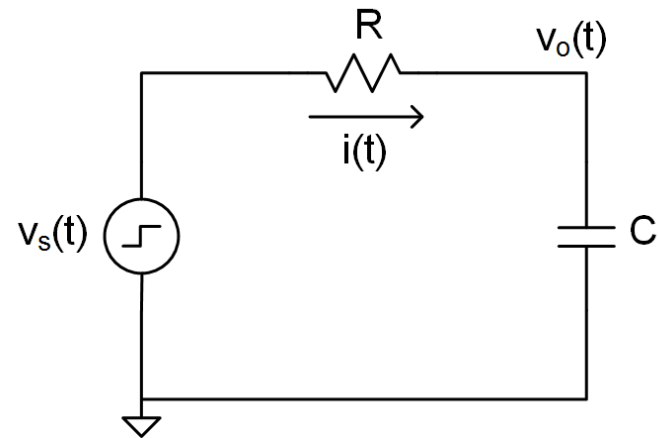

RC Step Response

60

□ **Step response**

- Solution to the non-homogeneous equation
- Sum of the complementary and particular solutions

$$v_o(t) = v_{o_c}(t) + v_{o_p}(t)$$

$$v_o(t) = K_0 e^{-\frac{t}{\tau}} + 1 \text{ V}$$

- Next, determine K_0 by applying an **initial condition**
- For $t < 0$
 - $v_s(t < 0) = 0 \text{ V}$
 - $v_o(t < 0) = 0 \text{ V}$
- At $t = 0$
 - $v_s(0) = 1 \text{ V}$
 - Capacitor voltage cannot change instantaneously
 - $v_o(0) = 0 \text{ V}$ – this is the **initial condition**

RC Step Response

61

- Apply the initial condition




$$v_o(0) = K_0 e^{-\frac{0}{\tau}} + 1 V = 0 V$$

$$v_o(0) = K_0 + 1 V = 0 V$$

$$K_0 = -1 V$$

- The step response is
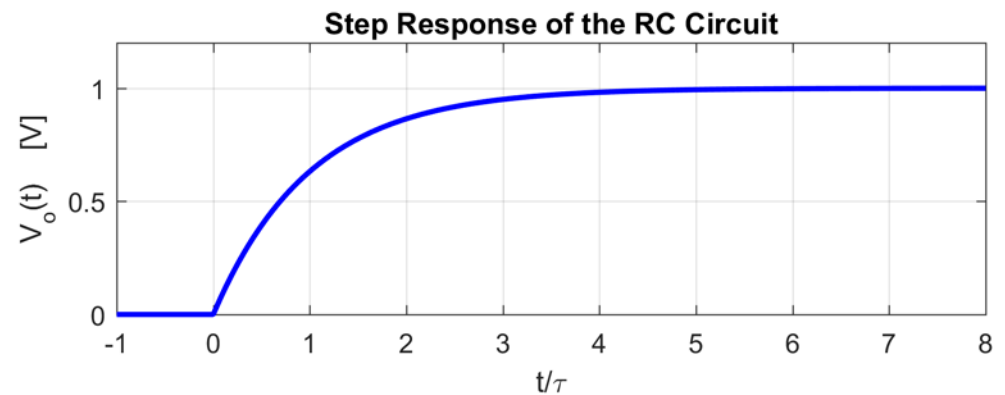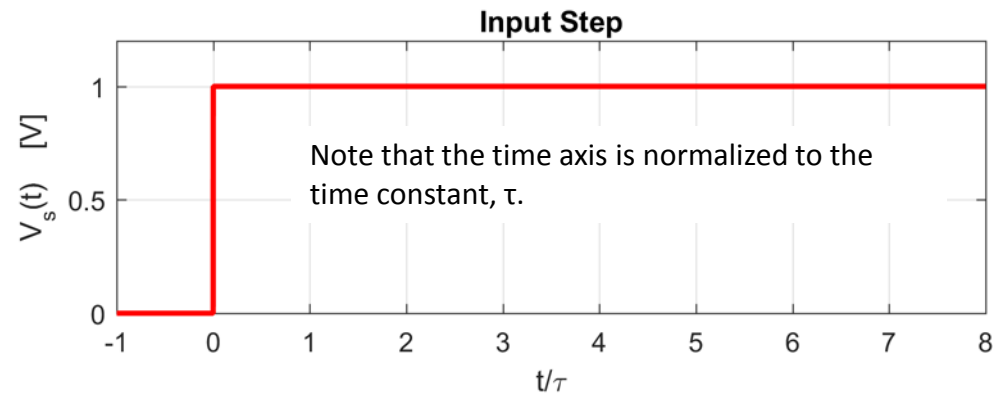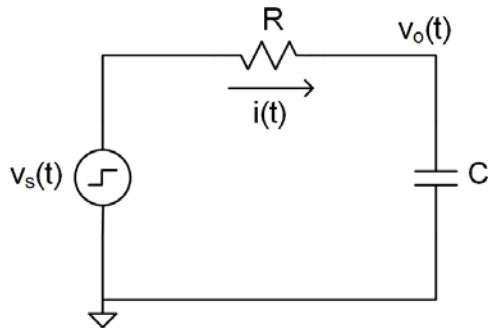
$$v_o(t) = -1 V e^{-\frac{t}{\tau}} + 1 V$$



Step Response – General Solution

62

$$v_o(t) = -1 V e^{-\frac{t}{\tau}} + 1 V$$

- This solution assumes an input that steps from 0 V to 1 V at $t = 0$
 - ▣ These are also the initial and final values of v_o
- Suppose the input steps between two arbitrary voltage levels:

$$v_i(t) = \begin{cases} V_i & t < 0 \\ V_f & t \geq 0 \end{cases}$$

- ▣ Now, the initial condition is

$$v_o(0) = V_i$$

- ▣ The particular solution is the steady-state value, which is now

$$v_{o_p}(t) = v_o(t \rightarrow \infty) = V_f$$

- ▣ Solution to the non-homogeneous equation is

$$v_o(t) = K_o e^{-\frac{t}{\tau}} + V_f$$

Step Response – General Solution

63

- Apply the initial condition to determine K_0

$$v_o(0) = K_0 e^{-\frac{0}{\tau}} + V_f = V_i$$

$$K_0 = V_i - V_f$$

- Substituting in for K_0 gives the general voltage step response:

$$v_o(t) = V_f + (V_i - V_f)e^{-\frac{t}{\tau}}$$

Step Response – General Solution

64

- General RC circuit step response:

$$v_o(t) = V_f + (V_i - V_f)e^{-\frac{t}{\tau}}$$

- General step response for any **first-order linear system** with a finite steady-state value:


$$y(t) = Y_f + (Y_i - Y_f)e^{-\frac{t}{\tau}}$$

- Not necessarily an electrical system
- $y(t)$ is any quantity of interest (voltage, current, temperature, pressure, displacement, etc.)
- $Y_i = y(0)$ is the **initial condition**
- $Y_f = y(t \rightarrow \infty)$ is the **steady-state value**

First-Order Step Response

65

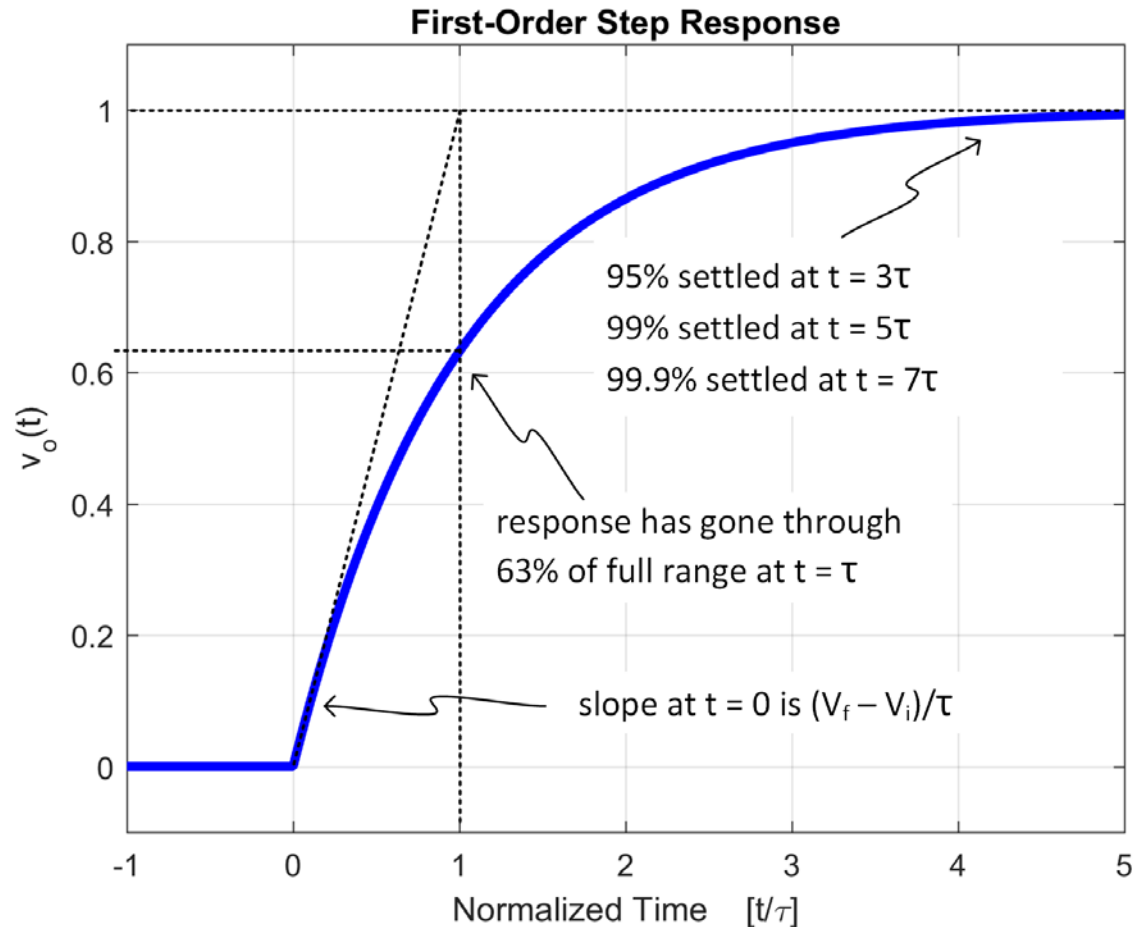- Initial slope is inversely proportional to time constant
- Response completes 63% of transition after one time constant
- Almost completely settled after 7τ



RC Circuit Response – Example

66

- RC circuit driven with negative-going step

$$v_s(t) = \begin{cases} 1\text{ V} & t < 0 \\ 0\text{ V} & t \geq 0 \end{cases}$$

- For $t < 0$



- $v_s(t) = 1\text{ V}$
- $v_o(t) = 1\text{ V}$

- At $t = 0$

- $v_s(0) = 0\text{ V}$
- $v_o(t)$ cannot change instantaneously
- $V_i = v_o(0) = 1\text{ V}$

- As $t \rightarrow \infty$

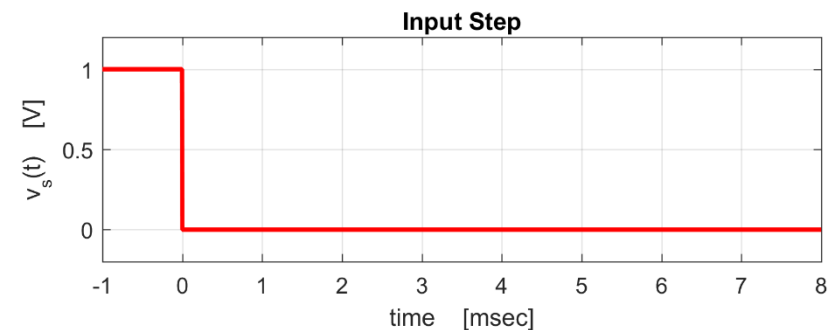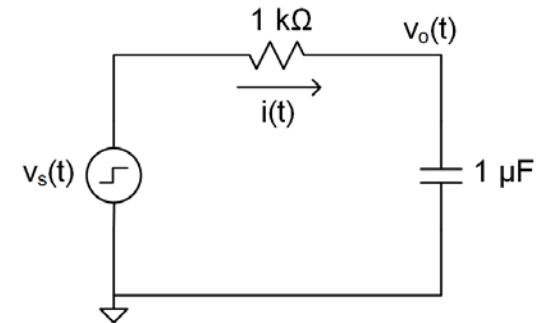- $v_s(t) = 0\text{ V} \rightarrow \text{DC}$
- Capacitor \rightarrow open circuit
- $i(t \rightarrow \infty) = 0\text{ A}$
- $v_o(t \rightarrow \infty) = 0\text{ V}$
- $V_f = 0\text{ V}$



RC Circuit Response – Example

67

- Time constant

$$\tau = RC = 1 \text{ k}\Omega \cdot 1 \mu\text{F}$$




$$\tau = 1 \text{ msec}$$

- Voltage step response

$$v_o(t) = V_f + (V_i - V_f)e^{-\frac{t}{\tau}}$$

$$v_o(t) = 0 \text{ V} + (1 \text{ V} - 0 \text{ V})e^{-\frac{t}{\tau}}$$
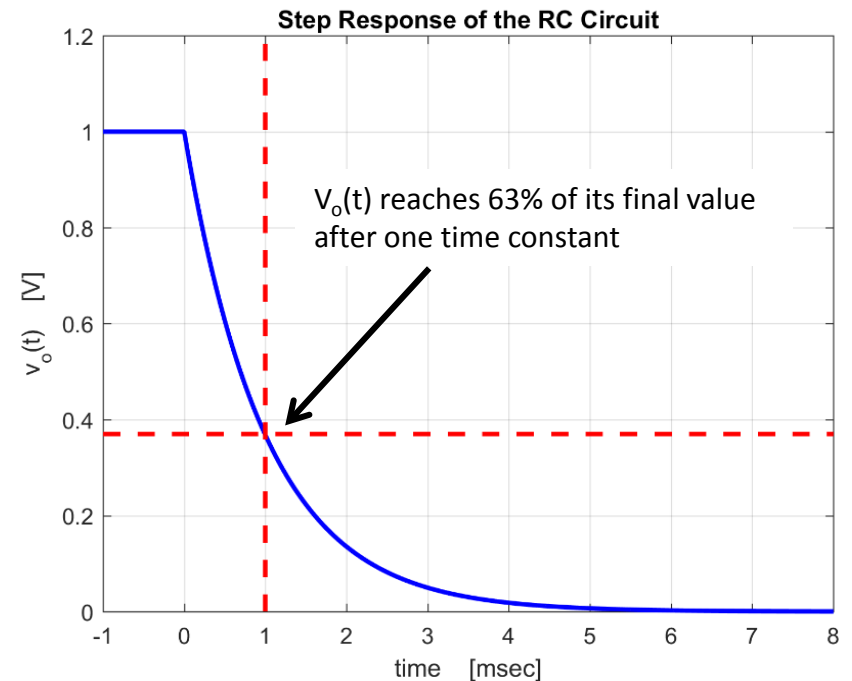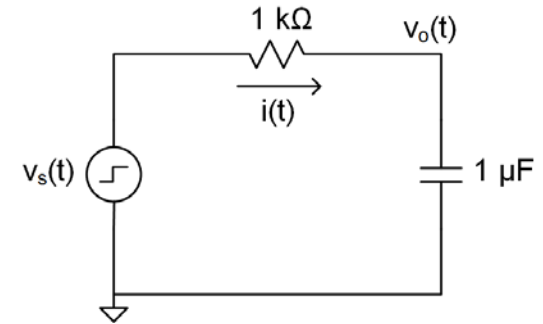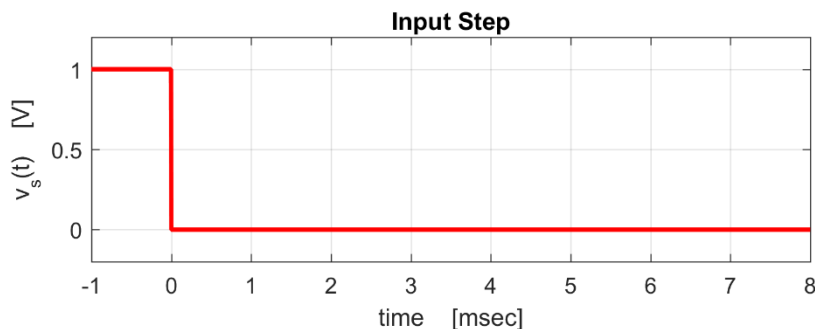
$$v_o(t) = 1 \text{ V} \cdot e^{-\frac{t}{1 \text{ msec}}}$$



Current Step Response

68

- Now, consider the **current** through an RC circuit driven by a positive-going $0\text{ V} \dots 1\text{ V}$ step

- At $t = 0$:



- $v_s(0) = 1\text{ V}$
- $v_o(0) = 0\text{ V}$
- Voltage across resistor:

$$v_s(0) - v_o(0) = 1\text{ V}$$

- Current through resistor:

$$I_i = i(0) = \frac{v_s(0) - v_o(0)}{R}$$

$$I_i = \frac{1\text{ V}}{R}$$

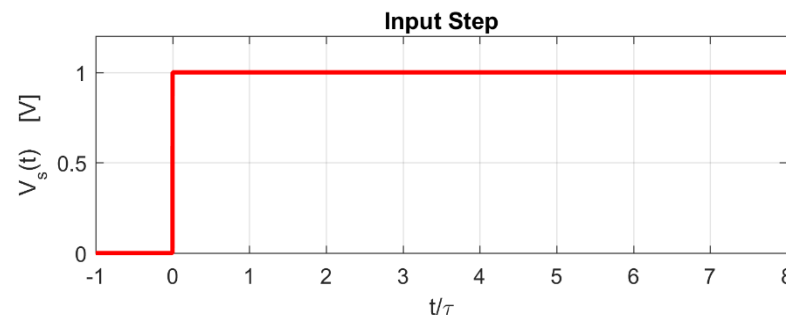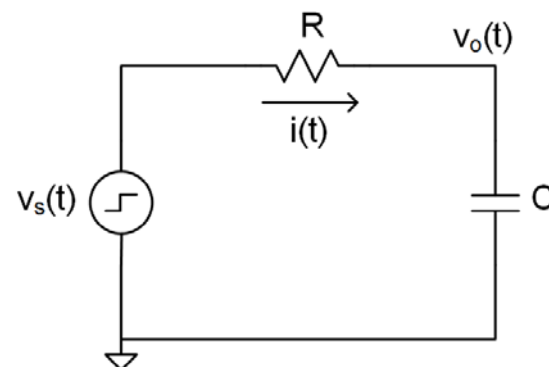

Current Step Response



69

- As $t \rightarrow \infty$:
 - Capacitor \rightarrow open circuit
 - Current $\rightarrow 0$
 $I_f = 0$

- The current step response:

$$i(t) = I_f + (I_i - I_f)e^{-\frac{t}{\tau}}$$
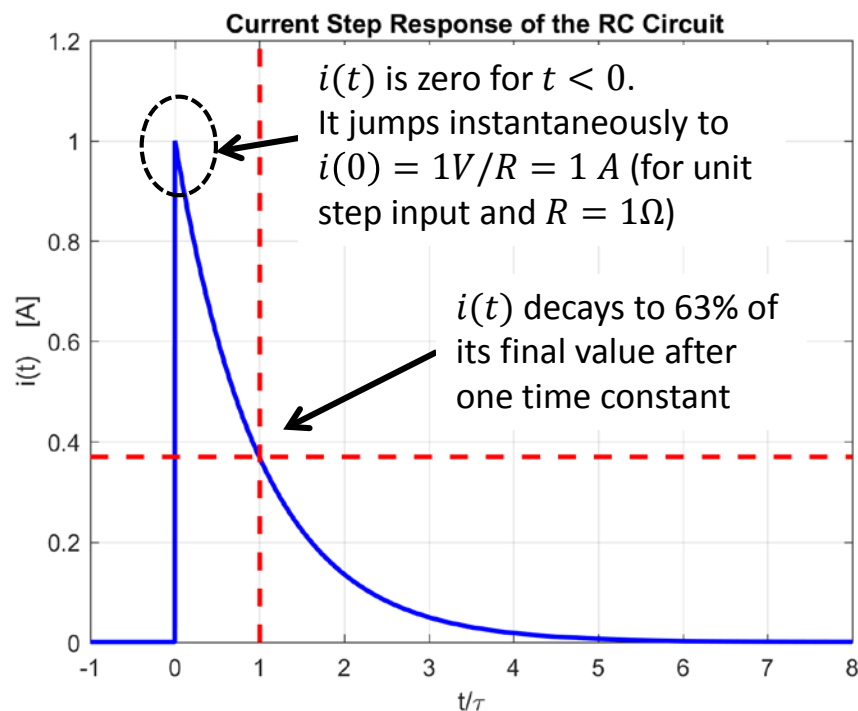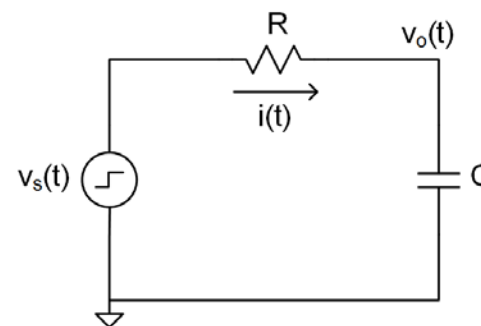
$$i(t) = \frac{1V}{R} e^{-\frac{t}{\tau}}$$




70

Example Problems

Determine $v_o(t)$ for $t \geq 0$.

The input source is:


$$v_s(t) = 2V \cdot u(t) - 1V$$

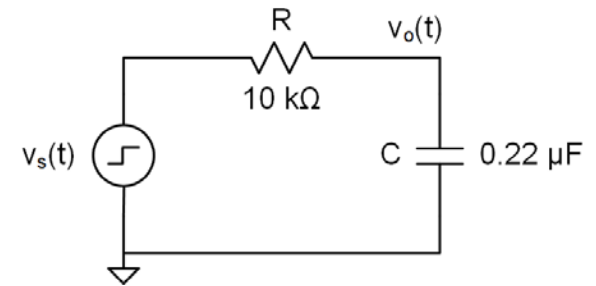

Determine $v_o(t)$ for $t \geq 0$.

The input source is:


$$v_s(t) = 1 \text{ V} \cdot u(t)$$

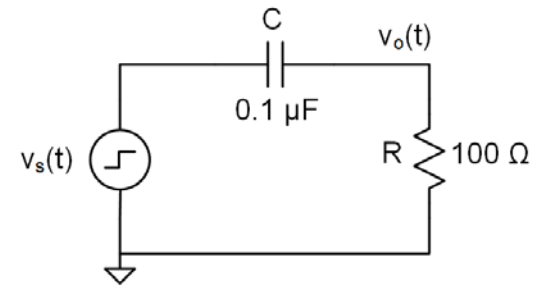

Determine $v_o(t)$ for $t \geq 0$.

The input source is:

$$v_s(t) = 1 \text{ V} \cdot u(t)$$

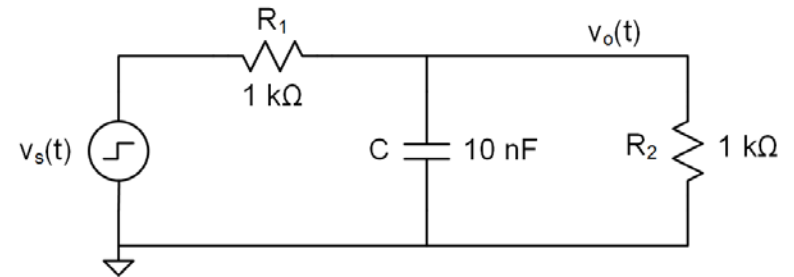



79

RL Circuits

RL Circuit – Step Response

80

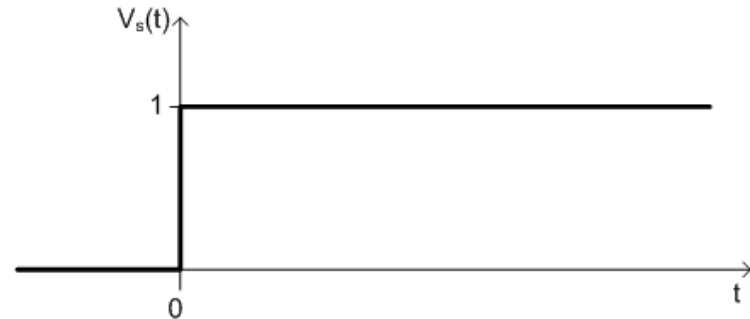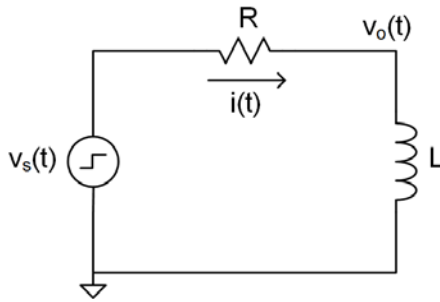- For the RL circuit, we'll first look at the *current* step response




How does $i(t)$ get from I_i to I_f ?

- For $t < 0$,
 - ▣ $v_s(t) = 0\text{ V}$
 - ▣ $i(t) = 0\text{ A}$

- At $t = 0$,
 - ▣ Current cannot change instantaneously
 - ▣ $i(0) = 0\text{ A} = I_i$

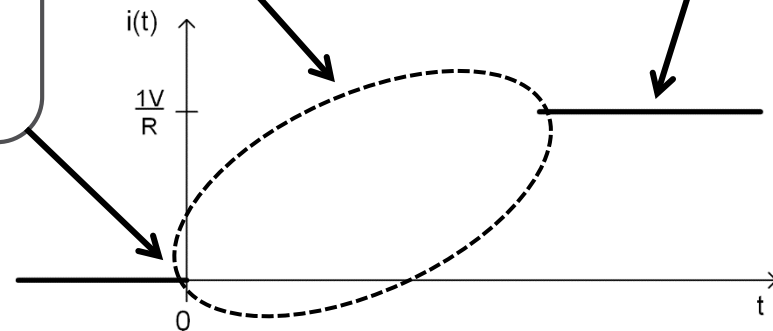- For $t \gg 0$,
 - ▣ $v_s(t) = 1\text{ V} \rightarrow \text{DC}$
 - ▣ $L \rightarrow \text{short circuit}$
 - ▣ $i(t) \rightarrow 1\text{ V}/R = I_f$



RL Circuit – Step Response


81

- To determine the step response, apply KVL around the circuit

$$v_s(t) - i(t)R - L \frac{di}{dt} = 0$$

- Here, we have a differential equation for $i(t)$
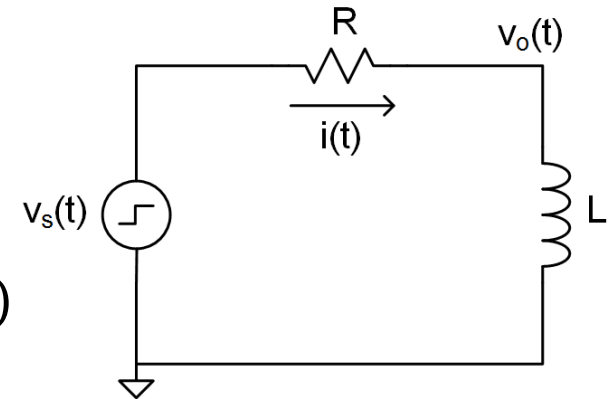
$$\frac{di}{dt} + \frac{R}{L}i(t) = \frac{1}{L}v_s(t)$$



- This is in the exact same form as the voltage ODE for the RC circuit
 - ▣ Same general solution applies

$$i(t) = I_f + (I_i - I_f)e^{-\frac{t}{\tau}}$$

- ▣ Where, now, the **time constant** is

$$\tau = \frac{L}{R}$$

RL Circuit – Step Response



82

□ Current step response:

$$i(t) = I_f + (I_i - I_f)e^{-\frac{t}{\tau}}$$

$$i(t) = \frac{1\text{ V}}{R} - \frac{1\text{ V}}{R}e^{-\frac{t}{\tau}}$$

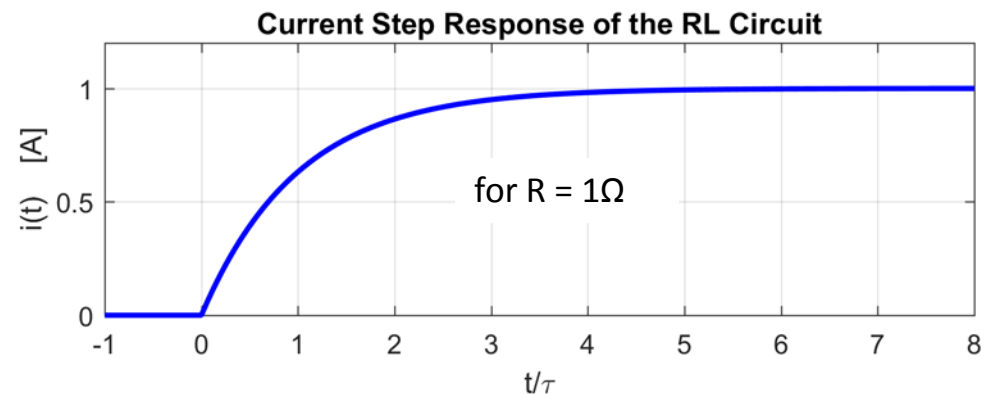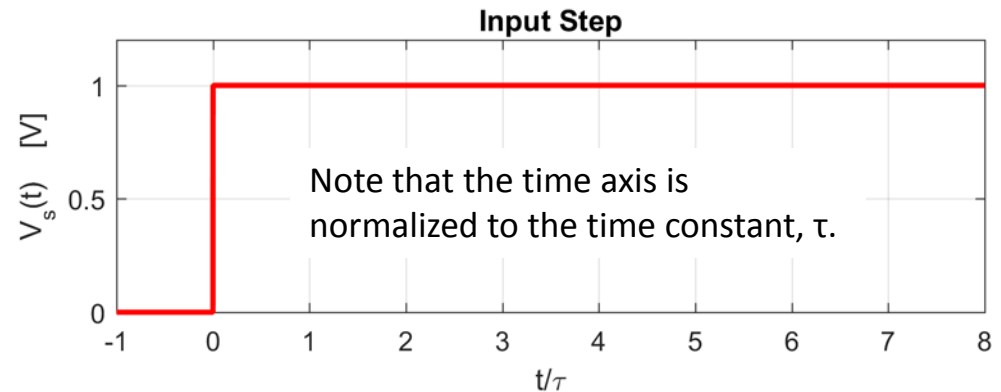
$$i(t) = \frac{1\text{ V}}{R} \left(1 - e^{-\frac{t}{\tau}}\right)$$



RL Circuit – Step Response

83

- Now consider the voltage step response
- Determine **initial** and **final values**:
 - For $t < 0$
 - $v_s(t) = 0 V$
 - $i(t) = 0 A$
 - $v_o(t) = 0 V$
 - At $t = 0$
 - $v_s(0) = 1 V$
 - Current through the inductor cannot change instantaneously, so $i(0) = 0 A$
 - No voltage drop across the resistor, so $v_o(0) = 1 V$
 - $V_i = 1 V$
 - As $t \rightarrow \infty$
 - $v_s(t) \rightarrow DC$
 - Inductor \rightarrow short circuit, so $v_o(t \rightarrow \infty) = 0 V$
 - $V_f = 0 V$

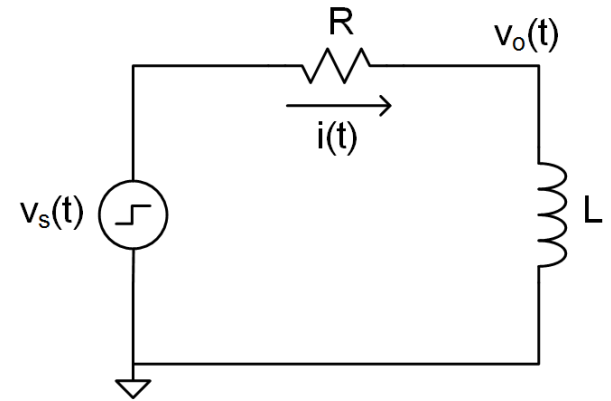

RL Circuit – Step Response


84

- Voltage step response:

$$v_o(t) = V_f + (V_i - V_f)e^{-\frac{t}{\tau}}$$

$$v_o(t) = 0\text{ V} + (1\text{ V} - 0\text{ V})e^{-\frac{t}{\tau}}$$
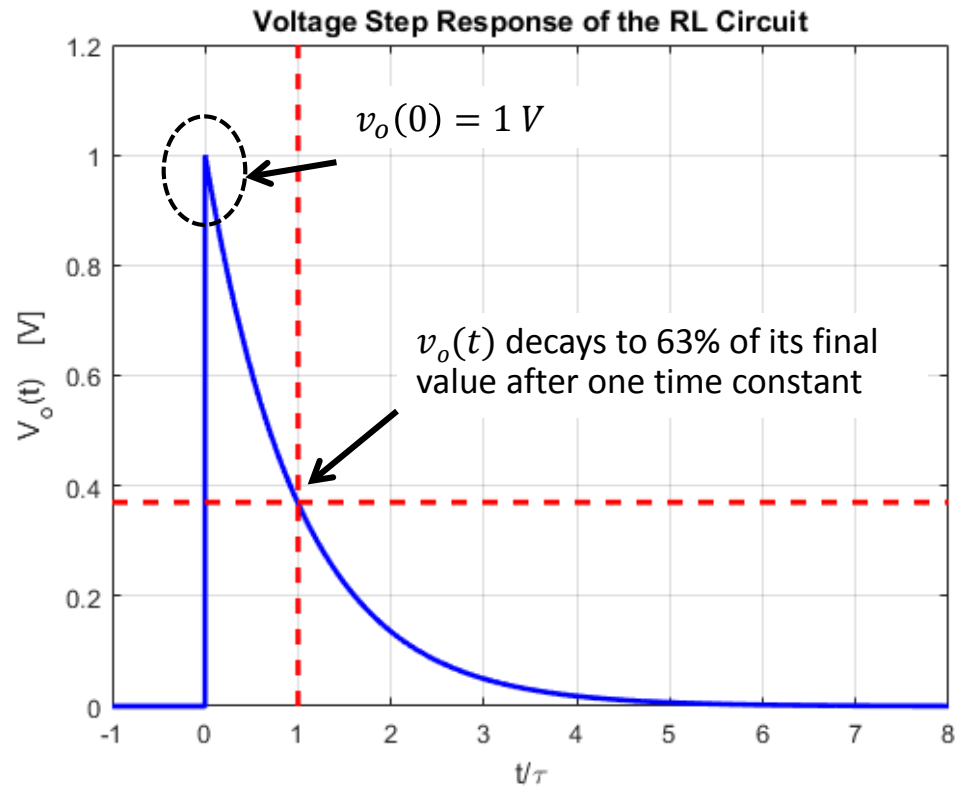
$$v_o(t) = 1\text{ V}e^{-\frac{t}{\tau}}$$



RL Circuit Response – Example

85

- RL circuit driven with negative-going step



$$v_s(t) = \begin{cases} 1 \text{ V} & t < 0 \\ 0.2 \text{ V} & t \geq 0 \end{cases}$$

- For $t < 0$

- $v_s(t) = 1 \text{ V}$ (DC)
- Inductor is a short circuit (DC)
- $v_o(t) = 0 \text{ V}$
- $i(t) = 1 \text{ V}/1 \text{ k}\Omega = 1 \text{ mA}$

- At $t = 0$

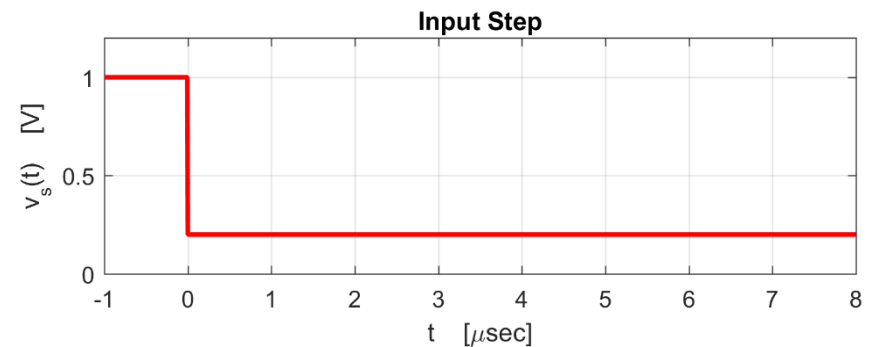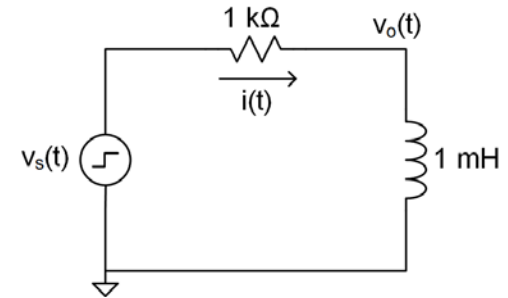- $v_s(0) = 0.2 \text{ V}$
- $i(t)$ cannot change instantaneously
 - $i(0) = 1 \text{ mA}$
 - $v_o(0) = v_s(0) - 1 \text{ mA} \cdot 1 \text{ k}\Omega = -0.8 \text{ V}$
 - $V_i = -0.8 \text{ V}$



- As $t \rightarrow \infty$

- $v_s(t) = 0.2 \text{ V} \rightarrow \text{DC}$
- Inductor \rightarrow short circuit
- $v_o(t \rightarrow \infty) = 0 \text{ V}$
- $V_f = 0 \text{ V}$

RL Circuit Response – Example

86

- Time constant

$$\tau = \frac{L}{R} = 1 \frac{mH}{1 k\Omega}$$




$$\tau = 1 \mu sec$$

- Voltage step response

$$v_o(t) = V_f + (V_i - V_f)e^{-\frac{t}{\tau}}$$

$$v_o(t) = 0 V + (-0.8 V - 0 V)e^{-\frac{t}{\tau}}$$
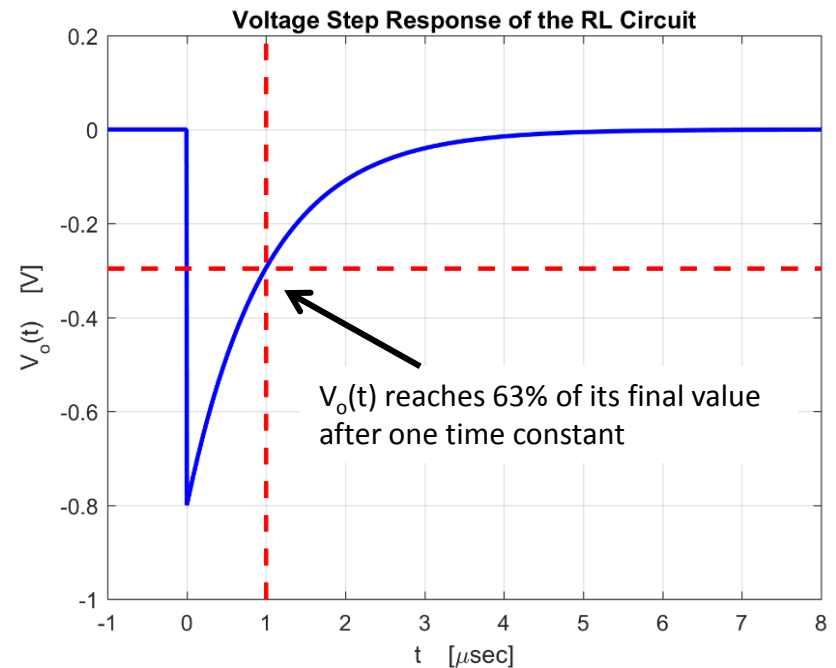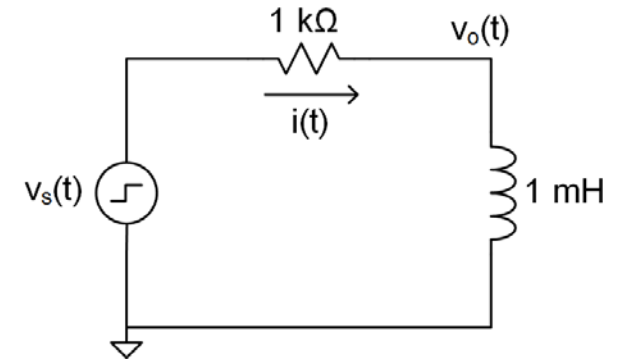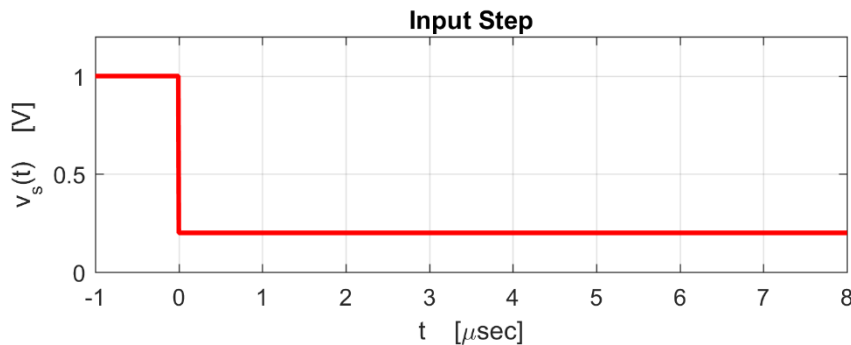
$$v_o(t) = -0.8 V \cdot e^{-\frac{t}{1 \mu sec}}$$




87


Example Problems


Determine $v_o(t)$ and $i(t)$ for $t \geq 0$.

The input source is:


$$v_s(t) = -2 V \cdot u(t) + 4 V$$

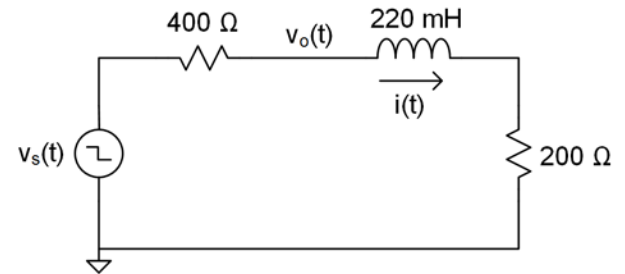


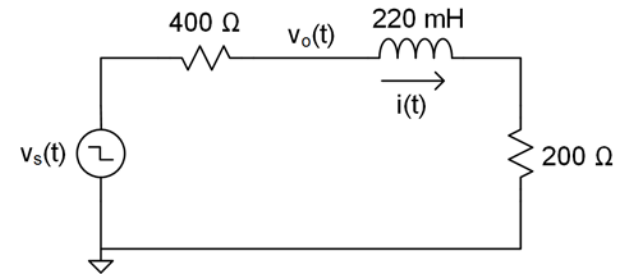

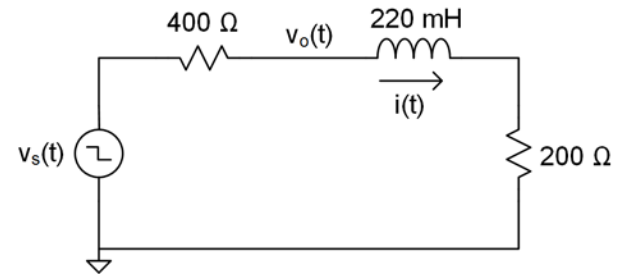

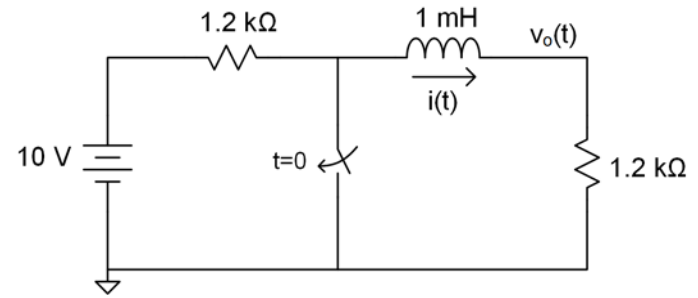Determine $v_o(t)$ and $i(t)$ for $t \geq 0$.



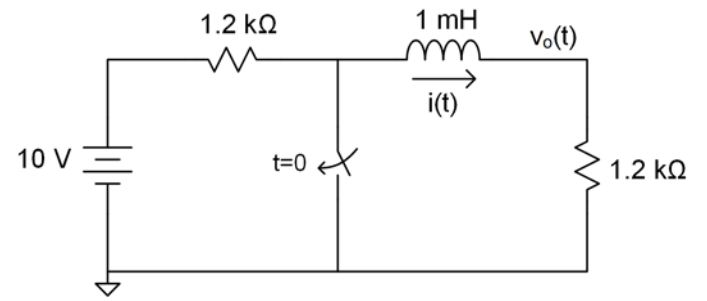

Determine $v_o(t)$
and $i(t)$ for $t \geq 0$.

