

SECTION 4: SECOND-ORDER TRANSIENT RESPONSE

2

Introduction

Second-Order Circuits

3

- In this and the previous section of notes, we consider second-order RLC circuits from two distinct perspectives:
 - ▣ ***Frequency-domain***
 - Second-order, RLC filters
 - ▣ ***Time-domain***
 - Second-order, RLC step response

4

Transient Response of Second-Order Circuits

Second-Order Transient Response


5

- In ENGR 201 we looked at the transient response of first-order RC and RL circuits
 - ▣ Applied KVL
 - Governing differential equation
 - ▣ Solved the ODE
 - Expression for the step response
- For ***second-order circuits***, process is the same:
 - ▣ ***Apply KVL***
 - Second-order ODE
 - ▣ ***Solve the ODE***
 - Second-order step response

Step Response of RLC Circuit

6

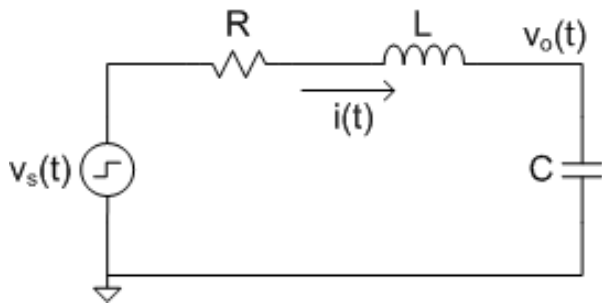- Determine the response of the following RLC circuit
 - Source is a voltage step: $v_s(t) = 1V \cdot u(t)$
 - Output is the voltage across the capacitor



- Apply KVL around the loop


$$v_s(t) - i(t)R - L \frac{di}{dt} - v_o(t) = 0$$

- Want an ODE in terms of $v_o(t)$
 - Need to eliminate $i(t)$
 - Can express $i(t)$ in terms of the output voltage:

$$i(t) = C \frac{dv_o}{dt} \quad \text{so,} \quad \frac{di}{dt} = C \frac{d^2v_o}{dt^2}$$

Step Response of RLC Circuit

7

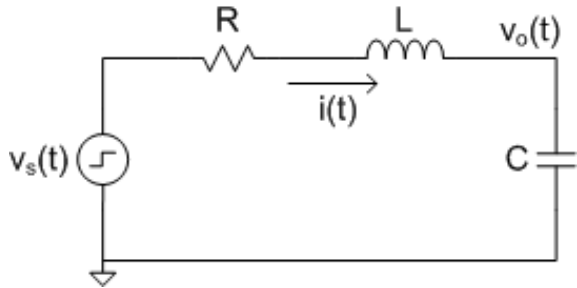

- Substituting in the expression for current, the KVL equation becomes

$$v_s(t) - C \frac{dv_o}{dt} R - LC \frac{d^2 v_o}{dt^2} - v_o(t) = 0$$

- Rearranging gives the governing second-order ODE:

$$\frac{d^2 v_o}{dt^2} + \frac{R}{L} \frac{dv_o}{dt} + \frac{1}{LC} v_o(t) = \frac{1}{LC} v_s(t)$$

- A second-order, linear, non-homogeneous, ordinary differential equation
- Non-homogeneous, so solve in two parts
 - 1) Find the complementary solution to the homogeneous equation
 - 2) Find the particular solution for the step input
- General solution will be the sum of the two individual solutions:

$$v_o(t) = v_{oc}(t) + v_{op}(t)$$

8

Complementary Solution

Complementary Solution – $v_{oc}(t)$

9

- The **homogeneous equation** is obtained by setting the forcing function (input) to zero

$$\frac{d^2 v_o}{dt^2} + \frac{R}{L} \frac{dv_o}{dt} + \frac{1}{LC} v_o(t) = 0$$

- For an ODE of this form, we assume a solution of the form

$$v_{oc}(t) = e^{st}$$

- Where s is an unknown *complex* value. Then

$$\frac{dv_{oc}}{dt} = s e^{st} \quad \text{and} \quad \frac{d^2 v_{oc}}{dt^2} = s^2 e^{st}$$

- Substituting back into the homogeneous ODE yields the **characteristic equation**

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

Complementary Solution – $v_{oc}(t)$

10

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

- The **characteristic equation** can be rewritten as

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

or

$$s^2 + 2\zeta\omega_0 s + \omega_0^2 = 0$$

- The **roots** of the characteristic equation (also called **poles**) tell us about the:
 - ▣ Form of the complementary solution
 - ▣ Nature of the response
- These roots (or **poles**) are

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

where

$$\alpha = \frac{R}{2L} \quad \text{and} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Complementary Solution – $v_{oc}(t)$

11

- We've said we can write the **characteristic equation** as

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

or

$$s^2 + 2\zeta\omega_0 s + \omega_0^2 = 0$$

- The **damping ratio**, ζ , can be defined as

$$\zeta = \frac{\alpha}{\omega_0}$$

- A few key points:
 - ▣ ω_0 is the resonant frequency
 - ▣ ζ characterizes the nature (sharpness) of the resonance
 - ▣ Both are related to the roots of the characteristic equation


Complementary Solution – $v_{oc}(t)$

12

- Complementary solution has the same form as that of a first-order circuit:

$$v_{oc}(t) = e^{st}$$

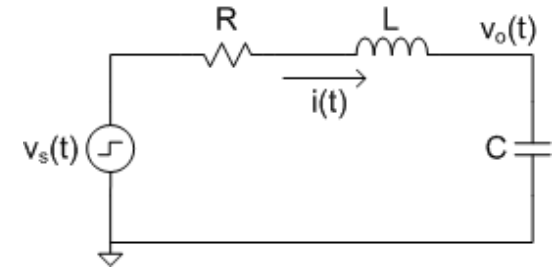- s is the roots of the characteristic equation
 - Now two values – identical or distinct
 - May be complex



- Form of the solution depends on the values of s
 - Can be characterized in terms of the value of ζ :

- $\zeta > 1$ – **over-damped** case:

$$v_{oc}(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

- $\zeta = 1$ – **critically-damped** case:

$$v_{oc}(t) = K_1 e^{s_1 t} + K_2 t e^{s_1 t}$$

- $\zeta < 1$ – **under-damped** case:

$$v_{oc}(t) = K_1 e^{-\alpha t} \cos(\omega_d t) + K_2 e^{-\alpha t} \sin(\omega_d t)$$

Over-Damped RLC Circuit – $\zeta > 1$

13

- Roots of the characteristic equation are

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

- These are related to the damping ratio as

$$\zeta = \frac{\alpha}{\omega_0}$$

- If $\zeta > 1$, then

- $\alpha > \omega_0$
- $\alpha^2 - \omega_0^2 > 0$ – i.e., the discriminant is **positive**
- s_1 and s_2 are **real and distinct**

- Complimentary solution has the following form

$$v_{oc}(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

- Recall that $\zeta > 1$ (actually, $\zeta \geq 0.707$) corresponded to no peaking in the frequency domain

Critically-Damped RLC Circuit – $\zeta = 1$

14

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} , \quad s_2 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

- If $\zeta = 1$, then
 - ▣ $\alpha = \omega_0$
 - ▣ $\alpha^2 - \omega_0^2 = 0$ – i.e., the discriminant is **zero**
 - ▣ s_1 and s_2 are ***real and identical***
- Complimentary solution has the following form

$$v_{oc}(t) = K_1 e^{s_1 t} + K_2 t e^{s_1 t}$$

- This is the lowest value of ζ for which the step response is ***monotonic***
 - ▣ Constantly increasing
 - ▣ ***No overshoot***

Under-Damped RLC Circuit – $\zeta < 1$

15

- If $\zeta < 1$, then
 - ▣ $\alpha < \omega_0$
 - ▣ $\alpha^2 - \omega_0^2 < 0$ – i.e., the discriminant is **negative**
 - ▣ s_1 and s_2 are a **complex conjugate pair**

- Complimentary solution has the following form

$$v_{oc}(t) = K_1 e^{-\alpha t} \cos(\omega_d t) + K_2 e^{-\alpha t} \sin(\omega_d t)$$

- ▣ ω_d is the **damped natural frequency**

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \omega_0 \sqrt{1 - \zeta^2}$$

- Response now contains **damped sinusoidal** components
 - ▣ Will exhibit **overshoot**
 - ▣ Possible **ringing**


Damping Cases – Geometric Interpretation

16

- Roots of characteristic equation (system poles) are, in general, complex
 - Can plot them in the **complex plane**
 - Pole locations tell us a lot about the nature of the response
 - Speed – risetime, settling time
 - Overshoot, ringing


Case 1:

$\zeta > 1$ – *overdamped*

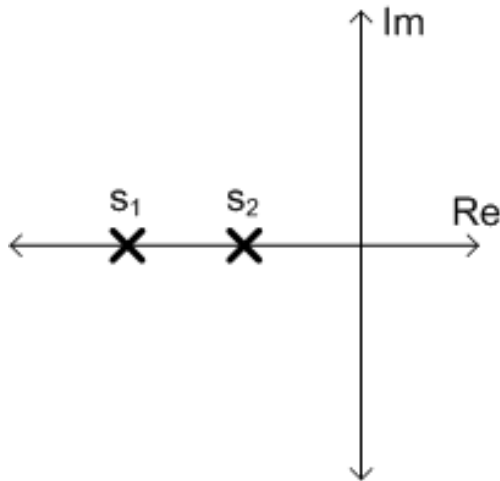


Case 2:

$\zeta = 1$ – *critically-damped*

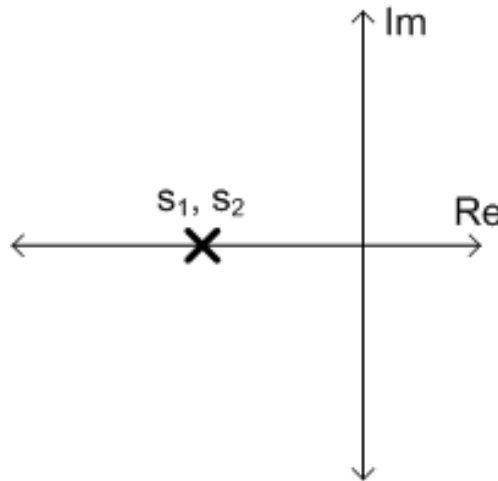

Case 3:

$\zeta < 1$ – *underdamped*

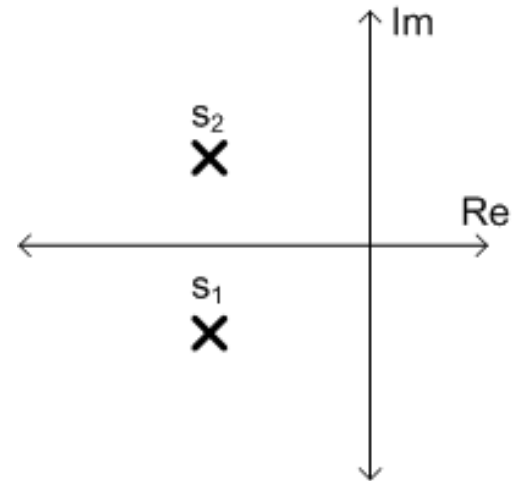

Under-Damped Case – α , ζ , and ω_0

17

- Under-damped case – $\zeta < 1$
- Roots are a complex-conjugate pair


$$s_{1,2} = -\alpha \pm j\omega_d$$

- ▣ α is the real part
- ▣ ω_d is the imaginary part
- ▣ The **magnitude** of the root is

$$\omega_0 = \sqrt{\alpha^2 + \omega_d^2}$$

- ▣ Angle between imaginary axis and vector to the poles is related to damping
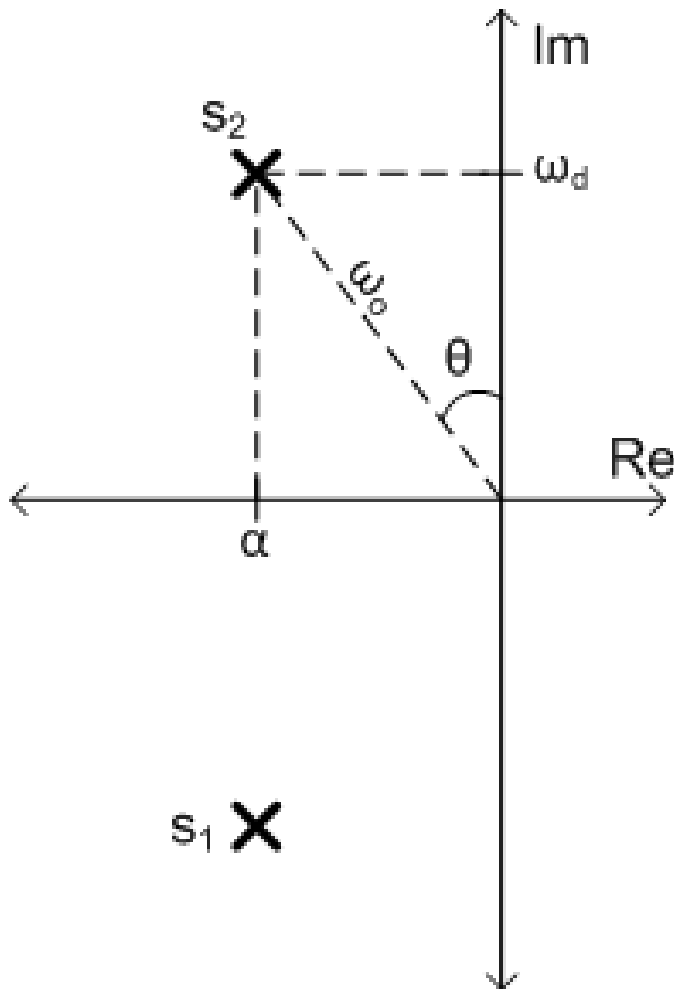
$$\zeta = \frac{\alpha}{\omega_0} = \sin(\theta)$$



18

Particular Solution

Particular solution – $v_{op}(t)$

19

- General solution for the RLC step response is the sum of the complementary and particular solutions


$$v_o(t) = v_{oc}(t) + v_{op}(t)$$

- We now have the complementary solution with two unknown constants, K_1 and K_2
 - ▣ Constants to be determined later through application of ***initial conditions***
- Next, determine the ***particular solution***, $v_{op}(t)$
 - ▣ For a circuit driven by a step input, this is simply the circuit's ***steady-state response***

$$v_{op}(t) = v_o(t \rightarrow \infty)$$

Particular solution – $v_{op}(t)$

20

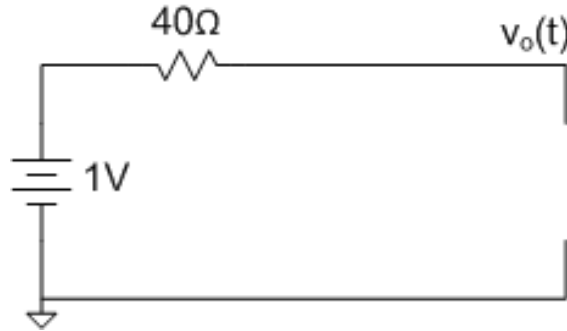

- Particular solution is the circuit's steady-state response
 - ▣ Inductor → short
 - ▣ Capacitor → open

$$v_{op}(t) = v_o(t \rightarrow \infty) = v_s(t > 0)$$


- For a unit step input, the particular solution is

$$v_{op}(t) = 1\text{ V}$$

21

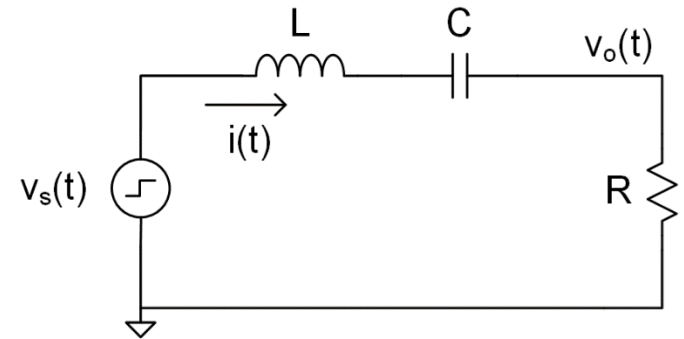
Example Problems

Derive the governing differential equation for the following circuit.



Determine:

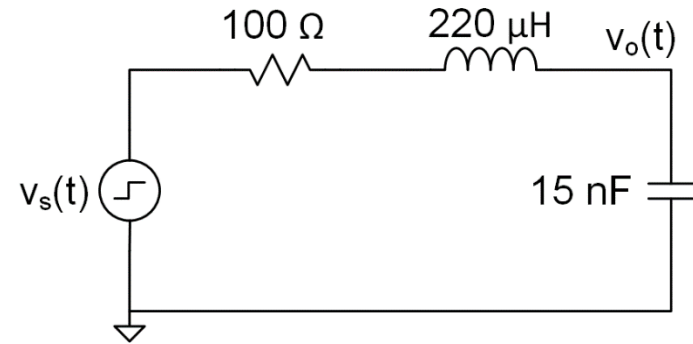- ▣ Damping ratio
- ▣ Damping case
- ▣ Characteristic equation
- ▣ Poles





Determine:


- ▣ Initial conditions
- ▣ Particular solution


For

$$v_s(t) = -1V \cdot u(t) + 2V$$

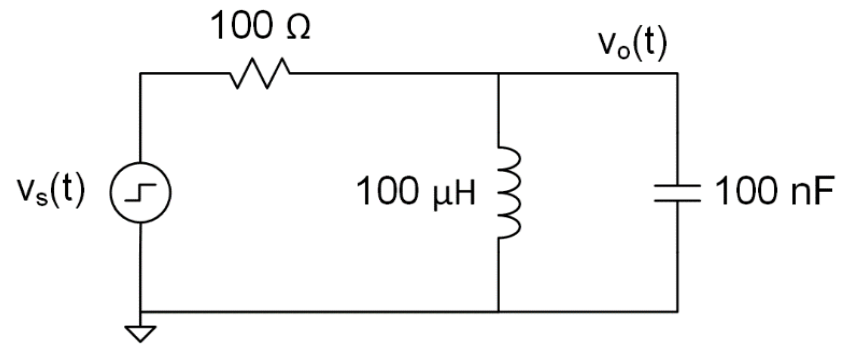


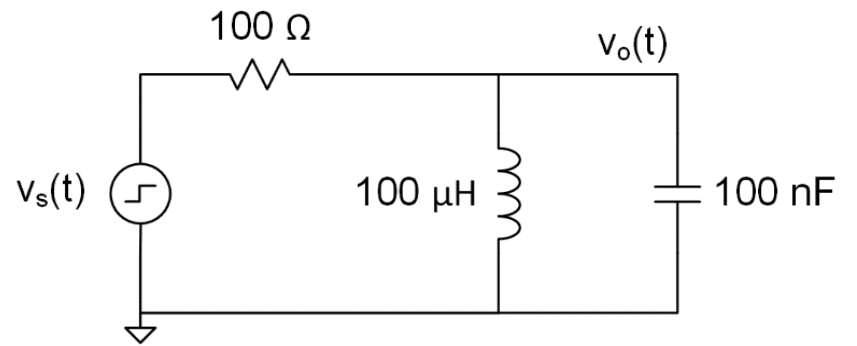

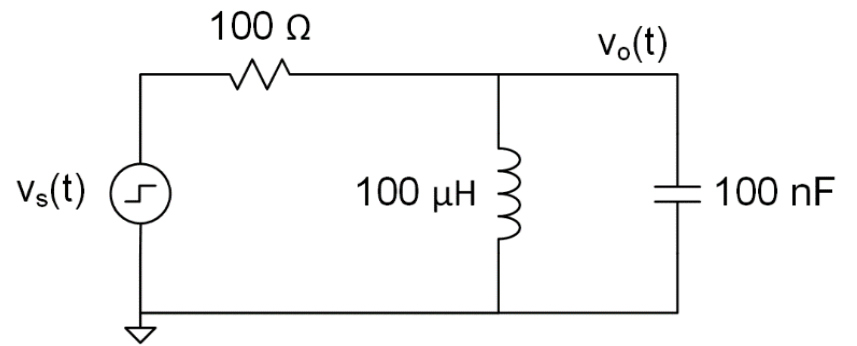

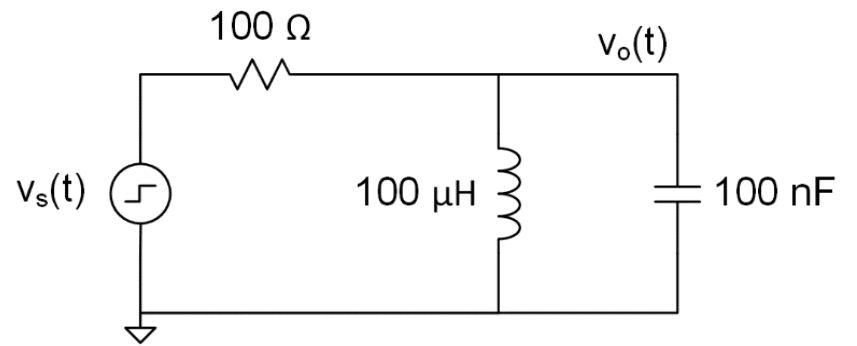

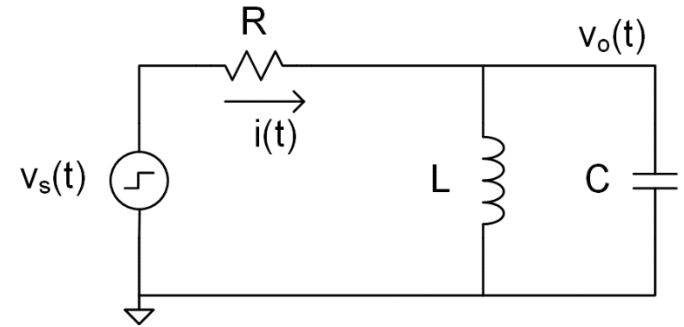Derive the governing differential equation for the following circuit.



32


Over-Damped Circuit Response

RLC Step Response – Example 1

33

- Determine $v_o(t)$
- Input is a unit voltage step

$$v_s(t) = 1V \cdot u(t)$$

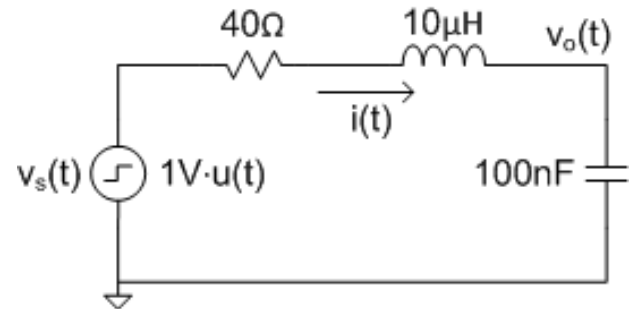

-
- First, apply KVL

$$v_s(t) - i(t)R - L \frac{di}{dt} - v_o(t) = 0$$

- Eliminate $i(t)$ using the i-v relationship for the capacitor

$$i(t) = C \frac{dv_o}{dt} \quad \text{and} \quad \frac{di}{dt} = C \frac{d^2v_o}{dt^2}$$

- This gives the second-order ODE in terms of $v_o(t)$, which can then be rearranged to standard form

$$v_s(t) - RC \frac{dv_o}{dt} - LC \frac{d^2v_o}{dt^2} - v_o(t) = 0 \quad \rightarrow \quad \frac{d^2v_o}{dt^2} + \frac{R}{L} \frac{dv_o}{dt} + \frac{1}{LC} v_o(t) = \frac{1}{LC} v_s(t)$$

RLC Step Response – Example 1

34

- Find the complementary solution, $v_{oc}(t)$
- The homogeneous equation

$$\frac{d^2 v_o}{dt^2} + \frac{R}{L} \frac{dv_o}{dt} + \frac{1}{LC} v_o(t) = 0$$

- The characteristic equation

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

- ▣ This can be rewritten as

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

where

$$\alpha = \frac{R}{2L} = \frac{40 \, \Omega}{2 \cdot 10 \, \mu H} = 2 \times 10^6 \frac{rad}{sec}$$

and

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10 \, \mu H \cdot 100 \, nF}} = 1 \times 10^6 \frac{rad}{sec}$$

RLC Step Response – Example 1

35

- The damping ratio is

$$\zeta = \frac{\alpha}{\omega_0} = \frac{2 \times 10^6}{1 \times 10^6} = 2$$

- ▣ $\zeta > 1$, so the circuit is over-damped

- Solution is of the form

$$v_{oc}(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

- s_1 and s_2 are the roots of the characteristic equation

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -268 \times 10^3 \frac{\text{rad}}{\text{sec}}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -3.73 \times 10^6 \frac{\text{rad}}{\text{sec}}$$

- The complementary solution is


$$v_{oc}(t) = K_1 e^{-268 \times 10^3 t} + K_2 e^{-3.73 \times 10^6 t}$$

RLC Step Response – Example 1

36

- The particular solution is the circuit's steady-state solution
- Steady-state equivalent circuit:
 - Capacitor → open
 - Inductor → short
- So, the **particular solution** is

$$v_{op}(t) = 1\text{ V}$$

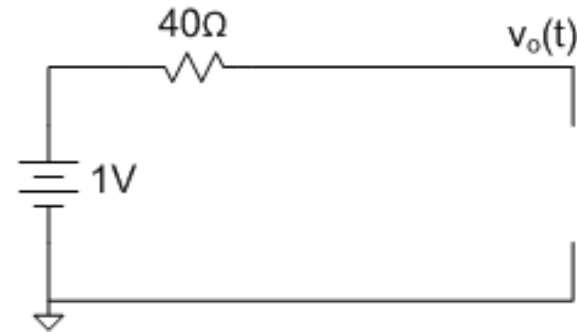

- The **general solution**:

$$v_o(t) = v_{oc}(t) + v_{op}(t)$$

$$v_o(t) = K_1 e^{-268 \times 10^3 t} + K_2 e^{-3.73 \times 10^6 t} + 1\text{ V}$$

- Next, we'll apply **initial conditions** to determine the unknown coefficients, K_1 and K_2

RLC Step Response – Example 1

37


□ Initial Conditions:

■ For $t < 0$

- $v_s(t < 0) = 0$
- $i(t < 0) = 0$
- $v_o(t < 0) = 0$

■ At $t = 0$

- $v_s(0) = 1\text{ V}$
- Capacitor voltage cannot change instantaneously
 - $v_o(0) = v_o(t < 0) = 0\text{ V}$
- Inductor current cannot change instantaneously
 - $i(0) = i(t < 0) = 0\text{ A}$
- And, current is related to the output voltage, so
 - $\left. \frac{dv_o}{dt} \right|_{t=0} = \dot{v}_o(0) = 0$

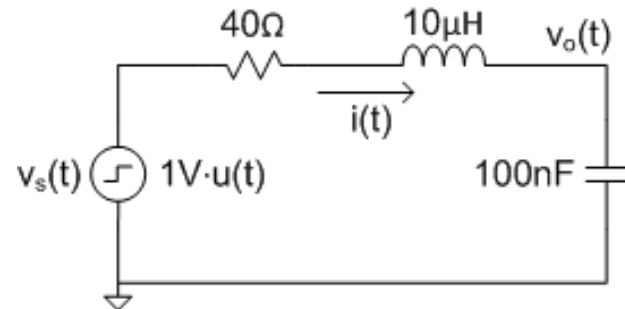


RLC Step Response – Example 1

38

- The two initial conditions are:

$$v_o(0) = 0 \quad (1)$$

$$\dot{v}_o(0) = 0 \quad (2)$$

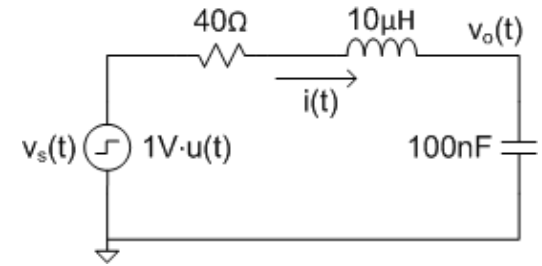

- Use the initial conditions to determine K_1 and K_2

- ▣ Applying the first initial condition

$$v_o(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t} + 1 V$$

$$v_o(0) = K_1 + K_2 + 1 V = 0$$

$$K_2 = -K_1 - 1 V \quad (3)$$

- ▣ Applying the second initial condition

$$\dot{v}_o(t) = s_1 K_1 e^{s_1 t} + s_2 K_2 e^{s_2 t}$$

$$\dot{v}_o(0) = s_1 K_1 + s_2 K_2 = 0 \quad (4)$$

RLC Step Response – Example 1

39

- Substituting (3) into (4)

$$s_1 K_1 - s_2 (K_1 + 1 \text{ V}) = 0$$

$$K_1 (s_1 - s_2) = s_2 \cdot 1 \text{ V}$$

$$K_1 = \frac{s_2}{s_1 - s_2} \cdot 1 \text{ V} = -1.08 \text{ V}$$


- Substituting the value of K_1 back into (3)

$$K_2 = -K_1 - 1 \text{ V} = 0.08 \text{ V}$$

- The step response for this over-damped RLC circuit is

$$v_o(t) = -1.08 \text{ V} \cdot e^{s_1 t} + 0.08 \text{ V} \cdot e^{s_2 t} + 1 \text{ V}$$

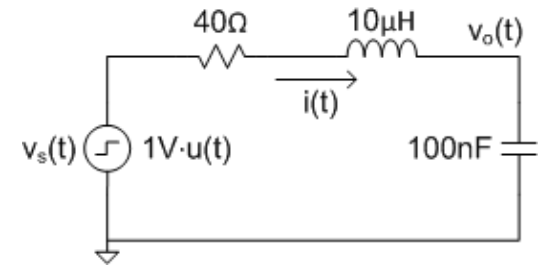
$$v_o(t) = -1.08 \text{ V} \cdot e^{-268 \times 10^3 t} + 0.08 \text{ V} \cdot e^{-3.73 \times 10^6 t} + 1 \text{ V}$$



RLC Step Response – Example 1

40
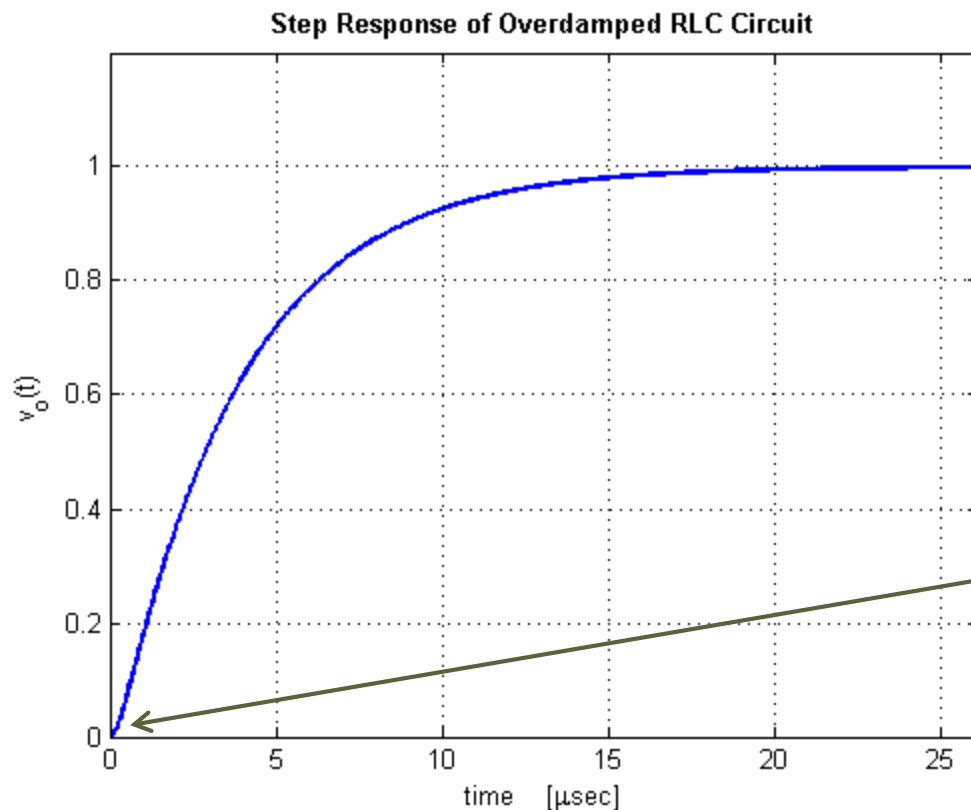
$$v_o(t) = -1.08 \text{ V} \cdot e^{-268 \times 10^3 t} + 0.08 \text{ V} \cdot e^{-3.73 \times 10^6 t} + 1 \text{ V}$$




- Similar to first-order response
 - ▣ Sum of *two* decaying exponentials
 - ▣ Monotonic increase to final value
- Initial slope differs from first-order response
 - ▣ Increases after $t = 0$

41

Critically-Damped Circuit Response

RLC Step Response – Example 2

42

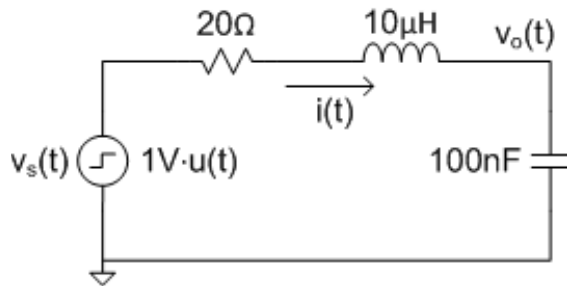

- Now consider the same circuit with decreased resistance
- To determine the form of the response, first determine the **damping ratio**, ζ

$$\zeta = \frac{\alpha}{\omega_0}$$

where

$$\alpha = \frac{R}{2L} = \frac{20\Omega}{2 \cdot 10\mu H} = 1 \times 10^6 \frac{rad}{sec}$$

and

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10\mu H \cdot 100nF}} = 1 \times 10^6 \frac{rad}{sec}$$

- The damping ratio is $\zeta = 1$, and the circuit is **critically-damped**
 - ▣ The **complementary solution** will be of the following form:

$$v_{oc}(t) = K_1 e^{s_{1,2}t} + K_2 t e^{s_{1,2}t}$$

RLC Step Response – Example 2

43

- The ***critically-damped*** circuit will have two real, identical poles

$$s_{1,2} = -\alpha = -1 \times 10^6 \frac{rad}{sec}$$

- The ***complementary solution*** is

$$v_{oc}(t) = K_1 e^{-1 \times 10^6 t} + K_2 t e^{-1 \times 10^6 t}$$

- The ***particular solution*** is still given by the steady-state response, and has not changed

$$v_{op}(t) = v_o(t \rightarrow \infty) = v_s(t > 0) = 1 \text{ V}$$

- The ***general solution*** is the sum of the complementary and particular solutions

$$v_o(t) = K_1 e^{-1 \times 10^6 t} + K_2 t e^{-1 \times 10^6 t} + 1 \text{ V}$$

RLC Step Response – Example 2

44

$$v_o(t) = K_1 e^{-1 \times 10^6 t} + K_2 t e^{-1 \times 10^6 t} + 1 \text{ V}$$

- Next, determine the unknown coefficients by applying initial conditions
 - ▣ Following the same reasoning as in the previous example, initial conditions are the same

$$v_o(0) = 0 \quad \text{and} \quad \dot{v}_o(0) = 0$$

- Applying the first initial condition

$$v_o(0) = K_1 + 1 \text{ V} = 0 \quad \rightarrow \quad K_1 = -1 \text{ V}$$

- Applying the second initial condition

$$\dot{v}_o(t) = K_1 s_{1,2} e^{s_{1,2} t} + K_2 (t s_{1,2} e^{s_{1,2} t} + e^{s_{1,2} t})$$

$$\dot{v}_o(0) = K_1 s_{1,2} + K_2 = 0 \quad \rightarrow \quad K_2 = -s_{1,2} K_1 = -1 \times 10^6 \text{ V}$$


- The step response of this critically-damped circuit:

$$v_o(t) = -e^{-1 \times 10^6 t} - 1 \times 10^6 t e^{-1 \times 10^6 t} + 1 \text{ V}$$

RLC Step Response – Example 2

45
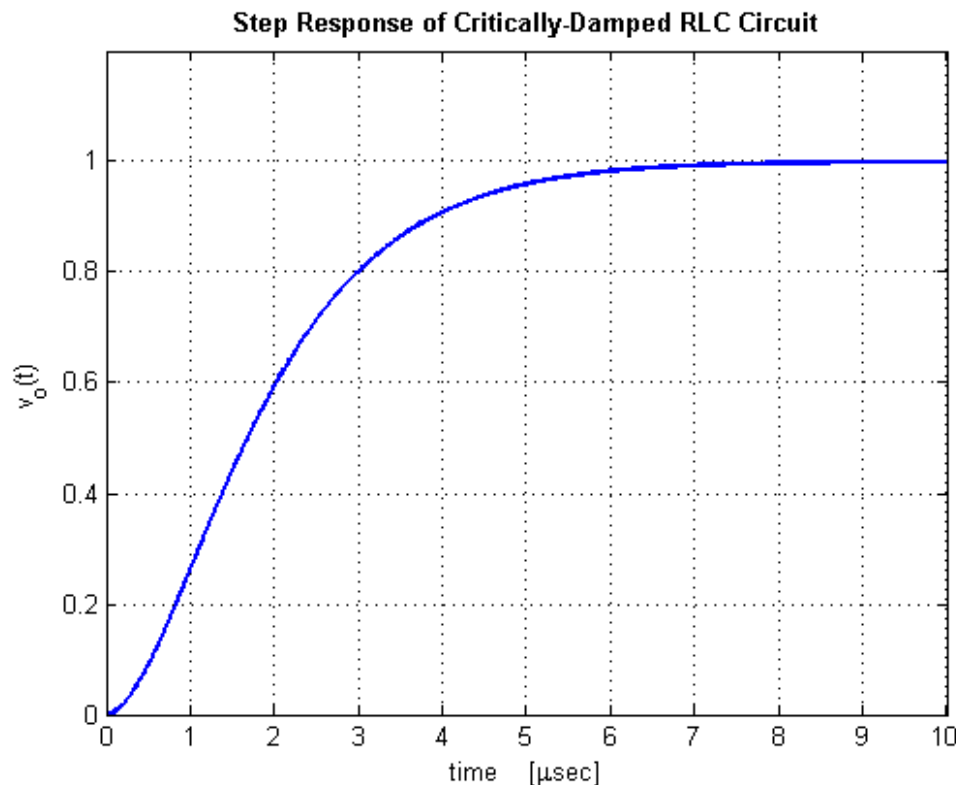
$$v_o(t) = -e^{-1 \times 10^6 t} - 1 \times 10^6 t e^{-1 \times 10^6 t} + 1 \text{ V}$$




- Similar to over-damped response
- Faster risetime
 - ▣ Dominant, slow pole replaced by higher-frequency double pole
- Again, increasing initial slope differs from first-order response
- Response never exceeds its final value

46

Under-Damped Circuit Response

RLC Step Response – Example 3

47

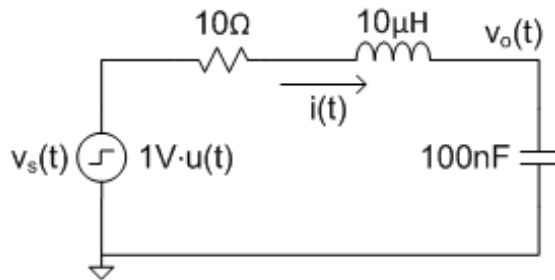

- Again decrease the resistance
- First, determine the **damping ratio**, ζ

$$\zeta = \frac{\alpha}{\omega_0}$$

where, now

$$\alpha = \frac{R}{2L} = \frac{10\Omega}{2 \cdot 10\mu H} = 500 \times 10^3 \frac{rad}{sec}$$

and

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10\mu H \cdot 100nF}} = 1 \times 10^6 \frac{rad}{sec}$$

- The damping ratio is $\zeta = 0.5$, and the circuit is **under-damped**
 - ▣ The **complementary solution** will be of the following form:

$$v_{oc}(t) = K_1 e^{-\alpha t} \cos(\omega_d t) + K_2 e^{-\alpha t} \sin(\omega_d t)$$

RLC Step Response – Example 3

48

$$v_{oc}(t) = K_1 e^{-\alpha t} \cos(\omega_d t) + K_2 e^{-\alpha t} \sin(\omega_d t)$$

- The **damped natural frequency** is

$$\omega_d = \omega_0 \sqrt{1 - \zeta^2} = \sqrt{\omega_0^2 - \alpha^2} = 866 \times 10^3 \frac{\text{rad}}{\text{sec}}$$

- The **complementary solution** is

$$v_{oc}(t) = K_1 e^{-500 \times 10^3 t} \cos(866 \times 10^3 t) + K_2 e^{-500 \times 10^3 t} \sin(866 \times 10^3 t)$$

- Once again, the **particular solution** is

$$v_{op}(t) = v_o(t \rightarrow \infty) = v_s(t > 0) = 1 \text{ V}$$

- The **general solution** is the sum of the complementary and particular solutions

$$v_o(t) = K_1 e^{-500 \times 10^3 t} \cos(866 \times 10^3 t) + K_2 e^{-500 \times 10^3 t} \sin(866 \times 10^3 t) + 1 \text{ V}$$

RLC Step Response – Example 3

49

$$v_o(t) = K_1 e^{-\alpha t} \cos(\omega_d t) + K_2 e^{-\alpha t} \sin(\omega_d t) + 1 \text{ V}$$

- Next, determine the unknown coefficients by applying initial conditions

$$v_o(0) = 0 \quad \text{and} \quad \dot{v}_o(0) = 0$$

- Applying the first initial condition

$$v_o(0) = K_1 + 1 \text{ V} = 0$$

$$K_1 = -1 \text{ V}$$

- Applying the second initial condition

$$\begin{aligned} \dot{v}_o(t) = & K_1 [-\omega_d e^{-\alpha t} \sin(\omega_d t) - \alpha e^{-\alpha t} \cos(\omega_d t)] \\ & + K_2 [\omega_d e^{-\alpha t} \cos(\omega_d t) - \alpha e^{-\alpha t} \sin(\omega_d t)] \end{aligned}$$

$$\dot{v}_o(0) = -K_1 \alpha + K_2 \omega_d = 0$$

$$K_2 = K_1 \frac{\alpha}{\omega_d} = -\frac{500 \times 10^3}{866 \times 10^3} = -0.58$$

RLC Step Response – Example 3

50


- The step response for this under-damped RLC circuit is

$$v_o(t) = -e^{-500 \times 10^3 t} \cos(866 \times 10^3 t) - 0.58e^{-500 \times 10^3 t} \sin(866 \times 10^3 t) + 1 \text{ V}$$

- Damped oscillatory components
 - Overshoot
 - Possible ringing
- Exponential damping
 - Oscillatory components decay to zero
 - Rate of decay determined by α , real part of poles

RLC Step Response – Example 3

51

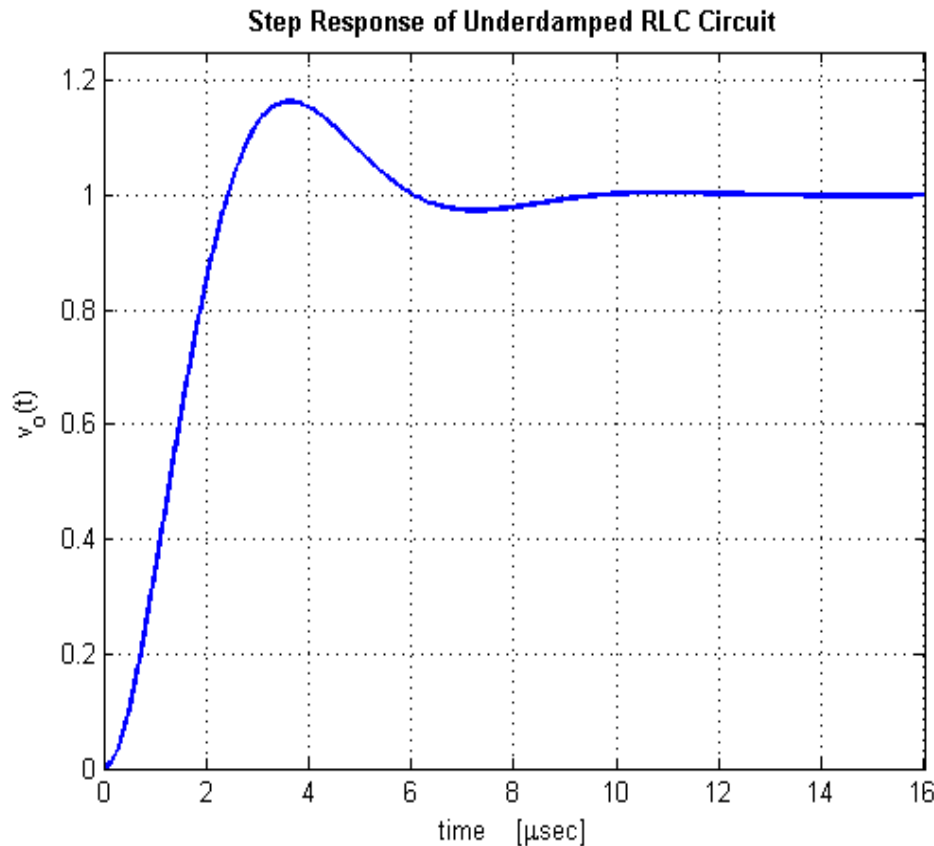

□ ***Overshoot***

- ▣ Response exceeds its final value

□ ***Ring***

- ▣ Response oscillate about its final value
- ▣ Not much ringing in this example

□ ***Damping ratio***

- ▣ Overshoot and ringing are inversely proportional to ζ

52

Step Response Characteristics


Step Response – Risetime

53

□ *Risetime*

- The time it takes a response to transition between two set levels
- Typically 10% and 90% of full swing
- Occasionally 20% and 80%
- Very rough approximation:

$$t_r \approx \frac{1.8}{\omega_0}$$

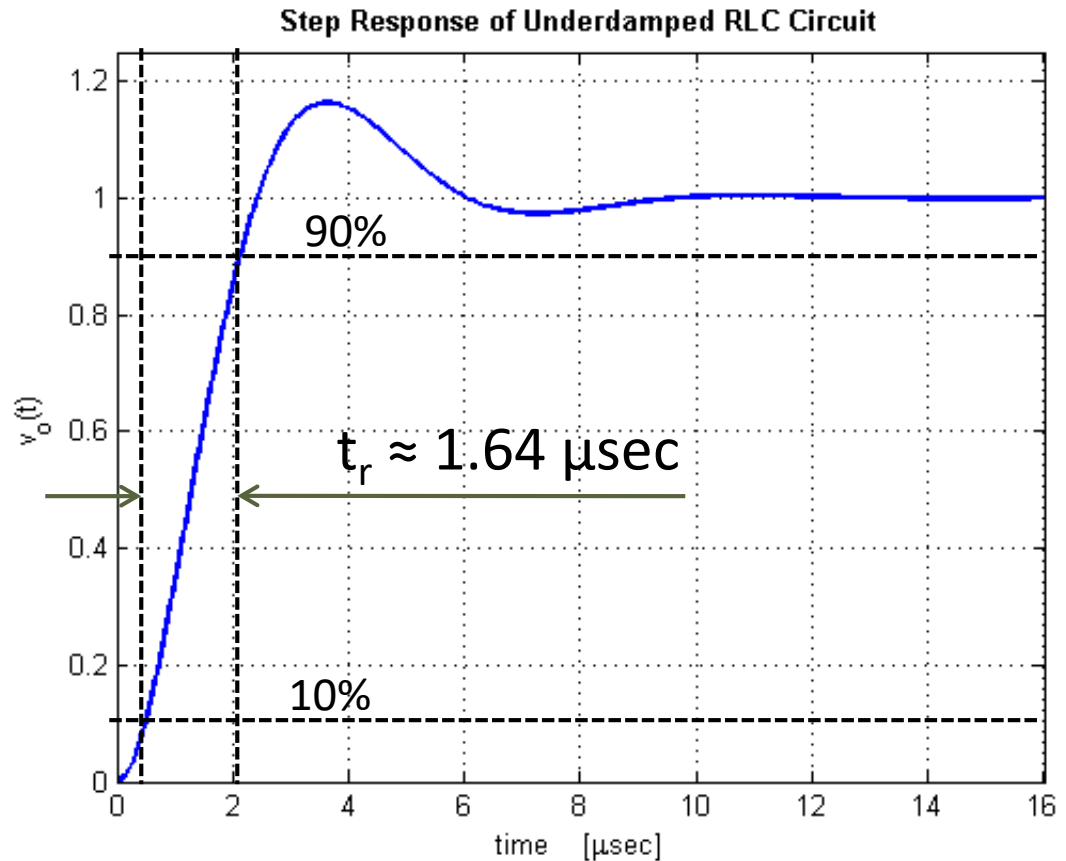


Step Response – Overshoot

54

□ **Overshoot**

- Response's excursion beyond its final value
- Expressed as a percentage of the full-scale swing
- Inversely proportional to damping ratio

ζ	%OS
0.45	20
0.5	16
0.6	10
0.7	5

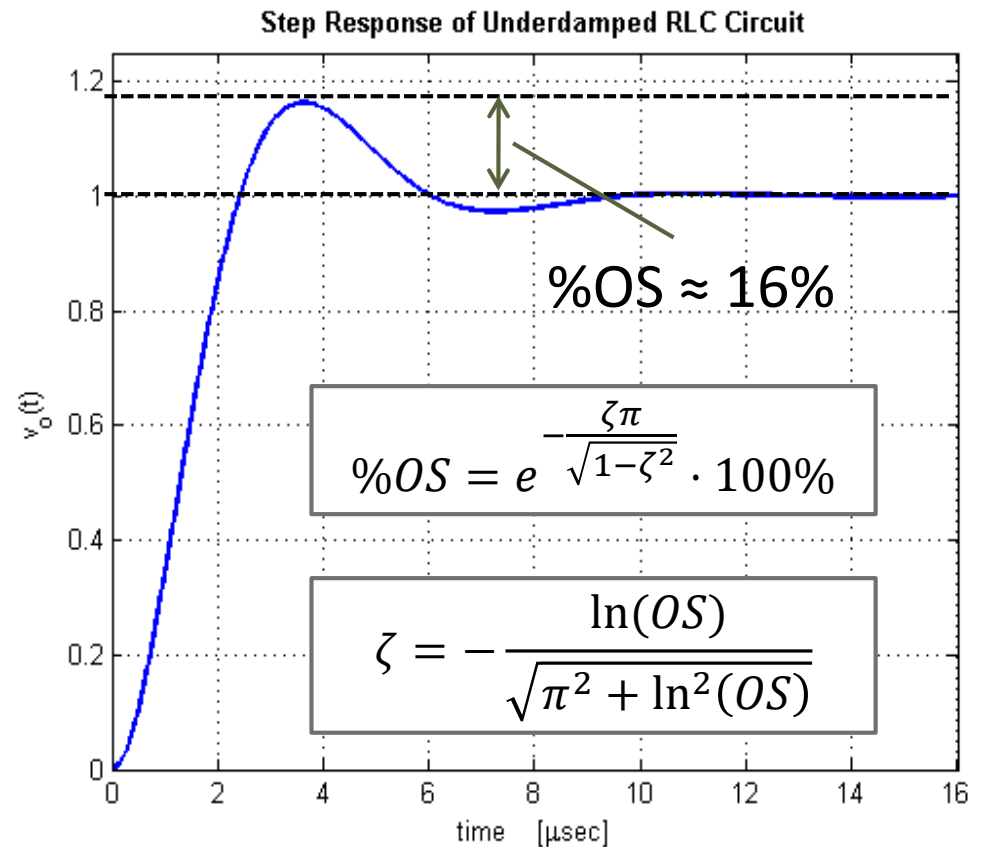


Step Response – Settling Time

55

□ *Settling time*

- The time it takes a response to settle (finally) to within some percentage of the final value
- Typically $\pm 1\%$, $\pm 2\%$, or $\pm 5\%$
- Inversely proportional to the real part of the circuit's poles (roots of the characteristic equation)
- For $\pm 1\%$ settling time:
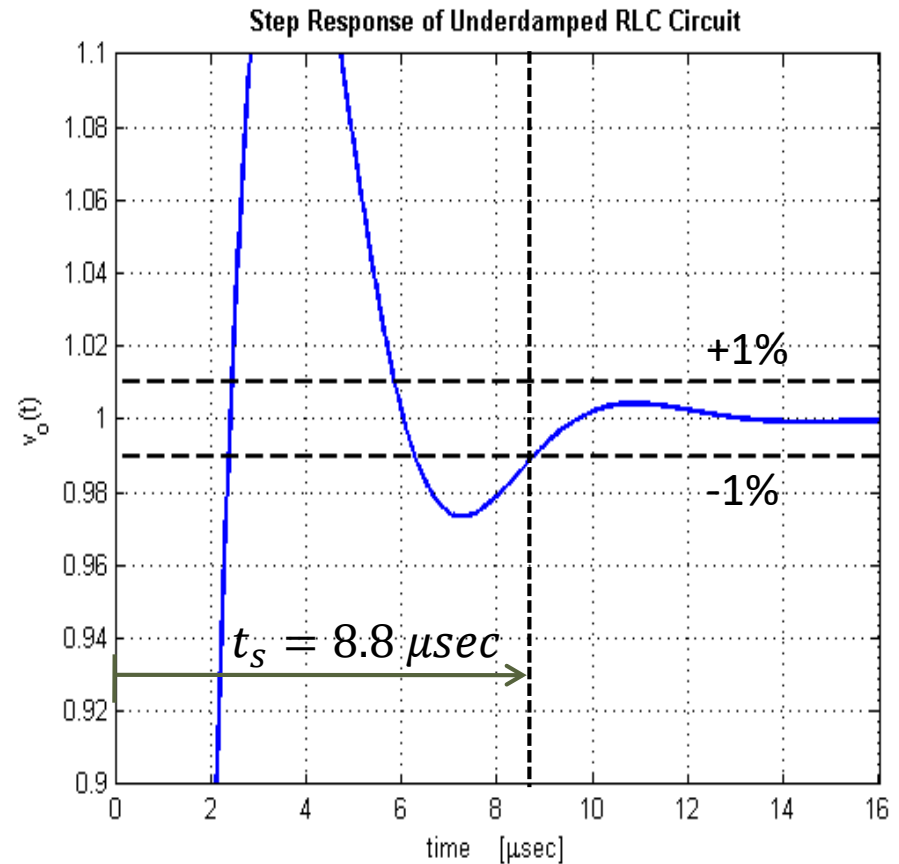
$$t_s \approx \frac{4.6}{\alpha} = \frac{4.6}{\zeta \omega_0}$$





56

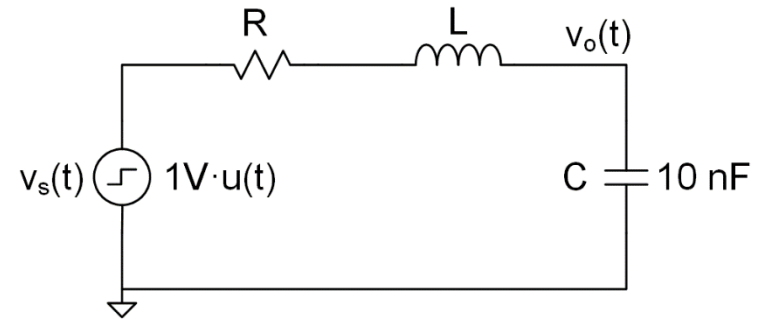
Example Problems


Determine:


- ▣ R and L, such that
 - $O.S. = 10\%$
 - $t_s \approx 2\mu\text{sec}$ ($\pm 1\%$)
- ▣ System poles
- ▣ $v_o(t)$ for $t \geq 0$




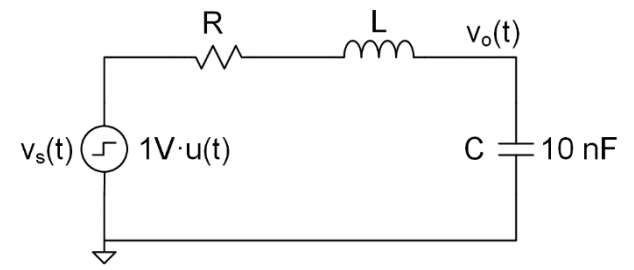

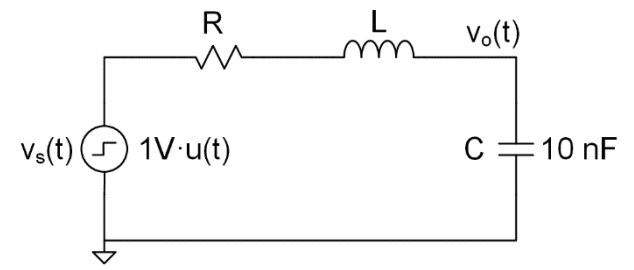

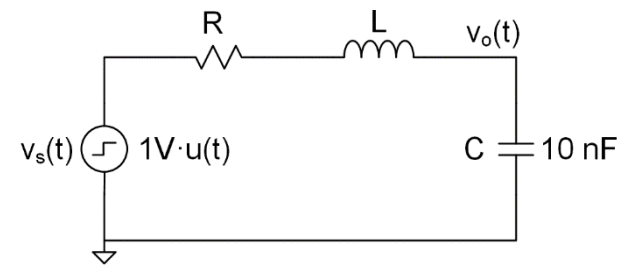

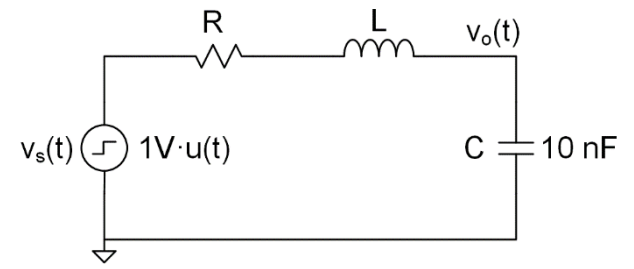

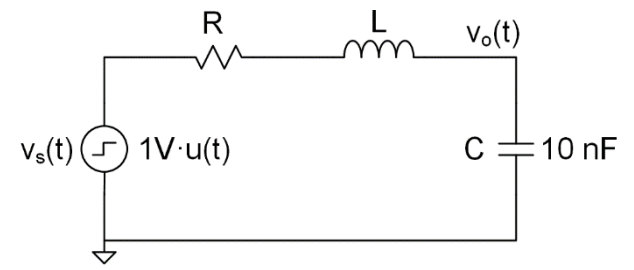

Determine the minimum resistance for 0% overshoot.

