

SECTION 6: AC POWER FUNDAMENTALS

ENGR 202 – Electrical Fundamentals II

2

Instantaneous Power

Instantaneous Power

3

□ Instantaneous power:


- Power supplied by a source or absorbed by a load or network element as a function of time

$$p(t) = v(t) \cdot i(t)$$

- The nature of this instantaneous power flow is determined by the impedance of the load
- Next, we'll look at the instantaneous power delivered to loads of different impedances
- Instantaneous power is a useful place to start our discussion of power, but is not how we typically characterize power

Instantaneous Power – Resistive Load

4

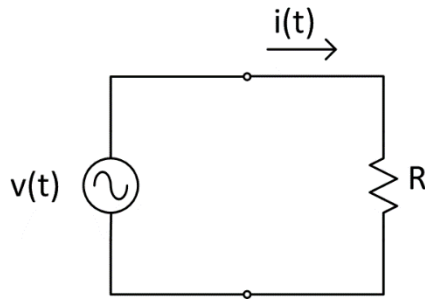

- The voltage across the resistive load is

$$v(t) = V_p \cos(\omega t + \delta)$$

- Current through the resistor is

$$i(t) = \frac{V_p}{R} \cos(\omega t + \delta)$$

- The instantaneous power absorbed by the resistor is

$$p_R(t) = v(t) \cdot i(t) = V_p \cos(\omega t + \delta) \cdot \frac{V_p}{R} \cos(\omega t + \delta)$$

$$p_R(t) = \frac{V_p^2}{R} \cos^2(\omega t + \delta) = \frac{V_p^2}{R} \frac{1}{2} [1 + \cos(2\omega t + 2\delta)]$$

Instantaneous Power – Resistive Load

5

$$p_R(t) = \frac{V_p^2}{2R} [1 + \cos(2\omega t + 2\delta)]$$

- Making use of the rms voltage

$$p_R(t) = \frac{(\sqrt{2} V_{rms})^2}{2R} [1 + \cos(2\omega t + 2\delta)]$$


$$p_R(t) = \frac{V_{rms}^2}{R} [1 + \cos(2\omega t + 2\delta)]$$

- The instantaneous power absorbed by the resistor has a non-zero average value and a double-frequency component

Instantaneous Power – Resistive Load

6

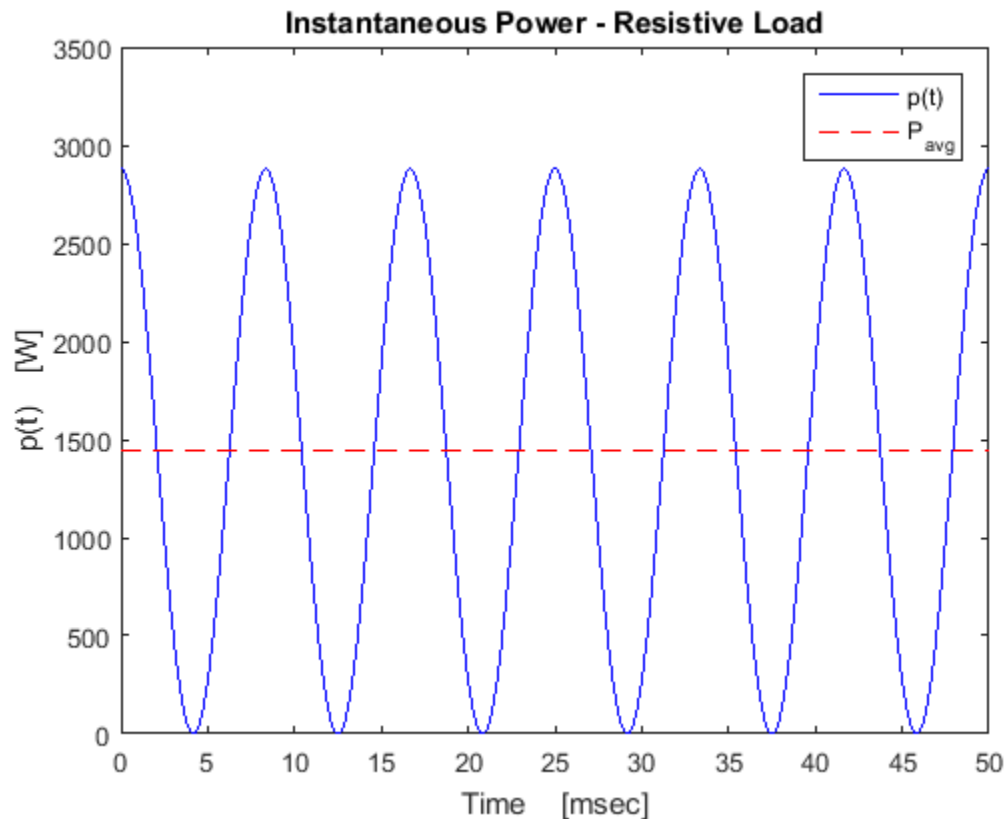- Power delivered to the resistive load has a non-zero average value and a double-frequency component



Instantaneous Power – Capacitive Load

7

- Now consider the power absorbed by a purely capacitive load

- ▣ Again, $v(t) = V_p \cos(\omega t + \delta)$

- The current flowing to the load is

$$i(t) = I_p \cos(\omega t + \delta + 90^\circ)$$


where

$$I_p = \frac{V_p}{X_C} = \frac{V_p}{1/\omega C} = \omega C V_p$$

- The instantaneous power delivered to the capacitive load is

$$p_C(t) = v(t) \cdot i(t)$$
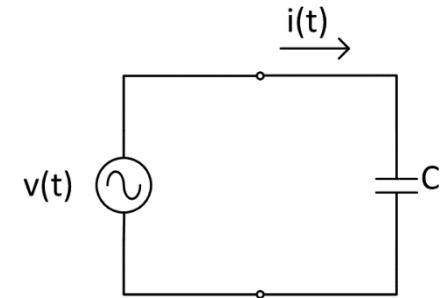
$$p_C(t) = V_p \cos(\omega t + \delta) \cdot \omega C V_p \cos(\omega t + \delta + 90^\circ)$$



Instantaneous Power – Capacitive Load

8


$$p_C(t) = \omega C V_p^2 \frac{1}{2} [\cos(-90^\circ) + \cos(2\omega t + 2\delta + 90^\circ)]$$

$$p_C(t) = \omega C \frac{V_p^2}{2} \cdot \cos(2\omega t + 2\delta + 90^\circ)$$

- In terms of rms voltage

$$p_C(t) = \omega C V_{rms}^2 \cdot \cos(2\omega t + 2\delta + 90^\circ)$$

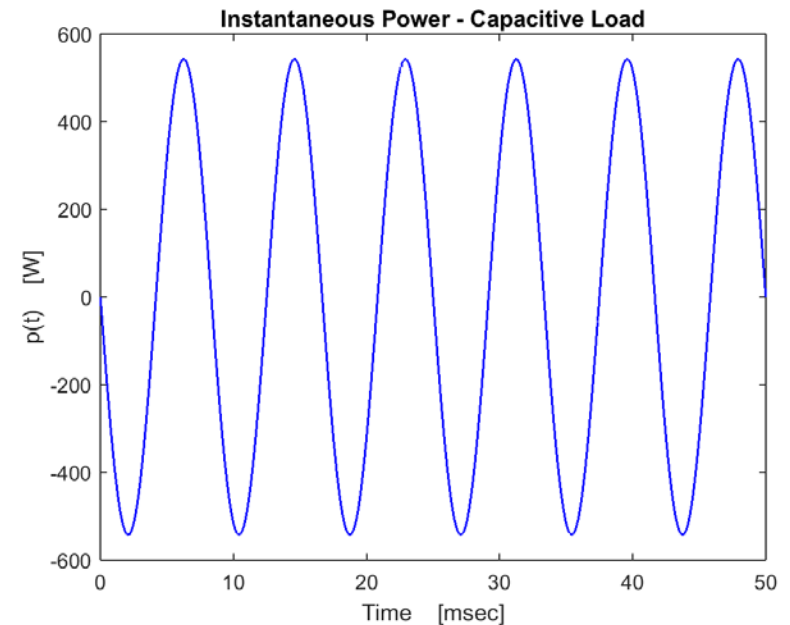- This is a double frequency sinusoid, but, unlike for the resistive load, the average value is zero



Instantaneous Power – Inductive Load


9

- Now consider the power absorbed by a purely inductive load
- Now the load current *lags* by 90°

$$i(t) = I_p \cos(\omega t + \delta - 90^\circ)$$

where
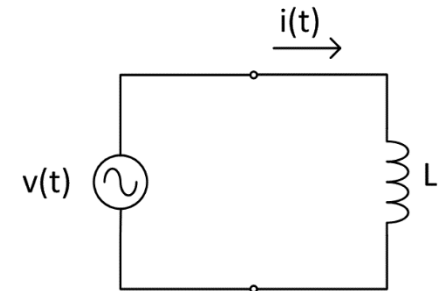
$$I_p = \frac{V_p}{X_L} = \frac{V_p}{\omega L}$$



- The instantaneous power delivered to the inductive load is

$$p_L(t) = v(t) \cdot i(t)$$

$$p_L(t) = V_p \cos(\omega t + \delta) \cdot \frac{V_p}{\omega L} \cos(\omega t + \delta - 90^\circ)$$

Instantaneous Power – Inductive Load

10


$$p_L(t) = \frac{V_p^2}{\omega L} \frac{1}{2} [\cos(90^\circ) + \cos(2\omega t + 2\delta - 90^\circ)]$$

$$p_L(t) = \frac{V_p^2}{2\omega L} \cdot \cos(2\omega t + 2\delta - 90^\circ)$$

- In terms of rms voltage

$$p_L(t) = \frac{V_{rms}^2}{\omega L} \cdot \cos(2\omega t + 2\delta - 90^\circ)$$

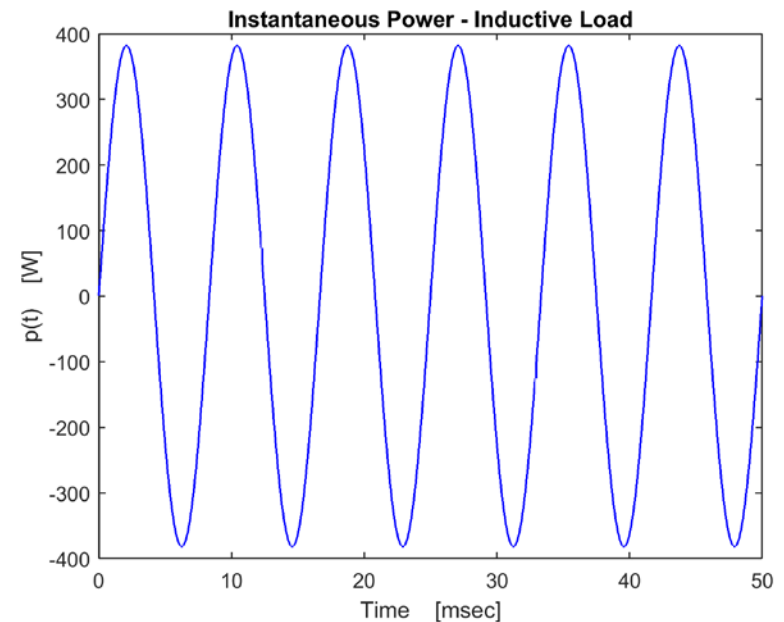- As for the capacitive load, this is a double frequency sinusoid with an average value of zero



Instantaneous Power – General Impedance

11

- Finally, consider the instantaneous power absorbed by a general RLC load
- Phase angle of the current is determined by the angle of the impedance


$$i(t) = I_p \cos(\omega t + \beta)$$

- The instantaneous power is

$$p(t) = V_p \cos(\omega t + \delta) \cdot I_p \cos(\omega t + \beta)$$

$$p(t) = \frac{V_p I_p}{2} [\cos(\delta - \beta) + \cos(2\omega t + \delta + \beta)]$$
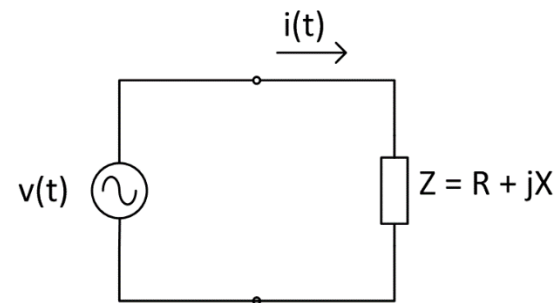
$$p(t) = V_{rms} I_{rms} [\cos(\delta - \beta) + \cos(2\omega t + 2\delta - (\delta - \beta))]$$



Instantaneous Power – General Impedance

12

- Using the following trig identity

$$\cos(A - B) = \cos(A) \cos(B) + \sin(A) \sin(B)$$

we get

$$p(t) = V_{rms} I_{rms} [\cos(\delta - \beta) + \cos(\delta - \beta) \cos(2\omega t + 2\delta) + \sin(\delta - \beta) \sin(2\omega t + 2\delta)]$$

and

$$p(t) = V_{rms} I_{rms} \cos(\delta - \beta) [1 + \cos(2\omega t + 2\delta)] + V_{rms} I_{rms} \sin(\delta - \beta) \sin(2\omega t + 2\delta)$$

Instantaneous Power – General Impedance

13

- Letting

$$I_R = I_{rms} \cos(\delta - \beta) \quad \text{and} \quad I_X = I_{rms} \sin(\delta - \beta)$$

we have

$$p(t) = V_{rms} I_R [1 + \cos(2\omega t + 2\delta)] \\ + V_{rms} I_X \sin(2\omega t + 2\delta)$$

- There are two components to the power:

$$p_R(t) = V_{rms} I_R [1 + \cos(2\omega t + 2\delta)]$$

is the power absorbed by the resistive component of the load, and

$$p_X(t) = V_{rms} I_X \sin(2\omega t + 2\delta)$$

is the power absorbed by the reactive component of the load

14

Real & Reactive Power

Real Power

15

- According to previous expressions, power delivered to a resistance has a non-zero average value
 - ▣ Purely resistive load or a load with a resistive component

- This is ***real power, average power, or active power***

$$P = V_{rms} I_R$$

$$P = V_{rms} I_{rms} \cos(\delta - \beta)$$

- Real power has units of ***watts*** (W)
- Real power is power that results in work (or heat dissipation)

Power Factor

16

- The phase angle ($\delta - \beta$) represents the phase difference between the voltage and the current
 - ▣ This is the **power factor angle**
 - ▣ The angle of the load impedance
- Note that the *real power* is a function of the *cosine of the power factor angle*

$$P = V_{rms} I_{rms} \cos(\delta - \beta)$$

- This is the **power factor**

$$p.f. = \cos(\delta - \beta)$$

- For a purely resistive load, voltage and current are in phase

$$p.f. = \cos(\delta - \beta) = \cos(0^\circ) = 1$$

$$P = V_{rms} I_{rms}$$

Power Factor

17

- For a purely capacitive load, current leads the voltage by 90°

$$p.f. = \cos(\delta - \beta) = \cos(-90^\circ) = 0$$

$$P = 0$$

- This is referred to as a **leading power factor**
- Power factor is *leading* for loads with *capacitive* reactance
- For a purely inductive load, current lags the voltage by 90°

$$p.f. = \cos(\delta - \beta) = \cos(90^\circ) = 0$$

$$P = 0$$

- Loads with inductive reactance have *lagging* power factors
- Note that power factor is defined to always be **positive**

$$0 \leq p.f. \leq 1$$

Reactive Power

18

- The other part of instantaneous power is the power delivered to the reactive component of the load

$$p_X(t) = V_{rms}I_{rms} \sin(\delta - \beta) \sin(2\omega t + 2\delta)$$

- Unlike real power, this component of power has zero average value
- The *amplitude* is the **reactive power**

$$Q = V_{rms}I_{rms} \sin(\delta - \beta) \text{ var}$$

- Units are **volts-amperes reactive**, or **var**
- Power that flows to and from the load reactance
 - ▣ Does not result in work or heat dissipation

RMS Phasors

19

□ Up to this point:

▣ Phasor magnitude has been ***peak amplitude***

$$v(t) = V_p \sin(\omega t + \phi) \leftrightarrow \mathbf{V} = V_p e^{j\phi} = V_p \angle \phi$$

□ For ***AC power systems***:

▣ Phasor magnitude is the ***RMS value***

$$v(t) = \sqrt{2} \cdot V_{rms} \sin(\omega t + \phi) \leftrightarrow \mathbf{V} = V_{rms} e^{j\phi} = V_{rms} \angle \phi$$

▣ Simplifies calculation of AC power quantities

20

Complex Power

Complex Power

21

- **Complex power** is defined as the product of the rms voltage phasor and *conjugate* rms current phasor

$$\mathbf{S} = \mathbf{V}\mathbf{I}^*$$

where the voltage has phase angle δ

$$\mathbf{V} = V_{rms} \angle \delta$$

and the current has phase angle β

$$\mathbf{I} = I_{rms} \angle \beta \quad \rightarrow \quad \mathbf{I}^* = I_{rms} \angle -\beta$$

- The complex power is

$$\mathbf{S} = \mathbf{V}\mathbf{I}^* = (V_{rms} \angle \delta)(I_{rms} \angle -\beta)$$

$$\mathbf{S} = V_{rms} I_{rms} \angle (\delta - \beta)$$

Complex Power

22

- Complex power has units of ***volts-amperes*** (VA)
- The *magnitude* of complex power is ***apparent power***

$$S = V_{rms} I_{rms} \text{ VA}$$

- Apparent power also has units of volts-amperes
- Complex power is the vector sum of real power (in phase with V) and reactive power ($\pm 90^\circ$ out of phase with V)

$$S = P + jQ$$

Complex Power

23

- **Real power** can be expressed in terms of complex power

$$P = \operatorname{Re}\{\mathbf{S}\}$$

or in terms of **apparent power**

$$P = S \cdot \cos(\delta - \beta) = S \cdot p.f.$$

- Similarly, **reactive power**, is the imaginary part of complex power

$$Q = \operatorname{Im}\{\mathbf{S}\}$$

and can also be related to **apparent power**

$$Q = S \cdot \sin(\delta - \beta)$$


- And, **power factor** is the **ratio** between **real power** and **apparent power**

$$p.f. = \cos(\delta - \beta) = \frac{P}{S}$$

Power Convention – Load Convention

24

- Applying a consistent sign convention allows us to easily determine whether network elements supply or absorb real and reactive power
- **Passive sign convention** or **load convention**
 - Positive current defined to enter the positive voltage terminal of an element
- If $P > 0$ or $Q > 0$, then real or reactive power is **absorbed** by the element
- If $P < 0$ or $Q < 0$, then real or reactive power is **supplied** by the element

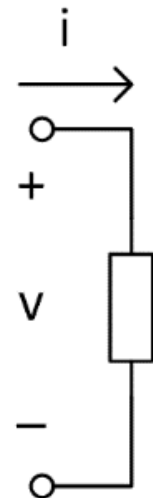

Power Absorbed by Passive Elements

25

- Complex power absorbed by a **resistor**

$$\mathbf{S}_R = \mathbf{V}\mathbf{I}_R^* = (V\angle\delta) \left(\frac{V}{R} \angle -\delta \right)$$

$$\mathbf{S}_R = \frac{V^2}{R}$$

- Positive and purely real
 - Resistors **absorb real** power
 - **Reactive** power is **zero**
- Complex power absorbed by a **capacitor**

$$\mathbf{S}_C = \mathbf{V}\mathbf{I}_C^* = (V\angle\delta)(-j\omega CV\angle -\delta)$$

$$\mathbf{S}_C = -j\omega CV^2$$

- Negative and purely imaginary
 - Capacitors **supply reactive** power
 - **Real** power is **zero**

Power Absorbed by Passive Elements

26

- Complex power absorbed by an **inductor**

$$\mathbf{S}_L = \mathbf{V}\mathbf{I}_L^* = (V\angle\delta) \left(\frac{V}{-j\omega L} \angle -\delta \right)$$

$$\mathbf{S}_L = j \frac{V^2}{\omega L}$$


- Positive and purely imaginary
 - Inductors **absorb reactive** power
 - **Real** power is **zero**
-
- In summary:
 - Resistors absorb real power, zero reactive power
 - Capacitors supply reactive power, zero real power
 - Inductors absorb reactive power, zero real power


27

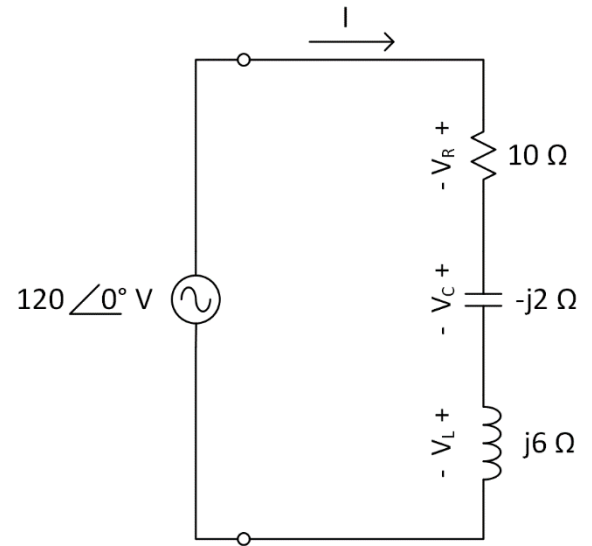
Example Problems


Determine:


- ❑ Complex, real, and reactive power delivered to the load
- ❑ Voltage across each element
- ❑ Power associated with each element
- ❑ Power factor




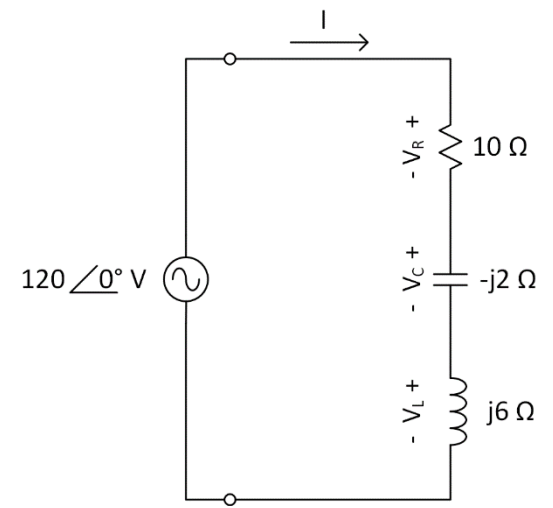


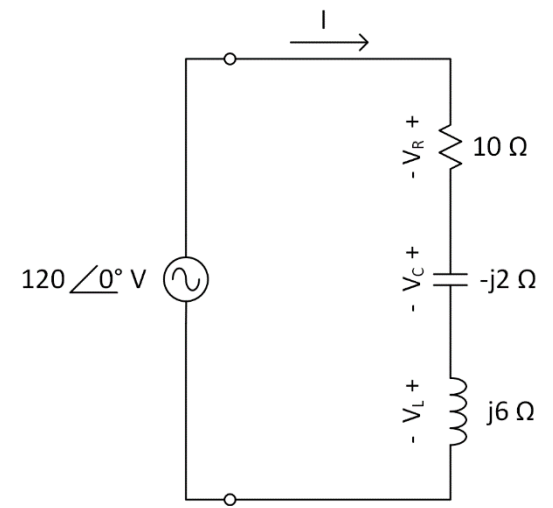

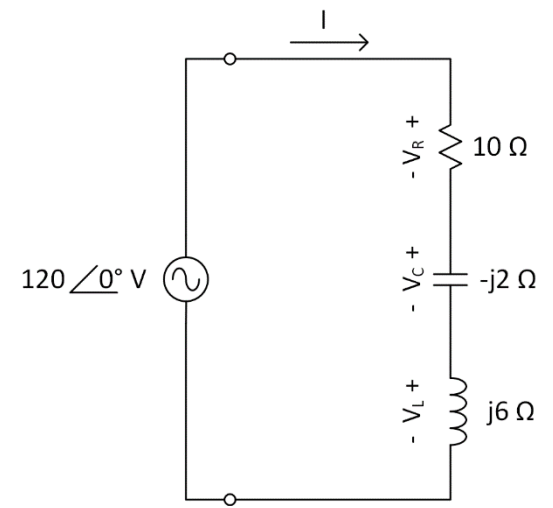

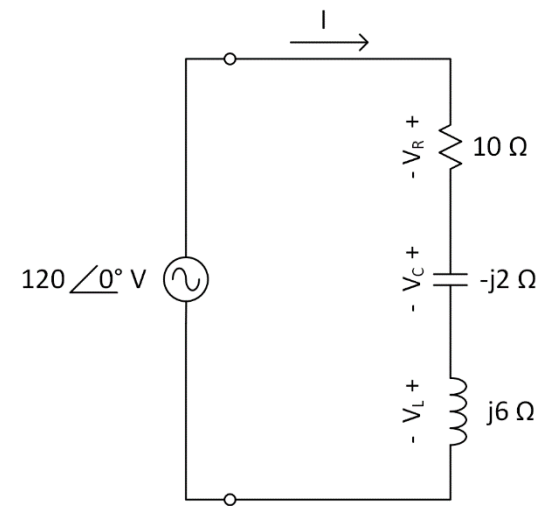

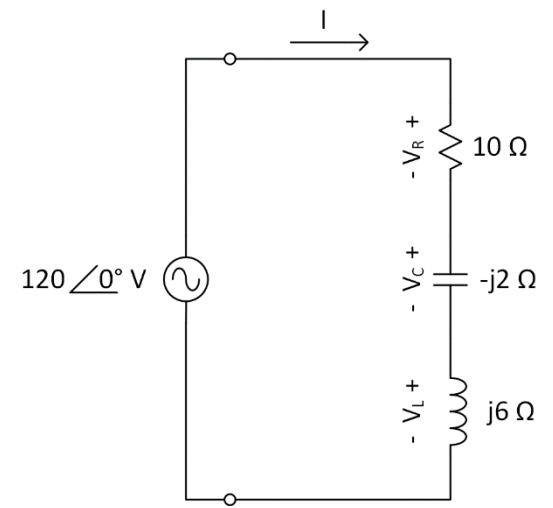

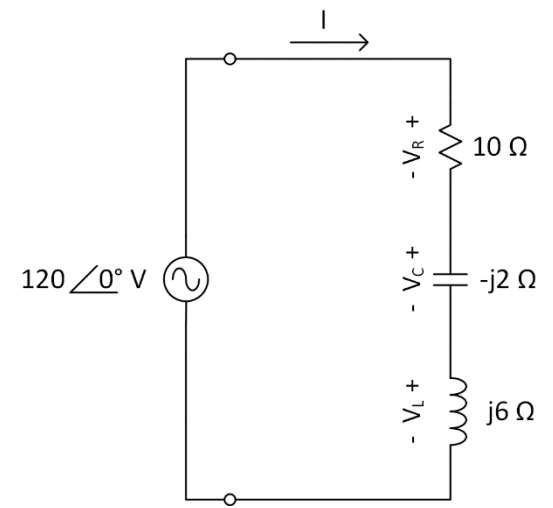

35

Power Triangle


Power Triangle

36

- Complex power is the vector sum of real power (in phase with V) and reactive power ($\pm 90^\circ$ out of phase with V)


$$S = P + jQ$$

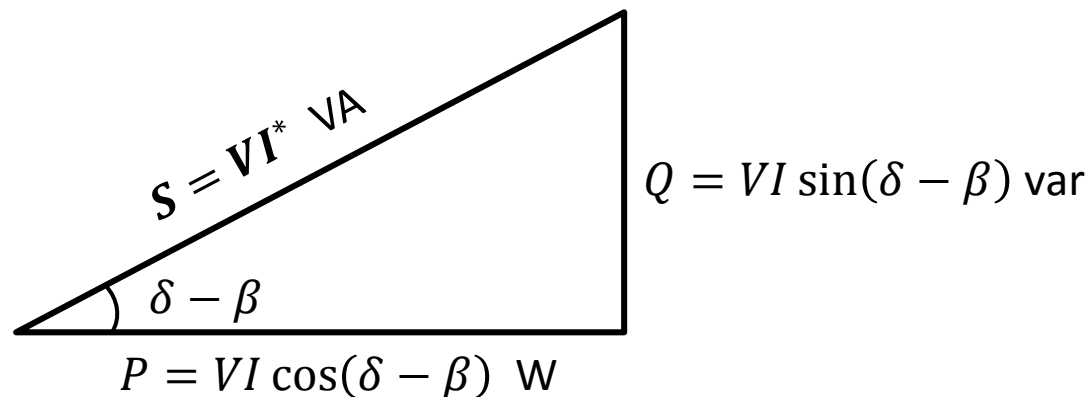- Complex, real, and reactive powers can be represented graphically, as a **power triangle**



Power Triangle

37

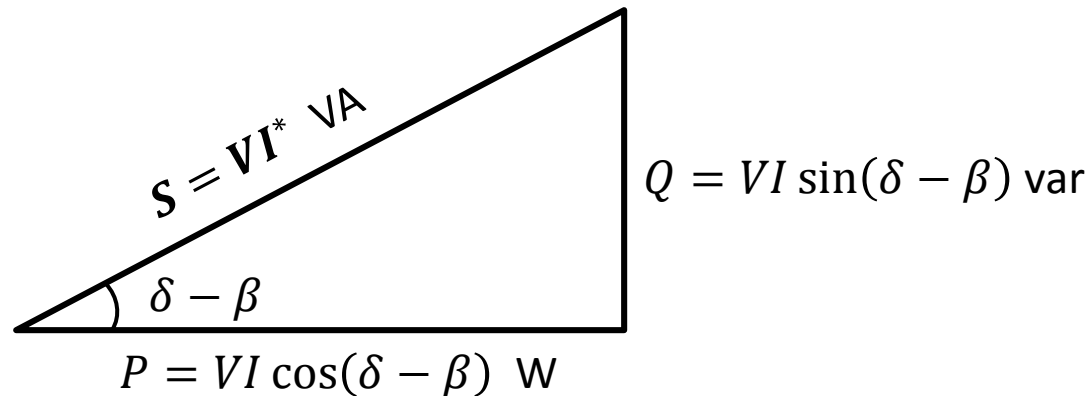


- Quickly and graphically provides power information
 - ▣ **Power factor** and power factor angle
 - ▣ **Leading** or **lagging** power factor
 - ▣ Reactive nature of the load – **capacitive** or **inductive**

Lagging Power Factor

38

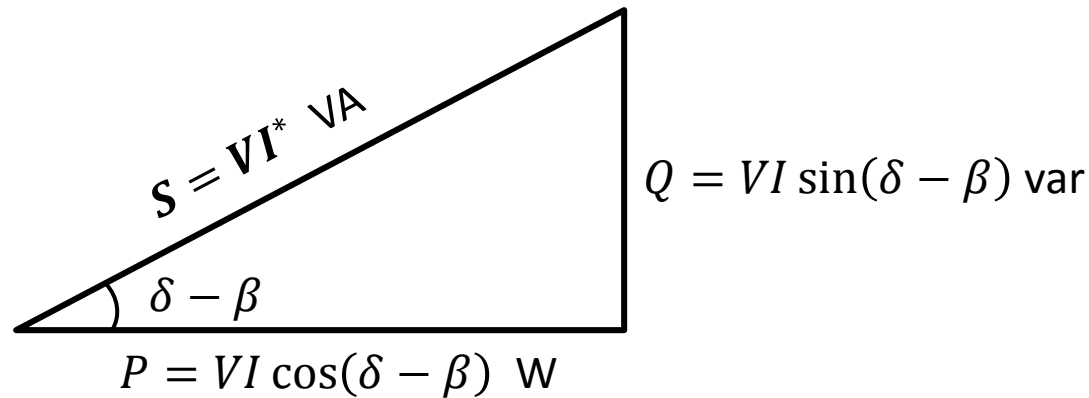- For loads with **inductive** reactance
 - Impedance angle is positive
 - Power factor angle is positive
 - Power factor is **lagging**




- Q is positive
 - The load **absorbs** reactive power

Leading Power Factor

39

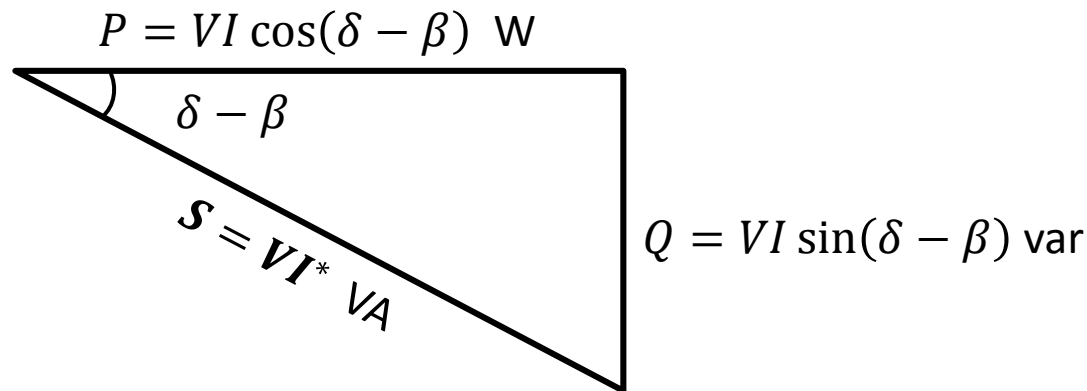- For loads with **capacitive** reactance
 - Impedance angle is negative
 - Power factor angle is negative
 - Power factor is **leading**



- Q is negative
 - The load **supplies** reactive power

40

Power Factor Correction

Power Factor Correction


41

- The overall goal of power distribution is to supply power to do work
 - ▣ *Real* power
- Reactive power does not perform work, but
 - ▣ Must be supplied by the source
 - ▣ Still flows over the lines
- For a given amount of real power consumed by a load, we'd like to
 - ▣ Reduce reactive power, Q
 - ▣ Reduce S relative to P , that is
 - ▣ Reduce the p.f. angle, and
 - ▣ Increase the p.f.
- ***Power factor correction***

Power Factor Correction – Example

42

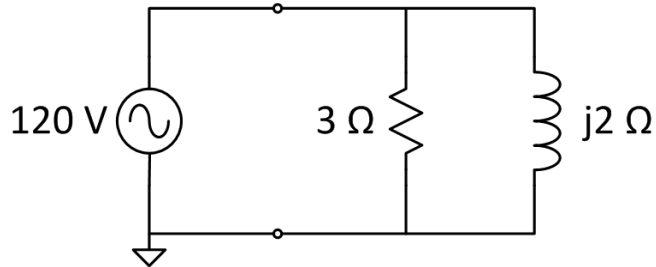- Consider a source driving an inductive load



- Determine:
 - ▣ Real power absorbed by the load
 - ▣ Reactive power absorbed by the load
 - ▣ p.f. angle and p.f.
- Draw the power triangle

- Current through the resistance is

$$I_R = \frac{120 V}{3 \Omega} = 40 A$$

- Current through the inductance is

$$I_L = \frac{120 V}{j2 \Omega} = 60 \angle -90^\circ A$$

- The total load current is

$$I = I_R + I_L = (40 - j60)A = 72.1 \angle -56.3^\circ A$$

Power Factor Correction – Example

43

- The power factor angle is

$$\theta = (\delta - \beta) = 0^\circ - (-56.3^\circ)$$

$$\theta = 56.3^\circ$$

- The power factor is

$$p.f. = \cos(\theta) = \cos(56.3^\circ)$$

$$p.f. = 0.55 \text{ lagging}$$

- Real power absorbed by the load is

$$P = VI \cos(\theta) = 120 \text{ V} \cdot 72.1 \text{ A} \cdot 0.55$$

$$P = 4.8 \text{ kW}$$

- Alternatively, recognizing that real power is power absorbed by the resistance

$$P = VI_R = 120 \text{ V} \cdot 40 \text{ A} = 4.8 \text{ kW}$$

Power Factor Correction – Example

44

- Reactive power absorbed by the load is

$$Q = VI \sin(\theta) = 120 V \cdot 72.1 A \cdot 0.832$$

$$Q = 7.2 \text{ kvar}$$

- This is also the power absorbed by the load inductance

$$Q = VI_L = 120 V \cdot 60 A = 7.2 \text{ kvar}$$

- Apparent power is

$$S = VI = 120 V \cdot 72.1 A = 8.65 \text{ kVA}$$

- Or, alternatively


$$S = \sqrt{P^2 + Q^2}$$

$$S = \sqrt{(4.8 \text{ kW})^2 + (7.2 \text{ kvar})^2} = 8.65 \text{ kVA}$$

Power Factor Correction – Example

45

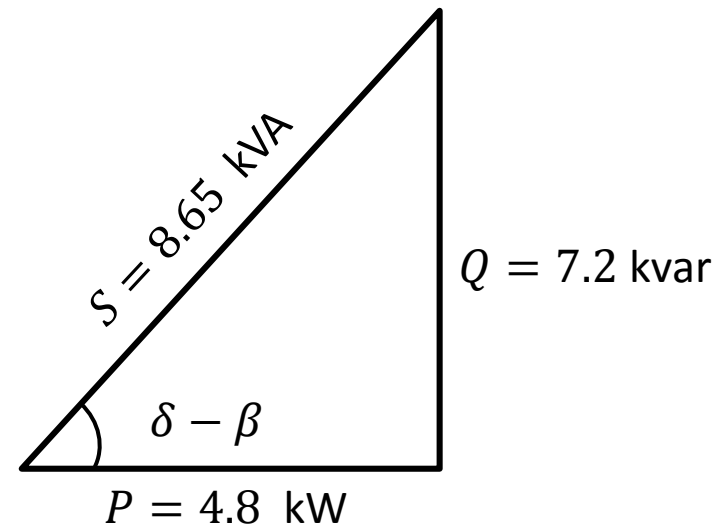- The ***power triangle***:
- Here, the source is supplying 4.8 kW at a power factor of 0.55 lagging
- Let's say we want to reduce the apparent power supplied by the source
 - Deliver 4.8 kW at a p.f. of 0.9 lagging
- Add ***power factor correction***
- Add capacitors to *supply* reactive power




Power Factor Correction – Example

46

- For $p.f. = 0.9$, we need a power factor angle of
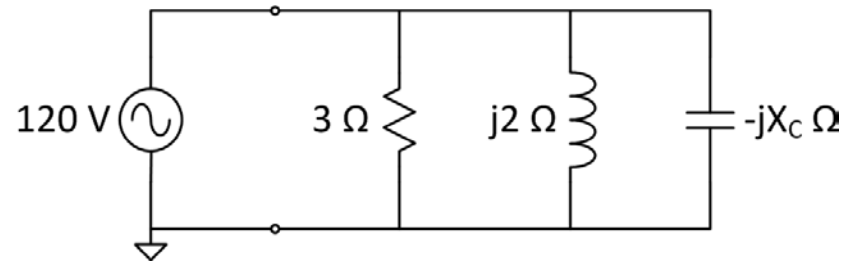
$$\theta' = \cos^{-1}(0.9) = 25.8^\circ$$



- This corresponds to a reactive power of

$$Q' = P \tan(\theta') = 4.8 \text{ kW} \cdot \tan(25.8^\circ)$$

$$Q' = 2.32 \text{ kvar}$$

- This means that the required reactive power absorbed (negative, so it is supplied) by the capacitors is

$$Q_C = 2.32 \text{ kvar} - 7.2 \text{ kvar} = -4.88 \text{ kvar}$$

Power Factor Correction – Example

47


- Reactive power absorbed by the capacitor is

$$Q_C = \frac{V^2}{X_C}$$

- So the required capacitive reactance is

$$X_C = \frac{V^2}{Q_C} = \frac{(120 \text{ V})^2}{-4.88 \text{ kvar}} = -2.95 \Omega$$

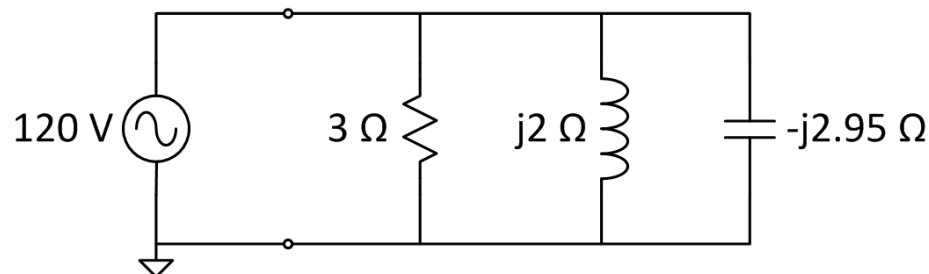- The addition of $-j2.95 \Omega$ provides the desired power factor correction



Power Factor Correction – Example

48

- Before power factor correction, current supplied to the load was

$$\mathbf{I} = 72.1 \angle -56.3^\circ \text{ A}$$

- Current through the added capacitor:

$$\mathbf{I}_C = \frac{\mathbf{V}}{Z_C} = \frac{120 \angle 0^\circ}{-j2.95 \Omega} = 40.7 \angle 90^\circ \text{ A}$$

- After power factor correction, current to the load is

$$\mathbf{I} = \mathbf{I}_R + \mathbf{I}_L + \mathbf{I}_C = 40 \angle 0^\circ + 60 \angle -90^\circ + 40.7 \angle 90^\circ$$

$$\mathbf{I} = 44.4 \angle -25.8^\circ \text{ A}$$

- Power factor correction has reduced current to the load:

$$\Delta I = \frac{72.1 - 44.4}{72.1} \cdot 100\% = 38\%$$

- In practice, losses would be reduced
 - ▣ I^2R losses in resistances between source and load