

SECTION 1: INTRODUCTION


ENGR 203 – Electrical Fundamentals III

2

Introduction

Introduction

3

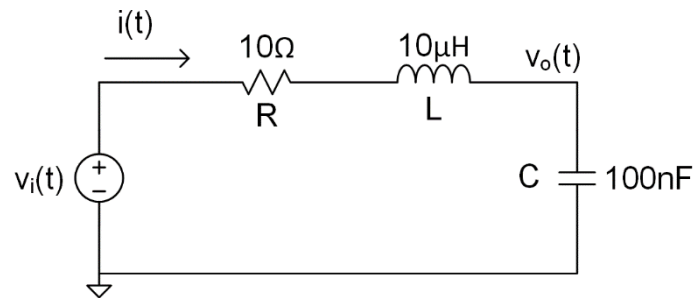


- In **ENGR 202**, we learned how to analyze circuits like this one in several ways:
 - ▣ *Sinusoidal steady-state (phasor) analysis*
 - ▣ *Frequency-response analysis*
 - ▣ *Step-response analysis*
- In **ENGR 203**, we will learn some new mathematical tools that we can apply to these same types of analyses
- First, we will briefly review each of the above analysis techniques

4

Review of Circuit Analysis Tools

Sinusoidal Steady-State Analysis

5

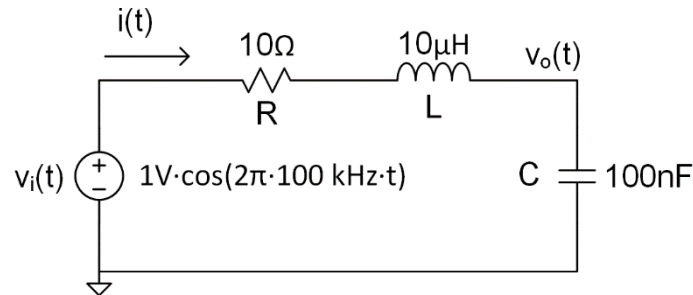

- For a sinusoidal input of a certain frequency, **phasor analysis** allows us to determine output quantities
 - ▣ Also sinusoidal, at the same frequency
- First, convert the circuit to the phasor domain:


$$\mathbf{V}_i = 1 \angle 0^\circ \text{ V}$$

$$Z_L = j\omega L = j \cdot 2\pi \cdot 100 \text{ kHz} \cdot 10 \mu\text{H} = j6.28 \Omega$$

$$Z_C = \frac{1}{j\omega C} = -j \frac{1}{2\pi \cdot 100 \text{ kHz} \cdot 100 \text{ nF}} = -j15.9 \Omega$$

Sinusoidal Steady-State Analysis

6

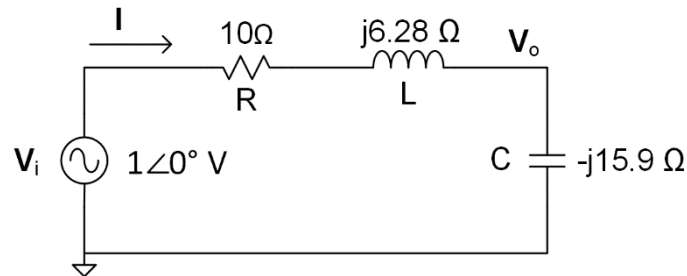

- With the circuit in the phasor domain, we can apply any of the usual circuit analysis tools
 - ▣ Here, we can treat the circuit as a voltage divider

$$\mathbf{V}_o = \mathbf{V}_i \frac{-j15.9\ \Omega}{10 + j(6.28 - 15.9)\ \Omega} = 1\angle 0^\circ \text{ V} \frac{-j15.9\ \Omega}{10 - j9.62\ \Omega}$$

$$\mathbf{V}_o = 1.15\angle -46.1^\circ \text{ V}$$

- Finally, transform back to the time domain

$$v_o(t) = 1.15 \text{ V} \cdot \cos(2\pi \cdot 100 \text{ kHz} \cdot t - 46.1^\circ)$$

Frequency Response Analysis

7


- Phasor analysis gets us the steady-state response of the circuit to a sinusoidal input at **one specific frequency**
 - ▣ The output will be at the same frequency but, in general, different amplitude and phase
- We also saw how to determine the circuit's **frequency response** function and generate its **Bode plot**
 - ▣ Response to sinusoidal input of varying frequency
 - ▣ **Gain** – ratio of output amplitude to input amplitude
 - ▣ **Phase** – phase shift from input to output

$$H(j\omega) = \frac{V_o}{V_i} \rightarrow |H(j\omega)|, \quad \angle H(j\omega)$$

Frequency Response Analysis

8

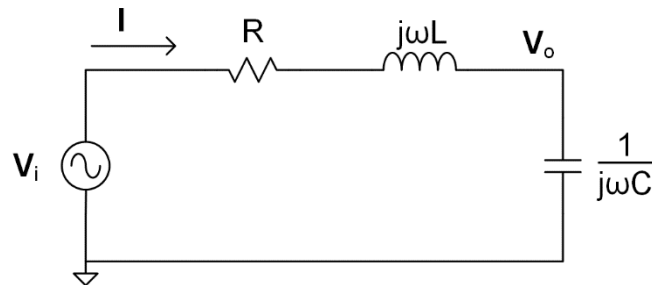- Express impedances as functions of frequency
- Treat the circuit as a voltage divider



$$H(j\omega) = \frac{V_o}{V_i} = \frac{\frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{(j\omega)^2 LC + j\omega RC + 1}$$

- The resulting frequency response function is


$$H(j\omega) = \frac{\frac{1}{LC}}{(j\omega)^2 + \frac{R}{L}j\omega + \frac{1}{LC}}$$

Frequency Response Analysis

9


$$H(j\omega) = \frac{1}{(j\omega)^2 + \frac{R}{L}j\omega + \frac{1}{LC}}$$

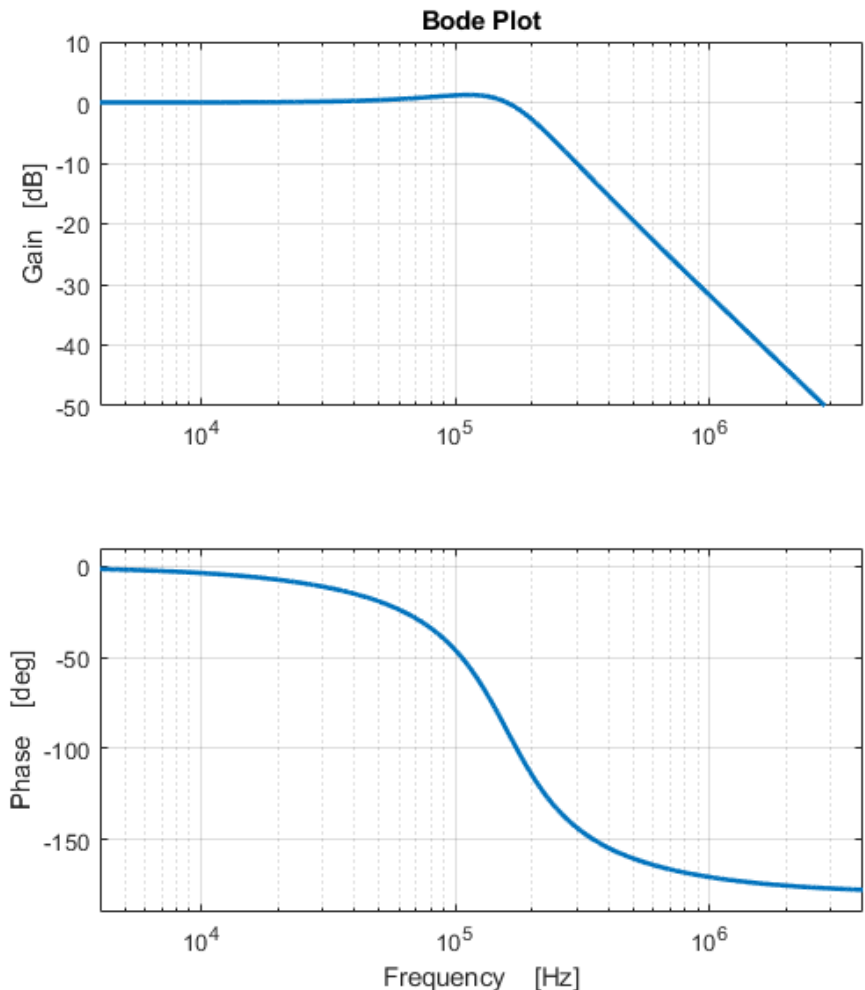- This type of analysis is particularly useful for ***filters***
 - ▣ Frequency-varying gain
 - ▣ Pass some frequencies, attenuate others



Step Response Analysis

10

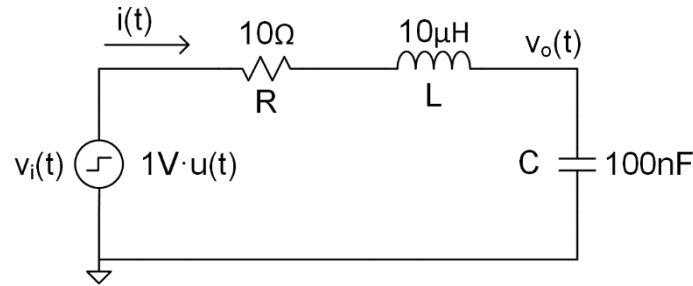


- Finally, in ENGR 202, we learned how to determine the circuit's step response
- The first step was to derive the governing differential equation
- Applying KVL around the loop yields

$$v_i(t) - i(t)R - L \frac{di}{dt} - v_o(t) = 0$$

Step Response Analysis

11

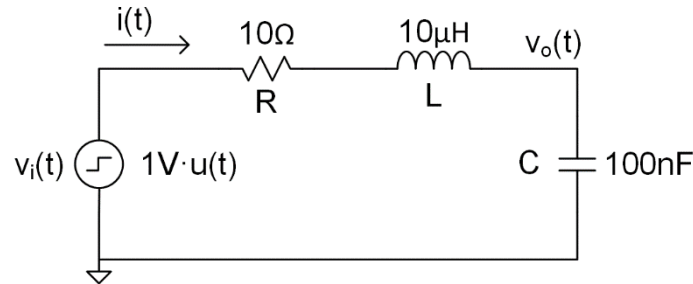

- After eliminating $i(t)$ and rearranging, we have the governing equation for the circuit

$$\frac{d^2 v_o}{dt^2} + \frac{R}{L} \frac{dv_o}{dt} + \frac{1}{LC} v_o(t) = \frac{1}{LC} v_i(t)$$

- A second-order, linear, non-homogeneous, ordinary differential equation
- Non-homogeneous, so we solve it in two parts
 - 1) Find the **complementary solution** to the homogeneous equation
 - 2) Find the **particular solution** for the step input
- General solution is the sum of the two individual solutions:

$$v_o(t) = v_{oc}(t) + v_{op}(t)$$

Step Response Analysis

12

- For the ***complementary solution***, we assume a solution of the form

$$v_{oc}(t) = e^{st}$$

where s is an unknown complex value

- Substituting this into the homogeneous equation allows us to generate the characteristic equation

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

which we can also write as

$$s^2 + 2\zeta\omega_0s + \omega_0^2 = 0$$

where

ζ is the damping ratio

ω_0 is the natural frequency

Step Response Analysis

13

- The damping ratio, and the roots of the characteristic equation, determine the form of the complementary solution
 - ▣ Roots are called the circuit **poles**

- $\zeta > 1$ – **over-damped**

- ▣ Two real, distinct poles, s_1 and s_2

$$v_{oc}(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

- $\zeta = 1$ – **critically-damped**

- ▣ Two real, identical poles, $s_1 = s_2$

$$v_{oc}(t) = K_1 e^{s_1 t} + K_2 t e^{s_1 t}$$


- $\zeta < 1$ – **Under-damped**

- ▣ Complex-conjugate pair of poles, $s_{1,2} = -\alpha \pm j\omega_d$

$$v_{oc}(t) = K_1 e^{-\alpha t} \cos(\omega_d t) + K_2 e^{-\alpha t} \sin(\omega_d t)$$

Step Response Analysis

14

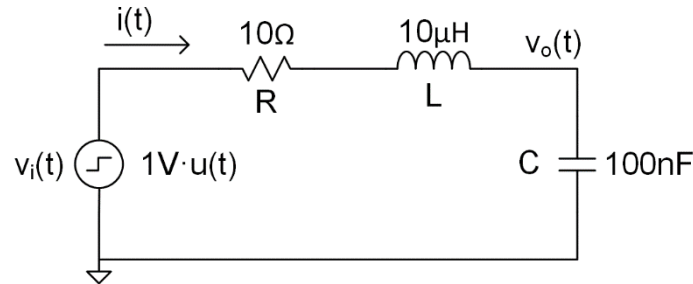

- The second piece of the general solution is the ***particular solution***
 - ▣ For a step input, this is simply the steady-state output

$$v_{op}(t) = v_o(t \rightarrow \infty) = 1V$$

- For our circuit, the characteristic equation is

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = s^2 + 1E6s + 1E12 = s^2 + 2\zeta\omega_0s + \omega_0^2 = 0$$

- ▣ From which we find


$$\omega_0 = 1E6 \text{ rad/sec}$$

$$\alpha = 500E3 \text{ rad/sec}$$

$$\zeta = 0.5$$

Step Response Analysis

15

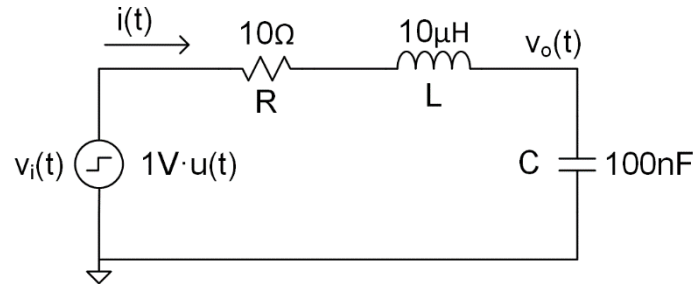

- $\zeta = 0.5$, so the circuit is under-damped
 - ▣ Complementary solution is a sum of damped sinusoids
 - ▣ General solution has the following form

$$v_o(t) = K_1 e^{-\alpha t} \cos(\omega_d t) + K_2 e^{-\alpha t} \sin(\omega_d t) + v_o(t \rightarrow \infty)$$

- The damped natural frequency is

$$\omega_d = \omega_0 \sqrt{1 - \zeta^2} = 866E3 \text{ rad/sec}$$

- ▣ General solution is

$$v_o(t) = K_1 e^{-500E3t} \cos(866E3t) + K_2 e^{-500E3t} \sin(866E3t) + 1 \text{ V}$$

Step Response Analysis


16

- The last step in determining the step response is to determine the unknown coefficients, K_1 and K_2
 - ▣ Apply the initial conditions:

$$v_o(0) = 0 \text{ and } \dot{v}_o(0) = 0$$

- The circuit's response to a 1 V step is
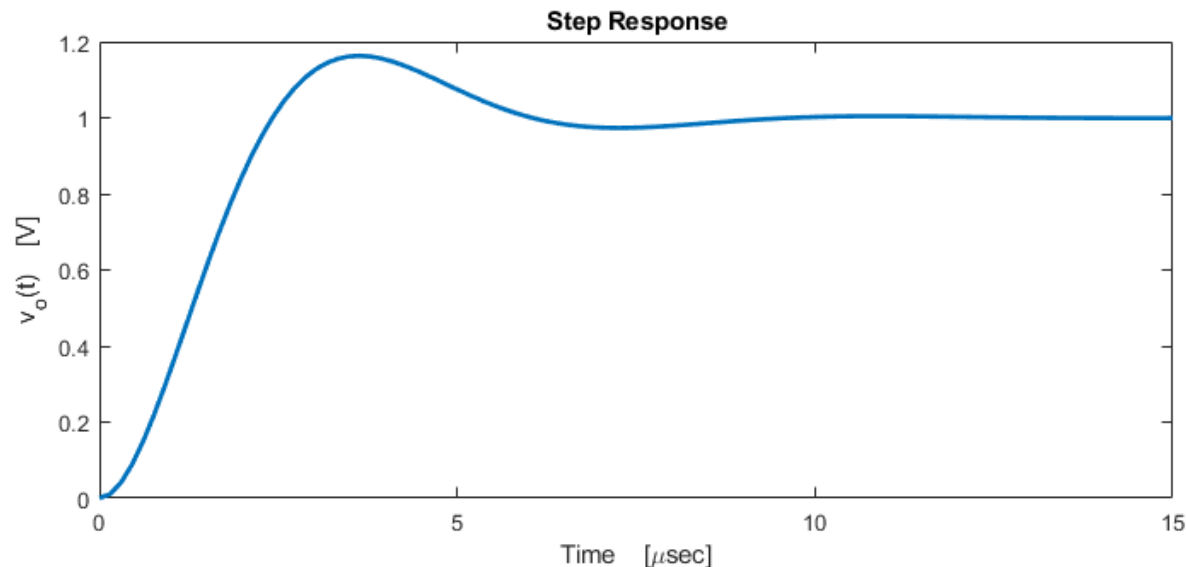
$$v_o(t) = -1V e^{-500E3t} \cos(866E3t) - 0.58V e^{-500E3t} \sin(866E3t) + 1V$$



17

ENGR 203 Course Preview

ENGR 203 Preview

18


- In this course, we will learn a new mathematical tool that will simplify and unify our circuit analyses
 - ▣ The ***Laplace transform***
- We will use the Laplace transform to:
 - 1) Solve a circuit's governing ODE to determine its transient response to any type of input
 - 2) Determine a circuit's time-domain response to any input without needing to derive the governing ODE
 - 3) Determine a circuit's frequency response and Bode plot
- We will now step through a preview of the application of Laplace transforms to various circuit analyses

19

Solving the Governing ODE with Laplace Transforms

Solving the Differential Equation

20

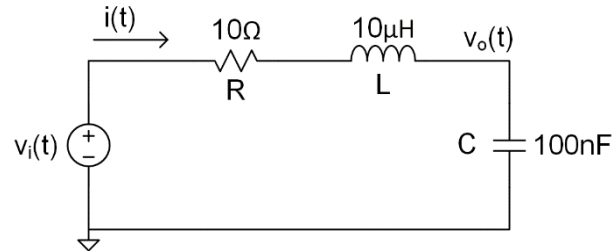

- First, we will see how we will use Laplace transforms to solve a circuit's governing ODE to determine its response to any type of input
- The governing ODE for our example circuit is

$$\frac{d^2 v_o}{dt^2} + \frac{R}{L} \frac{dv_o}{dt} + \frac{1}{LC} v_o(t) = \frac{1}{LC} v_i(t)$$

- Our first step will be to apply the Laplace transform to the governing equation

$$s^2 V_o(s) - s v_o(0) - \dot{v}_o(0) + \frac{R}{L} [s V_o(s) - v_o(0)] + \frac{1}{LC} V_o(s) = \frac{1}{LC} V_i(s)$$

- Assuming the same unit step input, and zero initial conditions, this simplifies to

$$s^2 V_o(s) + \frac{R}{L} s V_o(s) + \frac{1}{LC} V_o(s) = \frac{1}{LC} \frac{1}{s}$$

Solving the Differential Equation

21

$$s^2 V_o(s) + \frac{R}{L} s V_o(s) + \frac{1}{LC} V_o(s) = \frac{1}{LC} \frac{1}{s}$$

- Our differential equation has transformed to an algebraic equation
 - ▣ Solve algebraically for the Laplace transform of the output, $V_o(s)$

$$V_o(s) \left[s^2 + \frac{R}{L} s + \frac{1}{LC} \right] = \frac{1}{LC} \frac{1}{s}$$

$$V_o(s) = \frac{\frac{1}{LC}}{s \left(s^2 + \frac{R}{L} s + \frac{1}{LC} \right)}$$

$$V_o(s) = \frac{1E12}{s(s^2 + 1E6s + 1E12)}$$

Solving the Differential Equation

22

$$V_o(s) = \frac{1E12}{s(s^2 + 1E6s + 1E12)}$$

- This is the Laplace transform of the thing we are looking for, the output voltage, $v_o(t)$

$$V_o(s) = \mathcal{L}\{v_o(t)\}$$

- To get $v_o(t)$, we **inverse Laplace transform** $V_o(s)$

$$v_o(t) = \mathcal{L}^{-1}\{V_o(s)\}$$

- To inverse transform, we will make use of **partial fraction expansion**

Solving the Differential Equation

23

- The partial fraction expansion looks like

$$V_o(s) = \frac{1E12}{s(s^2 + 1E6s + 1E12)} = \frac{r_1}{s} + \frac{r_2(s + 500E3) + r_3 866E3}{(s + 500E3) + (866E3)^2}$$

- Solve for the unknown **residues**, r_1 , r_2 , and r_3 , giving the output voltage in the Laplace domain

$$V_o(s) = \frac{1}{s} - \frac{(s + 500E3)}{(s + 500E3) + (866E3)^2} - 0.58 \frac{866E3}{(s + 500E3) + (866E3)^2}$$

- This is now a sum of Laplace domain functions whose inverse transforms are known
 - ▣ Inverse transform by inspection


$$v_o(t) = \mathcal{L}^{-1}\{V_o(s)\}$$

$$v_o(t) = 1V - 1Ve^{-500E3t} \cos(866E3t) - 0.58Ve^{-500E3t} \sin(866E3t)$$

Solving the Differential Equation

24
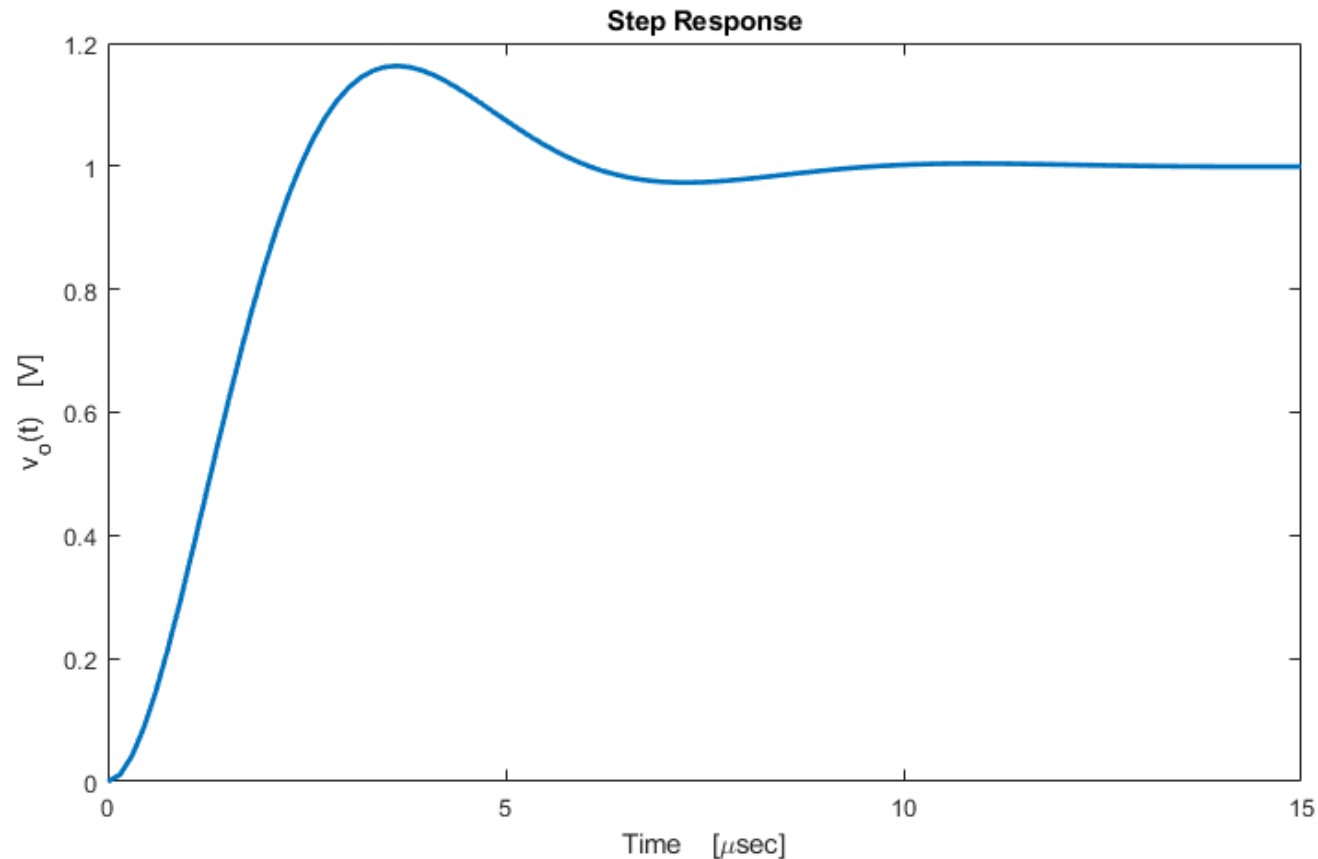
$$v_o(t) = 1V - 1Ve^{-500E3t} \cos(866E3t) - 0.58Ve^{-500E3t} \sin(866E3t)$$



25


Laplace Domain Circuit Analysis

Laplace Domain Circuit Analysis


26

- Previous analysis required derivation of the governing differential equation
- Can often skip that step
 - ▣ Transform the *circuit* to the Laplace domain
 - ▣ Apply usual circuit analysis tools
- Similar to transforming to the phasor domain

Time Domain:

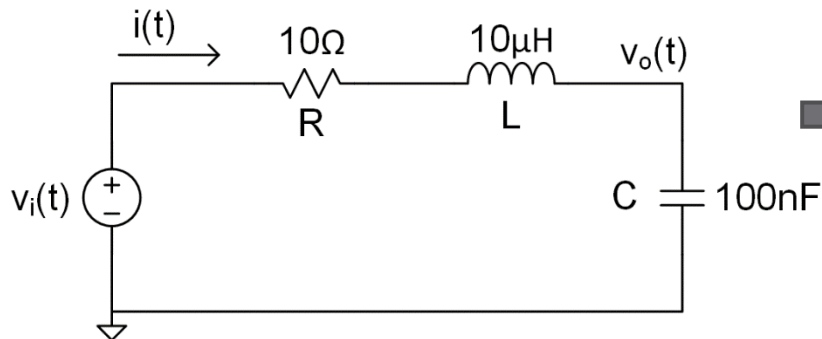


Laplace Domain:

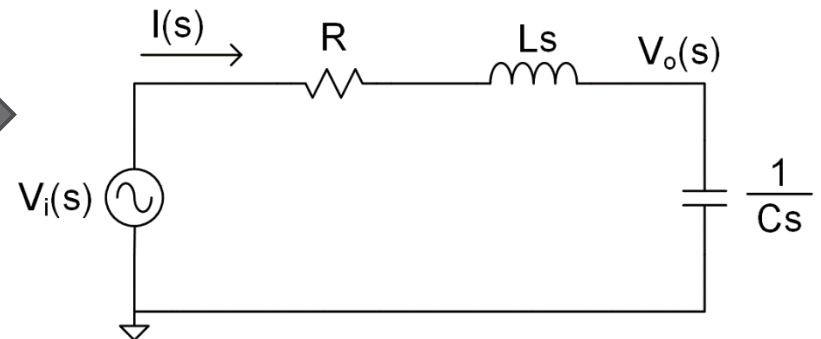

Laplace Domain Circuit Analysis

27

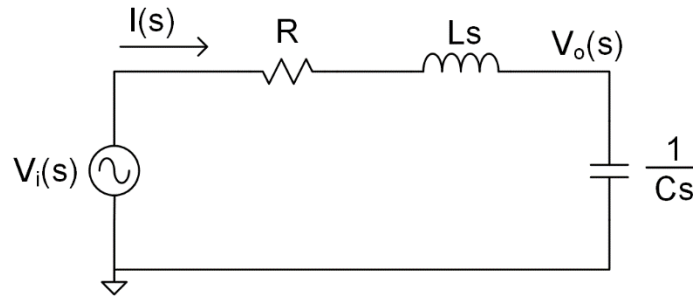

- With the circuit in the Laplace domain, we can apply any of the usual circuit analysis tools
 - ▣ Here, we are looking for $V_o(s)$, so treat it as a voltage divider

$$V_o(s) = V_i(s) \frac{\frac{1}{Cs}}{R + Ls + \frac{1}{Cs}} = V_i(s) \frac{1}{LCs^2 + RCs + 1}$$

$$V_o(s) = V_i(s) \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Laplace Domain Circuit Analysis

28

- For the given component values and a step input the output in the Laplace domain is

$$V_o(s) = \frac{1}{s} \frac{1E12}{s^2 + 1E6s + 1E12}$$

- The same result arrived at by transforming the governing ODE
 - Solve the same way: inverse Laplace transform via partial fraction expansion

$$v_o(t) = \mathcal{L}^{-1}\{V_o(s)\}$$

- Note that this did not involve derivation of the differential equation in the time domain


29

Laplace Domain Frequency-Response Analysis

Frequency Response via Laplace Transform

30

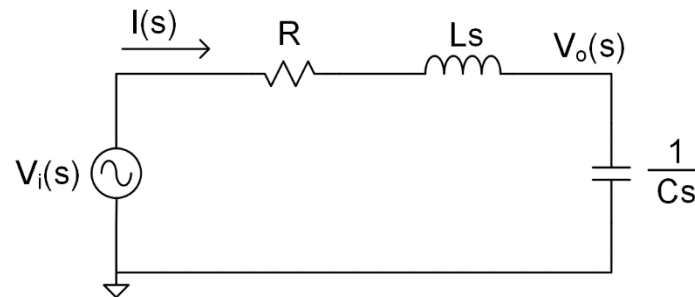- Finally, we will see how we can apply Laplace transforms to determine a circuit's **frequency response** and **Bode plot**
- First, convert the circuit to the Laplace domain



- As before, apply the usual circuit analysis techniques to determine the output

$$V_o(s) = V_i(s) \frac{1}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Frequency Response via Laplace Transform

31

$$V_o(s) = V_i(s) \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

- From here, we get the circuit's **transfer function**

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

- From the transfer function, we get the **frequency response function** by substituting in $j\omega$ for s



$$H(s) \xrightarrow{s \rightarrow j\omega} H(j\omega) = \frac{\frac{1}{LC}}{(j\omega)^2 + \frac{R}{L}(j\omega) + \frac{1}{LC}}$$

Frequency Response Analysis

32

$$H(j\omega) = \frac{1}{(j\omega)^2 + \frac{R}{L}(j\omega) + \frac{1}{LC}}$$

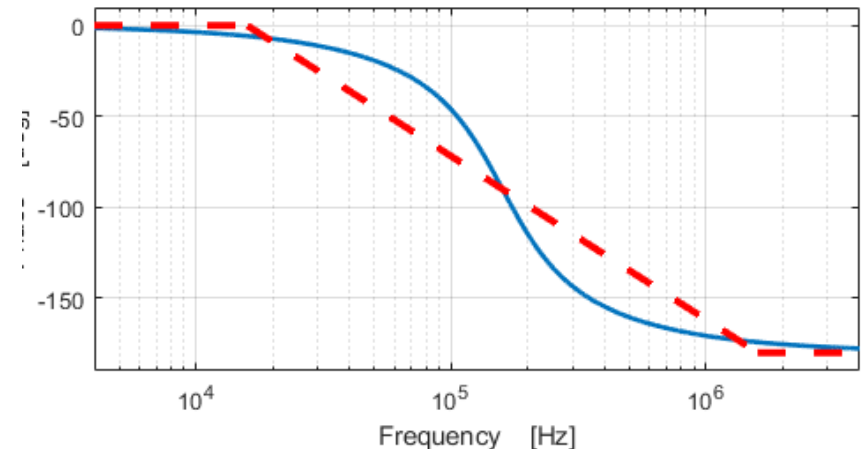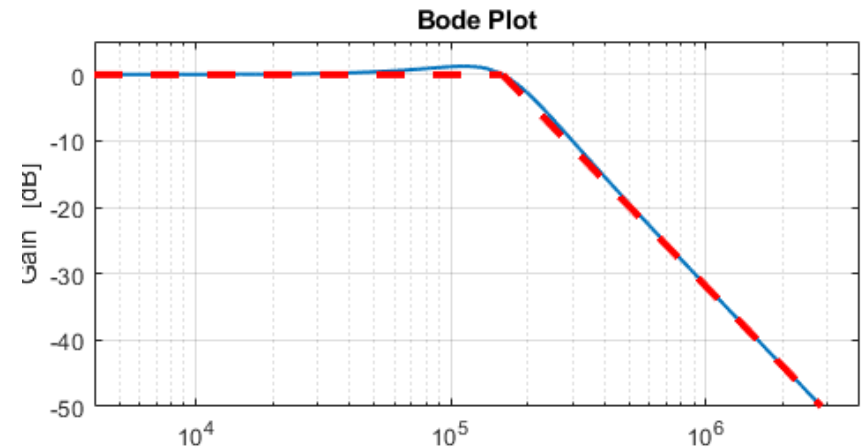- We will learn to generate **Bode plot** from the frequency response function or transfer function
 - ▣ Hand-sketching a straight-line approximation
 - ▣ Plotting in numerical tools like MATLAB or Python



33

Fourier Analysis

Fourier Analysis

34

- We will learn other mathematical tools to enable further circuit analysis
 - ***Fourier series***
 - ***Fourier transform***

- In ENGR 202 we introduced the ***frequency spectrum***
 - Frequency content of a signal
 - How will a signal be affected by a circuit with a particular frequency response?

- Fourier series/transform allow us to mathematically determine frequency spectra
 - Spectrum of input, along with circuit's frequency response, allow us to determine spectrum of output

Fourier Analysis

35

