

SECTION 3: INVERSE LAPLACE TRANSFORMS

ENGR 203 – Electrical Fundamentals III

2


Inverse Laplace Transform

We've just seen how time-domain functions can be transformed to the Laplace domain. Next, we'll look at how we can solve differential equations in the Laplace domain and transform back to the time domain.

Laplace Transforms – Differential Equations

3

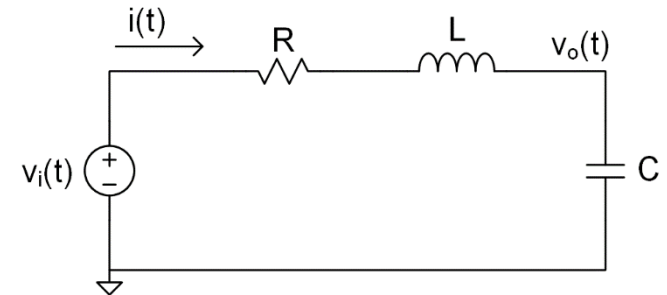- Consider the simple RLC circuit from the introductory section of notes:
- The governing differential equation is



$$\frac{d^2 v_o}{dt^2} + \frac{R}{L} \frac{dv_o}{dt} + \frac{1}{LC} v_o(t) = \frac{1}{LC} v_i(t)$$

- Or, using dot notation


$$\ddot{v}_o(t) + \frac{R}{L} \dot{v}_o(t) + \frac{1}{LC} v_o(t) = \frac{1}{LC} v_i(t) \quad (1)$$

Laplace Transforms – Differential Equations

4

- We'll now use Laplace transforms to determine the **step response** of the system
- 1 V step input
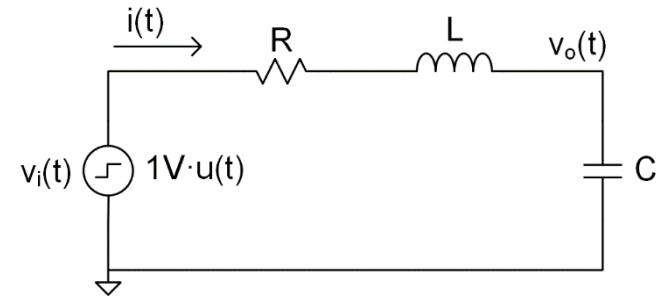
$$v_i(t) = 1 \text{ V} \cdot u(t) = \begin{cases} 0 \text{ V}, & t < 0 \\ 1 \text{ V}, & t \geq 0 \end{cases} \quad (2)$$



- For the step response, we assume **zero initial conditions**

$$v_o(0) = 0 \text{ and } \dot{v}_o(0) = 0 \quad (3)$$

- Using the derivative property of the Laplace transform, (1) becomes

$$s^2 V_o(s) - s v_o(0) - \dot{v}_o(0) + \frac{R}{L} s V_o(s) - \frac{R}{L} v_o(0) + \frac{1}{LC} V_o(s) = \frac{1}{LC} V_i(s)$$

$$s^2 V_o(s) + \frac{R}{L} s V_o(s) + \frac{1}{LC} V_o(s) = \frac{1}{LC} V_i(s) \quad (4)$$

Laplace Transforms – Differential Equations

5

- The input is a step, so (4) becomes


$$s^2 V_o(s) + \frac{R}{L} s V_o(s) + \frac{1}{LC} V_o(s) = \frac{1}{LC} \frac{1}{s} \quad (5)$$

- Solving (5) for $V_o(s)$

$$V_o(s) \left(s^2 + \frac{R}{L} s + \frac{1}{LC} \right) = \frac{1}{LC} \frac{1}{s}$$

$$V_o(s) = \frac{1/LC}{s \left(s^2 + \frac{R}{L} s + \frac{1}{LC} \right)} \quad (6)$$

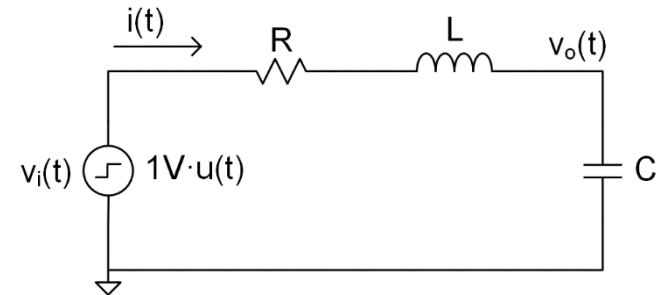- Equation (6) is the solution to the differential equation of (1), given the step input and I.C.'s
 - ▣ The system step response in the Laplace domain
 - ▣ Next, we need to transform back to the time domain



Laplace Transforms – Differential Equations

6


$$V_o(s) = \frac{1/LC}{s\left(s^2 + \frac{R}{L}s + \frac{1}{LC}\right)}$$

- The form of (6) is typical of Laplace transforms when dealing with linear systems

- ▣ A **rational polynomial** in s
- ▣ Here, the numerator is 0th-order

$$V_o(s) = \frac{B(s)}{A(s)}$$

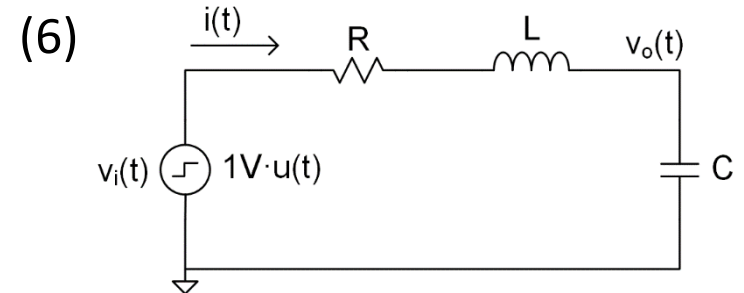- Roots of the numerator polynomial, $B(s)$, are called the **zeros** of the function
- Roots of the denominator polynomial, $A(s)$, are called the **poles** of the function



Inverse Laplace Transforms

7


$$V_o(s) = \frac{1/LC}{s\left(s^2 + \frac{R}{L}s + \frac{1}{LC}\right)}$$

- To get (6) back into the time domain, we need to perform an ***inverse Laplace transform***

- An integral inverse transform exists, but we don't use it
- Instead, we use ***partial fraction expansion***

- **Partial fraction expansion**

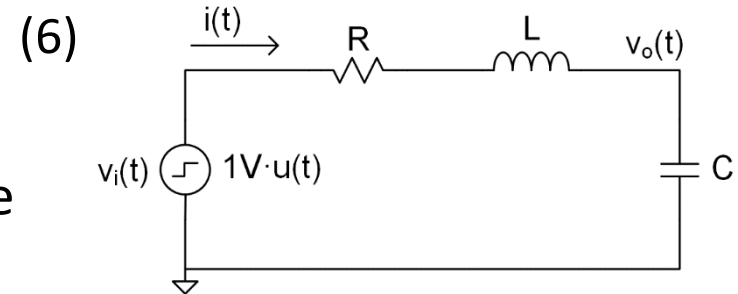- Idea is to express the Laplace transform solution, (6), as a sum of Laplace transform terms that appear in the table
- Procedure depends on the type of roots of the denominator polynomial
 - Real and distinct
 - Repeated
 - Complex



Inverse Laplace Transforms – Example 1


8

- Consider the following system parameters

$$R = 25 \Omega$$

$$L = 10 \mu H$$

$$C = 100 nF$$

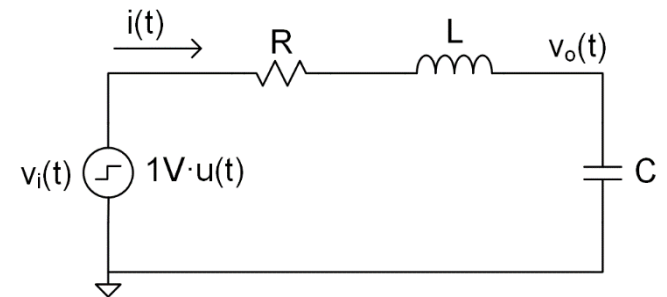

- Laplace transform of the step response becomes

$$V_o(s) = \frac{1E12}{s(s^2 + 2.5E6s + 1E12)} \quad (7)$$

- Factoring the denominator

$$V_o(s) = \frac{1E12}{s(s + 500E3)(s + 2E6)} \quad (8)$$

- In this case, the denominator polynomial has three **real, distinct roots**:


$$s_1 = 0, \quad s_2 = -500E3, \quad s_3 = -2E6$$

Inverse Laplace Transforms – Example 1

9

- Partial fraction expansion of (8) has the form
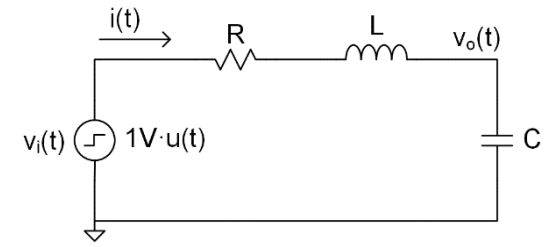
$$V_o(s) = \frac{1E12}{s(s+500E3)(s+2E6)} = \frac{r_1}{s} + \frac{r_2}{s+500E3} + \frac{r_3}{s+2E6} \quad (9)$$



- The numerator coefficients, r_1 , r_2 , and r_3 , are called **residues**
- Can already see the form of the time-domain function
 - Sum of a **constant** and **two decaying exponentials**
- To determine the residues, multiply both sides of (9) by the denominator of the left-hand side

$$1E12 = r_1(s + 500E3)(s + 2E6) + r_2s(s + 2E6) + r_3s(s + 500E3)$$

$$1E12 = r_1s^2 + 2.5E6r_1s + 1E12r_1 + r_2s^2 + 2E6r_2s + r_3s^2 + 500E3r_3s$$

- Collecting terms, we have

$$1E12 = s^2(r_1 + r_2 + r_3) + s(2.5E6r_1 + 2E6r_2 + 500E3r_3) + 1E12r_1 \quad (10)$$

Inverse Laplace Transforms – Example 1

10

- Equating coefficients of powers of s on both sides of (10) gives a system of three equations in three unknowns

$$s^2: \quad 0 = r_1 + r_2 + r_3$$

$$s^1: \quad 0 = 2.5E6r_1 + 2E6r_2 + 500E3r_3$$

$$s^0: \quad 1E12 = 1E12r_1$$

- Solving for the residues gives

$$r_1 = 1$$


$$r_2 = -1.333$$

$$r_3 = 0.333$$

- The Laplace transform of the step response is

$$V_o(s) = \frac{1}{s} - \frac{1.333}{s+500E3} + \frac{0.333}{s+2E6} \quad (11)$$

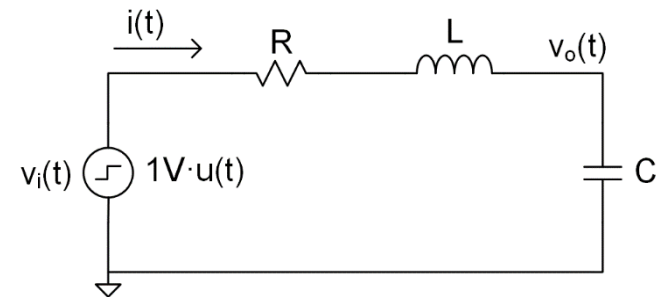- Equation (11) can now be transformed back to the time domain using the Laplace transform table




Inverse Laplace Transforms – Example 1

11

- The time-domain step response of the system is the **sum of a constant term and two decaying exponentials**:

$$v_o(t) = 1 \text{ V} - 1.333 \text{ V}e^{-500E3t} + 0.333 \text{ V}e^{-2E6t} \quad (12)$$

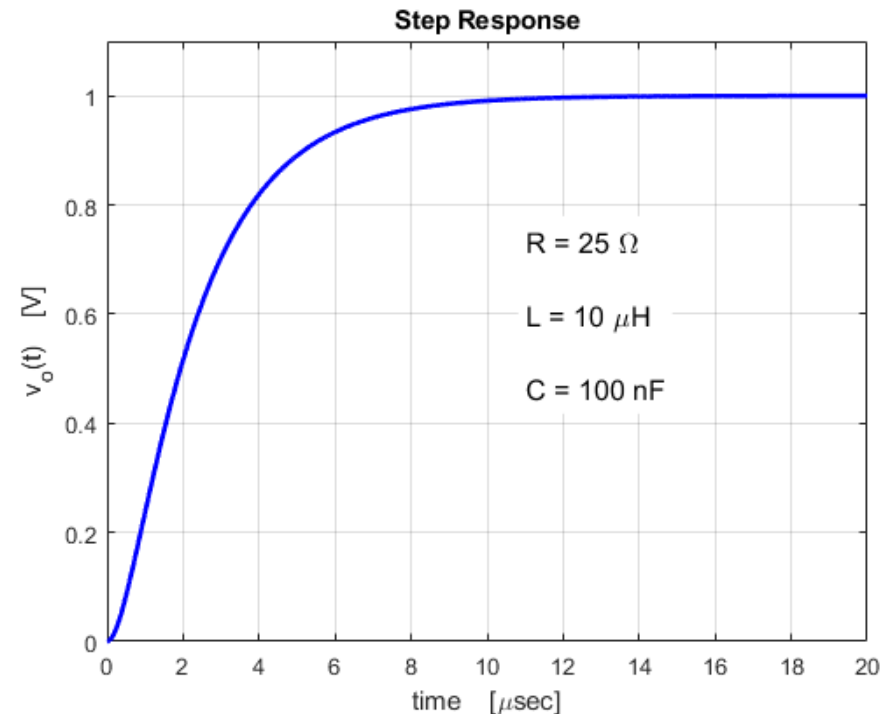- Step response plotted in MATLAB
- Characteristic of a signal having **only real poles**
 - ▣ No overshoot/ringing
- Steady-state voltage agrees with intuition




Inverse Laplace Transforms – Example 1

12

- Go back to (7) and apply the **initial value theorem**
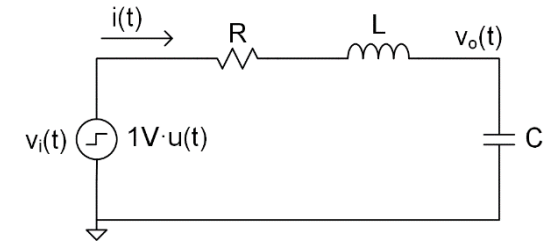
$$v_o(0) = \lim_{s \rightarrow \infty} sV_o(s) = \lim_{s \rightarrow \infty} \frac{1E12}{(s^2 + 2.5E6s + 1E12)} = 0 \text{ V}$$



- Which is, in fact our assumed initial condition

-
- Next, apply the **final value theorem** to the Laplace transform step response, (7)

$$v_o(\infty) = \lim_{s \rightarrow 0} sV_o(s) = \lim_{s \rightarrow 0} \frac{1E12}{(s^2 + 2.5E6s + 1E12)}$$

$$v_o(\infty) = \frac{1E12}{1E12} = 1 \text{ V}$$

- This final value agrees with both intuition and our numerical analysis

Inverse Laplace Transforms – Example 2


13

- **Reduce the resistance** and re-calculate the step response

$$R = 20 \Omega$$

$$L = 10 \mu H$$

$$C = 100 nF$$

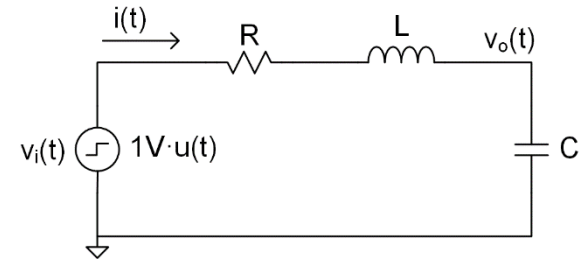

- Laplace transform of the step response becomes

$$V_o(s) = \frac{1E12}{s(s^2 + 2E6s + 1E12)} \quad (13)$$

- Factoring the denominator

$$V_o(s) = \frac{1E12}{s(s + 1E6)^2} \quad (14)$$

- In this case, the denominator polynomial has three **real roots**, two of which are **identical**


$$s_1 = 0, \quad s_2 = -1E6, \quad s_3 = -1E6$$

Inverse Laplace Transforms – Example 2

14

- Partial fraction expansion of (14) has the form
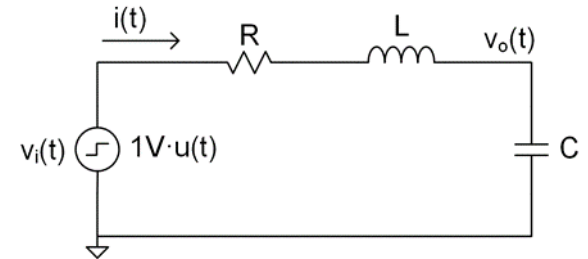
$$V_o(s) = \frac{1E12}{s(s+1E6)^2} = \frac{r_1}{s} + \frac{r_2}{s+1E6} + \frac{r_3}{(s+1E6)^2} \quad (15)$$



- Again, find residues by multiplying both sides of (15) by the left-hand side denominator

$$1E12 = r_1(s + 1E6)^2 + r_2s(s + 1E6) + r_3s$$

$$1E12 = r_1s^2 + 2E6r_1s + 1E12r_1 + r_2s^2 + 1E6r_2s + r_3s$$

- Collecting terms, we have

$$1E12 = s^2(r_1 + r_2) + s(2E6r_1 + 1E6r_2 + r_3) + 1E12r_1 \quad (16)$$

Inverse Laplace Transforms – Example 2

15

- Equating coefficients of powers of s on both sides of (16) gives a system of three equations in three unknowns

$$s^2: 0 = r_1 + r_2$$

$$s^1: 0 = 2E6r_1 + 1E6r_2 + r_3$$

$$s^0: 1E12 = 1E12r_1$$

- Solving for the residues gives

$$r_1 = 1$$


$$r_2 = -1$$

$$r_3 = -1E6$$

- The Laplace transform of the step response is

$$V_o(s) = \frac{1}{s} - \frac{1}{s+1E6} - \frac{1E6}{(s+1E6)^2} \quad (17)$$

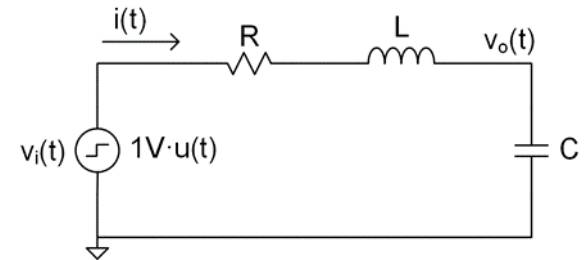- Equation (17) can now be transformed back to the time domain using the Laplace transform table




Inverse Laplace Transforms – Example 2

16

- The time-domain step response of the system is the **sum of a constant, a decaying exponential, and a decaying exponential scaled by time**:

$$v_o(t) = 1\text{ V} - 1\text{ V}e^{-1E6t} - 1E6\frac{\text{V}}{\text{s}}te^{-1E6t} \quad (18)$$

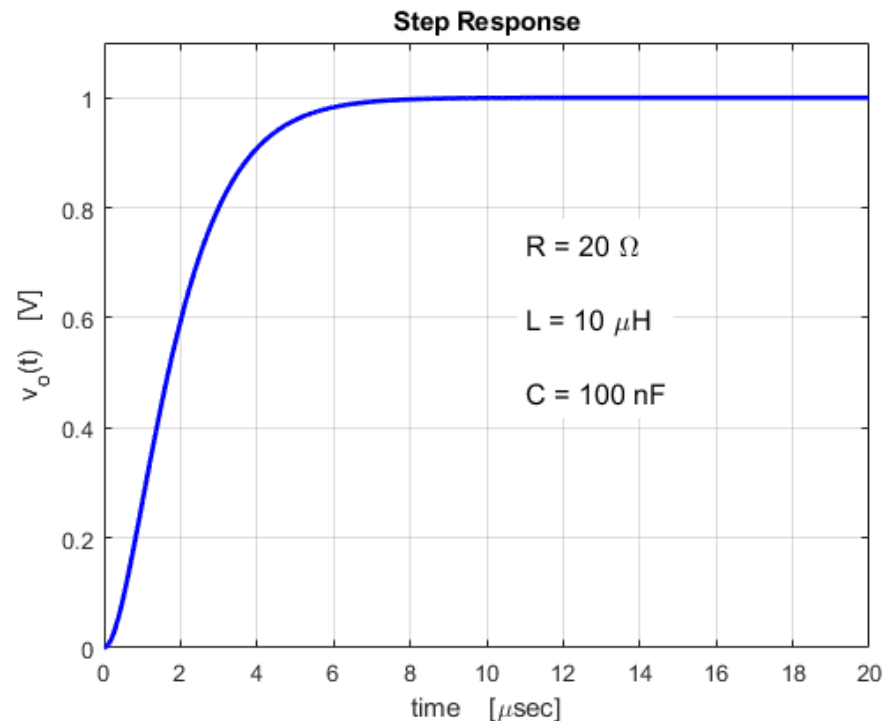- Step response plotted in MATLAB
- Again, characteristic of a signal having **only real poles**
 - ▣ Similar to the last case
 - ▣ A bit faster – slower pole at $s = -500E3$ was eliminated



Inverse Laplace Transforms – Example 3


17

- **Reduce the resistance even further** and go through the process once again

$$R = 10 \Omega$$

$$L = 10 \mu H$$

$$C = 100 nF$$

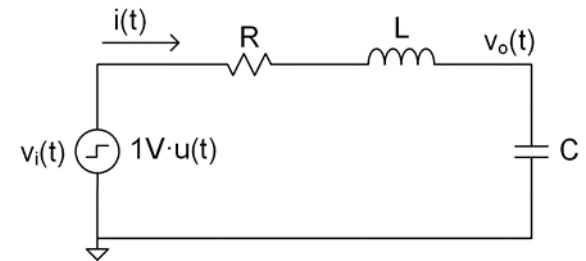

- Laplace transform of the step response becomes

$$V_o(s) = \frac{1E12}{s(s^2 + 1E6s + 1E12)} \quad (19)$$

- The second-order term in the denominator now has **complex roots**, so we won't factor any further
- The denominator polynomial still has a root at zero and now has two roots which are a **complex-conjugate pair**


$$s_1 = 0, \quad s_2 = -500E3 + j866E3, \quad s_3 = -500E3 - j866E3$$

Inverse Laplace Transforms – Example 3

18

- Want to cast the partial fraction terms into forms that appear in the Laplace transform table
- Second-order terms should be of the form
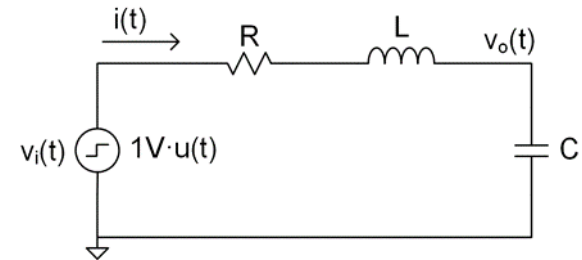
$$\frac{r_i(s+\sigma)+r_{i+1}\omega}{(s+\sigma)^2+\omega^2} \quad (20)$$



- This will transform into the sum of **damped sine** and **cosine** terms

$$\mathcal{L}^{-1} \left\{ r_i \frac{(s + \sigma)}{(s + \sigma)^2 + \omega^2} + r_{i+1} \frac{\omega}{(s + \sigma)^2 + \omega^2} \right\} = r_i e^{-\sigma t} \cos(\omega t) + r_{i+1} e^{-\sigma t} \sin(\omega t)$$

- To get the second-order term in the denominator of (19) into the form of (20), **complete the square**, to give the following partial fraction expansion


$$V_o(s) = \frac{1E12}{s(s^2+1E6s+1E12)} = \frac{r_1}{s} + \frac{r_2(s+500E3)+r_3(866E3)}{(s+500E3)^2+(866E3)^2} \quad (21)$$

Inverse Laplace Transforms – Example 3

19

- Note that the σ and ω terms in (20) and (21) are the **real** and **imaginary parts** of the complex-conjugate denominator roots
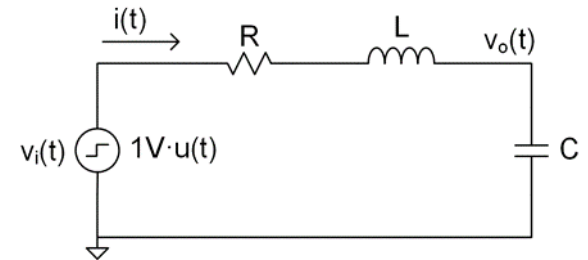
$$s_{2,3} = -\sigma \pm j\omega = -500E3 \pm j866E3$$



- Multiplying both sides of (21) by the left-hand-side denominator, equate coefficients and solve for residues as before:

$$r_1 = 1$$

$$r_2 = -1$$

$$r_3 = -0.577$$

- Laplace transform of the step response is

$$V_o(s) = \frac{1}{s} - \frac{(s+500E3)}{(s+500E3)^2 + (866E3)^2} - \frac{0.577(866E3)}{(s+500E3)^2 + (866E3)^2} \quad (22)$$


Inverse Laplace Transforms – Example 3

20

- The time-domain step response of the system is the **sum of a constant and two decaying sinusoids**:

$$y(t) = 1 \text{ V} - 1 \text{ V} e^{-500E3t} \cos(866E3t) - 0.577 \text{ V} e^{-500E3t} \sin(866E3t) \quad (23)$$

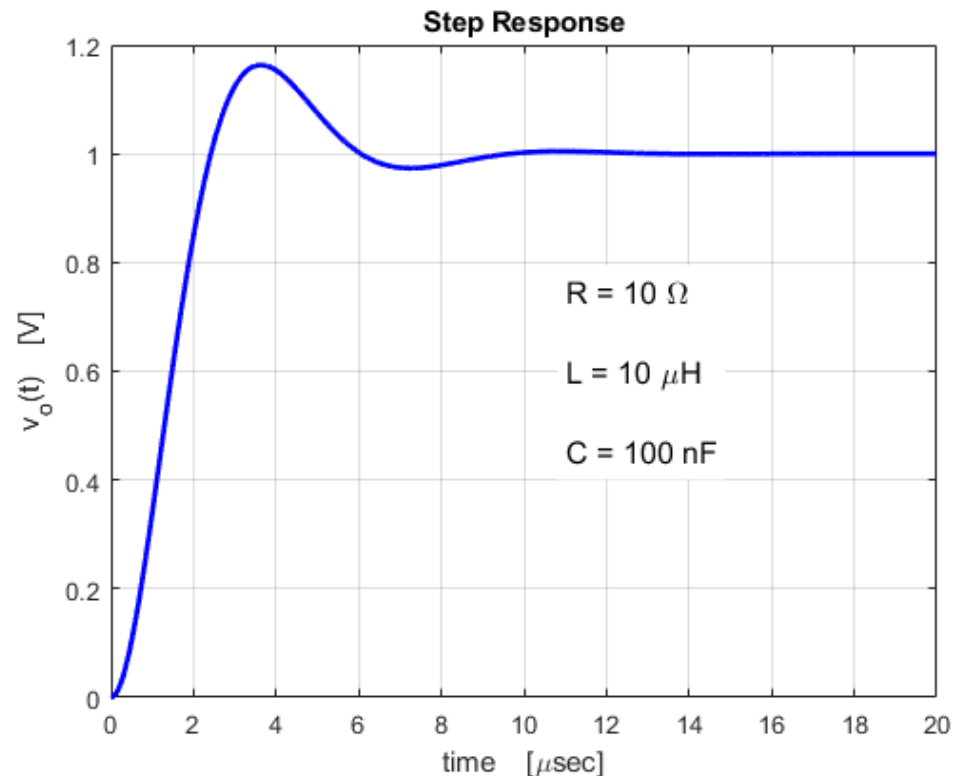- Step response and individual components plotted in MATLAB
- Characteristic of a signal having **complex poles**
 - ▣ Sinusoidal terms result in overshoot and (possibly) ringing



Laplace-Domain Signals with Complex Poles

21


- The Laplace transform of the step response in the last example had **complex poles**

- A **complex-conjugate pair**: $s = -\sigma \pm j\omega$

- Results in sine and cosine terms in the time domain

$$Ae^{-\sigma t} \cos(\omega t) + Be^{-\sigma t} \sin(\omega t)$$

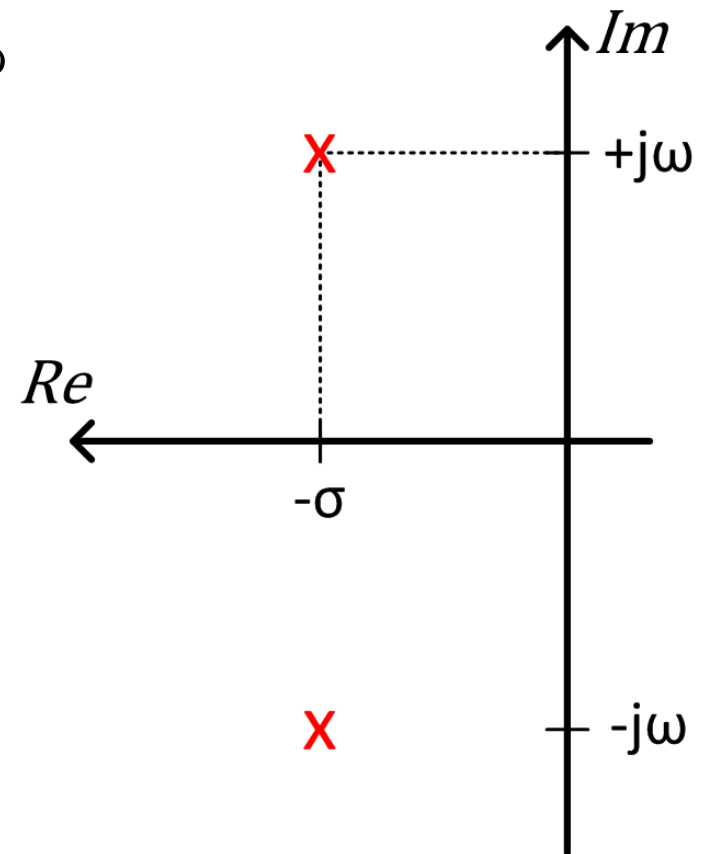- **Imaginary part** of the roots, ω
 - **Frequency of oscillation** of sinusoidal components of the signal
- **Real part** of the roots, σ ,
 - **Rate of decay** of the sinusoidal components
- Much more on this later




22

Natural & Driven Responses

Natural and Forced Responses

23

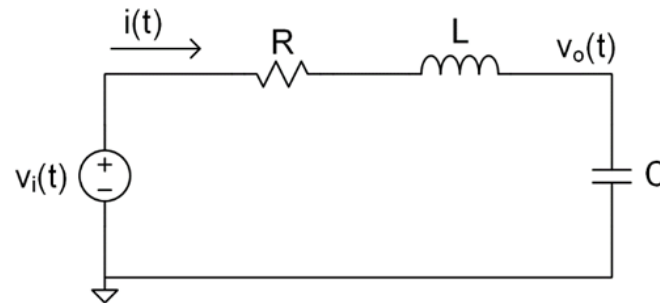

- In the previous section we used Laplace transforms to determine the response of a circuit to a step input, given zero initial conditions
 - ▣ The *driven response*
- Now, consider the response of the same system to non-zero initial conditions only
 - ▣ The *natural response*

Natural Response

24

- Same *under-damped* RLC circuit
- Now the input steps from 1 V to 0 V at $t = 0$


$$v_i(t) = 1V - 1V u(t)$$

- Since $v_i(t \geq 0) = 0$, the governing equation becomes

$$\ddot{v}_o + \frac{R}{L} \dot{v}_o + \frac{1}{LC} v_o = 0 \quad (24)$$

- Use the derivative property to Laplace transform (24)
 - ▣ Allow for non-zero initial-conditions
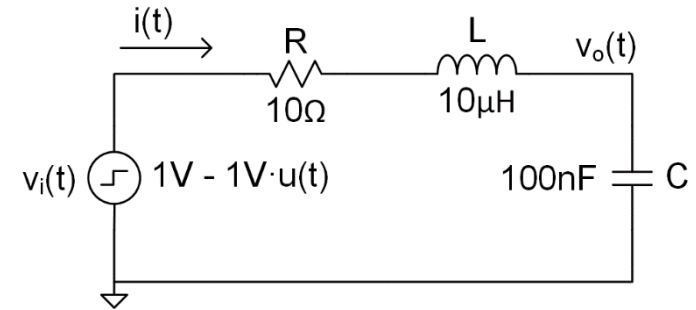
$$s^2 V_o(s) - s v_o(0) - \dot{v}_o(0) + \frac{R}{L} s V_o(s) - \frac{R}{L} v_o(0) + \frac{1}{LC} V_o(s) = 0 \quad (25)$$



Natural Response

25

- Solving (25) for $V_o(s)$ gives the Laplace transform of the output due solely to **initial conditions**
 - ▣ Laplace transform of the **natural response**

$$V_o(s) = \frac{sv_o(0) + \dot{v}_o(0) + \frac{R}{L}v_o(0)}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \quad (26)$$

- For the given input, for $t < 0$:
 - ▣ $v_i(t < 0) = 1 \text{ V}$
 - ▣ $i(t < 0) = 0 \text{ A}$
 - ▣ $v_o(t < 0) = 1 \text{ V}$
- At $t = 0$, neither $i(t)$ nor $v_o(t)$ can change instantaneously, so the initial conditions are:

$$v_o(0) = 1 \text{ V} \quad \text{and} \quad \dot{v}_o(0) = 0 \text{ V/s}$$

Natural Response

26

- Substituting component parameters and initial conditions into (26)

$$V_o(s) = \frac{s + 1E6}{(s^2 + 1E6s + 1E12)} \quad (27)$$

- Remember, it's the **roots of the denominator polynomial** that dictate the form of the response
 - **Real roots** – decaying exponentials
 - **Complex roots** – decaying sinusoids
- For the under-damped case, roots are complex
 - Complete the square
 - Partial fraction expansion has the form

$$V_o(s) = \frac{s + 1E6}{(s^2 + 1E6s + 1E12)} = \frac{r_1(s + 500E3) + r_2(866E3)}{(s + 500E3)^2 + (866E3)^2} \quad (28)$$

Natural Response

27

$$V_o(s) = \frac{s + 1E6}{(s^2 + 1E6s + 1E12)} = \frac{r_1(s + 500E3) + r_2(866E3)}{(s + 500E3)^2 + (866E3)^2} \quad (28)$$

- Multiply both sides of (28) by the denominator of the left-hand side

$$s + 1E6 = r_1s + 500E3r_1 + 866E3r_2$$

- Equating coefficients and solving for r_1 and r_2 gives

$$r_1 = 1, \quad r_2 = 0.577$$

- The Laplace transform of the natural response:

$$V_o(s) = \frac{(s + 500E3)}{(s + 500E3)^2 + (866E3)^2} + \frac{0.577(866E3)}{(s + 500E3)^2 + (866E3)^2} \quad (29)$$


Natural Response

28

- Inverse Laplace transform is the ***natural response***

$$y(t) = 1 V e^{-500E3t} \cos(866E3 \cdot t) + 0.577 V e^{-500E3t} \sin(866E3 \cdot t) \quad (30)$$

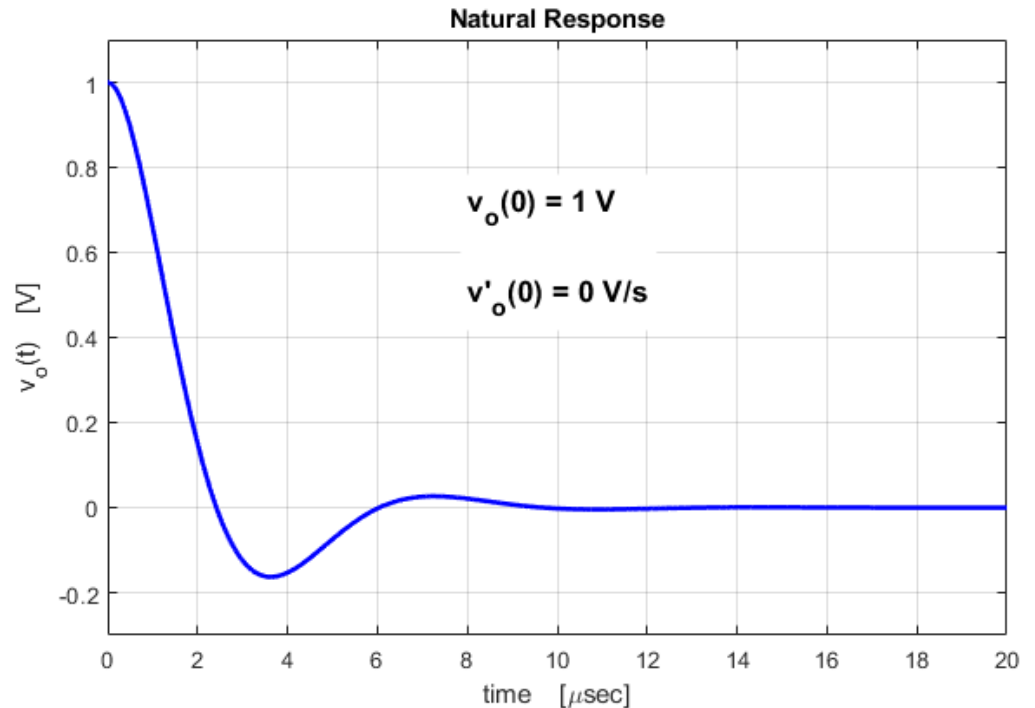- Under-damped response is the sum of ***decaying sine and cosine*** terms




Driven Response with Non-Zero I.C.s

29

- Now, change the source to provide both **non-zero input** (for $t \geq 0$) and **non-zero initial conditions**:

$$v_i(t) = -1V + 2V \cdot u(t)$$

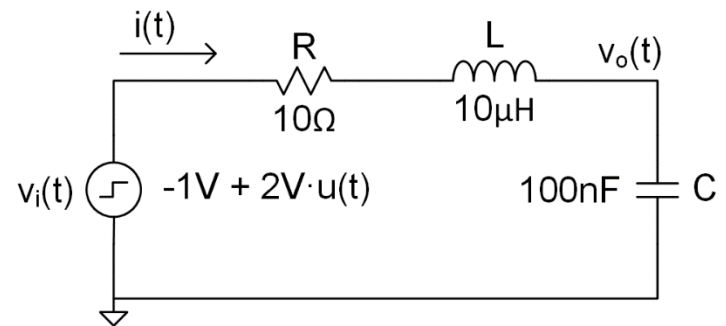

- The Laplace transform of the output including both input and initial conditions:

$$s^2 V_o(s) - s v_o(0) - \dot{v}_o(0) + \frac{R}{L} s V_o(s) - \frac{R}{L} v_o(0) + \frac{1}{LC} V_o(s) = \frac{1}{LC} V_i(s)$$

- Solving for $V_o(s)$ gives

$$V_o(s) = \frac{s v_o(0) + \dot{v}_o(0) + \frac{R}{L} v_o(0) + \frac{1}{LC} V_i(s)}{s^2 + \frac{R}{L} s + \frac{1}{LC}} \quad (31)$$

Driven Response with Non-Zero I.C.'s

30

- Laplace transform of the response has two components

$$V_o(s) = \underbrace{\frac{s v_o(0) + \dot{v}_o(0) + \frac{R}{L}v_o(0)}{\left(s^2 + \frac{R}{L}s + \frac{1}{LC}\right)}}_{\text{Natural response - initial conditions}} + \underbrace{\frac{\frac{1}{LC}F_{in}(s)}{\left(s^2 + \frac{R}{L}s + \frac{1}{LC}\right)}}_{\text{Driven response - input}} \quad (32)$$

Natural response - initial conditions

Driven response - input

-
- Total response is a superposition of the initial condition response and the driven response
 - Both have the same denominator polynomial
 - ▣ Same roots, same type of response
 - Over-, under-, critically-damped

Driven Response with Non-Zero I.C.s

31

- The input now is

$$v_i(t) = -1 V + 2 V \cdot u(t) = \begin{cases} -1 V & t < 0 \\ +1 V & t \geq 0 \end{cases}$$

- For $t \geq 0$, the input is $1 V$

- ▣ The same as a unit step, so it's Laplace transform is simply

$$V_i(s) = \frac{1}{s}$$

- ▣ The fact that $v_i(t < 0) = -1 V$ is accounted for by the initial conditions:

$$v_o(0) = -1 V \quad \text{and} \quad \dot{v}_o(0) = 0 V/s$$

Driven Response with Non-Zero I.C.'s

32

- Substituting in component and input values gives the Laplace transform of the **total** response

$$V_o(s) = \frac{-s - 1E6 + \frac{1E12}{s}}{(s^2 + 1E6s + 1E12)} = \frac{-s^2 - 1E6s + 1E12}{s(s^2 + 1E6s + 1E12)}$$

- Transform back to time domain via partial fraction expansion

$$V_o(s) = \frac{r_1}{s} + \frac{r_2(s + 500E3)}{(s + 500E3)^2 + (866E3)^2} + \frac{r_3(866E3)}{(s + 500E3)^2 + (866E3)^2}$$

- Solving for the residues gives

$$r_1 = 1, \quad r_2 = -2, \quad r_3 = -1.15$$

Driven Response with Non-Zero I.C.'s

33

- Total response:

$$v_o(t) = 1 - 2e^{-500E3t} \cos(866E3 \cdot t) - 1.15e^{-500E3t} \sin(866E3 \cdot t)$$

- Superposition of two components

- ▣ **Natural response**
due to initial conditions

- ▣ **Driven response**
due to the input

