

# SECTION 4: LAPLACE- DOMAIN CIRCUIT ANALYSIS


ENGR 203 – Electrical Fundamentals III

# Laplace-Domain Circuit Analysis
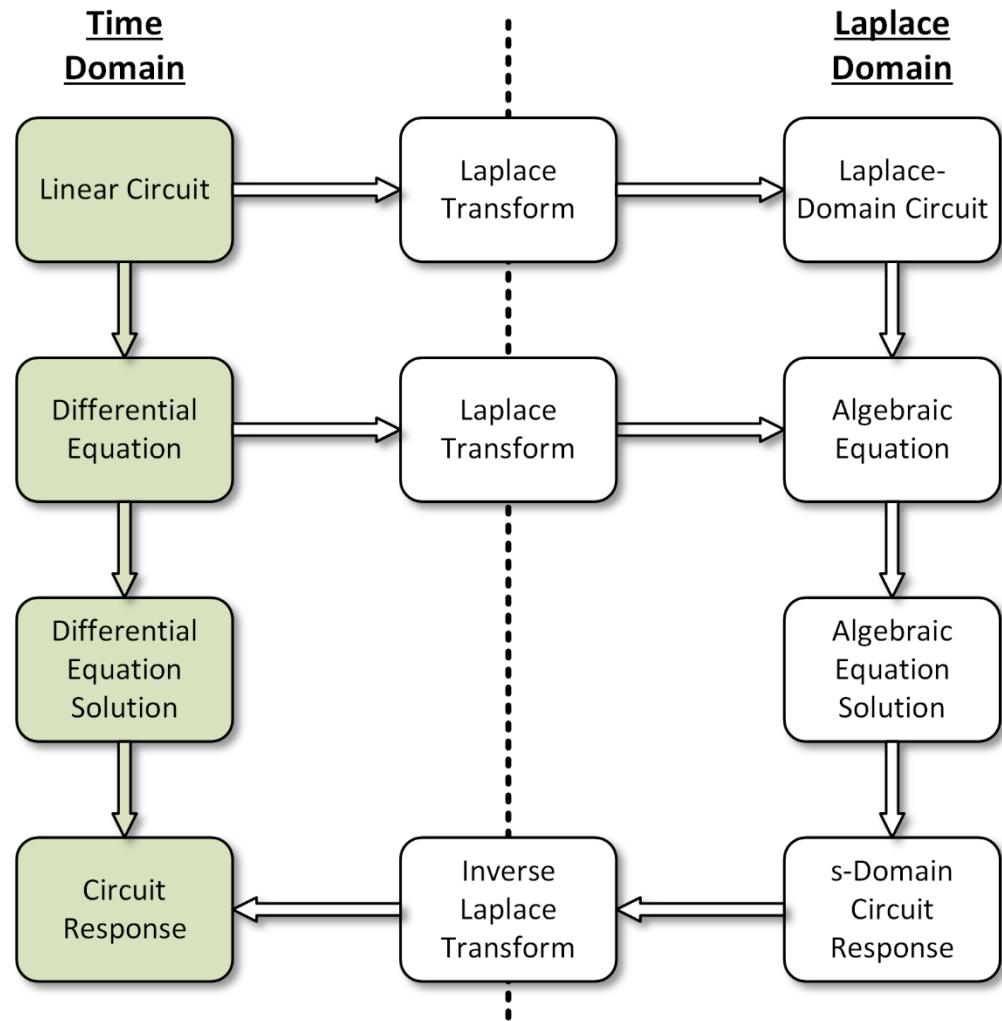
# Transient Analysis – Time-

3


- ENGR 201/202 transient analysis procedure:


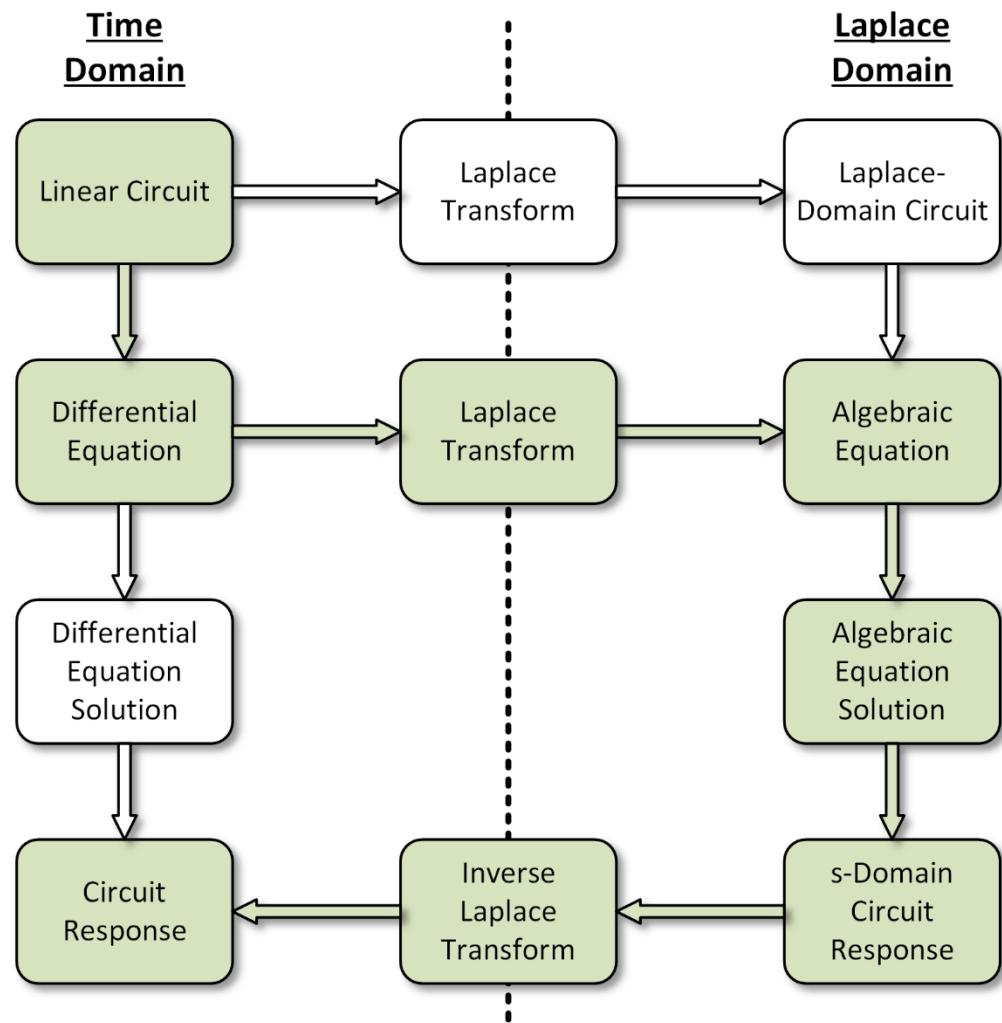
# Laplace Transform Solution to ODE

4


- In the previous sections, we used Laplace transforms to solve a circuit's governing ODE:


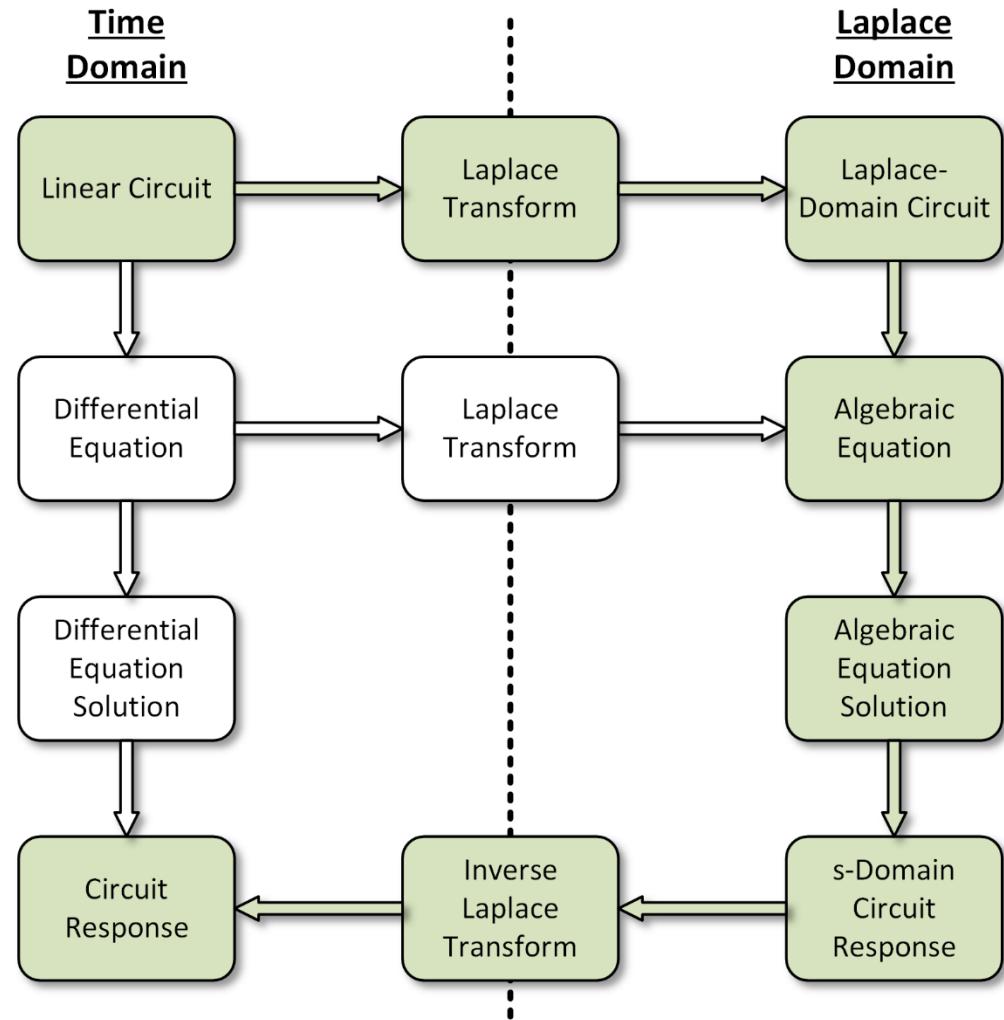
# Laplace-Domain Circuit Analysis

5

- Now, we will learn to analyze our circuits in the Laplace domain:



# Laplace-Domain Circuit Analysis

6


- Circuit analysis in the Laplace Domain:
  - ***Transform the circuit*** from the time domain to the Laplace domain
  - ***Analyze*** using the usual circuit analysis tools
    - Nodal analysis, voltage division, etc.
  - Solve ***algebraic*** circuit equations
    - Laplace transform of circuit response
  - ***Inverse transform*** back to the time domain
- First, we will learn to transform our circuits to the Laplace domain
  - Need Laplace-domain models for individual components

# Laplace-Domain Component Models


# Sources in the Laplace Domain

8

## □ Voltage source:

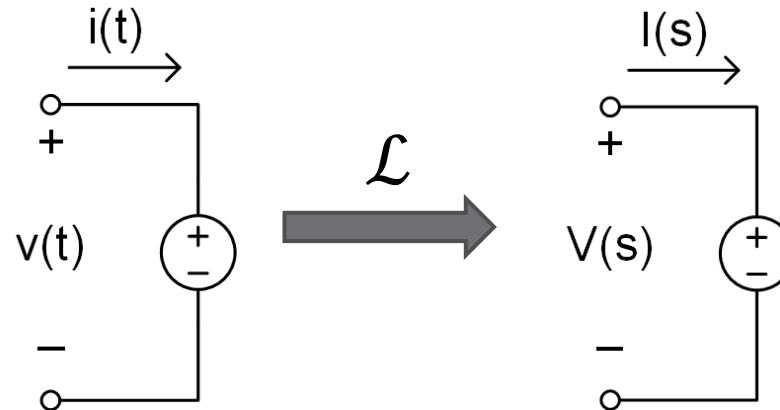

## □ Current source:

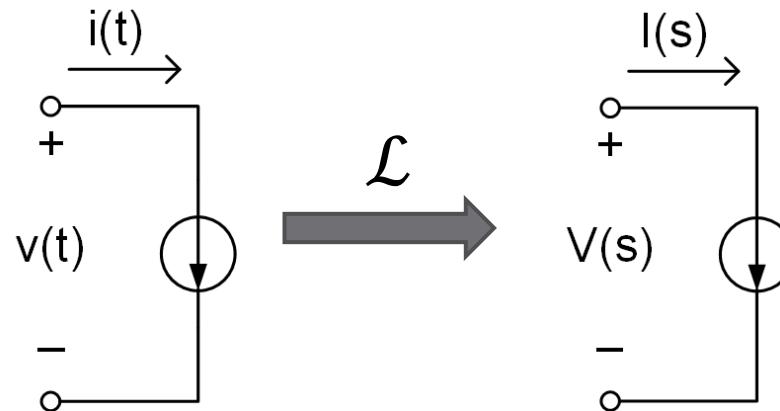

# Resistors in the Laplace Domain

9


- Ohm's law governs the behavior of resistors

$$v(t) = R \cdot i(t) \quad \text{or} \quad i(t) = \frac{1}{R} v(t)$$

- Laplace transforming these expressions gives us Ohm's law in the Laplace domain:

$$V(s) = R \cdot I(s) \quad \text{or} \quad I(s) = \frac{1}{R} V(s)$$

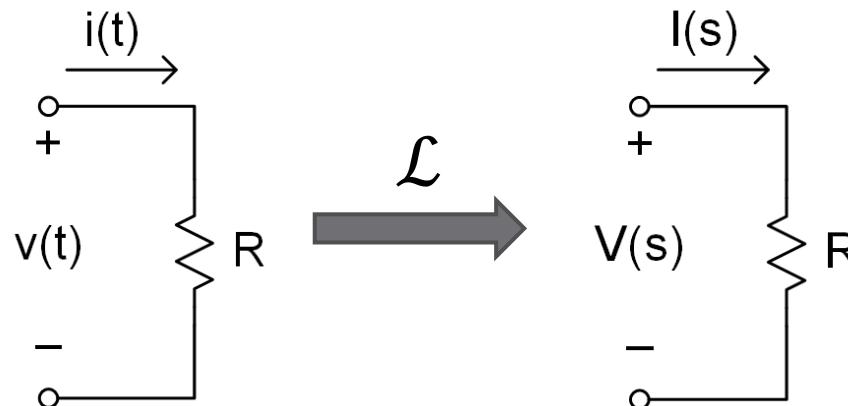- Resistors are the same in both domains:



# Capacitors in the Laplace Domain

10

- Current-voltage relationship for a capacitor:

$$i(t) = C \frac{dv}{dt}$$

- Transform using the derivative property of the Laplace transform

$$I(s) = C \cdot sV(s) - C \cdot v(0)$$

- Two components to the Laplace-domain capacitor current:

- One proportional to the capacitor voltage:  $C \cdot sV(s)$
  - One proportional to the **initial** capacitor voltage:  $-C \cdot v(0)$

- Assuming zero initial voltage,  $v(0) = 0$ , we have

$$I(s) = Cs \cdot V(s) = \frac{V(s)}{\frac{1}{Cs}} = \frac{V(s)}{Z_c(s)}$$

- $Z_c(s)$  is the **Laplace-domain capacitor impedance**


$$Z_c = \frac{1}{Cs}$$

# Capacitors in the Laplace Domain

11

$$I(s) = Cs \cdot V(s) - C \cdot v(0)$$

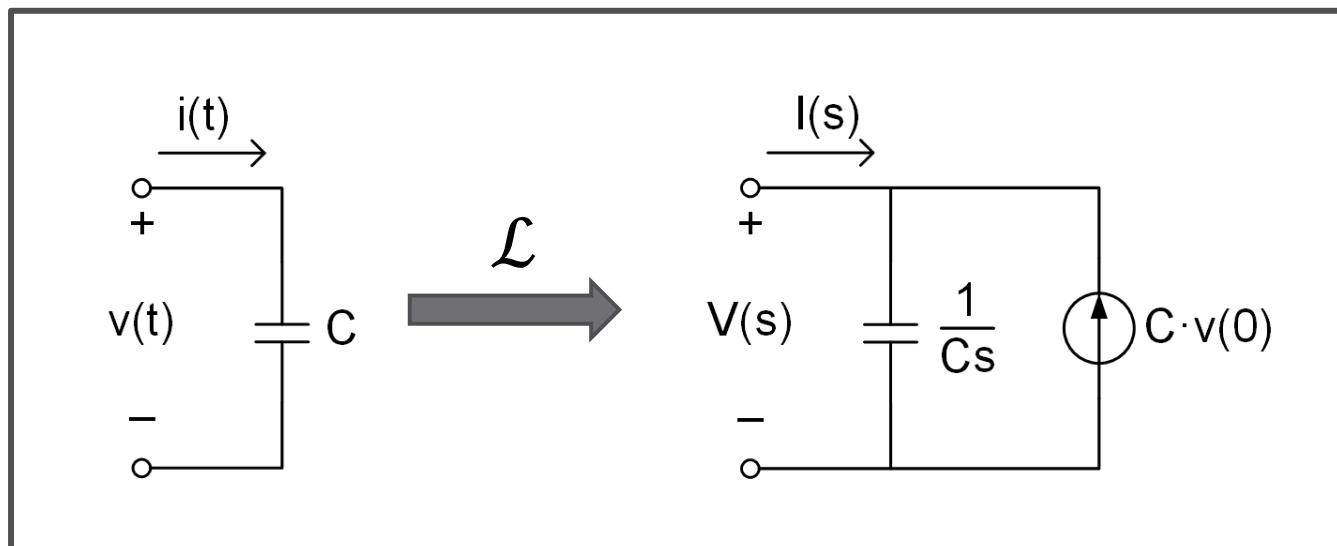- Capacitor model in the Laplace domain:
  - Two parallel branches, two currents
    - One given by Ohm's law
    - One set by the initial capacitor voltage



# Capacitors in the Laplace Domain

12


- Alternatively, the current-voltage relationship is:

$$v(t) = \frac{1}{C} \int i(t) dt + v(0)$$

- Transform using the integral property of the Laplace transform

$$V(s) = \frac{1}{Cs} I(s) + \frac{v(0)}{s}$$

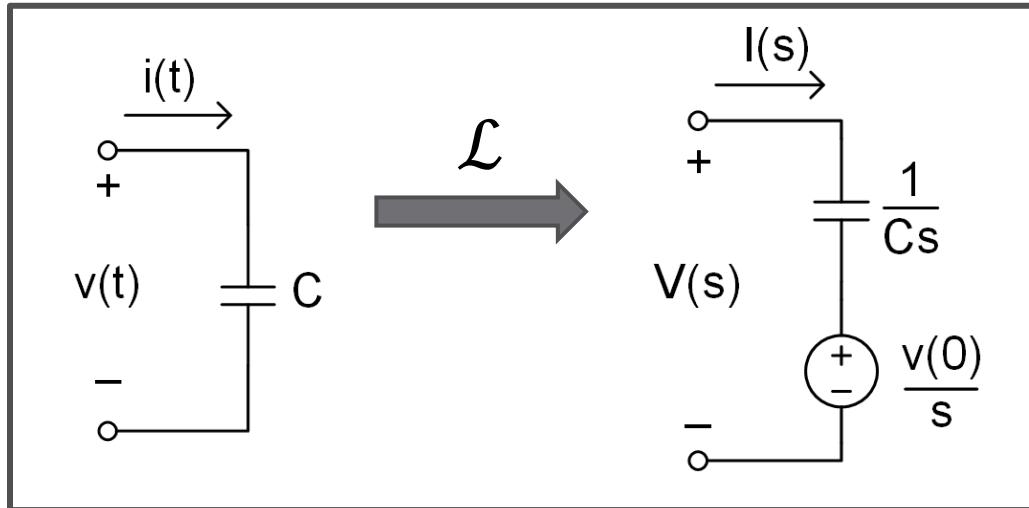- Two components to the Laplace-domain capacitor voltage:
  - One given by Ohm's law:  $1/Cs \cdot I(s)$
  - One proportional to the initial capacitor voltage:  $v(0)/s$



# Inductors in the Laplace Domain

13

- Current-voltage relationship for an inductor:

$$v(t) = L \frac{di}{dt}$$

- Transform using the derivative property of the Laplace transform

$$V(s) = Ls \cdot I(s) - L \cdot i(0)$$

- Two components to the Laplace-domain inductor voltage:

- One proportional to the inductor current:  $Ls \cdot I(s)$
  - One proportional to the *initial* inductor current:  $-L \cdot i(0)$

- Assuming zero initial current,  $i(0) = 0$ , we have

$$V(s) = Ls \cdot I(s) = Z_L(s) \cdot I(s)$$

- $Z_L(s)$  is the **Laplace-domain inductor impedance**


$$Z_L = Ls$$

# Inductors in the Laplace Domain

14

$$V(s) = Ls \cdot I(s) - L \cdot i(0)$$

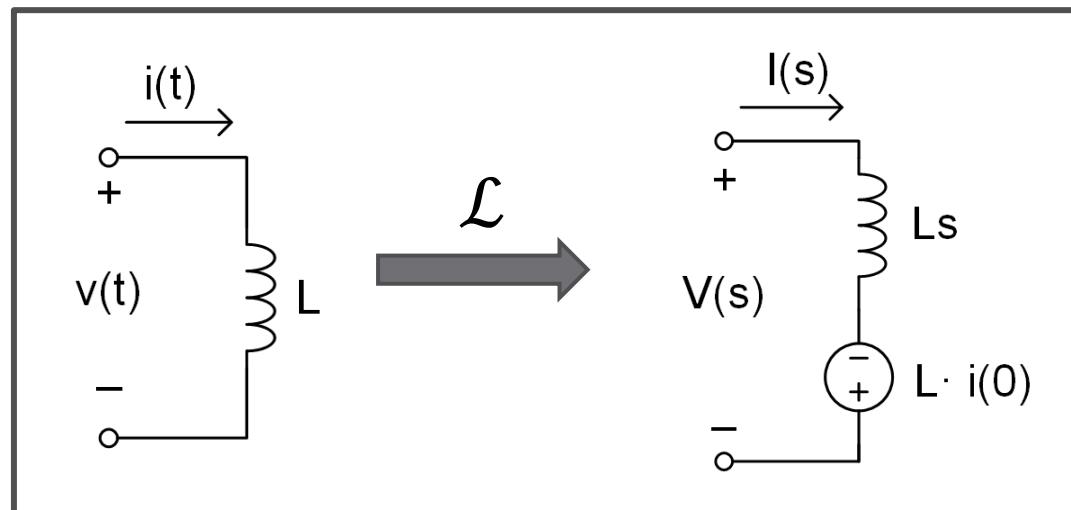- Inductor model in the Laplace domain:
  - Two series components, two voltages
    - One given by Ohm's law
    - One set by the initial inductor current



# Inductors in the Laplace Domain

15


- Alternatively, using the integral form of the current-voltage relationship:

$$i(t) = \frac{1}{L} \int v(t) dt + i(0)$$

- Transform using the integral property of the Laplace transform

$$I(s) = \frac{1}{Ls} V(s) + \frac{i(0)}{s}$$



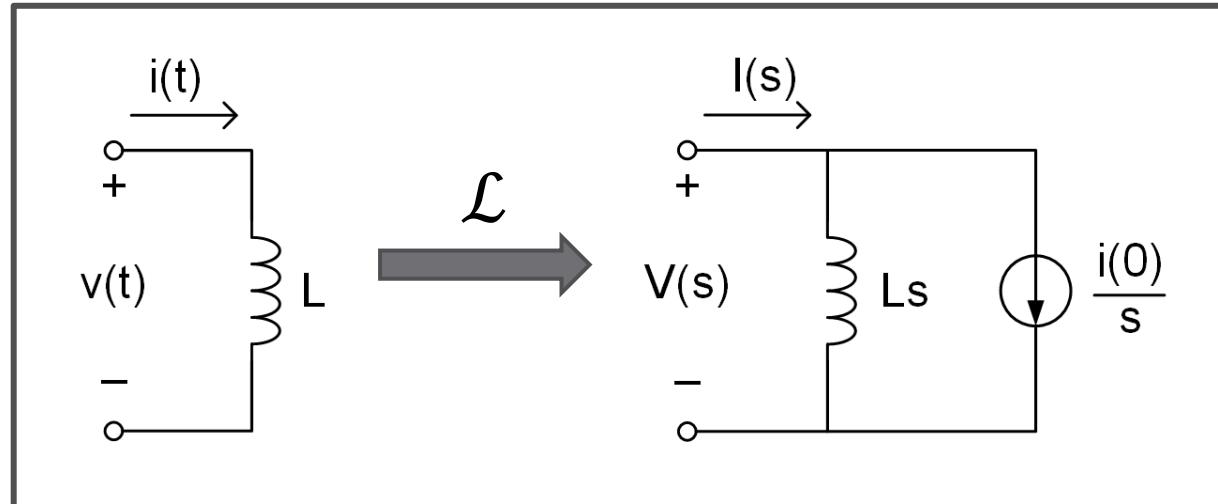
- Two components to the Laplace-domain inductor current:
  - One given by Ohm's law:  $1/Ls \cdot V(s)$
  - One proportional to the initial inductor current:  $i(0)/s$


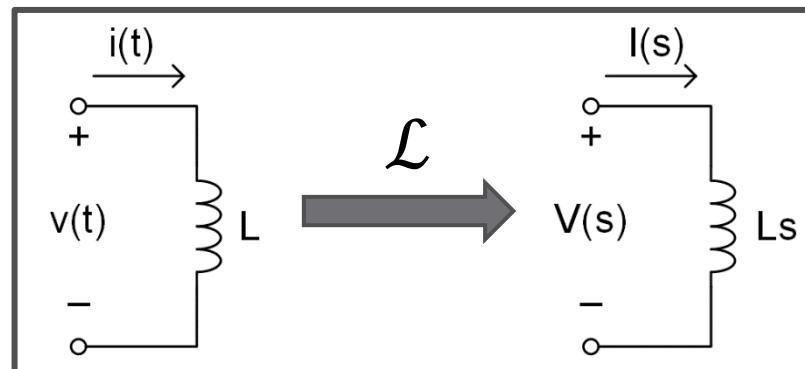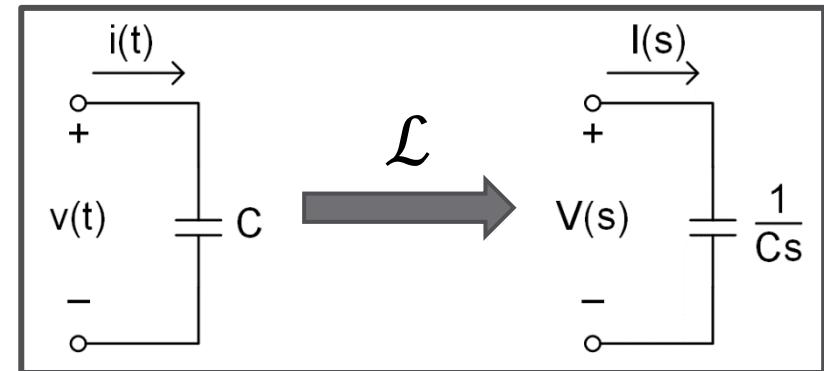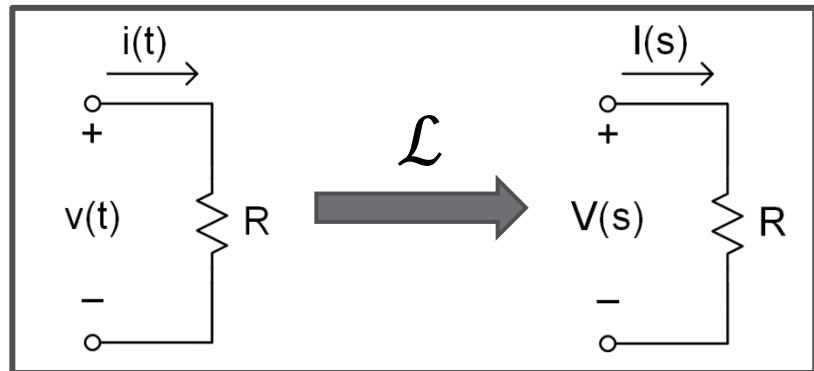
# Zero Initial conditions

16

- It is very common to have ***zero initial conditions***
  - Simply replace components with their **Laplace-domain impedances**



# Laplace-Domain Circuit Analysis

# Laplace-Domain Circuit Analysis


18

- All the familiar circuit analysis tools still apply in the Laplace domain, e.g.:
  - Ohm's law
  - Kirchhoff's laws, KVL and KCL
  - Nodal analysis
  - Mesh analysis
  - Voltage and current division
  - Thevenin and Norton equivalent circuits
- General procedure:
  - 1) Determine initial conditions
  - 2) Transform the circuit to the Laplace domain
  - 3) Analyze the circuit to determine the Laplace transform of the quantity of interest (e.g.,  $V_o(s)$ )
  - 4) Inverse transform back to the time domain via partial fraction expansion
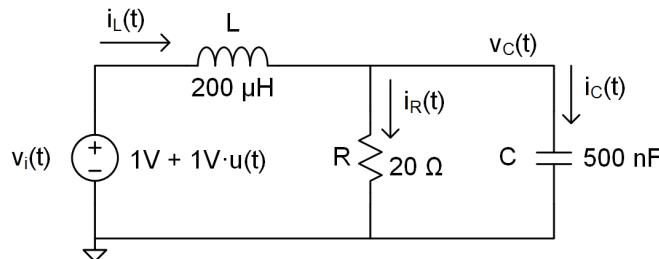
# Laplace-Domain Circuit Analysis – Example 1

19

- Determine  $v_C(t)$  for the following circuit



$$v_i(t) = 1V + 1V \cdot u(t) = \begin{cases} 1V & t < 0 \\ 2V & t \geq 0 \end{cases}$$

- First, determine the initial conditions,  $v_C(0)$  and  $i_L(0)$

- For  $t < 0$ :

- $v_i(t < 0) = 1V$
    - $i_L(t < 0) = 1V / 20\Omega = 50\text{ mA}$
    - $v_C(t < 0) = 1V$

- At  $t = 0$




- $v_i(0) = 2V$
    - $v_C(0) = 1V$
    - $i_L(0) = 50\text{ mA}$

# Laplace-Domain Circuit Analysis – Example 1

20

- Next, transform the circuit to the Laplace domain
  - Replace components with Laplace-domain equivalents
  - The input is  $2 V$  for  $t \geq 0$ , so

$$V_i(s) = \frac{2}{s}$$

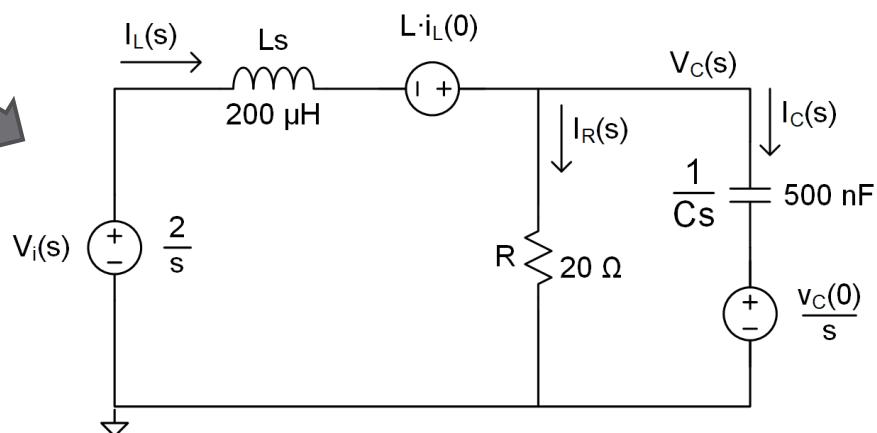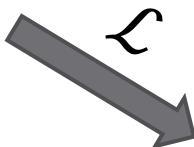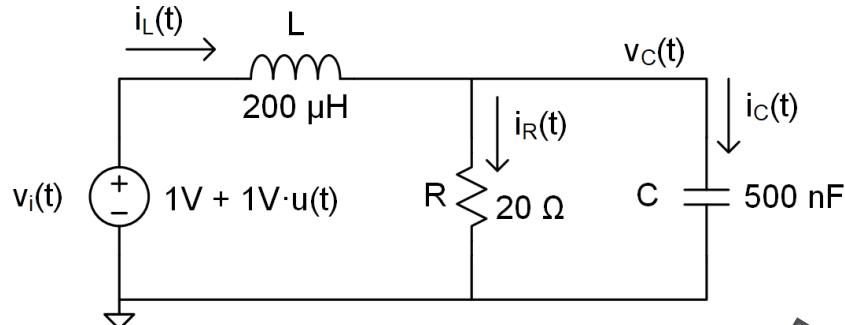


# Laplace-Domain Circuit Analysis – Example 1

21

- Want  $V_C(s)$ , so do a nodal analysis
- KCL at node  $V_C$ :

$$I_L(s) - I_R(s) - I_C(s) = 0$$

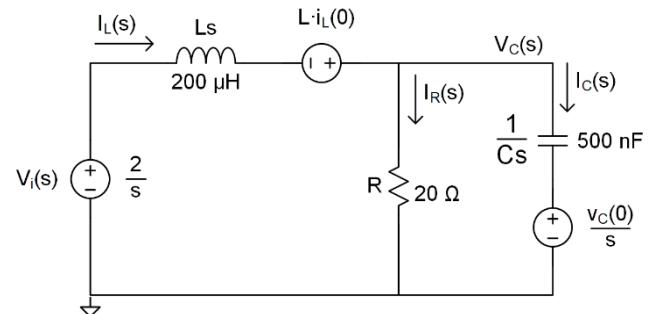

$$\frac{V_i(s) - (V_C(s) - L \cdot i_L(0))}{Ls} - \frac{V_C(s)}{R} - \frac{\left(V_C(s) - \frac{v_C(0)}{s}\right)}{1/Cs} = 0$$

$$\frac{V_i(s)}{Ls} + \left(-\frac{1}{Ls} - \frac{1}{R} - Cs\right)V_C(s) + \frac{i_L(0)}{s} + Cv_C(0) = 0$$

$$V_C(s) \left(\frac{1}{Ls} + \frac{1}{RC}s + Cs\right) = \frac{V_i(s)}{Ls} + \frac{i_L(0)}{s} + Cv_C(s)$$

$$V_C(s) \left(s^2 + \frac{1}{RC}s + \frac{1}{LC}\right) = \frac{1}{LC}V_i(s) + \frac{1}{C}i_L(0) + v_C(0)s$$

# Laplace-Domain Circuit Analysis – Example 1

22

- Solving for  $V_C(s)$  gives the output in the Laplace domain:

$$V_C(s) = \frac{\frac{1}{LC}V_i(s) + \frac{1}{C}i_L(0) + v_C(0)s}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

- Substituting in  $V_i(s)$ , initial conditions, and component values:

$$V_C(s) = \frac{s^2 + 100E3s + 20E9}{s(s^2 + 100E3s + 10E9)}$$

- One real pole and a complex-conjugate pair of poles:

$$s_1 = 0 \quad \text{and} \quad s_{2,3} = -50E3 \pm j86.6E3$$

# Laplace-Domain Circuit Analysis – Example 1

23

- Inverse transform via partial fraction expansion

$$V_C(s) = \frac{s^2 + 100E3s + 20E9}{s(s^2 + 100E3s + 10E9)} = \frac{r_1}{s} + \frac{r_2(s + 50E3) + r_3(86.6E3)}{(s + 50E3)^2 + (86.6E3)^2}$$

- Multiply through by the LHS denominator

$$s^2 + 100E3s + 20E9 = r_1s^2 + 100E3r_1s + 10E9r_1 + r_2s^2 + 50E3r_2s + 86.6E3r_3s$$

$$s^2 + 100E3s + 20E9 = (r_1 + r_2)s^2 + (100E3r_1 + 50E3r_2 + 86.6E3r_3)s + 10E9r_1$$

- Equating coefficients gives three equations for the residues:

$$s^2: 1 = r_1 + r_2$$

$$s^1: 100E3 = 100E3r_1 + 50E3r_2 + 86.6E3r_3$$

$$s^0: 20E9 = 10E9r_1$$

- Solving for the residues:

$$r_1 = 2 , \quad r_2 = -1 , \quad r_3 = -0.577$$

# Laplace-Domain Circuit Analysis – Example 1


24

- The Laplace transform of the output voltage:

$$V_C(s) = \frac{2}{s} - \frac{(s + 50E3)}{(s + 50E3)^2 + (86.6E3)^2} - 0.577 \frac{(86.6E3)}{(s + 50E3)^2 + (86.6E3)^2}$$

- Inverse transforming to the time domain:

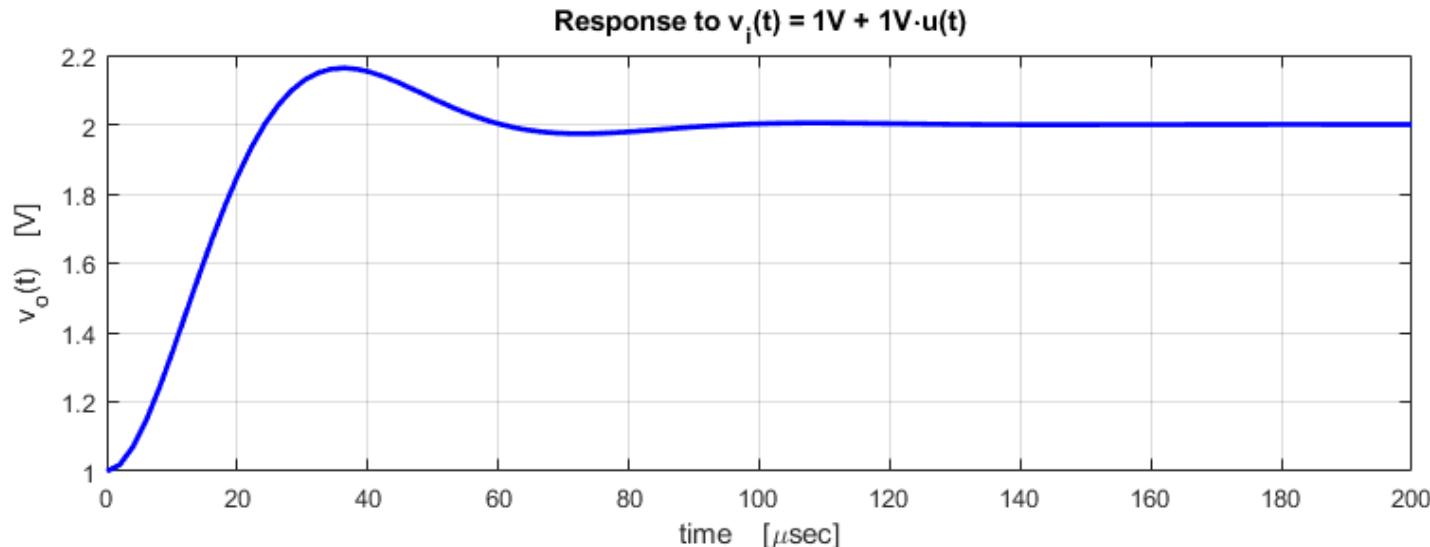
$$v_C(t) = 2 V - 1 V e^{-50E3t} \cos(86.6E3t) - 0.577 e^{-50E3t} \sin(86.6E3t)$$


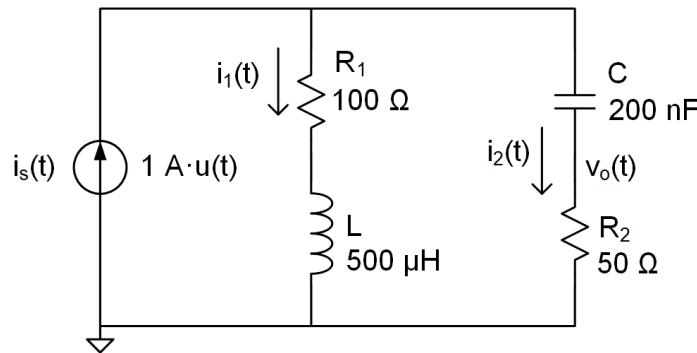
# Laplace-Domain Circuit Analysis – Example 2

25


- Determine  $v_o(t)$  for the following circuit



- Now, the initial conditions are zero

- $v_c(0) = 0 \text{ V}$
- $i_L(0) = 0 \text{ A}$

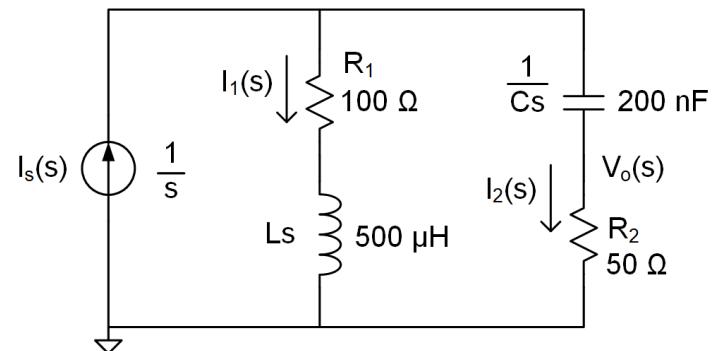- Laplace-domain component models are simplified
  - No sources




# Laplace-Domain Circuit Analysis – Example 2

26

- The output voltage is given by

$$V_o(s) = I_2(s) \cdot R_2$$

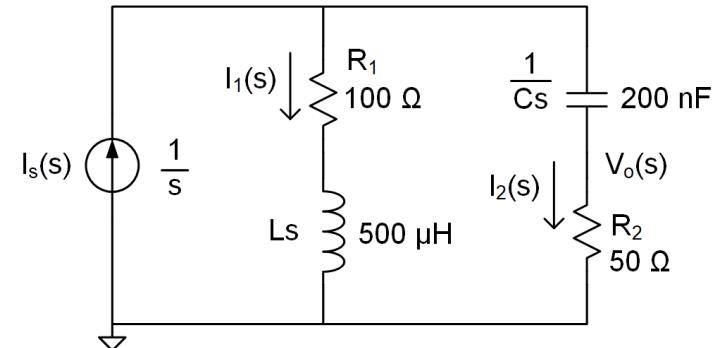- Apply current division to find  $I_2(s)$



$$I_2(s) = I_s(s) \cdot \frac{Y_2(s)}{Y_1(s) + Y_2(s)}$$

- The admittances of the parallel branches:

$$Y_1(s) = Z_1(s)^{-1} = \frac{1}{R_1 + Ls}$$


$$Y_2(s) = Z_2(s)^{-1} = \left( R_2 + \frac{1}{Cs} \right)^{-1} = \frac{Cs}{R_2 Cs + 1}$$

# Laplace-Domain Circuit Analysis – Example 2

27
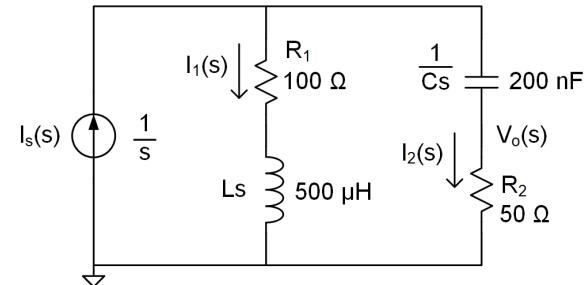
## □ Current division

$$I_2(s) = I_s(s) \cdot \frac{Y_2(s)}{Y_1(s) + Y_2(s)}$$



$$I_2(s) = \frac{1}{s} \cdot \frac{\frac{Cs}{R_2 Cs + 1}}{\frac{1}{R_1 + Ls} + \frac{Cs}{R_2 Cs + 1}} = \frac{1}{s} \cdot \frac{\frac{Cs}{R_2 Cs + 1}}{\frac{R_2 Cs + 1 + R_1 Cs + Ls^2}{(R_1 + Ls)(R_2 Cs + 1)}}$$

$$I_2(s) = \frac{1}{s} \cdot \frac{(R_1 + Ls)Cs}{R_2 Cs + 1 + R_1 Cs + Ls^2} = \frac{Ls^2 + R_1 Cs}{s(Ls^2 + (R_1 + R_2)Cs + 1)}$$

$$I_2(s) = \frac{Ls^2 + R_1 Cs}{Ls^2 + (R_1 + R_2)Cs + 1} = \frac{s + \frac{R_1}{L}}{s^2 + \frac{(R_1 + R_2)}{L}s + \frac{1}{LC}}$$

# Laplace-Domain Circuit Analysis – Example 2

28

- Ohm's law give the output voltage

$$V_o(s) = R_2 I_2(s)$$


$$V_o(s) = \frac{R_2 \left( s + \frac{R_1}{L} \right)}{s^2 + \frac{(R_1 + R_2)}{L} s + \frac{1}{LC}}$$

- Substituting in component values:

$$V_o(s) = \frac{50(s + 200E3)}{s^2 + 300E3s + 10E9}$$

- The denominator has two real roots
  - The voltage response is over-damped
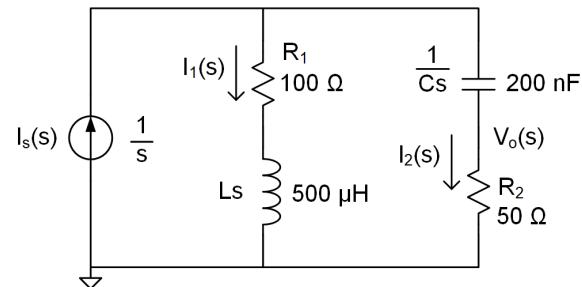
$$V_o(s) = \frac{50(s + 200E3)}{(s + 38.2E3)(s + 261.8E3)}$$



# Laplace-Domain Circuit Analysis – Example 2

29

- Inverse transform via partial fraction expansion

$$V_o(s) = \frac{50(s + 200E3)}{(s + 38.2E3)(s + 261.8E3)} = \frac{r_1}{(s + 38.2E3)} + \frac{r_2}{(s + 261.8E3)}$$

- Multiply through by the LHS denominator

$$50s + 10E6 = r_1s + 261.8E3r_1 + r_2s + 38.2E3r_2$$

$$50s + 10E6 = (r_1 + r_2)s + 261.8E3r_1 + 38.2E3r_2$$

- Equating coefficients gives three equations for the residues:

$$s^1: 50 = r_1 + r_2$$

$$s^0: 10E6 = 261.8E3r_1 + 38.2E3r_2$$

- Solving for the residues:

$$r_1 = 36.2, \quad r_2 = 13.8$$

# Laplace-Domain Circuit Analysis – Example 2


30

- The Laplace transform of the output voltage:

$$V_o(s) = \frac{36.2}{(s + 38.2E3)} + \frac{13.8}{(s + 261.8E3)}$$


- Inverse transforming to the time domain:
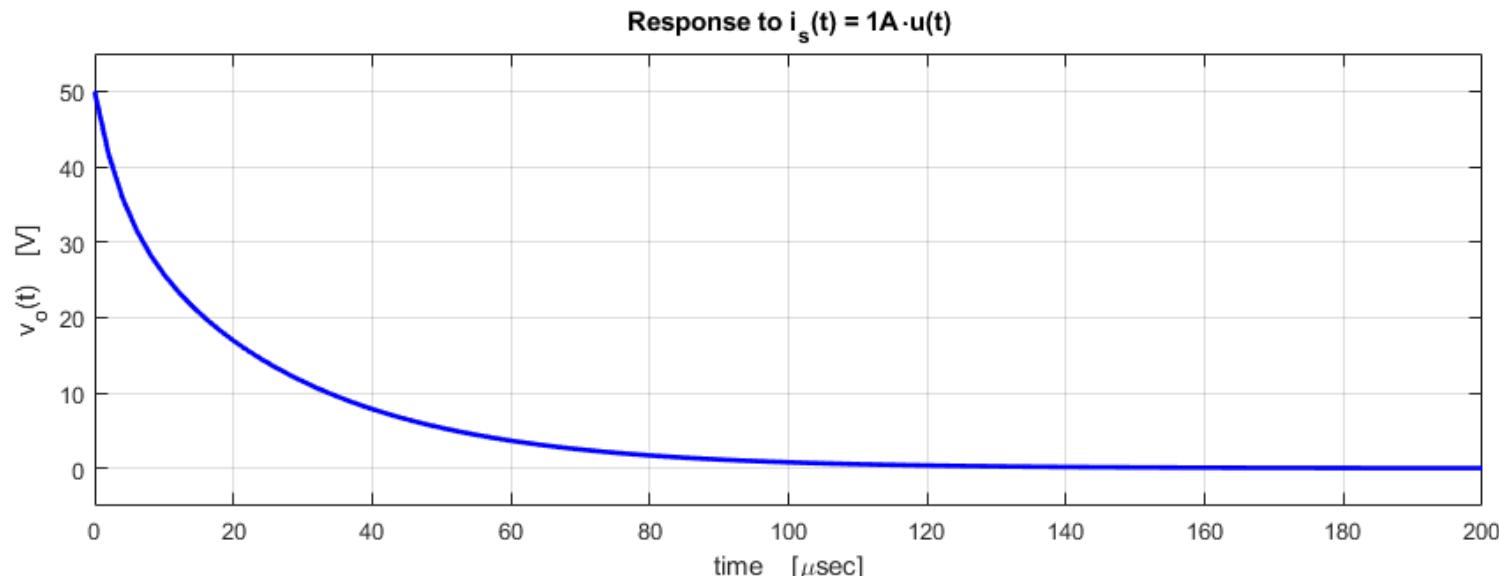
$$v_o(t) = 36.2 V e^{-38.2E3t} + 13.8 V e^{-261.8E3t}$$



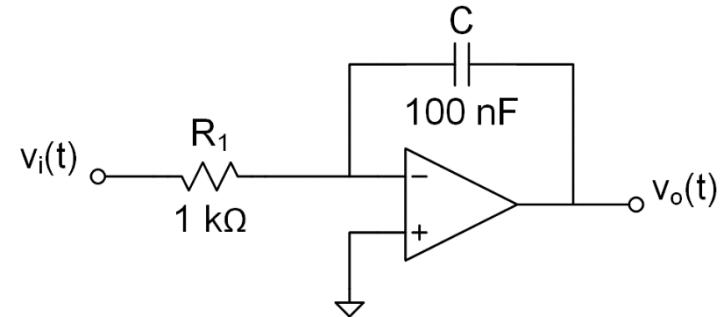
# Example Problems

- Determine the output of the following opamp circuit for  $v_i(t) = 1 \text{ V} \cos(100E3 \cdot t)$ 
  - What is the circuit's function?





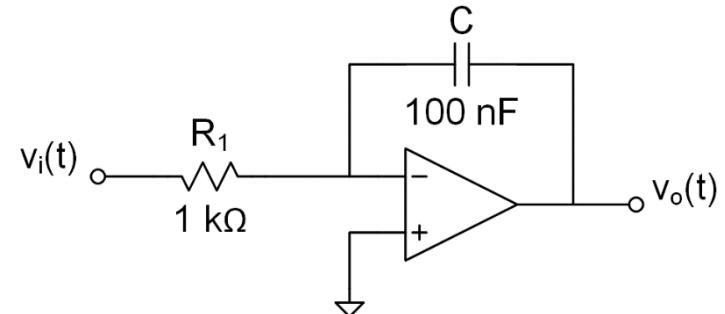
- Determine the Laplace-domain step response.
- Apply the final value theorem to determine the steady-state output.
- Find the time-domain step response.





- Determine the output of the following opamp circuit for  $v_i(t) = 1 \text{ V} \cos(100E3 \cdot t)$

- What is the circuit's function?

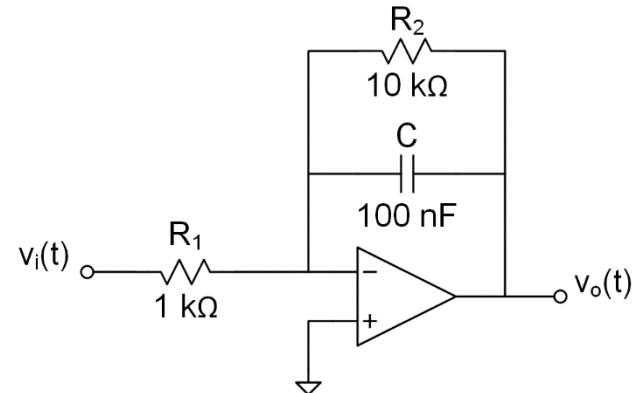



- Determine the Laplace-domain step response.
- Apply the final value theorem to determine the steady-state output.
- Find the time-domain step response.

